


Feedback

HW MOSFETs
Depletion
Enhancement

- * When present output depends only on input and not on the past output, there is no feedback
- * But when present output depends on past output as well, there is feedback.


Basic Amplifier
(Open Loop) *

No feedback

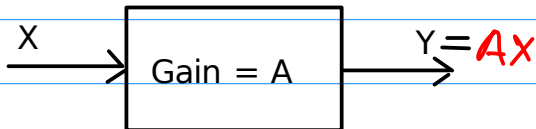

Open loop Gain = $\frac{Y}{X} = A$

Amp with feedback
(Closed Loop)

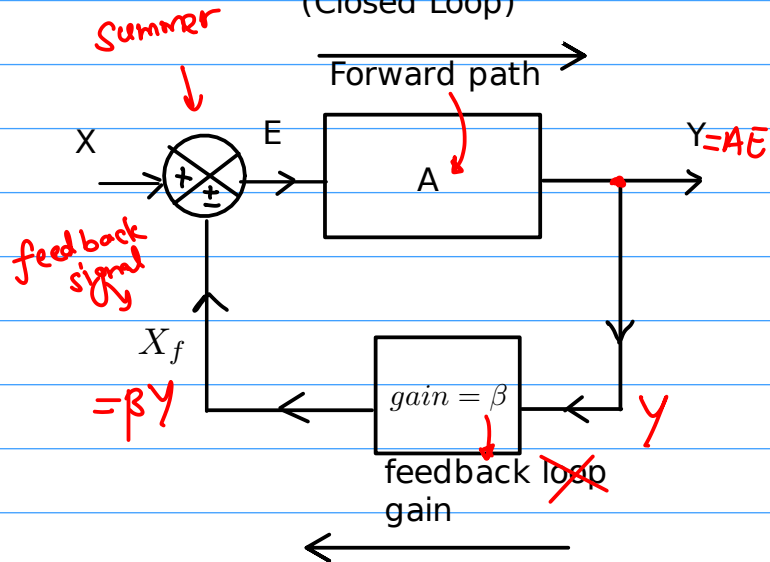

$A_f = \text{Closed loop Gain} = \frac{Y}{X} = ?$

Closed loop Gain

(i) +ve feedback :

$$Y = AE$$

$$E = X + X_f$$

$$X_f = \beta Y$$

$$\Rightarrow E = X + \beta Y$$

$$\Rightarrow Y = A[X + \beta Y]$$

$$\Rightarrow A_f = \frac{Y}{X} = \frac{A}{1 - A\beta}$$

(ii) -ve feedback :

$$Y = AE$$

$$E = X - X_f$$

$$X_f = \beta Y$$

$$\Rightarrow E = X - \beta Y$$

$$\Rightarrow Y = A[X - \beta Y]$$

$$\Rightarrow A_f = \frac{Y}{X} = \frac{A}{1 + A\beta}$$


Compare with open loop gain $\frac{Y}{X} = A$

* if $A\beta > 0$:


$$|A_f| > |A|$$

$$|A_f| < |A|$$

* Loop Gain : for -ve feedback:

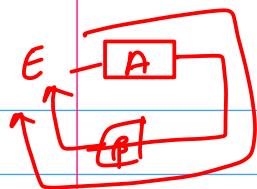
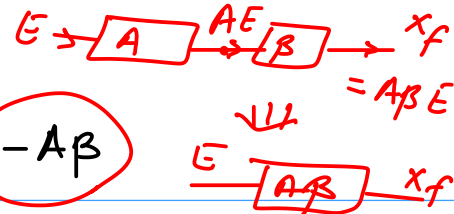
$$\text{Loop Gain} = -\frac{x_f}{E} = -A\beta$$



for +ve feedback:

$$\text{Loop Gain} = \frac{x_f}{E} = A\beta$$

* Return Difference: (or Desensitivity, D)**

$$D = 1 - \text{Loop Gain}$$

for -ve feedback : $D = 1 + A\beta$

for +ve feedback : $D = 1 - A\beta$

} denominator of A_f expression

* Feedback Gain β :

'if 10% output is 'sampled' and feedback, then

$$\beta = \frac{10}{100} = 0.1$$

* Amount of feedback (N, in decibels or dB) :



$$N = 20 \log_{10} \left| \frac{A_f}{A} \right| \quad (\text{dB})$$

for -ve f.b. : $|A_f| < |A|$
$$N = 20 \log_{10} \left(\frac{1}{1 + A\beta} \right) < 0 \quad (-ve)$$

for +ve f.b. : $|A_f| > |A|$
$$N = 20 \log_{10} \left(\frac{1}{1 - A\beta} \right) > 0 \quad (+ve)$$

Three conditions for feedback:

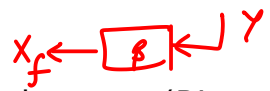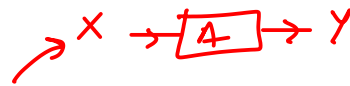1. Basic amp should be unidirectional.
2. Feedback network (beta) should be unidirectional
3. Beta should be independent of the load and source resistances (R_L and R_s)



-ve f.b. $A_f = \frac{A}{1 + A\beta}$

↑
feedback gain

for C.E. amp, $A = \beta \frac{R_L}{R_i}$

↑
O.L. gain (overall gain)

$\beta = \frac{I_C}{I_B}$

So, A_f depends on R_L (Bad)

But 'if' $A\beta \gg 1$, then

↑
Loop Gain

$A_f \approx \frac{A}{A\beta} \Rightarrow A_f \approx \frac{1}{\beta}$ **

↑
feedback gain

So, 'if' β is independent of R_L & R_s , A_f also will be independent (good!)

* Advantages of negative feedback:

1. Desensitivity of amplification:

* 'if' A can fluctuate due to environment or device variability, A_f should be insensitive to that change.

* Measure: Sensitivity, $S = \frac{dA_f/A_f}{dA/A}$

* fractional change (% change) in A_f should be less than that in A .

* So, $S < 1$ is desirable **

$$A_f = \frac{A}{1+A\beta} \quad (-ve \text{ f.b.})$$

$$\frac{dA_f}{dA} = \frac{1+A\beta - A(\beta)}{(1+A\beta)^2}$$

$$dA_f = \frac{dA}{(1+A\beta)^2}$$

Divide by A_f

$$\Rightarrow \frac{dA_f}{A_f} = \frac{dA}{(1+A\beta)^2} \times \frac{(1+A\beta)}{A} = \frac{(dA/A)}{(1+A\beta)}$$

$$\Rightarrow S = \frac{dA_f/A_f}{dA/A} = \frac{1}{1+A\beta} = \frac{1}{D}$$

$S < 1$ [if $A\beta > 0$]
 & $D > 1 \rightarrow$ % change in A_f is less than that A

2. Improved Stability:


Stability: Bounded i/p \Rightarrow Bounded o/p
 (BIBO)

* -ve feedback reduces gain ($A_f < A$). That improves stability.

3. Reduction in frequency Distortion :

* Gain should stay constant for a very wide frequency range (called Band Width). Ideally, for all freq., gain should be constant.

* A depends on freq.

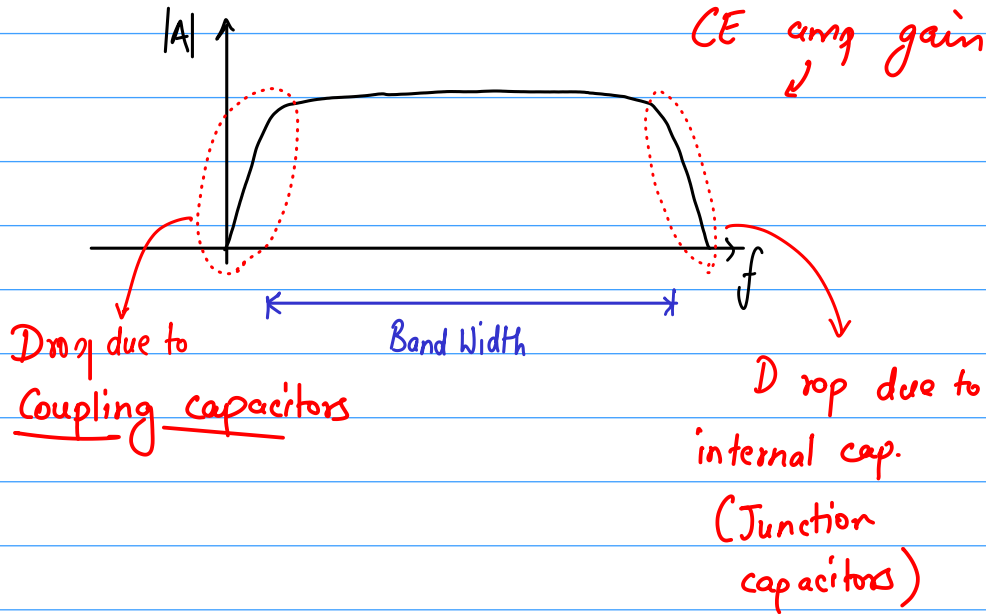

$$a_2 \sin 4\pi t$$

$$\downarrow$$

$$(10)a_2 \sin 4\pi t$$

$$a_3 \sin 6\pi t$$

$$\downarrow$$

$$(10)a_3 \sin 6\pi t$$

* Closed loop Gain

$$A_f \approx \frac{1}{\beta}$$

A depends on caps & hence freq.

$$\frac{A}{1+A\beta}$$

if feedback network (β) is made of only

resistances & no reactive components (like L & C) then β & A_f both will be independent (somewhat) of frequency.


* β should also not have any active comp (e.g. BJT, JFET or Mos FET)

* This reduces freq. & phase distortion

* Reactance of inductor, $X_L = 2\pi f L$ (in Ohms)

* Reactance of capacitor, $X_C = \frac{1}{2\pi f C}$ (in Ohms)

-ve feedback

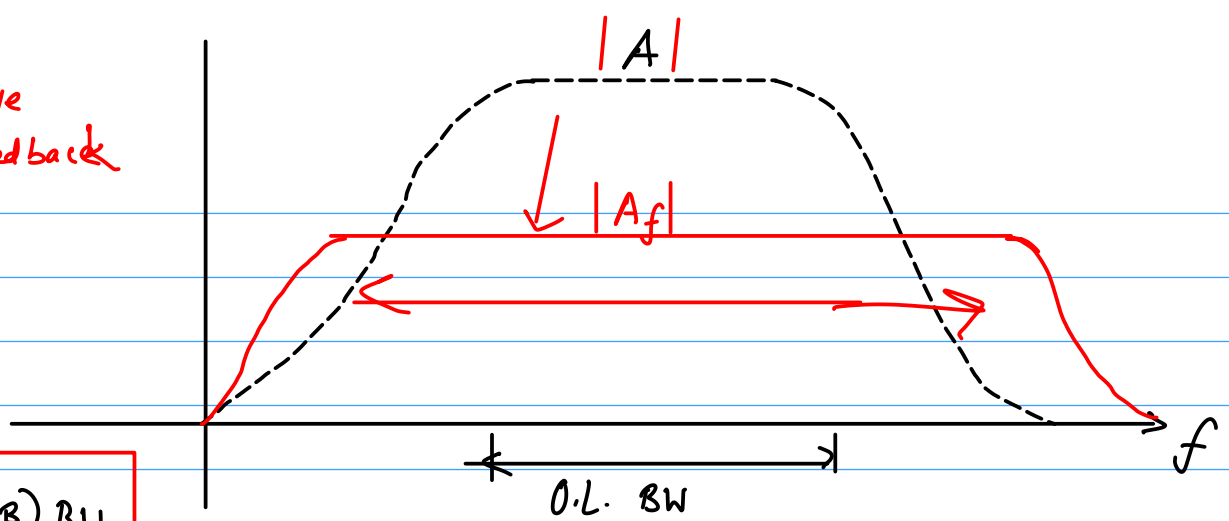

$$BW_f = (1 + A\beta) BW$$


$$A_f = \frac{A}{1 + A\beta}$$

C.L. BW

* In any amp, Gain BW product = GBW = constant

4. Reduction in Non Linear Distortion :

O.L. system :

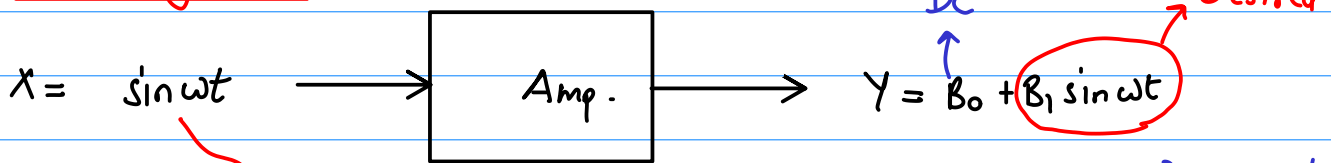

PN 5th

$$I \propto e^V$$

$$RT = V_0 \propto e^V = 1 + \frac{V}{V_T} + \frac{V^2}{2V_T^2} + \dots$$

$$\sin^2 \theta = 1 - \cos 2\theta$$

$$B_1 > B_2 > B_3 > B_4 \dots$$

unwanted DC

$$Y = B_0 + B_1 \sin \omega t$$

$$+ B_2 \sin 2\omega t$$

$$+ B_3 \sin 3\omega t$$

$$+ \dots$$

Desired

unwanted harmonics

Non Linear Distortion

* 2nd harmonic Distortion, $D_2 = \left| \frac{B_2}{B_1} \right| < 1$

3rd harmonic Distortion, $D_3 = \left| \frac{B_3}{B_1} \right| < 1$

$D_2 \gg D_3 \gg D_4 \dots$ (neglected)

* So, 2nd harmonic distortion is the main (dominant) one.

* So, in general, Non-Lin. Distortion $\equiv D_2^* = \left| \frac{B_2}{B_1} \right| < 1$

* distortion with -ve f.b.,

$$\overset{CL.}{\downarrow} D_{zf} = \frac{D_2}{(1 + A\beta)} \overset{O.L.}{\curvearrowright} < D_2$$

5. Noise Reduction: Noise power without f.b. = N_0

with f.b., $N_{of} = \frac{N_0}{1 + A\beta}$ *

So, -ve f.b. increases signal to noise ratio.

→ Disadvantages: ^{-ve f.b.} Reduces Gain

→ Application: ^{low noise} Good, Stable amplifiers.

→ Positive feedback:

Advantages: Increases Gain.


(Not really an adv.)

Disadvantages:

1. Reduces Band width (increases freq. distortion)
2. Increases noise, harmonic distortion.
3. Reduces stability.

Application: Oscillators.


The 4 Feedback Topologies

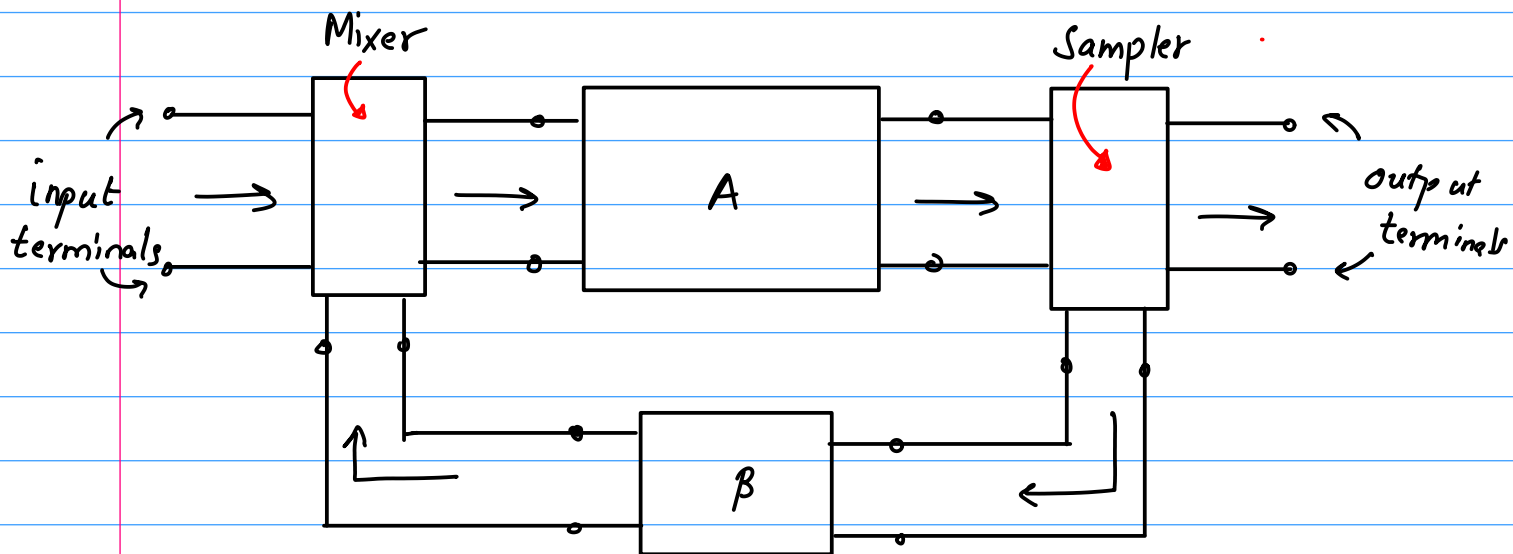


Sampler — { vol. sampling
 Current sampling }
Mixer — { vol. mixing
 Current Mixing } 4 topologies

→ Sampling :

(1) Voltage Sampling
or Shunt Sampling

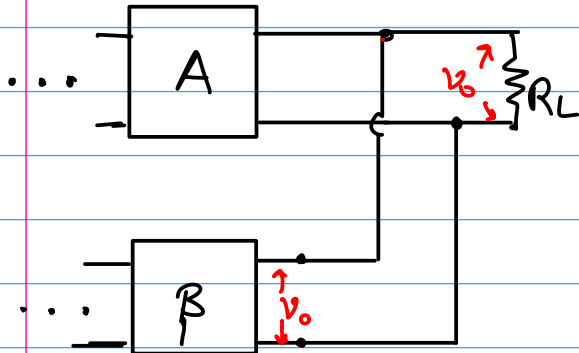


(2) Current Sampling
or Series Sampling

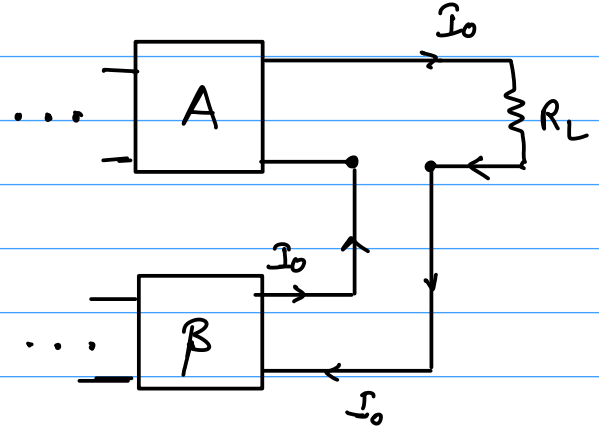


→ Mixing :

(1) Voltage or Series Mixing

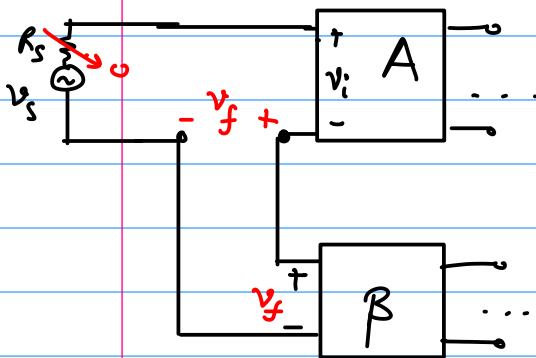

(2) Current or Shunt mixing

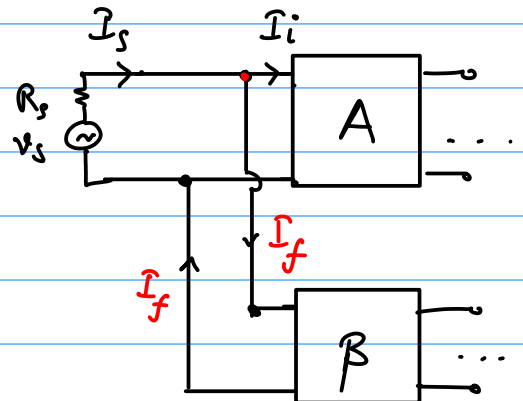

Assuming $R_s = 0$ (no vol. drop),

KVL: $v_i = v_s - v_f$
(-ve f.b.)



if polarities of v_f flipped,
 $v_i = v_s + v_f$ (+ve f.b.)

KCL: $I_i = I_s - I_f$
(-ve f.b.)

if direction of I_f flipped,
 $I_i = I_s + I_f$
(+ve f.b.)

Feedback Topology		Basic Amp	Closed loop stabilized Gain	unit of β	Other name	
O/p (Sampling)	I/p (Mixing)				i/p	O/p
1) Voltage - Series (<u>V</u>) (<u>V</u>)		A_v (<u>Vol. Amp</u>)	$A_{vf} \approx \frac{1}{\beta}$	unitless	series - shunt (<u>V</u>) (<u>V</u>)	
2) Current - Series (<u>I</u>) (<u>V</u>) <u>o/p</u> <u>i/p</u>		G_m (<u>Trans-Cond. Amp</u>)	$G_{mf} \approx \frac{1}{\beta}$	<u>Ohm</u>	Series - Series <u>i/p</u> <u>o/p</u>	
3) Voltage - Shunt (<u>V</u>) (<u>I</u>) <u>o/p</u> <u>i/p</u>		R_m (<u>Trans-Resistance Amp</u>)	$R_{mf} \approx \frac{1}{\beta}$	ohm	Shunt - Shunt <u>i/p</u> <u>o/p</u>	
4) Current - Shunt (<u>I</u>) (<u>I</u>) <u>o/p</u> <u>i/p</u>		A_i (<u>Current Amp</u>)	$A_{if} \approx \frac{1}{\beta}$	unitless	Shunt - Series <u>i/p</u> <u>o/p</u>	

→ Voltage-Series f.b. :

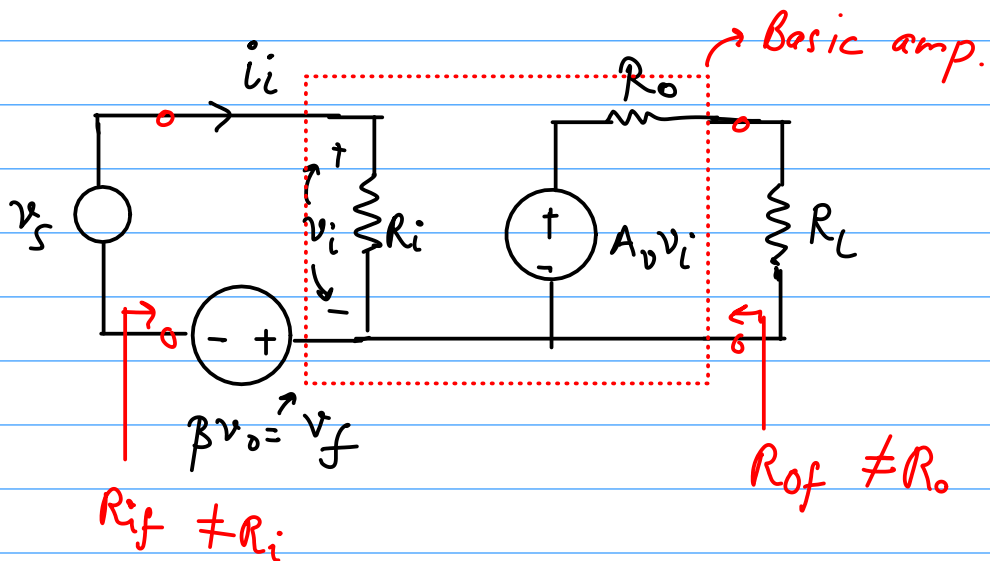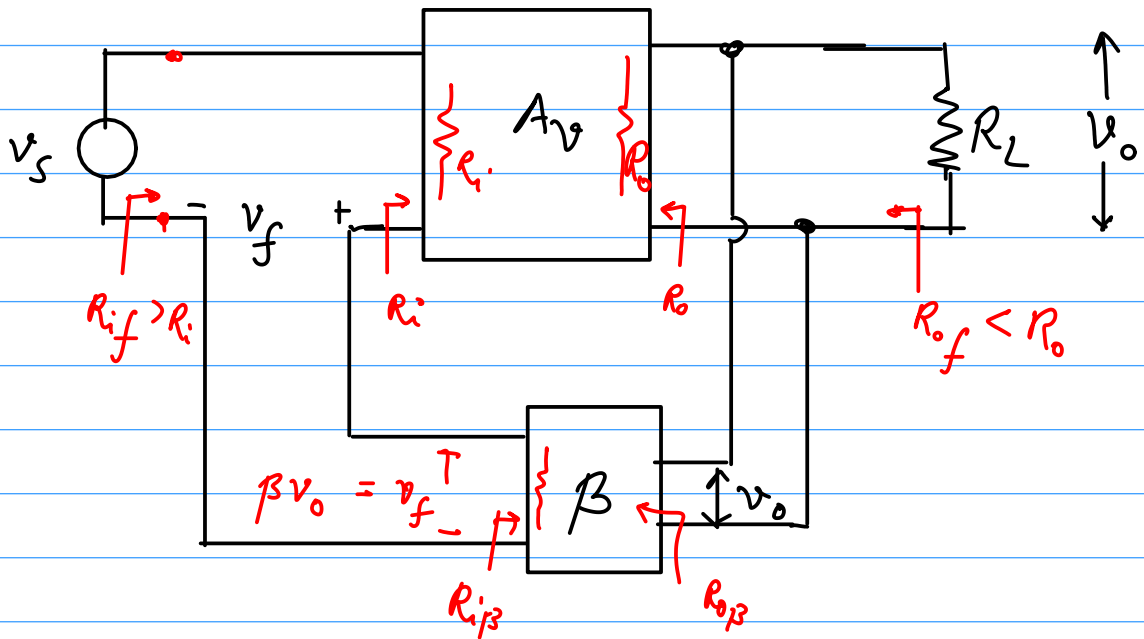



$$R_{if} = (1 + \beta A_v) R_i$$

$$R_{of} = \frac{R_o}{1 + \beta A_v}$$

B JT

Examples: Emitter follower (Common collector), Source follower (Common Drain), Voltage follower (Non-inverting OpAmp)

→ 2) Current series f.b. :

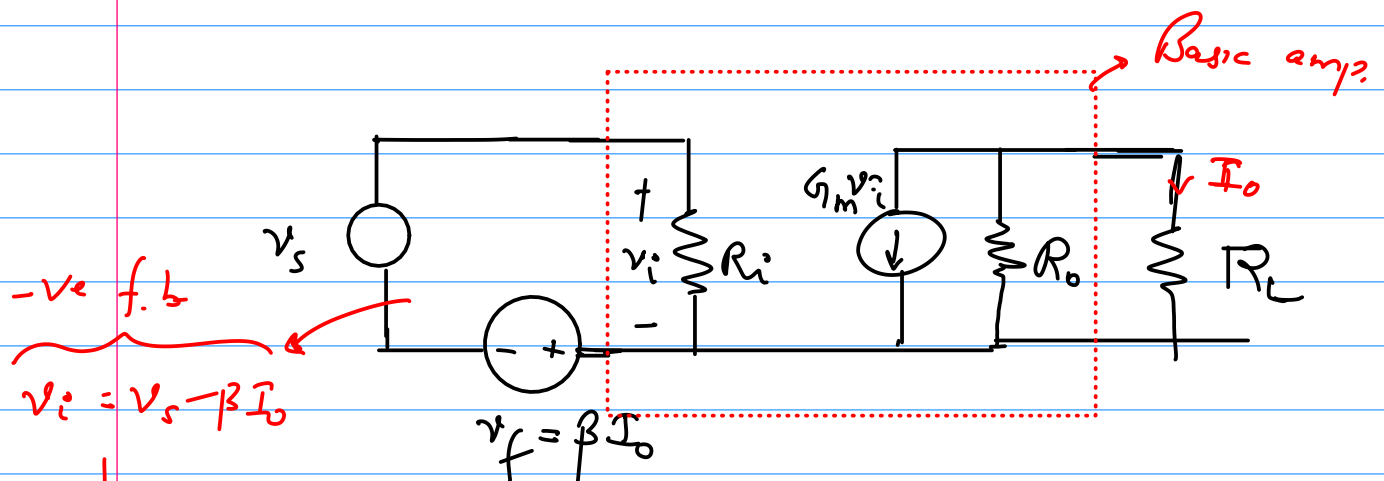
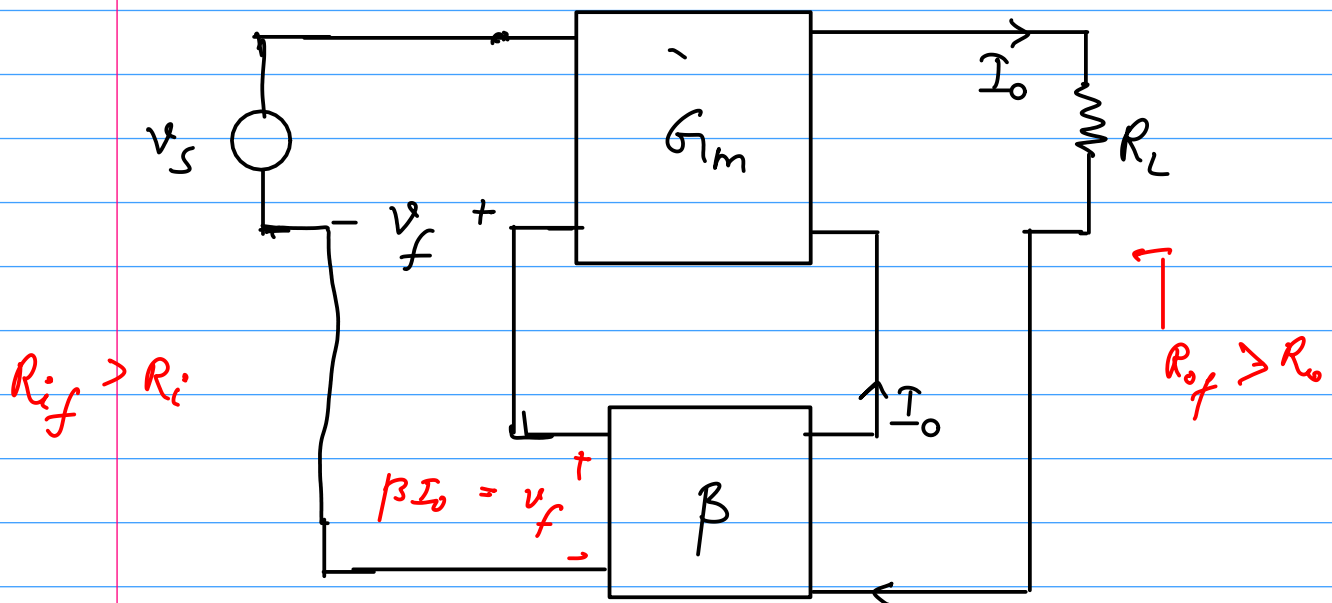


$$R_{if} = (1 + \beta G_m) R_i$$

$$R_{of} = (1 + \beta G_m) R_o$$

Better



→ 3) Voltage-Shunt f.b:

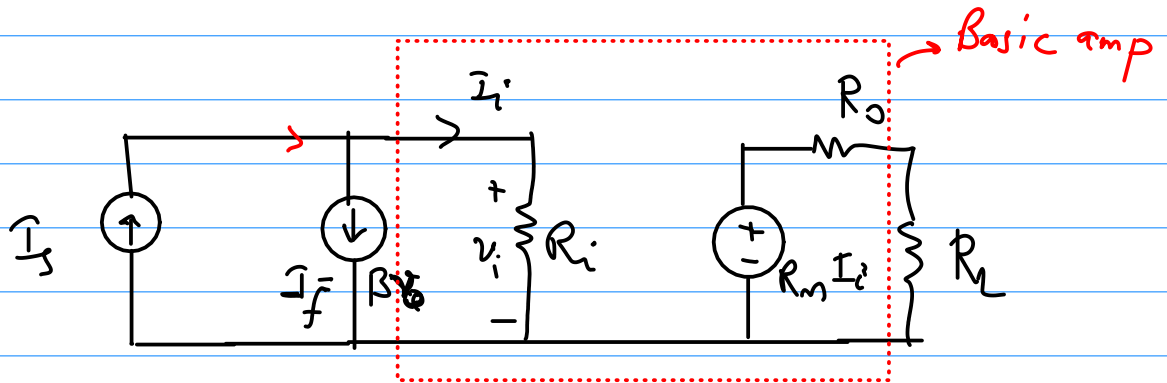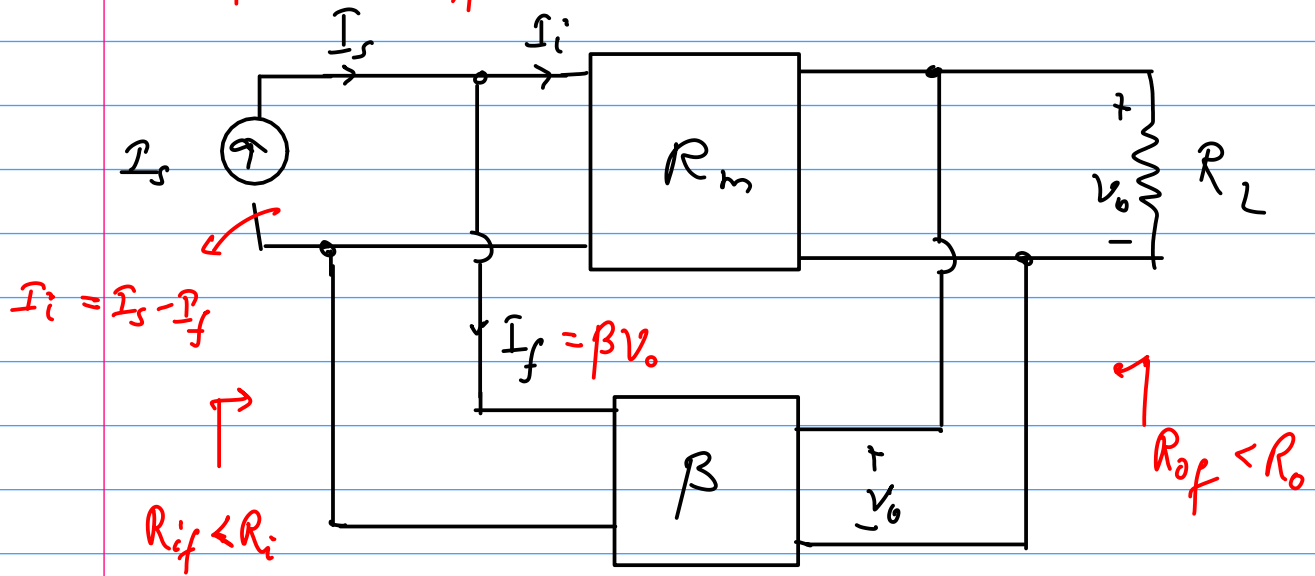

$$R_{if} = \frac{R_i}{(1 + \beta R_m)}$$

$$R_{of} = \frac{R_o}{(1 + \beta R_m)}$$

4) Current Shunt fb:

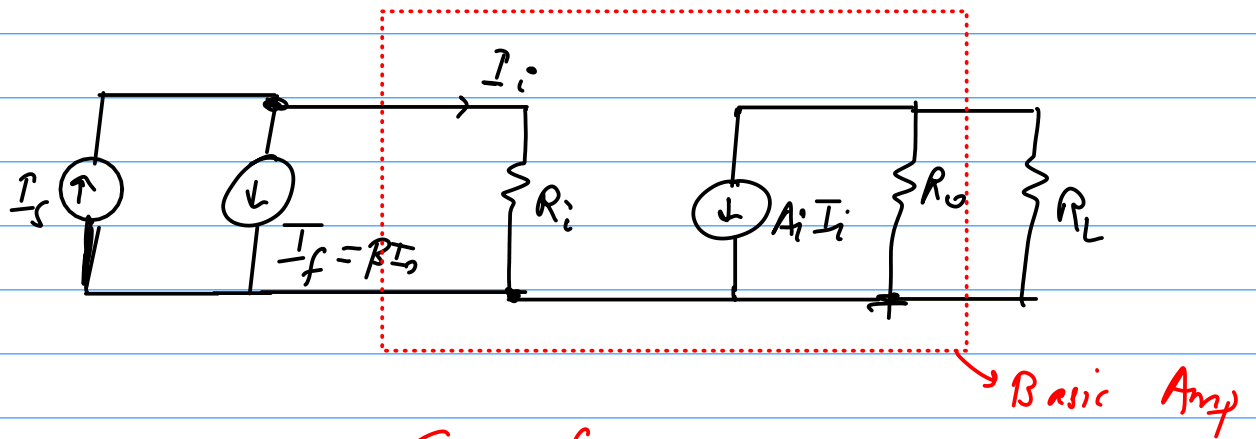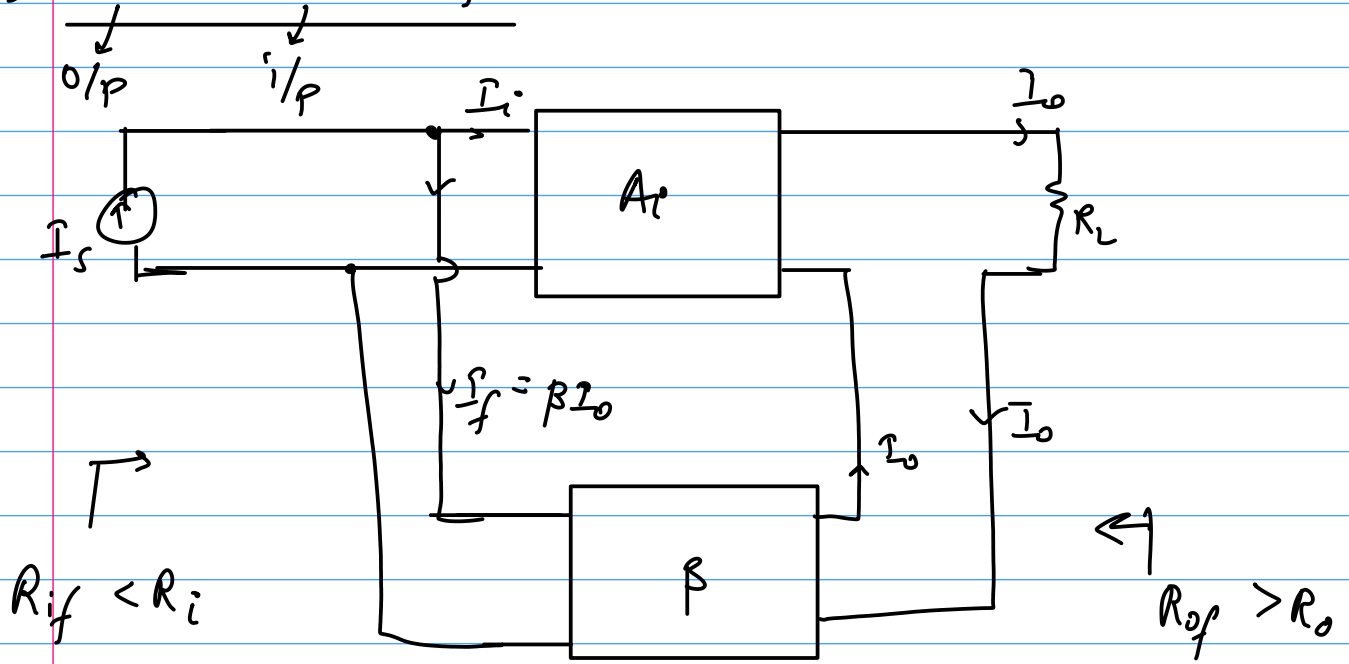

-ve f.b.

$$R_{if} = \frac{R_i}{1 + \beta A_i}$$

$$R_{of} = (1 + \beta A_i) R_o$$

Oscillators → o/p is periodic waveform (osc.)


Generator → Generates an o/p without any i/p

(it does need power supply
e.g. V_{cc} or V_{DD})




→ Barkhausen's Criterion:

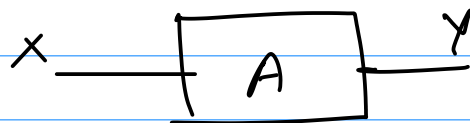Some conditions for sustained oscillations




(Amp. no osc.)

∴ there is an input

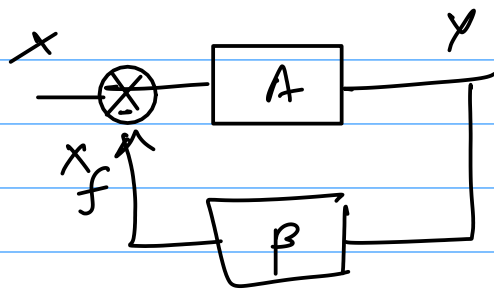

≡

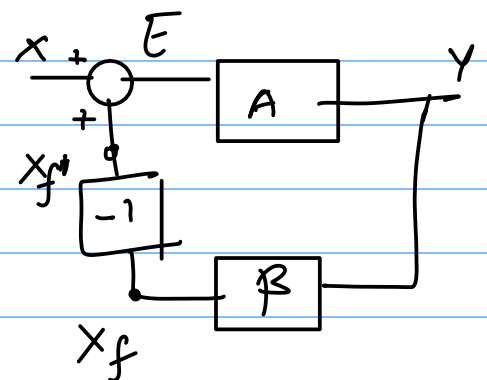


Negative feedback


$$X_{f'} = -X_f$$

if $X_f = X_i$ then

$$E = X - X_f = 0$$

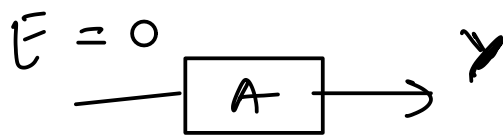

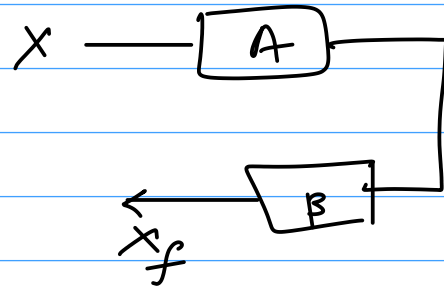we get o/p y with no i/p $\therefore E=0$
 $\underline{\underline{=}}$



to get $x_f = x_i$

$$AB = 1^*$$

Barkhausen's criterion :


1) $|AB| = 1$

2) $\angle AB = 0^\circ, \text{ or } 360^\circ \text{ or } 2n\pi$
 for -ve f-b system


Then no i/p is needed to generate o/p-

* if $|AB| < 1$ then


Unsustained osc.

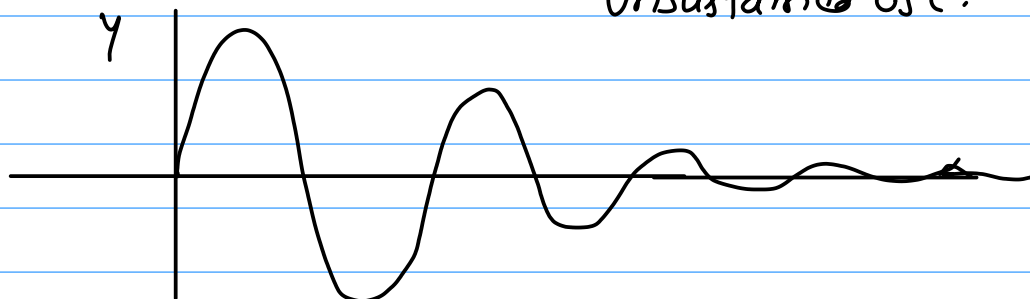


* If $|A\beta| > 1$

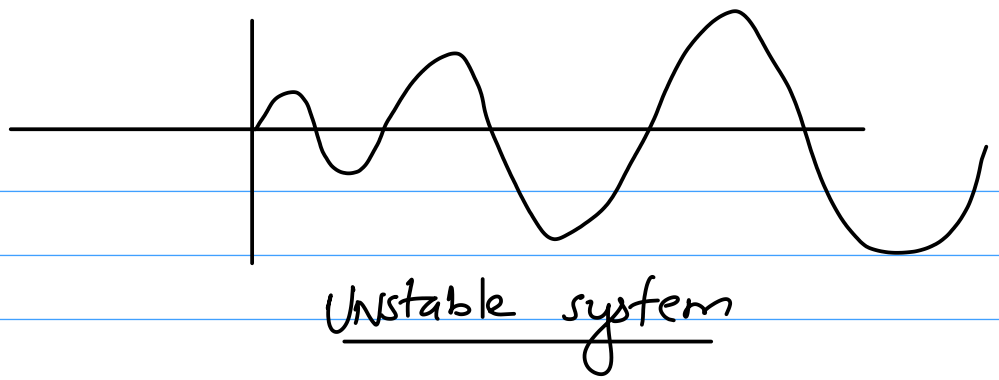

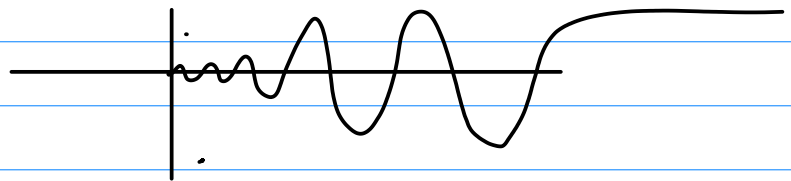Osc. don't keep \uparrow blindly. They are ultimately limited by supply vol, V_{CC} or V_{DD} .




So, ideally we want $|A\beta| = 1$

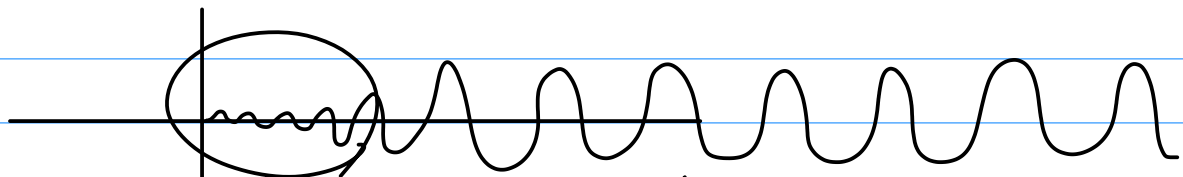

No i/p, so, some noise gets amplified

sustained osc.

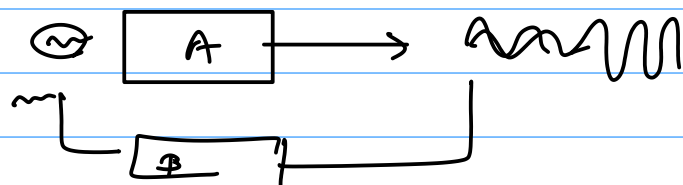

Practical considerations :

The noise initially needs to be amplified,

so,

$$|A\beta| \gtrsim 1$$

slightly

for sustained osc.

- * Also there are losses in the ckt so they prevent the o/p from keep increasing even if $|A\beta| > 1$


$\therefore |A\beta|$ is only slightly bigger than 1 & that is compensated by losses in the ckt.

* Properties of Osc :

1. Gain is ∞ (A_f) or v. large
2. +ve feedback \therefore loop gain = $A\beta \pm +ve$
3. System stability is less as compared to amplifier.
4. No i/p required externally.

The noise is sufficient to generate oscillations.

→ RC Phase Shift Osc. :

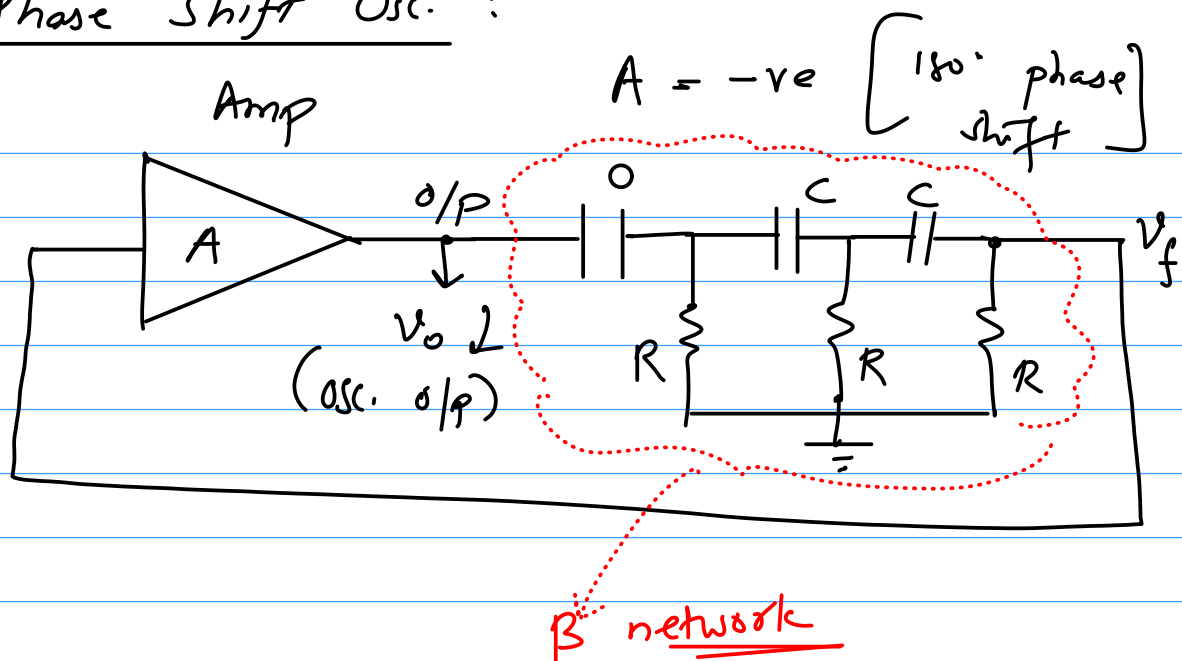

A, e.g. could be a CE amp, a CS amp or inverting Op-Amp.

if A provides 180° phase shift to the signal then the R-C network (β) should also provide 180° phase shift

i.e. if $A = -ve$


then $\beta = -ve$ should be

so, $\text{loop gain } A\beta = +ve = 360^\circ \text{ phase shift}$
 ↓
 +ve feedback

also, $|\beta| \geq \frac{1}{|A|}$ so that $|A\beta| \geq 1$

* 3 RC stages give 180° phase shift

So,

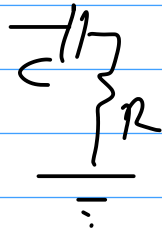


single RC stage

should give 60° phase.

* But if it is giving 60° then

overall ~~of~~ phase of 3 RC stages is

bigger than 180°

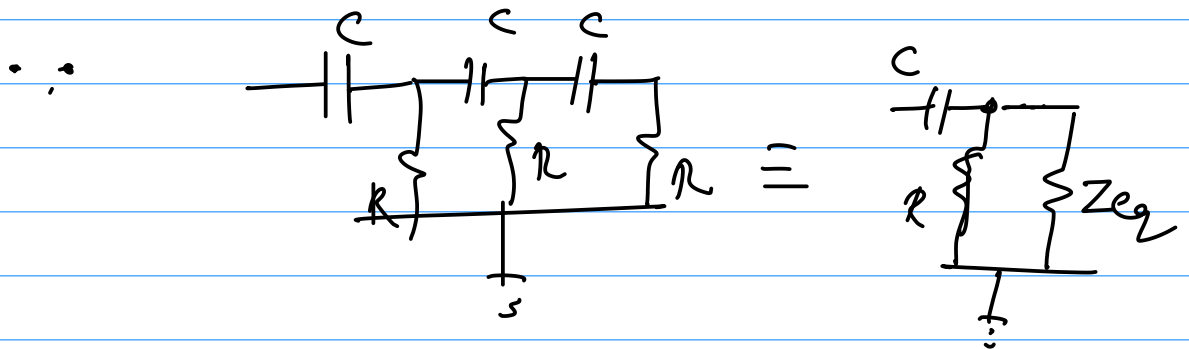

ϕ of first stage

$$= \phi_1 = \tan^{-1} \left(\frac{1}{\omega R_{eq}} \right) > \tan^{-1} \left(\frac{1}{\omega R} \right)$$

if $\tan^{-1} \left(\frac{1}{\omega R} \right) = 60^\circ$ (as per design)

$$R_{eq} = R \parallel Z_{eq} < R$$


$$\text{So, } \phi_1 > 60^\circ$$

* So, single RC stage phase, R & C should be designed such that

$$\tan^{-1} \left(\frac{1}{\omega R} \right) < 60^\circ$$

* Find Osc freq. :


1) find β

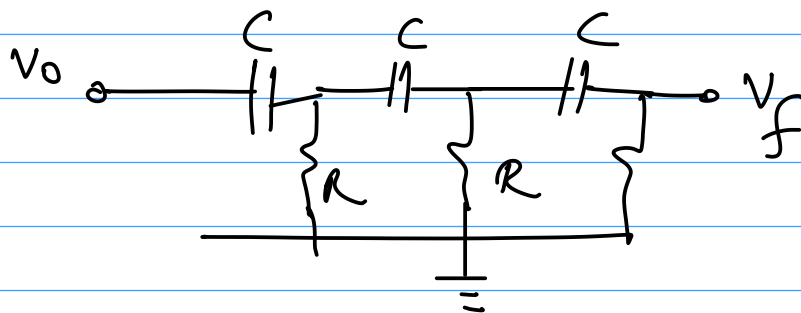

$$\beta = \frac{V_f}{V_o}$$

Replace C by $\frac{1}{j\omega C} = X_C$ (Reactance)

$$j = \sqrt{-1}$$

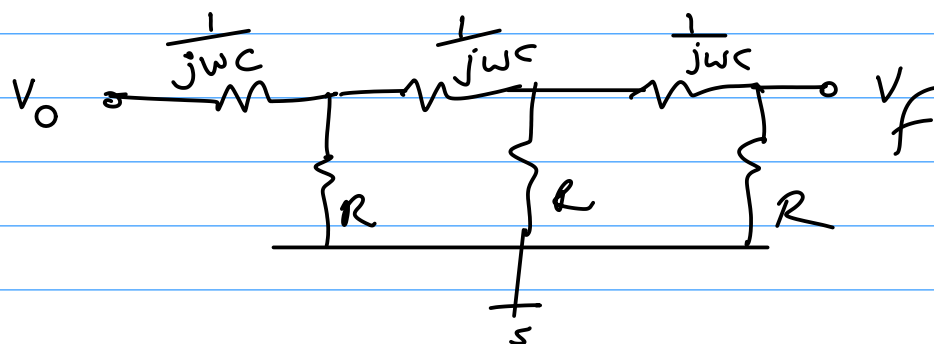

find $\frac{V_f}{V_o}$ from KVL & KCL = β

So, β will be a complex number.

$$\beta = X + jY \quad \angle \beta = \tan^{-1}\left(\frac{Y}{X}\right) = 180^\circ$$

Since $A = -ve$

phase = 180°

, β should be $-ve$

$\beta = -0.5$ e.g.
real number (no imag. part)

$$\tan^{-1}\left(\frac{Y}{X}\right) = 180^\circ$$

if $Y=0$ & $X = -ve$

2) Put $\text{Imag.}(\beta) = 0$ $\therefore \beta = f(j\omega)$
that gives ω

$$\omega = 2\pi f$$


\swarrow rad/sec \searrow Hz

This f is the freq. of osc.

3) So, $\beta = X + j0 \Rightarrow \boxed{\beta = X}$

So, Amp gain A should be $\boxed{A = \frac{1}{X}}$

Then we have an osc.

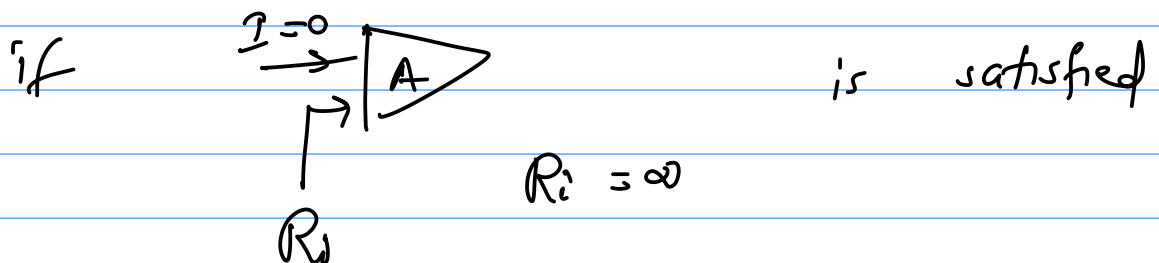

then $\boxed{f_o = \frac{1}{2\pi(\sqrt{6})RC}}$


\downarrow
osc. freq.

& in this case

$$\beta = -\frac{1}{29}$$

$$\text{So, } A = -29$$

or $|A| \geq 29$ slightly bigger

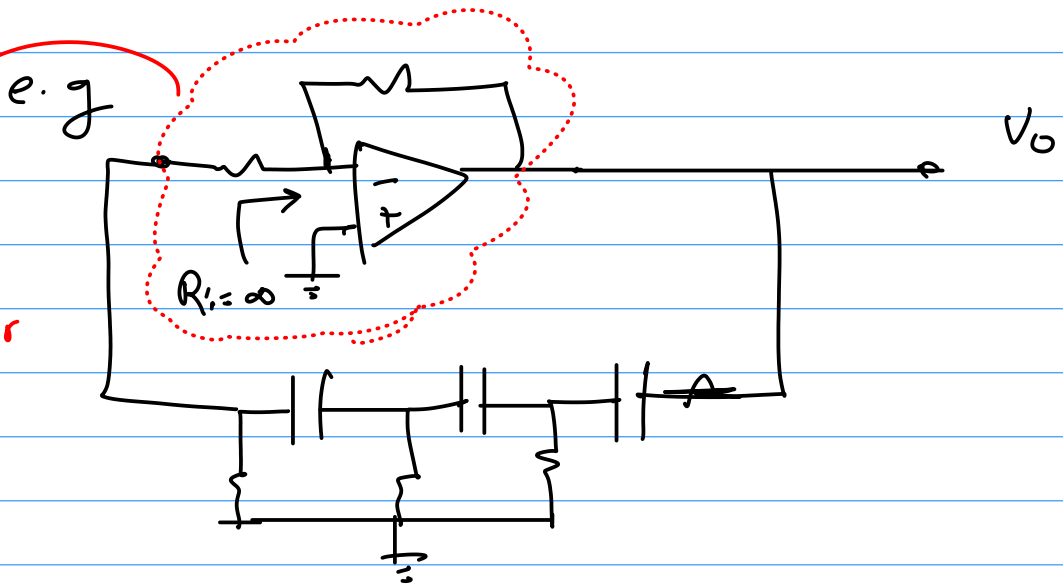

Inverting
Op Amplifier

$$|A| \geq 29$$

$$f_0 = \frac{1}{2\pi RC\sqrt{6}}$$