
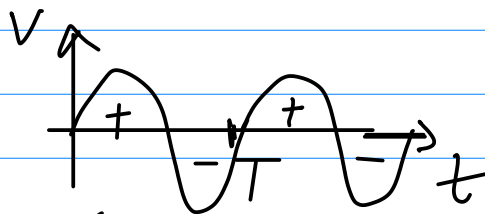


→ Rectifiers —

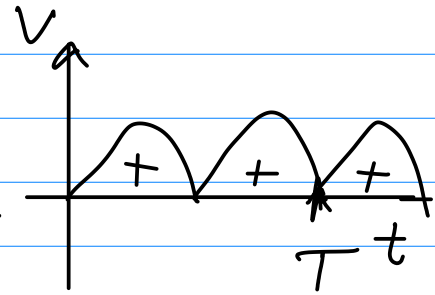

Rectifier




In ac signal
avg. vol. = 0

$$V_{avg} = \frac{1}{T} \int_0^T V(t) dt$$

Area under
vol. curve


(+ve area + (-ve) area)

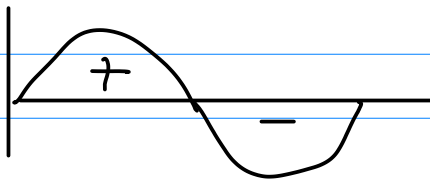

So, total area = 0

So, $V_{avg} = 0$

(or)

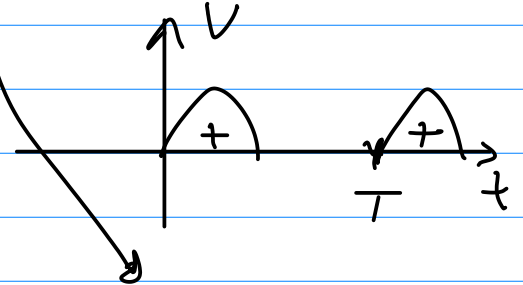

$V_{avg} = +ve$



∴ +ve area + 0

or +ve area
+ (+ve) area



* So, Rectifier is used to get +ve avg vol. or current from a zero avg vol. or current signal (symmetric ac)

* (Or) rectifier increases the avg vol. or current in a signal.



* Avg vol can also be called 'dc' vol.

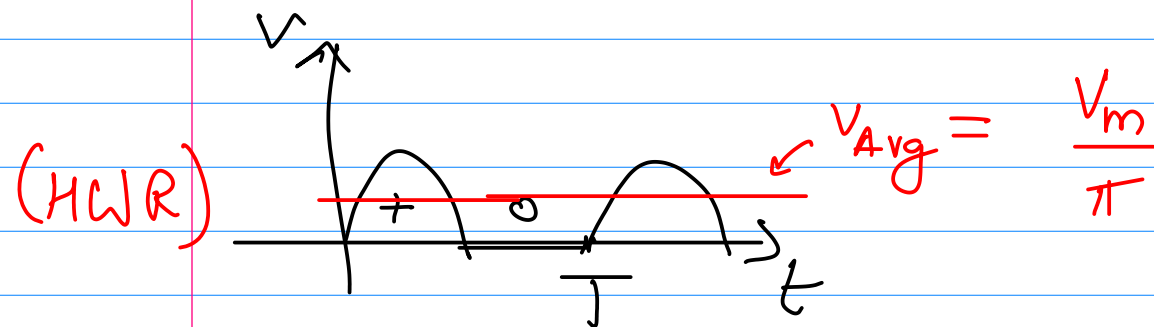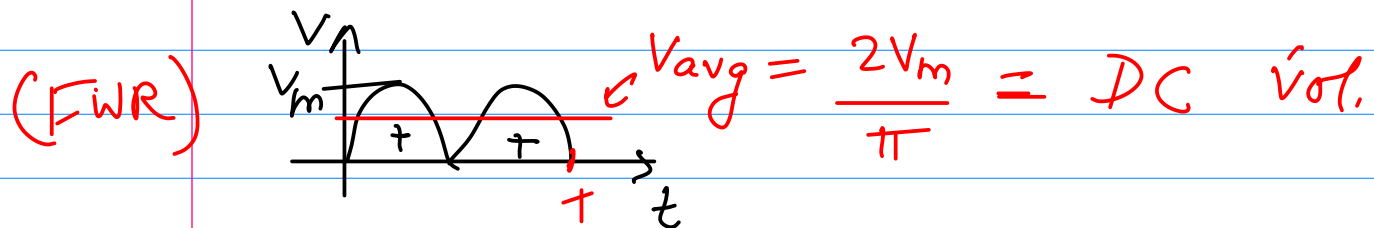

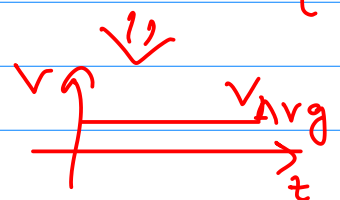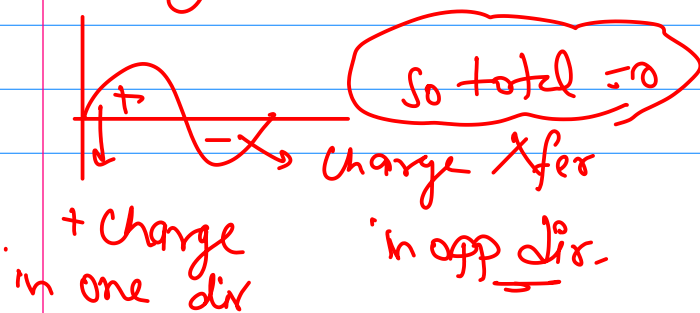
* Avg vol is that DC vol which if applied to a resistance will cause same amount of charge transfer as the original non constant signal



→ Half wave Rectifier- (HWR) -

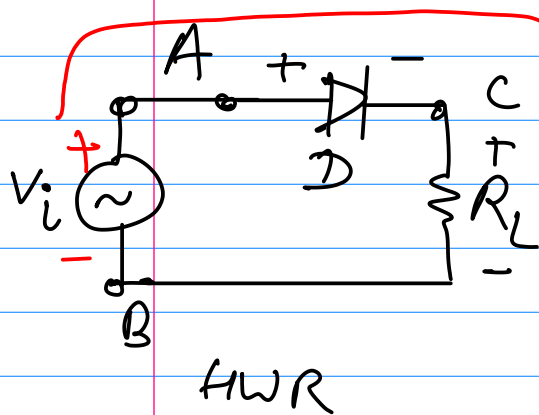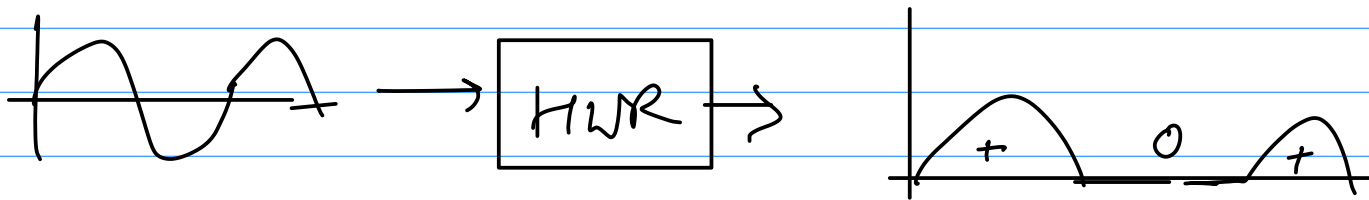

(i) for +ve half cycle of V_i

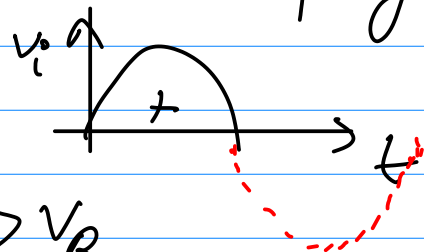


$$V_A > V_B$$

$$\underline{V_A > V_C > V_B}$$



$$\boxed{V_o = V_{CB} = V_C - V_B}$$

So, Diode \$D\$ is F.B. $A \rightarrow D \rightarrow C \equiv A \text{ --- } C$
(assuming ideal diode)



So ckt
(for +ve
half cycle)

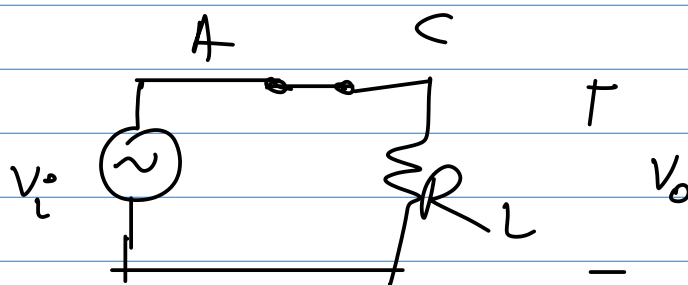


By KVL, $V_i = V_o$

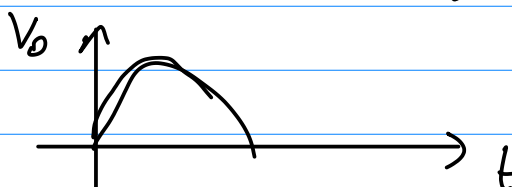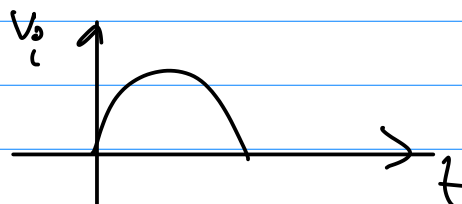

(ii) -ve half cycle -

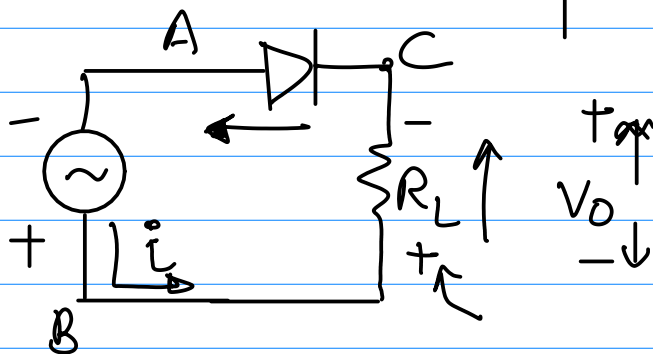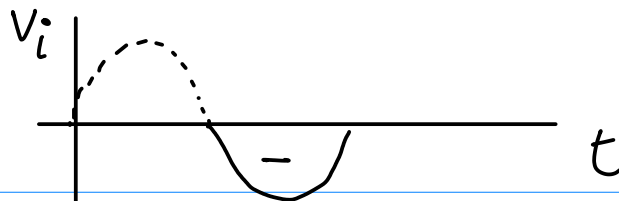

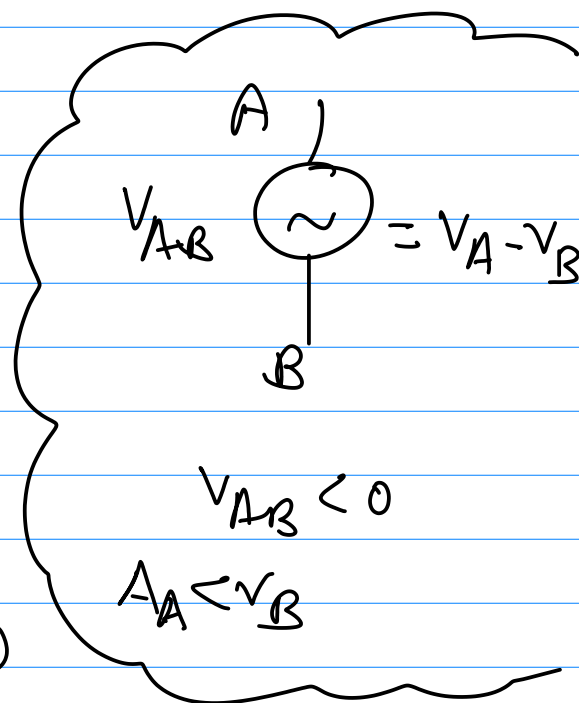$V_B > V_C$ (it seems)
if there is
current (anti-clockwise)




$$V_B > V_A$$

For anticlockwise current, Diode current is from N to P (Reverse Bias)

(or) $V_A < V_C$

For R.B., $A \text{ --- } \text{Diode} \text{ --- } C \equiv A \text{ --- } \circ \text{ --- } \circ \text{ --- } C$


So, ckt becomes

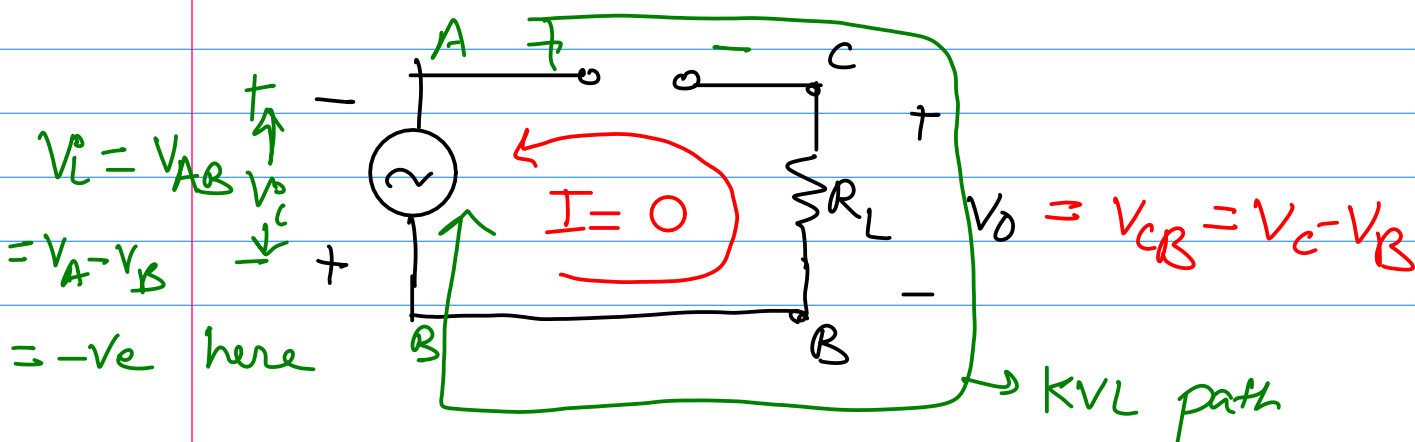

\therefore o.c., $I = 0$, Using KVL,

$$+V_i - V_{AC} - V_D = 0 \Rightarrow V_i = V_{AC} = V_{AB}$$

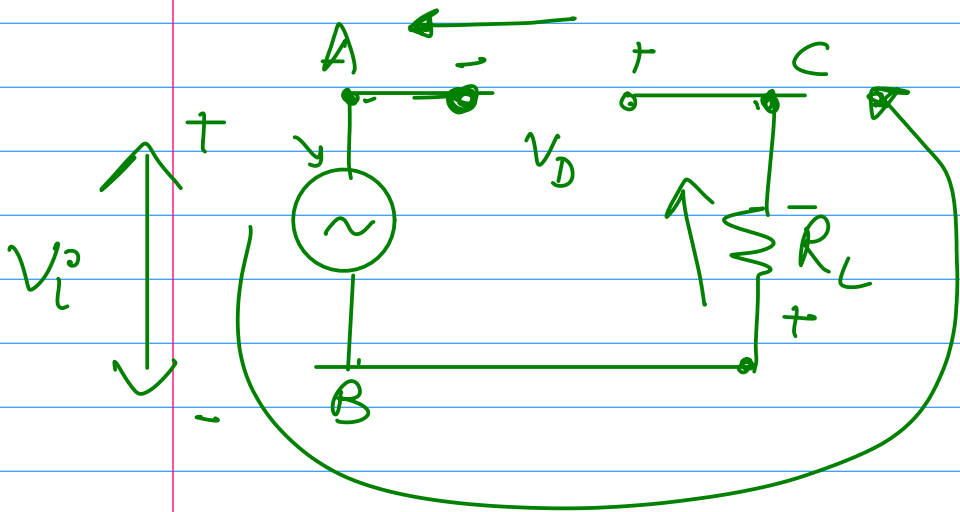also, $V_D = -I \cdot R_L = 0$ ($\because I = 0$)



\rightarrow (-ve value)
 $V_i = V_{AB}$
 $= V_A - V_B$
 (by def.)

$$-V_i - V_{R_L} - V_D = 0$$

$$V_{R_L} = I \cdot R_L = 0 \quad (\because I = 0)$$

$$-V_i - V_D = 0 \Rightarrow V_D = -V_i$$



(Where $V_D = V_C - V_A = V_{CA}$)

$$V_{CA} = -V_i \quad (\text{or}) \quad V_{AC} = V_i = V_{AB}$$

$$V_B = V_C \quad (\because V_{BC} = V_{R_L} = 0)$$


$S_0, V_D = V_{CB} = 0$

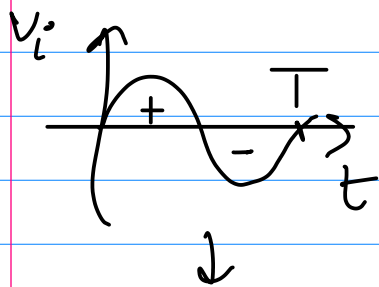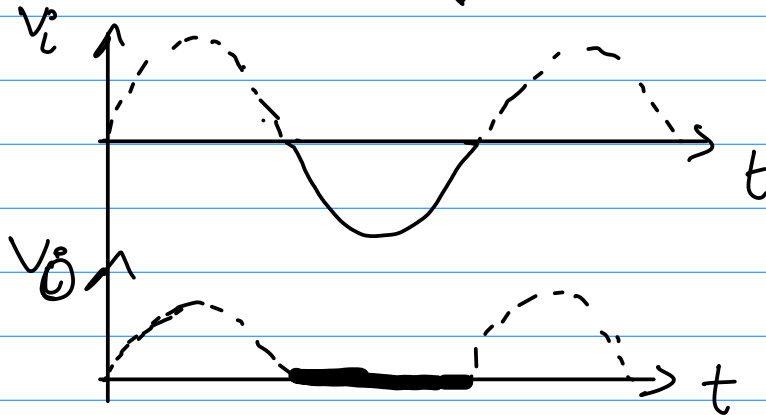& $V_{AC} = V_i = -ve$ (So, diode is actually R.B)
 P \swarrow \searrow N (-ve half cycle)



$V_{Avg} = V_{dc} = 0$

→ HWR →

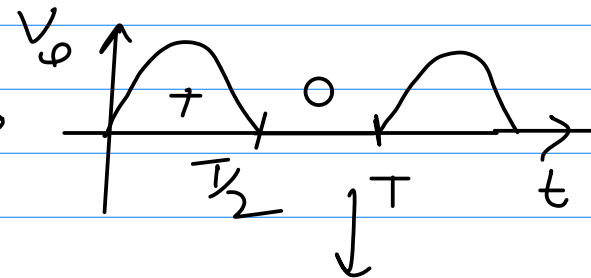

$V_{avg} = V_{dc} = +ve$

*

$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt$$

for any $v(t)$

→ Definitions - let's have a vol. signal $v(t)$

1. V_{RMS} - (root _{of} mean _{of} square) → (avg)

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

let $v_1(t) = V_m \sin(\omega t + \phi)$





$$V_{RMS} = \frac{V_m}{\sqrt{2}}$$

ϕ can be anything,
 ω can be anything,


*

RMS value is independent of freq & phase of a signal. It only depends on the shape.

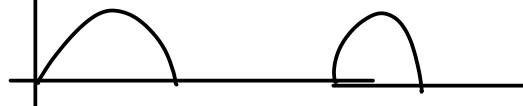ex2) $V_2(t)$  $V_{2rms} = \frac{1}{\sqrt{2}} \frac{V_m}{\sqrt{2}} = \frac{V_m}{2}$

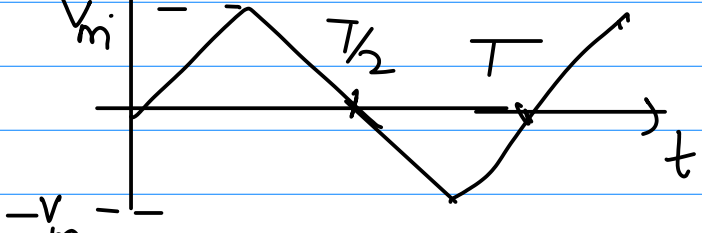$V_3(t)$  $V_{3rms} = \frac{V_m}{\sqrt{2}}$

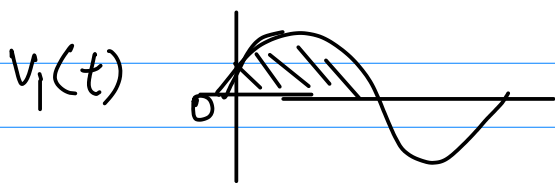(2) $V_{avg} = V_{dc} = \frac{1}{T} \int_0^T V(t) dt$




if Avg is taken over 1 period (T)

$V_{avg} = 0$

But for sinusoidals (or osc. signals),
avg is taken over $\frac{1}{2}T$.


$V_{avg} = \frac{2V_m}{\pi}$

 $\rightarrow V_{avg} = \frac{2V_m}{\pi}$ (over T)

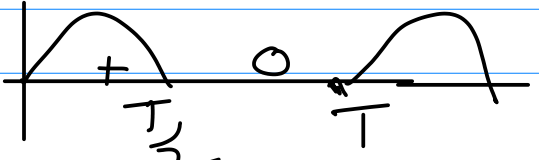 $V_{avg} = \frac{V_m}{\pi}$ (over T)

3) Ripple vol. - assume $v(t) = 5 + 2 \sin \omega t$

Plot it $v(t) = v_1(t) + v_2(t)$

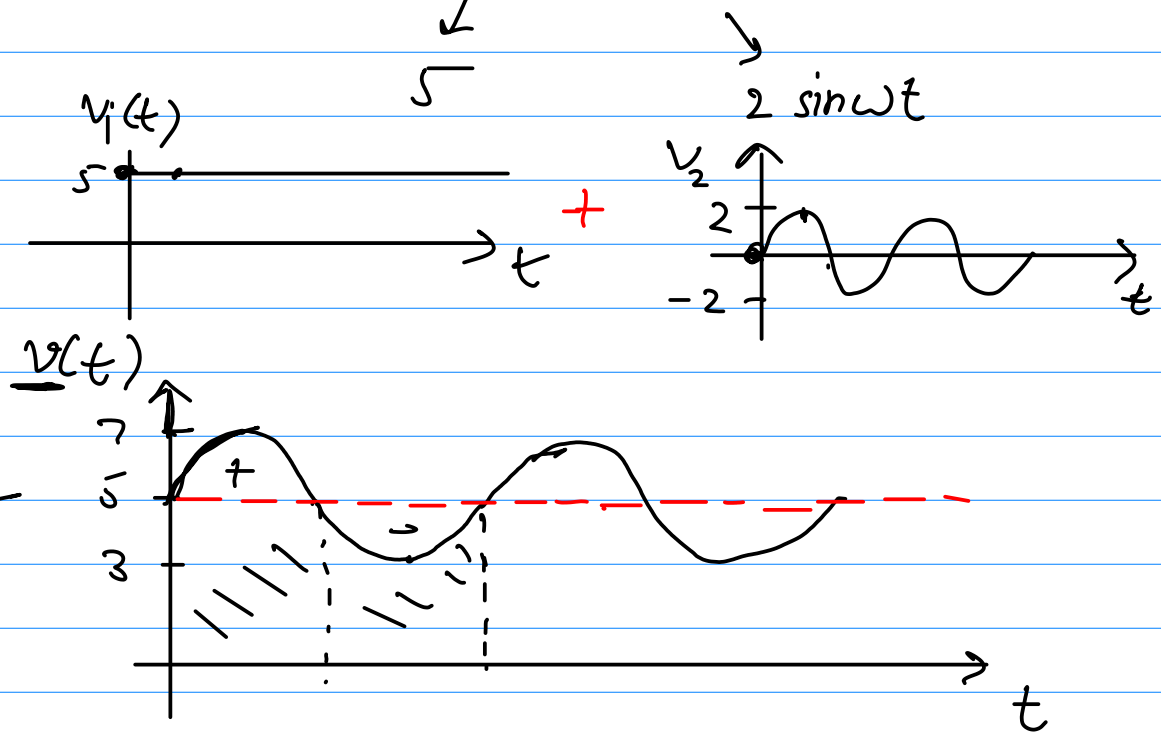

has 2 parts —
 → DC part (avg) constant
 → ac part (osc. about the avg value)

avg or dc value = 5

$$V_{dc} = 5$$

other part is called the ac vol.

$$V_{ac} = 2 \sin \omega t \quad \& \quad v(t) = V_{dc} + V_{ac}$$

Now the max deviation of $v(t)$ from avg value V_{dc} is called the "Ripple vol." (V_r)

* Ripple vol is amplitude of the osc part,

$$v(t) = 5 + 2 \sin \omega t$$

V_{rms} ?

$$V = V_1 + V_2$$

$$V_{Rms} = \sqrt{V_{1rms}^2 + V_{2rms}^2}$$

(comes from power)

$$\text{Power} = I^2 R = I_{rms}^2 R = \frac{V_{rms}^2}{R}$$

$$\left(\because V_{rms} = I_{rms} R \right)$$

$$\text{Power due to } V = \text{Power}_{V_1} + \text{Power}_{V_2}$$

$$\frac{V_{rms}^2}{R} = \frac{V_{1rms}^2}{R} + \frac{V_{2rms}^2}{R}$$

$$V_{rms} = \sqrt{V_{1rms}^2 + V_{2rms}^2}$$

$$V(t) = 5 + 2 \sin \omega t$$

for V_{dc} , RMS value is same as V_{dc}

$$\begin{array}{c} 5 \\ | \\ \hline \end{array} \rightarrow \underline{\underline{RMS = 5}}$$

$$V_{rms} = \sqrt{5^2 + \left(\frac{2}{\sqrt{2}}\right)^2}$$

$$V_{rms} = \sqrt{V_{dc}^2 + (V_{ac rms})^2}$$

$$V_{ac rms} = \sqrt{V_{rms}^2 - V_{dc}^2}$$

$$V_{ac rms} = V_{dc} \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$$

4) Ripple factor - $\gamma = \frac{V_{ac rms}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}}$

$$\gamma = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$$

5) Form factor —

$$F = \frac{V_{rms}}{V_{dc}}$$

$$\text{So, } \gamma = \sqrt{F^2 - 1}$$

*

For Rectifiers, O/p should as DC as possible so, ripple factor γ should be as low as possible

$$\text{Ideally } \gamma = 0 \\ \& F = 1$$


① Crest factor = $C = \frac{\text{Peak vol.}}{\text{rms vol.}}$

→ Rectifier efficiency,

$$\eta = \frac{\text{o/p dc power}}{\text{i/p ac power}} \times 100\%$$

[* $V_i = V_m \sin(\omega t)$]
for HWR-

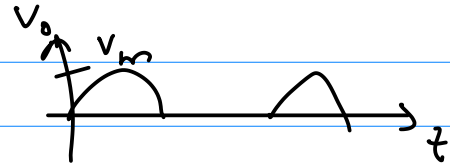(i) V_{orms} or $V_{\text{rms}} = \frac{V_m}{2}$



(ii) V_{avg} or V_{dc} (o/p) = $\frac{V_m}{\pi}$

(iii) Form factor - $F = \frac{V_{\text{rms}}}{V_{\text{dc}}} = \frac{V_m/2}{V_m/\pi} = \frac{\pi}{2}$

$F = 1.57$

(iv) Ripple factor - $r = \sqrt{F^2 - 1} = 1.21$

(vi) Crest factor - $\frac{\text{peak}}{\text{rms}} = C = \frac{V_m}{V_m/2} = 2$



(vi) PIV - (Peak inverse vol) -

during -ve $\frac{1}{2}$ cycle

(\because diode is Oc)



$$V_D = V_i = -ve$$

(R.B.)

$$V_i /_{max} = V_m$$

$$V_D /_{max} = -V_m$$

$$\boxed{PIV = -V_m} \text{ for HWR}$$

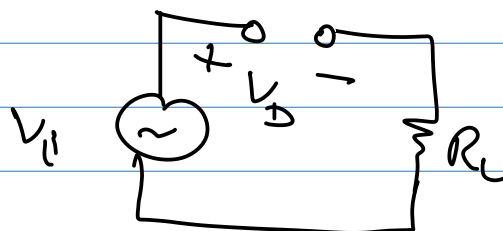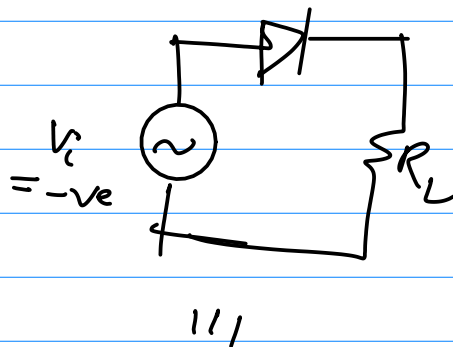

* PIV for any ckt should be as low as possible.

* Transfer Characteristics of HWR-


(ideal diode) **

	V_i	V_o
(i)	+ve	V_i
(ii)	-ve	0

V_o vs V_i

$$V_i = -ve$$

$$V_o = 0$$

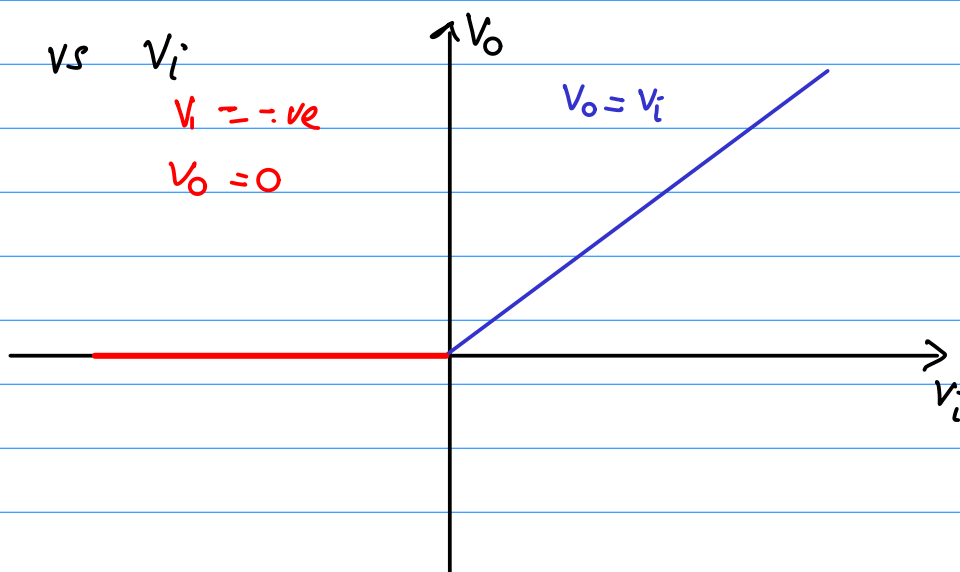


for practical diode-

(i)

$$V_i > V_f$$

$$(V_i = V_{AB} = V_A - V_B)$$

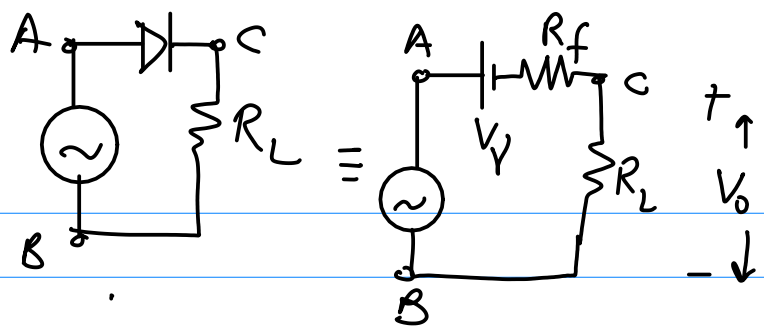

By KVL, $V_o = V_i - V_f - I R_f$

$$R_L I = V_o$$

$$V_o = V_i - V_f - \frac{V_o}{R_L} \cdot R_f$$


$$V_o \left[1 + \frac{R_f}{R_L} \right] = V_i - V_f$$

$$V_o = \frac{R_L}{R_L + R_f} (V_i - V_f)$$

$$\Rightarrow V_o = \left(\frac{R_L}{R_L + R_f} \right) \cdot V_i - \left(\frac{R_L}{R_L + R_f} \right) V_f$$




$$y = mx + c$$

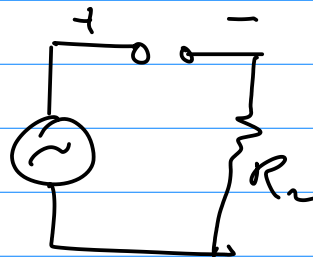(ii) $V_i < V_f$ Diode \rightarrow R.B. \rightarrow





$$V_o = 0$$




(by KVL)

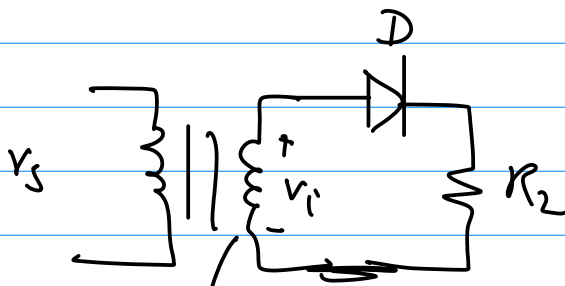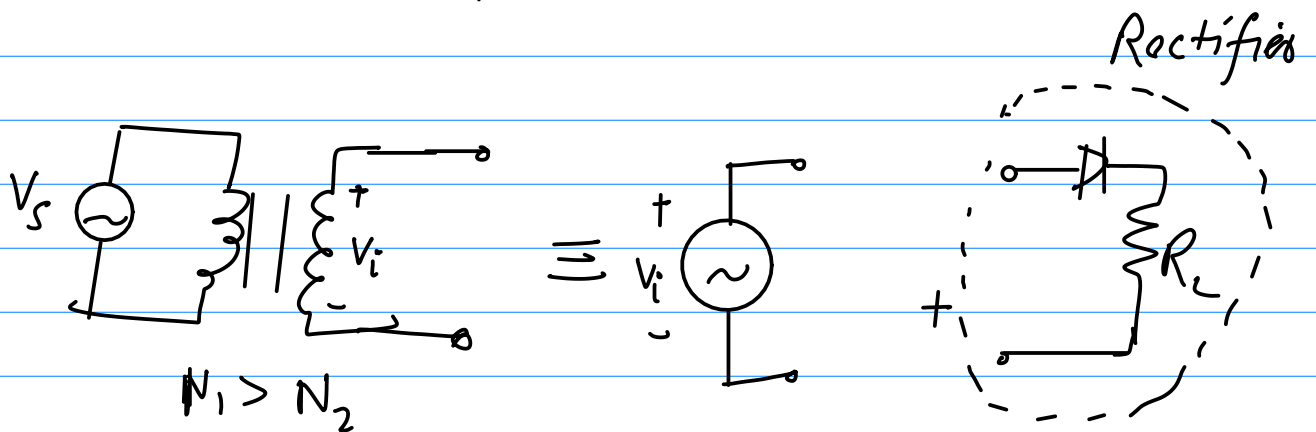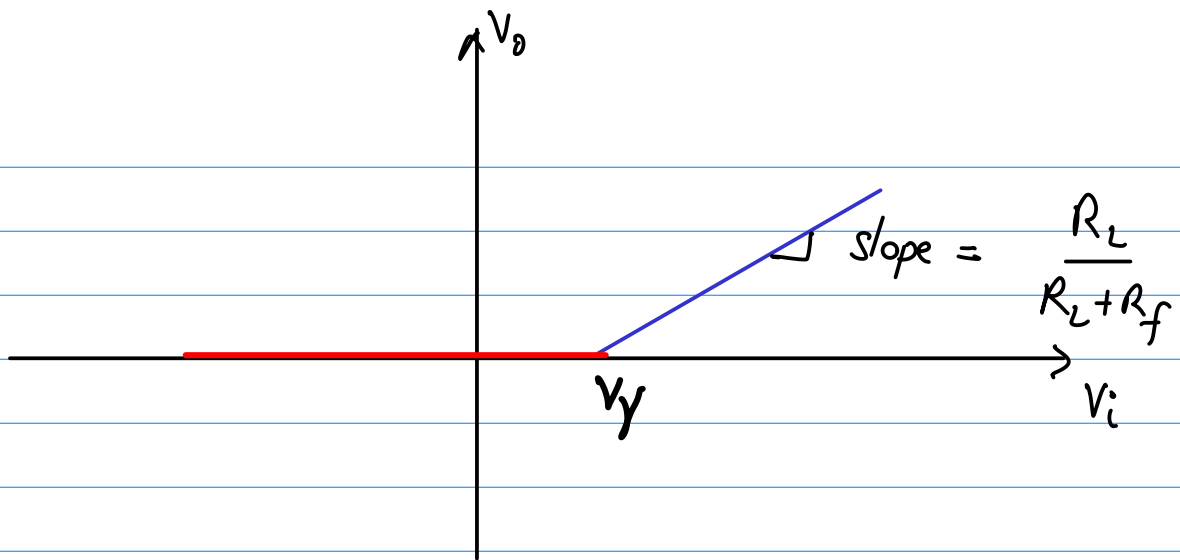


$$V_i = V_m \sin \omega t$$

(same analysis)

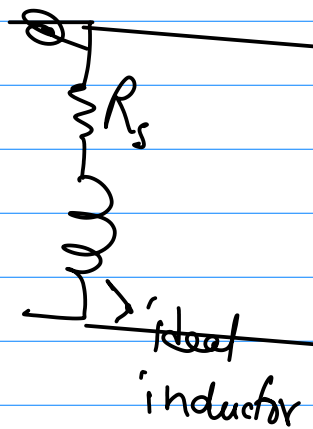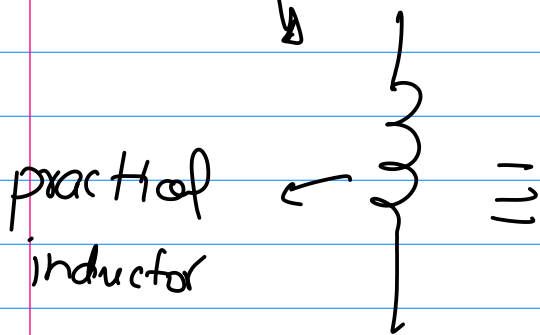

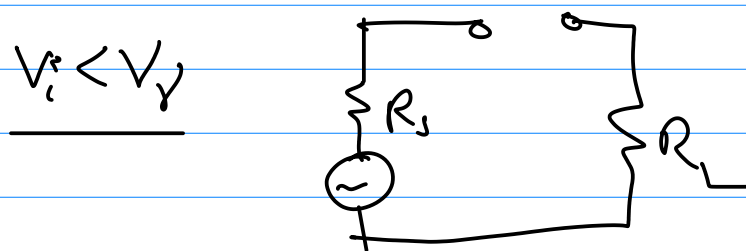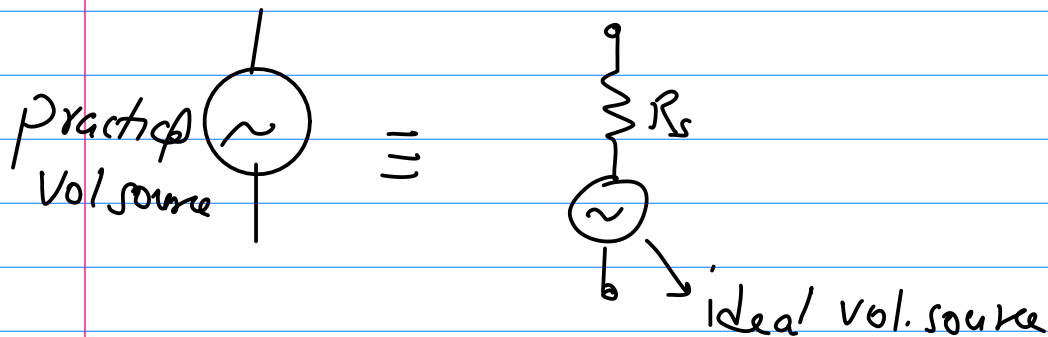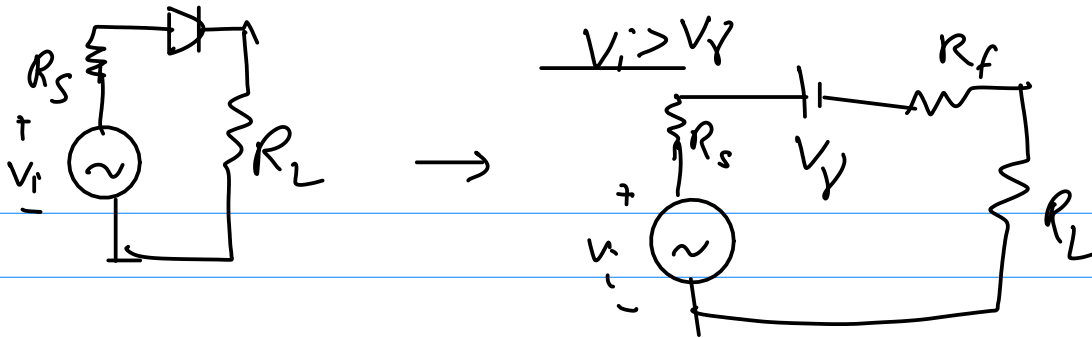

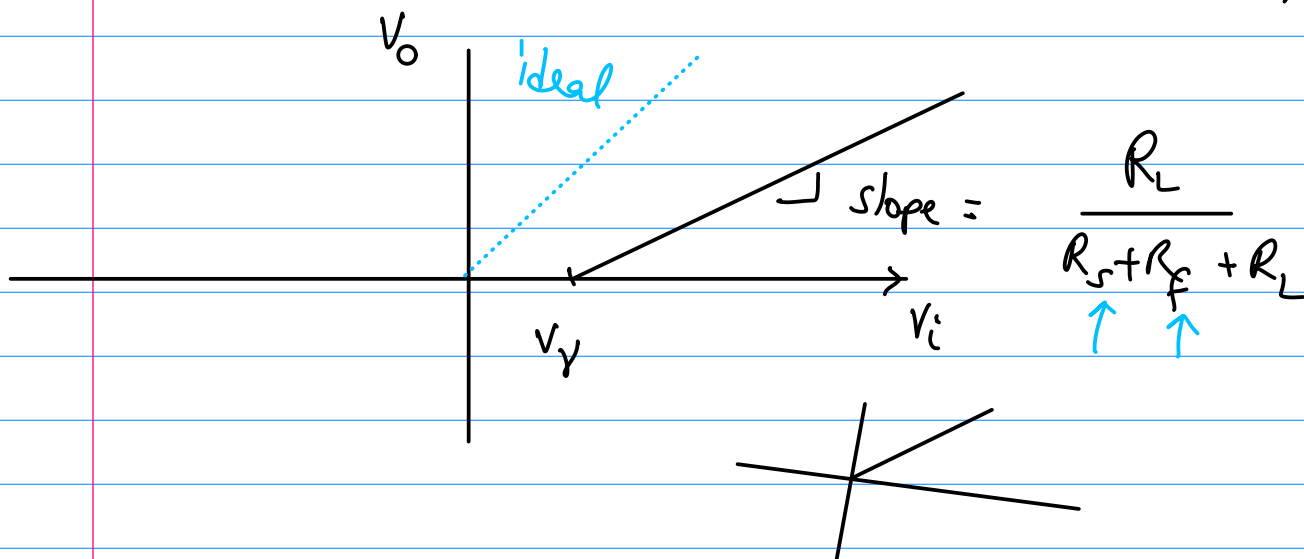
for $V_i > V_Y$, $V_o = \left(\frac{R_L}{R_S + R_f + R_L} \right) V_i - \left(\frac{R_L}{R_S + R_f + R_L} \right) V_Y$



When $V_i = V_m$

$$V_o = \left(\frac{R_L}{R_s + R_f + R_L} \right) V_m - \left(\frac{R_L}{R_s + R_f + R_L} \right) V_i$$

$$V_o < V_m$$

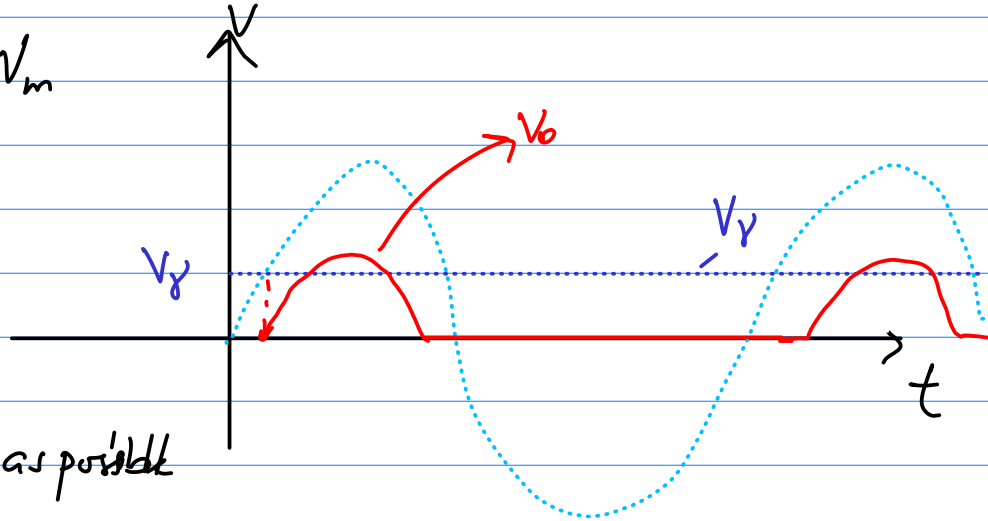

make as small as possible


if $(R_s + R_f) \ll R_L$

then
$$\frac{R_L}{(R_s + R_f) + R_L} \approx \frac{R_L}{R_L} = 1$$

 \downarrow
 neglected

2) FWR — { 1. Centre tapped
 2. Bridge

2.1) Centre Tapped X formor FWR -

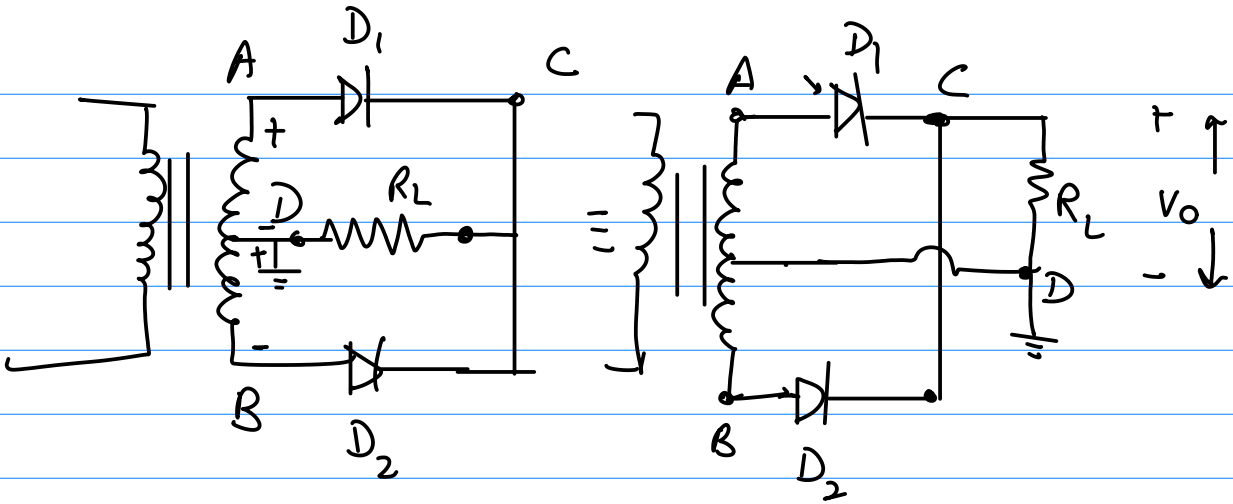

in +ve $\frac{1}{2}$ cycle of i_p

$$V_{AD} = V_m \sin \omega t \quad (+ve)$$


$$V_{DB} = V_D - V_B = V_m \sin \omega t \quad (+ve)$$

$$V_{BD} = -ve$$

$D_1 \rightarrow F.B. \quad (V_A > V_C)$

$D_2 \rightarrow R.B. \quad (V_B < V_C)$



(ideal diodes)

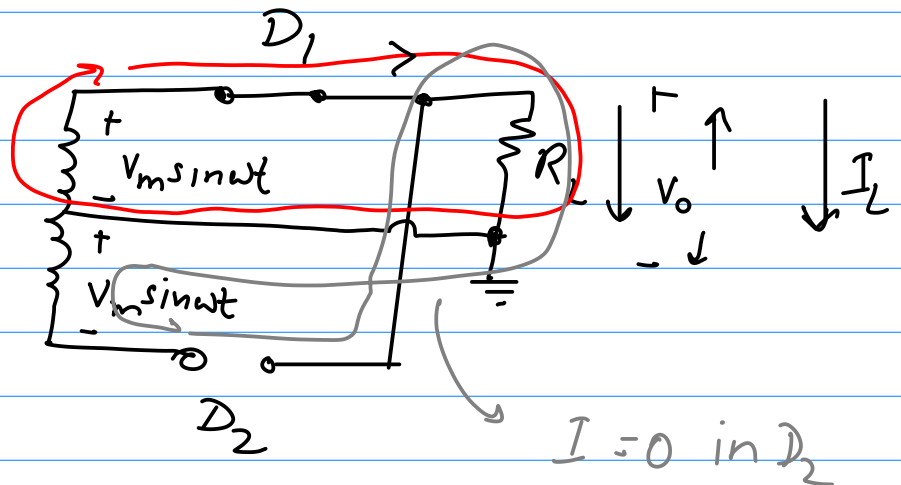

KVL \rightarrow



$$V_o = V_m \sin \omega t$$

-ve $\frac{1}{2}$ cycle -

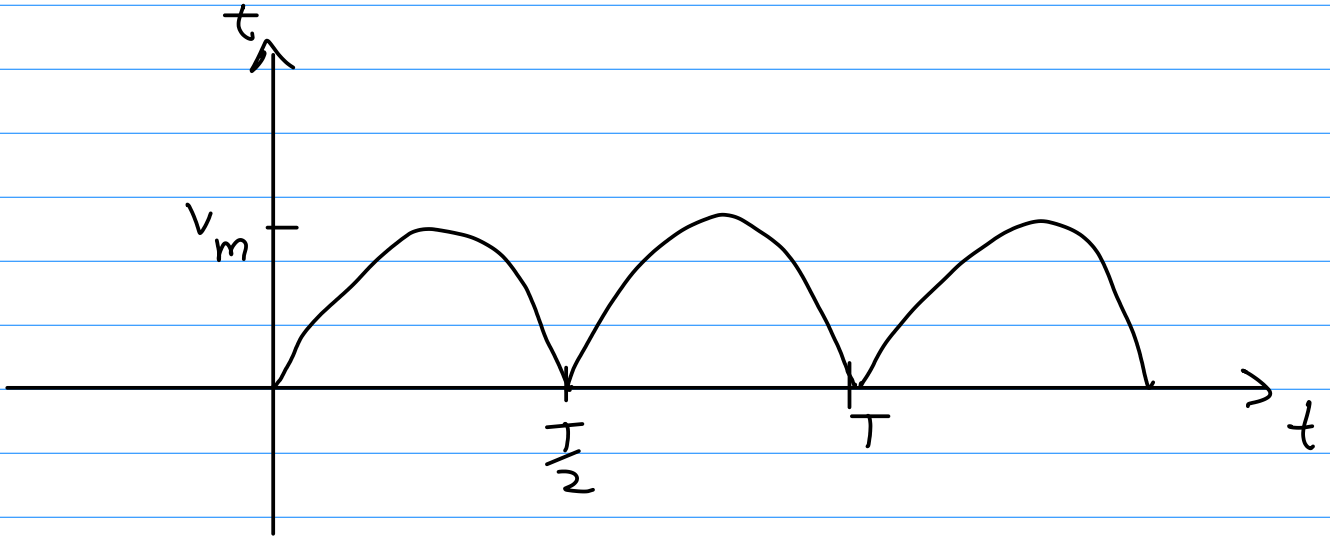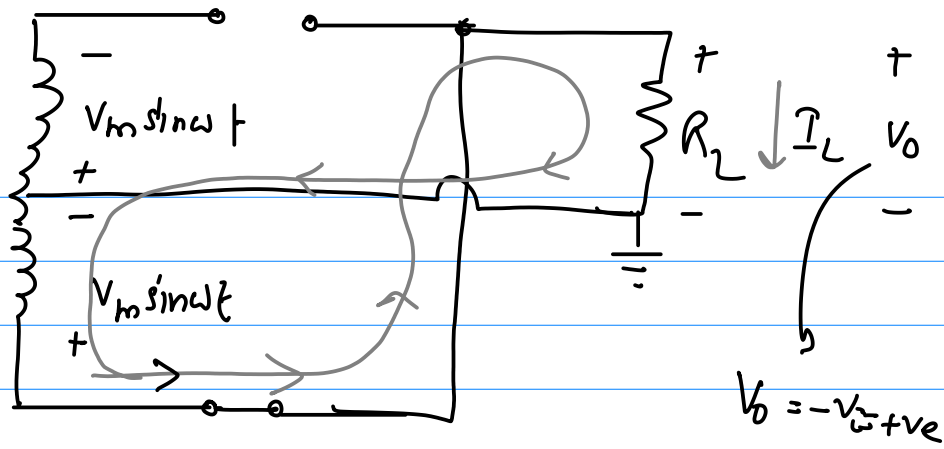

* Using practical diodes (& practical windings in Xformer)
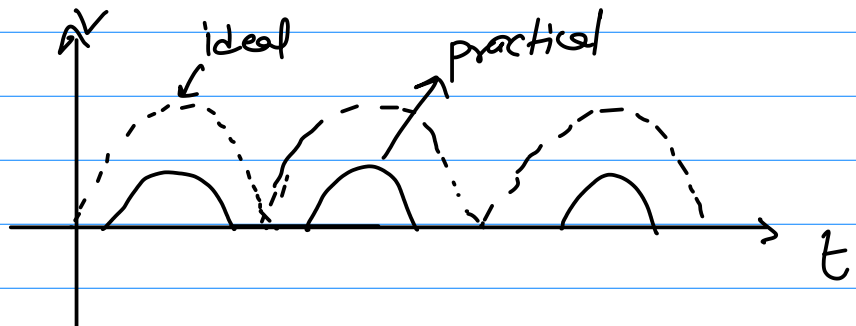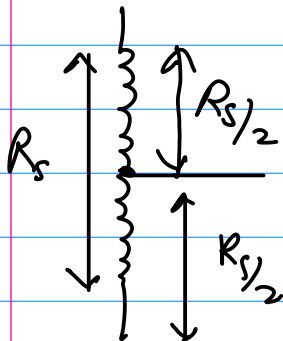
$$V_o = \left(\frac{R_L}{R_f + \frac{R_s}{2} + R_L} \right) V_i - \left(\frac{R_L}{R_f + \frac{R_s}{2} + R_L} \right) V_f$$



* Rectifier Efficiency, $\eta = \frac{\text{o/p dc power}}{\text{i/p ac power}} \times 100\%$


o/p dc power - dc power consumed by load (R_L)

$$= I_{Ldc}^2 R_L$$

$$I_{Ldc} = ?$$

$$I_L = \begin{cases} I_m \sin \omega t & \text{for } 0 < t < \frac{T}{2} \\ -I_m \sin \omega t & \text{for } \frac{T}{2} < t < T \end{cases}$$

+ve
+ve

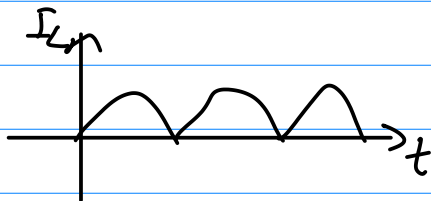

$$I_m = \frac{V_m}{R_L}$$

$$I_{avg} = I_{Ldc} = \frac{2I_m}{\pi}$$


i/p ac power -

$$V_{i_{rms}} \cdot I_{i_{rms}}$$

input vol current from the i/p vol source

(at secondary windings)

$$V_{i_{rms}} = \frac{V_m}{\sqrt{2}}$$

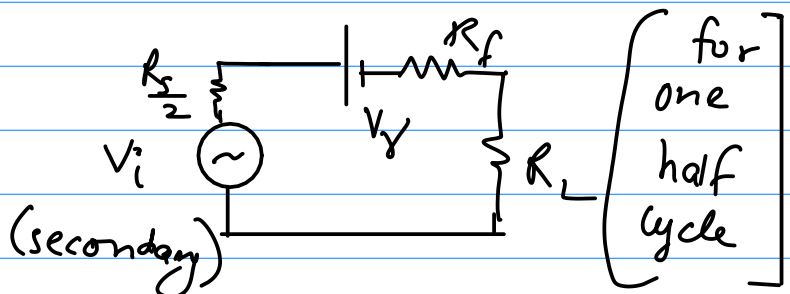

(let's ignore the effect of V_f)

write KVL ($V_p = 0$ assumption),

$$V_i = I_i (R_{S/2} + R_f + R_L) \rightarrow \left\{ \begin{array}{l} V_m \sin \omega t = I_i (R_{S/2} + R_f + R_L) \\ \end{array} \right.$$
$$\downarrow \quad \downarrow$$
$$V_{i_{rms}} = I_{i_{rms}} \left(\frac{R_S}{2} + R_f + R_L \right)$$

$$\text{ac i/p power} = V_{i_{rms}} \cdot I_{i_{rms}}$$
$$= I_{i_{rms}}^2 \left(\frac{R_S}{2} + R_f + R_L \right)$$

$$I_{i_{rms}} = I_{L_{rms}}$$
$$= \frac{I_m}{\sqrt{2}}$$


(\because in series ckt,
same current flows
everywhere)

$$\text{where } I_m = \frac{V_m}{R_L}$$

$$\eta = \frac{I_{dc}^2 R_L}{I_{rms}^2 (R_{S/2} + R_f + R_L)} \times 100\% = \frac{\left(\frac{2 I_m}{\pi} \right)^2 R_L}{\left(\frac{I_m}{\sqrt{2}} \right)^2 \left(\frac{R_S}{2} + R_f + R_L \right)}$$

$$\eta = \left(\frac{8}{\pi^2} \right) \left(\frac{R_L}{R_{S/2} + R_f + R_L} \right) \times 100\%$$

* for HWR $\eta = \frac{I_{dc}^2 R_L}{I_{rms}^2 (R_s + R_f + R_L)} \times 100\%$ $\rightarrow \because$ no centre tapping

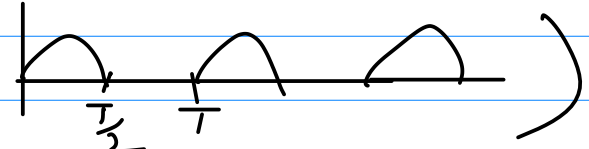$I_{dc} (HWR) = \frac{I_m}{\pi}$ $(\because$ )

$I_{rms} (HWR) = \frac{I_m}{2}$

$\therefore \eta = \frac{\left(\frac{I_m}{\pi}\right)^2 R_L}{\left(\frac{I_m}{2}\right)^2 (R_s + R_f + R_L)} \times 100\%$

$$\eta_{HWR} = \frac{4}{\pi^2} \left(\frac{R_L}{R_s + R_f + R_L} \right) \times 100\%$$


$\eta_{max} (HWR) = \frac{4}{\pi^2} \times 100\% \approx 40.6\%$
 (when $(R_s + R_f) \ll R_L$)

$\eta_{max} (FWR) = \frac{8}{\pi^2} \times 100\% = 81.2\%$

When $\frac{R_s}{2} + R_f \ll R_L$

- * another disad. of CTFWR is PIV

$$|P_1 V| = 2 V_m$$

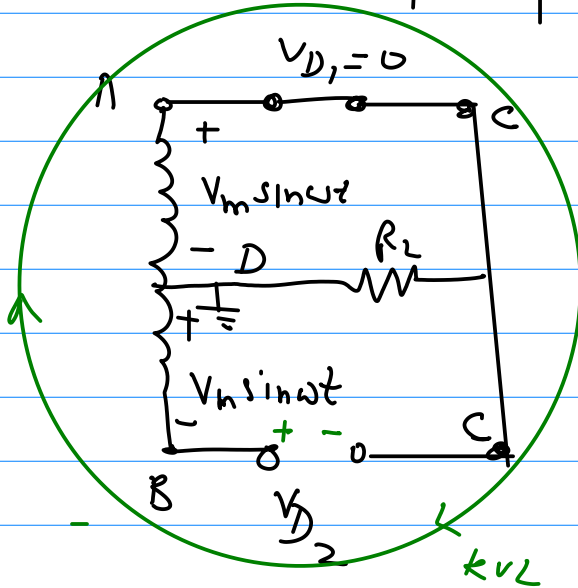

$$V_{D_2} = ? \quad V_{D_2} = V_{BC}$$

KVL-


$$+V_{PB} + V_{AD} + V_{D1} + V_{D2} = 0$$

$$V_m \sin \omega t + V_m \sin \omega t + V_L = 0$$

$$V_{D_2} = -2V_m \sin \omega t$$

$$|V_{p_2}|_{\max} = 2V_m (R, R) = PIV$$

* Transfer charc. -

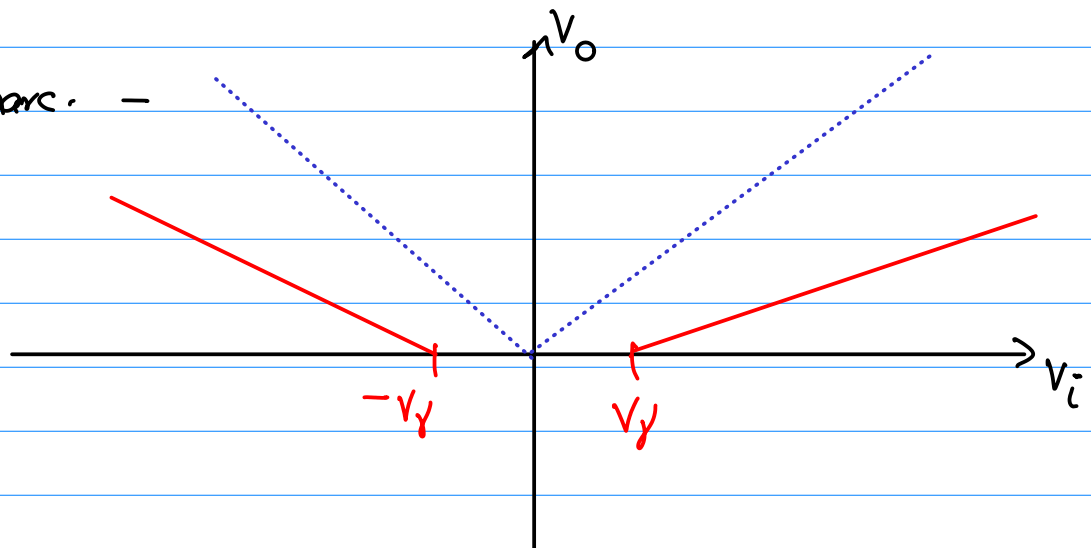

$$* \quad V_{dc} = \frac{2}{\pi} V_m$$

(o/p)

$$* \quad V_{rms} = \frac{V_m}{\sqrt{2}}$$

(o/p)

$$* \quad F = \frac{V_{rms}}{V_{dc}} = \frac{\frac{V_m}{\sqrt{2}}}{\frac{2V_m}{\pi}} \Rightarrow \boxed{F = 1.11}$$

$$* \quad \gamma = \sqrt{F^2 - 1} = \sqrt{1.11^2 - 1} = 0.48$$

(FWR)


$$\gamma_{HWR} = 1.21$$

$\gamma_{FWR} < \gamma_{HWR}$
 \downarrow
 better


$$* \quad \text{Crest factor, } C = \frac{\text{peak}}{V_{rms}} = \frac{V_m}{V_m/\sqrt{2}} = \sqrt{2}$$

(o/p)

2.2) Bridge Rectifier -

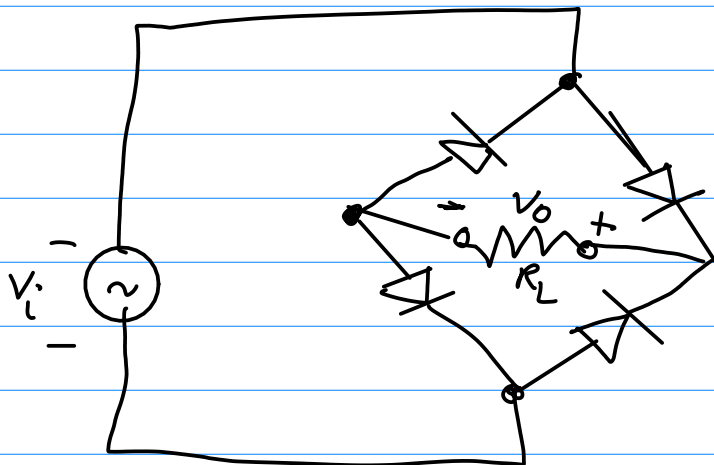

FWR

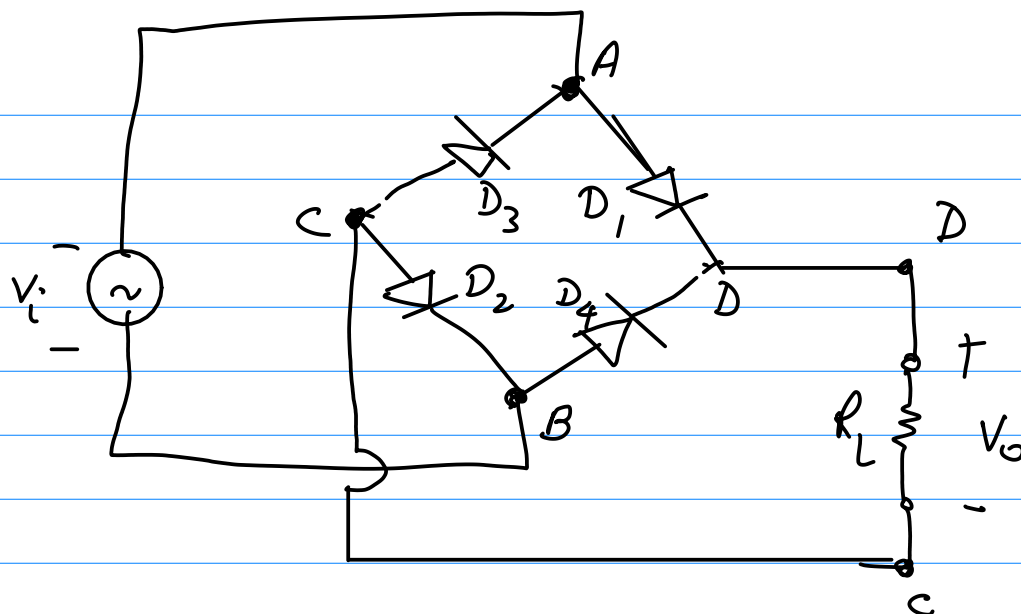

* +ve $\frac{1}{2}$ cycle- $V_i = V_{AB} = +ve$


A \rightarrow highest vol $V_C < V_A$

B \rightarrow lowest vol $V_D > V_B$


$\therefore D_1 \rightarrow F.B$ (on) $\because V_A > V_D$

$D_2 \rightarrow F.B$ (on) $\because V_C > V_B$

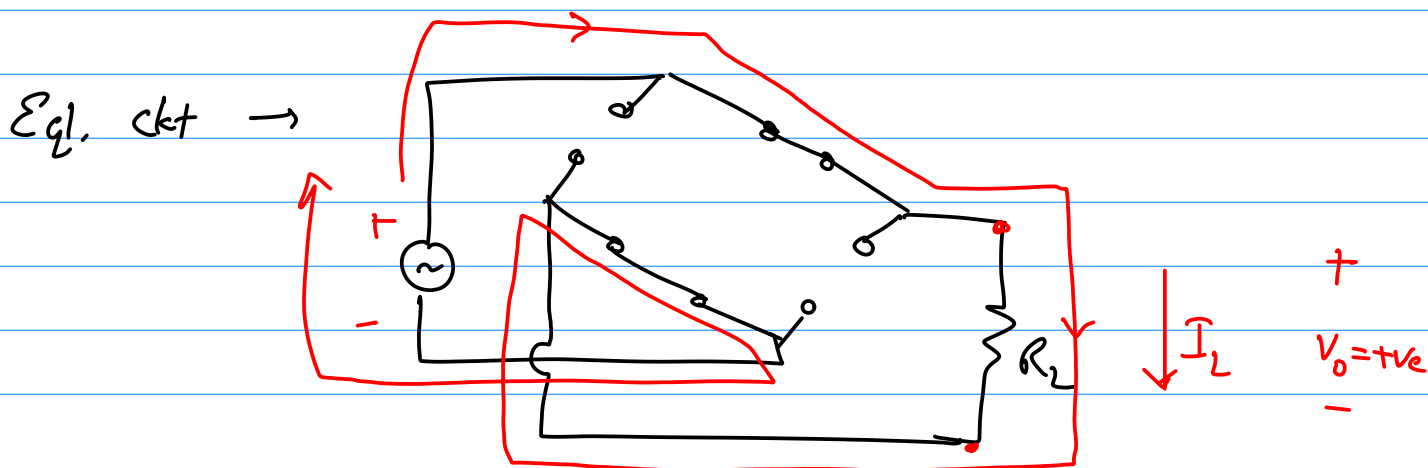$D_3 \& D_4 \rightarrow R.B$ (off) $\because V_C < V_A$
& $V_B < V_D$




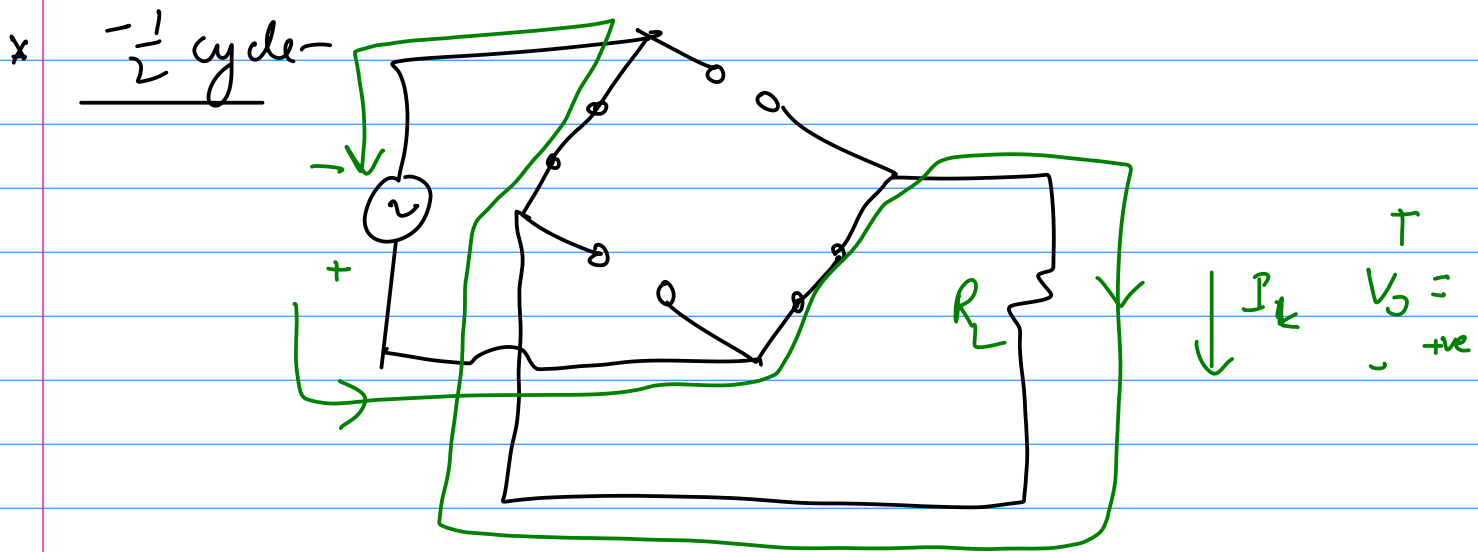
By KVL, $V_o = V_i = V_m \sin \omega t$ (ideal diodes)




$$V_o = -V_i = -V_m \sin \omega t = +ve$$

$$\therefore \frac{T}{2} \leq t < T$$

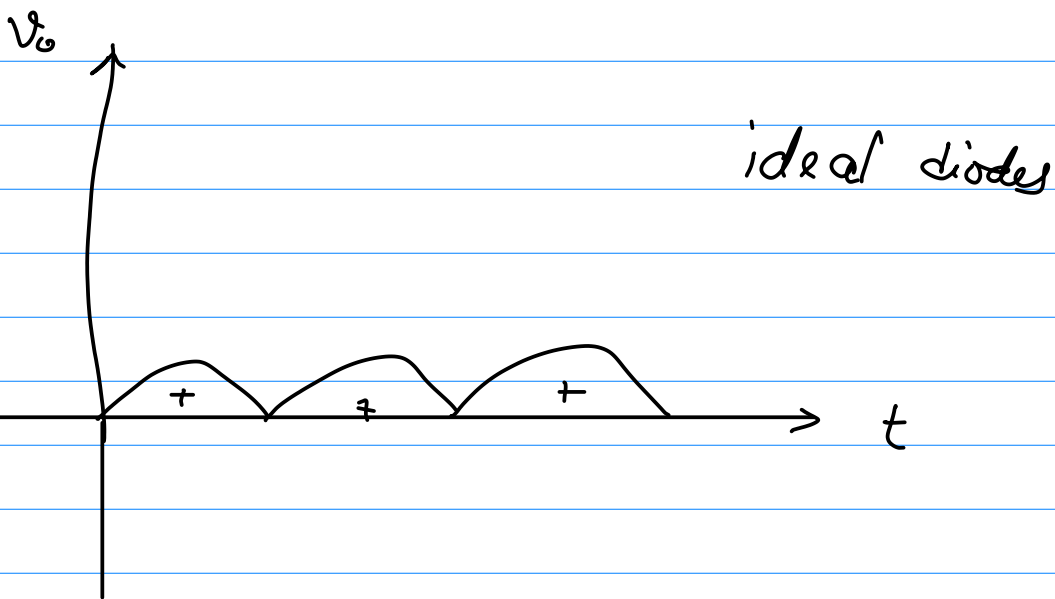

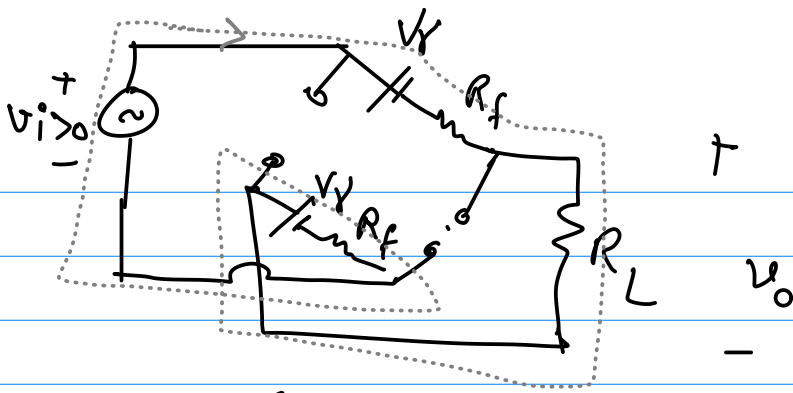
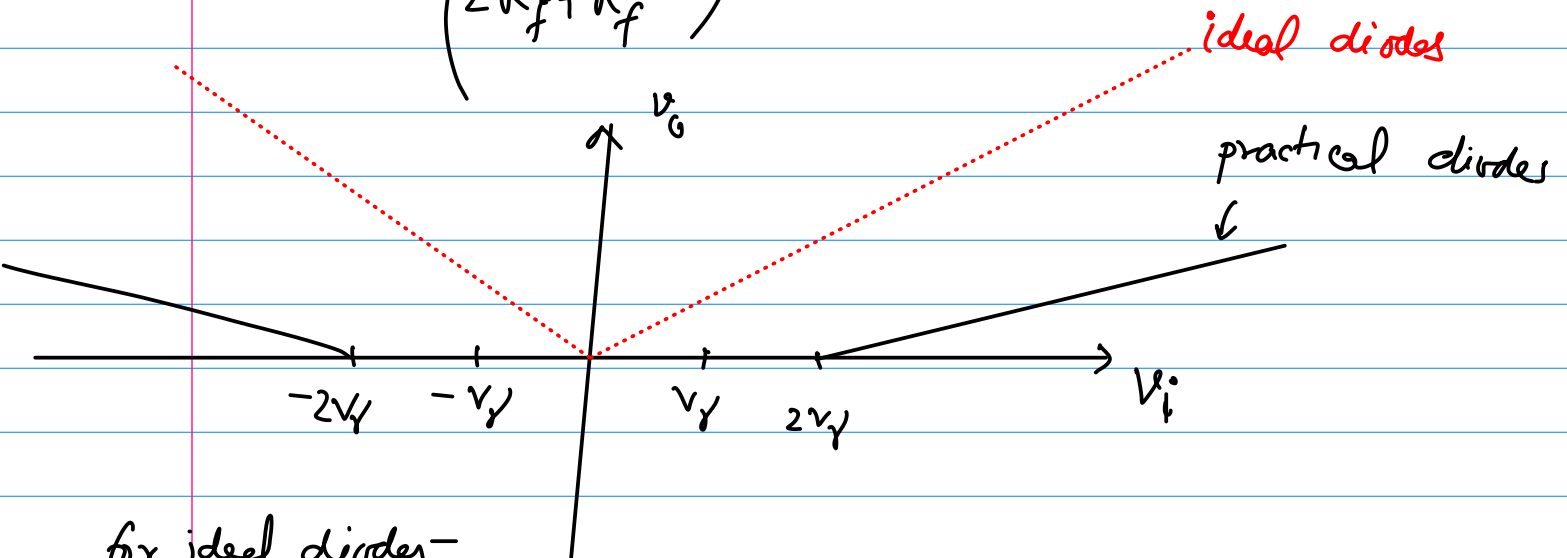
$$v_o = \left(\frac{R_L}{2R_f + R_L} \right) (v_i - 2V_f)$$



for ideal diodes-

$$* \quad V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$* \quad V_{dc} = \frac{2V_m}{\pi}$$


$$* \quad F = \frac{rms}{dc} = \frac{\pi}{2\sqrt{2}}$$

$$* \quad r = \sqrt{F^2 - 1} \approx 0.48$$

$$* \quad \text{Efficiency} = \eta = 0.806 \times \left(\frac{R_L}{2R_f + R_L} \right) \times 100\%$$

$$\eta_{max} = 80.6\% \quad \text{when} \quad 2R_f \ll R_L$$

* PIV \rightarrow

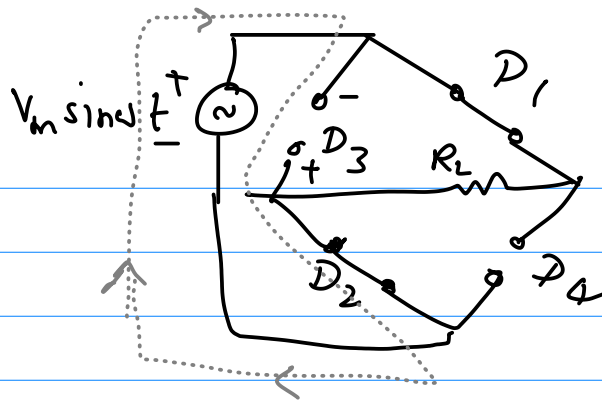

KVL -

$$+V_m \sin \omega t + V_{D3} = 0$$

$$\text{So, } V_{D3} = -V_m \sin \omega t \quad \left(\text{where } \sin \omega t = +ve \right)$$


$$\therefore +\frac{1}{2} \text{ cycle}$$

$$\text{So } |V_{D3}|_{\text{max}} = V_m$$

(R.B.)

$$\boxed{PIV = V_m}$$

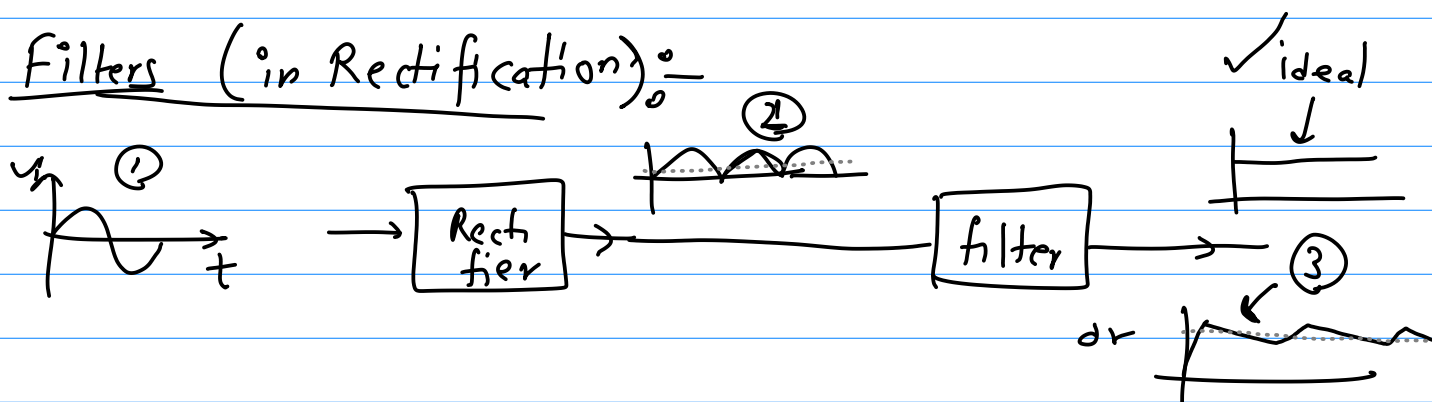\rightarrow Filters (in Rectification) :-




Compare (2) & (3)

$$V_{dc(3)} > V_{dc(2)}$$

$$r_{(3)} < r_{(2)}$$

filtering reduces the ripple factor (So makes pure dc ideally)

Inductor -
 L

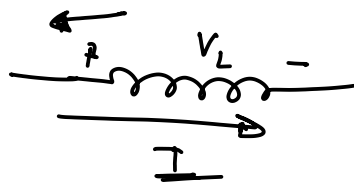


$$V_L = L \frac{dI}{dt}$$

Ohm's law for
inductor


- * Inductor opposes change in current flowing through it.
- * $V_L = L \frac{dI}{dt}$ if I is constant with time (steady state, dc source), then $\frac{dI}{dt} = 0$
So, $V_L = 0$ i.e., inductor behaves as a short ckt for dc sources under steady state.
- * Inductor does not allow sudden change in current. [if there is any resistance in series]
sudden change - $dt \rightarrow 0$, $dI \rightarrow$ finite non zero
 $L \frac{dI}{dt} \rightarrow \frac{\text{finite}}{0} \rightarrow \infty$ So, $V_L \rightarrow \infty$ (impossible)
- * Inductor acts as short ckt (r.v. low vol. drop (V_L)) for low frequency input sources (e.g. dc) in steady state

* Inductor can be assumed to be open ckt for ω high frequencies.

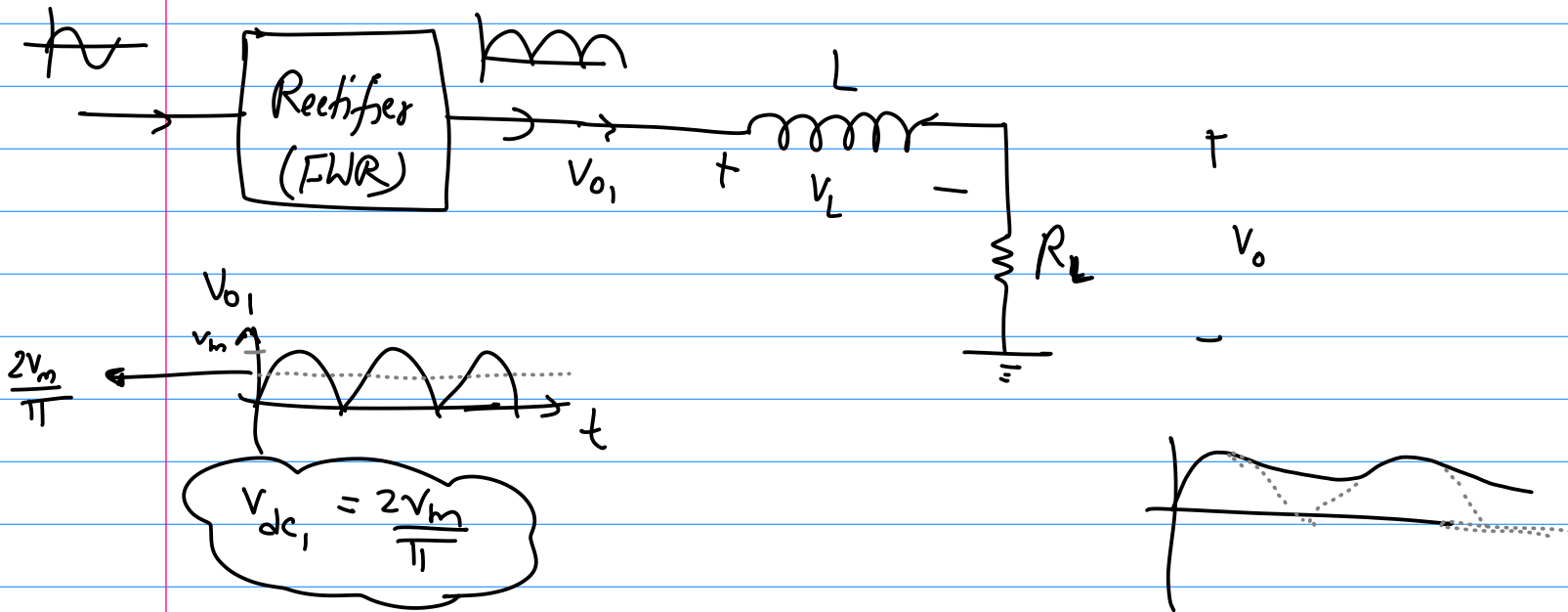* So, inductor passes low frequencies (like dc) & blocks high frequency signals (like ac).



→ Capacitor -

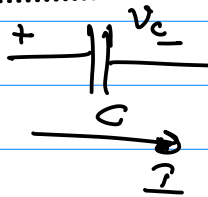

$$I = C \frac{dV_c}{dt}$$




Ohm's law for Cap

* Cap. opposes change in vol. across it -

* Cap. does not allow sudden change in vol. across it

$\therefore \frac{dV_c}{dt} \rightarrow \infty \Rightarrow I = \infty$

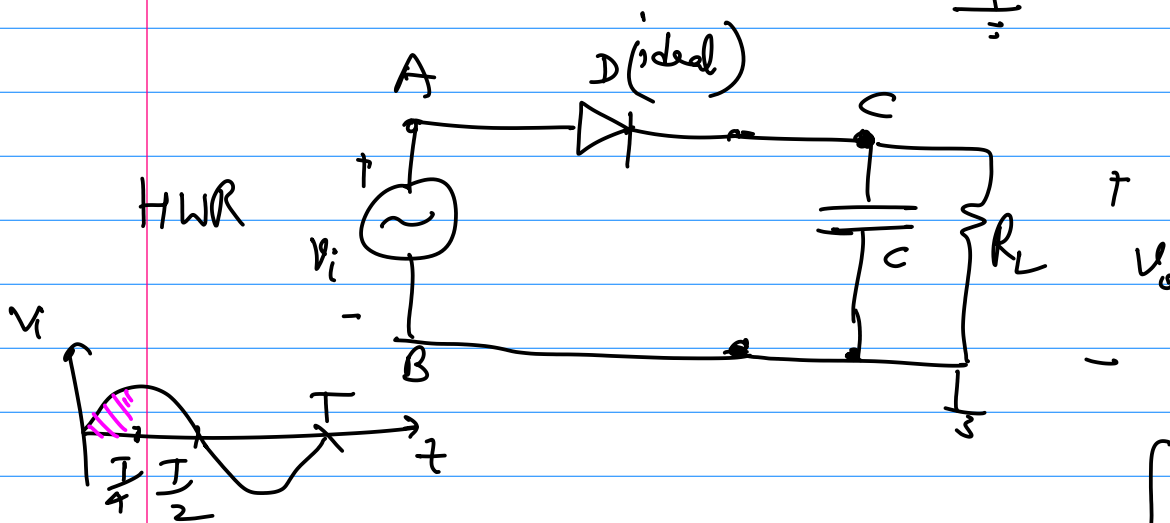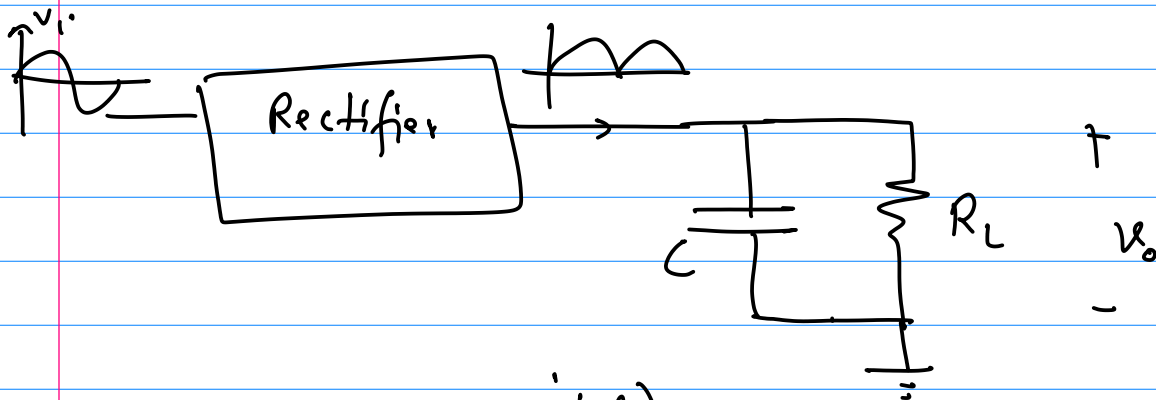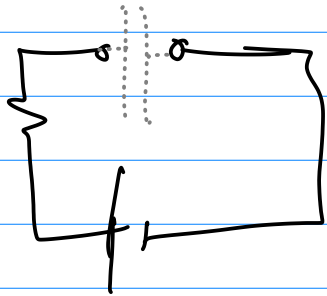
- * ∞ current is needed to change V_C suddenly.
- * V_C can change suddenly only if there is no series resistance in the ckt.
- * Cap. acts as O.C. for low freq. (like dc) in steady state & S.C. for v. high freq.



$$[V_C = 0 \text{ at } t=0]$$


for $0 < t < \frac{T}{4}$ \rightarrow D is 'ON'

$$\therefore V_A = +V_C, \quad V_C = 0$$

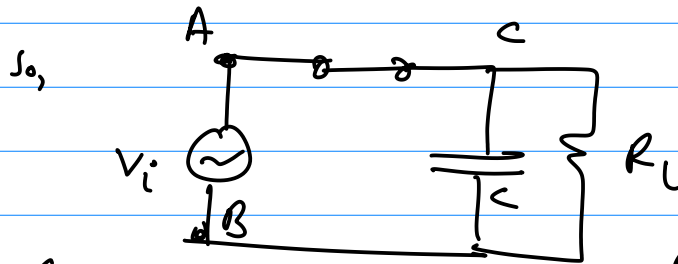

(by KVL)


$$V_C = V_i = V_0$$

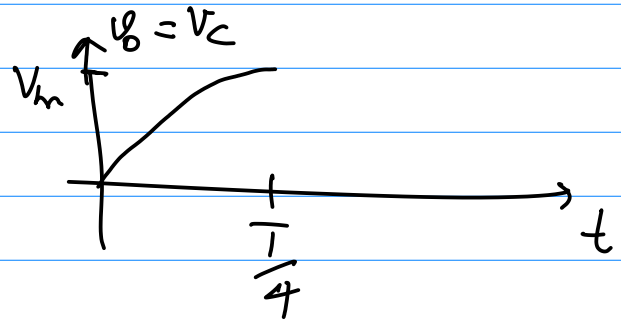


(ii) for $\frac{T}{4} < t < \frac{T}{2} \rightarrow$

$$\text{at } t = \frac{T}{4} \Rightarrow V_C = V_m$$


but $V_i < V_m$ for $t > \frac{T}{4}$

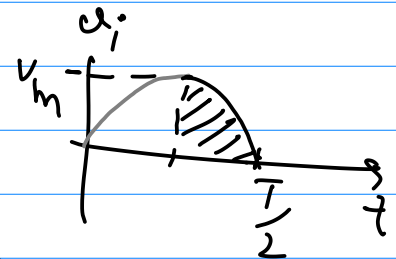

$$S_0, \quad V_A < V_C$$

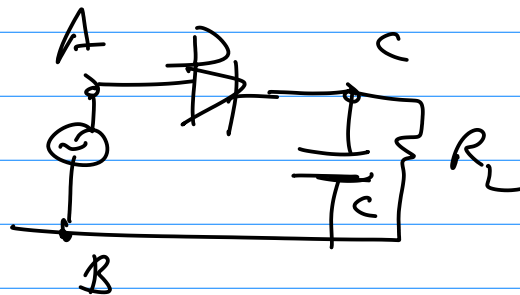

$S_0, \quad D = \text{off}$

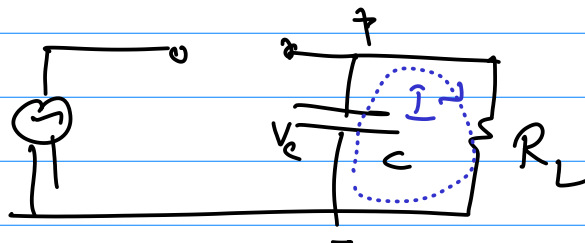

$$V_C = V_m \quad \left(\text{at } t = \frac{T}{4} \right)$$


$$v_o = v_c$$

$$\Delta \quad I = -C \frac{dv_o}{dt}$$


also, $IR_L = v_o$

$$\frac{v_o}{R_L} = -C \frac{dv_o}{dt}$$

$$v_o = v_m e^{-t/CR_L}$$

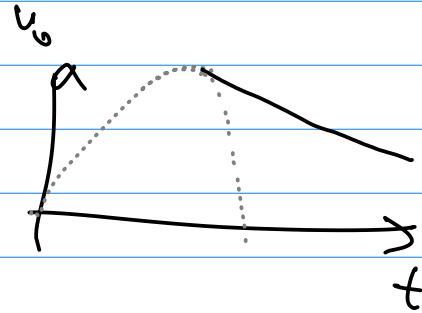

* Time constant -

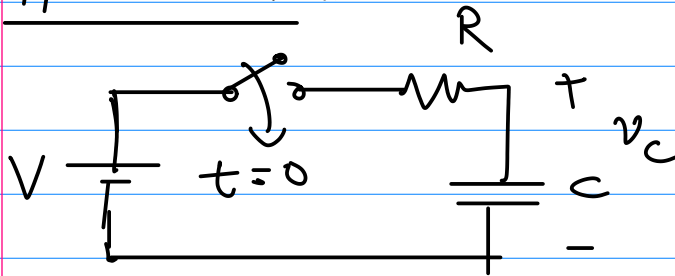

Capacitor charging

for $t > 0$ -

$$V - IR - v_c = 0$$


$$I = C \frac{dv_c}{dt}$$

$$V - CR \frac{dv_c}{dt} - v_c = 0$$

$$\boxed{\frac{dv_c}{dt} + \frac{v_c}{RC} = \frac{V}{RC}}$$

Solution -

$$v_c(t) = V(1 - e^{-t/RC})$$

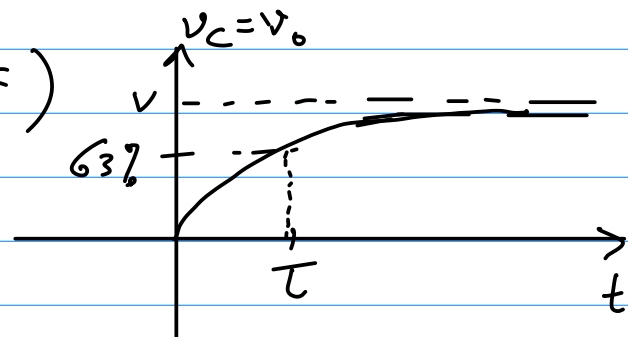

τ (or time constant) is the time where rising o/p reaches $\sim 63\%$ of max value

$$e^{-t/\tau}$$

$$\tau = RC$$


at $t = 2\tau$, $V_c = ?$

$t = 3\tau$, $V_c = ?$ (95% of V)

$t = 4\tau$ $V_c \approx 98\%$ of V

$t = 5\tau$ $V_c > 99\%$ of V

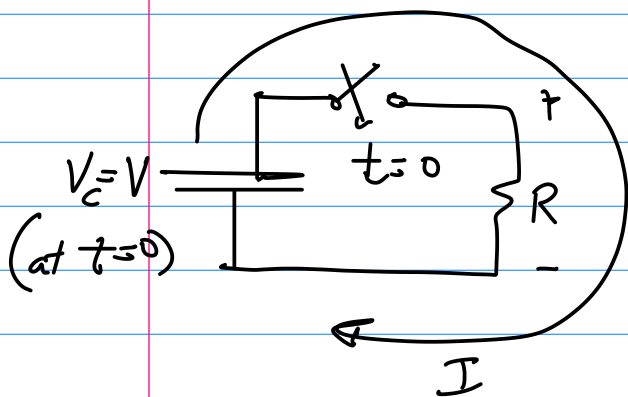
steady state \rightarrow o/p doesn't change
(if i/p is constant)



$$C \frac{dV_c}{dt} \cdot R = V_c$$

$$V_c(t) = V e^{-t/RC} = V e^{-t/\tau}$$

$$\tau = RC$$

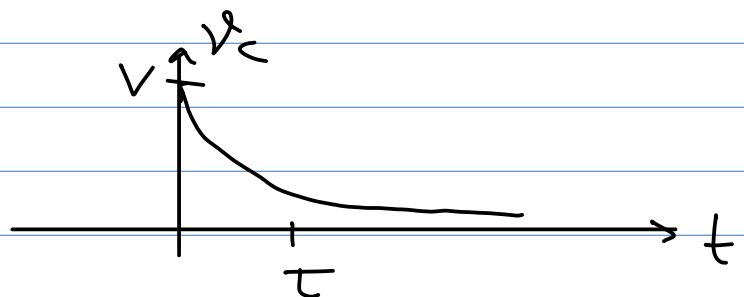


at $t = \tau$, $V_c = V_0 \approx 37\%$ of V

* if τ is large, C takes a long time to change its vol.

* If τ is small, V_C changes quickly

for HWR with C-filter —

(1) during $+\frac{1}{2}$ cycle,

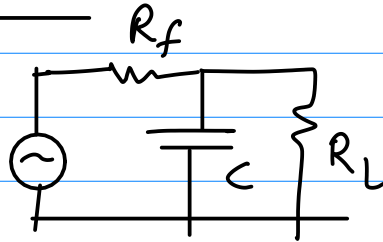


How to find τ ?

- (i) - Replace all ideal vol sources by S.C.
- & all ideal current sources by O.C.

(Replace any source by its internal resistance)

- (ii) Across the 2 nodes of concern, find Equivalent resistance R_{eq} & C_{eq}

(iii) $\tau = R_{eq} \cdot C_{eq}$

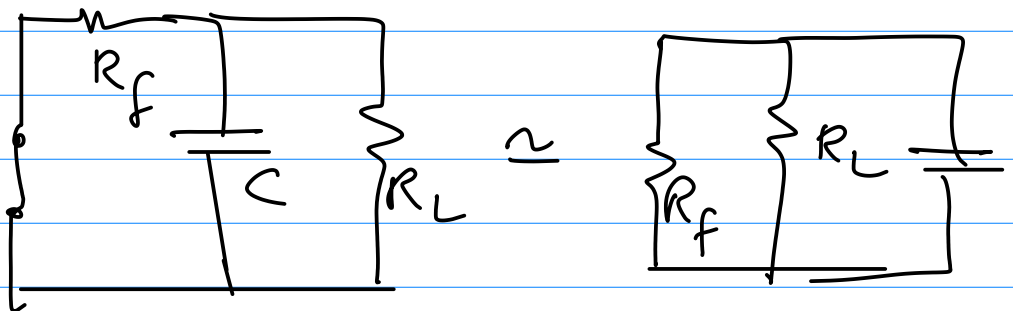

$$R_{eq} = R_f \parallel R_L \approx R_f \quad \because R_f \ll R_L$$

$$C_{eq} = C$$

$$T = R_f C \quad = \text{v.v. small}$$

$$\therefore R_f \rightarrow 0$$


So, during $0 < t < T/4$, cap charges

to follow v_i v. quickly

$$\text{by KVL } v_c = v_i - v_D \approx v_i$$

$$\therefore v_D = 0 \text{ (ON)}$$

for $t > T/4$ - D = off

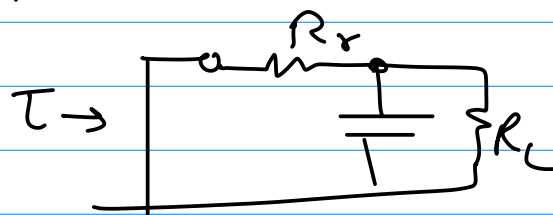

$$R_{eq} = R_r \parallel R_L$$

$$\approx R_L$$

$$\therefore R_r \gg R_L$$

$$C_{eq} = C$$


$$\tau = R_L C$$

→ can be designed so that

$$R_L C > T$$

time period of i/p

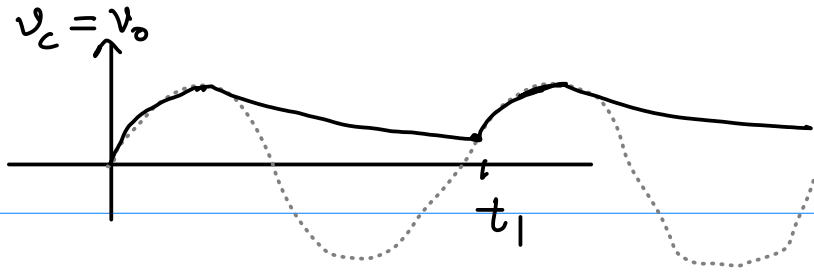
The Cap discharges through R_L 'slowly' as compared to T .




at $t = t_1^+$, $v_i > v_c$

s.o., $D \rightarrow 0$, $\tau \Rightarrow R_L C \approx 0$


s.o. cap follows v_i
again (quickly)

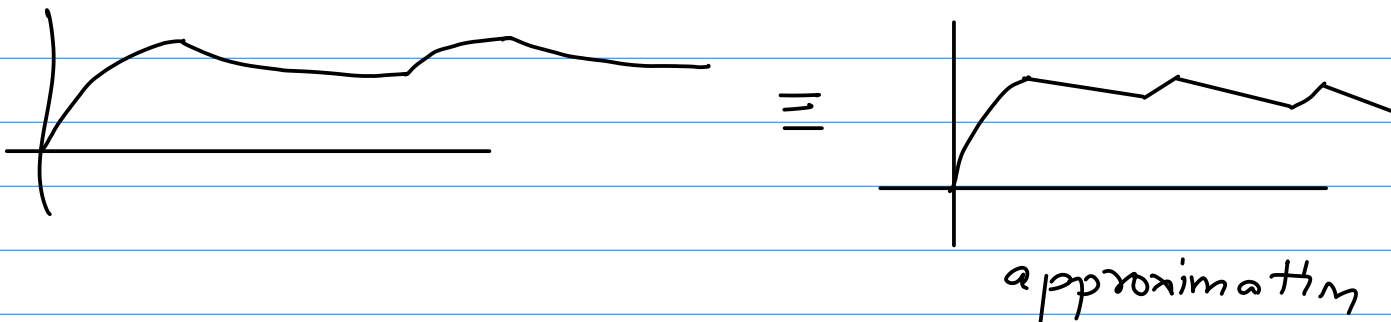

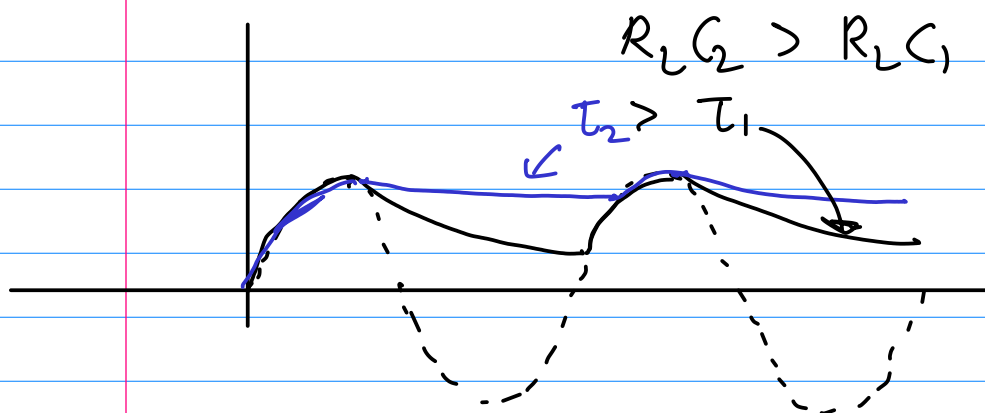
if $\tau \uparrow$ ($R_L C$) then discharge time \uparrow




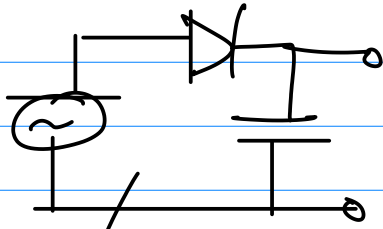
$R_L C \rightarrow \infty$ (by using $R_L = \infty$) or O.C.



Cap never discharges

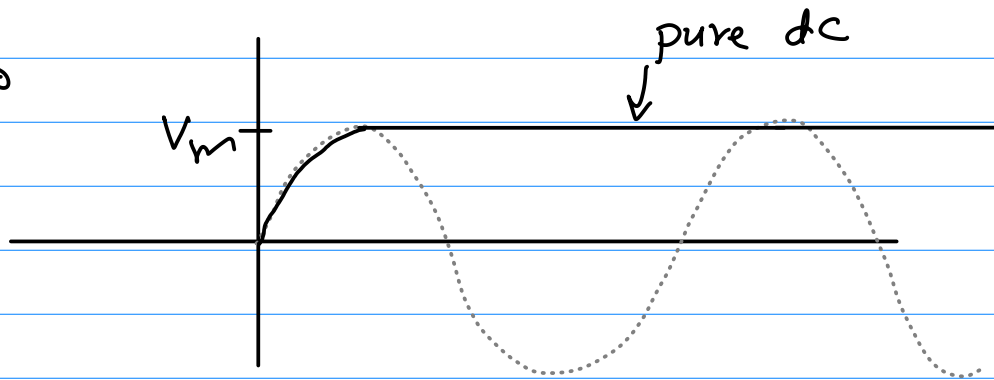

"Peak Detector ckt"

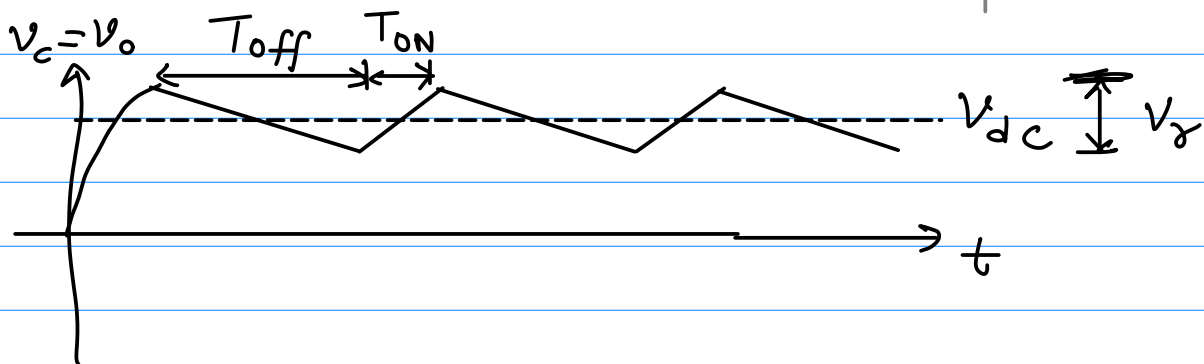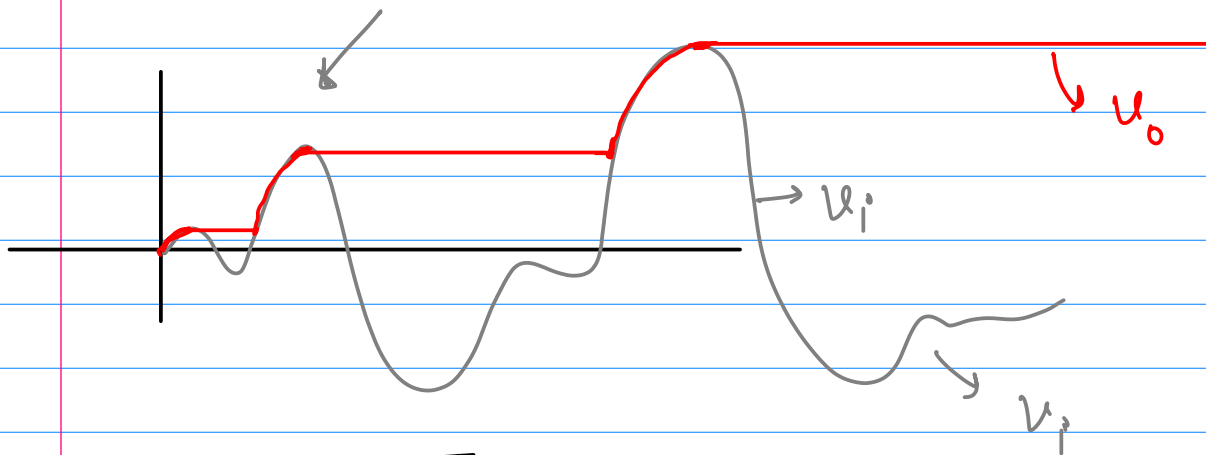

$$V_o = V_{dc} + V_r$$

↓
ac part


$T_{off} \rightarrow D \text{ off}$

$T_{on} \Rightarrow D = \text{on}$

$$T_{\text{off}} + T_{\text{on}} = T = \frac{1}{f} \quad (\text{time period of i/p})$$

\searrow '1/p freq.

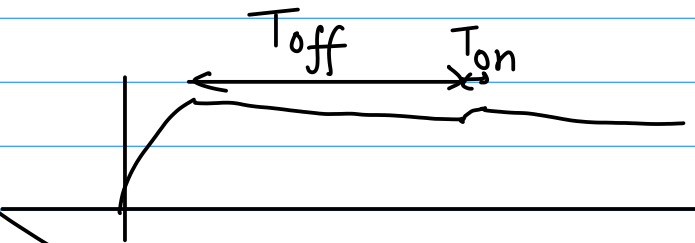if $R_L C \gg T$ the cap almost never discharges
(v. little discharge)



$$\rightarrow T_{\text{off}} \gg T_{\text{on}} \quad \text{So,}$$

$$T_{\text{off}} \approx T$$

$$V_r = \Delta V_o = \text{change in o/p vol.}$$

$$Q = CV \quad \text{or} \quad \boxed{\Delta Q = C \Delta V}$$

$$\Delta Q = \frac{I_{dc}}{f} \quad \& \quad \Delta V = V_r$$

$$\text{So,} \quad \boxed{V_r \approx \frac{I_{dc}}{fC}}$$

*

approximation



Now

$$\boxed{V_{dc} \approx V_m - \frac{V_r}{2}}$$

for HWR with C-filter

$$\gamma \propto \frac{1}{R_L C}$$

for FNR with C-filter-

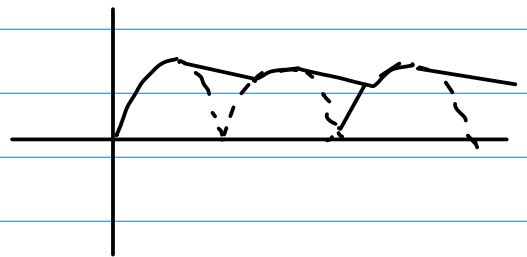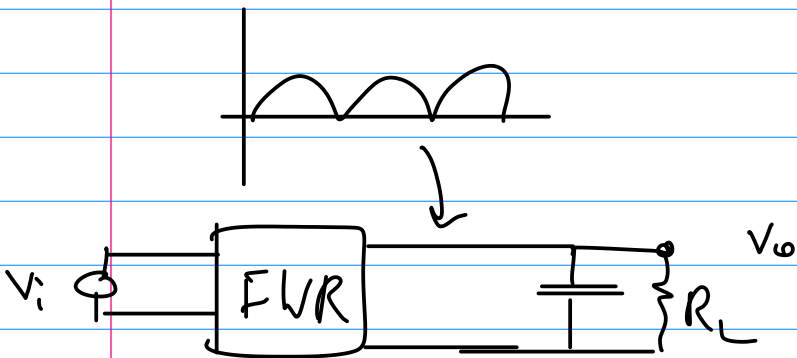

$$V_r = \frac{I_{dc}}{2fC}$$

$\left[\begin{array}{l} 2f \therefore \text{FWR o/p} \\ \text{has a freq } 2f \end{array} \right]$

$$\gamma = \frac{1}{4\sqrt{3} f R_L C}$$




C - filter		
HWR	Centre tapped	Bridge
$PIV = 2V_m$ (gets bad) (HW)	$PIV = 2V_m$ (same)	$PIV = V_m$ ✓ (same)

HW →

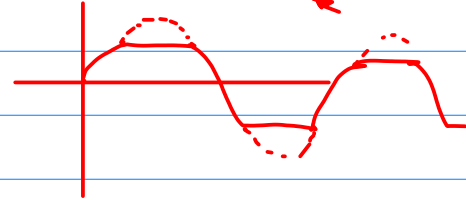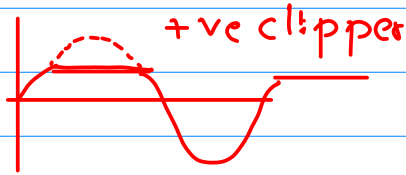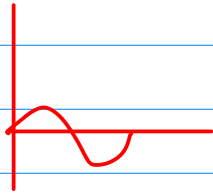1) Clipper dcts

KVL & Ohm's law


series — $\begin{cases} +ve \\ -ve \end{cases}$
shunt — $\begin{cases} +ve \\ -ve \end{cases}$
2 level clipper



2) Zener diode vol. regulators

Problem from "Sedra & Smith"


→ Clamper

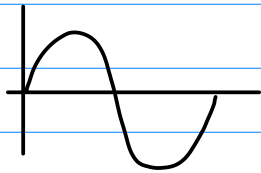

→


Clamper

→

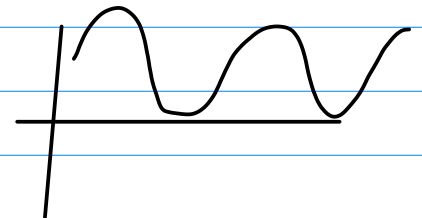


or

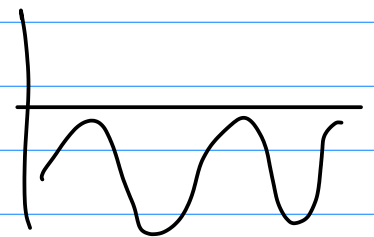$\left\{ \begin{array}{l} * \text{ Adds or subtracts} \\ \text{a dc vol from i/p} \end{array} \right\}$



1) -ve clamper

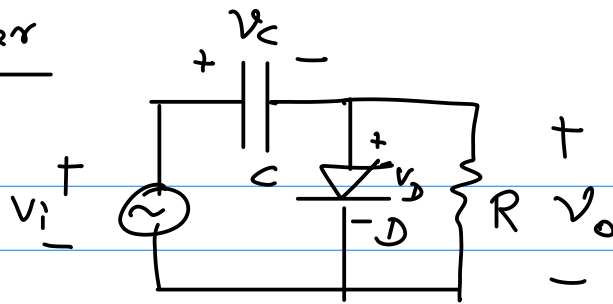


$$v_c(t=0) = 0$$

$+\frac{1}{2}$ cycle -

$$v_i - v_c = v_D = v_o \quad (\text{KVL})$$
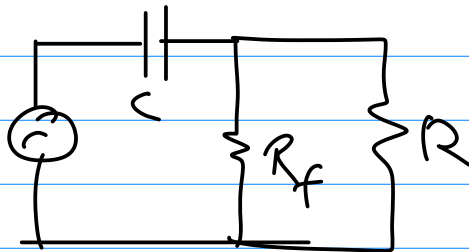
$$v_i = v_D = +ve \quad \underline{D = ON}$$



$$(V_{cut-in} = 0)$$

time constant



$$\tau = R_f C$$

$$\therefore R_f \ll R$$

small τ so, cap charges quickly to follow v_i

$$\therefore v_D \approx 0 \quad (\text{s.c. } D = ON)$$
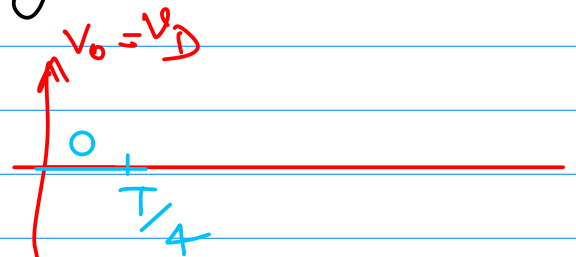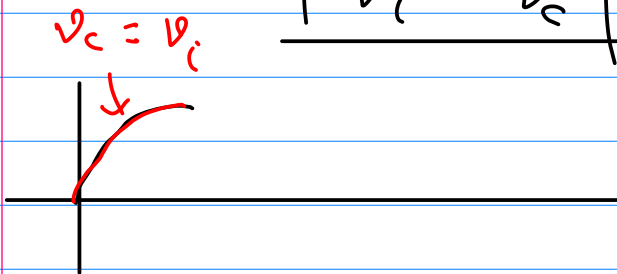
$$\boxed{v_i = v_c} \quad (\text{by KVL})$$



for $t > \frac{T}{4} \rightarrow$

at $t = \frac{T}{4}, \boxed{V_c = V_i = V_m}$

for $t > \frac{T}{4}$ (or $t = \frac{T}{4} +$),


$$V_i < V_m$$

$$V_o = V_i - V_c \quad (\text{from KVL})$$

$$= -V_c$$

$$D = R \cdot B. \quad = \text{off}$$

So, $\tau = RC$

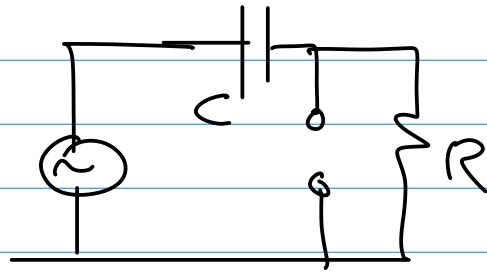

Let $RC \gg T$

then C doesn't discharge

$$V_c = V_m \quad (\text{constant})$$

$$V_o = V_o = V_i - V_c$$

$$\boxed{V_o = V_i - V_m}$$


If $V_i = 0$ $V_o = -V_m$

If $V_i = -V_m$ $V_o = -V_m - V_m = -2V_m$


If $V_i = +V_m$, $V_o = V_m - V_m = 0$

} Diode vol

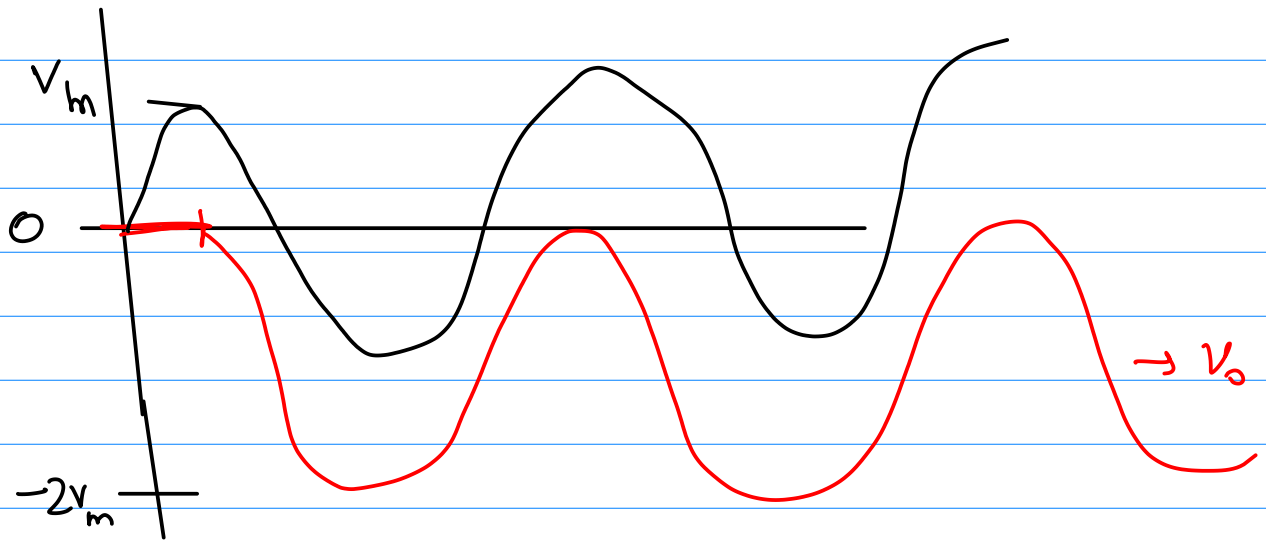" (for $t > \frac{T}{4}$, Diode Never turns ON again)



(11) +ve clamper -

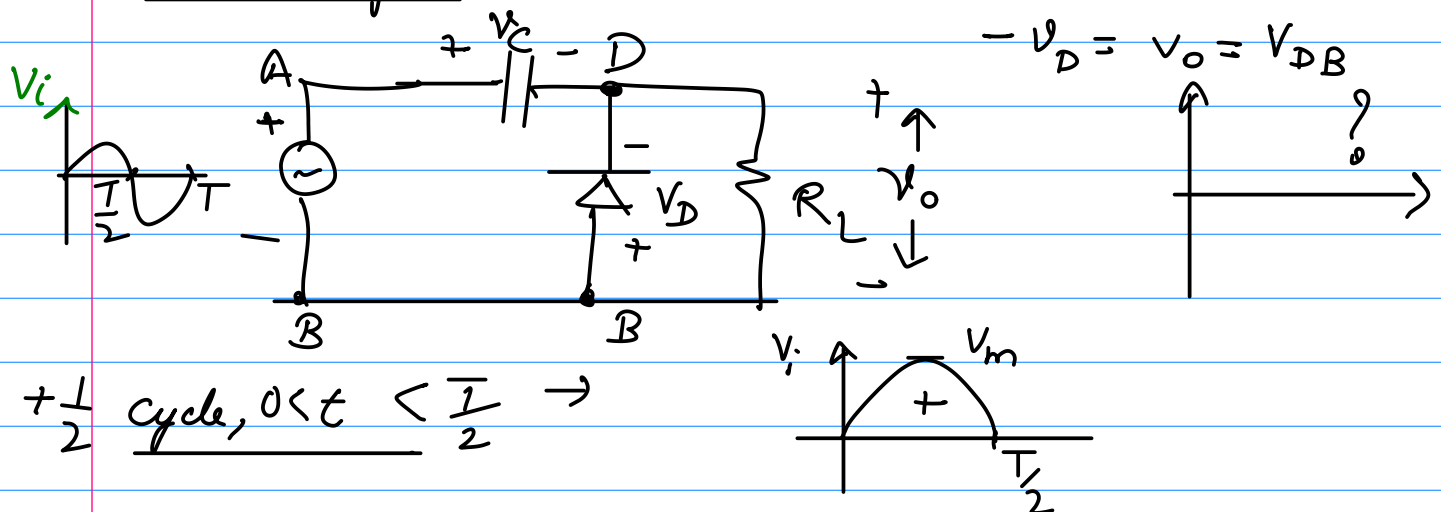

$+\frac{1}{2}$ cycle, $0 < t < \frac{T}{2} \rightarrow$

Assumption -


$V_c(t=0) = 0 = V_{AD}$

$$+v_i - \cancel{V_c} + v_D = 0$$

(+ve) (initially, $t=0$)


$$\Rightarrow v_D = -v_i = -ve$$

R.B. ($t \sim 0^+$)

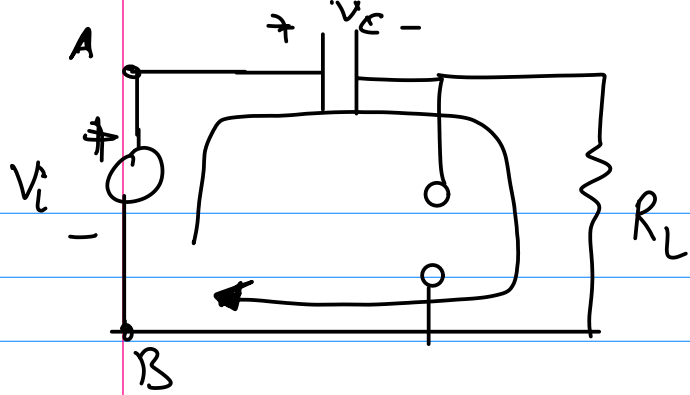

$V_B = \text{lowest pot in the ckt}$
 $(+\frac{1}{2} \text{ cycle})$

$$\tau = R_L C$$

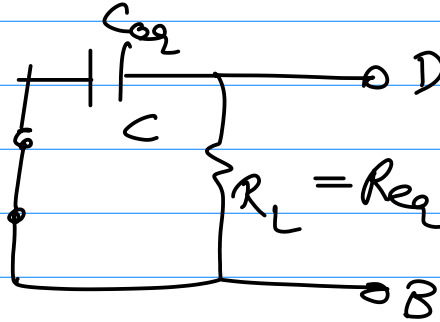

if $R_L C \gg T$ (which usually is the case)



So, cap. charges v.v. slowly as comp. to 'T'.

So, during $+\frac{1}{2}$ cycle, we can assume that

C doesn't change, $V_C = 0$ ($0 \leq t \leq \frac{T}{2}$)


By KVL $\rightarrow V_i - V_C - V_o = 0$
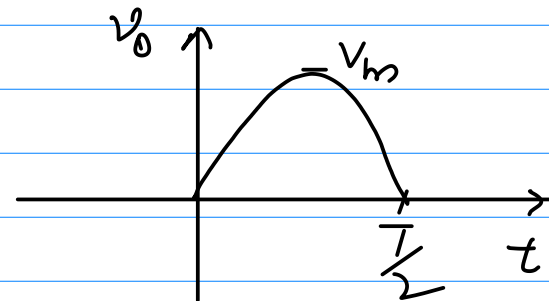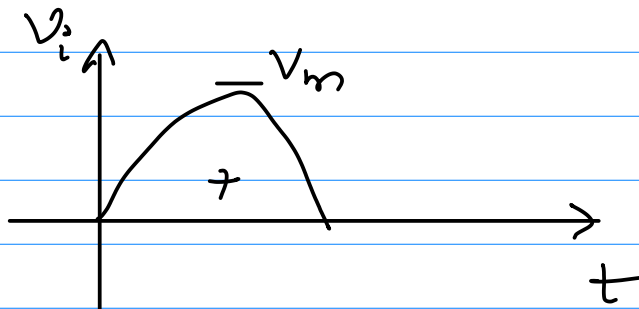
$$\Rightarrow V_o = V_i \quad (\text{for } 0 \leq t \leq \frac{T}{2})$$



$\left\{ \begin{array}{l} \star \text{ Diode} = R.B. \\ \star C = \text{doesn't change} \end{array} \right\}$

$-\frac{1}{2}$ cycle -

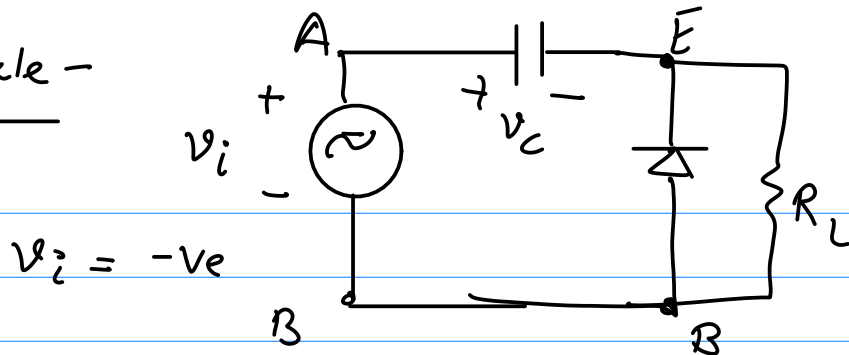

$\therefore v_c \approx 0$; v_i is the only source
(at $t = \frac{T}{2}$)

$V_B =$ highest pot. in the ckt
($\because v_i = -ve$)

by KVL, $V_A - \cancel{V_D} = V_E$ at $t = \frac{T}{2}$
 ~ 0

$$V_E \approx V_A$$


$$V_D = V_B - V_E = V_B - V_A$$

$$\approx -v_i$$


$$\approx (+ve)$$

So, $D = F.B.$

for $t > \frac{T}{2} \rightarrow$

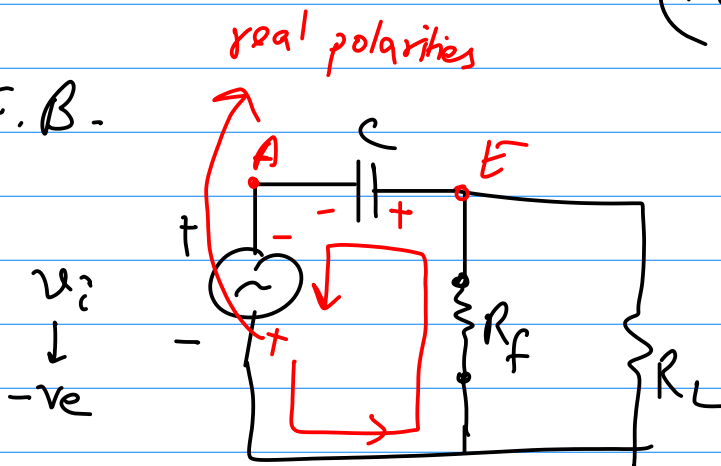

time constant \rightarrow

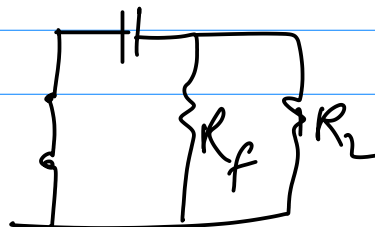


$$R_{eq} = R_f \parallel R_L$$

Since $R_f \ll R_L$ so, $R_f \parallel R_L \approx R_f$

so, $\tau(t > T) \approx R_f C = \text{v.v. small}$

so, C charges quickly

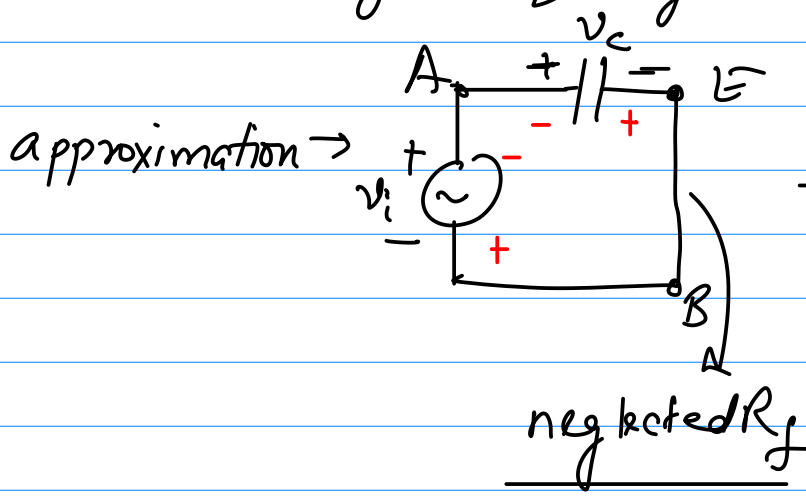


Red = Real polarity

KVL $\rightarrow v_i - v_c = 0$
 $\Rightarrow v_c \approx v_i = -v_e$


$v_{EB} = v_o \approx 0$ (for $\frac{T}{2} < t < \frac{3T}{4}$)

at $t = \frac{3T}{4}$; $v_i = -V_m = v_c$

$v_o = 0$

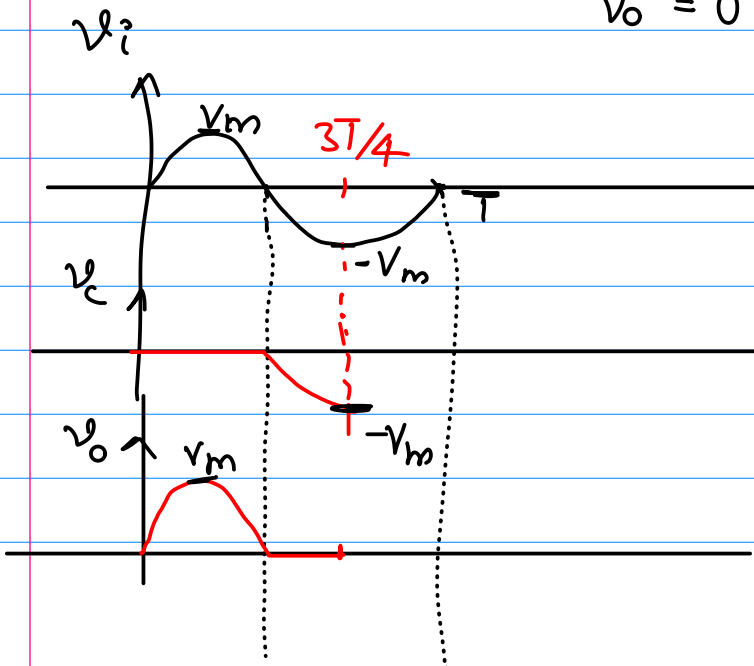

for $t = \frac{3T}{4}$

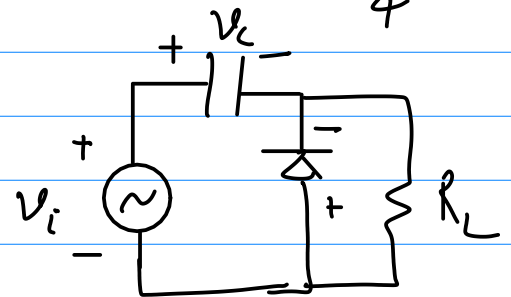

$v_i - v_c + v_D = 0 \Rightarrow v_D = v_c - v_i$
 $v_c = -V_m \mid v_i < V_m$
 $v_i > -V_m$

$$v_D = \overset{\downarrow}{(-v_m)} - \underset{\downarrow}{v_i} = -ve \Rightarrow \underline{\underline{D = R.B}}$$


$v_i > -v_m$

Since KVL is valid always,

& $v_i \geq -v_m$ always


$$T = \underline{R_L C} = \underline{v \cdot high}$$

(cap vol. doesn't change)

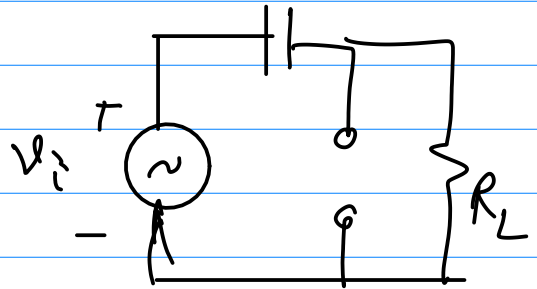

So, D stays R.B. forever

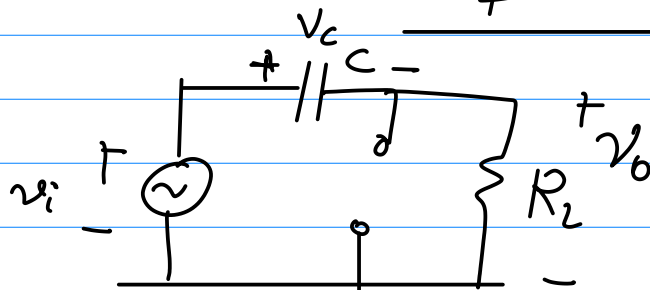So, for $t > \frac{3T}{4}$ & $t < \infty \rightarrow$



$$R_L C \gg T$$

$$\text{So, } v_c = -v_m \text{ (always)}$$



$$\& \quad v_o = v_i - v_c \quad (\text{by KVL})$$

$$v_o = v_i - (-v_m)$$

$$\Rightarrow \underline{v_o = v_i + v_m}^*$$

$$\text{for } \frac{3T}{4} < t < \infty$$


Shiram 42

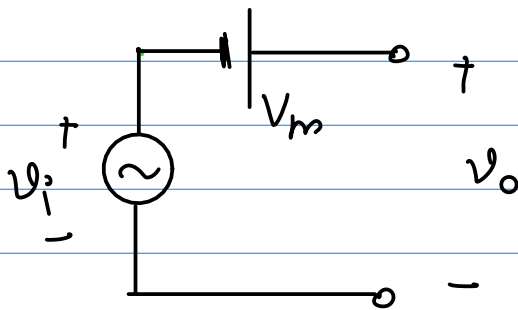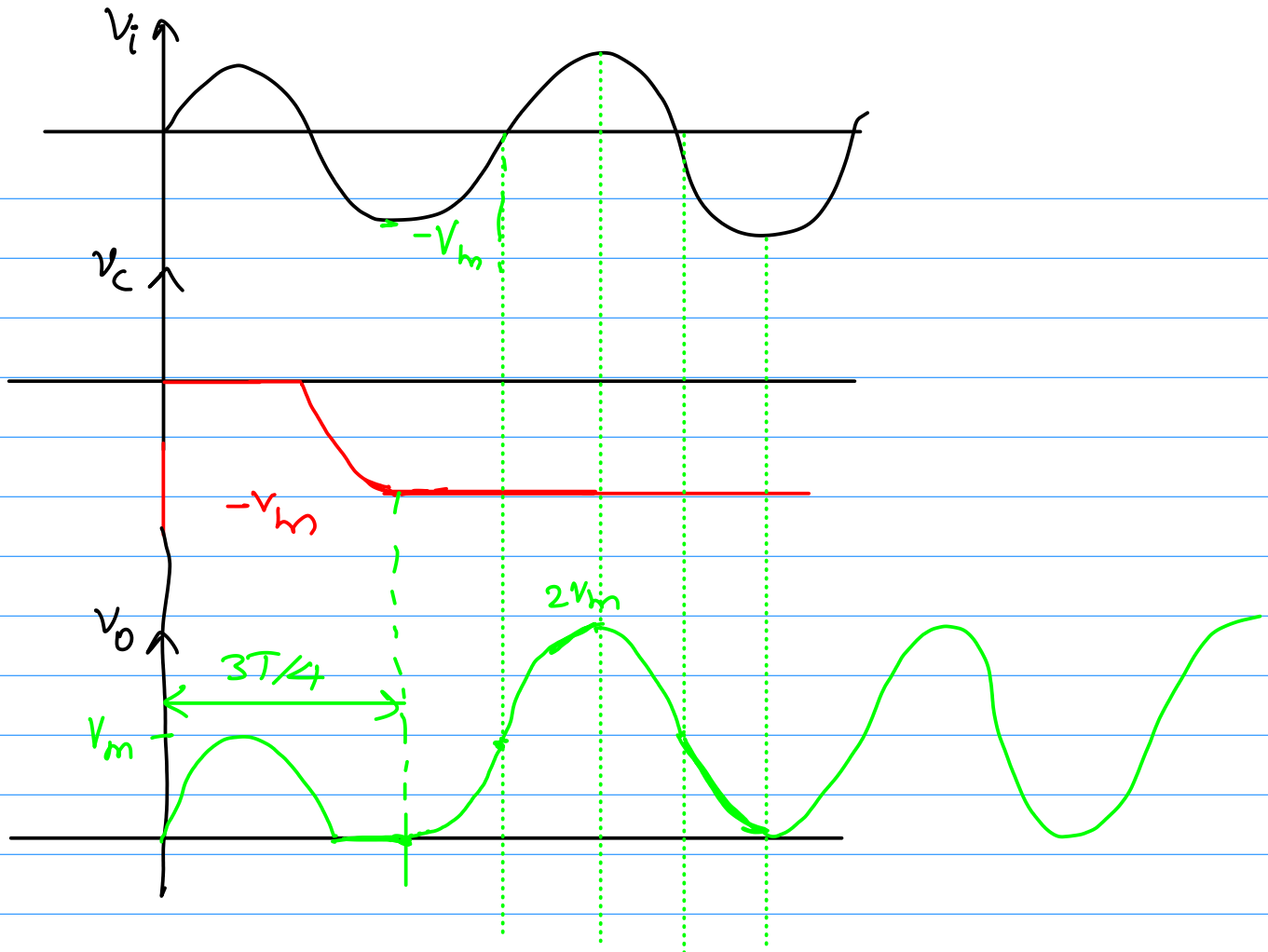

KVL \rightarrow


$$v_i + V_m - v_o = 0$$

$$\Rightarrow \boxed{v_o = v_i + V_m}$$

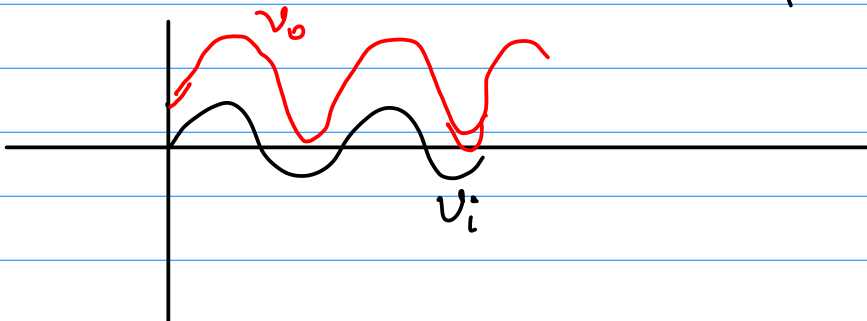

tips - (Diode ckt)

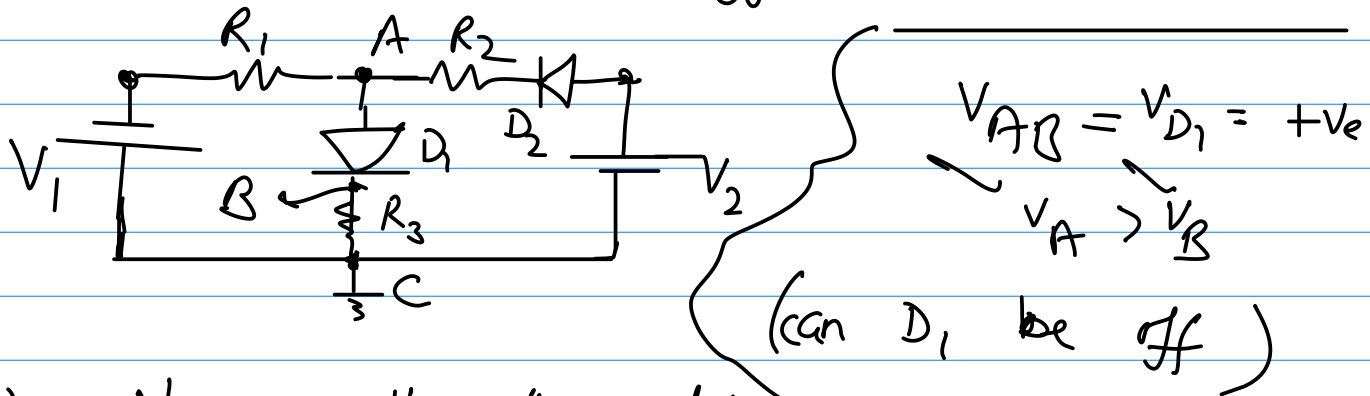(i) When in doubt, Assume all diodes to be off (R.B.)



(ii) Name all the nodes



(iii) ^{use} KVL \rightarrow to find Diode vol.

'If $V_{D1} = +ve \rightarrow D_1$ assumption wrong
(D_1 is ON)

$V_{D2} = -ve \rightarrow D_2$ assumption is
right ($D_2 \rightarrow$ off)

(iv) finally re-analyse the ckt (again find all the vol.) now with the correct diode states (on or off)

Bipolar Junction transistor

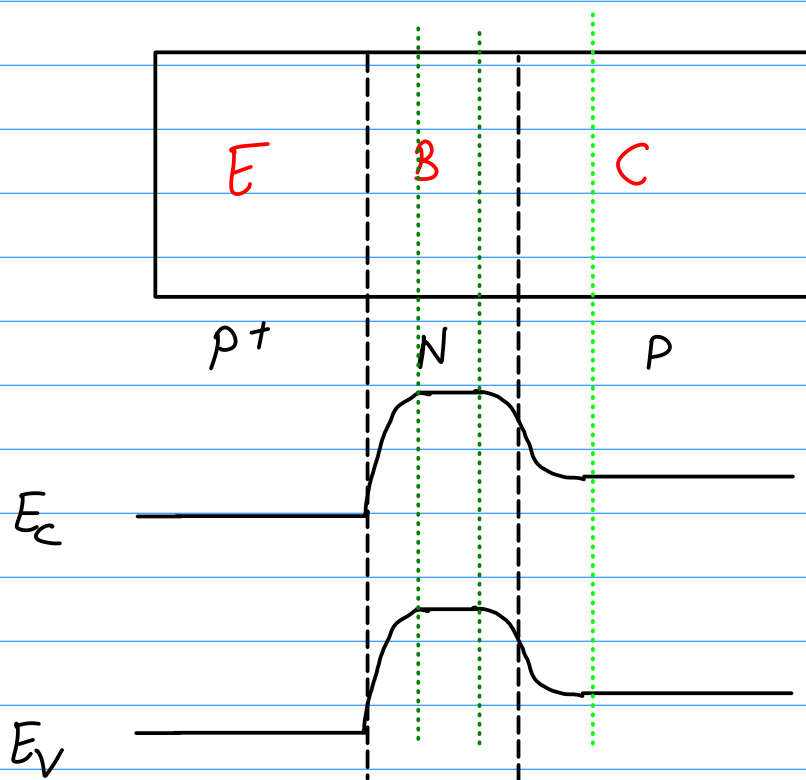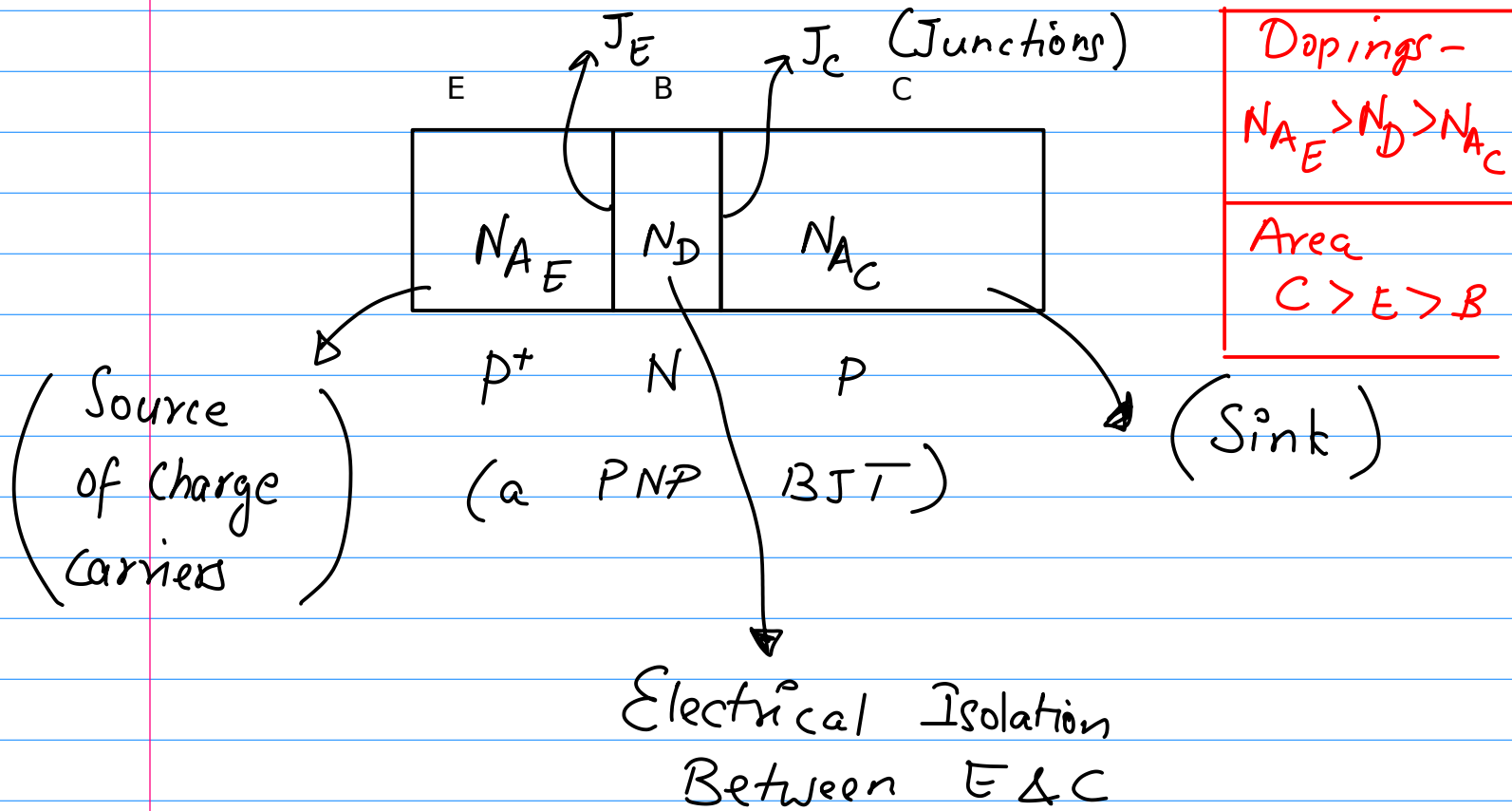

MODES OF OPERATION

	Mode	J_E	J_C	APPLICATION
1)	Forward Active	F.B.	R.C.	Amplification
2)	Saturation	F.B.	F.B.	} Switching (Digital- ON/OFF I/O)
3)	Cut-off	R.B.	R.B.	
4)	Reverse Active	R.B.	F.B.	Rarely used for Amp.

OPERATION (ACTIVE MODE)

