

Name: Sandesh Shrestha  
Roll no: 2K21/CO/427

A6 Batch

COA Assignment I

2) Simplify the following expressions using Boolean algebra.

a)  $A + AB$

$$\text{Soln, } A + AB = A \cdot (1 + B)$$

$$= A \cdot (1)$$

$$= A \quad (\text{absorption law})$$

Truth table

A	B	$AB$	$A+BA$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

$$\therefore (A = A+BA)$$

b)  $AB + AB'$

Soln,

$$= A(B+B')$$

$$= A \cdot 1$$

$$= A$$

Truth table

A	B	$AB$	$AB'$	$AB+AB'$
0	0	0	0	0
0	1	0	0	0
1	0	0	0	0
1	1	1	0	1

$$\therefore A = AB + AB'$$

c)  $A'B'C + AC$

Soln,

$$= A'B'C + AC$$

$$= C(A'B + A)$$

$$= CA + CB$$

d)  $A'B + ABC' + ABC$

Soln,

$$= A'B + AB(C+C')$$

$$= A'B + AB \cdot 1$$

$$= B(A' + A)$$

$$= B$$

2) Simplify using Boolean algebra.

a)  $AB + A(CD + CD')$

$= AB + AC(D+D')$  (distributive law)

$= AB + AC - 1$

$= AB + AC$

$= A(B+C)$

• Truth table

A	B	C	D	AB	CD	CD'	$A(BC)$	Z
0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0	0
0	0	1	0	0	0	1	0	0
0	0	1	1	0	0	1	0	0
0	1	0	0	0	1	0	0	0
0	1	0	1	0	1	0	0	0
0	1	1	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0	0
1	0	1	0	0	1	0	0	0
1	0	1	1	0	1	0	0	0
1	1	0	0	1	0	1	1	1
1	1	0	1	1	0	1	1	1
1	1	1	0	1	1	0	1	1
1	1	1	1	1	1	0	1	1

equivalent so proved.

5)  $(BC' + A'D)(AB' + CD')$

SOLN,

$$= BC'(AB' + CD') + A'D(AB' + CD')$$

$$= ABB'C' + BC'CD' + AA'B'D + A'DD'C$$

$$= 0 + 0 + 0 + 0 + 0 \quad [\because A \cdot A' = 0]$$

3) Using DeMorgan's theorem, show that:

a)  $(A+B)'(A'+B')' = 0$

SOLN, ~~Suppose~~,

using DeMorgan's theorem,

$$= (A' \cdot B')(A'+B')'$$

$$= (A' \cdot B')(A \cdot B)$$

$$= (A \cdot A')(B \cdot B')$$

$$= 0 \cdot 0$$

$$= 0$$

b)  $A+A'B+A'B'=1$

SOLN,

$$= (A+B) + (A+B)' \quad [\because A+A'B=A+B]$$

$$= 1 \quad [\because A+A'=1]$$

4) Simplify using 3-variable K-map.

a)  $F(x, y, z) = \Sigma(0, 1, 5, 7)$

Note:  $\Sigma \rightarrow$  SOP form  $x \rightarrow \bar{A}$

$2^3 = 8$  cells in the K-map

	00	01	11	10	2
0	1	0	1	1	3
1	4	1	5	1	6
2					

$$F = I + II + III \rightarrow F = A'B' + AC$$

Thus,  $F = A'B' + AC \rightarrow F = x'y' + xz$

ps: got confused and wrote ABC instead of xyz, sorry

b)  $F(x, y, z) = E(1, 2, 3, 6, 7)$

$x \setminus yz$	00	01	11	10	II
0	0	1	1	1	1
1	4	5	1	1	II

group of 2

group of 4

$$F = I + II$$

$$\therefore F = B + A'C \rightarrow F = y + x'z$$

c)  $F(x, y, z) = E(3, 5, 6, 7)$

$x \setminus yz$	00	01	11	10	III
0	0	1	1	2	
1	4	5	1	1	III

group of 2

group of 4

$$F = I + II + III \rightarrow BC + AB + AC$$

$$= BC + AB + AC$$

$$\therefore F = BC + AB + AC$$

$$\therefore F = YZ + XY + XZ$$

d)  $F(A, B, C) = \Sigma(0, 2, 3, 4, 6)$

$A \backslash B \backslash C$	000	001	010	011	100	101	110	111
0	1		1	1				0
1	1		0	1		1	0	0

$$F = I + ZZ = C' + A'B$$

-) Simplify the following Boolean functions w.r.t  
four-variable maps

@  $F(A, B, C, D) = \Sigma(4, 6, 7, 15)$

$$2^4 = 16 \text{ cells}$$

$AB \backslash CD$	00	01	11	10	00	01	11	10
00								
01	1		1	1				
11		1	1	1				
10								
	0	1	3	2	4	5	6	7
	128	138	158	168	128	138	158	168
	108	689	19	109	108	689	19	109

$$F = I + ZZ = A'B'D' + B'C'D'$$

b)  $F(A, B, C, D) = \Sigma(3, 7, 11, 13, 14, 15)$   
So 1^n

AB\CD	00	01	11	10
00	0	1	1	2
01	4	2	5	6
11	12	1	13	14
10	8	,	11	10

$$F = I + II + III$$

$$= B'C'D + CAB + ABD$$

c)  $F(A, B, C, D) = \Sigma(0, 1, 2, 4, 5, 7, 11, 15)$

So 1^n

AB\CD	00	01	11	10
00	1	1		1
01	1	1		1
11			1	
10			1	

$$F = A'D' + B'D' + BD$$

d)  $F(A, B, C, D) = \Sigma(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$

So 1^n

AB\CD	00	01	11	10
00	1			1
01	1	1	1	1
10	1		1	
11			1	
10	1			1

$$F = A'D' + B'D' + BD$$

Good Write

Q) Simplify the given expressions in

- 1) sum of products form
- 2) product of sums form

Q)  $x'z' + y'z' + yz' + xy$   
So, n,

Note: replace z by

$$m_1 = x'z'$$

$$(A + \bar{A})$$

$$m_2 = y'z'$$

$$A \cdot I = A$$

$$m_3 = yz'$$

$$A + I = A$$

$$m_4 = xy$$

	y				z				
n	y'z'00	0z	z'z	z'0	01	x'y'z'00	01	0z'z	11
0	1				1	0		0	0
x'z	1		1	1		1		0	0

for SOP  $\uparrow^2$  for POS

$$F = z + xy$$

$$F' = x'z + y'z$$

$$\therefore F = (x+z')(y+z')$$

Thus, required SOP form is  $F = z + xy$  and  
POS form is  $F = (x+z')(y+z')$

Q)  $AC' + B'D + A'C'D + ABCD$   
So, n,

required  $2^4 = 16$  terms

PRO →

for SOP form

AB		CD				F			
00	01	00	01	10	11	00	01	10	11
00	01	00	01	10	11	00	01	10	11
01	10	00	01	10	11	00	01	10	11
10	11	00	01	10	11	00	01	10	11

$$F = AC' + CD$$

for POS form

AB		CD				F'			
00	01	00	01	10	11	00	01	10	11
00	01	00	01	10	11	00	01	10	11
01	10	00	01	10	11	00	01	10	11
10	11	00	01	10	11	00	01	10	11

$$F' = A'C' + CD'$$

$$F = (A+C)(C'+D)$$

Good Write

Q7) Simplify the following Boolean function in sum of products form by means of 4 variable map.  
 Draw the logic diagram with  
 a) AND - OR gates  
 b) NAND gates

$$F(A, B, C, D) = \Sigma(0, 2, 8, 9, 10, 11, 14, 15)$$

SOP form


	AB	CD	00	01	11	10	
00	1					1	
01							
11							
10	(1)		1	1	1	1	

$$F = BC \bar{A}C + A\bar{B} + \bar{B}\bar{D}$$

$\therefore F = AC + A\bar{B} + \bar{B}\bar{D}$  which is required SOP form.

@

Logic diagram using AND-OR gates

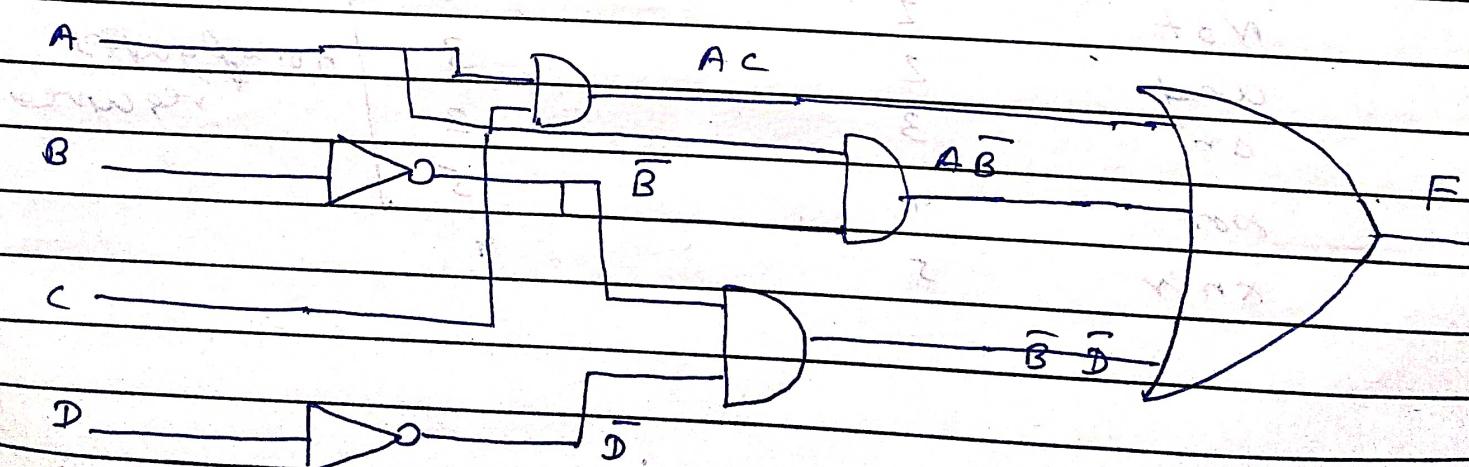

NAND  $y = \overline{A \cdot B}$


SPP DATE: \_\_\_/\_\_\_/\_\_\_  
PAGE: \_\_\_

(b) using NAND gate and inverters


Given  $F = A\bar{C} + A\bar{B} + \bar{B}\bar{D}$  and 2 inverters

Now  $\overline{F} = \overline{(A\bar{C} + A\bar{B} + \bar{B}\bar{D})}$
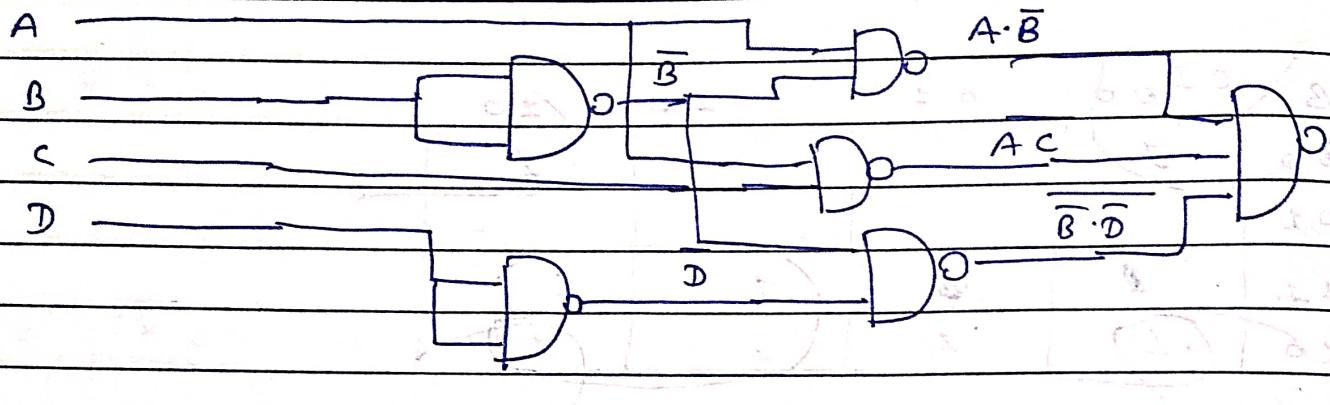
$$= (\overline{A\bar{C}} \cdot \overline{A\bar{B}} \cdot \overline{\bar{B}\bar{D}})$$



Notes:

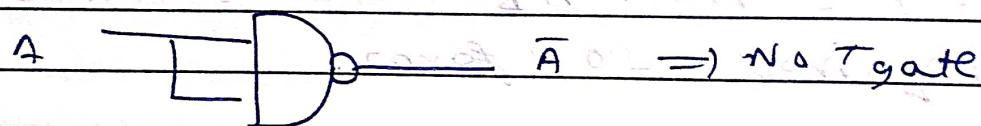

	<u>NAND</u>	<u>NOR</u>
Not	1	1
and	2	3
or	3	2
xor	4	5
xnor	5	4

no. of gates required

Q) Simplify the following Boolean function in product of sums form by means of a 4 variable map. Draw logic diagram with a) OR-AND gates, b) NOR gates.

$$F(w, x, y, z) = \sum_{SOP} (2, 3, 4, 5, 6, 7, 11, 14, 15)$$

$wz$	yz	00	01	10	11
00				1	1
01	1	1		1	1
11				1	1
10				1	

$$F = \bar{A}C + CD + \bar{A}B + BC \rightarrow SOP \text{ form}$$


$wz$	yz	00	01	10	11
00	0	0			
01	0	0			
11	0	0			
10	0	0		0	

$$F = (\bar{w}\bar{x}\bar{y}) \cdot \bar{x}\bar{y} + w\bar{y} + w\bar{x}\bar{z}$$

$$\therefore F = (x+y) (\bar{w}+y) (\bar{w}+x+z)$$

which is required POS form.

(a) using OR & AND gates

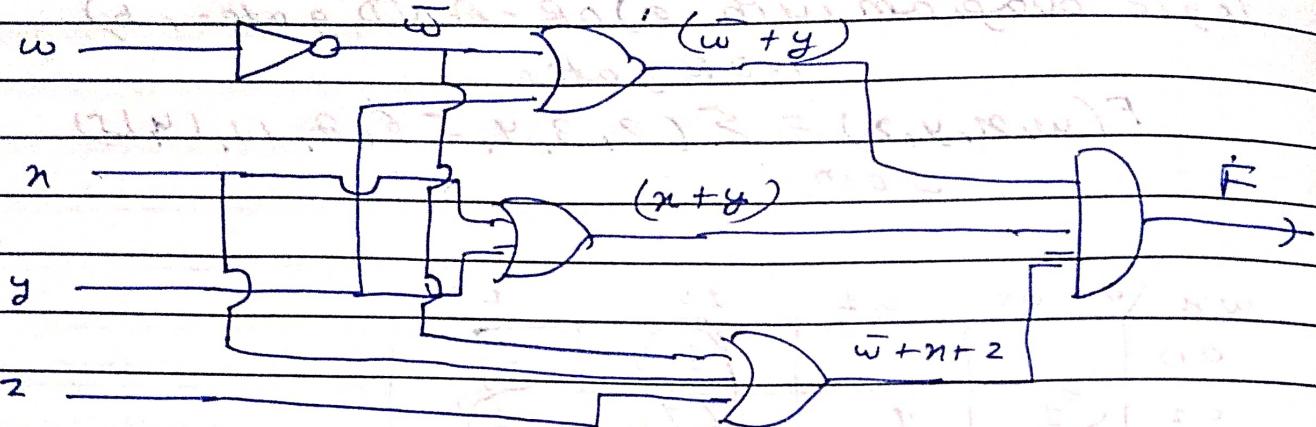


(b) using NOR gate

$$NOR \Rightarrow Y = \overline{A+B}$$

$$F = (\bar{x} + y)(\bar{w} + y)(\bar{w} + \bar{x} + z)$$
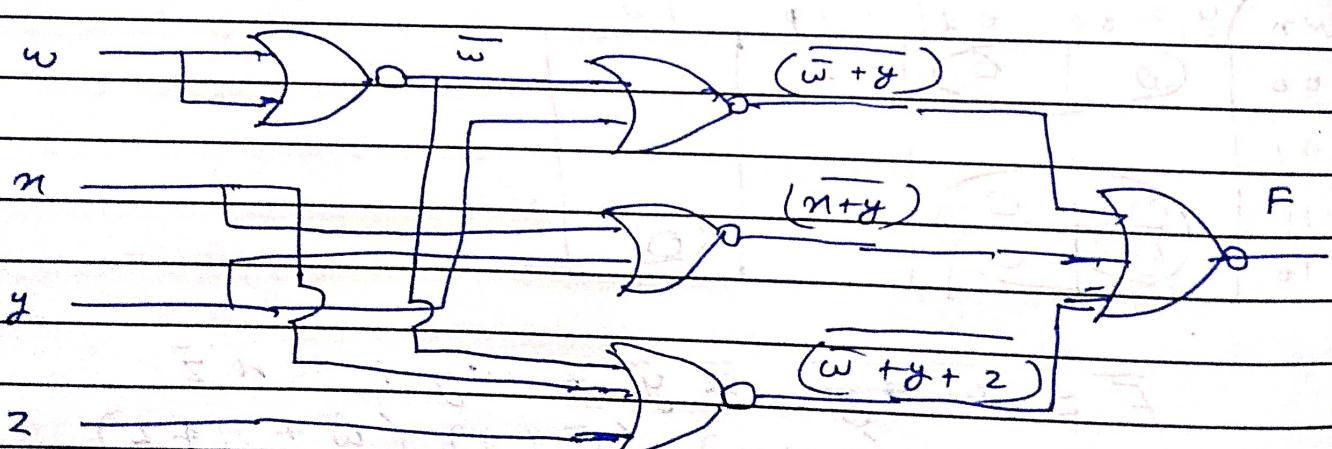
$$\bar{F} = (\bar{\bar{w}} + y) + (\bar{\bar{w}} + y) + (\bar{\bar{w}} + \bar{x} + z)$$



g) Simplify Boolean function  $F$  together with the don't care conditions  $d$  in 1) SOP 2) POS form

$$F(w, n, y, z) = \Sigma(0, 1, 2, 3, 7, 8, 10)$$

$$d(w, n, y, z) = \Sigma(5, 6, 11, 15)$$

SOP,

$wn \backslash yz$	00	01	11	10	
00	1	1	1	1	$Q_1$
01	X		1	X	$Q_2$
11		X			
10	1		X	1	

$$F = Q_1 + Q_2$$

$$= \bar{w} \bar{z} + \bar{x} \bar{z} \text{ which is required SOP form.}$$

$wn \backslash yz$	00	01	11	10	
00					
01	0	X		X	$Q_1$
11	0		X	0	
10		0	X		$Q_2$

$$\bar{F} = Q_1 + Q_2$$

$$= w z + x \bar{z}$$

$$\therefore F = (\bar{w} + \bar{z})(\bar{x} + z) \text{ which is required POS form.}$$