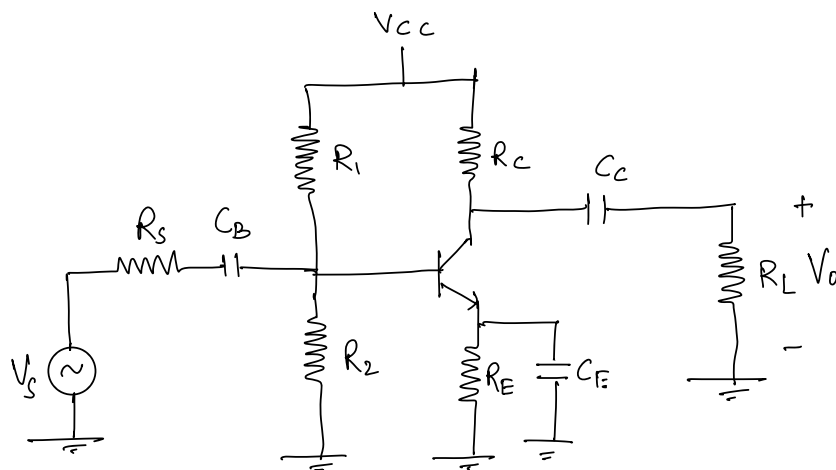


## AC Analysis of CE, CB, CC Configuration:

### 1. Common Emitter Amplifier with bypass Capacitor:



$C_B$ : Blocking Capacitor: To fix Q-point i.e. it provides DC isolation to biasing circuit. [To block DC]

$C_C$ : Coupling Capacitor: To fix Q-point i.e. it provides DC isolation to biasing circuit. [To block DC]

$C_E$ : Emitter bypass Capacitor: To prevent the fall in voltage gain at midband.

$C_B, C_C, C_E$ : Large Capacitance [MF Range]

- $C_B, C_C$  are connected to provide DC isolation to the biasing circuit so that external elements i.e.  $R_L, V_s$  and  $R_s$  does not disturb the operating point.



### Procedure to Analyse Amplifier:

Step 1: Identify the BJT Configuration in given circuit.

Step 2: Draw medium frequency AC equivalent circuit by replacing

1. Large Capr with s/c.
2. Small Capr with o/c.

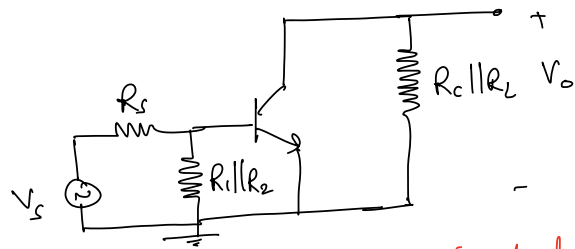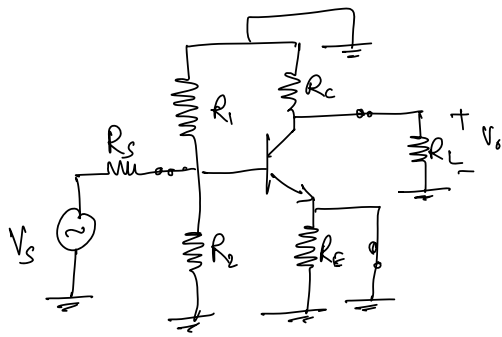
3. By connecting  $V_{CC}$  nodes to ground (In AC Analysis, DC supply  $V_{CC}$ 's deactivated)



Medium frequency AC equivalent circuit  
 $[R_B = R_1 || R_2, R'_L = R_C || R_L]$

Step 3: Replace BJT with small signal hybrid  $\pi$  equivalent model and calculate required values.

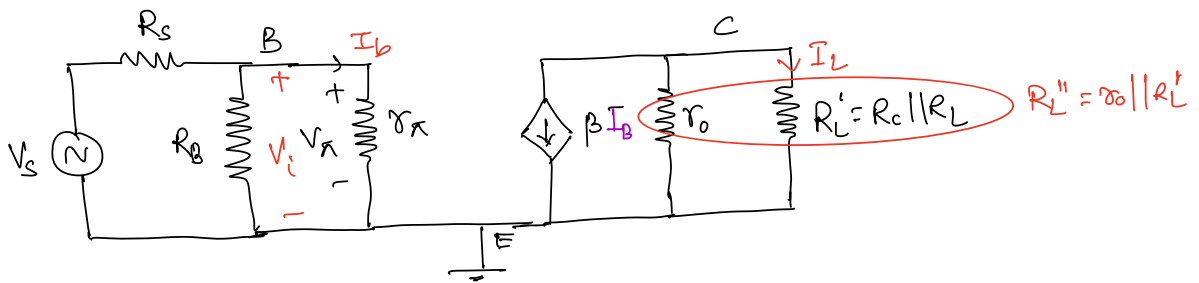1. Common Emitter amplifier with bypass capacitor



1. Current Gain ( $A_I$ )

$$A_I = \frac{I_L}{I_B}$$

$$A_I = \frac{-\beta I_B \times r_o}{I_B (r_o + R'_L)} = \frac{-\beta r_o}{r_o (1 + \frac{R'_L}{r_o})}$$

$$A_I = \frac{-\beta}{1 + \frac{R'_L}{r_o}}$$

$$I_B \frac{R'_L}{r_o} \ll 1$$

$$A_I = -\beta$$

Indicate load current is opposite to collector current.

2. Input Resistance ( $R_i$ ):

$$R_i = \frac{V_i}{I_b}$$

$$R_i = \frac{r_\pi I_b}{I_b}$$

$$R_i = r_\pi$$

3. Voltage Gain ( $A_v$ ):

$$A_v = \frac{V_o}{V_i}$$

$$A_v = \frac{-\beta I_b R_L''}{I_b r_\pi}$$

$$A_v = -\frac{\beta}{r_\pi} R_L''$$


$$A_v = -g_m R_L''$$

If  $r_o$  is neglected then,

$$A_v = -g_m R_L'$$

-ve sign indicates phase shift of  $180^\circ$  between  $V_i$  and  $V_o$ .

4. Output Resistance ( $R_o$ ):

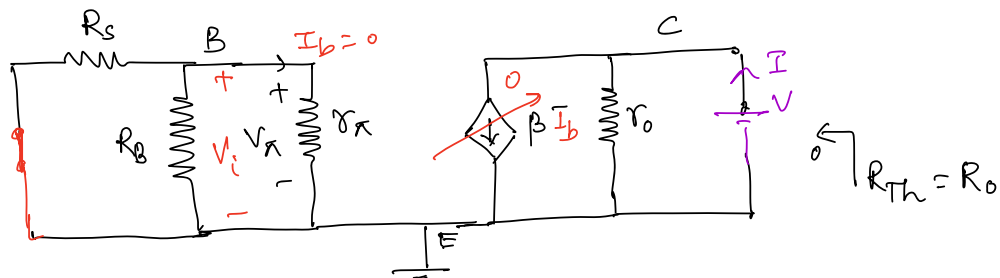

$$R_o = R_{Th} = \frac{V}{I} = r_o$$


## 2. Common Base amplifier :

$C_1, C_2, C_3$  are large Capacitors


i/p Node: Emitter

O/p Node: Collector

Common Node: Base

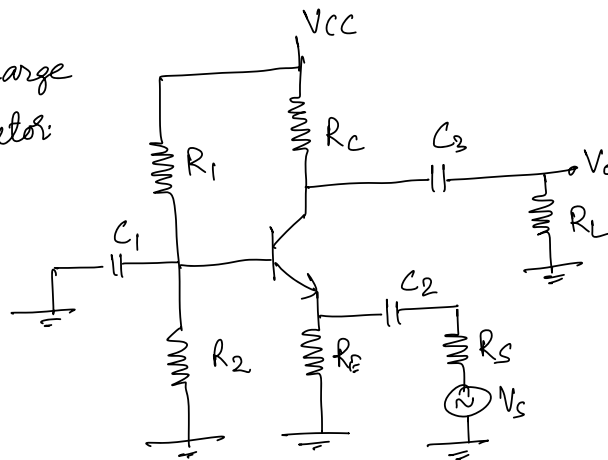

Medium frequency AC Equivalent circuit

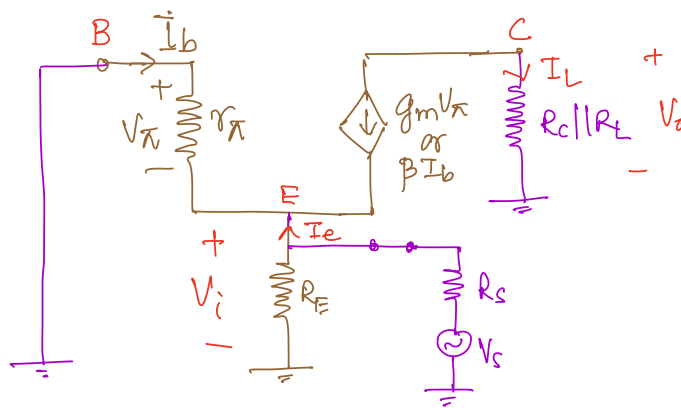

### 1. Current Gain ( $A_I$ ) :

$$A_I = \frac{I_L}{I_e}$$

$$I_L = -\beta I_b$$

$$I_e = -(I_b + \beta I_b) = -(1+\beta) I_b$$

$$A_I = \frac{I_L}{I_e} = \frac{-\beta I_b}{-(1+\beta) I_b} = \frac{\beta}{1+\beta} \approx 1$$

CB Amp has Unity Current Gain.

2. Input Resistance ( $R_i$ ) :

$$R_i = \frac{V_i}{I_e}$$

Apply KVL in loop (1),

$$V_i = -V_{\pi} = -I_b r_{\pi}$$

$$I_e = -(1+\beta) I_b$$

$$R_i = \frac{V_i}{I_e} = \frac{-I_b r_{\pi}}{-(1+\beta) I_b} = \frac{r_{\pi}}{1+\beta}$$

3. Voltage Gain ( $A_v$ ) :

$$A_v = \frac{V_o}{V_i} = \frac{-\beta I_b R_L'}{-V_{\pi}}$$

$$R_L' = R_C || R_L$$

$$A_v = \frac{-\beta \cancel{I_b} R_L'}{\cancel{I_b} r_{\pi}}$$

$$A_v = -\frac{\beta}{r_{\pi}} R_L' = -g_m R_L'$$

$$A_v = -g_m R_L'$$


CB Amplifier has large voltage gain.

4. Output Resistance ( $R_o$ ) :

$$R_o = \frac{V}{I}$$

$$I_b = 0, I = 0$$

$$R_o = \frac{V}{0} = \infty$$

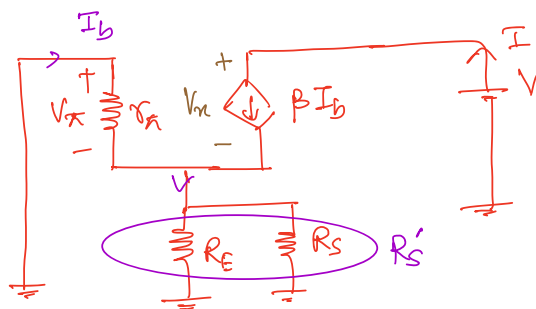

O/P Resistance is large in CB Amplifier.

Apply KVL in loop(1);

$$V - (I - \beta I_b) r_o - (I + I_b) R_s' = 0$$

$$V = I(r_o + R_s') + I_b(R_s' - \beta r_o) \quad \text{--- (1)}$$

Apply KVL in loop(2);

$$V - (I - \beta I_b) r_o + I_b r_\pi = 0$$

$$V = I r_o + I_b(r_\pi + \beta r_o)$$

$$I = \frac{V - I_b(r_\pi + \beta r_o)}{r_o} \quad \text{--- (2)}$$


from Eqn(1) & Eqn(2);

$$V = \left[ \frac{V}{r_o} - \frac{I_b}{r_o} (r_\pi + \beta r_o) \right] (r_o + R_s') + I_b(R_s' - \beta r_o)$$

$$V = V \left( 1 + \frac{R_s'}{r_o} \right) - I_b \left( 1 + \frac{R_s'}{r_o} \right) (r_\pi + \beta r_o) + I_b(R_s' - \beta r_o)$$

$$-V \frac{R_s'}{r_o} = -I_b \left[ \left( 1 + \frac{R_s'}{r_o} \right) (r_\pi + \beta r_o) - (R_s' - \beta r_o) \right]$$

$$(1 + \beta r_o)$$

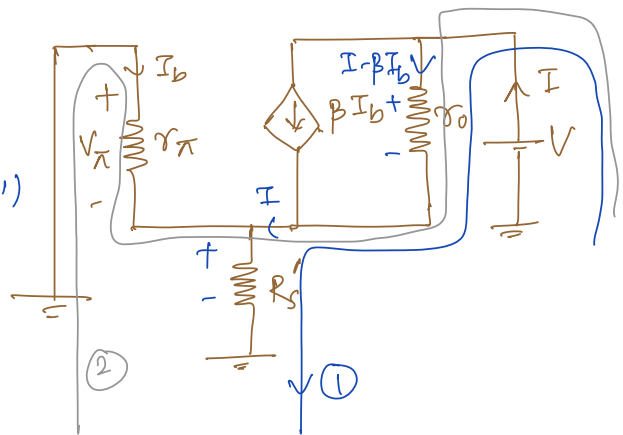


### 3. Common Collector Amplifier:


i/p Node: Base

o/p Node: Emitter

Common Node: Collector

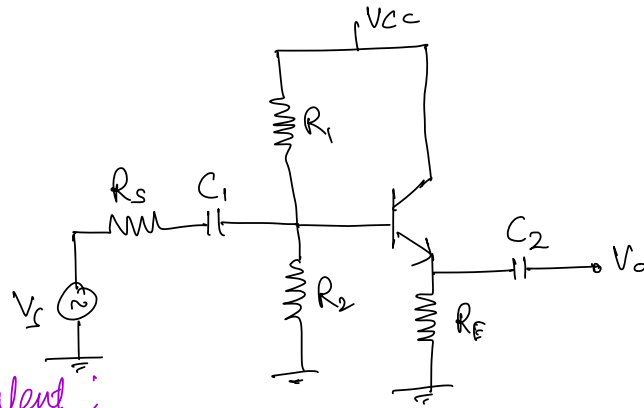

Medium frequency AC equivalent;

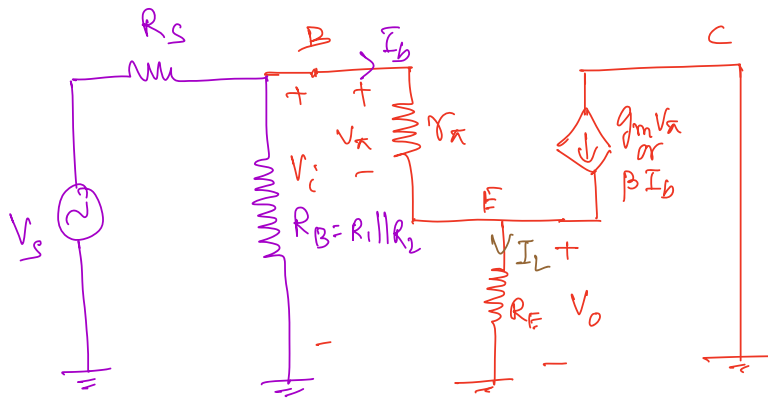

#### 1. Current Gain ( $A_I$ ):

$$A_I = \frac{I_L}{I_b} = \frac{(1+\beta) I_b}{I_b} = 1+\beta$$

$$A_I = 1+\beta$$

#### 2. Input Impedance ( $R_i$ ):

$$R_i = \frac{V_i}{I_b} = \frac{I_b r_\pi + (1+\beta) I_b R_E}{I_b}$$

$$R_i = r_\pi + (1+\beta) R_E$$

3. Voltage Gain ( $A_v$ ):


$$A_v = \frac{V_o}{V_i} = \frac{(1+\beta) I_b R_E}{I_b r_\pi + (1+\beta) I_b R_E}$$

$$A_v = \frac{(1+\beta) R_E}{r_\pi + (1+\beta) R_E}$$

4. Output Impedance ( $R_o$ ):

$$R_o = \frac{V}{I}$$

$$R_o = \frac{R_s' + r_\pi}{1+\beta}$$

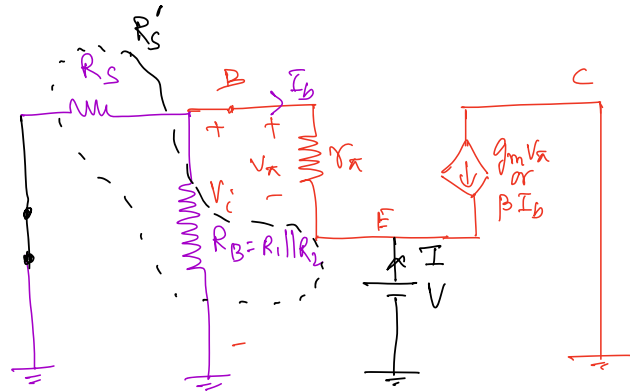

$$I = -(1+\beta) I_b$$

Apply KVL in loop (1);

$$+V + I_b r_\pi + I_b R_s' = 0$$

$$V = -I_b (r_\pi + R_s')$$

$$V = \frac{I}{1+\beta} (r_\pi + R_s')$$

$$R_o = \frac{V}{I} = \frac{r_\pi + R_s'}{1+\beta}$$

