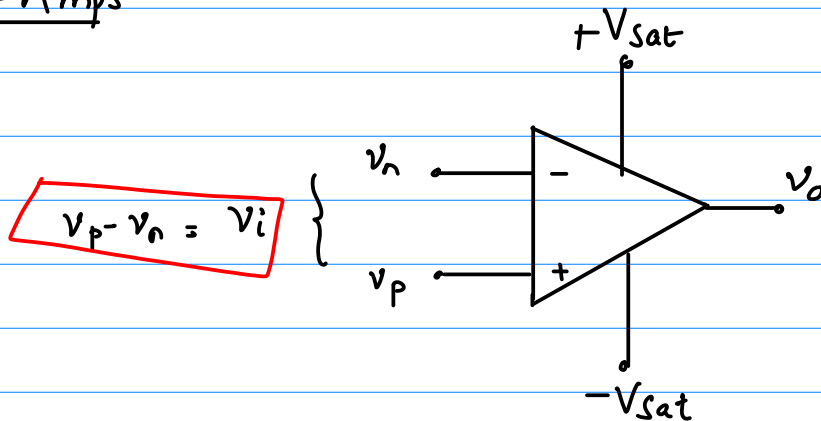


Operational Amplifiers

→ Op-Amps-




IC 741

max supply = $\pm 15V$


* It is a Voltage Amp or a VCVS

* Equivalent ckt :

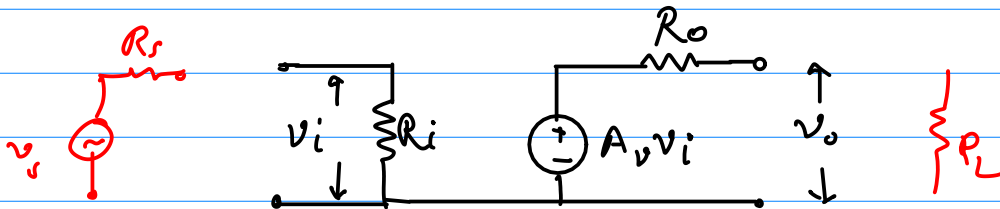

* x	Ideal Op-Amp :	Practical
Open loop Gain, A_v	∞	10^6
I/p Resistance, R_i	∞	$10^6 \Omega$
O/p Resistance, R_o	0	10-100 Ω
Gain BW Product, f_{GBW}	∞	10^6 Hz or 1 MHz
Bandwidth, BW	∞	1 MHz (i.e. when gain = 1 or 0 dB)

Open loop Operation:

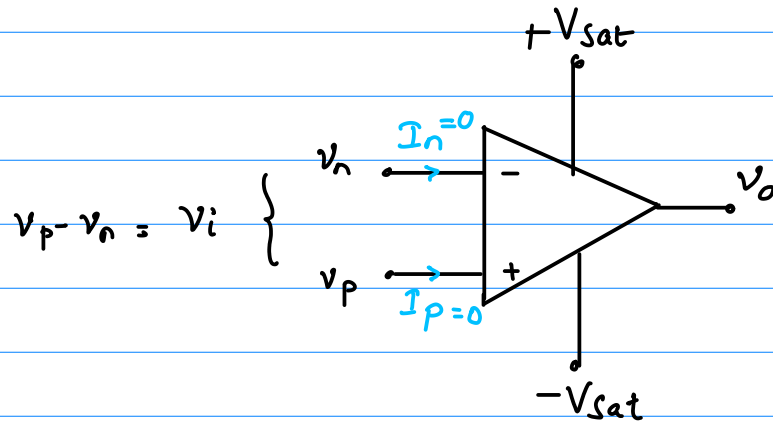


Ideal Op-Amp. $A_v = \infty$

$I_n = I_p = 0$

$\therefore R_i = \infty$ (whether O.L. or C.L.)

$v_o = A_v v_i$ ($\because R_o = 0$)

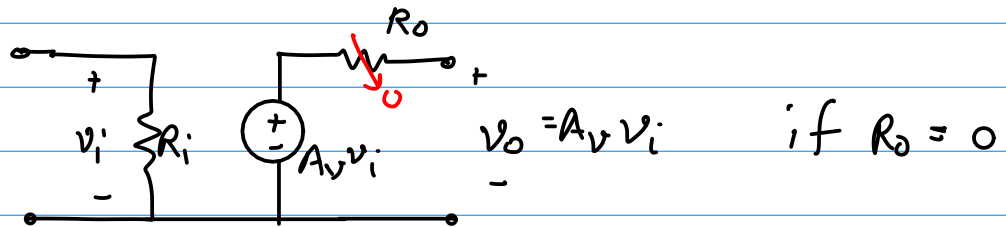

But $\because A_v = \infty$, $v_o \rightarrow \infty$ (Not possible, limited by $\pm V_{sat}$)

So, if $v_i = +ve \rightarrow v_o = +V_{sat}$ *

if $v_i = -ve \rightarrow v_o = -V_{sat}$ *

* So, for O.L. operation:

$v_i = +ve \Rightarrow v_p - v_n > 0 \Rightarrow v_p > v_n \rightarrow v_o = +V_{sat}$

$v_i = -ve \Rightarrow v_p - v_n < 0 \Rightarrow v_n > v_p \rightarrow v_o = -V_{sat}$

* In O.L., Op-Amp acts as a comparator.

if $v_p > v_n \rightarrow v_o = +V_{sat}$ (logic '1')

if $v_p < v_n \rightarrow v_o = -V_{sat}$ (logic '0')

→ Closed loop Operation: (feedback)

(i) +ve feedback

* o/p connected to +ve
i/p terminal (p) directly
or through some component
or combo of components
(like R, L, C, diode, transistors
etc.)



* $|A_{CL}| \gg |A_{OL}| (=A_v)$

* Since $A_v \approx \infty$ large,

$A_{CL} \rightarrow \infty$ as well

* $v_o = \pm V_{sat}$ depending
on whether $v_p > v_n$ or
 $v_p < v_n$
(Just like O.L. case)

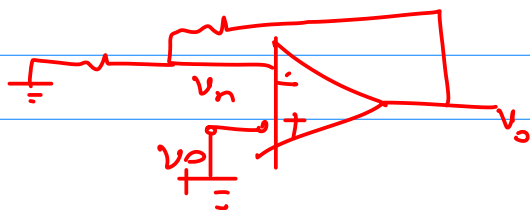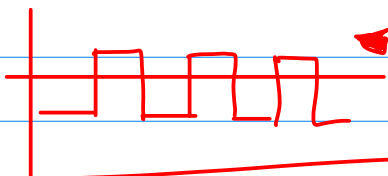* Used in Oscillators,
Schmidt trigger etc.



(ii) -ve feedback

o/p connected to -ve
i/p terminal (n) directly
or through some component
or combo of components
(like R, L, C, diode, transistors
etc.)

* $|A_{CL}| \ll |A_{OL}|$ or $|A_v|$

* e.g. $|A_{CL}|$ could be 10

* $|v_o| \leq |V_{sat}|$

* $|v_o|$ depends on source
vol. (Amplifier)

****** In -ve f.b., $v_i = 0$
(always, regardless of source
vol.)


i.e. $v_p = v_n$ (-ve f.b. only)

VIRTUAL SHORT

If v_p or $v_n = 0$, both are
 $0 \Rightarrow$ **VIRTUAL GROUND**

→ ONLY for -ve f.b.
Not for +ve f.b. or O.L.

* Virtual Short & Virtual Ground :

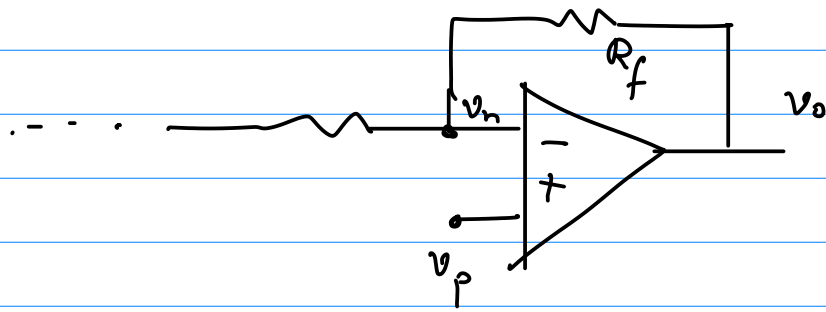


Happens only if A_v (O.L gain) is very large

then

$$v_p = v_n$$

Virtual short

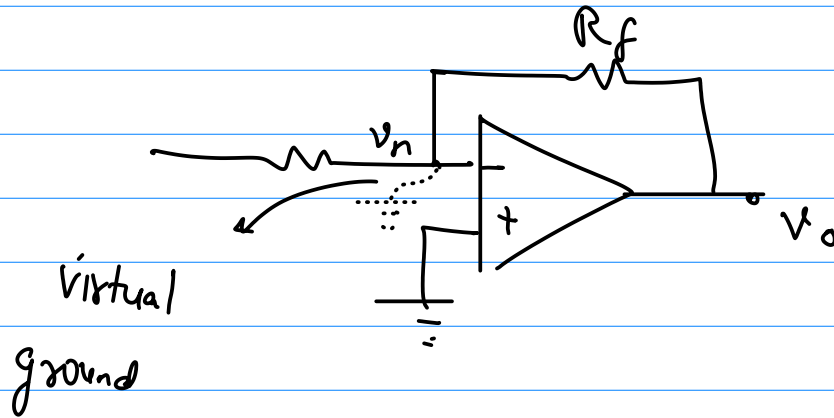


$$\text{then } v_n = 0$$


$$\therefore v_p = 0$$

Virtual Ground

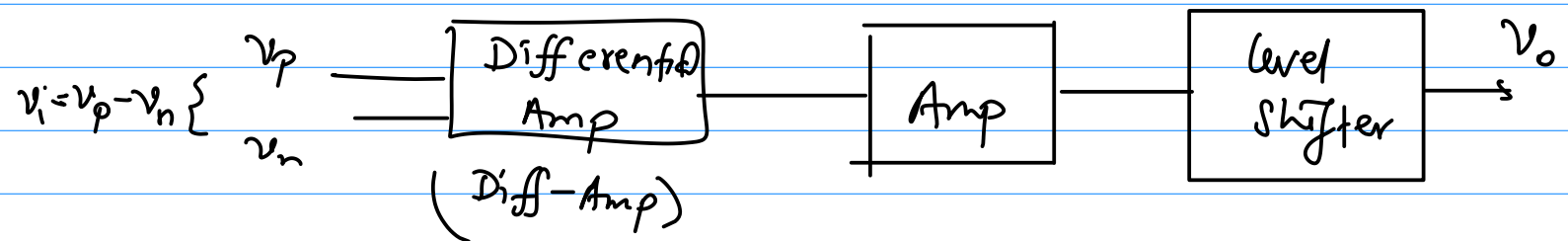HW) Read about the internal ckt stages of Op - Amp




* Op amp is a Multistage Amplifier.

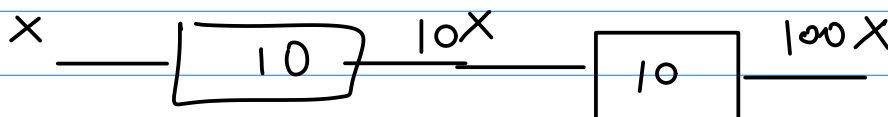

Negative feedback :

Modes of Operation :

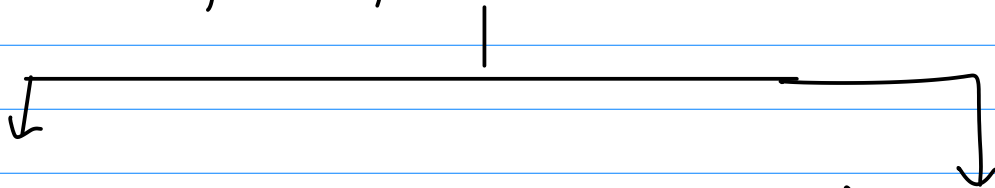

1) Inverting Amp



* Phase diff b/w v_p & source, $\phi = 180^\circ$

* $v_o \propto -v_s$

2) Non-Inverting Amp

* $\phi = 0^\circ$ or 360°

* $v_o \propto +v_s$


3) Differential Mode :-

$$v_o \propto (v_p - v_n)$$

if A_v is not very large

∴ Here virtual short is not applicable so, $v_p \neq v_n$

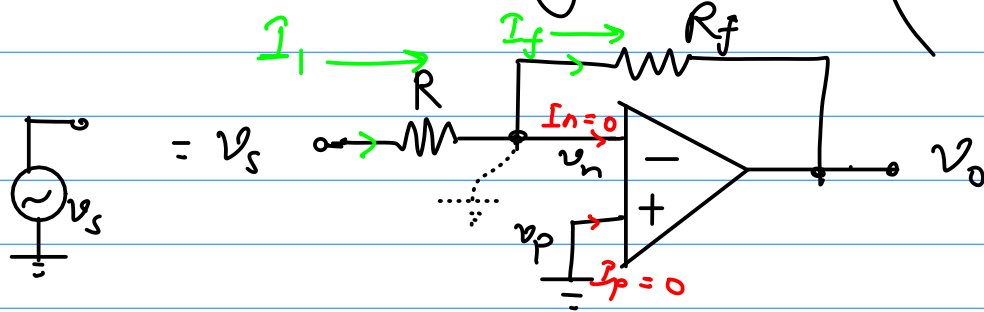→ * Inverting Amp: (Ideal OpAmp, $A_i = \infty$, $R_i = \infty$, $R_o = 0$)




$$v_n = 0$$

$$\therefore v_p = 0$$

(Virtual Ground)

$v_o = ?$

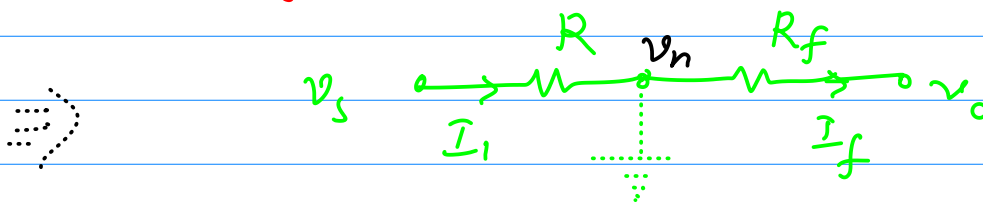

* KCL $\rightarrow I_1 = I_f + I_n = I_f$ ($\because I_n = 0$)

$$\Rightarrow I_1 = I_f \quad \text{--- (1)}$$


Ohm's law $\rightarrow I_1 = \frac{v_s - v_n}{R}$ ($v_n \rightarrow 0$)

$$\Rightarrow I_1 = \frac{v_s}{R} \quad \text{--- (2)} \quad (\because v_n = 0)$$

Ohm's law : $I_f = \frac{v_n - v_o}{R_f}$ ($v_n \rightarrow 0$)

$$\Rightarrow I_f = -\frac{v_o}{R_f} \quad \text{--- (3)}$$

Now from ①, $I_1 = I_f$

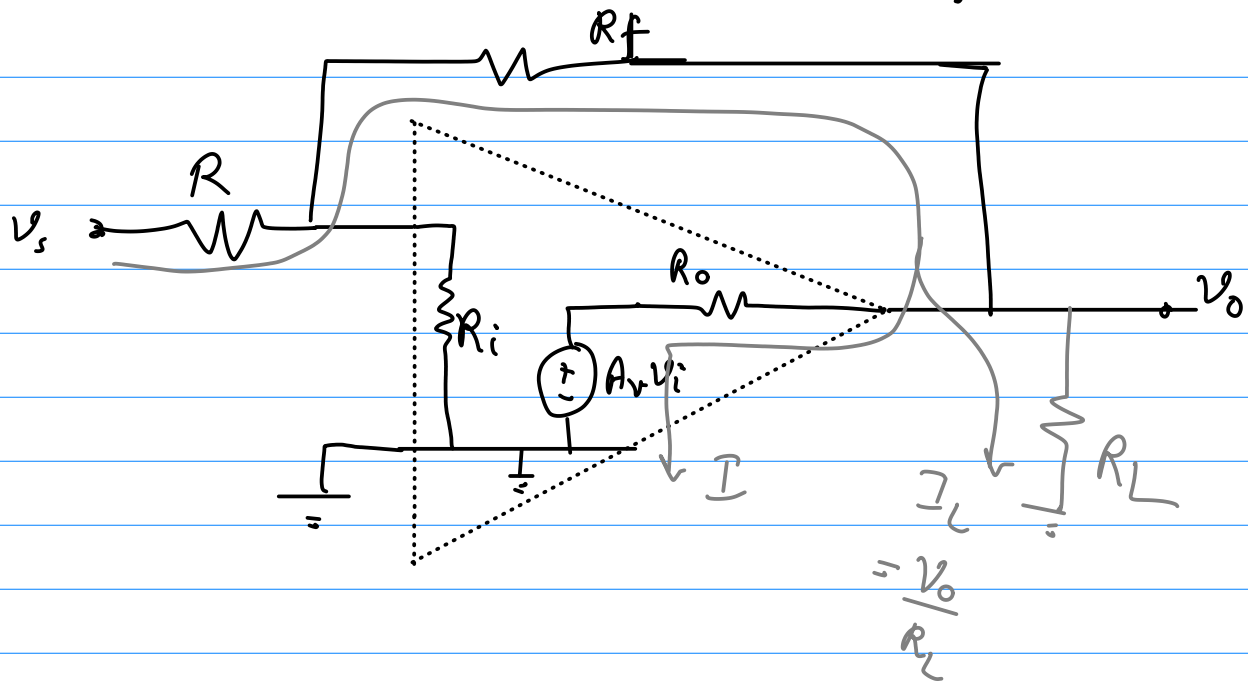

v_o will depend on R_L for ideal

opamp $\therefore R_o = 0$

So,

$$I_1 = I_f$$

$$\frac{v_s}{R} = -\frac{v_o}{R_f}$$

$$\Rightarrow v_o = \left(-\frac{R_f}{R} \right) v_s$$

(or)

$$\frac{v_o}{v_s} = A_{CL} = -\frac{R_f}{R}$$


$$v_o \propto -v_s$$

$$\phi = 180^\circ$$

hence inverting

Gain of Inverting
Amp. (Always)

→ Non Inverting Amp :-

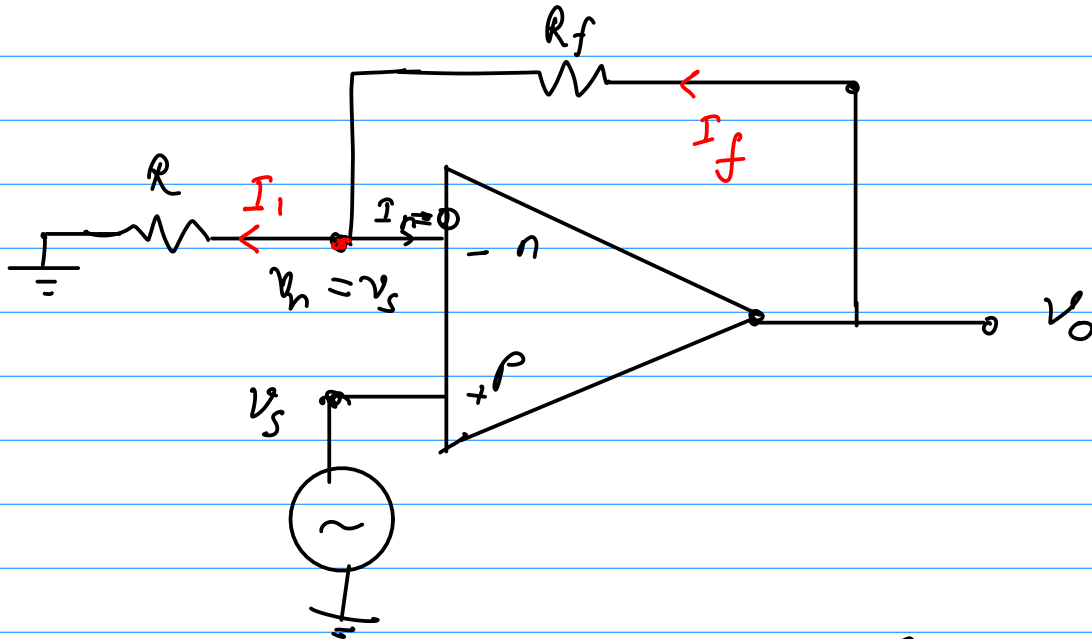

Virtual Short → $v_p = v_s$ (by connection)
 $v_n = v_p$ (\because -ve f.b.)

$\therefore, v_n = v_s$

KCL at 'n' node $\Rightarrow I_1 = I_f$

Ohm's law : $\rightarrow I_1 = \frac{v_n - 0}{R} = \frac{v_s - 0}{R}$

$\Rightarrow I_1 = \frac{v_s}{R}$

$I_f = \frac{v_o - v_n}{R_f} = \frac{v_o - v_s}{R_f}$

$$\therefore I_1 = I_f$$

$$\frac{V_s}{R} = \frac{V_o - V_s}{R_f}$$

$$\Rightarrow V_s \left(\frac{1}{R} + \frac{1}{R_f} \right) = \frac{V_o}{R_f}$$

$$\Rightarrow V_o = R_f \left(\frac{1}{R_f} + \frac{1}{R} \right) V_s$$

$$\Rightarrow V_o = \left(1 + \frac{R_f}{R} \right) V_s$$

or


$$\frac{V_o}{V_s} = A_{CL} = \left(1 + \frac{R_f}{R} \right)$$

→ +ve


Non inverting
Amp
gain

Special case of Non Inv Amp:

$$R \neq 0$$

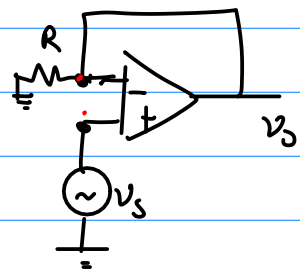

(or)

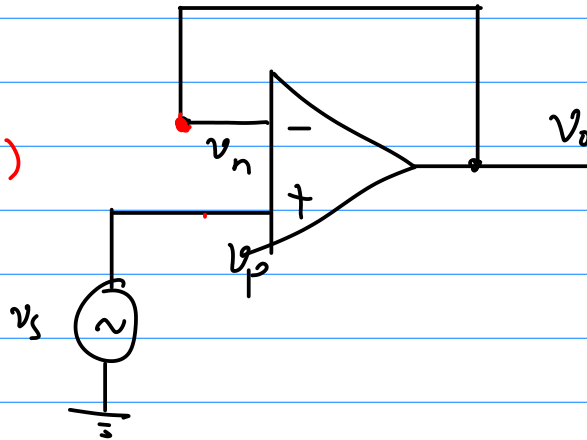

$$R_f = 0$$

Voltage-Follower

$$v_p = v_s, \quad v_n = v_s \quad (\because -ve \text{ f.b. virtual short})$$

So

$$v_o = v_n = v_s$$

short ckt


$$* \quad v_o = v_s \quad *$$

Voltage Follower **



Buffer (or driver) : They are used

for impedance matching.

e.g.

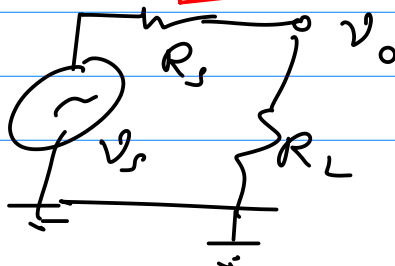
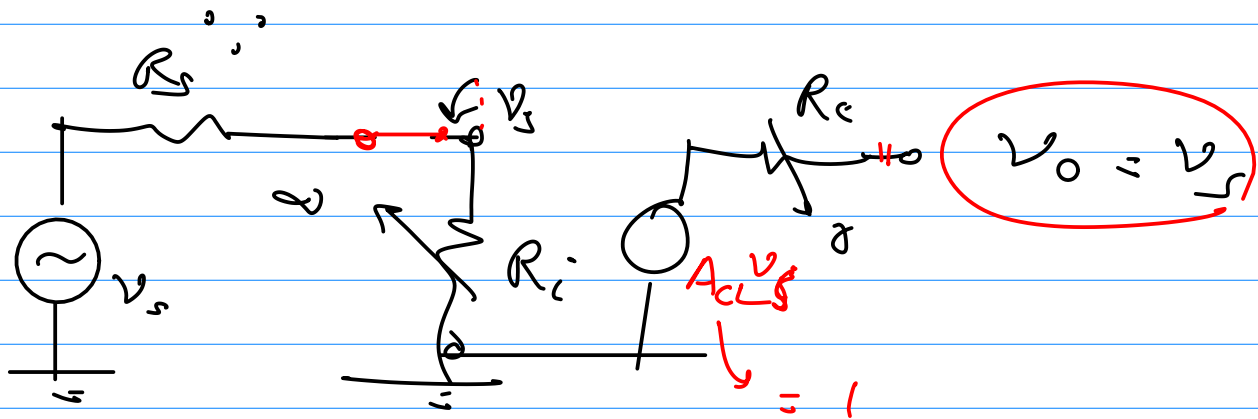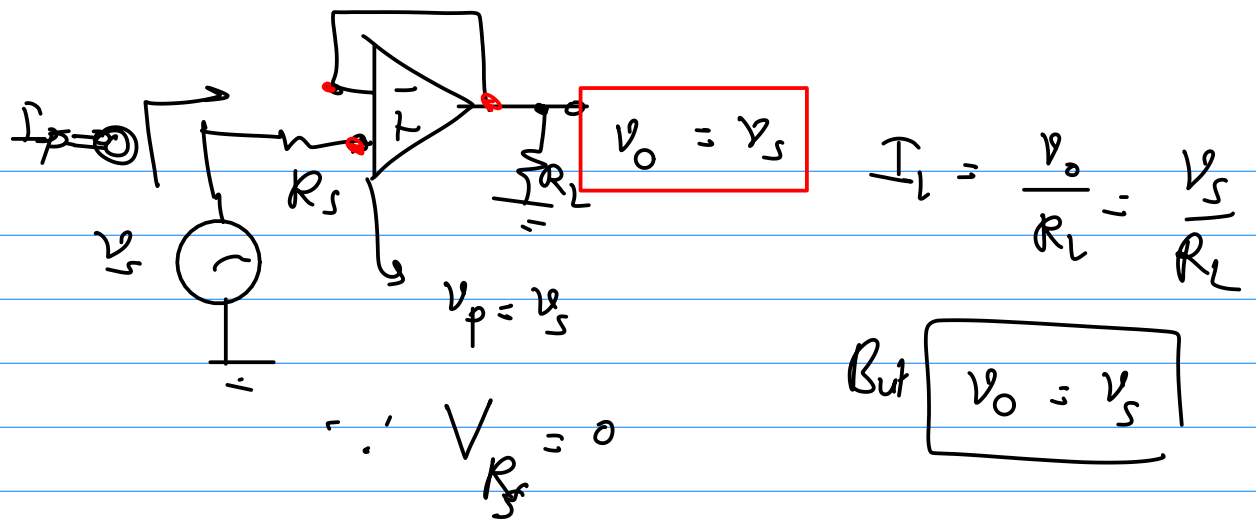
$$v_o = \left(\frac{R_L}{R_L + R_s} \right) v_s \neq v_s < v_s$$




$$A_{CL} = \left(1 + \frac{R_{f0}}{R} \right) = 1$$

Op-Amp Ckts :

1) Adder :

(1) Inverting Adder :

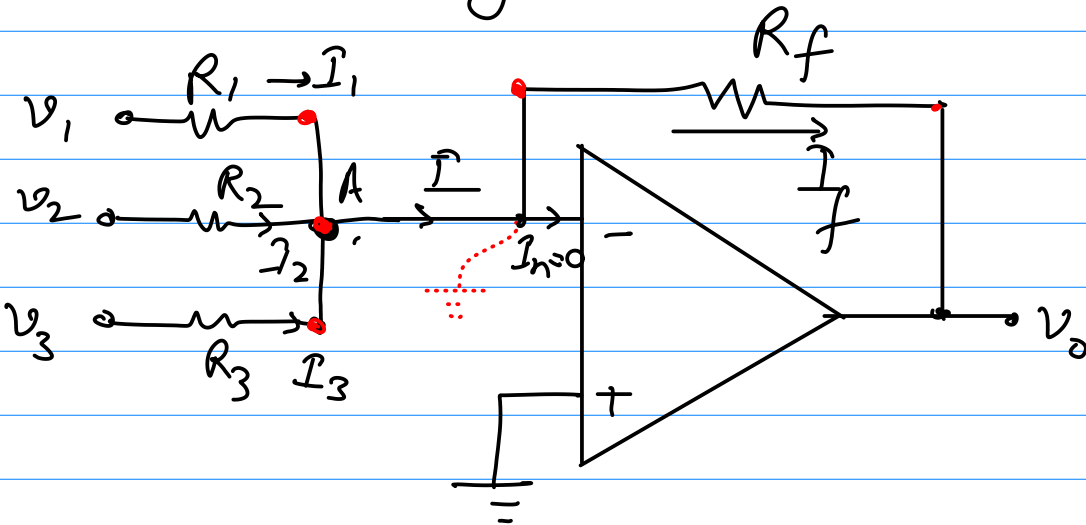

$$\boxed{V_A = 0} \quad \therefore \quad V_A = V_n = V_p = 0 \quad (\text{virtual gnd})$$

$$I_1 = \frac{V_1 - V_A}{R_1} \Rightarrow \hat{I}_1 = \frac{V_1}{R_1}$$

|| by

$$I_2 = \frac{V_2}{R_2}$$

$$\& \quad I_3 = \frac{V_3}{R_3}$$

KCL at A -

$$I_1 + I_2 + I_3 = I = I_f \quad \text{--- (1)}$$

Also,

$$I_f = \frac{V_n - V_o}{R_f} = \frac{0 - V_o}{R_f}$$

$$I_f = -\frac{V_o}{R_f}$$

from (1),

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = -\frac{V_o}{R_f}$$

$$\Rightarrow V_o = -R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$

if $R_1 = R_2 = R_3 = R$

$$\Rightarrow V_o = \left(-\frac{R_f}{R} \right) [V_1 + V_2 + V_3]$$

gain of inv. amp

sum


If $R_f = R$

then

$$v_o = -(v_1 + v_2 + v_3)$$

inverting


2) Non Inv Adder:

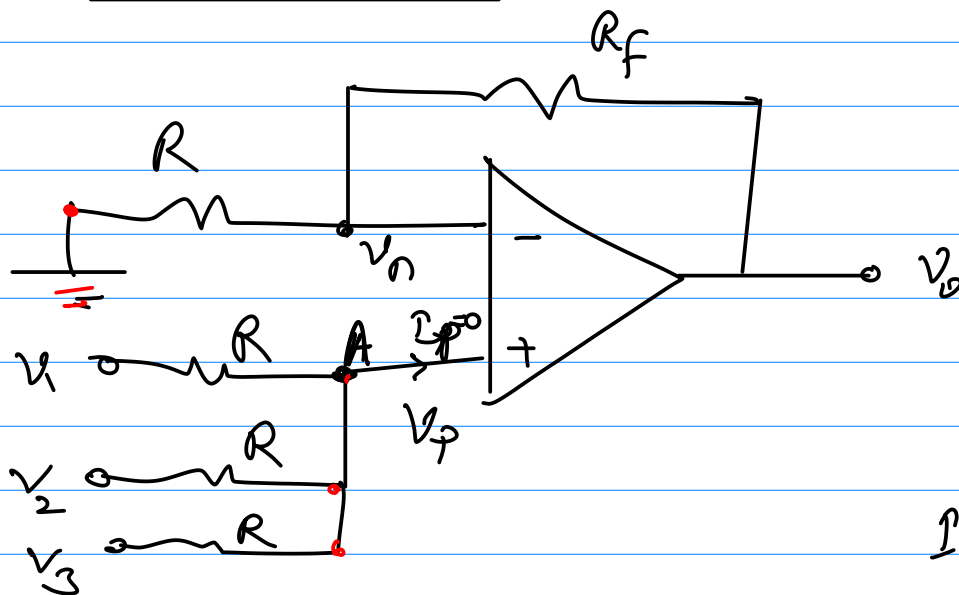

gain of Non-Inv-Amp


$$v_o = \left(1 + \frac{R_f}{R}\right) v_p$$

$$I_P = 0$$

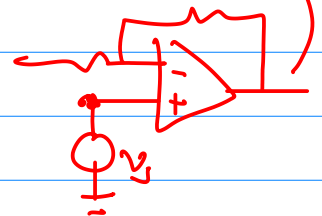


Principle of Superposition :

(i)

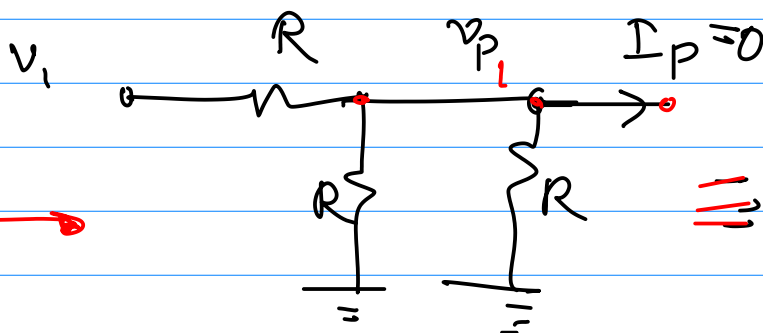


$$v_2 = 0 \quad v_3 = 0$$

\equiv

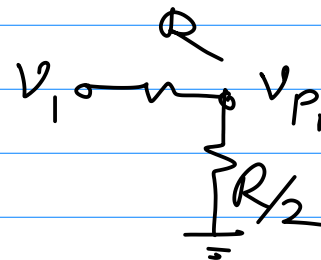

$$v_{p1} = \frac{R/2}{R + R/2} v_1$$

$$v_P = \frac{v_1}{3}$$

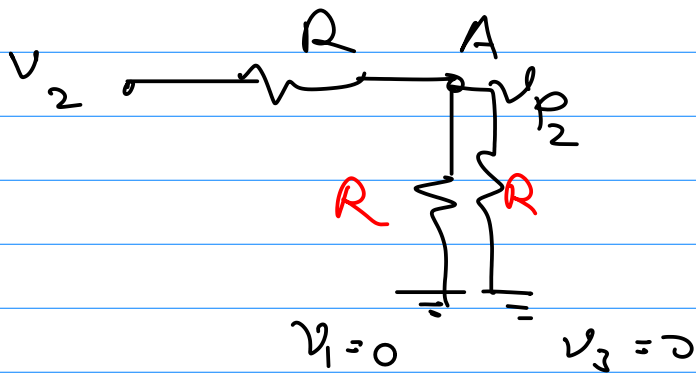

$$v_{P2} = \frac{v_2}{3}$$

Similarly,

$$v_{P3} = \frac{v_3}{3}$$


* Superposition :

$$v_P = v_P + v_{P2} + v_{P3}$$

total effect
= Algebraic sum
of individual
effects

$$v_P = \frac{v_1}{3} + \frac{v_2}{3} + \frac{v_3}{3}$$
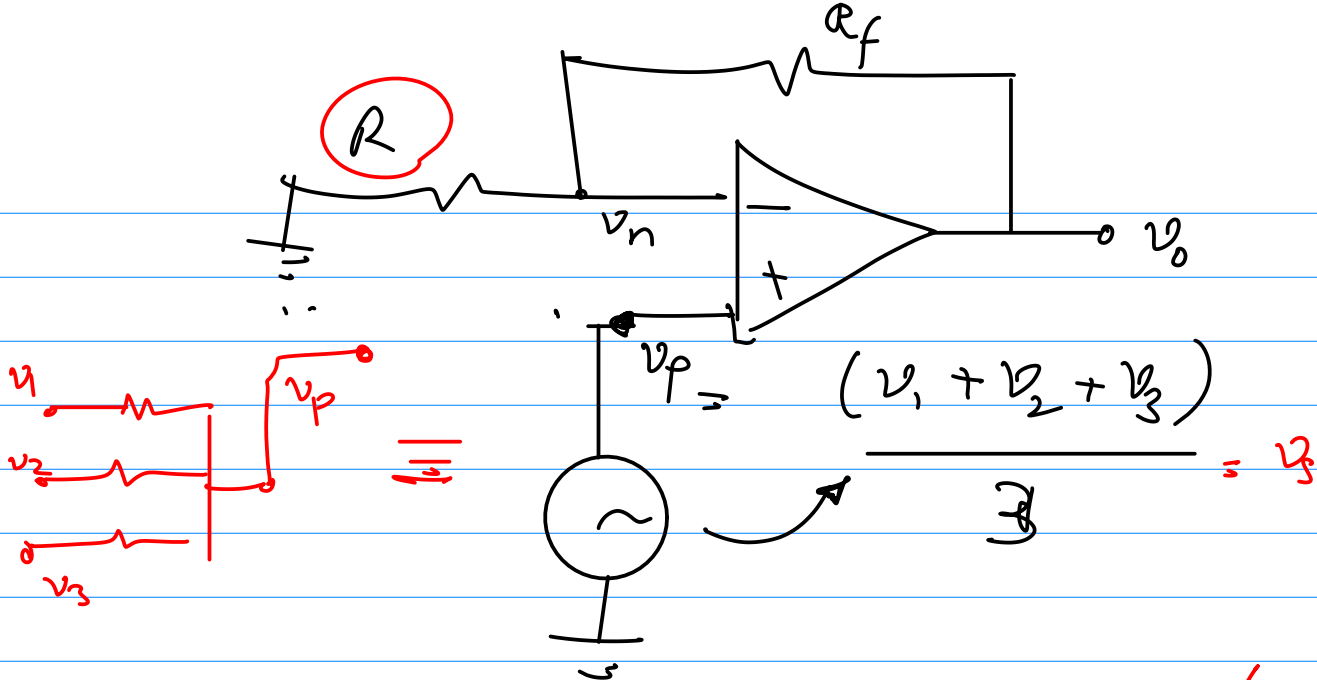
$$\Rightarrow v_P = \frac{(v_1 + v_2 + v_3)}{3}$$



Non 'inv. Amp. :-

$$v_0 = \left(1 + \frac{R_f}{R}\right) v_p$$

$v_s = v_p$

$$v_0 = \left(1 + \frac{R_f}{R}\right) v_p$$


$$\Rightarrow v_0 = \left(1 + \frac{R_f}{R}\right) \left[\frac{v_1 + v_2 + v_3}{3} \right]$$

If $\left(1 + \frac{R_f}{R}\right) = 3$ (or) $\frac{R_f}{R} = 2$

(or) $R_f = 2R$


then

$$v_0 = (v_1 + v_2 + v_3)$$

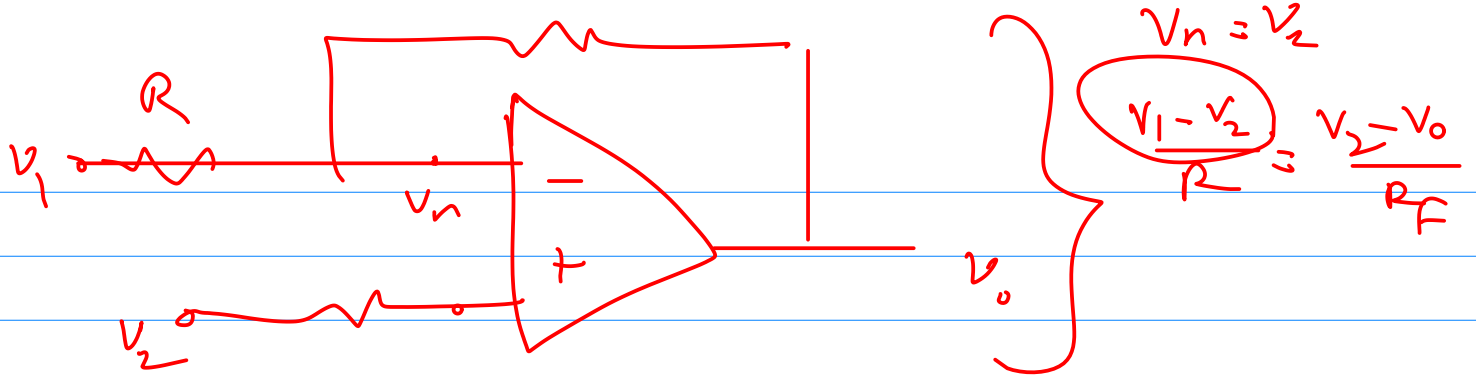


Superposition :-

(i)

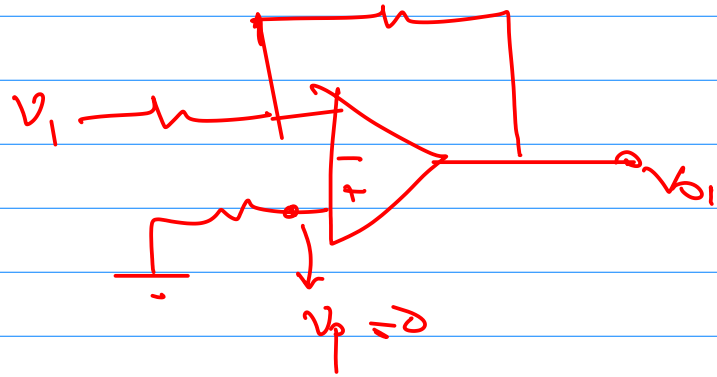

$$V_{o1} = -\left(\frac{R_f}{R}\right) V_1$$

(ii)

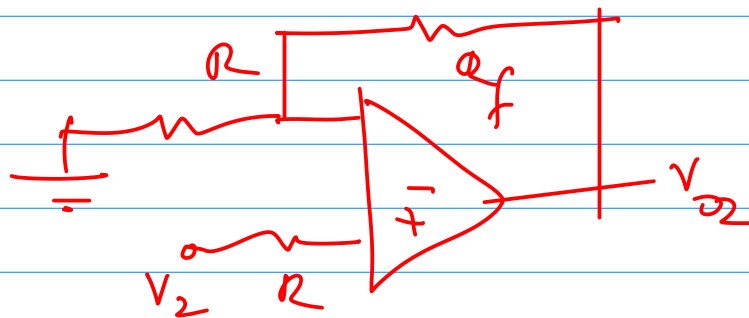


$$V_{o2} = \left(1 + \frac{R_f}{R}\right) V_2$$


$$V_o = V_{o1} + V_{o2} \Rightarrow \left(1 + \frac{R_f}{R}\right) V_2 - \left(\frac{R_f}{R}\right) V_1$$

Subtractor ?

HW

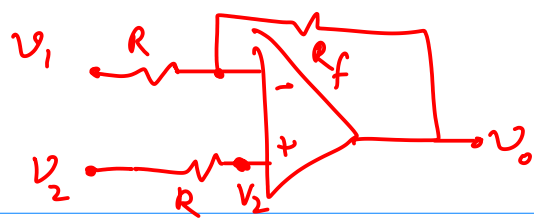

Integrator :

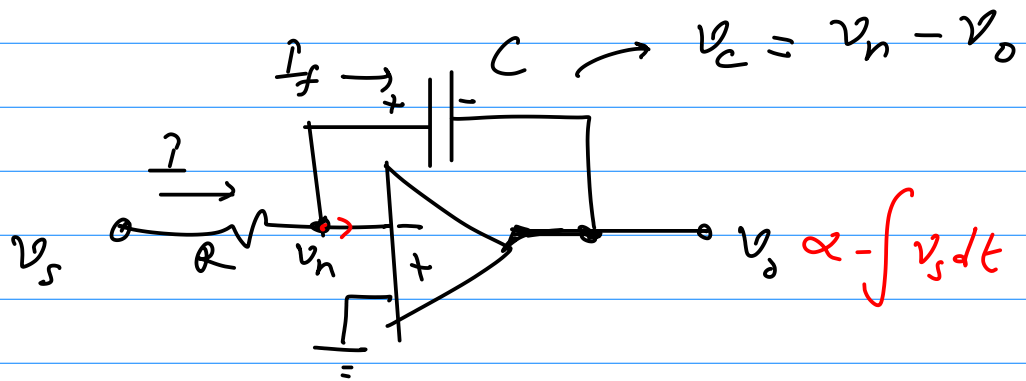

$$v_n = 0 \quad (\because -ve \text{ f.b.}, V_{OH})$$

$$I = \frac{V_s}{R} \quad \therefore v_n = 0$$


$I_f =$ current through C

$$I_c = C \frac{dv_c}{dt}$$

where

v_c is vol

across cap

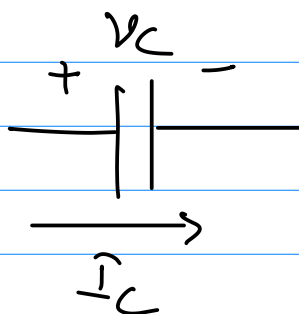

$$\text{So, } I_f = C \frac{dv_c}{dt} = C \frac{d(v_n - v_o)}{dt}$$

$$v_n = 0$$

$$\text{So, } I_f = -C \frac{dv_o}{dt} = I \quad (\text{by KCL})$$


$$\text{So, } -C \frac{dv_o}{dt} = \frac{v_s}{R}$$

Integrate both sides



$$v_o = -\frac{1}{RC} \int v_s dt$$

v_o is integration of v_s
with -ve sign

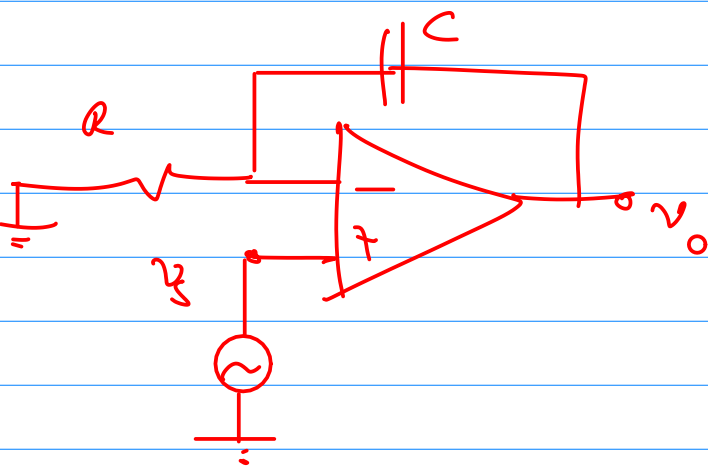Inverting $\rightarrow \therefore v_s$ connected
at -ve terminal




$$v_o = +\frac{1}{RC} \int v_s dt$$

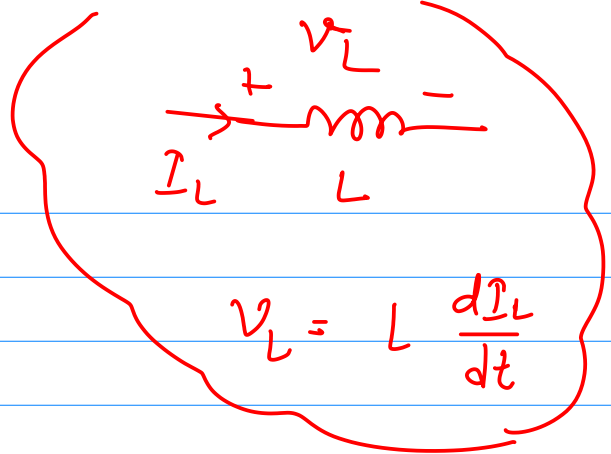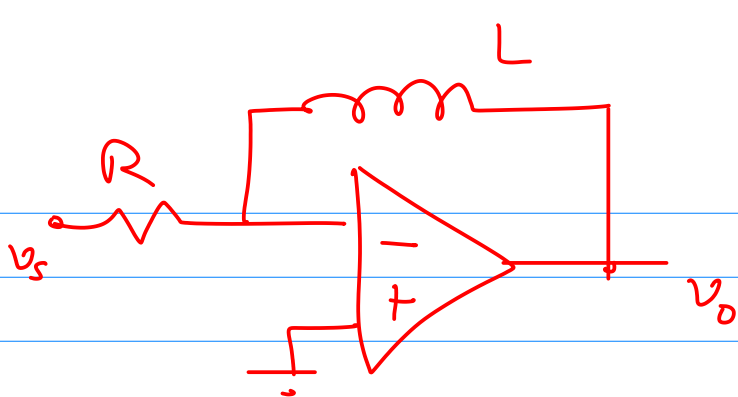


$$0 - v_o = L \frac{dI_L}{dt} = L \frac{d(I)}{dt} = L \frac{d(v_s/R)}{dt}$$
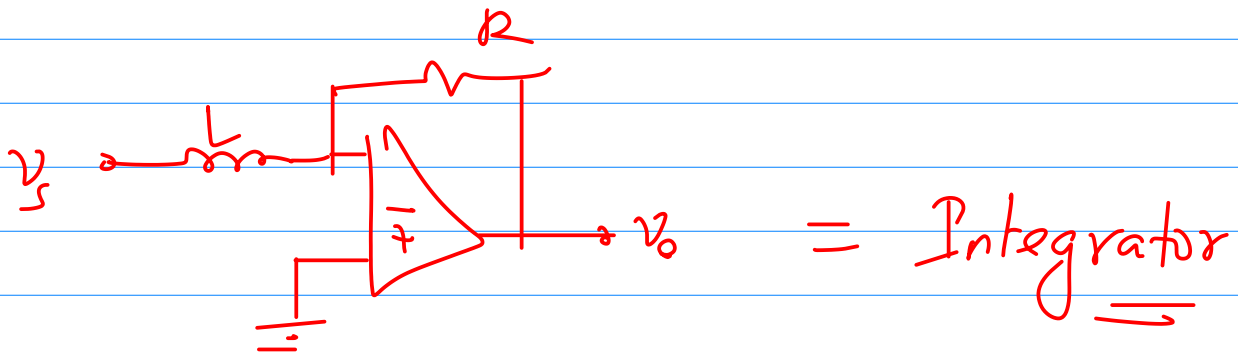
$$v_o = - \frac{L}{R} \frac{dv_s}{dt} \quad \left(\text{DIFFERENTIATOR} \right)$$




→ Differentiator →

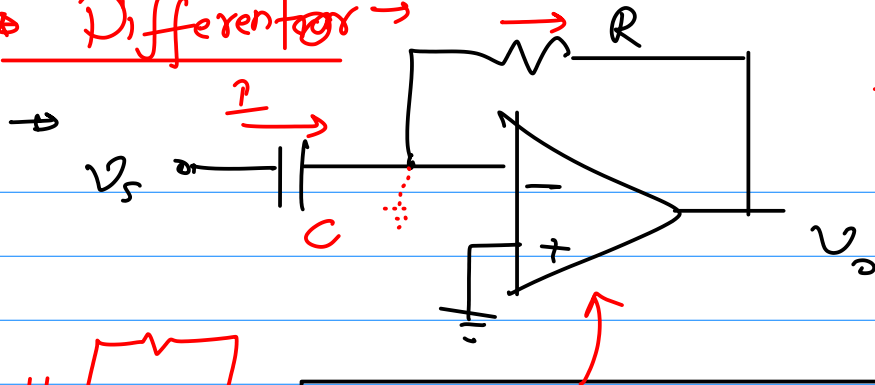

$$v_n = 0 \quad (V.G.)$$

$$I_f = \frac{0 - v_o}{R} = I = C \frac{d(v_s - 0)}{dt}$$
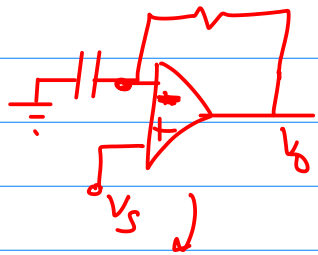
$$\Rightarrow -\frac{v_o}{R} = C \frac{dv_s}{dt}$$




$$v_o \propto - \frac{d v_s}{dt}$$

$$\Rightarrow v_o = -RC \frac{dv_s}{dt}$$

$$v_o = -RC \frac{dv_s}{dt}$$

→ Log - Amplifier :

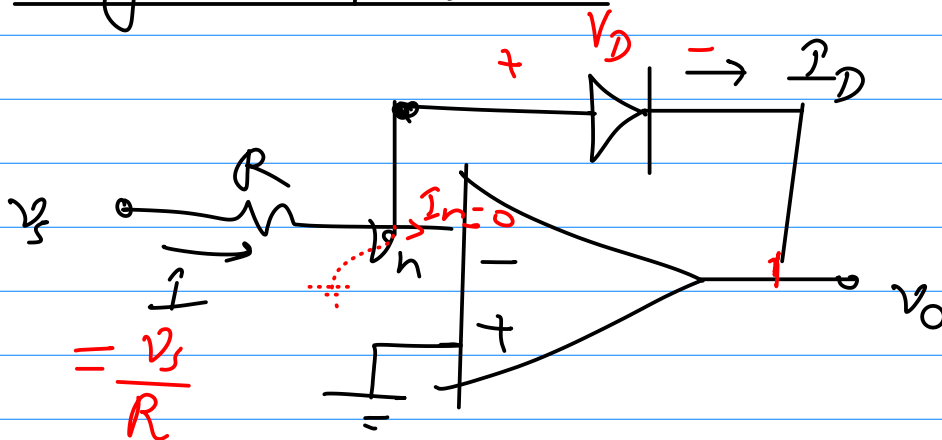

$$v_D = v_n - v_o$$

$$v_n = 0 \quad (V.G.)$$

$$I = \frac{v_s}{R} \quad \Rightarrow \quad I_D = I_0 \left(e^{\frac{v_D}{nV_T}} - 1 \right)$$


$$\frac{V_s}{R} = I_0 \left[e^{\frac{V_n - V_0}{\eta V_T}} - 1 \right]$$

$$\Rightarrow e^{-\frac{V_0}{\eta V_T}} = \frac{V_s}{I_0 R} \quad \text{neglect}$$

$$V_0 = -\eta V_T \log_e \left(\frac{V_s}{I_0 R} \right)$$

**

Anti-log Amp:

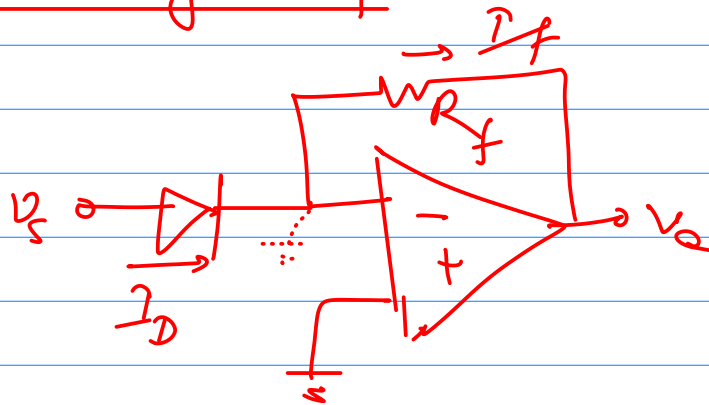

$$I_D = I_0 \left(e^{\frac{V_s - V_0}{\eta V_T}} - 1 \right)$$


$$= I_f = \frac{0 - V_0}{R_f}$$

$$\Rightarrow V_0 = -R_f I_0$$


$$\exp \left(\frac{V_s}{\eta V_T} - 1 \right)$$

$$V_0 \propto \exp(V_s)$$

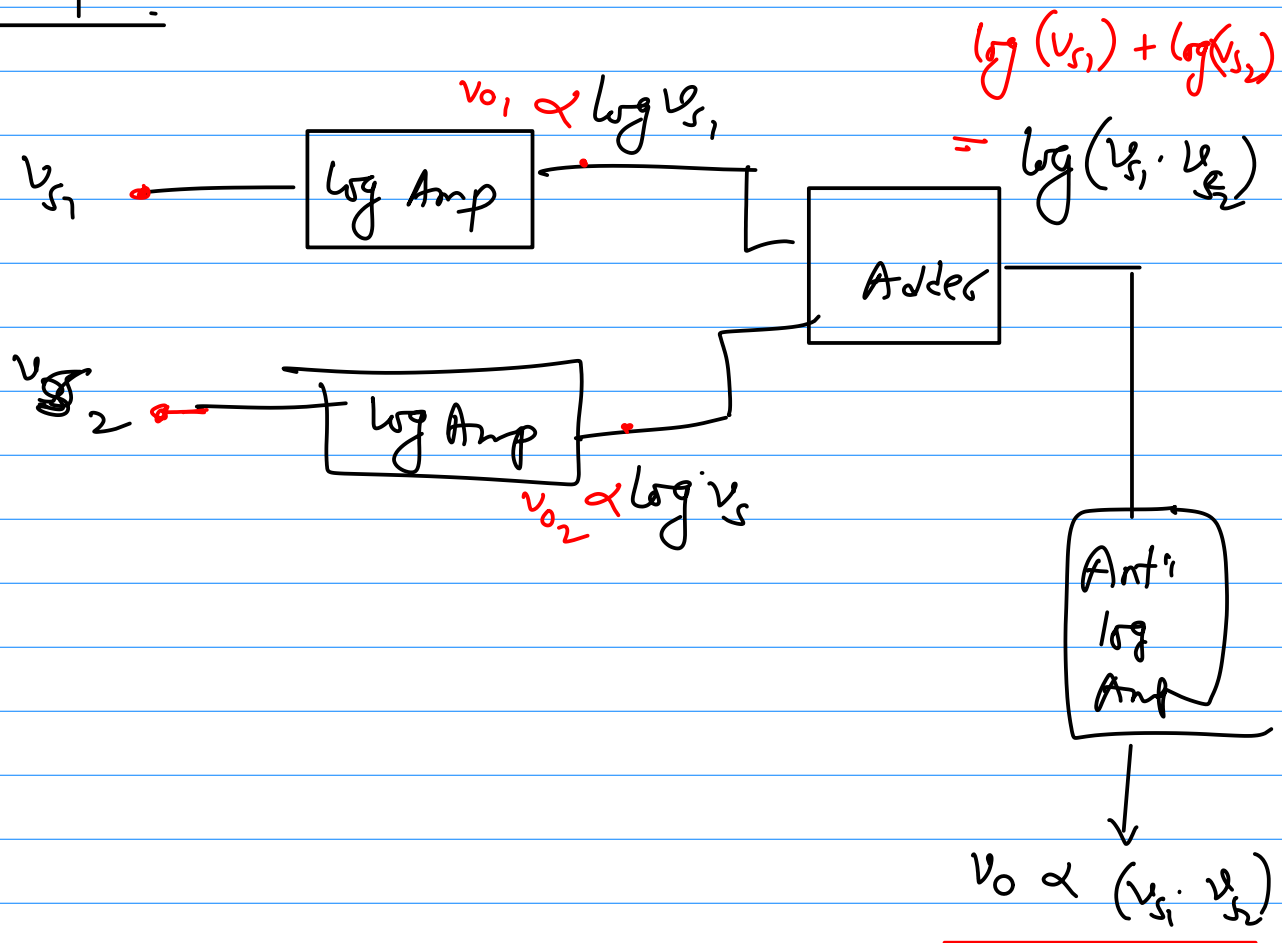
→ Multiplier — $v_o \propto (v_{s1} \cdot v_{s2})$




→ Current to voltage converter :-

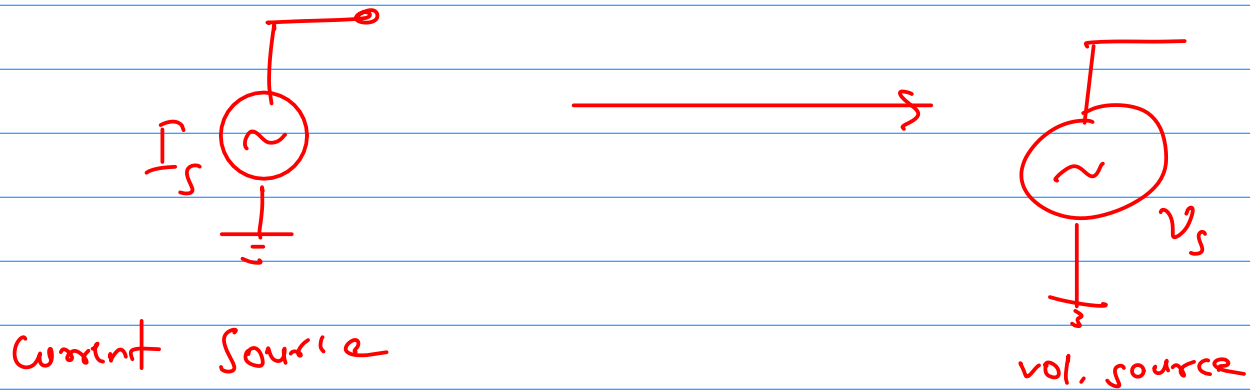

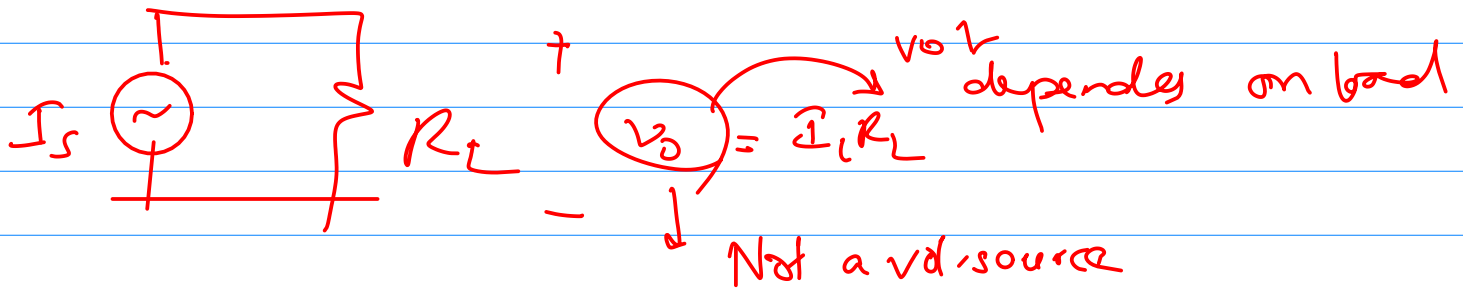Source value should be independent
of load →



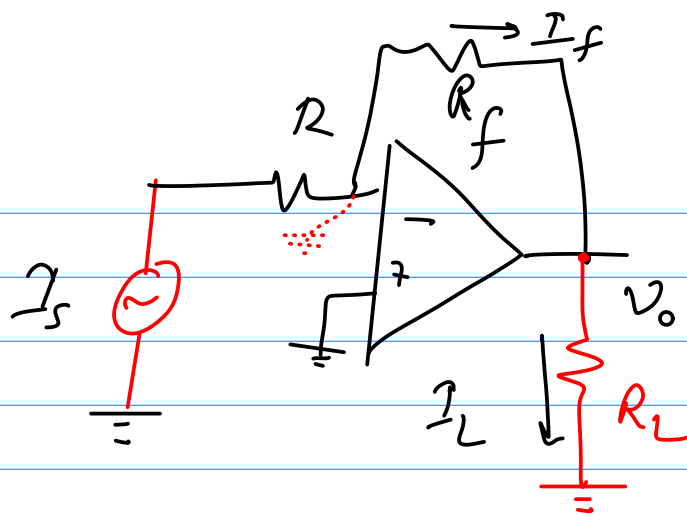

$$I_s = I_f = \frac{0 - v_o}{R_f}$$


$$\text{So, } v_o = -R_f I_s$$

$$I_L = \frac{v_o}{R_L} = -\frac{R_f}{R_L} I_s$$

$$V_{\text{Load}} = v_o = -R_f I_s = \text{Independent of } R_L$$

$v_o \propto I_s$
Conversion

Vol. to current Conversion :

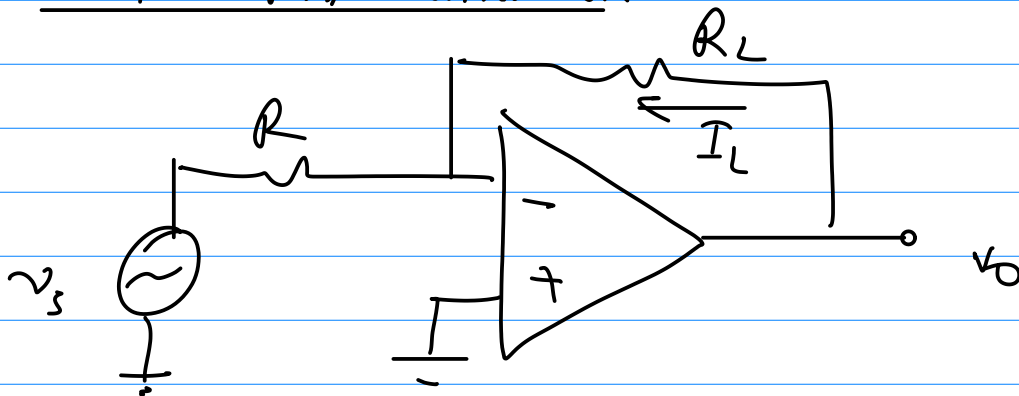

$$I_L = ?$$

(indep of R_L)