

# Junction Field Effect Transistor (JFET)


BJT : Bipolar  $\rightarrow$   $e^-$ s & holes both contribute to  $I$  in both NPN & PNP

JFET : Unipolar  $\rightarrow$  only 1 type of carrier conduct  
 n-channel JFET :  $e^-$   
 p-channel JFET : holes

3 terminals  $\rightarrow$  Gate (G)


Drain (D)  $\equiv$  Collector in BJT

Source (S)  $\equiv$  Emitter in BJT

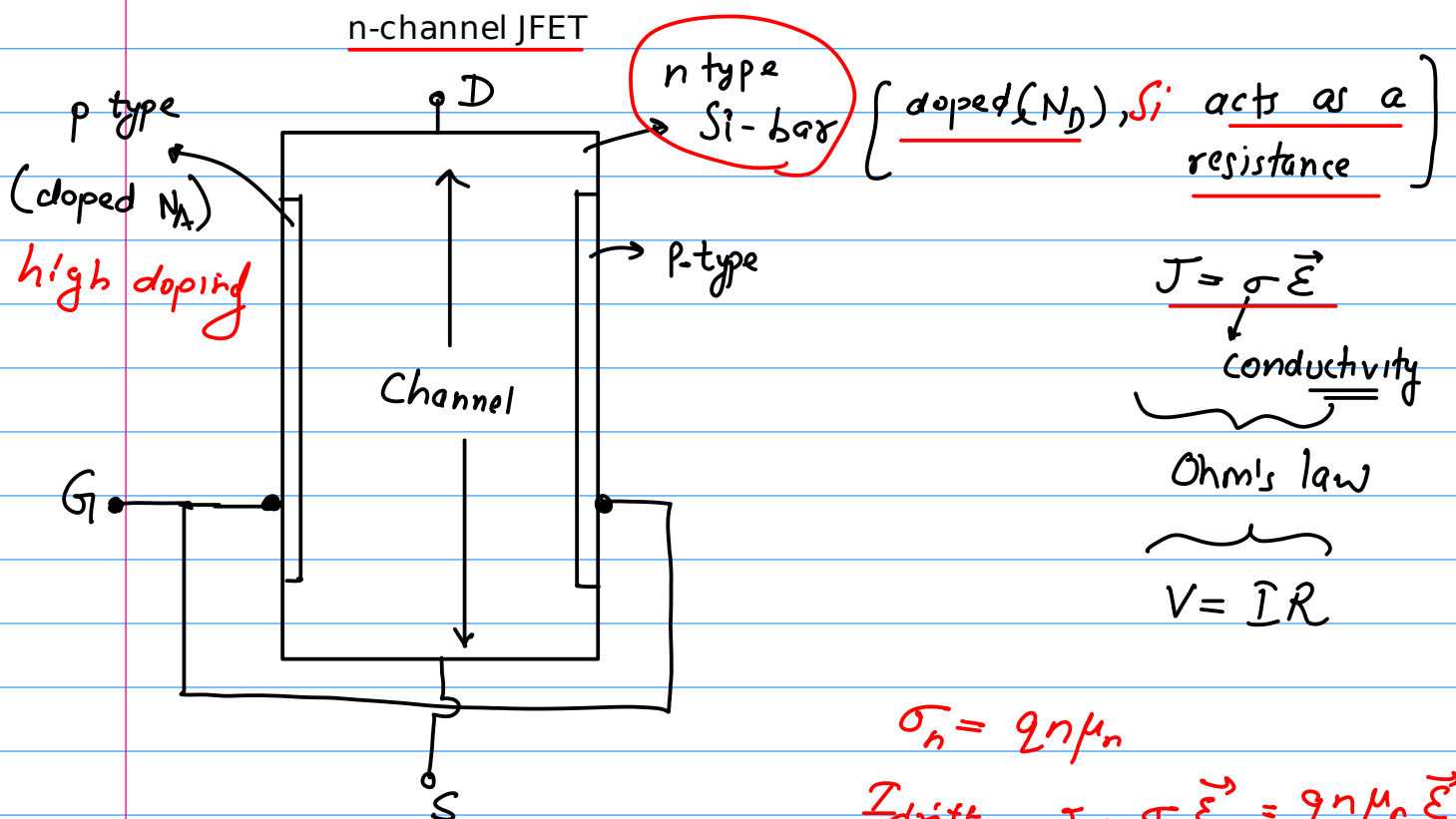

Channel : Undepleted , doped Si region between S & D

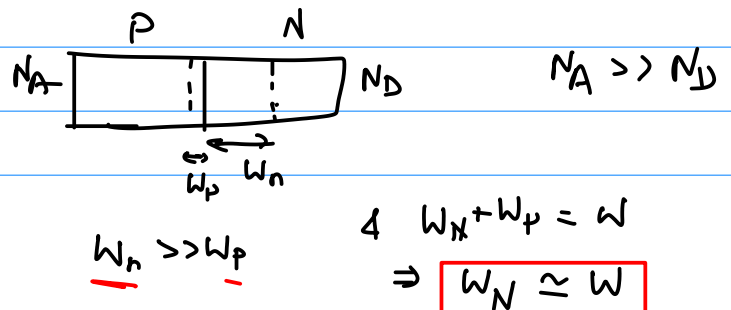$N_A \gg N_D$   
(p<sup>+</sup>)      (n)




Let

$$\begin{cases} V_{DS} > 0 \\ V_{GS} = 0 \end{cases}$$

$$R = \rho \frac{L}{A}$$

$I_D$

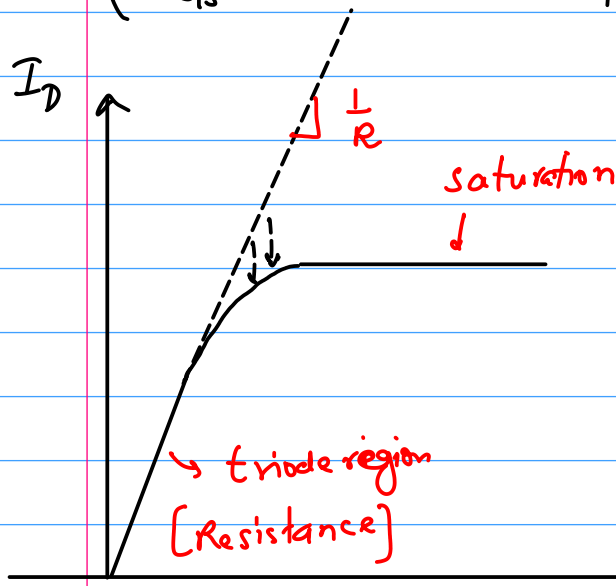

Depletion

$n-Si$

$p^+-Si$

$G$

$$V_{GS} = 0$$

$$V_{DS}$$

$D$

$I_D$

5V

4V

3V

$V(x)$

2V

1V

0V

$I_D$



$S$

5V



$V_{DS}$

$x$

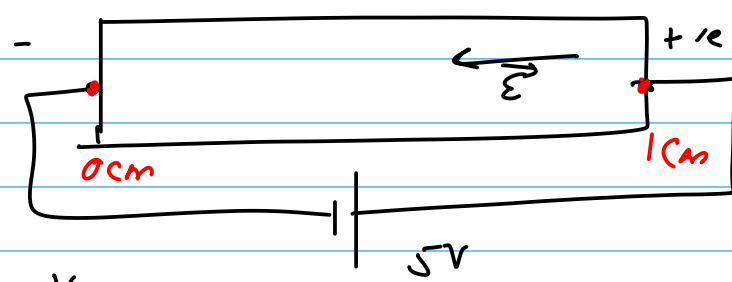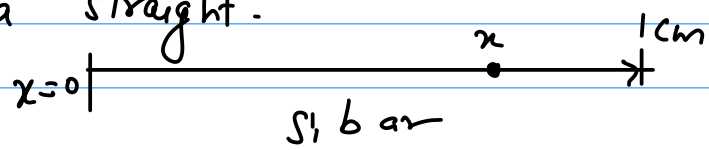c) for  $V_{DS} = \underline{v. small}$ , channel is a resistance (follows Ohm's law) so,  $I_D - V_{DS}$  curve is a straight.



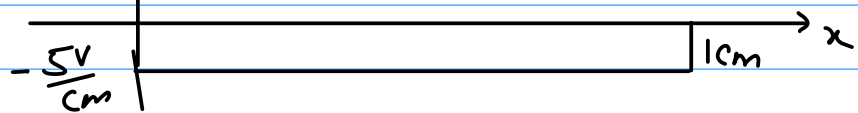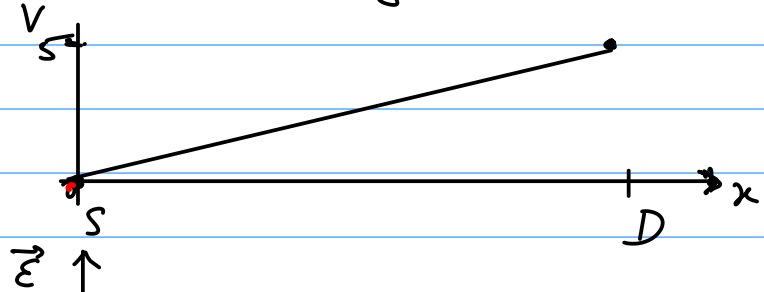$V(x)$  is a straight line  
 $V(x)$  increases as  $x$  increases



$$V_D > V_S$$

$$(V_D - V_G) > (V_S - V_G)$$


$$\Rightarrow V_D - V_G > 0$$

$$V_{DG} > 0$$

370, 156

at any  $x$   $V(x) > 0$

$$V_G = 0 \text{ V,}$$

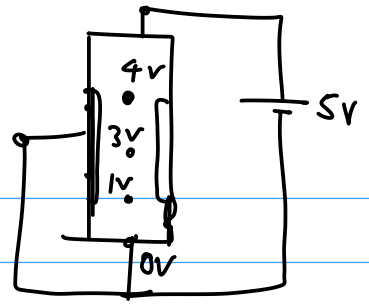

$V(x) - V_G$  increases as  $x$  increases

R.B. vol across the p-n junction



increases  $W$

So, closer to drain  $V(x)$  is more +ve, so, more R.B., more dep. width  $W$

\* If  $V_{DS} \uparrow$ , near D,  $W \uparrow$ , effective channel width  $\downarrow$ .




channel resistance  $\uparrow$

$$R = \rho \frac{L}{a}$$

$$a = \text{channel width} \times \text{thickness}$$

effective channel width

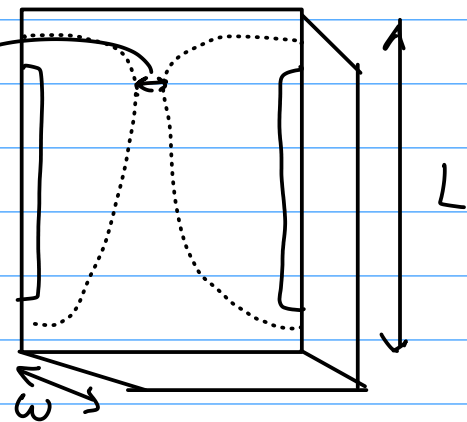


$I_D$  smaller than expected at that  $V_{DS}$

At some  $V_{DS}$

Depletion regions come

in contact\* with each other (Pinch Off)

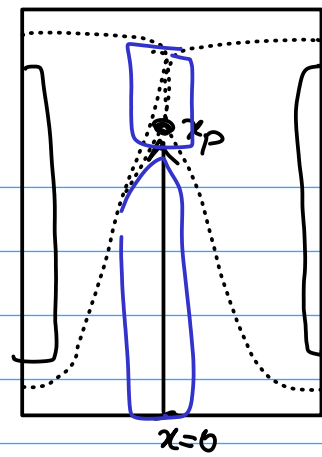effective channel width  $\sim$  v.v. small



$x$

$\sigma = qn$

$n \rightarrow 0$

$\sigma \rightarrow 0$

there should be

No conduction.  $\rightarrow$

$(\sim 0)$

$I_D = 0$

(not actually)

$V(x_p) = V_s = 0$

Vol. no drop in the resistive part

no R.B. at that point  $\rightarrow$  dep. region shrinks back




Dep. doesn't touch each other

So in pinch-off

$(\delta \rightarrow 0)$

there a v.tiny gap b/w the 2 dep regions

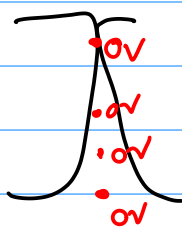


$I \sim 0$

$V \sim 0$


$V(x_p) \sim 0$

$V_{RB} \sim 0 \rightarrow w \downarrow$

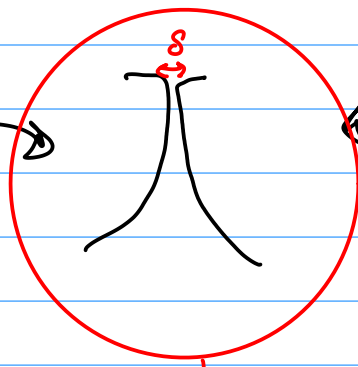

Settling point

Pinch off point

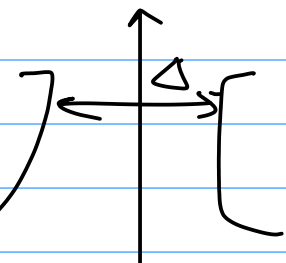

$I$  high


$V(x_p) \uparrow$

$V_{RB} \uparrow$

$w \uparrow, \delta \downarrow$

$V = IR$

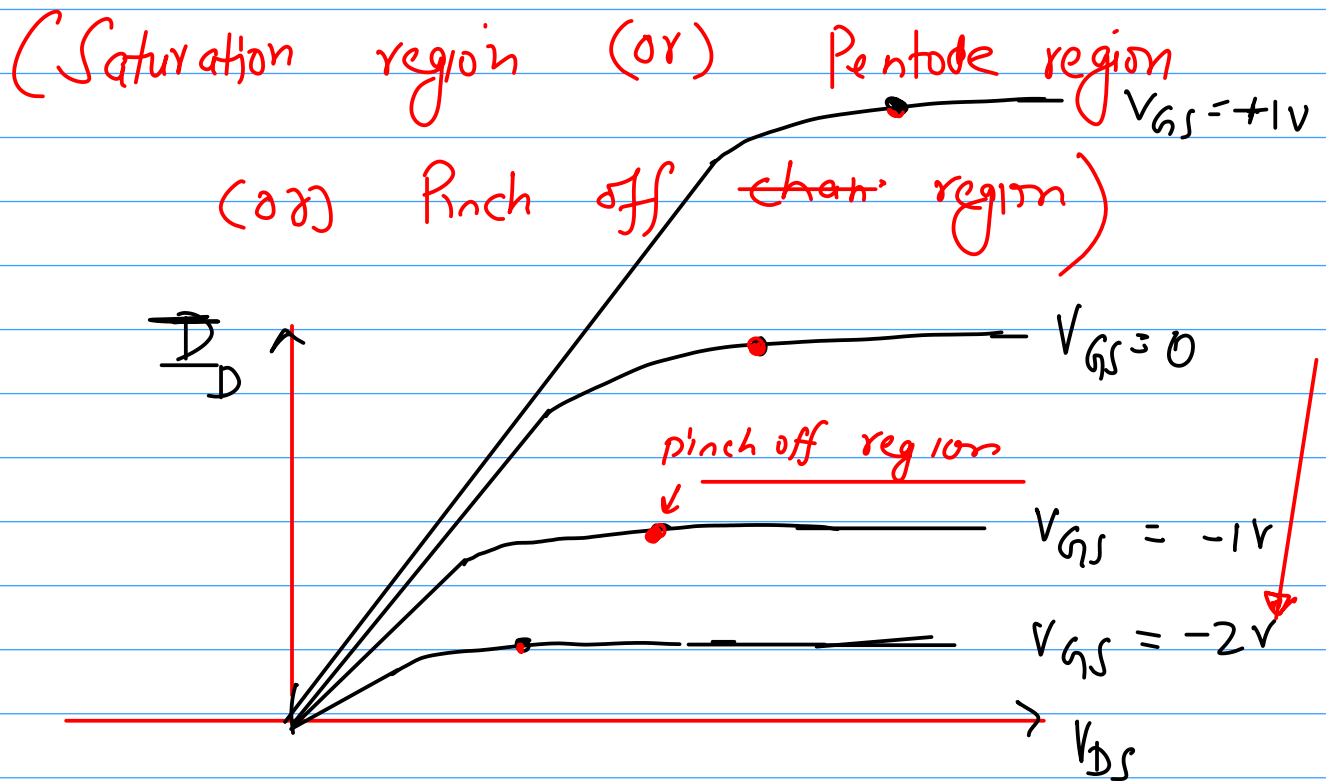\* after pinch off point  $I_D$  no longer increases with  $V_{DS}$




\* Pinch Off Voltage:  $(V_P)$  !  $V_{GS}$  vol. at which channel width becomes 0

(ie. for any  $V_{DS}$  bias,  $\rightarrow 0V$  there is no drain current)

$$\boxed{I_D = 0 \quad \text{at} \quad V_{GS} = V_P}$$

R.B. vol.

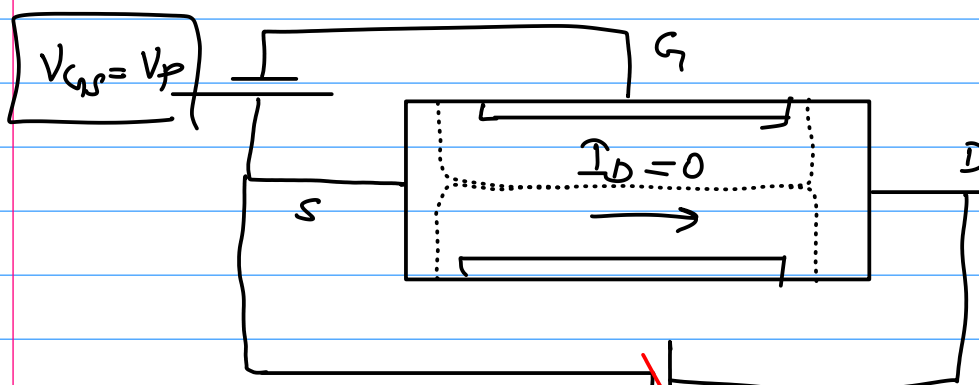So, for n-channel JFET,  $V_P = -ve$  vol.



Cut-off region

$\rightarrow 0V$  or anything


$$W_p \ll W_N$$

$\therefore N_A \gg N_D \rightarrow$  channel doping

$$\underline{W_p \approx W_N}$$

$$\underline{W(x)} = a - b(x) = \sqrt{\frac{2\epsilon}{q} \left( \frac{1}{N_D} \right) \left( \overbrace{V_0}^{V_{\text{barrier}}} - \underline{V(x)} \right)}$$

-ve

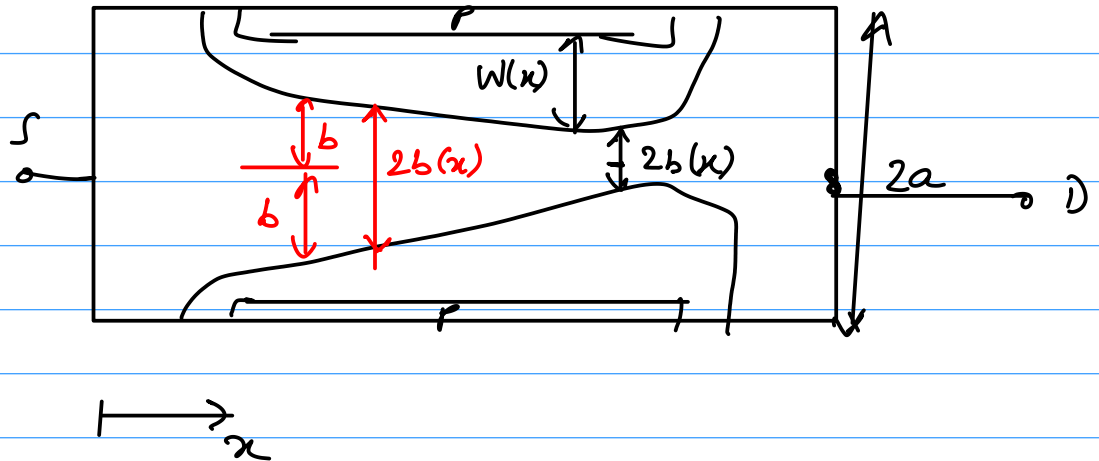

built-in pot.

Let  $|V_0| \ll |V(x)|$

at pinch off vol. ( $V_{GS} = V_p$ ),  $I_D = 0$

$$V(x) = \underline{V}$$

$$\underline{b(x)} = \underline{b} = \underline{0}$$

$$\text{So, } |V_p| = \frac{qN_D}{2\epsilon} a^2$$

$a =$  half width of JFET

Relation between reverse bias gate to source voltage and the effective channel width

2b

$$V_{GS} = \left( 1 - \frac{b}{a} \right)^2 V_p$$

\*  $I_D$  expression in different operating regions :

1) Triode Region: JFET acts a resistance.

drain current is drift current

$$I_D = q A n v_d$$


$2b w$   $\rightarrow$  drift vel

$2b w$

$N_D$   
(uniform doping)

$$v_d = \mu_n \vec{E} = \mu_n \frac{V_{DS}}{L}$$

mobility

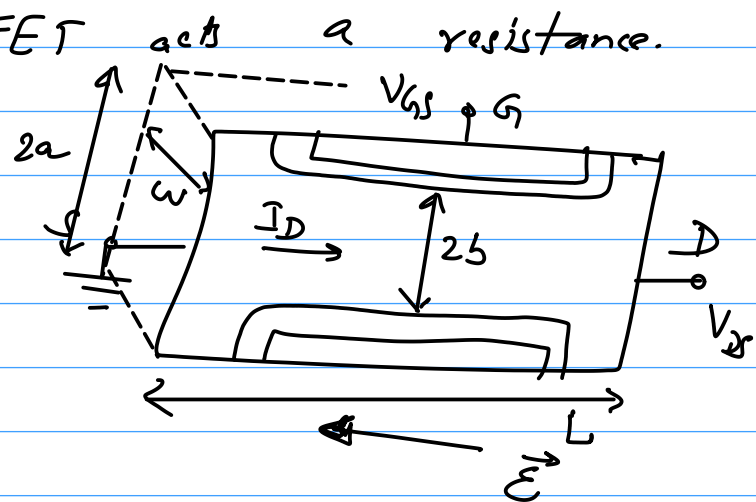

for low  $V_{DS}$

$$I_D = 2b w q N_D \mu_n \frac{V_{DS}}{L}$$

$$I_D \propto V_{DS}$$

[Ohm's Law]

for low  $V_{DS}$  (proper or deep triode region),

$b \sim a$  (low depletion)

$$r_{D,ON} = \frac{L}{2a w q N_D \mu_n}$$


$\rightarrow$  for  $V_{GS} = 0$

(from  $V_{GS} = (1 - \frac{b}{a})^2 V_P$ )

Replacing  $b$  in  $I_D$  expression

$$I_D = \frac{2a\omega q N_D \mu_n}{L} \left[ 1 - \left( \frac{V_{GS}}{V_P} \right)^{\frac{1}{2}} \right] V_{DS}$$

$I_D \propto V_{DS}$   
(Ohm's law)

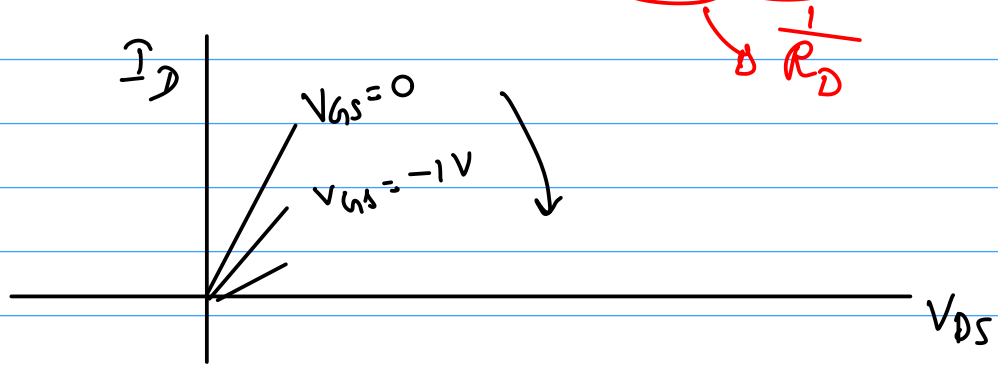


\* ~~Pinch off region~~ : (Saturation region)


here, ideally  $I_D$  is independent of  $V_{DS}$

$$\underline{I_{DS}} = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_P} \right]^2$$

saturation

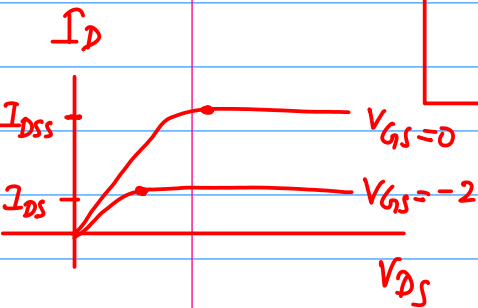

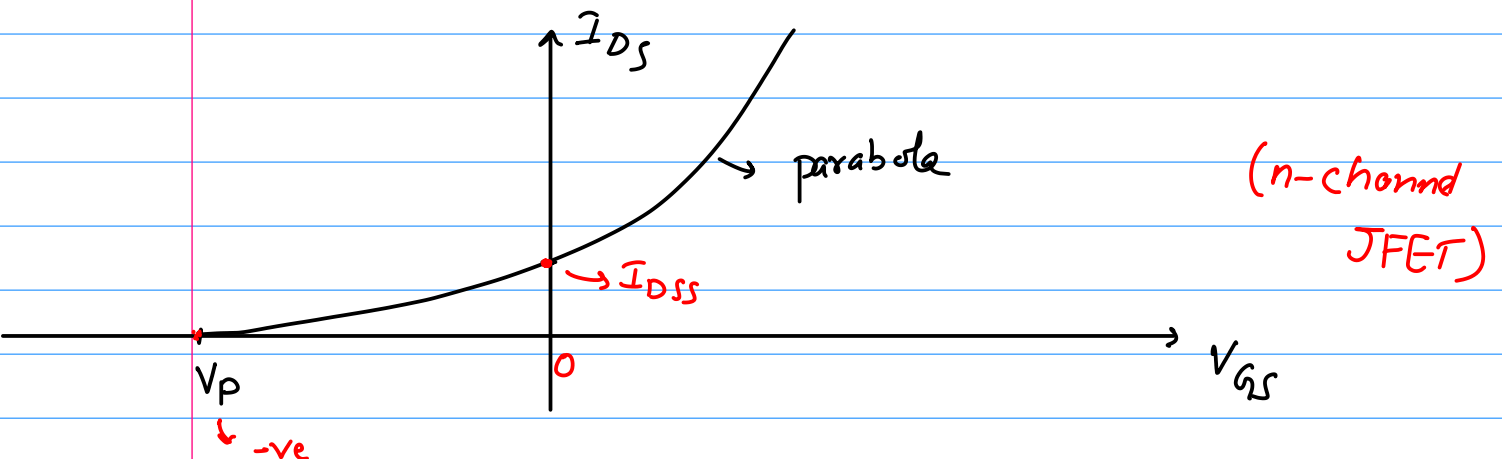$I_{DSS}$  is saturation drain current  
when  $V_{GS} = 0$





Cut-off :

$$\underline{V_{GS} = V_P}$$

$$I_D = 0$$

↓  
negligible

$$|V_{GS}| > |V_P|$$

→ Small signal model :




AI

total  $\leftarrow i_D = f(V_{GS}, v_{DS})$

$$\Delta i_D = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{DS}} \Delta v_{GS} + \left. \frac{\partial i_D}{\partial v_{DS}} \right|_{v_{GS}} \Delta v_{DS}$$

small signal

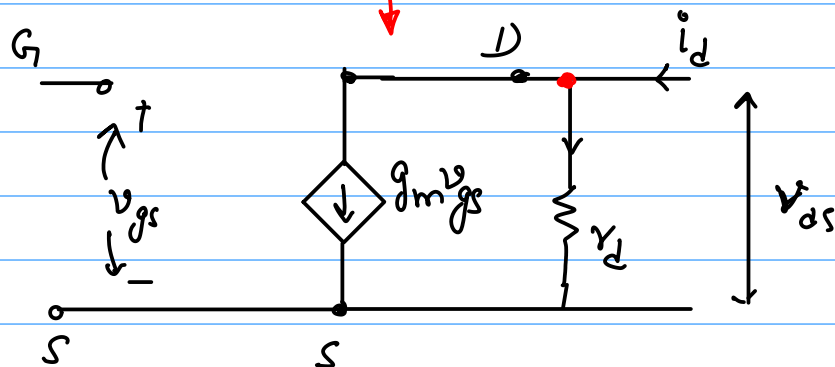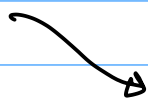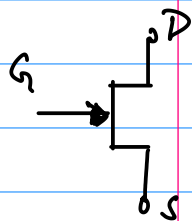
$$i_d = g_m v_{gs} + \frac{1}{r_d} v_{ds}$$



Low Frequency Small signal model

G-S is R.B.  $J^n \rightarrow$  v.v. high resistance  $\equiv$  Open ckt.

high freq. small signal model

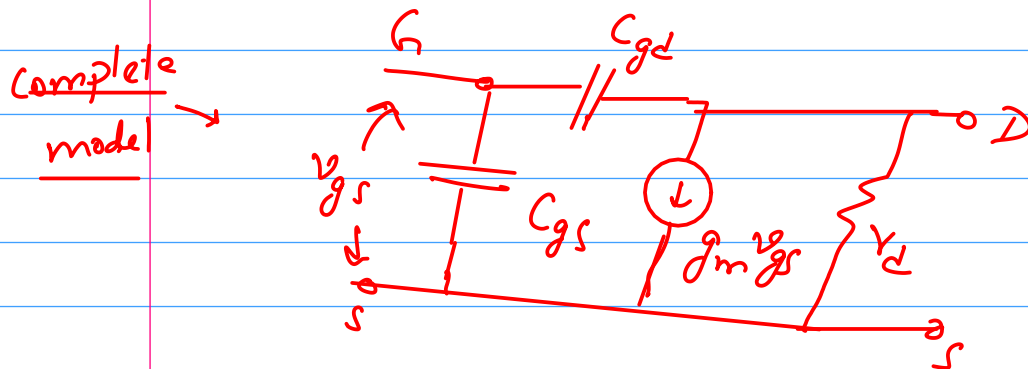

at low freq. cap → O.C.

\* Transconductance:

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{DS}}$$

$$I_{DS} = I_{DSS} \left[ 1 - \frac{v_{GS}}{V_P} \right]^2$$

$$g_m = -\frac{2}{V_P} \sqrt{I_{DSS} I_{DS}} \rightarrow \text{n-channel}$$

$$g_m = g_{m0} \left[ 1 - \frac{v_{GS}}{V_P} \right]$$

$g_{m0}$  is trans-  
cond. when  
 $v_{GS} = 0$

where

$$g_{m0} = \frac{-2 I_{DSS}}{V_P} \rightarrow \begin{matrix} +ve \\ -ve \text{ for n-channel} \end{matrix}$$


\*  $I_{DSS}$  and  $V_P$  always have opposite signs. So,  $g_{m0}$  will always be positive

o/p resistance  $r_d = \left. \frac{\partial v_{ds}}{\partial i_{ds}} \right|_{v_{gs}} = \left. \frac{v_{ds}}{i_d} \right|_{v_{gs}}$

Amplification factor,  $\mu = - \left. \frac{\partial v_{ds}}{\partial v_{gs}} \right|_{I_D}$

$$\mu = - \left. \frac{v_{ds}}{v_{gs}} \right|_{I_D}$$

$$\mu = g_m r_d$$

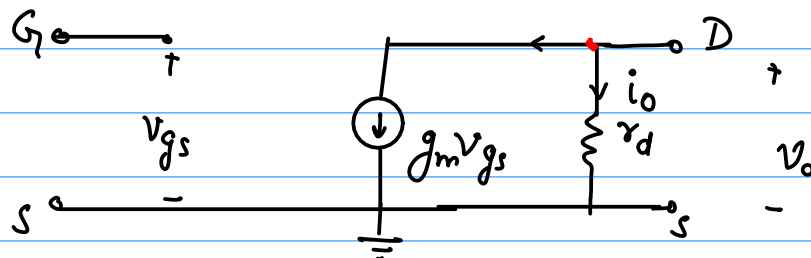

If no load is connected :-

$$v_o = v_{ds} = i_o r_d$$


$$i_o = -g_m v_{gs}$$

$$v_o = -g_m v_{gs} r_d$$

$$A_v = \frac{v_o}{v_{gs}} = -g_m r_d$$

for common source  
JFET amp.  
=

## Thevenin's Theorem :

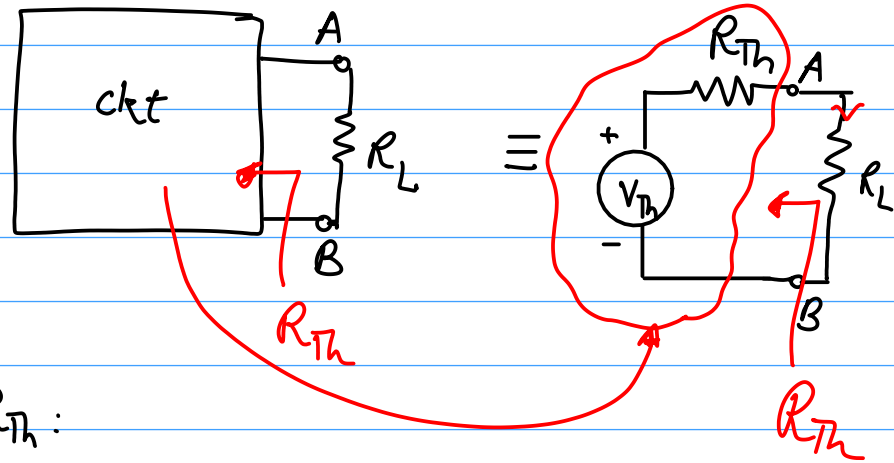

To find  $R_{Th}$  :


- (1) Remove the external load.
- (2) Replace all indep. sources by their internal (source) resistance :




→



→

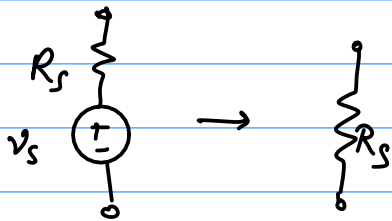

→

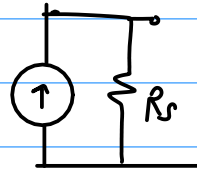

→




- (3) Find the equivalent resistance <sup>(Req)</sup> across the output terminals (A & B)

$$R_{Th} = R_{eq}$$

→ To find  $V_{Th}$  :


- (1) Step 1 is same as above
- (2) Find the net vol. across the 2 output terminals (A, B). So,  $V_{AB} = V_{Th}$

## BJT CE amp:

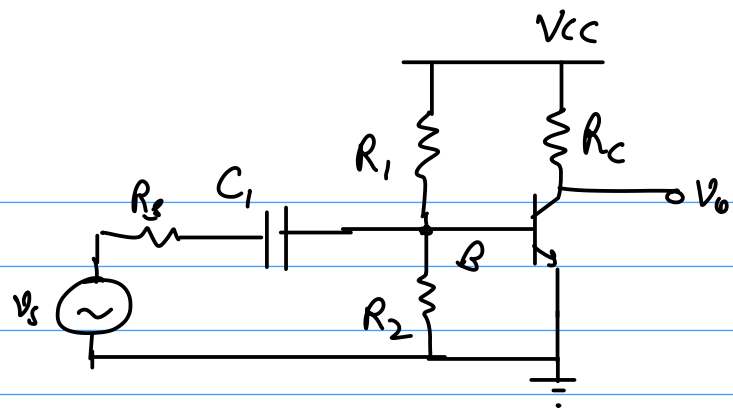


for DC:

$C_1 \rightarrow \text{O.C.}$

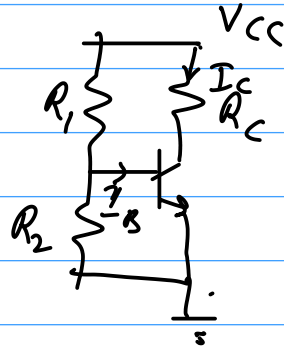

Assumption - High  $\beta'$ . v. low  $I_B$ . (neglect)


then  $R_1$  &  $R_2$  are in series.

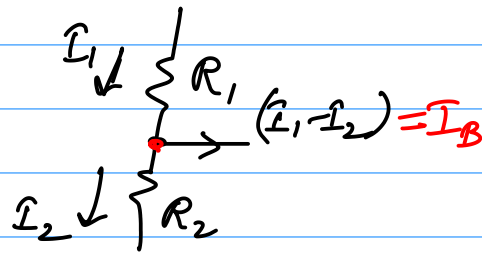

$R_1$  &  $R_2$  Not in series


But if  $I_1 - I_2 = I_B$   
is negligible

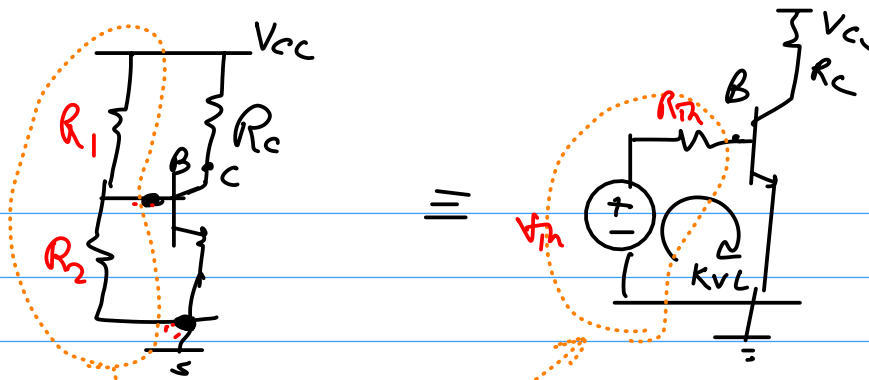then  $R_1$  &  $R_2$   
have roughly same  
current  
They can be considered  
to be in series



$$V_{Th} = \frac{R_2}{R_1 + R_2} V_{cc}$$


$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2}$$

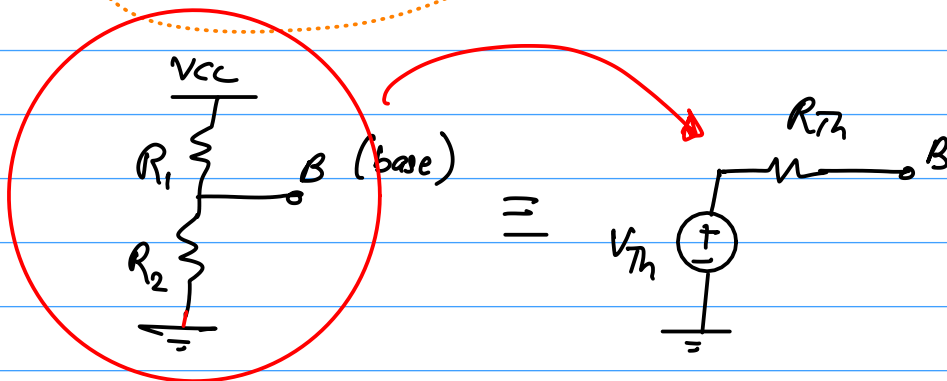

BJT is the load to this network.


(1) So remove the BJT

(2) S.C.  $V_{cc}$

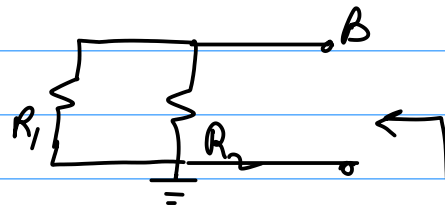


$$R_{eq} = R_{Th} = R_1 \parallel R_2$$

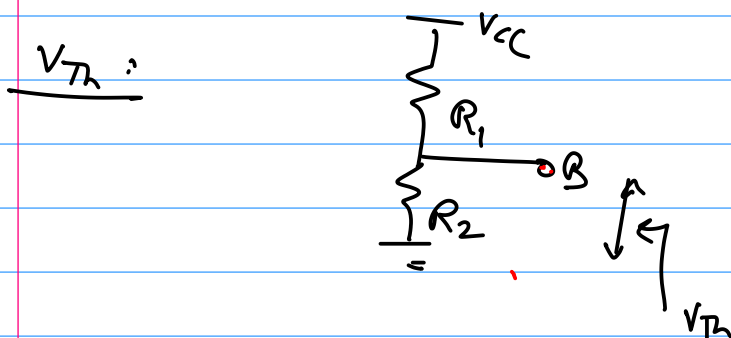
(3) 
$$R_{Th} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$


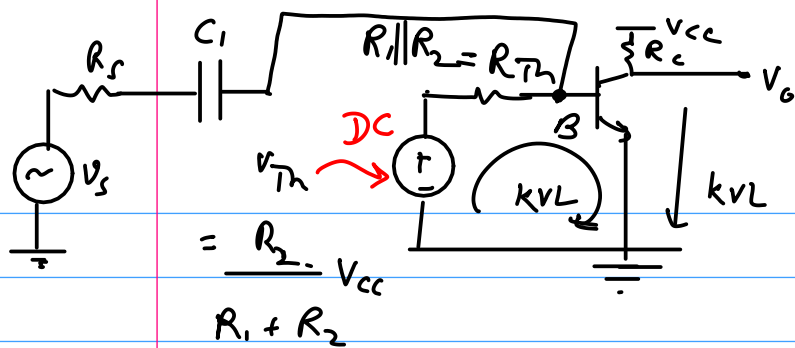
$$V_{Th} = \frac{R_2}{R_1 + R_2} V_{cc}$$




↓ Small signal (low freq.)

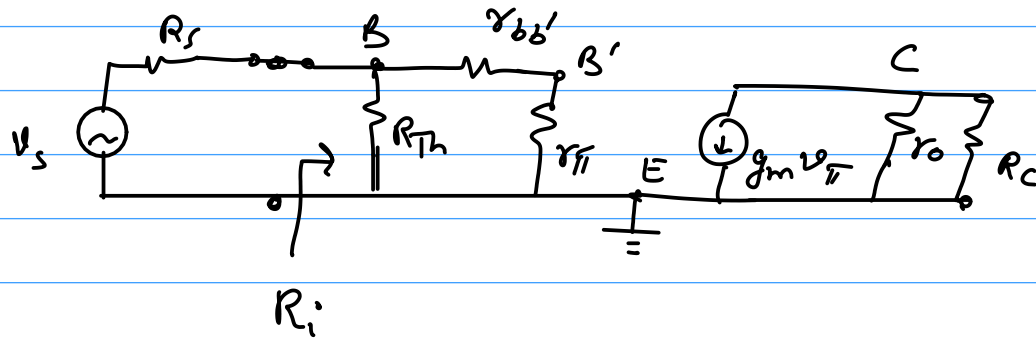


Common Source:

In saturation,  
G<sub>1</sub> junction is

$\frac{R_1 R_2}{R_1 + R_2} \approx 0$

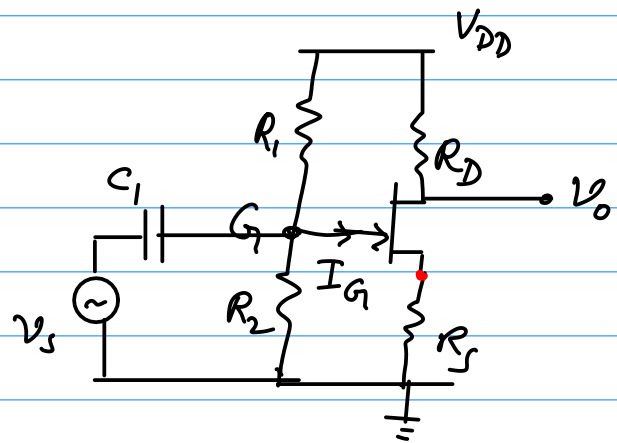


So  $R_1$  &  $R_2$  are in series.

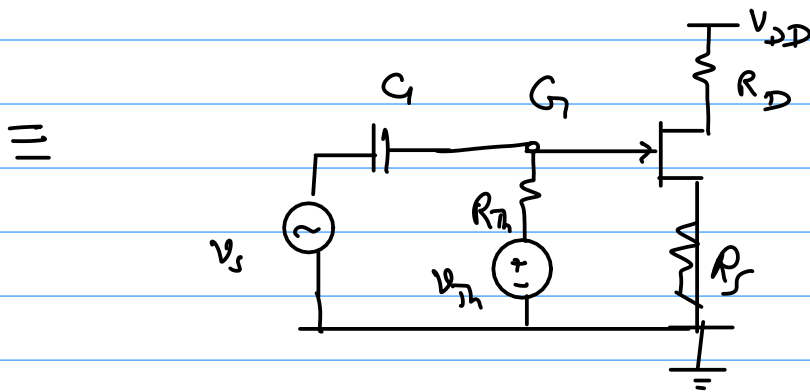

$$R_{Th} = R_1 || R_2$$

$$V_{Th} = \frac{R_2}{R_1 + R_2} V_{DD}$$

DC analysis -  $C_1 \rightarrow O.C.$

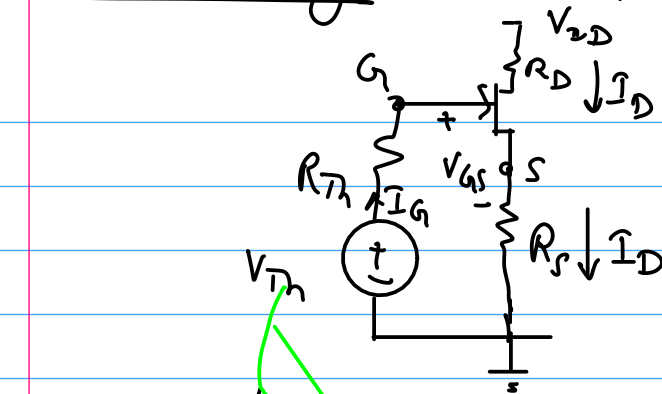

i/p KVL -


$$V_{Th} - I_G R_{Th} - V_{GS} - I_D R_S = 0$$

$$V_{GS} = V_{Th} - I_D R_S$$

O/p KVL -


$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$
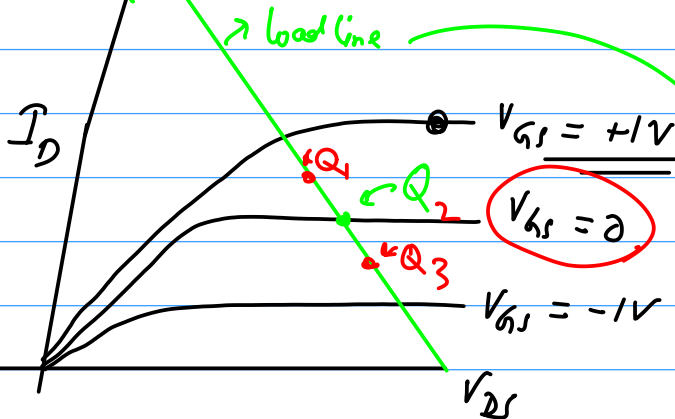
$$I_D = \frac{V_{DD} - V_{DS}}{R_D + R_S}$$



$$I_D = \underbrace{I_{DSS}}_{\text{(saturation)}} = \underbrace{I_{DSS}}_{\text{given}} \left[ 1 - \underbrace{\frac{V_{GS}}{V_P}}_{\text{given}} \right]^2$$

Small signal -

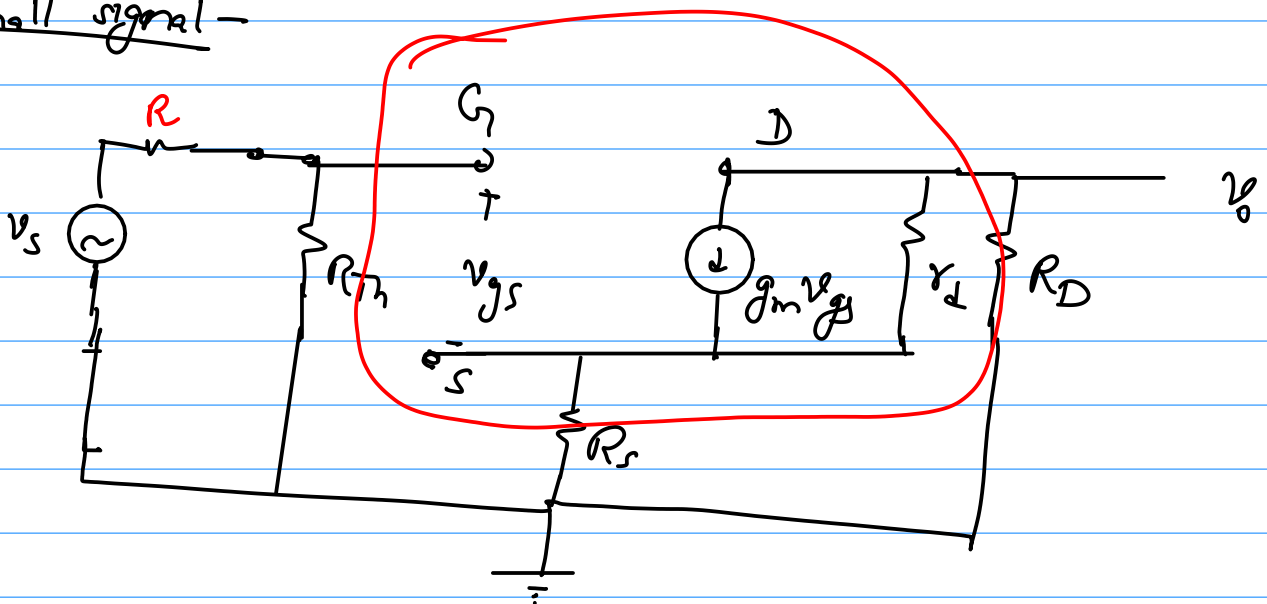

HW: MOSFET

Depletion

Enhancement

