

Feedback Amplifiers

UNIT IV

Why Feedback Amplifiers?

The gain of a **common source** amplifier = $g_m R_D$

The gain of a **common emitter** amplifier = $g_m R_C$

g_m = transconductance

- (1) Ambient temperature changes
- (2) Parameter variations



g_m , R_C and R_D
changes



Gain changes


The aim is to make the **gain less sensitive** to temperature and other device parameter variation.

For this, feedback is used in amplifiers

Feedback Amplifiers - Introduction

What is an amplifier?

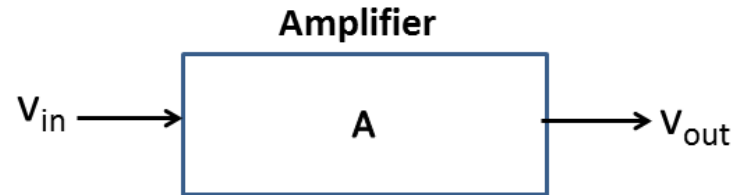It is a circuit that amplifies (increases the strength of) the input signal.




$$A = V_{out} / V_{in}$$

$$V_{out} = A V_{in}$$

What is feedback ? What is meant by feedback? Define feedback


- ❖ In the field of electronics, **feedback** is a process (method) in which a portion (fraction, part) of the output signal (which may be voltage or current) is returned (fed back) to the input.
- ❖ **Feedback** can be applied to amplifier circuits to **modify** their performance characteristics such as **gain**, **bandwidth**, input and output resistance etc
- ❖ **Feedback** is the fundamental concept in the design of a stable amplifier and an unstable oscillator circuit.

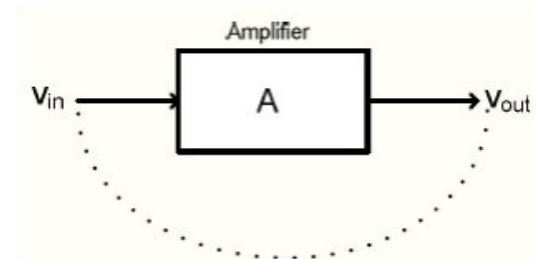

Feedback Amplifiers - Introduction





What is feedback amplifier?

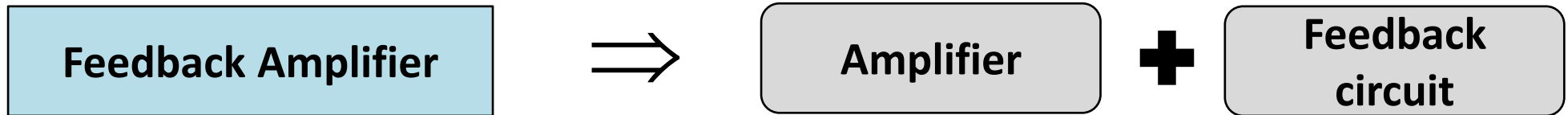- ❖ Feedback amplifier is an amplifier in which a feedback path exists from output to input.
- ❖ A feedback amplifier consists of (contains) two parts: an amplifier and a feedback circuit.



- ❖ The purpose of feedback circuit is to return a fraction of the output voltage to the input of the amplifier.
- ❖ In a feedback amplifier, a fraction (portion) of the output signal is fed back to the input.

Feedback Amplifiers - Introduction

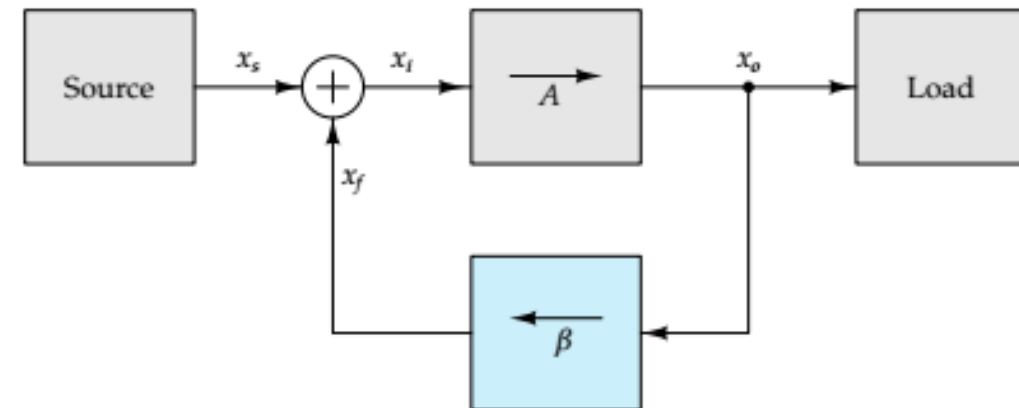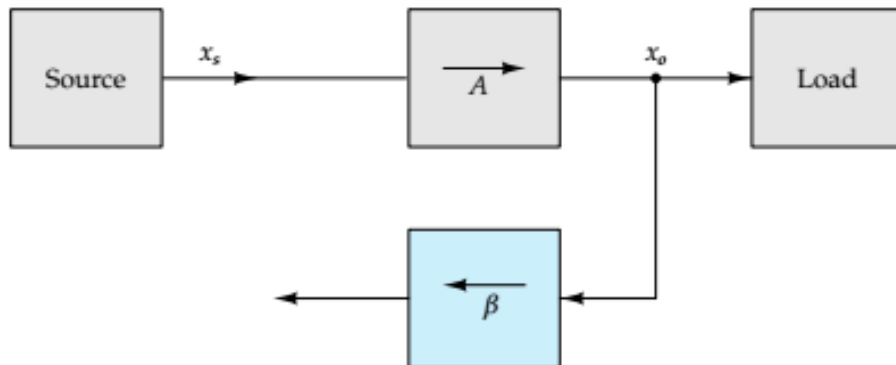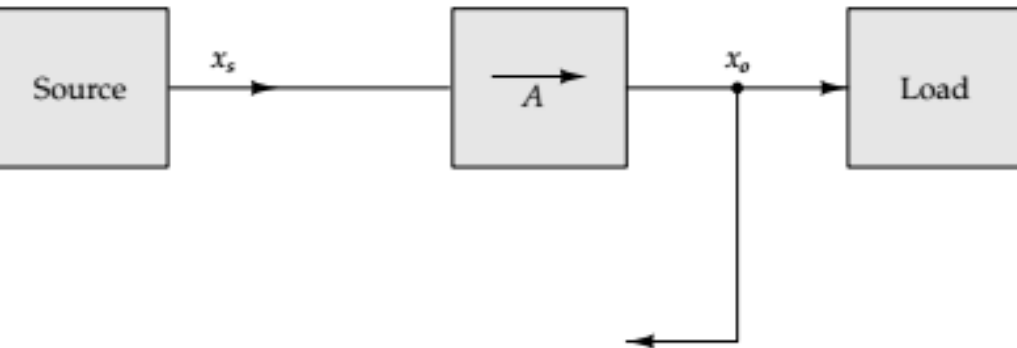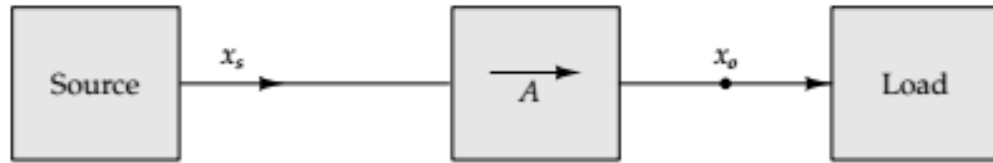

Feedback Amplifier: Block diagram


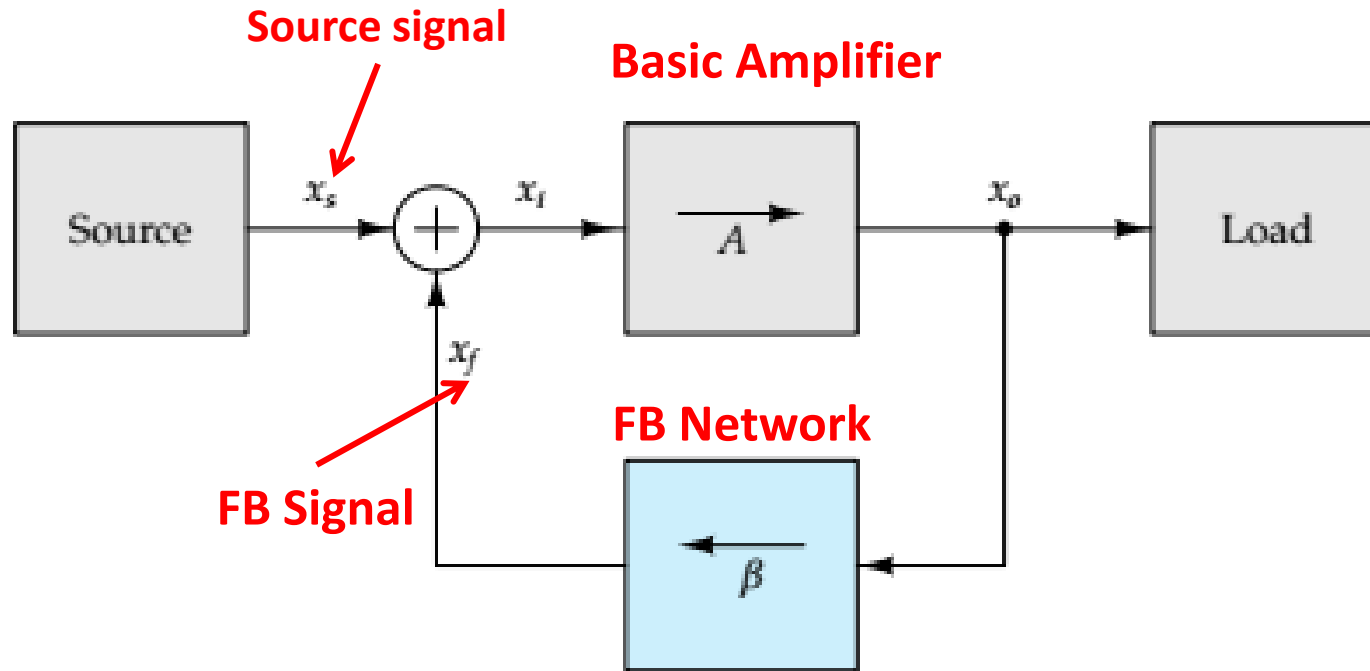


Figure: Block diagram of a feedback amplifier

Another name feedback amplifier

- ❖ A **feedback amplifier** is sometimes referred to as a **Closed-Loop amplifier** because the feedback forms a closed loop between the input and output.

Nomenclature

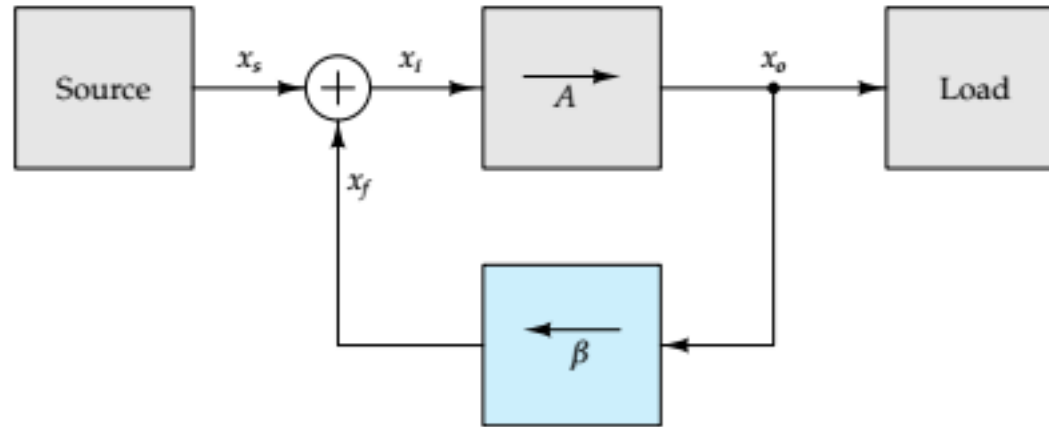

A: Gain without feedback (Open-loop gain)

A_f : Gain with feedback (closed-loop gain)

β : Feedback factor

$A\beta$: Loop gain

$1 + A\beta$: Amount of feedback

Types of Feedback

The feedback can be classified into two types:

(1) **Negative feedback** (2) **Positive feedback**

■ Negative feedback

- ❖ If the feedback signal applied to the input is out of phase with the input signal (i.e., feedback signal is 180° out of phase with the input signal), then the feedback is called negative Feedback.
- ❖ The polarity of the feedback signal is opposite that of the input signal.
- ❖ Negative feedback is also known as **degenerative feedback** because it degenerates (or reduces) the output signal
- ❖ **In the negative feedback**, the feedback signal is **subtracted** from the source signal. So, the feedback signal **reduces** the strength of the input signal that appears at the input of the basic amplifier. i.e. the feedback signal **opposes** the source signal.
- ❖ **Negative feedback** concept is used in **amplifiers**.

Negative Feedback Amplifier: Block diagram

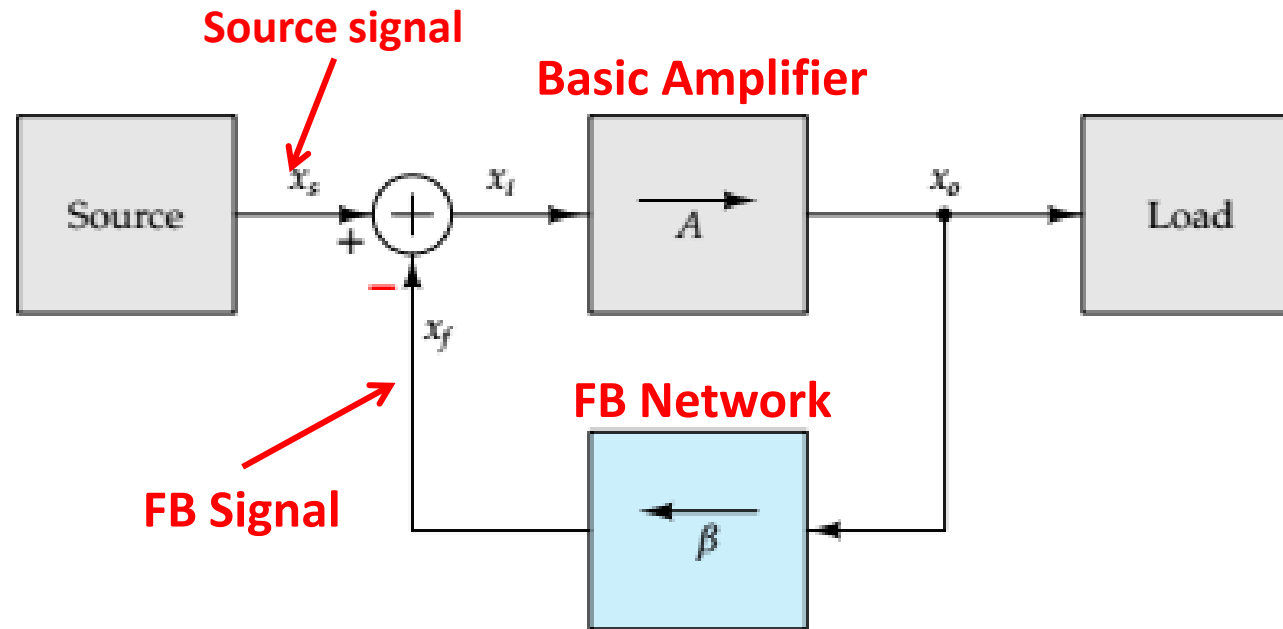


Figure: Block diagram of a negative feedback amplifier

Positive Feedback

- ❖ If the feedback signal applied to the input is in phase with the input signal, then the feedback is called **positive Feedback**.
- ❖ The polarity of the feedback signal is same as that of the input signal.
- ❖ Positive feedback is also known as **regenerative feedback** because it increases the output signal
- ❖ **In the positive feedback**, the feedback signal is **added to** the source signal. So, the feedback signal **increases** the strength of the input signal that appears at the input of the basic amplifier. i.e. the feed back signal **aids** the source signal.
- ❖ **Positive feedback** concept is used in **oscillators**

Positive Feedback Amplifier: Block diagram

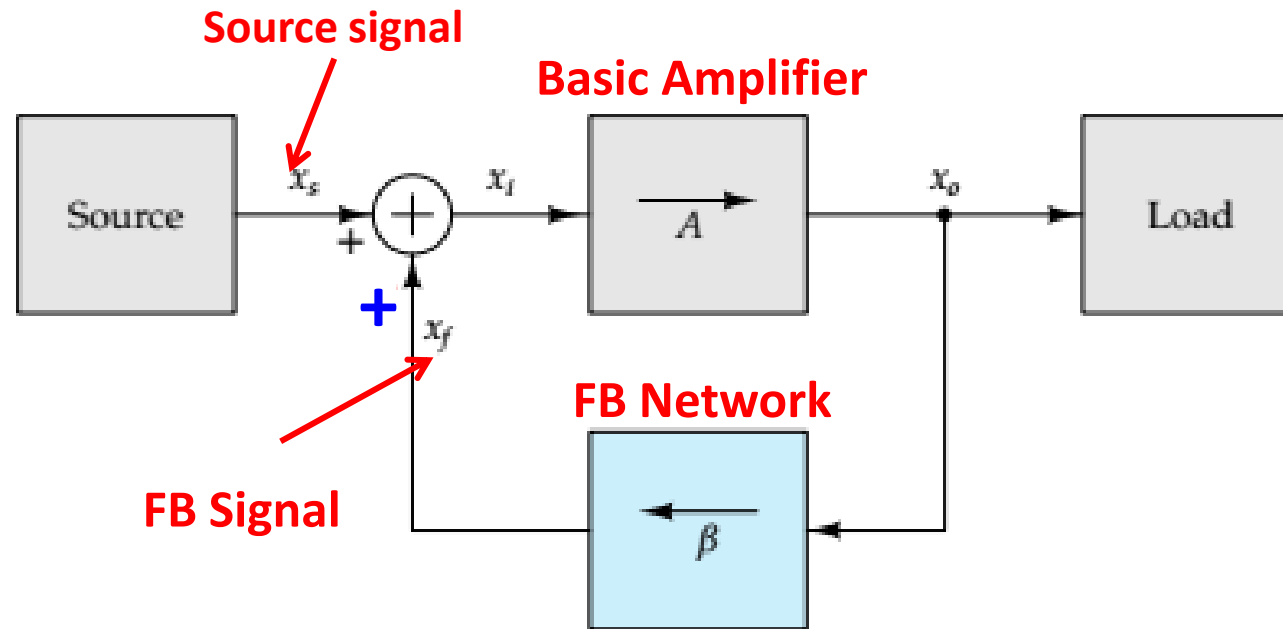


Figure: Block diagram of a positive feedback amplifier

Voltage gain with negative feedback

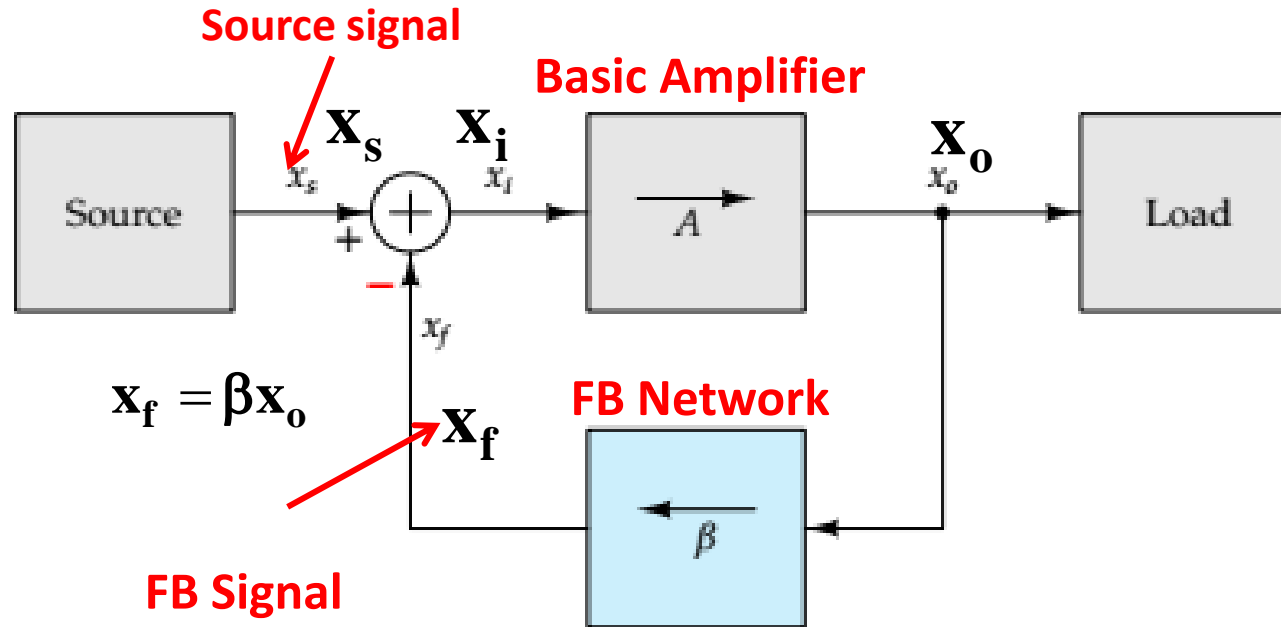


Figure: Block diagram of a **negative** feedback amplifier

❖ The x signals can be voltage or current

Without feedback

The gain of an amplifier (A) without feedback is given by

$$A = \frac{x_o}{x_s} = \frac{x_o}{x_i} \quad [1]$$

With feedback

For a negative feedback, the input to the amplifier is

$$x_i = x_s - x_f \quad \Rightarrow \quad x_s = x_i + x_f$$

The gain of the amplifier with feedback is

$$A_f = \frac{x_o}{x_s}$$

$$A_f = \frac{x_o}{x_i + x_f}$$

But the feedback signal is

$$x_f = \beta x_o$$

$$A_f = \frac{x_o}{x_i + \beta x_o} \quad [2]$$

From (1), we get

$$x_o = Ax_i \quad [3]$$

Substituting (3) in (2), we get

$$A_f = \frac{Ax_i}{x_i + \beta Ax_i}$$

This can be written as

$$A_f = \frac{A}{(1 + A\beta)}$$

- ❖ In the case of negative feedback, the gain of the feedback amplifier (A_f) is smaller than the open-loop gain (A) by a factor of $(1+A\beta)$

If $A\beta \gg 1$, then the above equation becomes

$$A_f \cong \frac{A}{A\beta} \cong \frac{1}{\beta}$$

- ❖ It means that the **gain of the feedback amplifier** is almost entirely determined by the **feedback network**.
- ❖ In other words, the overall gain will have **very little dependence** on the gain of the basic amplifier.
- ❖ The gain A is usually a function of
 - (1) Ambient temperature changes
 - (2) Device parameter variations
- ❖ Thus closed-loop gain would be **more stable** and is nearly independent of changes of open-loop gain.

Some properties of Negative feedback

Advantages of Negative feedback

- It helps to **stabilize the gain**
- It **increases bandwidth** [Bandwidth of amplifier with feedback is greater than bandwidth of amplifier without feedback].
- It **reduces distortions**
- It improves the linearity of operation
- It improves the **signal to noise ratio (SNR)**.
- It improves the **input resistance and output resistance**

Disadvantages of Negative feedback

- ❖ **It reduces the gain of the circuit.**

$$A_f = \frac{A}{(1 + A\beta)}$$

Some properties of **positive feedback**

Advantages of Positive feedback

- **It increases the gain of the amplifier** (It is used to increase the gain of the signal.

When the input signal strength is very weak and if we want to increase its strength, we go for a carefully designed positive feedback amplifier.

- **It is used to produce oscillation.**


Disadvantages of Negative feedback

- It **reduces the bandwidth**
- It **reduces the stability of the gain.**

Feedback Topologies (Feedback Configurations)

Based on the **input signal** (voltage or current) and on the **output signal** (voltage or current), amplifiers can be classified into four categories.

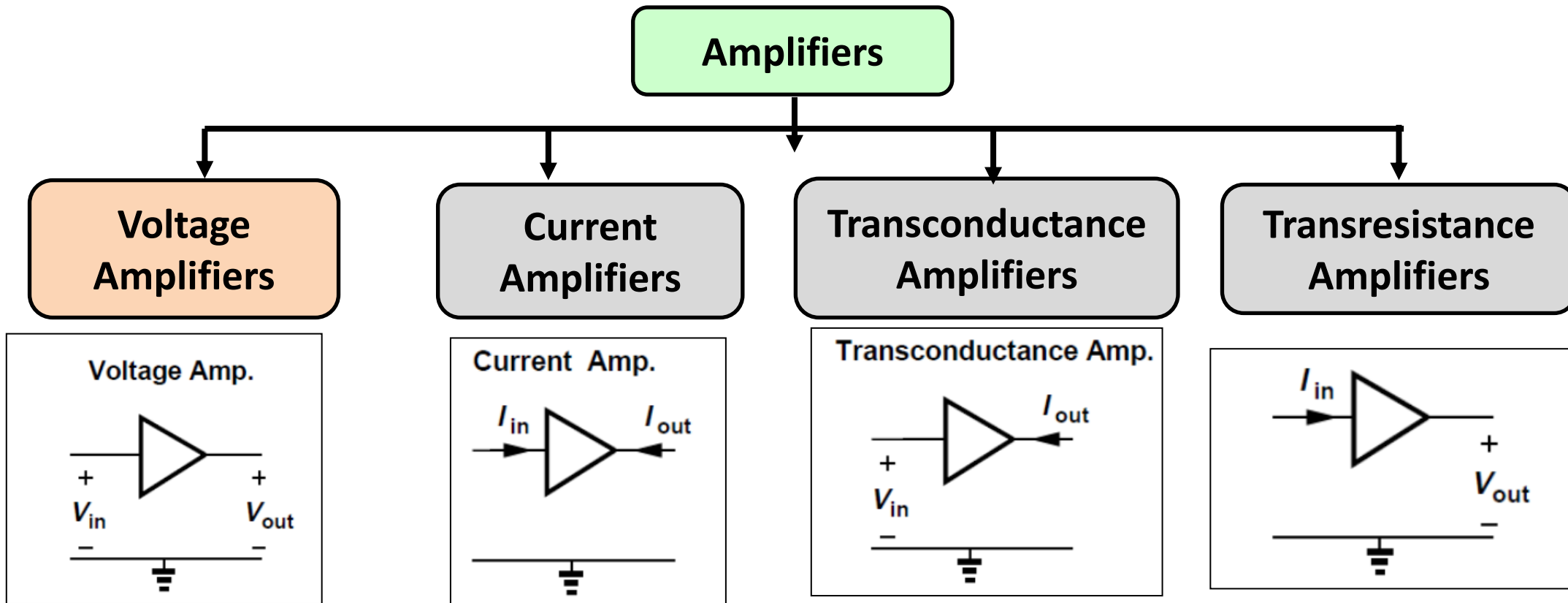1. **Voltage** amplifiers
2. **Current** amplifiers
3. **Transconductance** amplifiers
4. **Transresistance** amplifiers



Feedback in electronics

NOTE

How to measure voltage and current?


Voltage is measured with *voltmeters*

- Voltmeters are **connected in parallel** to the circuit

Current is measured with **ammeters**

- Ammeters are **connected in series** to the circuit

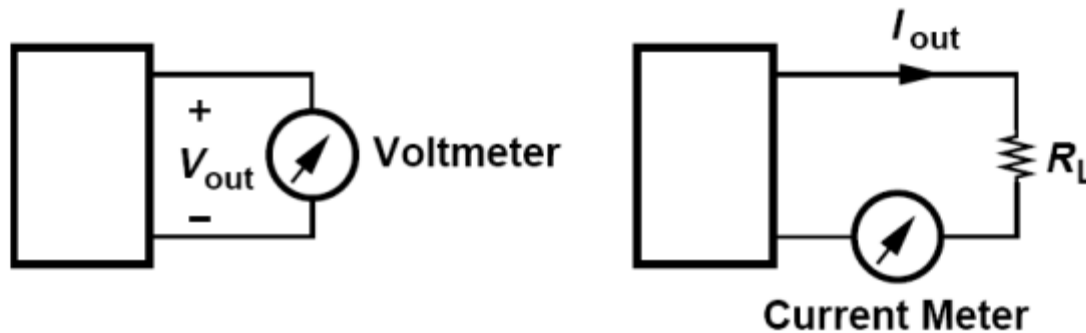- How do we sense a voltage or a current?





To sense a **voltage**, we place a voltmeter in **parallel**.

To sense a **current**, current meter is inserted in **series** with the signal

How to ADD voltage and current?

- Voltages are added by connecting voltage sources in series
- Currents are added by connecting current sources in parallel (“shunt”)

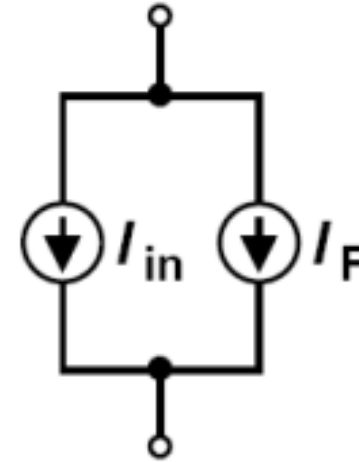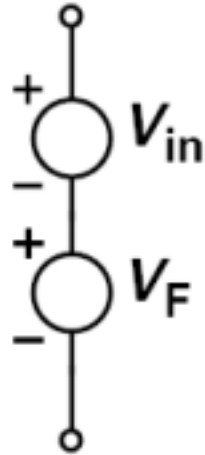How do we add two voltages or two currents?



- Voltages are added in series

- Currents are added in parallel

Feedback in electronics

NOTE

- **measure** the output:

Voltage

or

Current

- “**mix**” (feed back) the signal to the input as:


Voltage

or

Current

Feedback Voltage Amplifier

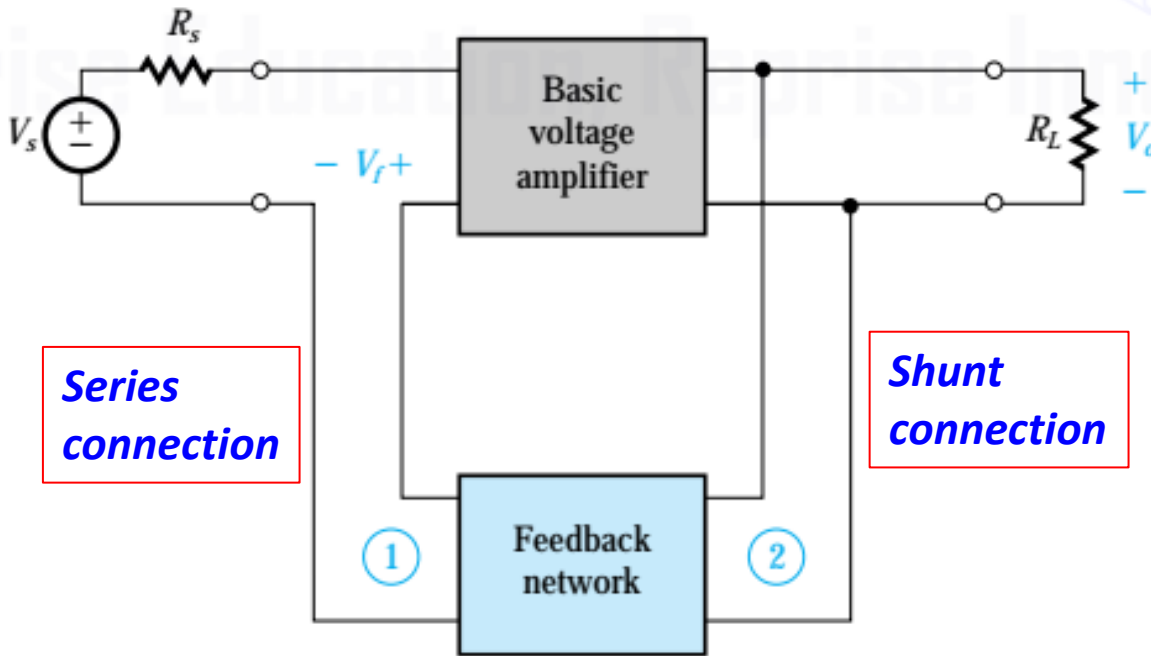Input signal: Voltage
Output Signal: Voltage



Here, the output voltage is sensed (**sampled**). The feedback signal (voltage) is **mixed** with the source voltage.


The suitable feedback topology for the voltage amplifier is the **voltage-mixing, voltage-sampling**

Because of the **series connection at the input** and the **parallel or shunt connection at the output**, this feedback topology is also known as **series-shunt feedback** topology.

Block diagram of a **feedback** voltage amplifier.

“series-shunt” feedback

“series-shunt” feedback

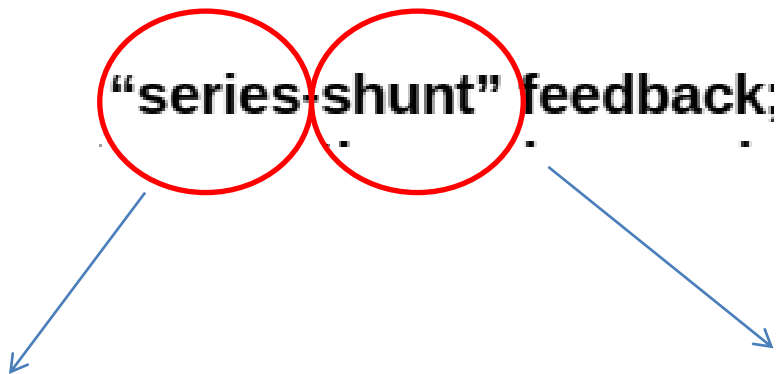


First term refers to connection at the amplifier input

Second term refers to the Connection at the amplifier output

- Feedback topologies are named according to the connections: eg “series-shunt feedback” means series connection at the input and shunt connection at the output


Feedback Voltage Amplifier

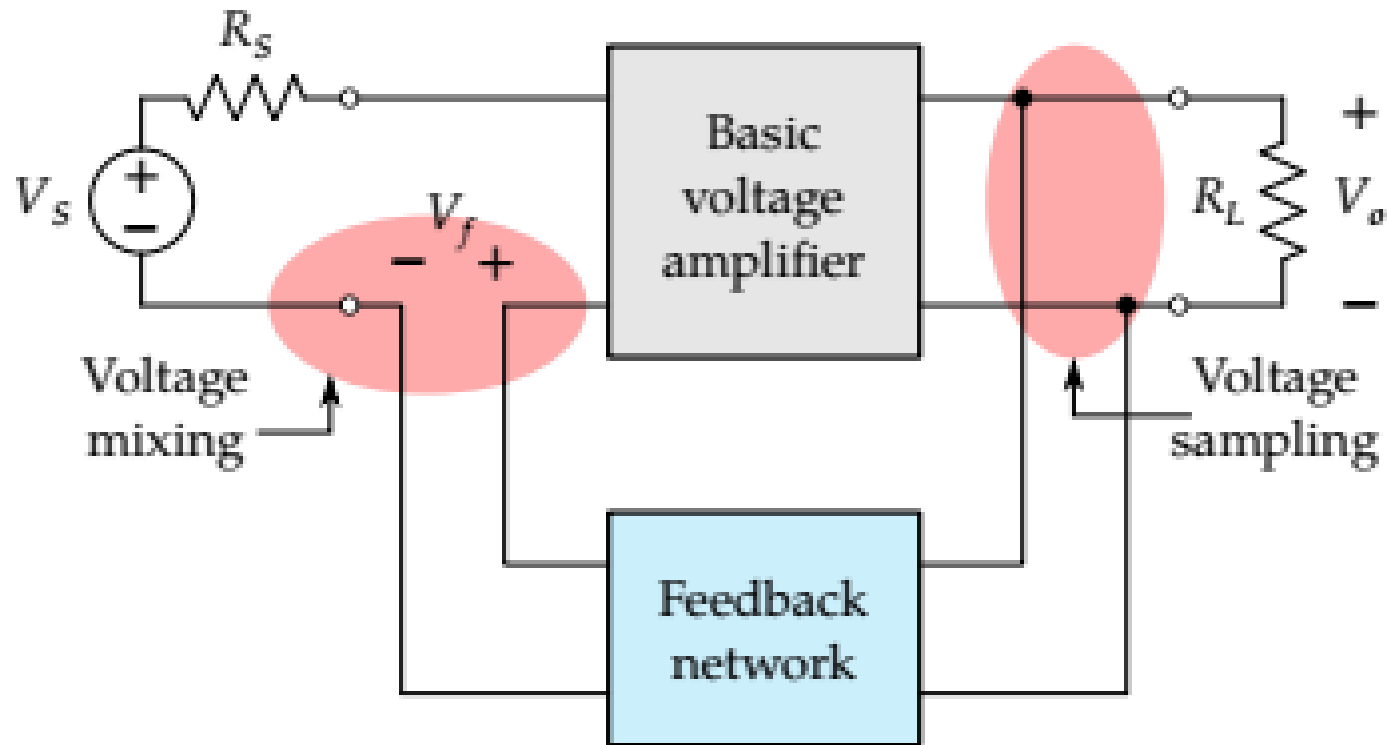

- Here, **voltage mixing** and **voltage sampling** are highlighted by the pink color shaded regions.

Feedback Current Amplifier

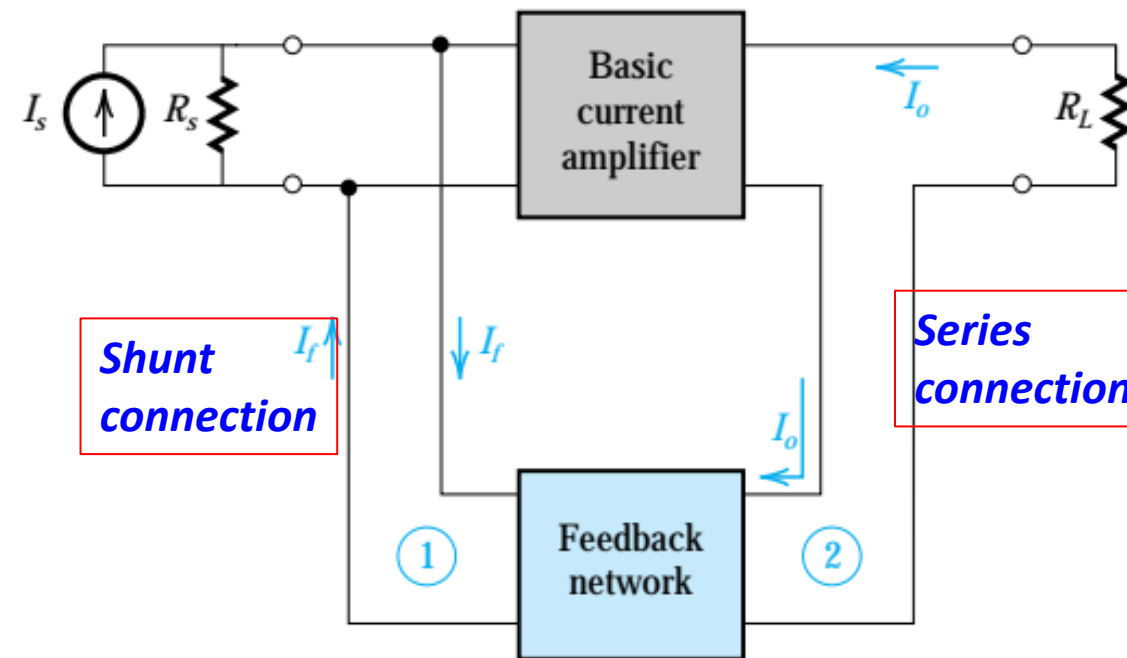Input signal: **Current**
Output Signal: **Current**



Here, the output current is sensed (**sampled**). The feedback signal (current) is **mixed** with the source current


The suitable feedback topology for the current amplifier is the **current-mixing, current-sampling**

Because of the **parallel (or shunt) connection at the input** and the **series connection at the output**, this feedback topology is also known as **shunt-series feedback** topology.

Block diagram of a **feedback current** amplifier.

Feedback Transconductance Amplifier

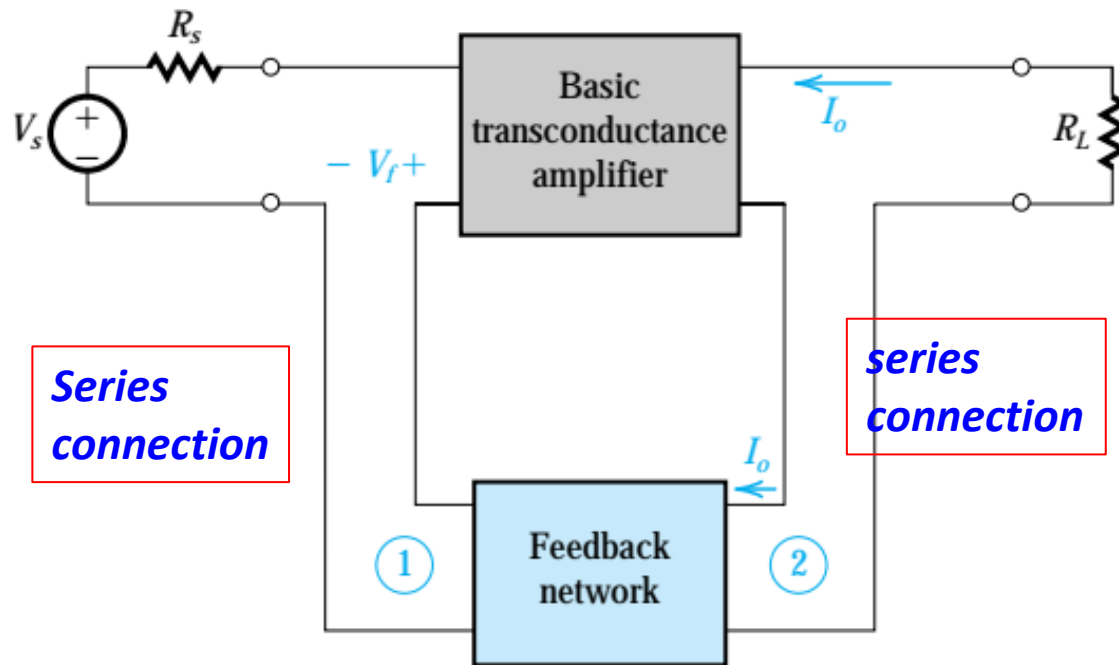Input signal: **Voltage**
Output Signal: **Current**



Series connection

series connection

Block diagram of a **feedback** transconductance amplifier.


Here, the circuit senses (**samples**) the **output current** and returns a voltage as the feedback signal. This voltage **mixes** with the signal voltage.

The suitable feedback topology for the transconductance amplifier is the **voltage-mixing, current-sampling**

Because of the **series connection at both the input and the output**, this feedback topology is also known as **series-series feedback** topology.

Feedback Transresistance Amplifiers

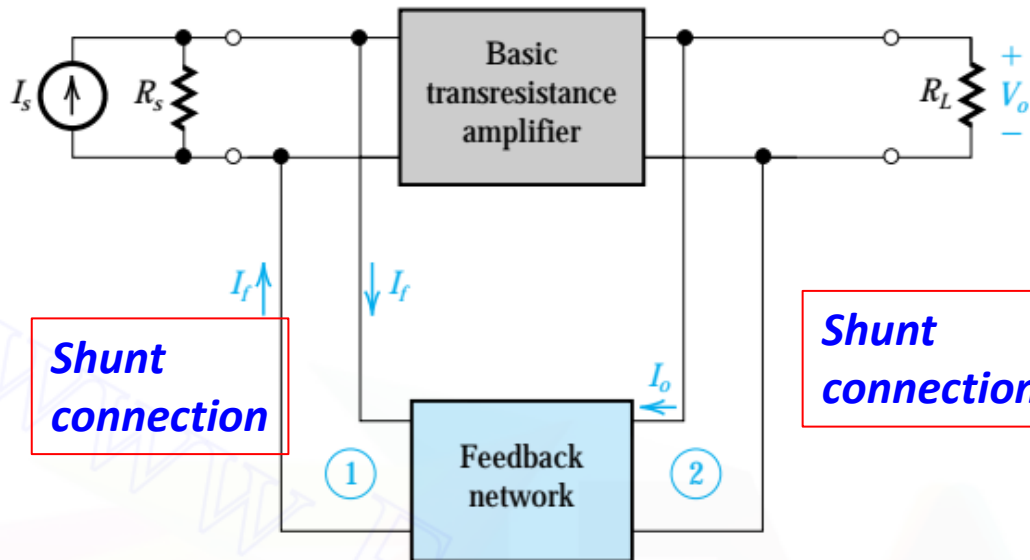Input signal: **Current**
Output Signal: **Voltage**



Here, the output voltage is sensed (**sampled**) and a proportional current is returned to the input. This current **mixes** with the source current.

The suitable feedback topology for the transresistance amplifier is the **current-mixing, voltage-sampling**

Because of the **parallel (or shunt) connection at both the input and the output**, this feedback topology is also known as **shunt-shunt feedback** topology.

Block diagram of a **feedback** transresistance amplifier.

The four basic feedback topologies

- Series-shunt feedback [*voltage mixing and voltage sampling*]
- Shunt-series feedback [*Current mixing and current sampling*]
- Series-series feedback [*Voltage mixing and current sampling*]
- Shunt-shunt feedback [*Current mixing and voltage sampling*]

❖ A feedback amplifier is denoted either by its **input–output type** (e.g. voltage-to-voltage) or its **mixing–sampling** type (e.g. series–shunt).

□ The two descriptions are equivalent.

Typical amplifier type	Gain	Reference topology name	Alternate topology name
Voltage Amplifier	V_O/V_{IN}	voltage-mixing voltage-sampling	series–shunt
Current Amplifier	I_O/I_{IN}	current-mixing current-sampling	shunt–series
Transconductance Amp	I_O/V_{IN}	voltage-mixing current-sampling	series–series
Transimpedance Amp	V_O/I_{IN}	current-mixing voltage-sampling	shunt–shunt

Feedback relationship

	Gain	Input resistance	Output resistance
Without feedback	A	R_i	R_o
Series-shunt	$A_f = \frac{A}{1 + \beta A}$	$R_{if} = R_i (1 + \beta A)$	$R_{of} = \frac{R_o}{1 + \beta A}$
Series-series	$A_f = \frac{A}{1 + \beta A}$	$R_{if} = R_i (1 + \beta A)$	$R_{of} = R_o (1 + \beta A)$
Shunt-shunt	$A_f = \frac{A}{1 + \beta A}$	$R_{if} = \frac{R_i}{1 + \beta A}$	$R_{of} = \frac{R_o}{1 + \beta A}$
Shunt-series	$A_f = \frac{A}{1 + \beta A}$	$R_{if} = \frac{R_i}{1 + \beta A}$	$R_{of} = R_o (1 + \beta A)$



END