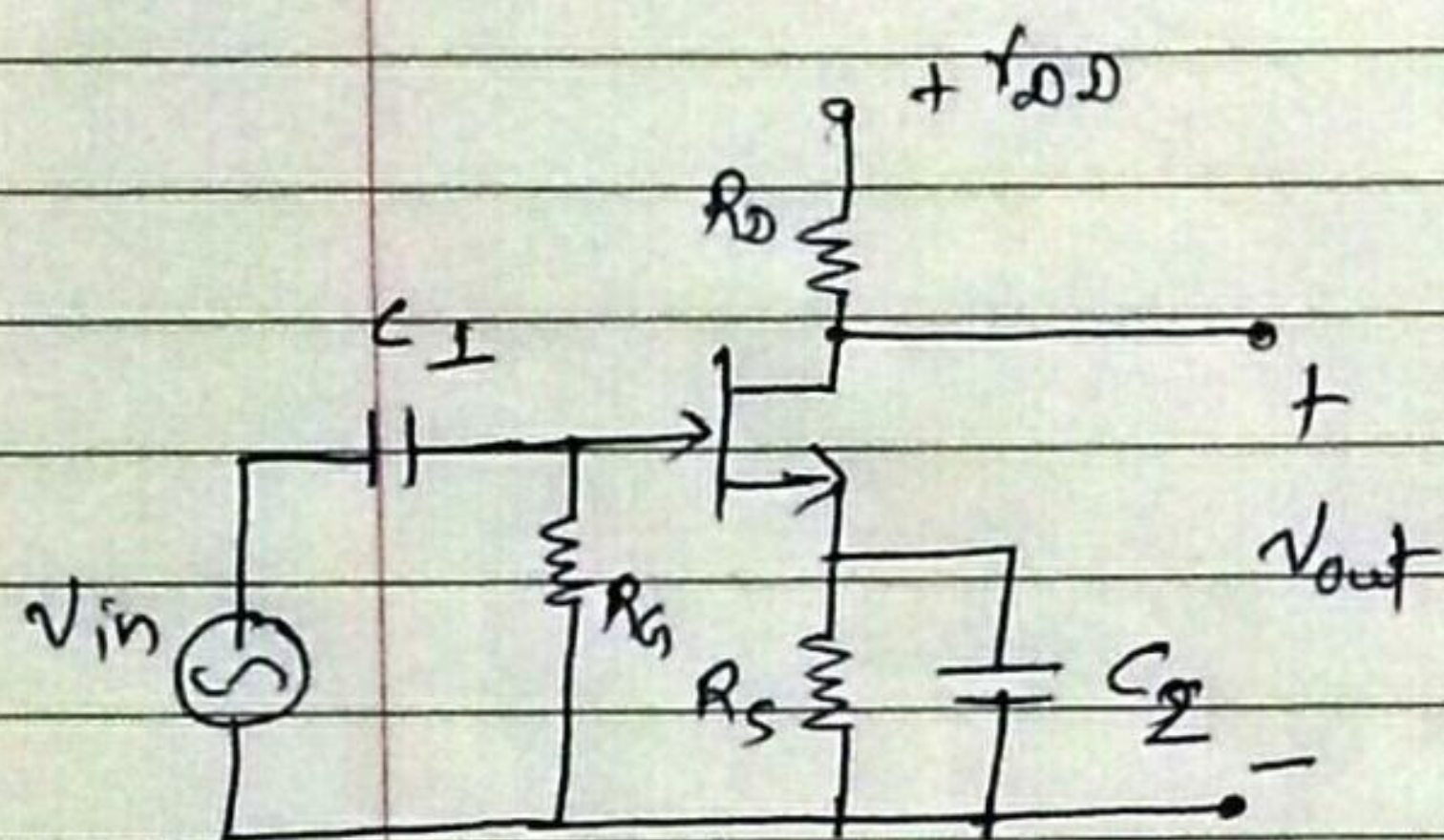


FET Amplifiers

- ★ Common Source Amplifier
- ★ Common Drain Amplifier or Source follower
- ★ Common Gate Amplifier

Common Source Amplifier




C_1 = Coupling Capacitor


C_2 = Bypass Capacitor

For drawing AC equiv. ckt.

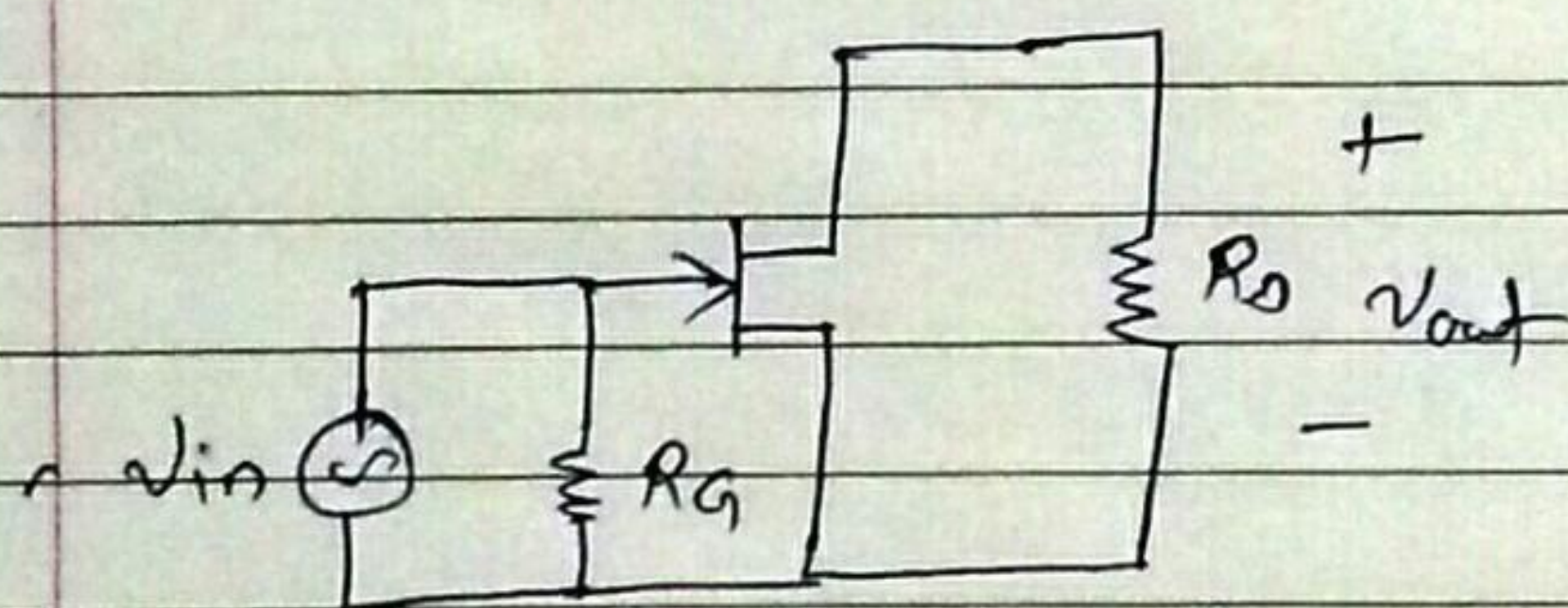- ① DC voltage sources are grounded
- ② Capacitors C_1 & C_2 are taken as short ckt.




AC equivalent ckt

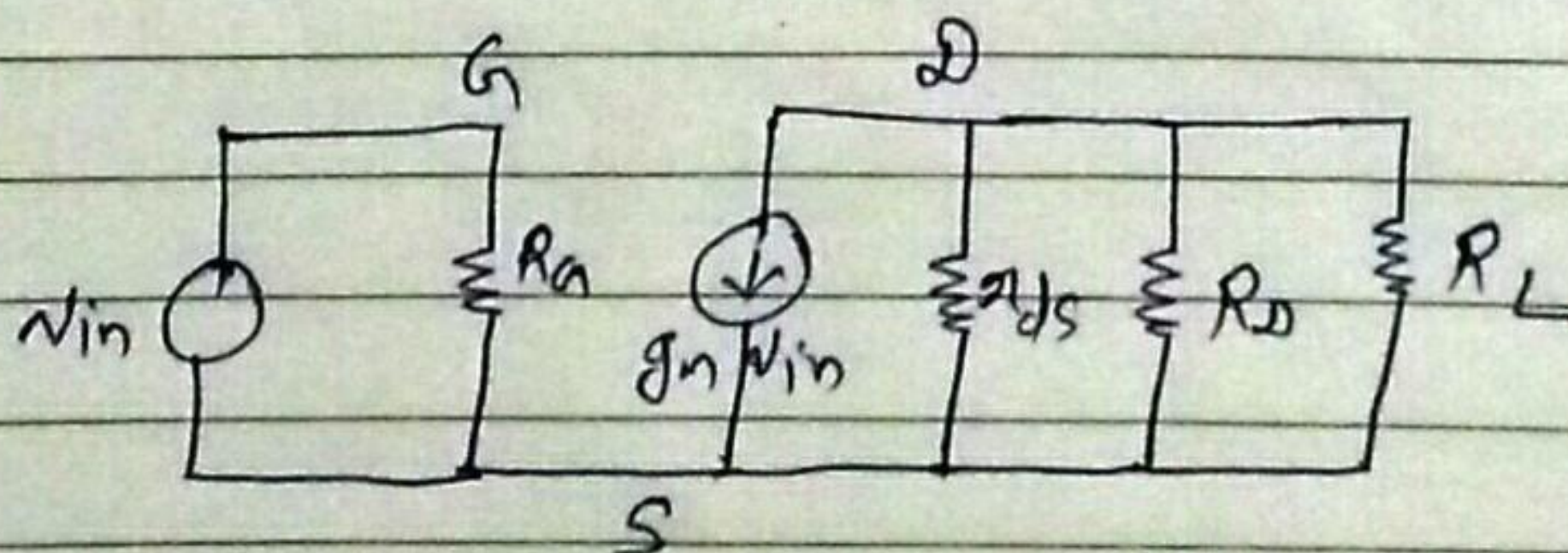

$v_{in} = v_{gs}$ True because R_1 is very high.
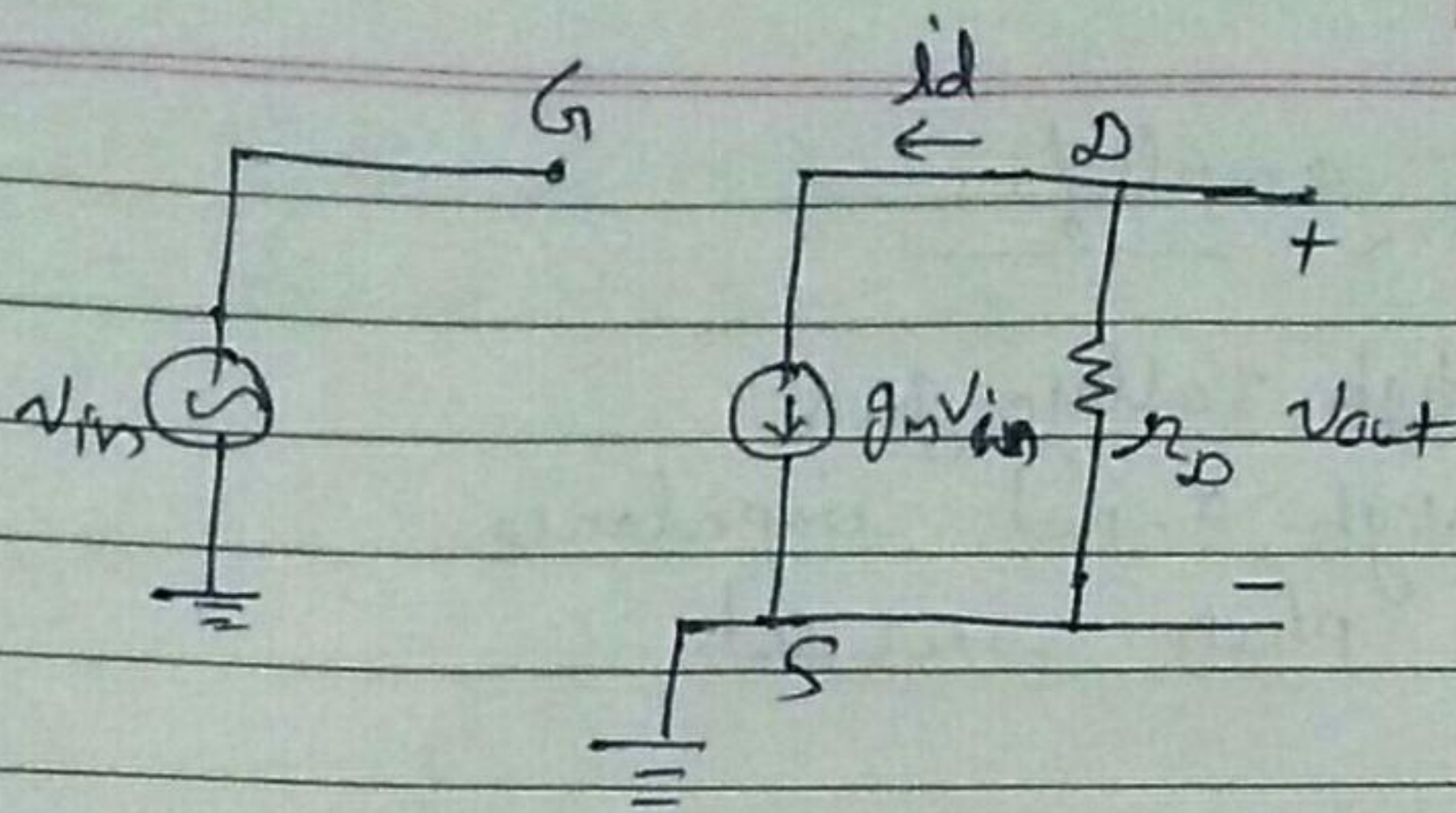
$$R_D = r_{ds} \parallel R_D \parallel R_L \approx R_D \parallel R_L$$



$$i_d = g_m v_{in}$$

$$v_{out} = -r_D i_d$$

$$v_{out} = -g_m r_D v_{in}$$

Voltage gain

$$A_v = \frac{v_{out}}{v_{in}} = \ominus g_m r_D \quad \rightarrow \text{phase inversion}$$

magnitude $\boxed{A_v = g_m r_D}$

$$g_m = 4000 \mu S, \text{ let } r_D = 4 k\Omega$$

$$A_v = 4 \times 10^{-3} \times 4 \times 10^3$$

$$\boxed{A_v = 16}$$

If R_S is not by-passed


$$\boxed{A_v = \frac{g_m r_D}{1 + g_m R_S}}$$

Input impedance of the Amplifier

$$Z_i = R_G \quad \text{Very high} \quad R_G = 100 k\Omega - 1 \text{M}\Omega$$

CS amplifier

- ① High Voltage gain
- ② High Input impedance
- ③ phase reversal

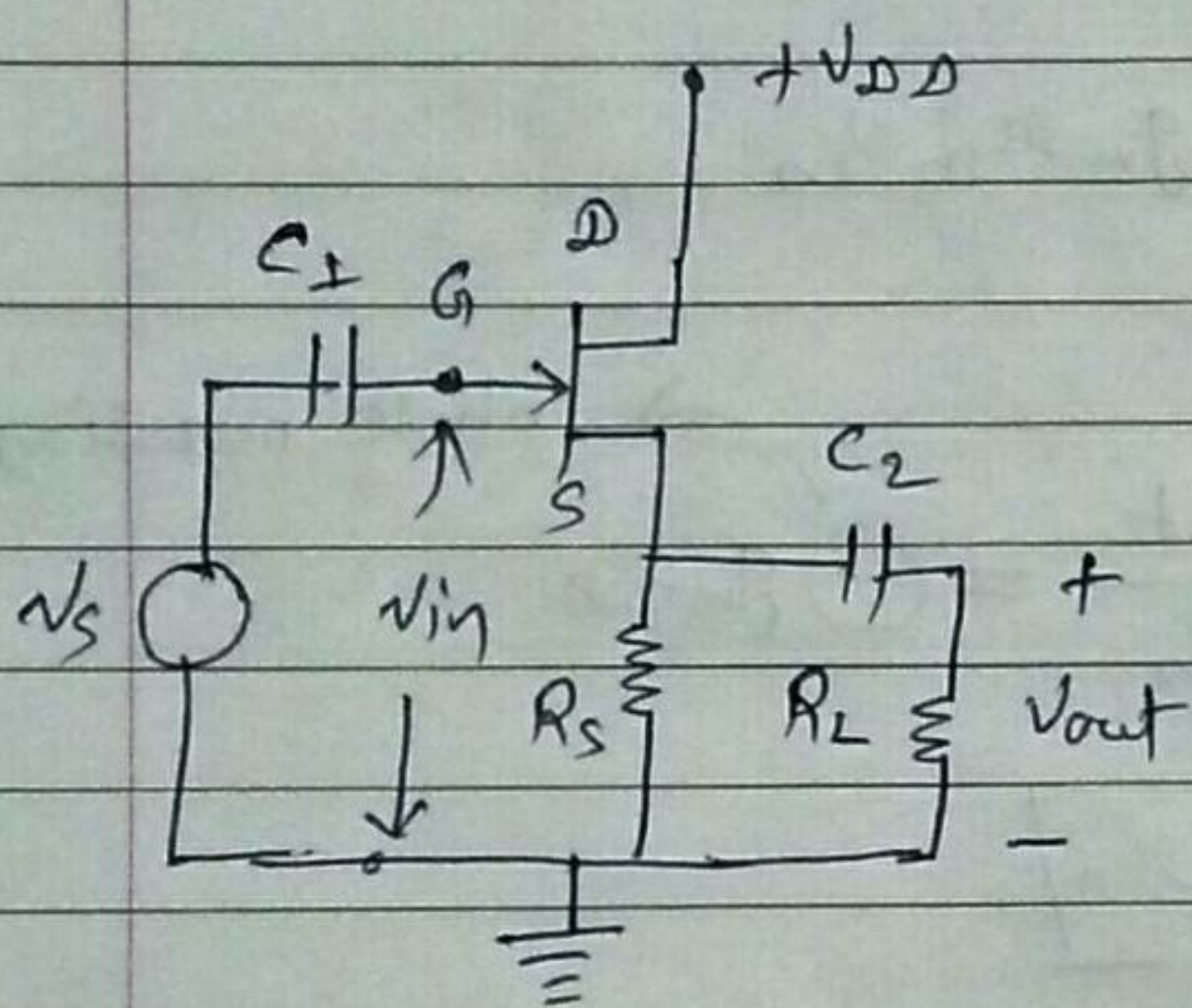
Common Drain Amplifier

* Drain is at ac ground

* Load is connected at source.

output is taken from source with respect to ground

AC

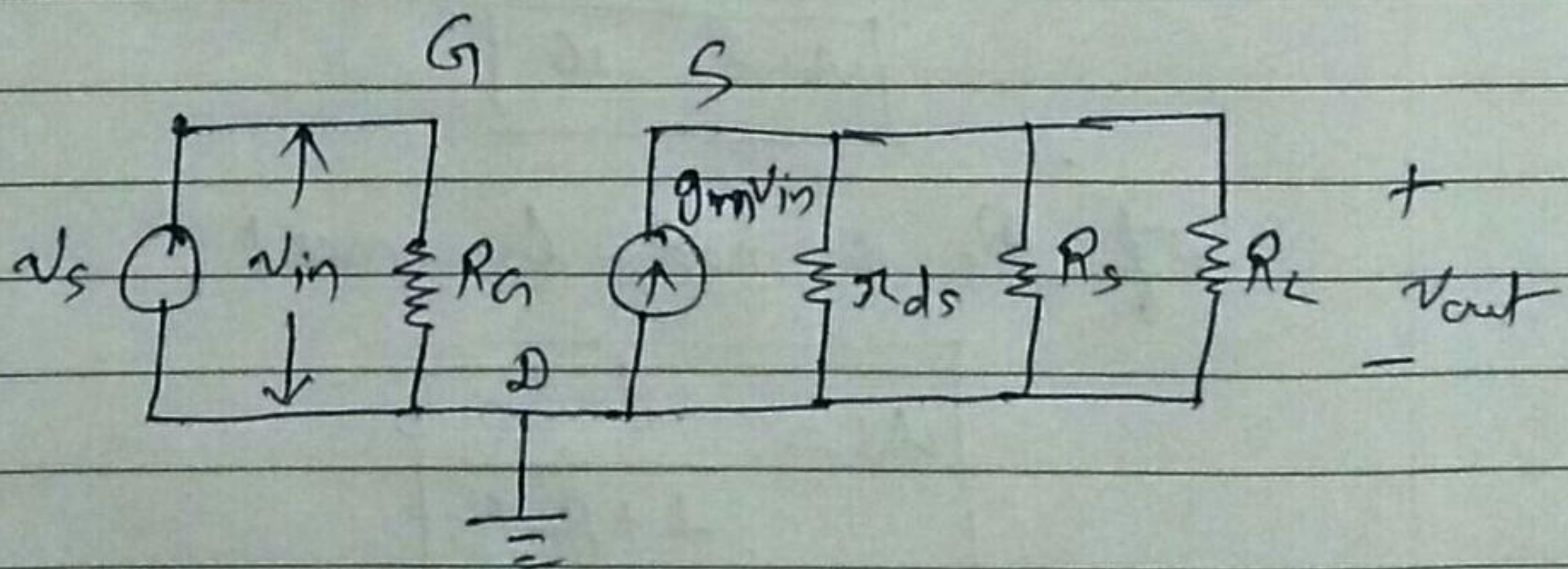
AC equivalent of CD Amplifier

$$R_L = r_{ds} \parallel R_S \parallel R_L$$

$$R_L = R_S \parallel R_L$$

Gate at V_{in} with respect to ground
 Source is at V_{out} with respect to ground
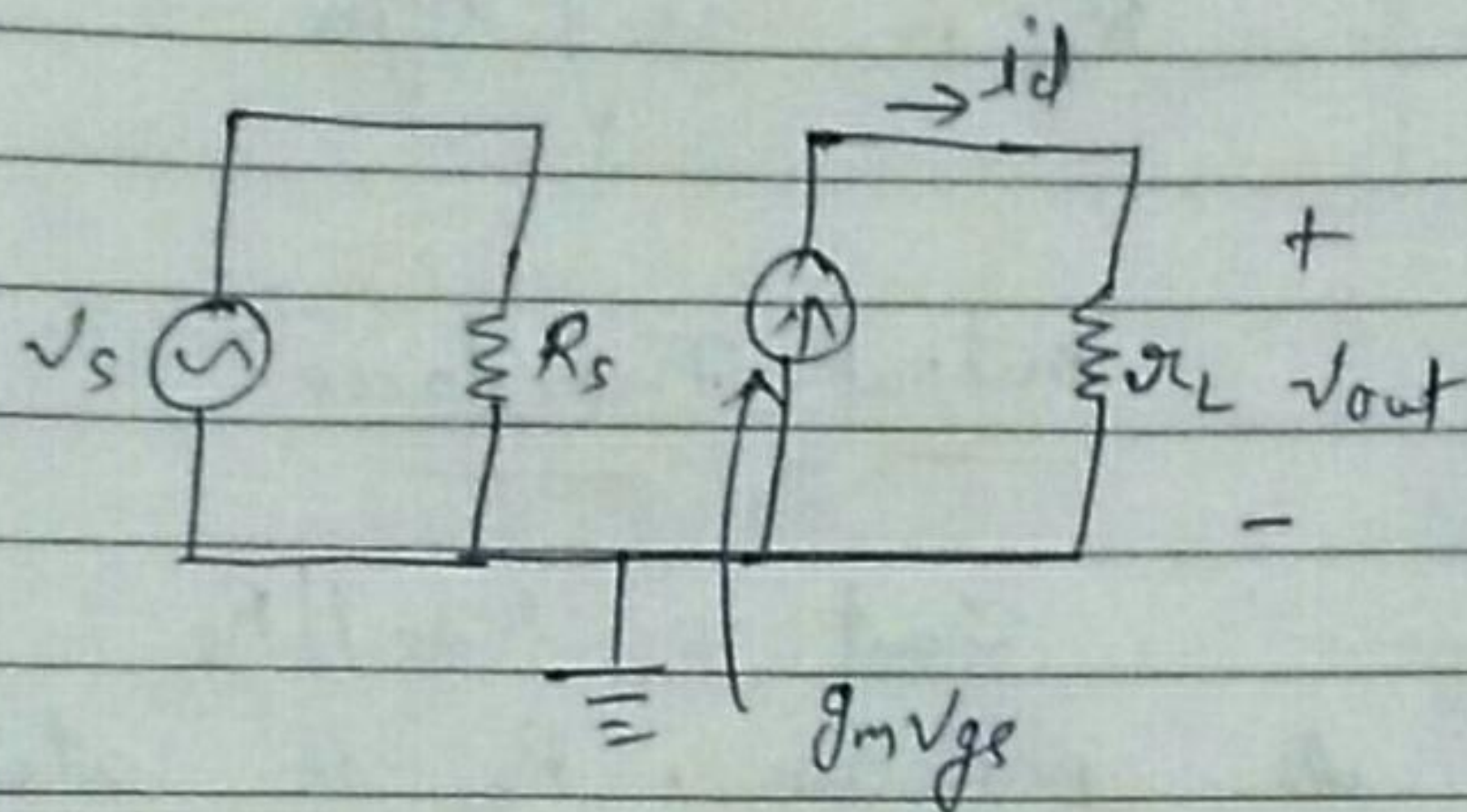
$$V_{gs} = V_{in} - V_{out} \quad \text{--- (1)}$$



$$V_{out} = i_d R_L \quad i_d \cdot R_L$$

Since $i_d = g_m V_{gs}$

$$V_{out} = g_m R_L \cdot V_{gs}$$

putting for V_{gs} from Eq. (1)

$$V_{out} = g_m R_L (V_{in} - V_{out})$$

$$\text{or } V_{out} (1 + g_m R_L) = g_m R_L V_{in}$$

Voltage gain

$$A_V = \frac{V_{out}}{V_{in}} = \frac{g_m R_L}{1 + g_m R_L}$$

Normally $g_m R_L \gg 1$

$$A_V \approx 1$$

Input Impedance

$$Z_{in} = R_G$$

R_G is very high

Output Impedance

$$Z_{out} = r_{ds} \parallel R_S$$

As practice, R_L is always removed from the ckt. to measure Z_{out} .

$$\boxed{Z_{out} \approx R_S}$$

Low o/p impedance

$$R_S = 200 - 400 \Omega$$

CD amplifier

* Known as Source follower


$$A_V \approx 1, \quad A_V < 1$$

$$Z_{in} = R_G \text{ (high)}$$

$$Z_{out} = R_S \text{ (low)}$$

used as buffer

Common gate Amplifier

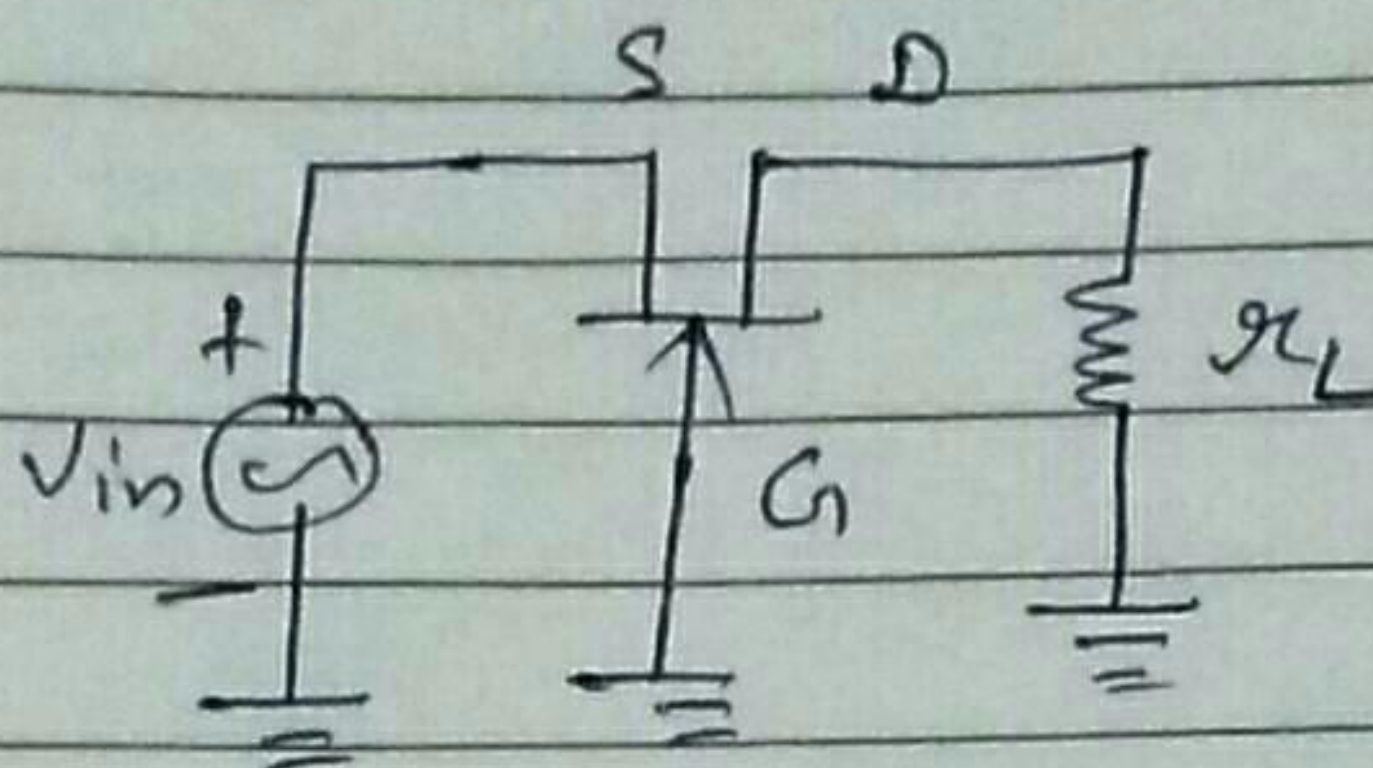

$$V_{out} = i_d R_L$$

$$i_d = g_m V_{gs}$$

$$V_{gs} = V_{in}$$

$$V_{out} = g_m V_{in} R_L$$

$$\text{or } A_v = \frac{V_{out}}{V_{in}} = g_m R_L \quad (\text{High})$$

Input Impedance

$$i_{in} = i_d = g_m V_{gs}$$

$$= g_m V_{in}$$

$$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{1}{g_m} \quad (\text{Very low})$$

$$\text{Let } g_m = 4000 \text{ MS}, \quad \text{A}$$

$$Z_{in} = \frac{1}{4 \times 10^{-3}} = 250 \, \Omega$$