

Answer All Questions Assume suitable missing data, if any

1. (a) Design Full Subtractor by using two half subtractors and derive the expression also.
- (b) Express the switching circuit shown in the Fig.1. in binary logic notation [3+1]

 


Fig.1.

2. Analyze the two output circuit shown in Fig. 2. Indicate the logic expression associated with every gate output [4]

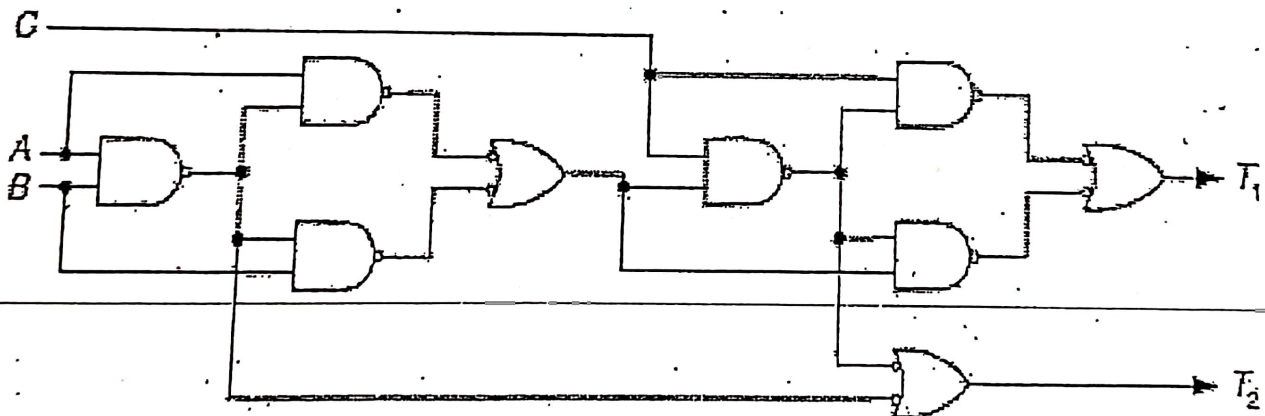


Fig. 2.

3. (a) Implement the Boolean following function by using 8:1 MUX
 $P(QWER) = \pi M(1,2,4,5,9,11,12,15)$
- (b) Minimize the given POS expression by using Karnaugh-Map method
 $F = \pi M(0,2,3,5,6,10,12)$ with M8, M13, M15 as don't care terms. [2+2]

4. (a) Design a circuit using De-Mux to convert 8421 BCD code to Ex code
(b) If $X = 01110$ and $Y = 11001$ are two 5-bit binary numbers represented in two's complement format. Represent the sum of X and Y in two's complement format using 6 bits. [2+2]
5. With neat circuit diagram, explain the working Master Slave JK flip-flop and show that it overcome racing condition. [4]
6. (a) Design a 32:1 Mux, using 4:1 mux and a basic gate calculate how many 4:1 Mux are required? [2]
(b) Design an three even parity generator [2]