

The monolithic IC form of the simple circuit of Fig. 14.1 has already been shown in Fig. 14.2 (e). Another example is shown in Fig. 14.3A which incorporates circuit components like a diode (D), a resistor (R), an npn transistor (T), and a capacitor (C). The circuit is shown in Fig. 14.3A (a) whose monolithic IC layout is depicted in Fig. 14.3A (b). Isolation between the components is achieved by connecting the p -type substrate to the most negative voltage. The $p-n$ junctions separating the components are then reverse biased, offering a dc isolation resistance higher than $10 \text{ M}\Omega$.

14.4 LIMITATIONS OF ICs

- (i) Very small resistors (less than a few ohms) and very large resistors (of the order of meg ohm) cannot be obtained by the IC technology.
- (ii) Large capacitances (greater than 200 pF) cannot be produced.
- (iii) Inductors and transformers cannot be fabricated in the IC.
- (iv) The tolerance of the IC passive components is large (typically ± 20 per cent).
- (v) The IC components are voltage-sensitive and have large temperature coefficients.
- (vi) The performance of the $p-n-p$ transistor is poor.
- (vii) The power dissipation capacity is small.
- (viii) The high-frequency performance of ICs is limited by the parasitic capacitances.

With the progress in technology, some of these limitations are expected to be removed in future.

The fabrication of ICs on the top of the wafer results in the unutilization or significant wastage of the semiconductor material in the bulk of the wafer. The material loss can be averted if the circuit could be grown on thin films of the material. This enhances the importance of *thin film technology*.

14.5 OPERATIONAL AMPLIFIERS

(The operational amplifier (abbreviated OP AMP) is the best known example of a general-purpose linear integrated circuit. The IC OP AMP was developed by Robert Widlar in 1964. Basically, the OP AMP is a direct-coupled high-gain differential-input amplifier. The significance of the term 'operational' is that the OP AMP can perform mathematical operations such as summation, subtraction, integration, and differentiation. Such operations are important in analog computers. In addition, the OP AMPS can be used in signal amplification, wave forming, servocontrols, impedance transformation, active filters, oscillators, voltage regulators, analog-to-digital and digital-to-analog converters, to mention but a few. IC OP AMPs are useful in communication equipment, instrumentation, and data processing.)

The advantage of OP AMPs is that negative feedback can be applied. The performance of the OP AMP with negative feedback is controlled by the feedback elements independent of the characteristics of the transistors and other elements that constitute the OP AMP. As the feedback elements are usually passive, the circuit operation is very stable and predictable. The IC OP AMPs are inexpensive and have temperature stabilisation. The user of the device need not know the detailed internal circuit configuration of the OP AMP. He simply needs to be acquainted with its terminal properties, so that by connecting external circuit components he can use the OP AMP for a specific purpose.

Circuit Symbol: Figure 14.4 shows the circuit representation of an operational amplifier. It has two input terminals (marked a and b) and one output terminal (marked c). Terminal a is known as the *inverting input terminal* and is labelled ' $-$ '. The significance of the negative sign is that a signal applied at the terminal a appears at the terminal c with its polarity reversed.

Terminal b is called the *noninverting input terminal* and is labelled '+'. A signal applied to the terminal b appears at the terminal c with the same polarity. The output voltage at c is proportional to the *difference* of the two signal voltages applied at the two input terminals simultaneously. The constant of proportionality gives the *open-loop voltage gain* (A) of the operational amplifier. A is a real constant, and for an ideal amplifier A approaches infinity for all frequencies.

The power supply voltages which are usually balanced with respect to ground are applied to the terminals d and e .

The terminals d and e are, however, often omitted in schematic circuits.

OP AMP Characteristics: The ideal OP AMP has the following properties:

1. An infinite voltage gain.
2. An infinite input impedance.
3. Zero output impedance.
4. An infinite bandwidth.
5. Characteristics not drifting with temperature.
6. Perfect balance, i.e. the output voltage is zero when equal voltages are applied to the two input terminals.

For a practical OP AMP, the dc or the low-frequency voltage gain is typically 10^3 to 10^6 . The bandwidth is finite, the voltage gain being constant up to several hundred kilohertz and then decreasing with increase in frequency. The input impedance is between 150 kilohm and a few hundred meg ohm. The output impedance lies in the range 0.75 to 100 ohm. The practical OP AMPS do not have a prefect balance and their characteristics also change somewhat with temperature.

Common-mode rejection ratio. An OP AMP is basically a differential amplifier with signal voltages v_1 and v_2 each measured with respect to ground, applied to the noninverting terminal b and the inverting terminal a respectively (Fig. 14.4). The output voltage appearing at the terminal c is v_o , measured with respect to ground. In practice, the *difference signal*

$v_d (= v_1 - v_2)$ and also the *average signal*, called the *common-mode signal* $v_c \left(= \frac{v_1 + v_2}{2} \right)$ are amplified to produce the output voltage. We have

$$v_o = A_1 v_1 + A_2 v_2 \quad (14.1)$$

where A_1 is the voltage gain when the terminal a is grounded and A_2 is that when the terminal b is grounded. Now

$$v_1 = v_c + \frac{1}{2} v_d \quad (14.2)$$

$$v_2 = v_c - \frac{1}{2} v_d \quad (14.3)$$

and

Using Eqs. (14.2) and (14.3) in (14.1) we get

$$v_o = \frac{1}{2} (A_1 - A_2) v_d + (A_1 + A_2) v_c = A_d v_d + A_c v_c \quad (14.4)$$

$$A_d = \frac{1}{2} (A_1 - A_2) \quad (14.5)$$

$$A_c = A_1 + A_2 \quad (14.6)$$

where

and

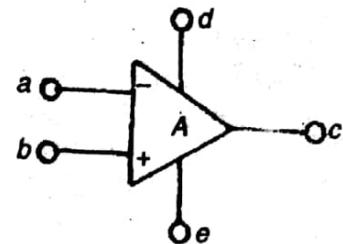


Fig. 14.4 Circuit symbol of a basic OP AMP.

A_d is the voltage gain for the difference signal and A_c is that for the common-mode signal. In the ideal case, A_d is infinitely large while A_c is zero. In practice, the situation is not truly ideal, and a figure of merit, called the *common-mode rejection ratio* (CMRR) of the OP AMP has to be introduced. It is defined by

$$\text{CMRR} = \left| \frac{A_d}{A_c} \right|. \quad (14.7)$$

Since A_d needs to be large and A_c very small, the amplifier must be so designed that the CMRR is much larger than unity.

Offset error voltages and current: An ideal OP AMP is perfectly balanced, i.e. $v_o = 0$ when $v_1 = v_2$. In practice, an OP AMP shows an unbalance due to a mismatch of the built-in transistors following the inverting and the noninverting input terminals. This mismatch gives unequal bias currents flowing through the input terminals. Thus an input offset voltage has to be applied between the two input terminals to balance the output.

The *input bias current* is half the sum of the individual currents entering the two input terminals of a balanced amplifier [Fig. 14.5(a)]. The input bias current is

$$i_B = \frac{i_{b1} + i_{b2}}{2}, \text{ when } v_o = 0.$$

The *input offset current* i_{io} is the difference between the individual currents entering the input terminals of a balanced amplifier [Fig. 14.5(a)]. Thus

$$i_{io} = i_{b1} - i_{b2}, \text{ when } v_o = 0.$$

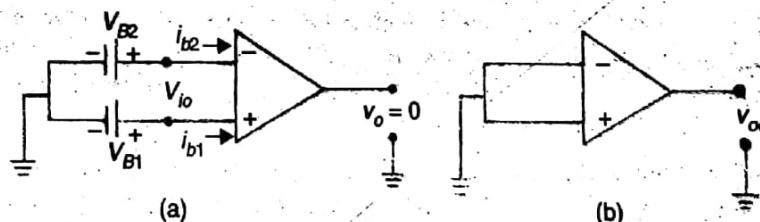


Fig. 14.5 (a) Input offset voltage (b) Output offset voltage.

The *input offset voltage* v_{io} is the voltage to be applied between the input terminals to balance the amplifier [Fig. 14.5(a)].

The *output offset voltage* v_{o0} is the voltage at the output terminal when the two input terminals are grounded [Fig. 14.5(b)].

Practical OP AMPS have arrangements to balance the offset voltage.

14.6 CIRCUIT OF AN OP AMP

The circuit of a general-purpose monolithic IC OP AMP is shown in Fig. 14.5A. The high input impedance is provided by the Darlington connection of two *n-p-n* transistors. There are two differential gain stages; the output is taken from a single-ended emitter follower. The transistors T_1 and T_2 are identical; so are the transistors T_3 and T_4 . Also, $R_1 = R_2$. The errors from the thermal drift are reduced, since the corresponding components of each pair are affected almost equally owing to their close spacing in the IC chip.

Let the inverting input terminal a be grounded and a small positive voltage v_1 be applied to the noninverting input terminal b . This will drop the potential of the point M , so that T_4 will conduct more. The potential of the point N increases consequently. The transistor T_5 now conducts less, so that the output voltage (at the terminal c) becomes more positive. Thus a

signal applied to b appears with the same polarity (though amplified) at c . If A_1 is the voltage gain, the output voltage is $v_0 = A_1 v_1$. Since v_0 and v_1 have the same polarity, A_1 is positive.

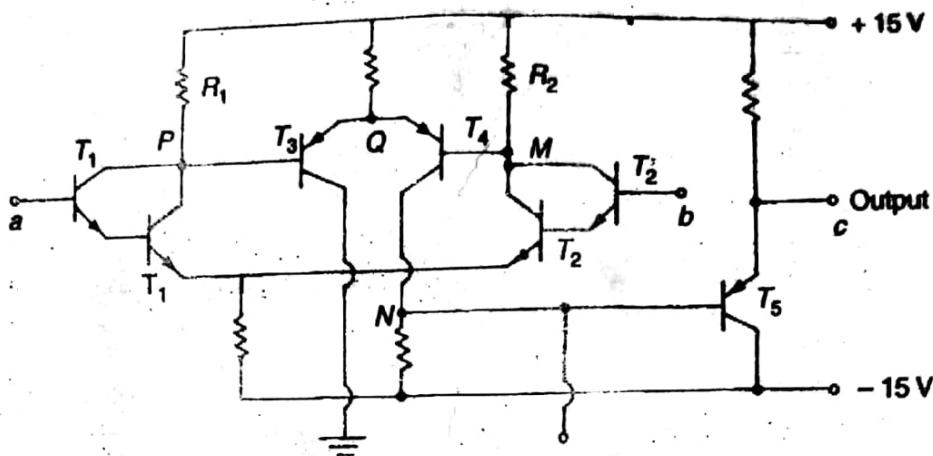


Fig. 14.5A Circuit of an IC OP AMP.

Now, let b be grounded and a small positive voltage v_2 be applied to a . The point P becomes less positive, so that T_3 conducts more. As a result, the potential of the point Q falls and T_4 conducts less. The potential of N thus becomes more negative, so that T_5 conducts more. The potential of the output terminal c thus falls. So, a signal applied to a appears in an amplified form with its polarity reversed at c . If A_2 is the voltage gain, we have for the output voltage, $v_0 = A_2 v_2$. Since v_0 and v_2 have opposite polarity, A_2 is negative.

When v_1 and v_2 are simultaneously applied to b and a , respectively, the output voltage can be written as $v_0 = A_1 v_1 + A_2 v_2$, which is Eq. (14.1). Ideally, $A_1 = -A_2$, so that we obtain $v_0 = 0$ for $v_1 = v_2$.

AC equivalent circuit of an OP AMP

The AC equivalent circuit of an OP AMP is shown in Fig. 14.5B. The input resistance between the inverting input terminal and ground is R_{ia} , that between the noninverting input terminal

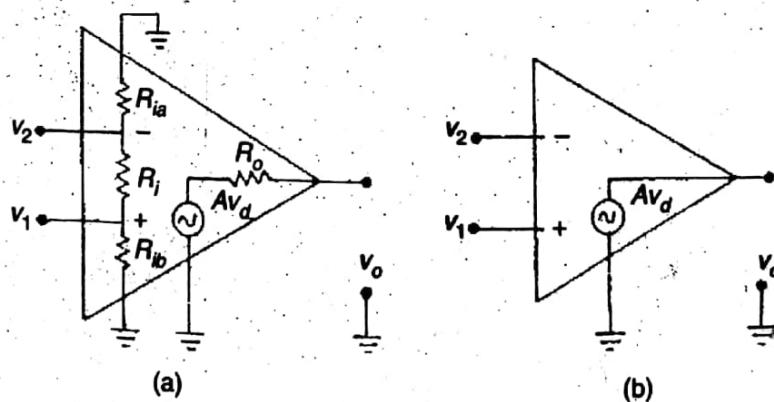


Fig. 14.5B AC equivalent circuit of an OP AMP : (a) practical, (b) ideal.

and ground is R_{ib} , and that between the two input terminals is R_i . All the three resistances R_{ia} , R_{ib} and R_i are typically very high. The output voltage is the amplifier gain A multiplied by the difference input signal v_d ($= v_1 - v_2$), taken through the output resistance R_0 , which is typically very low. The gain A is the voltage gain A_d for the difference signal and is typically very high. In the ideal equivalent circuit of Fig. 14.5B(b), R_{ia} , R_{ib} and R_i are infinite, R_0 is zero, and A is infinite.

Open-loop characteristic

Figure 14.5C shows the open-loop characteristic of an OP AMP, where the output voltage v_o is plotted against the difference input signal voltage v_d . Since the open-loop gain A_d is very high, v_o attains nearly the positive DC supply voltage $+V$ when v_d is slightly positive. With further increase of v_d , v_o remains saturated at $+V$. Again, v_o attains nearly the negative DC supply voltage $-V$ when v_d is slightly negative. As v_d becomes more negative, v_o remains saturated at $-V$. $+V$ and $-V$ are called the positive saturation voltage and the negative saturation voltage, respectively.

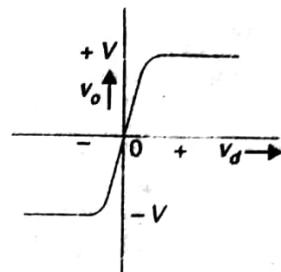


Fig. 14.5C Open-loop characteristic of an OP AMP.

14.7 OP-AMP APPLICATIONS

We give below some useful applications of the OP AMP. In these applications, all voltages are measured with respect to ground. The OP AMPS generally require balanced DC supplies (such as $+15\text{ V}$ and -15 V) with respect to ground to energise the circuit. These supply voltages are connected externally to the proper pins of the OP AMP, and are not shown in the schematic circuits discussed below.

When the magnitude of the output signal voltage is less than the magnitude of the power supply voltage, the OP AMP is said to be in the linear region because the input voltage-output voltage relationship is then linear. Usually, the OP AMP is operated in the linear region. If the magnitude of the output voltage equals the magnitude of the power supply voltage, the OP AMP is said to be in the saturated region. In this region, the output voltage does not increase with the input voltage, but, remains constant at the supply voltage.

1. Inverting amplifier: A basic inverting amplifier using an OP AMP connected with an input resistance R_1 and a feedback resistance R_f is shown in Fig. 14.6. Since R_f connects the output terminal to the inverting input terminal, it provides a negative feedback. The noninverting input terminal is grounded. The input and the output voltages are v_1 and v_o , respectively. Let v be the voltage at the inverting input terminal. As the open-loop gain A of the OP AMP is very high, and the output voltage v_o is finite due to negative feedback, we have $v = v_o/A \rightarrow 0$ as $|A| \rightarrow \infty$. Therefore, the inverting input terminal is practically at the ground potential. Thus, though the point G is not actually connected to ground it is held virtually at ground potential, whatever be the magnitudes of v_1 and v_o .

There is an important difference between an 'actual ground' and a 'virtual ground'. When a terminal is actually grounded, any amount of current can flow to ground through the terminal. Thus an actual ground can serve as a 'sink' for infinite current. But the input impedance of an OP AMP being infinite, no current can flow into the OP AMP through the virtual ground. So a virtual ground cannot serve as a sink for current.

The current i through the resistance R_1 is

$$i = \frac{v_1 - v}{R_1} \quad (14.8)$$

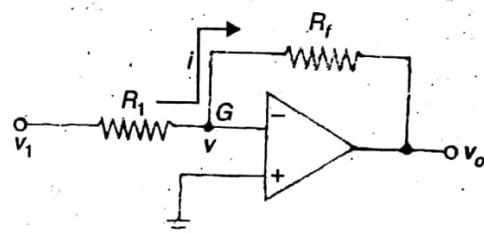


Fig. 14.6 Inverting amplifier.

Assuming that the OP AMP is an ideal one with an infinite input impedance, the current i passes through R_f and not into the OP AMP. Kirchhoff's current law at the point G gives

$$\frac{v_1 - v}{R_1} = \frac{v - v_0}{R_f} \quad (14.9)$$

As the point G is a *virtual ground*, $v \approx 0$. Hence Eq. (14.9) reduces to

$$\frac{v_1}{R_1} = -\frac{v_0}{R_f} \quad (14.10)$$

The ratio of the output voltage v_0 and the input voltage v_1 is the *closed-loop gain* of the amplifier. So, the closed-loop gain of the inverting amplifier is

$$\frac{v_0}{v_1} = -\frac{R_f}{R_1} \quad (14.11)$$

Thus the closed-loop voltage gain is the ratio of the feedback resistance R_f to the input resistance R_1 . The negative sign signifies that the output voltage is *inverted* with respect to the input voltage.

The input resistance of the amplifier system is

$$R_{in} = \frac{v_1}{i} = \frac{v_1}{(v_1 - v)/R_1} \approx R_1 \quad (14.12)$$

using Eq. (14.8) and noting that $v \approx 0$. It should be noted that R_{in} refers to the entire amplifier system and not to the OP AMP which has an infinite input impedance. The output resistance of the inverting amplifier is very small.

2. Phase shifter: Let the resistances R_1 and R_f in the circuit of Fig. 14.6 be replaced respectively by the impedances Z_1 and Z_f which have equal magnitudes but different phase angles. Hence

$$\frac{v_0}{v_1} = -\frac{Z_f}{Z_1} = -\frac{|Z_f| \exp(j\theta_f)}{|Z_1| \exp(j\theta_1)} = \exp[j(\pi + \theta_f - \theta_1)] \quad (14.13)$$

Since $|Z_f| = |Z_1|$ and $\exp(j\pi) = -1$. The angles θ_f and θ_1 are respectively the phase angles of Z_f and Z_1 . Equation (14.13) shows that v_0 leads v_1 by $(\pi + \theta_f - \theta_1)$, but $|v_0| = |v_1|$. Obviously, the circuit shifts the phase of a sinusoidal input voltage leaving its magnitude unaltered. The phase shift can be anything between 0° and 360° .

3. Scale changer: Let $R_f/R_1 = K$ (a real constant) in the circuit of Fig. 14.6. The output voltage can be written as

$$v_0 = -K v_1. \quad (14.14)$$

Thus the output voltage scale is obtained by multiplying the input voltage scale by $-K$, called the *scale factor*. Using precision resistors, accurate values of K can be achieved. The inverting amplifier can then serve as a *scale changer*. A low voltage can be accurately measured by amplifying the voltage by the scale changer and dividing the amplified voltage by the scale factor.

4. Noninverting amplifier: Figure 14.7 depicts the circuit diagram of a noninverting amplifier. The input voltage v_1 is applied to the noninverting terminal. Since the voltage gain of the OP AMP is infinite, the potential of the point G is also v_1 . The current flowing into the OP AMP is negligible, its input impedance being very large. Hence, applying Kirchhoff's current law at the point G we obtain

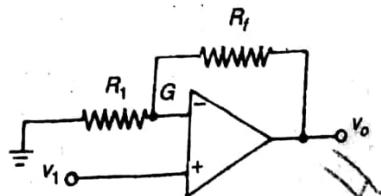


Fig. 14.7 Noninverting amplifier.

$$\frac{v_0 - v_1}{R_f} = \frac{v_1}{R_1} \quad (14.15)$$

or

$$\frac{v_0}{v_1} = 1 + \frac{R_f}{R_1} \quad (14.16)$$

which is the voltage gain of the amplifier system. The voltage gain is greater than unity by a factor R_f/R_1 . As the gain is positive, there is no phase difference between the input voltage v_1 and the output voltage v_0 . The input impedance of the circuit is high and the output impedance is low.

In the circuit of Fig. 14.7, if $R_f = 0$ and $R_1 = \infty$, the circuit reduces to that of Fig. 14.8. Equation (14.16) shows that the voltage gain in this case is unity. Therefore, the circuit of Fig. 14.8 is referred to as a *unity-gain buffer* or a *voltage follower*. This circuit offers a high input impedance and a low output impedance, and therefore can be employed as an impedance matching device between a high-impedance source and a low-impedance load.

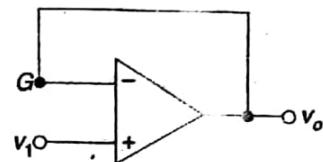


Fig. 14.8 A voltage follower.

✓ 6. Adder or summing amplifier: Figure 14.9 gives the circuit diagram of an adder or a summing amplifier. The same reasoning as in the case of the inverting amplifier shows that the point G is a virtual ground, i.e. G is at ground potential. The input impedance of the OP AMP being infinite, the sum of the currents i_1, i_2, \dots, i_n will be equal to i_0 , by Kirchhoff's current law. That is,

$$i_1 + i_2 + \dots + i_n = i_0$$

or

$$\frac{v_1}{R_1} + \frac{v_2}{R_2} + \dots + \frac{v_n}{R_n} = -\frac{v_0}{R_f}$$

or

$$v_0 = -\left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \dots + \frac{R_f}{R_n} v_n \right) \quad (14.17)$$

If $R_1 = R_2 = \dots = R_n = R$, Eq. (14.17) gives

$$v_0 = -\frac{R_f}{R} (v_1 + v_2 + \dots + v_n) \quad (14.18)$$

With $R_f = R$, Eq. (14.18) reduces to

$$v_0 = -(v_1 + v_2 + \dots + v_n). \quad (14.19)$$

This equation shows that the output voltage v_0 is numerically equal to the algebraic sum of the input voltages v_1, v_2, \dots, v_n . Hence the circuit is termed a *summing amplifier* or an *adder*. If the algebraic sum of the input voltages is very small, the output voltage v_0 is measured with $R_f > R$. From Eq. (14.18), the desired sum is obtained accurately by dividing v_0 by R_f/R_1 .

✓ 6. Differential amplifier: A differential (or difference) amplifier amplifies the difference of two voltages. Figure 14.10 shows the circuit diagram of a differential amplifier. Suppose that the difference between the voltages v_2 and v_1 is to be amplified. The voltage v_2 is applied to the

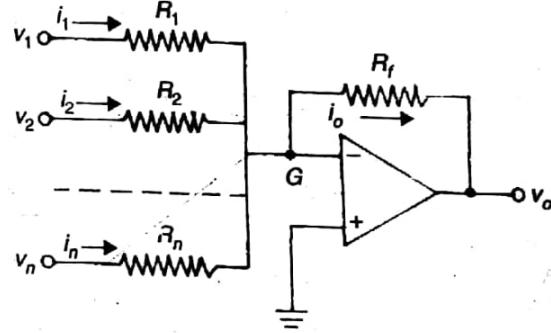


Fig. 14.9 Summing amplifier

noninverting input terminal and v_1 to the inverting input terminal of the OP AMP. The output voltage is v_o . The voltage gain of the OP AMP being infinite, the points a and b will have the same potential, say, v_x . Applying Kirchhoff's current law at a and b , we obtain respectively

$$\frac{v_1 - v_x}{R_1} = \frac{v_x - v_o}{R_2} \quad (14.20)$$

and

$$\frac{v_2 - v_x}{R_1} = \frac{v_x}{R_2} \quad (14.21)$$

where we have assumed that the input impedance of the OP AMP is infinite. Subtracting Eq. (14.20) from Eq. (14.21), we get

$$v_o = \frac{R_2}{R_1} (v_2 - v_1) \quad (14.22)$$

Thus v_o is the amplified version of the difference voltage ($v_2 - v_1$), the voltage gain of the amplifier system being R_2/R_1 .

7. Oscillator: Owing to its high gain and wide bandwidth, the IC OP AMP can be used in oscillator circuits. Figure 14.11 shows the circuit diagram of a phase-shift RC oscillator using an OP AMP. The RC network is connected at the output of the OP AMP. The resistance R_3 of the potentiometer is greater than R . Also, the feedback resistance R_2 is greater than R_1 to achieve a proper voltage gain of the inverting amplifier system. The potentiometer slider is adjusted for unity loop gain. Sustained oscillations at a frequency determined by the network parameters can then be obtained.

The use of an OP AMP as the active element in the Wien-bridge oscillator circuit is shown in Fig. 14.12. The oscillation frequency is $f_0 = 1/(2\pi RC)$. The principle of oscillation has been discussed in detail in Chapter 11. From Eq. (11.58) we find that the voltage gain A of the active element must be δ , where δ (a positive number greater than 3) is given by Eq. (11.54).

8. Differentiator: The circuit of Fig. 14.13 gives an output voltage v_o which is proportional to the derivative of the input voltage v_1 with respect to time. Therefore, the circuit is termed a *differentiator*. The infinite voltage gain of the OP AMP makes G a virtual ground. The charge on the capacitor C is therefore $q = Cv_1$

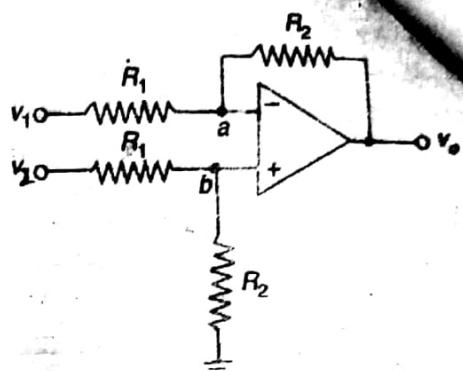


Fig. 14.10 Differential amplifier.

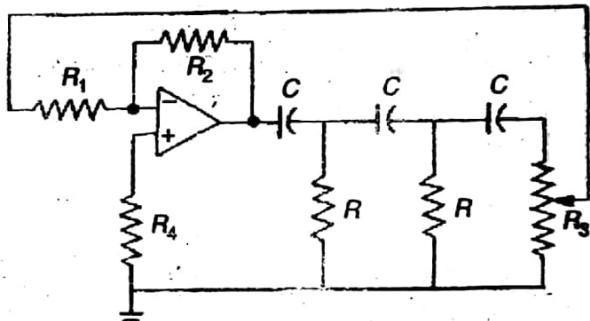


Fig. 14.11 Phase-shift oscillator using OP AMP.

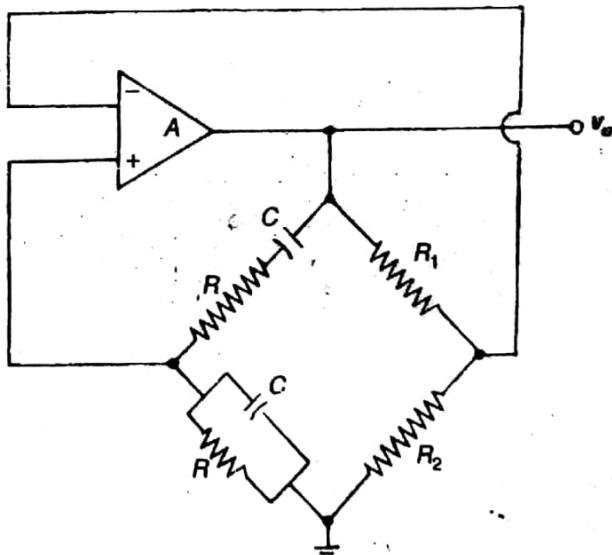


Fig. 14.12 Wien-bridge oscillator using OP AMP.

or

$$v_1 = \frac{q}{C}. \quad (14.23)$$

Differentiating with respect to time, we obtain

$$\frac{dv_1}{dt} = \frac{1}{C} \frac{dq}{dt} = \frac{i}{C} \quad (14.24)$$

where i is the current flowing through the capacitor. Since the input impedance of the OP AMP is infinite, the current i flows through the resistance R also. Therefore, $i = -v_0/R$, so that Eq. (14.24) gives

$$v_0 = -CR \frac{dv_1}{dt} \quad (14.25)$$

Obviously, the output voltage v_0 is proportional to the time derivative of the input voltage v_1 , the proportionality constant being $-CR$.

✓ 9. Integrator: If the positions of R and C in the circuit of Fig. 14.13 are interchanged, the resulting circuit, depicted in Fig. 14.14, is an integrator. As the gain of the OP AMP is infinite, the point G is a virtual ground. The current i flowing through the resistance R is $i = v_1/R$. The input impedance of the OP AMP being infinite, the current i flows through the feedback capacitor C to produce the output voltage v_0 . Therefore,

$$v_0 = -\frac{1}{C} \int_0^t i dt = -\frac{1}{CR} \int_0^t v_1 dt. \quad (14.26)$$

The output voltage v_0 is thus proportional to the time integral of the input voltage v_1 , the proportionality constant being $-1/(CR)$. Hence the circuit is referred to as an *integrator*. Integrators find applications in sweep or ramp generators, in filters, and in simulation studies in analog computers.

The basic integrator circuit of Fig. 14.14 has the drawback that since the capacitor is an open circuit for dc, the dc gain of the OP AMP circuit is infinite. So, any dc voltage at the input would drive the OP AMP output to saturation. To avoid this possibility, a resistance R_1 is connected in parallel with the capacitance C , which limits the dc gain of the circuit. The value of R_1 is so chosen that $R_1 \gg |1/\omega C|$, where ω is the angular frequency of the input signal. Then v_0 is, to a good approximation, given by Eq. (14.26).

10. Voltage-to-current converter: If the output current of a device is proportional to its input signal voltage, the device is called a voltage-to-current converter. The noninverting amplifier circuit of Fig. 14.7, redrawn in Fig. 14.15, can serve as a voltage-to-current converter, the load resistance R_L replacing the resistance R_f . If i_L is the current through R_L , we have

$$i_L = \frac{v_1}{R_1} \quad (14.27)$$

the point G having the input voltage v_1 due to the infinite gain of the OP AMP. Observe that the current i_L does not depend on the load resistance R_L and is proportional to the input voltage v_1 . Voltage-to-current converters are used in analog-to-digital converters and in driving the deflection coils of cathode ray tubes in television.

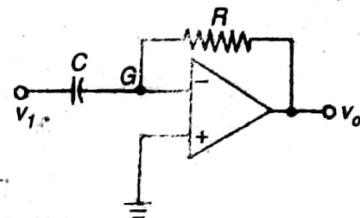


Fig. 14.13 Differentiator.

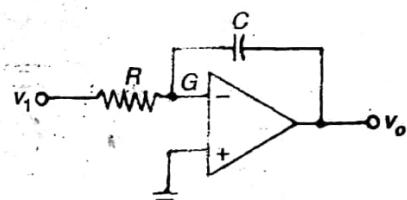


Fig. 14.14 Integrator.

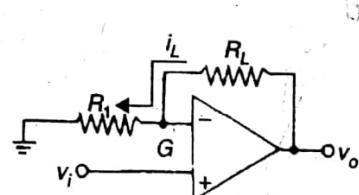


Fig. 14.15 Voltage-to-current converter.

11. Current-to-voltage converter: If the output voltage of a device is proportional to its input signal current, the device is termed a current-to-voltage converter. Figure 14.16 shows the circuit diagram of a current-to-voltage converter. The input signal current i_s can be provided by the output current (independent of the load) of a photocell or a photomultiplier tube. Since the point G serves as a virtual ground, the current through the resistance R_s must be zero. The whole input signal current i_s flows through the feedback resistor R_f to produce the output voltage v_o . We have

$$v_o = -i_s R_f \quad (14.28)$$

Thus the output voltage v_o is proportional to the input current i_s , the proportionality constant being $-R_f$.

12. Logarithmic amplifier: If the feedback resistor R_f in the circuit of Fig. 14.6 is replaced by a diode, we obtain a logarithmic amplifier giving an output voltage v_o that changes as the logarithm of the input voltage v_1 . The circuit of a logarithmic amplifier is shown in Fig. 14.17.

The volt-ampere characteristic of the diode is given by Eq. (5.5), viz.

$$i = I_s \left[\exp\left(\frac{ev_f}{\eta k_B T}\right) - 1 \right]$$

Here i is the diode current for the forward voltage v_f . If $e v_f / (\eta k_B T) \gg 1$ or, $i \gg I_s$, we have

$$i \approx I_s \exp\left(\frac{ev_f}{\eta k_B T}\right)$$

$$\text{or, } \ln\left(\frac{i}{I_s}\right) = \frac{ev_f}{\eta k_B T}$$

$$\text{or, } v_f = \frac{\eta k_B T}{e} \ln\left(\frac{i}{I_s}\right)$$

Since G is a virtual ground in Fig. 14.17, we have $i = v_1/R_1$ and the output voltage is

$$v_o = -v_f = -\frac{\eta k_B T}{e} \ln\left(\frac{v_1}{I_s R_1}\right).$$

Hence v_o responds to the logarithm of v_1 .

13. Half-wave rectifier: The half-wave rectifier circuit of Fig. 14.18 operates in the following manner. During the negative half cycle of the sinusoidal input voltage v_i (Fig. 14.19), the voltage v is positive, since v_i is fed to the inverting terminal of the OP AMP. Now, D_1 is forward biased and D_2 is reverse biased. So, D_1 is ON and D_2 is OFF. Neglecting the diode resistance, the gain of the inverting amplifier is $-R_2/R_1$. Thus $v_o = -(R_2/R_1)v_i$. The amplified output voltage v_o is positive, as shown in Fig. 14.19.

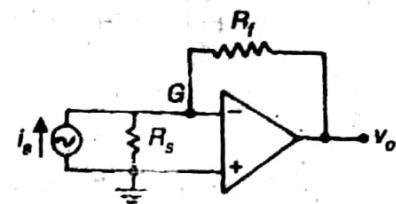


Fig. 14.16 Current-to-voltage converter.

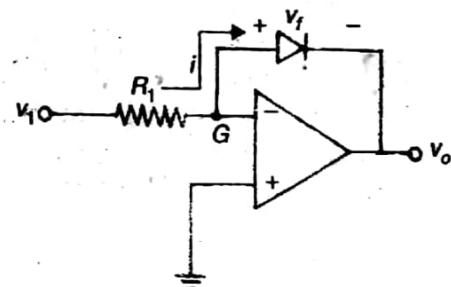


Fig. 14.17 A logarithmic amplifier for positive input voltage v_1 .

Common mode rejection Ratio (CMRR) :-

(4)

→ An op-amp is basically a differential amplifier with signal voltages v_1 and v_2 each measured with respect to ground applied to the non-inverting and inverting terminal^a, respectively.

In practice, difference signal $v_d (= v_1 - v_2)$ and the common-mode or average signal $v_c (= \frac{v_1 + v_2}{2})$ are amplified to produce the output voltage. so, we have,

$$v_o = A_1 v_1 + A_2 v_2 \dots (i)$$

A_1 → voltage gain when terminal a is grounded.

A_2 → voltage gain when terminal b is grounded.

$$v_1 - v_2 = v_d \dots (ii)$$

$$v_1 + v_2 = 2v_c \dots (iii)$$

$$\text{so, } v_1 = v_c + \frac{1}{2}v_d$$

$$v_2 = v_c - \frac{1}{2}v_d$$

$$\text{from eqn (i), } v_o = \frac{1}{2} (A_1 - A_2) v_d + (A_1 + A_2) v_c$$

$$\Rightarrow v_o = A_d v_d + A_c v_c$$

$$\text{where, } A_d = \frac{1}{2} (A_1 - A_2) \text{ and } A_c = A_1 + A_2$$

A_d → voltage gain for the difference signal v_d

A_c → voltage gain for the common-mode signal v_c

$$\text{CMRR} = \left| \frac{A_d}{A_c} \right|$$

A_d needs to be large and A_c very small, the amplifier must be so designed that the CMRR is much larger than unity. For good op-amps, the ratio is above 100 dB.

D) Practical op-AMPS

- Practical op-AMPS exhibit some limitations when compared with the ideal amplifier characteristics.
- Input and output resistances are finite and non-zero in practical amplifiers.
- R_{ic} → the common mode input resistance seen between each input and ground terminals. Two common mode input resistances are almost equal and their values are very high.
- R_{id} → the differential input resistance, seen between the two input terminals, value is also high but it is less than R_{ic} .
- R_o → the output resistance seen between the output terminal and ground. Both the input terminal connected to the ground.

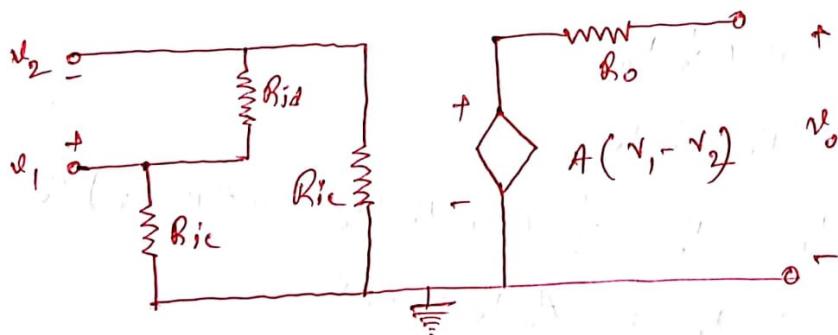


Fig: Equivalent circuit of a practical op-AMP.