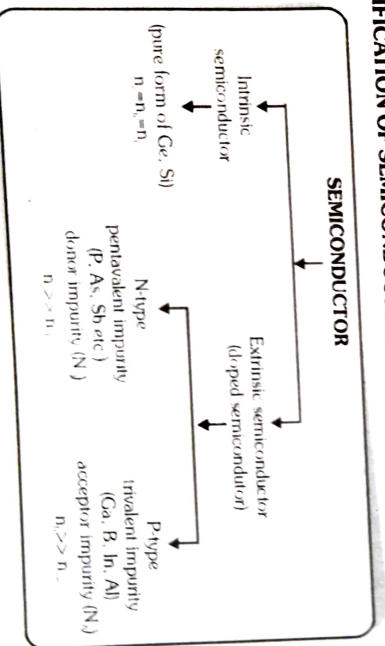


# Semiconductor & Digital Electronics

## COMPARISON BETWEEN CONDUCTOR, SEMICONDUCTOR AND INSULATOR

Properties	Conductor	Semiconductor	Insulator
Resistivity	$10^{-8} - 10^{-6} \Omega m$	$10^{-5} - 10^3 \Omega m$	$10^{11} - 10^{18} \Omega m$
Conductivity	$10^7 - 10^8 \text{ mho/m}$	$10^{-6} - 10^5 \text{ mho/m}$	$10^{-19} - 10^{-11} \text{ mho/m}$
Temp. Coefficient of resistance ( $\alpha$ )	Positive	Negative	Negative
Current	Due to free electrons	Due to electrons and holes	No current
Energy band diagram	<p>Conductor</p>	<p>Semiconductor</p>	<p>Insulator</p>
Forbidden energy gap	$\approx 0 \text{ eV}$	$\approx 1 \text{ eV}$	$\geq 3 \text{ eV}$
Example	Pt, Al, Cu, Ag	Ge, Si, GaAs, GaP, Zn	Wood, plastic, Diamond, mica

- Number of electrons reaching from valence band to conduction band :  $n = AT^{3/2} e^{-\frac{E_g}{2kT}}$
- CLASSIFICATION OF SEMICONDUCTORS :



- **MASS-ACTION LAW** :  $n_i^2 = n_e \cdot n_h$
- For N-type semiconductor  $n_e \approx N_D$
- For P-type semiconductor  $n_h \approx N_A$

### CONDUCTION IN SEMICONDUCTOR

Intrinsic semiconductor	P - type	N - type
$n_e = n_h$	$n_e \gg n_h$	$n_h \gg n_e$
$j = ne [v_e + v_h]$ (Current density)	$j \approx e n_e v_e$	$j \approx e n_h v_h$
$\sigma = \frac{1}{\rho} = en [\mu_e + \mu_h]$ (Conductivity)	$\sigma \approx \frac{1}{\rho} \approx e n_e \mu_e$	$\sigma \approx \frac{1}{\rho} \approx e n_h \mu_h$





## BREAKDOWN ARE OF TWO TYPES

**Zener Break down**

Where covalent bonds of depletion layer, itself break, due to high electric field of very high Reverse bias voltage.

This phenomena take place in

- (i) P - N junction having "High doping"
  - (ii) P - N junction having thin depletion layer
- Here P - N junction does not damage permanently  
"In D.C voltage stabilizer zener phenomena is used".

**Avalanche Break down**







Here covalent bonds of depletion layers are broken by collision of "Minorities" which acquire high kinetic energy from high electric field of very-very high reverse bias voltage.

This phenomena takes place in

- (i) P - N junction having "Low doping"
  - (ii) P - N junction having thick depletion layer
- Here P - N junction damages permanently due to abruptly increment of minorities during repeatabe collisions.

**APPLICATION OF DIODE**

- **Zener diode** : It is highly doped p-n junction diode used as a voltage regulator.
- **Photo diode** : A p-n junction diode use to detect light signals operated in reverse bias.
- **LED** : A p-n junction device that emits optical radiation under forward bias conditions
- **Solar cell** : Generates emf of its own due to the effect of sun radiations.

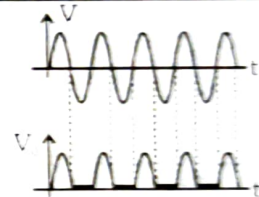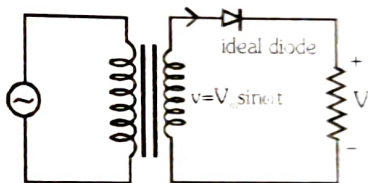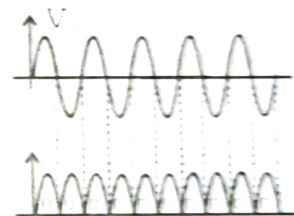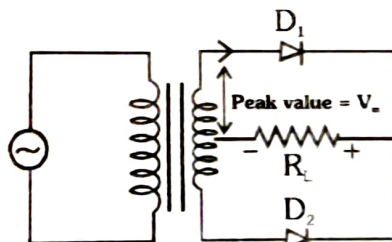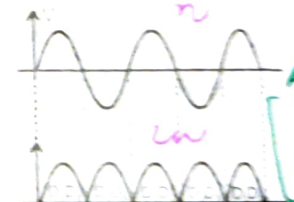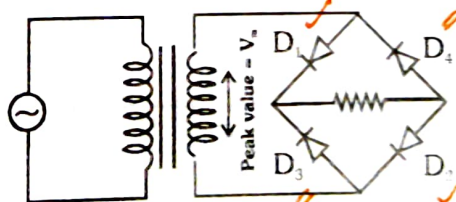**HALF WAVE RECTIFIER****CENTRE - TAP FULL WAVE RECTIFIER****FULL WAVE BRIDGE RECTIFIER**

**RIPPLE FACTOR :**  $r = \frac{I_{r_{rms}}}{I_{dc}}$


- ☐ For HWR  $r = 1.21$
- ☐ For FWR  $r = 0.48$

**RECTIFIER EFFICIENCY:**  $\eta = \frac{P_{dc}}{P_{ac}} = \frac{I_{dc}^2 R_L}{I_{rms}^2 (R_L + R_f)}$


For HWR :  $\eta = \frac{40.6}{1 + \frac{R_f}{R_L}}$  & FWR  $\eta = \frac{81.2}{1 - \frac{R_f}{R_L}}$

# FOR TRANSISTOR

$$I_i = I_B + I_C$$

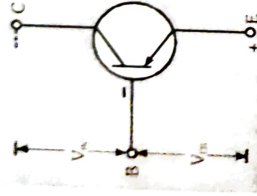

(a)

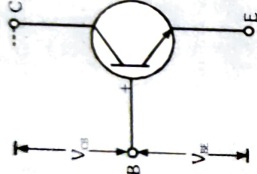

(b)

## COMPARATIVE STUDY OF TRANSISTOR CONFIGURATIONS

- Common Base (CB)
- Common Emitter (CE)
- Common Collector (CC)

	CB	CE	CC
<b>Input Resistance</b>	Low ( $100 \Omega$ )	High ( $750 \Omega$ )	Very High $\approx 750 \text{ k}\Omega$
<b>Output resistance</b>	Very High	High	Low
<b>Current Gain</b>	$(A_i \propto \alpha)$	$(A_i \text{ or } \beta)$	$(A_i \text{ or } \gamma)$
	$\alpha = \frac{I_C}{I_E} < 1$	$\beta = \frac{I_C}{I_B} > 1$ <i>missing</i>	$\gamma = \frac{I_E}{I_B} > 1$
<b>Voltage Gain</b>	$A_v = \frac{V_o}{V_i} = \frac{I_C R_L}{I_E R_i}$	$A_v = \frac{V_o}{V_i} = \frac{I_C R_L}{I_B R_i}$	$A_v = \frac{V_o}{V_i} = \frac{I_E R_L}{I_B R_i}$
	$A_v = \alpha \frac{R_L}{R_i} \approx 150$	$A_v = \beta \frac{R_L}{R_i} \approx 500$ <i>1500</i>	$A_v = \gamma \frac{R_L}{R_i} < 1$
<b>Power Gain</b>	$A_p = \frac{P_o}{P_i} = \alpha^2 \frac{R_L}{R_i}$	$A_p = \frac{P_o}{P_i} = \beta^2 \frac{R_L}{R_i}$	$A_p = \frac{P_o}{P_i} = \gamma^2 \frac{R_L}{R_i}$
<b>Phase difference (between output and input)</b>	same phase	opposite phase	same phase
<b>Application</b>	For High Frequency	For Audible frequency	For Impedance Matching

## TRANSISTOR CHARACTERISTICS

□ <b>Input resistance (<math>r_i</math>)</b>	$\left( \frac{\Delta V_{BE}}{\Delta I_B} \right)_{V_{CE} = \text{constant}}$	□ <b>Current amplification factor</b>	$\beta_{ac} = \left( \frac{\Delta I_C}{\Delta I_B} \right)_{V_{CE} = \text{constant}}$
□ <b>Output resistance (<math>r_o</math>)</b>	$\left( \frac{\Delta V_{CE}}{\Delta I_C} \right)_{I_B = \text{constant}}$	• <b>For CE (n-p-n)</b>	$\alpha_{ac} = \left( \frac{\Delta I_C}{\Delta I_E} \right)_{V_{CE} = \text{constant}}$
□ <b>Relation between <math>\alpha</math> and <math>\beta</math> :</b> $\beta = \frac{\alpha}{1 - \alpha}$ & $\alpha = \frac{\beta}{1 + \beta}$		• <b>For CB (p-n-p)</b>	

## APPLICATIONS OF TRANSISTORS

**There are three regions of transistor operation:**

- **Cut off region \* Active region \* Saturation region**

□ **Transistor as Voltage amplifier**

- To operate it as an amplifier we need to fix its operating voltage somewhere in active region where it increases the strength of input ac signal and produces an amplified output signal.

• Voltage gain  $A_V = \frac{V_o}{V_i} = -\beta_{ac} \frac{R_{out}}{R_{in}}$

• Power gain  $A_p = A_V \times \beta_{ac}$

□ **Transistor as a Switch**

A transistor can be used as a switch if it is operated in its cutoff and saturation states only.

□ **Transistor as an Oscillator**

An oscillator is a generator of an ac signal using positive feedback


Frequency of oscillations if  $f = \frac{1}{2\pi\sqrt{LC}}$

□ **Relation between  $\alpha$ ,  $\beta$  and  $\gamma$  :**

$\beta = \frac{\alpha}{1 - \alpha}$ ,  $\gamma = 1 + \beta$ ,  $\gamma = \frac{1}{1 - \alpha}$

## IMPORTANT NOTES

Q. Current through Zener diode

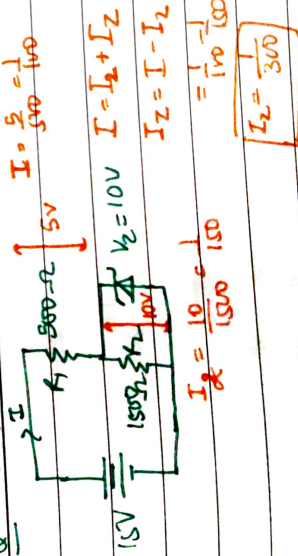

Q.  $I_B = 35 \text{ mA}$  find  $R_B$ ?



$I_B = 35 \text{ mA}$   
 $q = 35 \times 10^3$