

Total no. of pages: 02

**FOURTH SEMESTER  
END SEMESTER EXAMINATION**

DTU/ELI5/CO/  
Roll No..... 049

**B.Tech (CO /IT/SE)  
MAY-2017**

**EC 262 DIGITAL ELECTRONICS**

**TIME: 3 Hrs.**

**Maximum Marks: 40**

**Note:- Attempt total five questions out of the following questions, Q1. is compulsory.  
Assume suitable missing data, if any.**

- Q1.** Write short notes on the following with reference to the various logic families: [2\*4]
- a. Volatile and Non-volatile memory. ✕
  - b. Different types of ROM.
  - c. Flash type Analog to Digital Converter.
  - d. Difference between latches and flip-flops.
- Q2. (i).** Design a Gray to BCD converter using one 1:16 demultiplexer with complemented outputs and NAND gates. [4]
- (ii)** Explain the working of a 4 bit R-2R ladder type Digital to Analog Converter with suitable example. [4]
- Q3. (i).** Design a combinational circuit that generates the 9's complement of a BCD digit. [4]
- (ii).** Realize  $F(A,B,C,D) = \prod(0,1,3,7,9,10,11,13,14,15)$  using: [4]
- a. 4 to 16 line decoder with complemented outputs and AND gates.
  - b. 4 : 1 Multiplexer
- Q4. (i).** Implement the BCD counter using JK flip-flop. [4]
- (ii).** Explain the working principle of the Master Slave flip-flop with suitable diagram. [4]

- Q5. (i). Find the equivalent analog output, for the circuit shown in Fig.5(i), if digital input is 1101 and the reference voltage for logic 1 is 5Volts. [4]

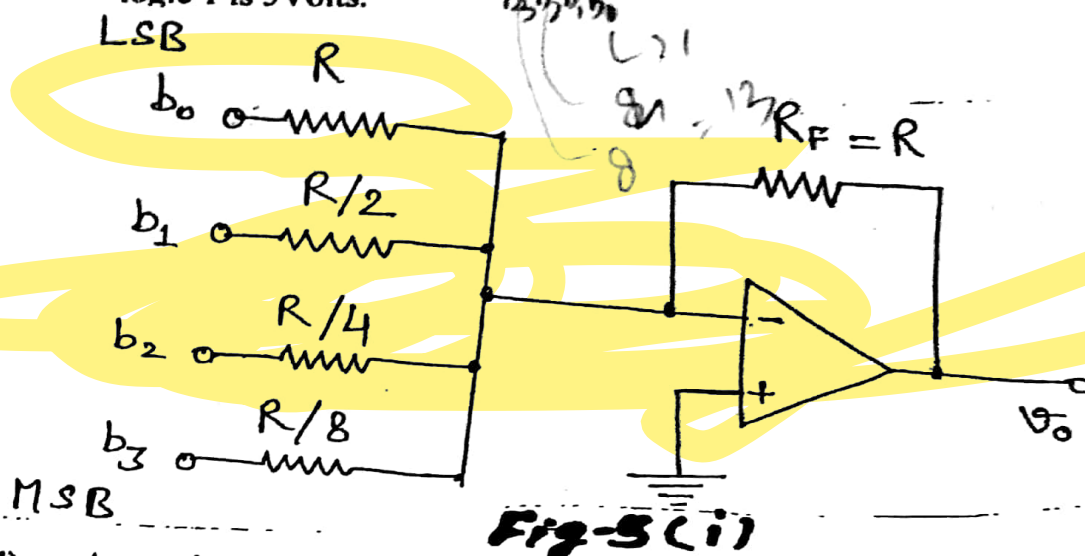


Fig-5(i)

- (ii). Assuming that all flip-flops are in reset condition initially, for the circuit shown in Fig.5(ii), find the count sequence observed at  $Q_A$  till the seventh clock pulse. [4]

Output