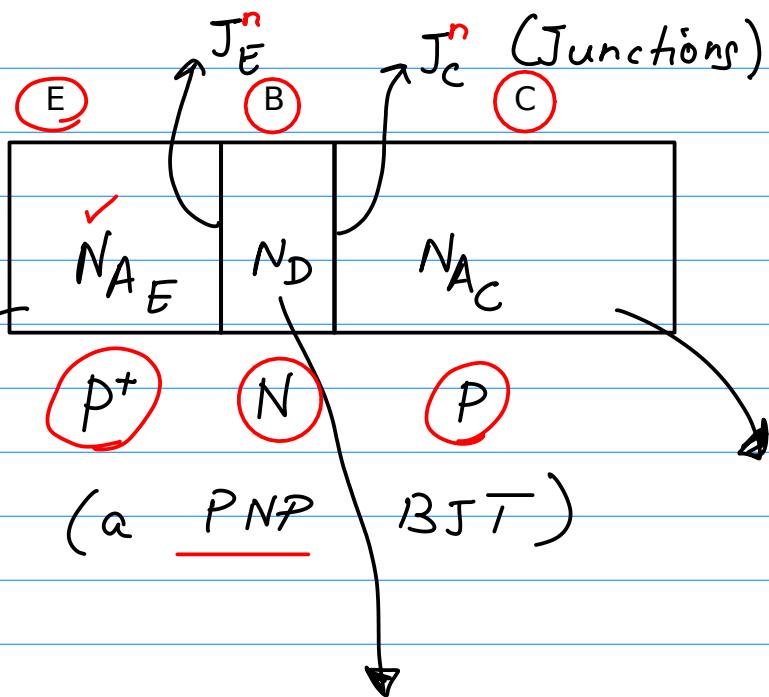


Bipolar Junction transistor

3 electrode




Dopings -

$$N_{A_E} > N_D > N_{A_C}$$

Area (width)
 $C > E > B$



Electrical Isolation
Between E & C

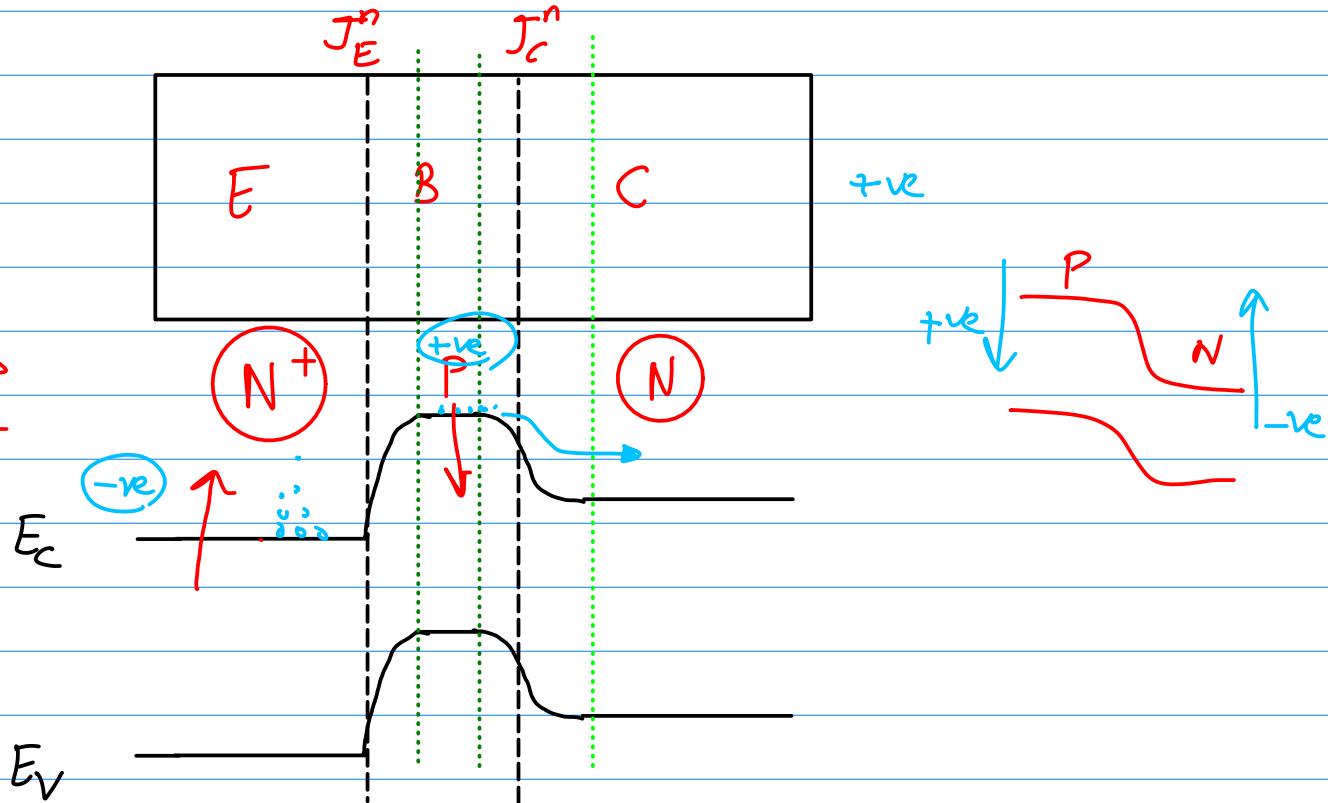


$$\frac{1}{q} \frac{dE_C}{dx} = \vec{E}$$

MODES OF OPERATION

Mode	I_E^n	I_C^n	APPLICATION
1) <u>Forward Active</u>	F.B.	R.B.	Amplification
2) Saturation <u>ON</u>	F.B.	F.B.	Switching
3) Cut-off <u>OFF</u>	R.B.	R.B.	(Digital- ON/OFF I/O)
4) Reverse Active	R.B.	F.B.	Rarely used for Amp.

OPERATION (ACTIVE MODE)


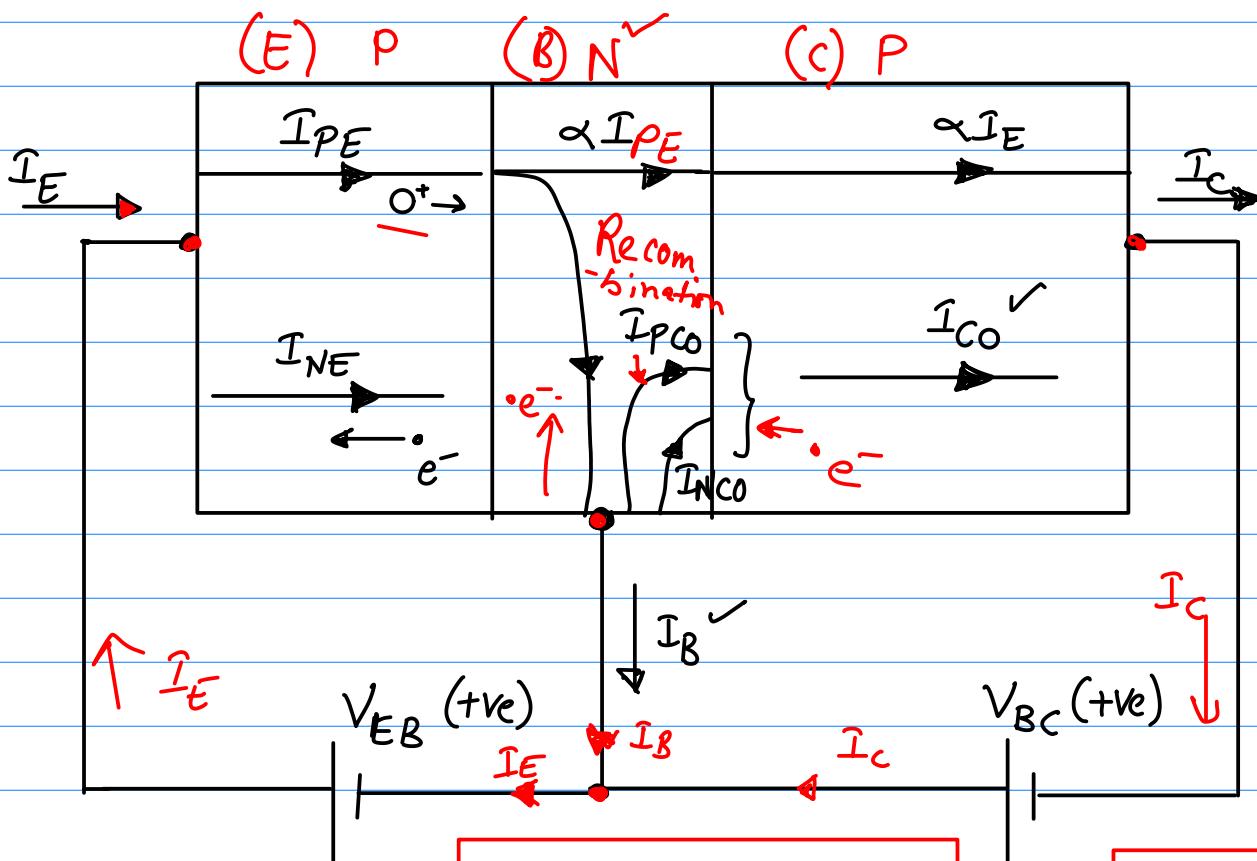


$$I_C = \alpha I_E + I_{CO}$$

* * $I_E = I_C + I_B$ (Always) [KCL]

PNP or NPN
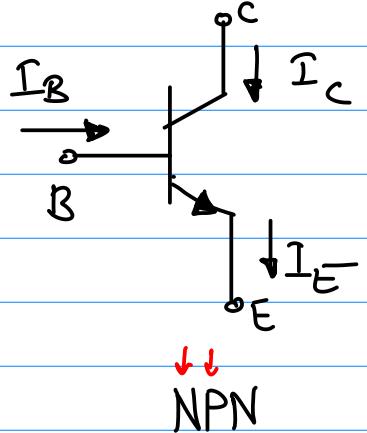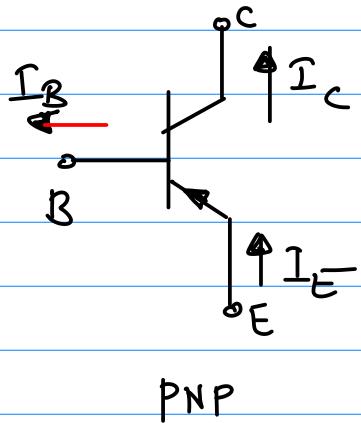
$$I_E = I_{PE} + \frac{I_{NE}}{\beta_{NE}} \approx I_{PE} \quad (\because N_{AE} \gg N_D)$$



By KVL -

* * $V_{CE} + V_{EB} + V_{BC} = 0$

$$\therefore V_C - V_E + V_E - V_B + V_B - V_C = 0$$


[NPN or PNP] (always)

CONFIGURATIONS

Config	i/p	o/p	Common	Av	vol gain, Ai	Current gain,	i/p resist. Ri	o/p resist. Ro
CE <i>(Common emitter)</i>	B	C	E	High ✓	High ✓	High ✓	High ✓	High ✓
CC <i>[Emitter Follower] (Common collector)</i>	B	E	C	Low ≈ 1 < 1	v. high	v. high	v. low	v. low
CB <i>(common base)</i>	E	C	B	V. high	Low ≈ 1 < 1	v. low	v. high	v. high

CE → power gain $A_p = A_v \cdot A_i$ = highest

EARLY EFFECT / BASE WIDTH MODULATION

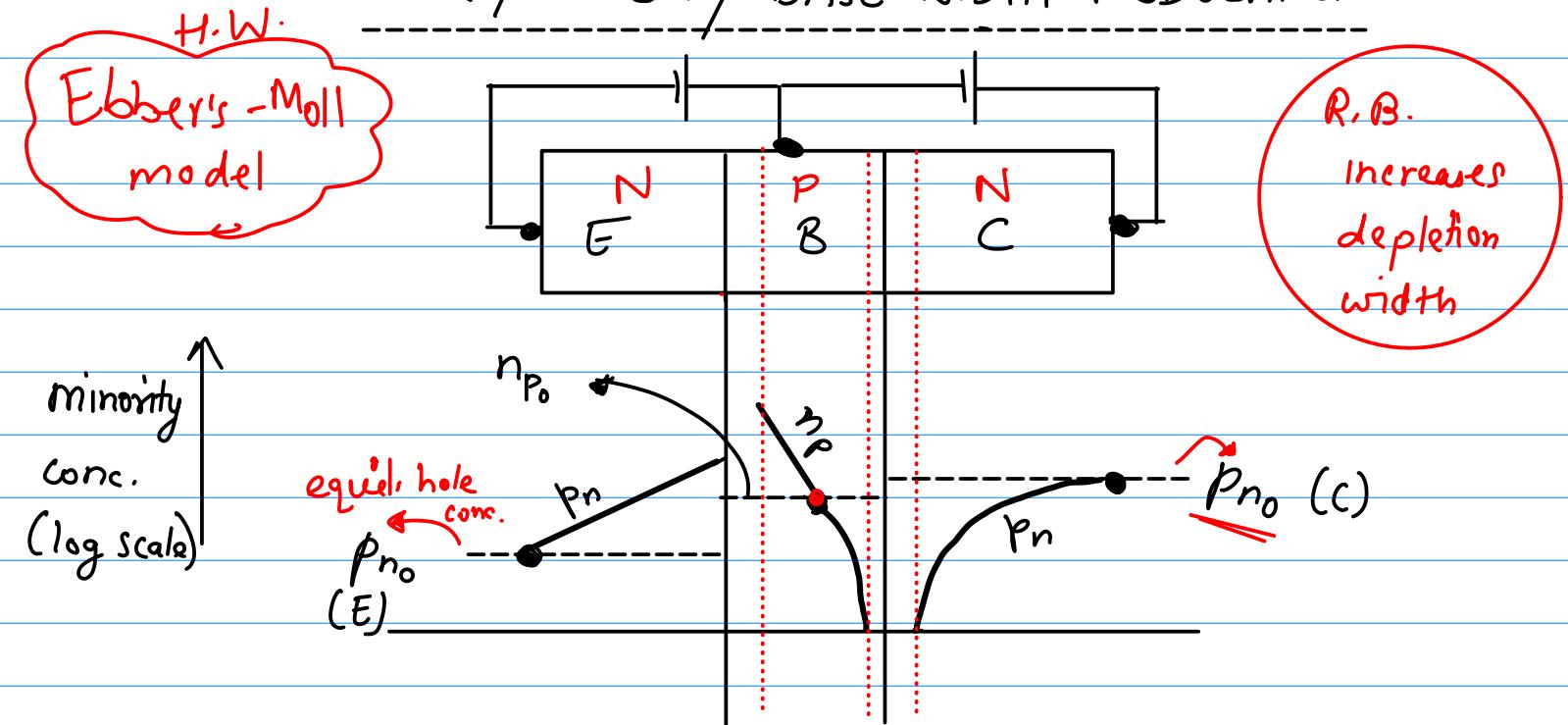


External contacts are always under thermal equilibrium, so concentrations near the contacts are the equilibrium concentrations.

- * Collector junction is R.B. so, increasing V_{cb} causes depletion width to increase.
- * When depletion region increases into base, 3 things happen:
 - ✓ 1. Recombination decreases. So base current decreases (*Recomb happens in quasi-neutral base*)
 - ✓ 2. Alpha increases because recombination decreases.
 - ✓ 3. Emitter current increases because minority concentration gradient increases in the base.

as J_C^r R.B. \uparrow

*$W_{base-effective} \downarrow$
(B.W. Mod.)*

Base width modulation

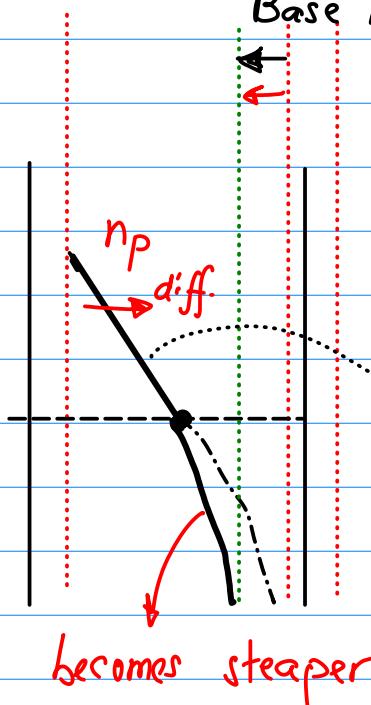

I_E is due to diffusion of these minority carriers towards C.

$I_E \uparrow$ (slightly)

Punch Through:

If base becomes completely depleted, then no recombination takes place in the base and collector current shoots up.

Since depletion regions have electric fields, collector and emitter are now electrically connected (base acts as short circuit) because there is a continuous electric field region from collector to emitter. Now reverse bias on Collector junction reduces barrier of emitter junction and both emitter and collector currents increase to very high values.

* Due to R.B. collector junction might also go into breakdown and that might cause current to increase rapidly.

Any of these effects might cause burning of the BJT.



Punch-through




1. Common Base Config.:



i/p at E ✓

o/p at C ✓

Common terminal = B

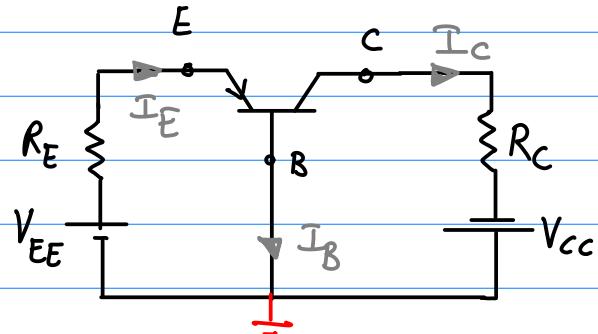

* I/p Characteristics : $V_{EB} = f_1(I_E, V_{CB})$

Dependent var. independent var.

* O/p Characteristics : $I_C = f_2(I_E, V_{CB})$

i) O/p Char: * $I_C = \alpha I_E + I_{CO}$

$$I_E = I_C + I_B$$

I_C independent of V_{CB} (O/p current) (O/p vol, how?) (KCL)


* ACTIVE :

* $I_C = \alpha I_E + I_{CO}$

$\Rightarrow I_C \approx \alpha I_E$


$\alpha < 1$ but $\alpha \approx 1$

$I_C < I_E$ (slightly)

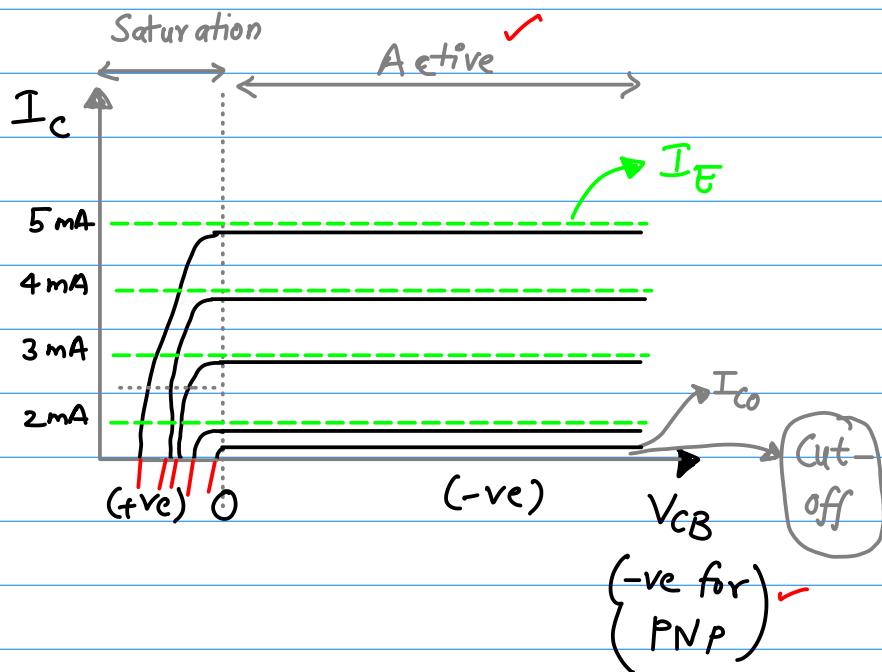

* As $V_{CB} \uparrow$ (-ve); $\alpha \uparrow$, $I_E \uparrow$ (slightly) so, $I_C \uparrow$

(negligible changes)

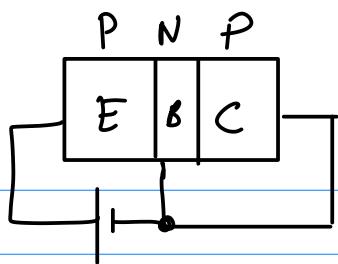

→ Active mode

∴ S.C. is treated as
R.B. in BJT

* Cut-off -

$$I_E = 0 ; I_c = I_{c0}$$

* Saturation -

$$V_{CB} = \begin{matrix} +ve \\ (\text{small}) \end{matrix} \rightarrow J_c^n = F.B.$$

(out-of C terminal)


$$I_c = \alpha I_E - I_{c0} \left[\exp\left(\frac{V_{CB}}{\eta V_T}\right) - 1 \right]$$

-ve sign ∵ I_E is B to C but F.B. current at J_c^n will be C to B.

as $V_{CB} \uparrow (+ve)$, I_c quickly ↓

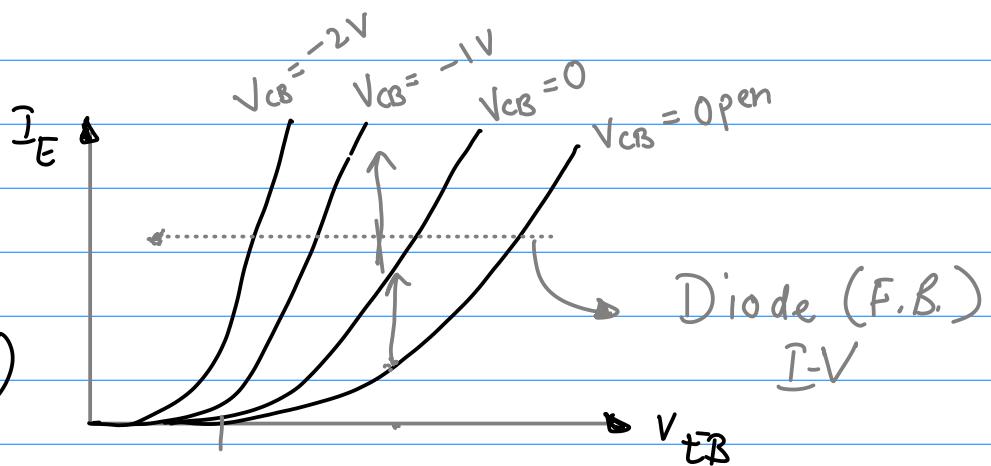2. T/P char. :

$(I_E \uparrow \text{ only slightly as } V_{CB} (-ve) \uparrow)$



$$V_Y = 0.7V$$

for Si

= 0.2 V for Ge

Properties - (CB)

1. Lowest R_i ($< 100 \Omega$) [i/p is F.B. Diode]

2. Highest R_o (output resistance)

3. Lowest Current Gain -
o/p current = I_C^{\checkmark}
i/p current = $I_E^{\cancel{E}}$

$$I_C \approx \alpha I_E$$

$$\Rightarrow \text{Current gain} = A_I = \frac{\text{o/p curr.}}{\text{i/p curr.}}$$

$$\Rightarrow A_I = \frac{I_C}{I_E} = \alpha$$

$$\begin{cases} \alpha < 1 \\ \alpha \approx 1 \end{cases}$$

(+ve)

4. Highest vol. gain A_v (also +ve)

5. Power Gain, $A_p = A_v \cdot A_I = \text{moderate}$

6. Phase (or angle) difference between o/p & i/p voltages, $\phi = 0^\circ$ ($\because A_v = +ve$)

7. Largest Bandwidth. Suitable for high frequency ops.

Applications -

1. Constant current source. [Since o/p current doesn't change (or depend on) o/p vol. or load.]


CB is known as "**CURRENT BUFFER**" ($I_C \approx I_E$)

2. Non inverting vol. amplifier ($A_V = +ve$)


3. High freq. (or speed) amp.

4. Impedance matching [low imp to high imp.]
 ↓
 (or resistance)

Imp. Match. ckt

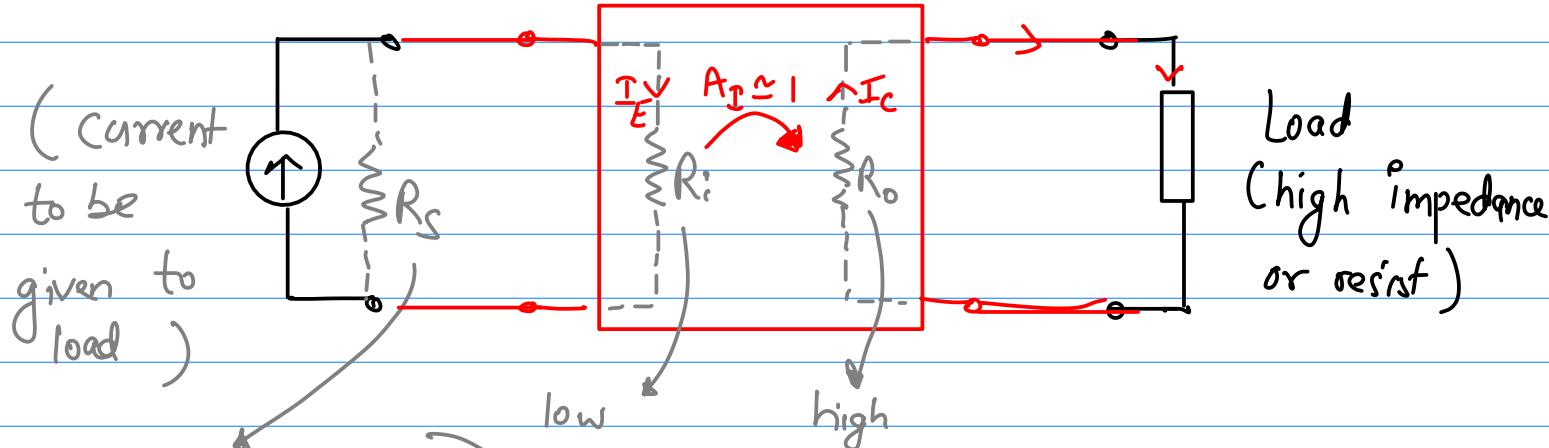


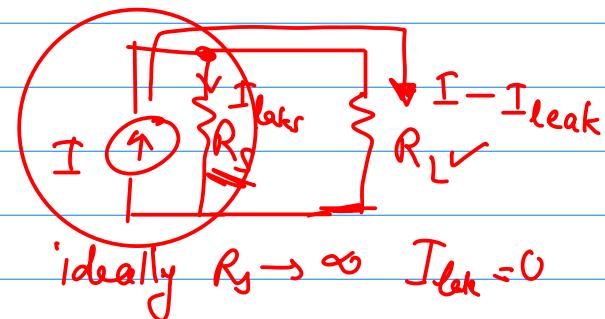Low Source
resistance (bad source)
in parallel to current
source



→ COMMON Emitter - (CE)

'i/p at B
o/p at C
E → common

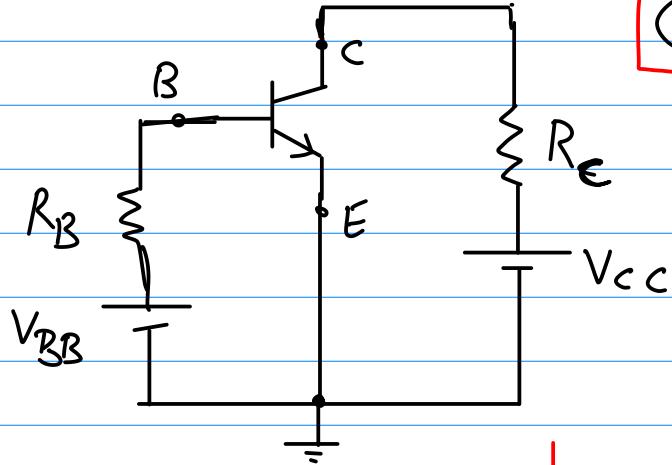

(NPN BJT)

$$I_C = \alpha I_E + I_{CO} \quad (\text{always})$$

$$I_E = I_C + I_B \quad (\text{always}) \quad (KCL)$$

$$I_C = \alpha (I_C + I_B) + I_{CO}$$

α = CB current gain

β = CE current gain

$$\Rightarrow I_C = \left(\frac{\alpha}{1-\alpha} \right) I_B + \frac{I_{CO}}{1-\alpha}$$

Let

$$\beta = \frac{\alpha}{1-\alpha}$$

So,

$$I_C = \beta I_B + (1+\beta) I_{CO}$$

$$\alpha = 0.98$$


$$\beta = 49$$

* I/P char -


i/p Current
($V_{CE} \uparrow$)

$\propto V_C \uparrow, R_{BS} \propto I_C^n \uparrow,$

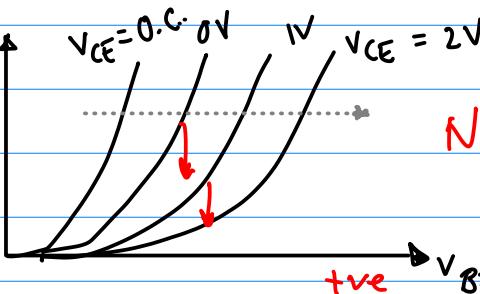$\alpha \uparrow, I_B \downarrow$ (recomb. reduced)



Not f-B. current curve

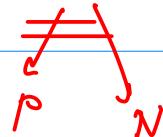

I. Active Mode -

$$I_C = \beta I_B + (1+\beta) I_{C0}$$

$$I_C = f_1(I_B, V_{CE})$$

I_C seems to be independent of V_{CE}

But actually as $V_{CE} \uparrow$ ($= V_C - V_E = V_C$; $\because V_E = 0$)


$\therefore V_C \uparrow$, Collector junction (J_C^n) R.B. \uparrow ,

$\alpha \uparrow$ (due to early effect), so, $\beta \uparrow\uparrow$

e.g. $\alpha = 0.98$ (large increment)
 \downarrow \downarrow \downarrow
 $(> 1\% \uparrow)$ $\alpha = 0.99$ $\beta = 99$ ($> 100\% \uparrow$)

as $\beta \uparrow\uparrow$, $I_B \downarrow$ (\because recomb. decreases)


so, I_C also \uparrow .

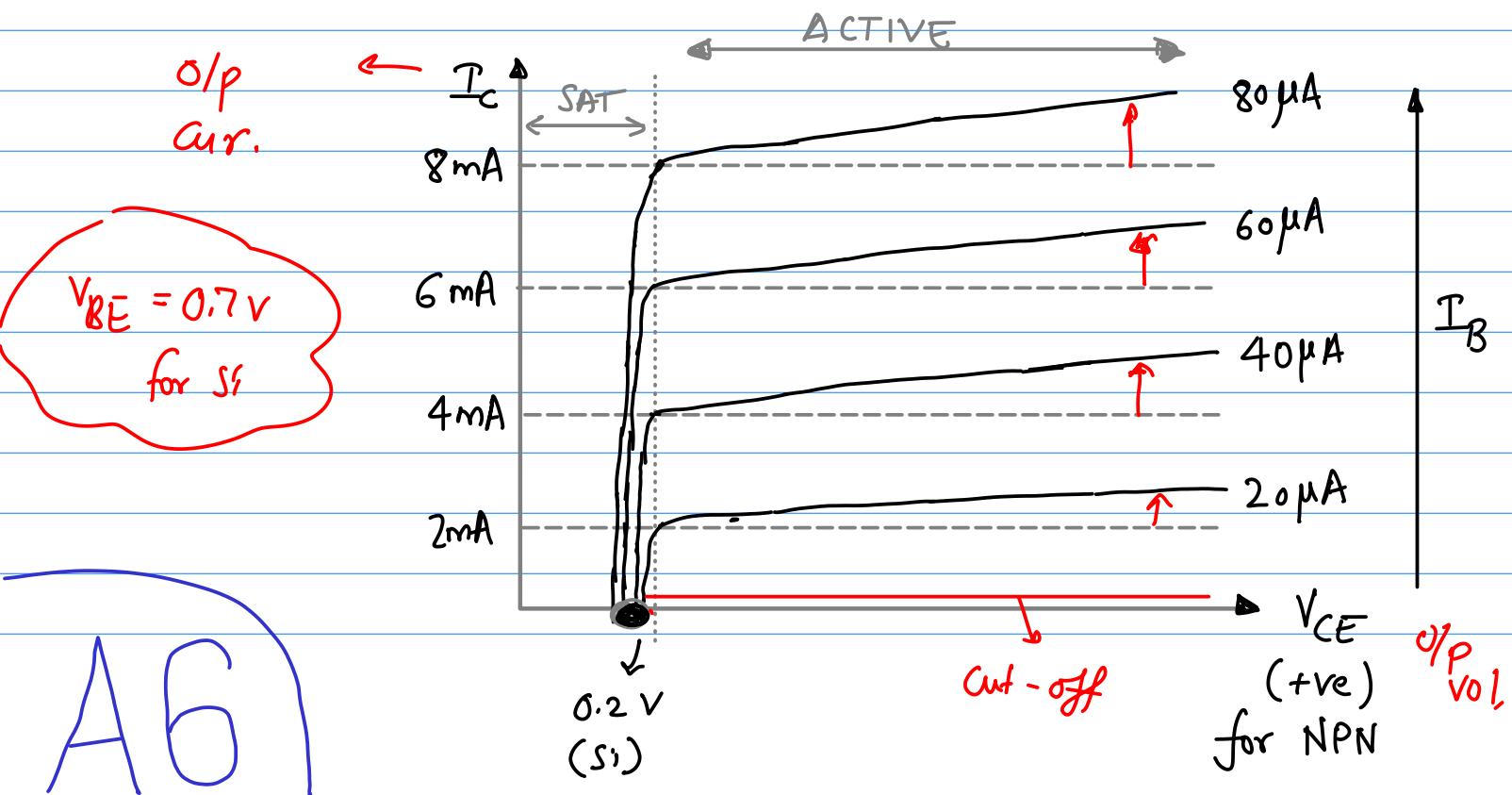

2. Saturation -

KVL

$$V_{CC} = I_C R_C + V_{CE}$$

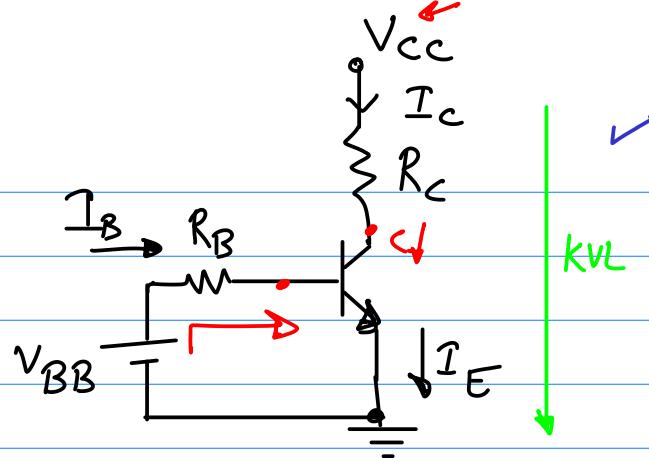

$$\Rightarrow I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

load
line

(or)

$$V_{CE} = V_{CC} - I_C R_C$$

as $V_{BB} \uparrow$, $I_B \uparrow$ ($v_{BE} \uparrow$ slightly), so, $I_C \uparrow$
 $I_C \approx \beta I_B$ (active)
 so, $\underline{V_{CE}}$ ↓

But V_{CE} cannot go below 0.2 V (for Si)

So, as $V_{BB} \uparrow$, $V_{CE} \downarrow$ & finally becomes constant at 0.2 V

So, I_c becomes constant beyond this point.

i.e. I_c doesn't ↑ as I_B ↑

(saturates)


at Saturation,

$$V_{BE} = 0.8V$$

$$V_{CE} = 0.2V$$

} (Silicon)

As KVL $V_{CB} + V_{BE} + V_{EC} = 0$

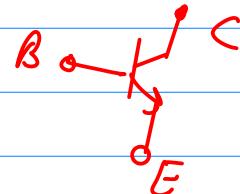

$$\text{So, } \underline{V_{CB}} = -0.8 + 0.2 = -0.6V$$

or $V_{BC} = 0.6V$ (Forward bias for NPN J_C^n)

* So, both J_C^n & J_E^n are F.B \Rightarrow Saturation

→ How to find 'if CE BJT is in saturation or active mode?

(i) Assume Saturation

$$(ii) \left. \begin{array}{l} \text{KVL} \\ \text{at o/p} \end{array} \right\} I_{C-sat} = \frac{V_{CC} - V_{CE-sat}}{R_C} \quad \begin{array}{l} \xrightarrow{\checkmark} (0.2 \text{ V for Si}) \\ \text{(find } I_{C-sat} \text{)} \end{array}$$

Collector current can't ↑ above I_{C-sat}

$$(ii') \text{ find } I_{B-min} = \frac{I_{C-sat}}{\beta}$$

low $I_B \rightarrow$ active mode

$\uparrow I_B$, eventually we get saturation

(iv) Find actual base current I_B from KVL at input.

(v) * If $I_B > I_{B-min}$, BJT is in saturation & I_{C-sat} is the actual I_C

* If $I_B < I_{B-min}$, BJT is in active mode

& $I_C \neq I_{C-sat}$ but $I_C = \beta I_B + (1+\beta) I_{C_0}$

$\Rightarrow I_C \approx \beta I_B$ * for active mode only

* Over-drive factor = $\frac{I_B}{I_{B\text{-min}}} (> 1)$ [if BJT in saturation]

* Forced $\beta = \boxed{\beta_{\text{forced}} = \frac{I_{C\text{-sat}}}{I_B}}$


3. Cut-off - for any config.

* Condition for cut-off ↑ is $I_E = 0$ $I_C = \alpha I_F + I_0$
i.e., $I_C = I_{C0}$

* if we make $I_B = 0$ ✓

then $I_C = (1+\beta) I_{C0} = 100 I_{C0}$ (if $\beta = 99$)
(NOT CUT-OFF)

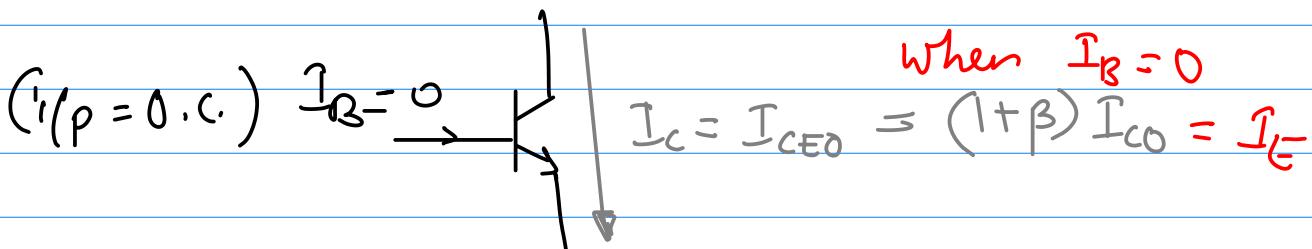
So $I_B = 0$ is not sufficient for cut-off.



when $I_C = I_{CEO} = \frac{(1 + \beta) I_{C0}}{1 - \alpha}$ $I_B = 0$

for cut-off

$I_B = -ve$ needed

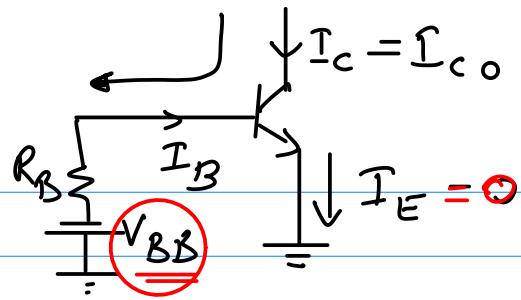

i.e., B-E jn should be slightly R.B.

here

$$I_B = -I_{CBO}$$

So,

$$I_{CEO} > I_{CBO} \gtrsim I_{CO}$$

for Si,

$$V_{BE} = 0 \checkmark$$

is sufficient

for Ge,

$$V_{BE} = -0.1 \text{ V}$$

needed

→ Properties - 1. High i/p resistance R_i ($\sim 1 \text{ k}\Omega$)

2. High vol. gain A_v (also it is -ve)

3. High current gain A_i ($= \beta$) ($\because A_i = \frac{I_c}{I_B}$)

4. Phase diff. between o/p & i/p is

$$\boxed{\phi = 180^\circ}$$


5. Highest power Gain

$$A_p = A_v \cdot A_i$$

* Most popular config for amplifier application.

→ EARLY VOLTAGE -

C.E. (NPN)

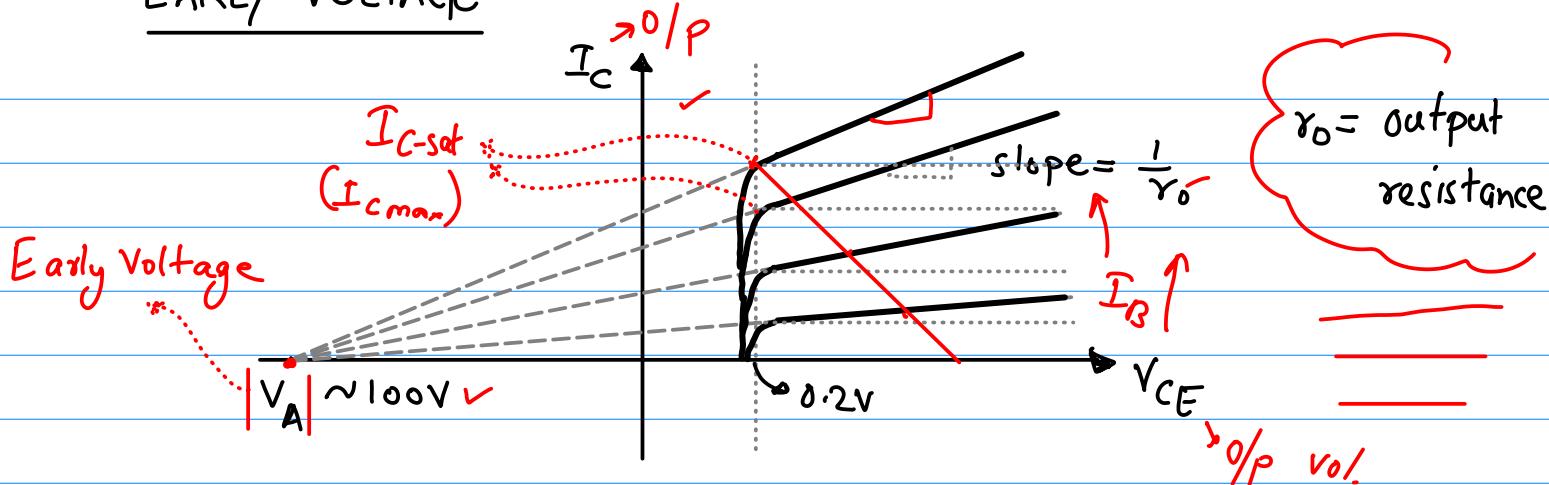


$$\text{Slope} = \frac{1}{r_o} = \frac{I_{C-sat}}{V_A + 0.2} \Rightarrow r_o \approx \frac{V_A}{I_{C-sat}} \underset{\approx V_A}{\sim}$$

* if early effect is neg. $\rightarrow I_C = \text{constant}$ with $V_{CE} \Rightarrow \frac{1}{r_o} \rightarrow 0 \Rightarrow r_o = \infty$

→ How Amplification happens -

Assuming active region,

$$A_V = \frac{\Delta V_O}{\Delta V_I}$$

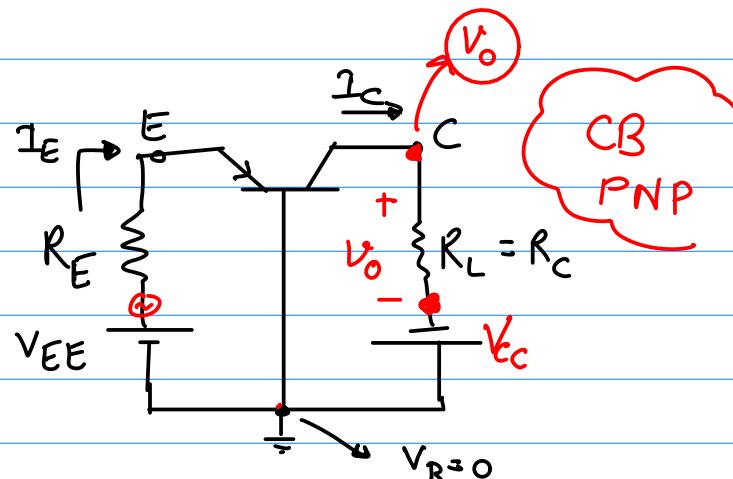

$$I_C \approx \alpha I_E$$

CB, PNP

Let I_E ↑ by ΔI_E (by superimposing a small +ve signal on V_{EE})

$$\text{then } (I_C + \Delta I_C) = \alpha (I_E + \Delta I_E) \Rightarrow \Delta I_C = \alpha \Delta I_E$$

$$V_o = I_C R_L \Rightarrow \underline{\Delta V_o} = \underline{\Delta I_C R_L} = \alpha \underline{\Delta I_E R_L}$$

Let $\underline{\Delta V_i}$ = (change in i/p vol.)

& r_e = dynamic resistance of transistor

* *

$$r_e = \frac{\eta V_T}{I_E}$$

✓


$$r_e = \frac{V_T}{I_E}$$

* *

$$[\because \eta = 1]$$

$$\text{where } V_T = \frac{T}{11,600}$$

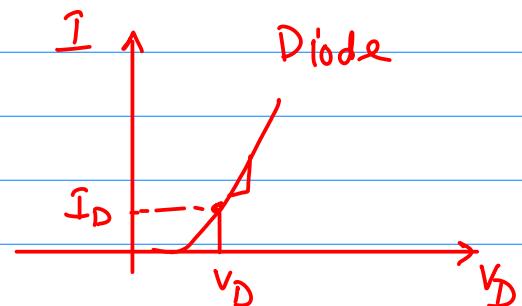Static Resistance = $R_D = \frac{V_D}{I_D}$



Dynamic Resistance = $\boxed{\gamma = \frac{dV_D}{dI_D}}$

for diode \rightarrow

$$I_D = I_0 \left(\exp \left(\frac{V_D}{\eta V_T} \right) - 1 \right)$$

$$\frac{dI_D}{dV_D} = \frac{1}{\eta V_T} I_0 \left(\exp \left(\frac{V_D}{\eta V_T} \right) \right) = \frac{I_D}{\eta V_T}$$

dyn resis

$$\boxed{\gamma = \frac{\eta V_T}{I_D}}$$

Since emitter is f.b., it can be treated like a F.B. diode so, its dyn. resist -

$$r_e = \frac{\eta V_T}{I_E}$$

$$\Delta V_i = \Delta I_E r_e \quad \therefore r_e = \frac{\Delta V_{EB}}{\Delta I_E} = \frac{\Delta V_{EB}}{\Delta I_E}$$

$$A_v = \frac{\Delta V_o}{\Delta V_i} = \frac{\alpha \Delta I_E R_L}{\Delta I_E r_e}$$

$$A_v = \frac{\alpha R_L}{r_e} *$$

$$A_v \propto \frac{R_L}{r_e} \begin{matrix} \rightarrow o/p \text{ side} \\ \rightarrow i/p \text{ side} \\ \text{resist.} \end{matrix}$$


If $R_L > r_e \quad A_v > 1$
 (usually)

- * Amplification comes from ^{having} different o/p & i/p
 resistance
- $(\text{load}) \parallel (r_o) \xrightarrow{\text{BJT}} (\text{dyn resis. of BJT})$

Transfer + resistor = Transistor

Q1) Find all currents if $\beta = 100$ & $I_{C0} = 20\text{nA}$

(a)

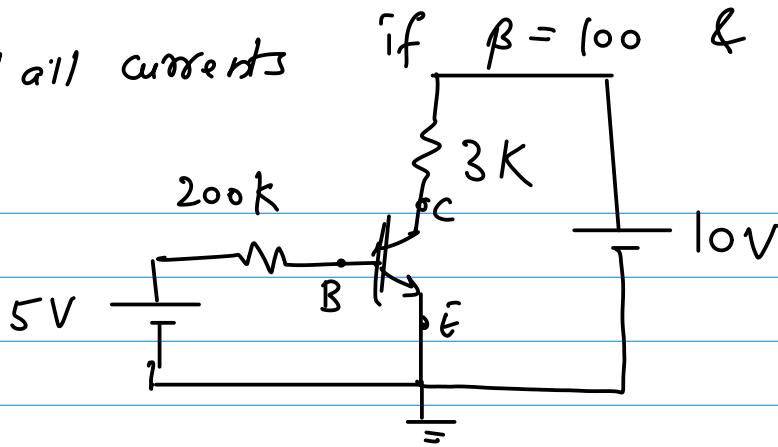

DC Analysis

(large signal analysis)

Sol.

$$I_C = \beta I_B + (1 + \beta) I_{C0} \quad [(\text{E config})]$$

for active

or

$$I_C = \frac{V_{CC} - V_{CE\text{ sat}}}{R_C} \quad \text{for sat.}$$

(i) Assume sat., $V_{CE\text{ sat}} = 0.2\text{V}$ (st)

by KVL, $\underline{I_{C\text{sat}}} = \frac{V_{CE} - V_{CE\text{sat}}}{R_C}$

$$\underline{\underline{I_{C\text{sat}}}} = \frac{10 - 0.2}{3\text{k}} = \frac{9.8}{3} \text{ mA}$$

(ii) $I_{B\text{min}} = \frac{I_{C\text{sat}}}{\beta} = \frac{9.8}{300} \text{ mA} \approx \frac{3.3}{100} \text{ mA}$
 $\approx 33 \mu\text{A}$

(iii) KVL at i/p $V_{BB} - R_B I_B - V_{BE} = 0$
 $\Rightarrow 5 - 200k I_B - 0.7 = 0$

$$I_B = \frac{4.3}{200} \text{ mA} \approx 22 \mu\text{A}$$

$$I_B < I_{B\min}$$

So, BJT is in "Active mode"

$$I_B \approx 21.5 \mu A$$

Now $I_C = \beta I_B + (I_{FB})$


I_{FB} is negligible

$$I_C = 100 \times 21.5 \mu A \Rightarrow 2.15 mA$$

$$I_E = I_C + I_B = 2.15 mA + 0.0215 mA$$

$$I_E = 2.17 mA$$

(b)

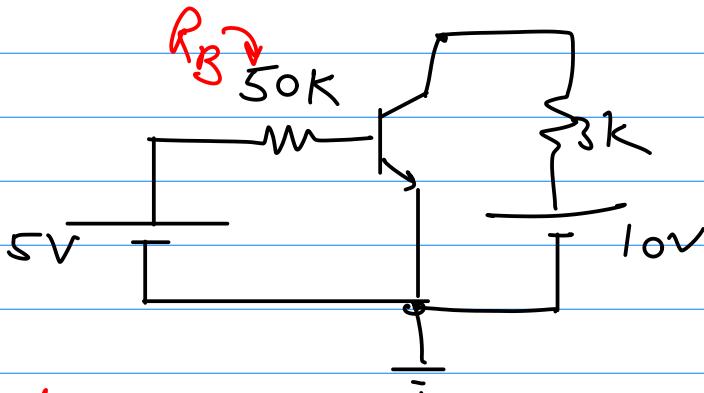

Find all currents

Shiram 5 Marks



427

Saturation

29 - 5 marks

A |

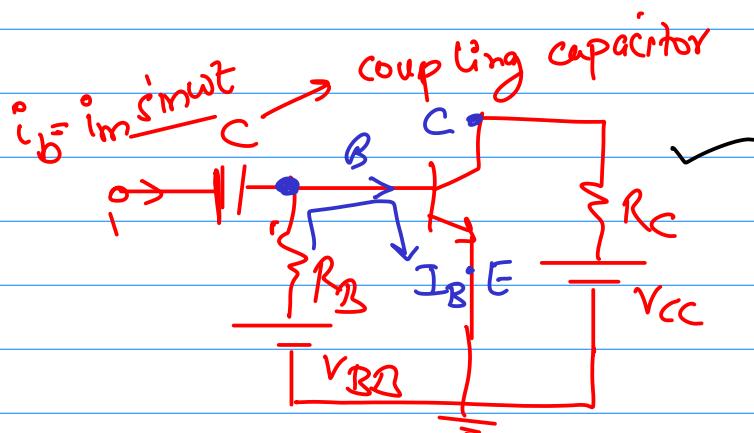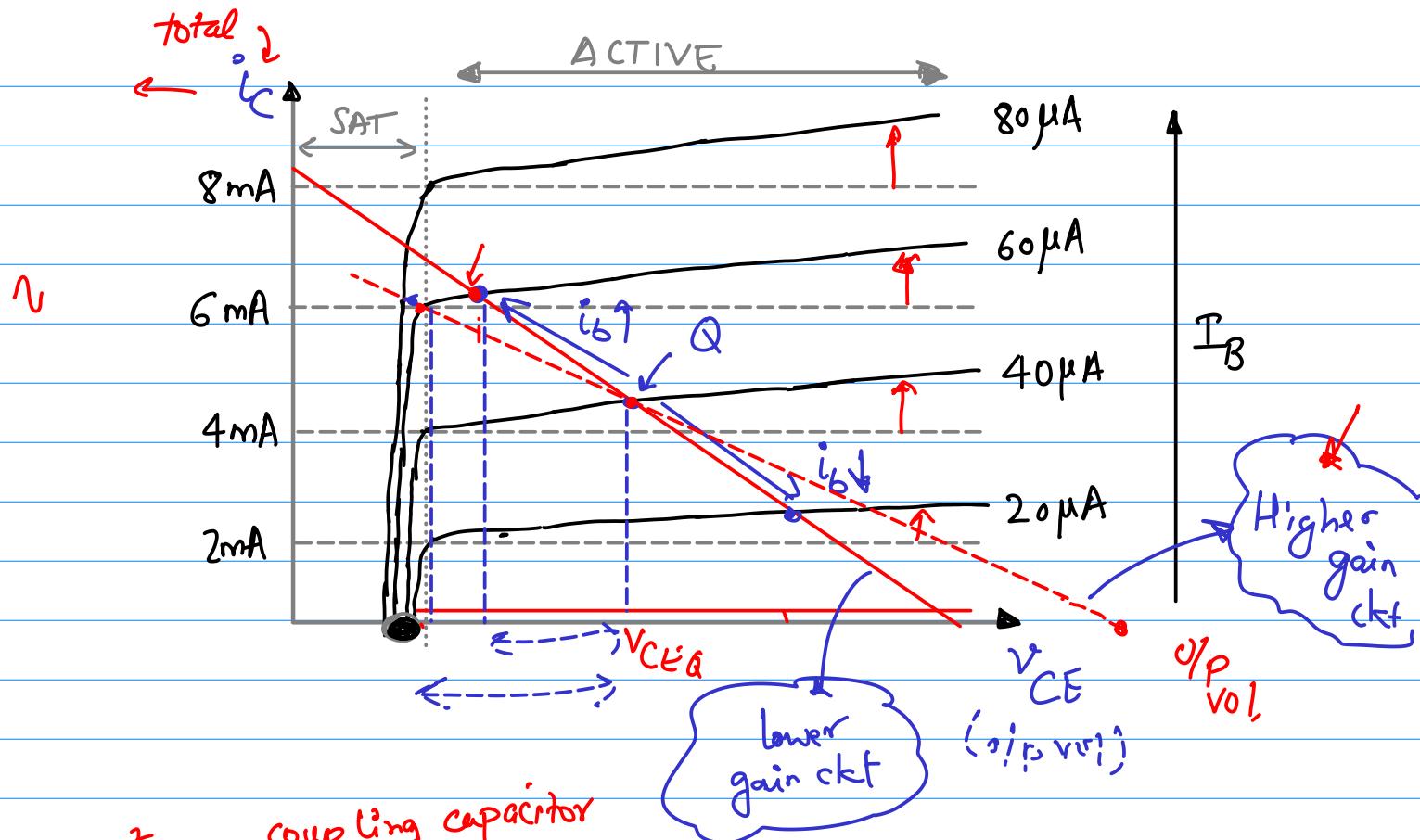CE \rightarrow LOAD LINE - CE \rightarrow 180° phase shift



$$\{I_B, I_C, V_{CE}\} \rightarrow DC$$

$$\{i_b, i_c, v_{be}\} \rightarrow AC \text{ signal}$$

$$i_c = I_c + i_c$$

total base current

$$i_B = I_B + i_b$$

DC load line -

KVL -

$$V_{CC} - I_C R_C - V_{CE} = 0$$



$$I_C = \frac{1}{R_C} V_{CC} - \frac{1}{R_C} V_{CE}$$

$$y = C + mx$$

$$I_c \approx \beta I_B \quad \text{if } i_b \uparrow, (\text{e.g. by } \uparrow i_b)$$

$$i_c \approx \beta i_b \quad \text{then } i_c \uparrow$$

$$V_C = V_C + V_C$$

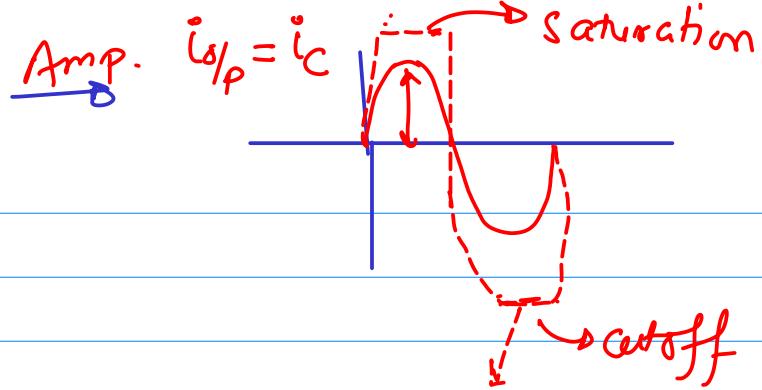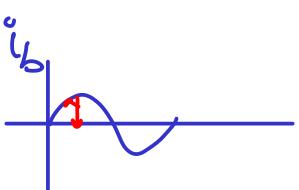

if amp. or gain is too high, then shape of

$i/o/p$ may not be preserved at $\delta/o/p$

"DISTORTION"

- * To avoid "distort" in +ve or -ve side, operating point should be set in the middle (near middle) of Load line (active region range)
- * Q point should be stable. \rightarrow Should not change (bias pt.) (or operating pt.) with environment conditions
 \because otherwise "Distortion" will ↑
- * if Q shifts away from the middle, +ve or -ve vol. swing will decrease

Bias Stabilisation -

Bias stability
affected by

|

(1)



Thermal Instability

(i) $\underline{I_{C0}} \rightarrow$ ^{**}

doubles for every 10° rise in temp.

(ii) $V_{BE} \rightarrow V_{BE}$ (cut-in) decreases

at rate of $-2.3 \text{ mV}/{}^\circ\text{C}$

→ (iii) $\underline{\beta} \rightarrow \beta \uparrow$ slightly as
temp \uparrow (can ignore)

$$I_C = \underline{\beta I_B} + (1 + \beta) I_{C0}$$

as $T \uparrow$, $I_{C0} \uparrow$,

then

$$\underline{I_C \uparrow \uparrow}$$

↳ operating point shifts

Distortion

Measuring bias stability -

Stability factors -



$$S = \frac{\Delta I_C}{\Delta I_{C0}}$$

V_{BE} & β constant

- * We want S to be as small as possible.

Bad ckt-example:

- * Fixed Bias -

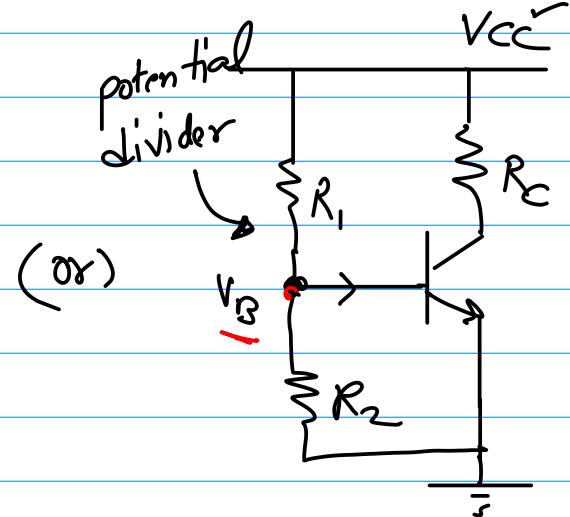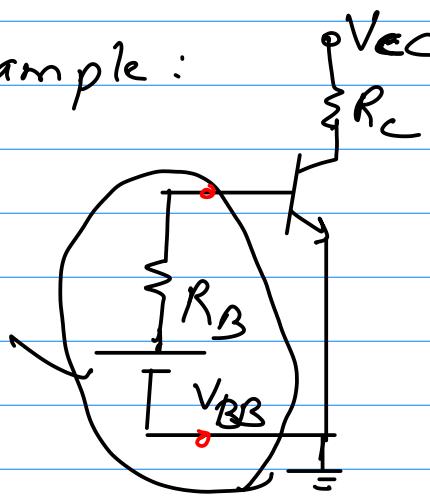


If β is high ($I_B \ll I_C$) then

the 2 ckt's are equivalent if

$$V_{Th} = V_{BB} = \frac{R_2}{R_1 + R_2} V_{CC} \quad \text{&} \quad R_{Th} = R_B = R_1 // R_2$$

THEVENIN'S THEOREM

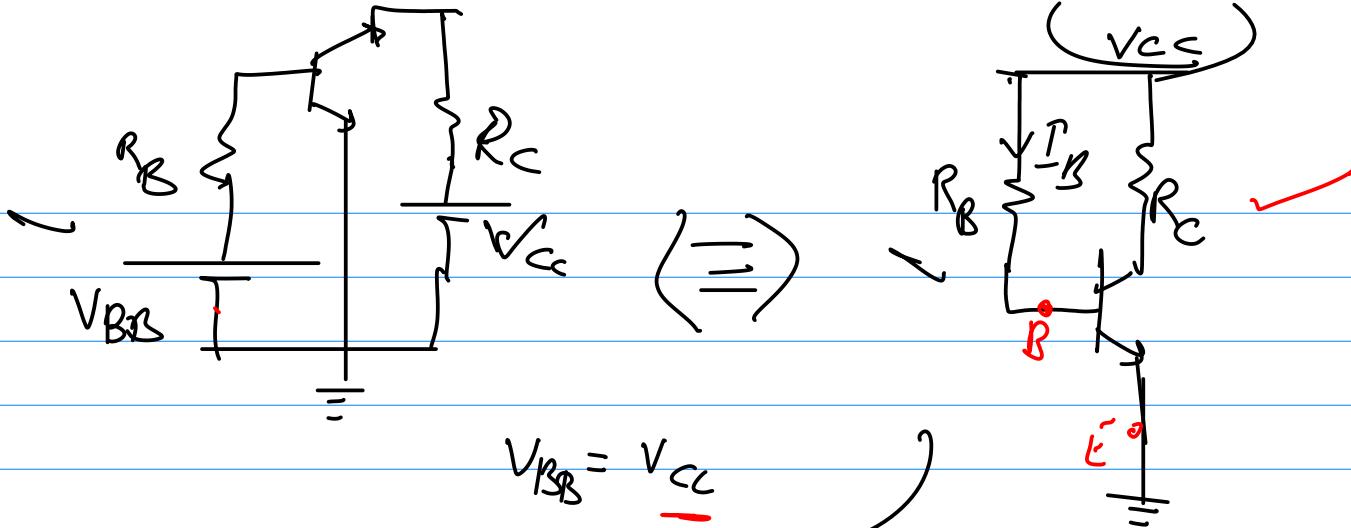

KVL at i/p - $V_{CC} - I_B R_B - V_{BE} = 0$

$$\uparrow I_B = \frac{V_{CC} - V_{BE}}{R_B} \text{ as } T \uparrow$$

M

$$I_C = R_B \frac{\uparrow}{\uparrow} (1 + \beta) I_{C_0} \quad \text{①}$$

as $T \uparrow$, $(I_{C_0} \uparrow, V_{BE} \downarrow)$, $\rightarrow I_B \uparrow, I_C \uparrow \uparrow$

BAD

$$S = \frac{dI_C}{dI_{C_0}}$$

Differentiate ① wrt I_{C_0}

$$\frac{dI_C}{dI_{C_0}} = \beta \frac{dI_B}{dI_{C_0}} + (1 + \beta)$$

$$\frac{dI_c}{dI_{C_0}} = \beta \frac{dI_B}{dI_C} \cdot \frac{dI_c}{dI_{C_0}} + (1+\beta)$$

$$\frac{dI_c}{dI_{C_0}} = S = \frac{1+\beta}{1-\beta \frac{dI_B}{dI_C}}$$

for any biasing ckt in active region.

for Fixed bias,

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

I_B is fixed
 $\therefore V_C, V_{BE}, R_B$ are constant

$$\frac{dI_B}{dI_C} = 0$$

$$S_0, \frac{dI_c}{dI_{C_0}} \quad S = 1+\beta$$

v. high

BAD

* Self biasing - (Good ckt example)

$I_B \downarrow$ if $I_C \uparrow$

$$s = \frac{1+\beta}{1-\beta \frac{\frac{\partial I_B}{\partial I_C}}{\frac{\partial I_C}{\partial I_C}}}$$

if $\frac{\partial I_B}{\partial I_C} = -V_E$


e.g. = -1.

then $s = \frac{1+\beta}{1-\beta} = 1$ (lowest possible)


A6

$$1 \leq s \leq (1+\beta)$$

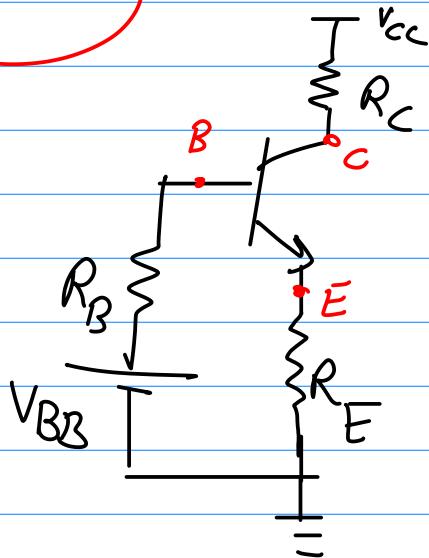
$$\frac{\partial I_C}{\partial I_C} = 1$$




(or)

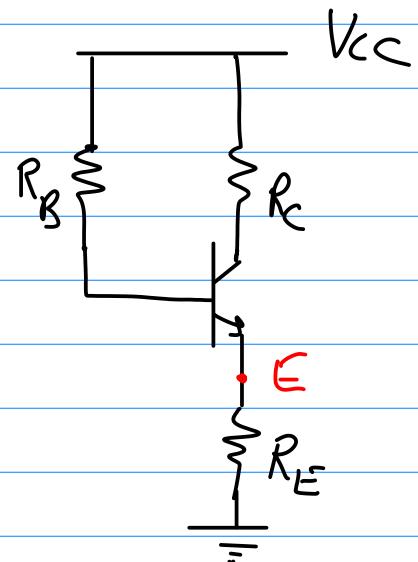

(or)

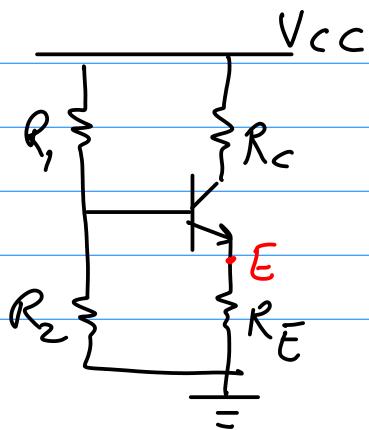

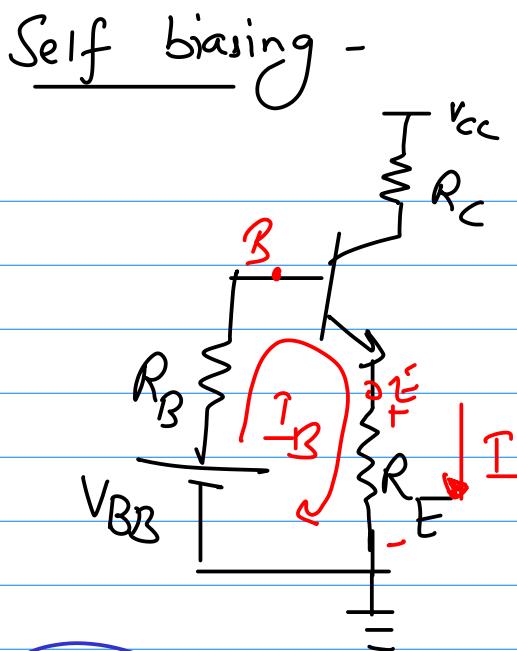

i/p KVL -

$$V_{BB} - I_B R_B - V_{BE} - \frac{I_E}{\beta} R_E = 0$$

$$\underline{I_E = I_c + I_B}$$

$$-I_B R_B - I_B R_E - \frac{I_c}{\beta} R_E + \gamma_B V_{BE} = 0$$

$$= 0$$

feedback

$$\Rightarrow I_B = \frac{V_{BB} - V_{BE} - I_c R_E}{R_B + R_E}$$

$$\frac{dI_B}{dI_c} = -\frac{R_E}{R_B + R_E}$$

$$s = \frac{1+\beta}{1-\beta \left(\frac{dI_B}{dI_c} \right)}$$

$$s = \frac{1+\beta}{1+\beta \left(\frac{R_E}{R_E + R_B} \right)}$$

$$s < 1+\beta \quad (\text{Good})$$

$$\text{if } R_E \gg R_B \quad \text{then } \frac{R_E}{R_E + R_B} \approx 1$$

Good bias stability } $S = \frac{1+\beta}{1+\beta \times 1} = 1$ (best case)

* large R_E is desirable

* Problem with too large R_E -

$$O/P KVL \rightarrow V_{CC} - I_C R_C - V_{CE} - \frac{V_E}{R_E} R_E = 0$$

$I_C \approx I_E$

So, $I_C = \frac{V_{CC} - V_{CE}}{R_C + R_E}$

if R_E (large) $\rightarrow \infty$, I_C (small) $\rightarrow 0$
 (Bad Q point)

[cut-off]

So, maybe Reduce R_B ↘

* Problem with too small R_B -

if $R_B \ll R_E$ then $S = 1$ (Good!)

\downarrow \downarrow
 v. small moderate

but if R_B is small, $I_B \uparrow$, Transistor goes towards (or into) saturation
 (Bad Q-point)

How it works - as $T \uparrow$, $I_{CO} \uparrow$, $I_C \uparrow$, $V_E \uparrow$, $I_B \downarrow$, $I_C \downarrow$

Robust system


So, change in I_C got compensated

- * Self biasing ckt is an example of a negative feedback amplifier.

\therefore the output current (I_C) converted into voltage V_E reduces the input current (I_B)


($I_C R_E$) \downarrow (-ve feedback) \rightarrow (i/p KVL)

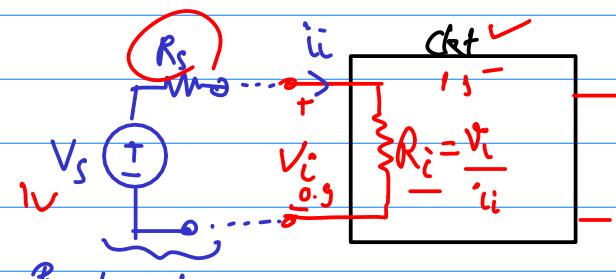HW \rightarrow Common Collector Config. (CC)



Pract. vol. source


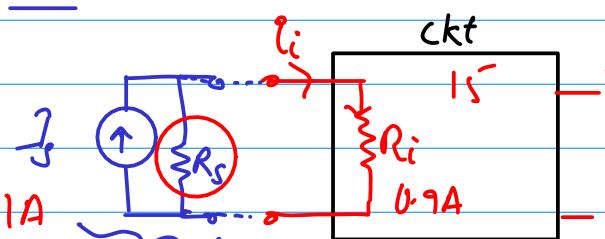
entire source vol
or current should
"enter" the Ckt
Which amplifies it.



Practical Current
source


The entire result
of amp should
be transferred
to the Load

Good Amp.

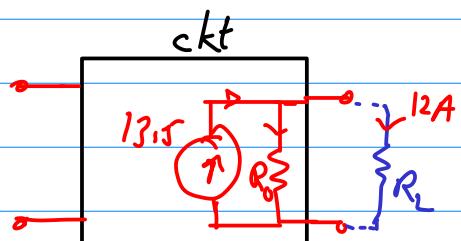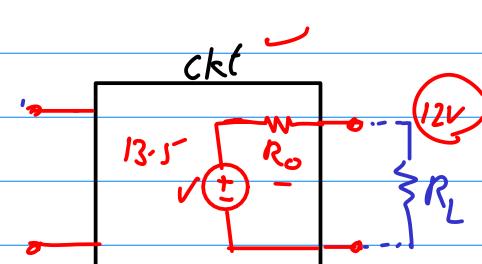

If resist of a ckt is raised seen by external source at the i/p terminals of the ckt

Amplifiers

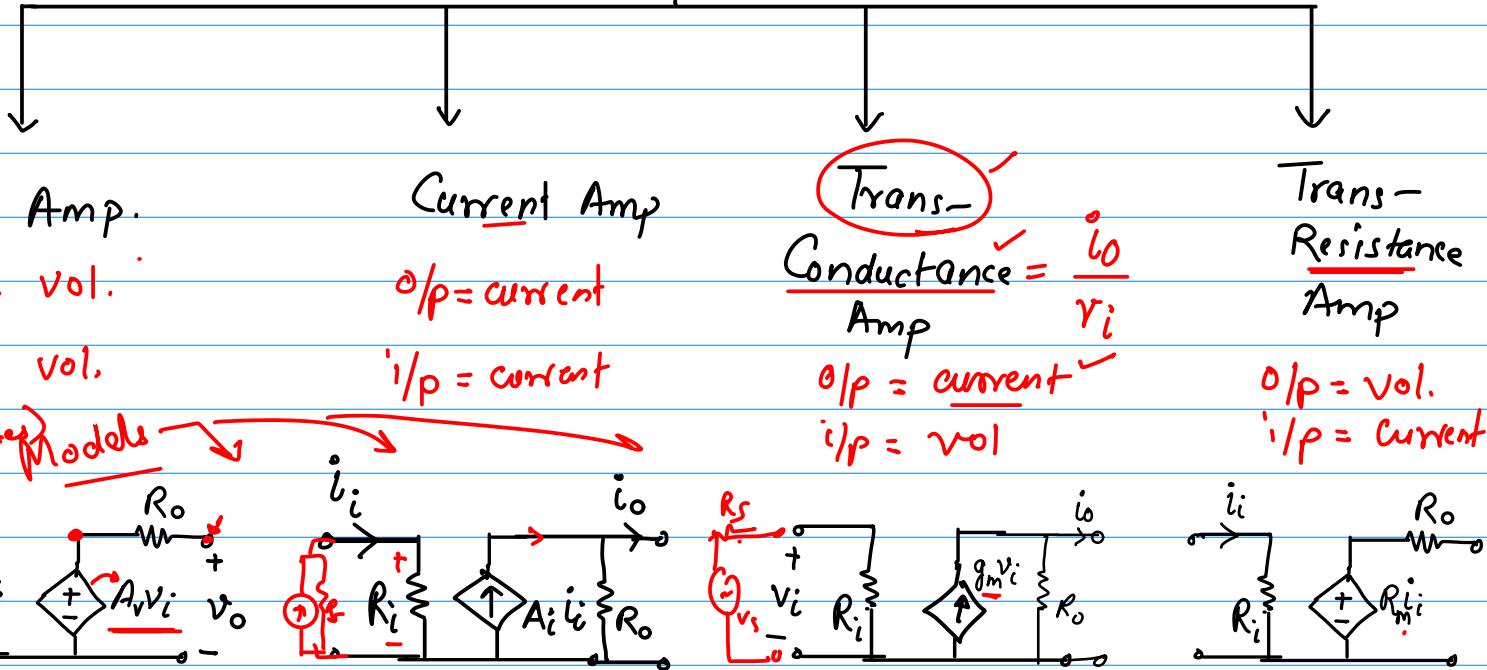

Desirables

$R_i : \text{High } (\infty)$

$R_o : \text{low } (0)$

$A_v = \text{unitless}$

Desirables

$R_i : \text{low } (0)$

$R_o : \text{High } (\infty)$

$A_i = \text{unitless}$

Desirables

$R_i : \text{High } (\infty)$

$R_o : \text{High } (\infty)$




$$g_m = \frac{1}{R_L}$$


Desirables

$R_i : \text{low } (0)$


$R_o : \text{Low } (0)$

$$R_m = \Omega$$

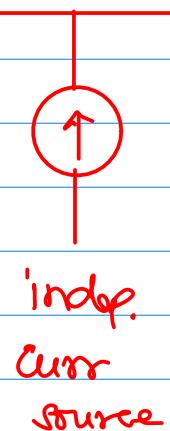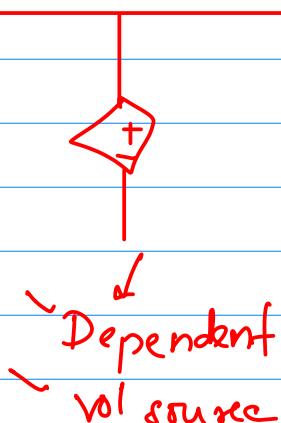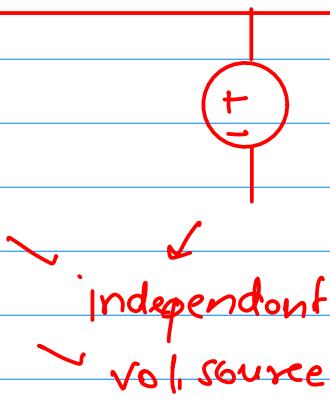


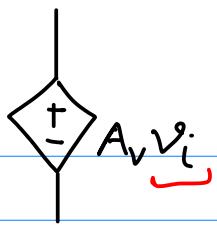


Voltage Controlled
Voltage Source (VCVS)

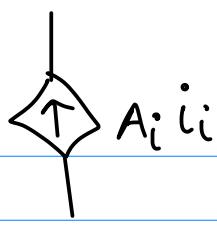

Current controlled
current source (CCCS)

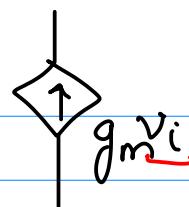

Voltage controlled
current source (VCCS)

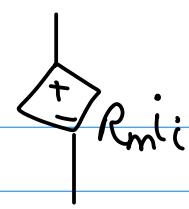



Current controlled
voltage source
(CCVS)

Small Signal Analysis:


(NPN) CE

Small signal
to be amplified


Large DC
bias vol.

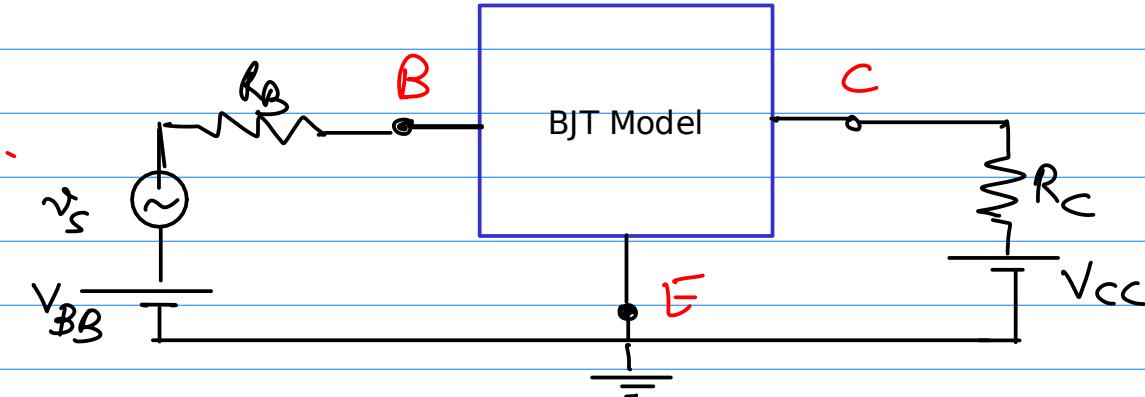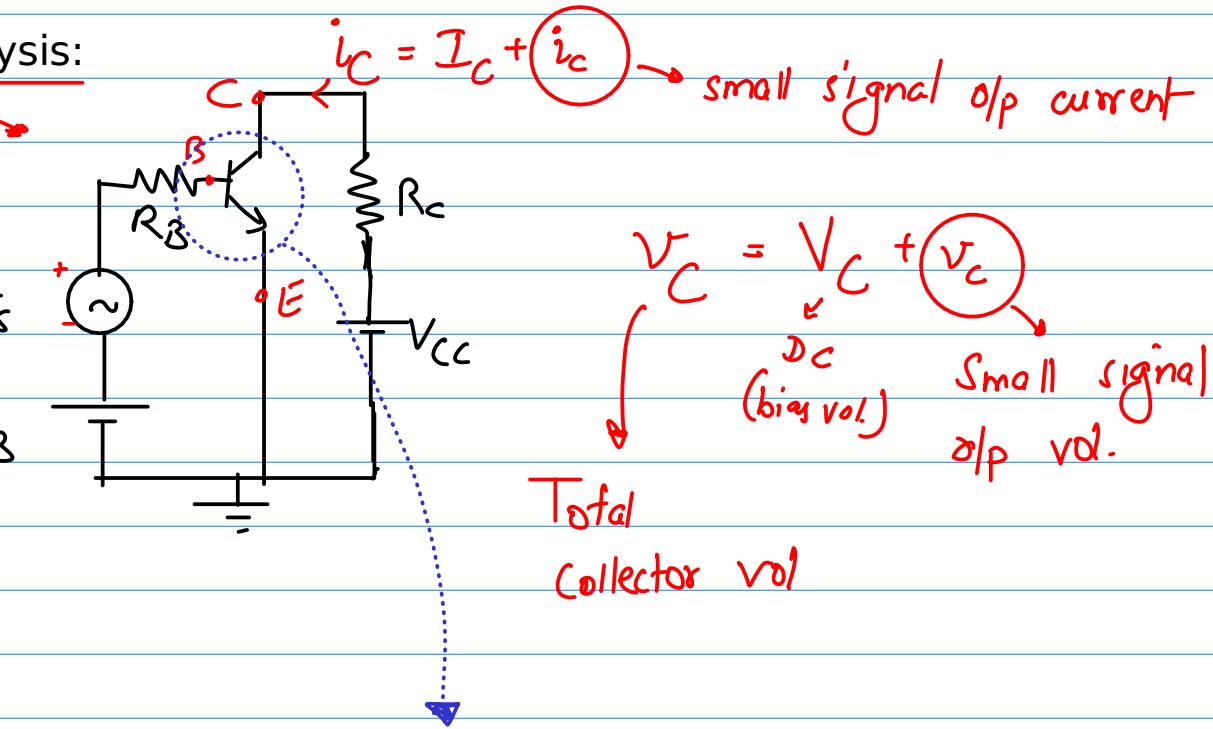

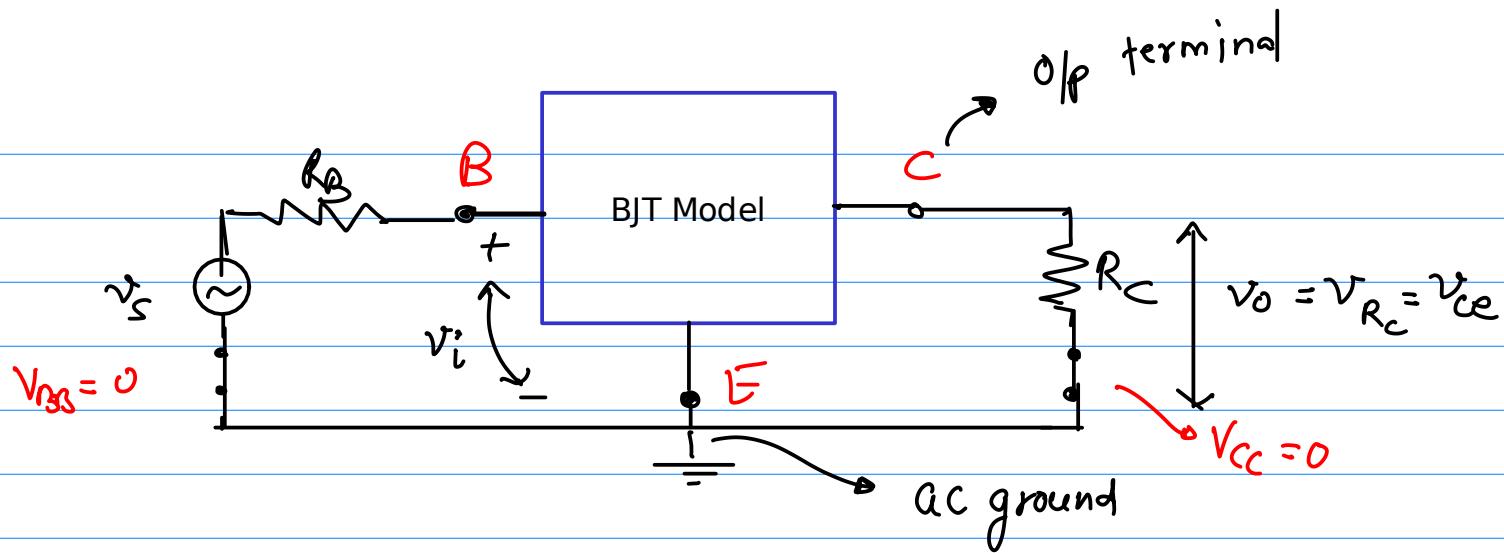- * We want to see the effect of ac signal (small signal alone)
- * Superposition principle says that effect of different sources can be studied individually (assuming other sources to be 0).
- * So, $V_{BB} = 0$, and $V_{CC} = 0$ can be assumed to see the effect of ac input signal V_s (assuming active mode biasing, which comes due to the DC voltages)



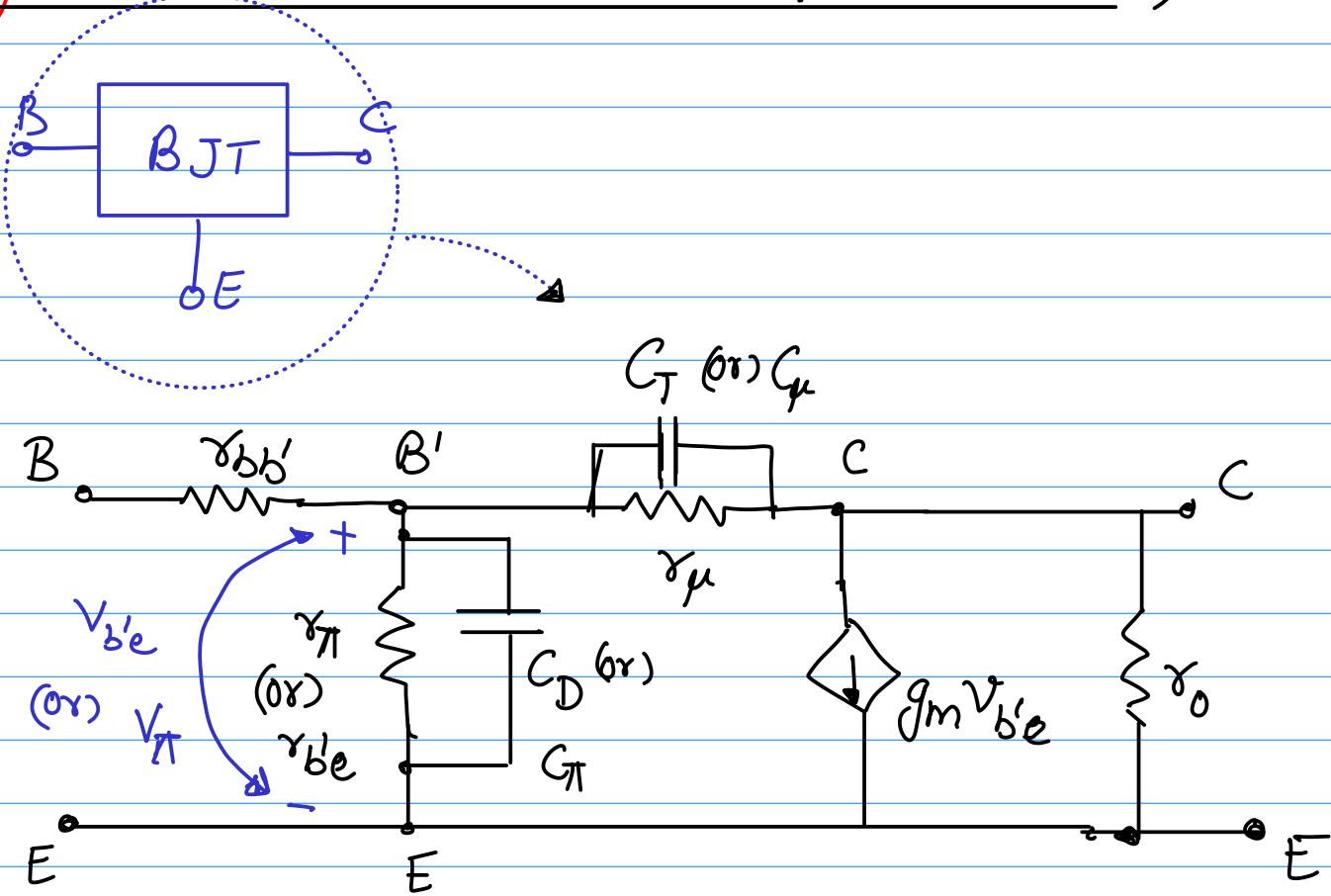Hybrid- π model for BJT (Giacoletto model) :-



$r_{bb'} \equiv$ Base spread resist- ($\sim 100 \Omega$)

$$\gamma_{\pi} \text{ or } \gamma_{B'E} = B-E \quad f.b. j^n \text{ resistance } (\sim 1k\Omega)$$

\rightarrow depends on dc operating current (I_{CQ})

$$C_D = B.E \quad f.b. j^n \text{ capacitance (Diffusion cap)}$$

$$\gamma_{\mu} = C-B \quad R.B- j^n \text{ resistance (r. high)}$$

$$C_T \text{ or } \gamma_{\mu} = C-B \quad R.B \quad j^n \text{ Capacitance (Transition cap)}$$

$$g_m = \text{Transconductance of BJT}$$

\rightarrow also depends on DC operating point


$$g_m = \left| \frac{I_{CQ}}{V_T} \right|$$

$$V_T = \frac{I}{11,600} \rightarrow (in K)$$

$\simeq 26 \text{ mV at } 300 \text{ K}$

$\gamma_0 = \text{o/p resistance. Models the early effect}$


$$\gamma_0 = \frac{V_A}{|I_{C\text{-sat}}|}$$

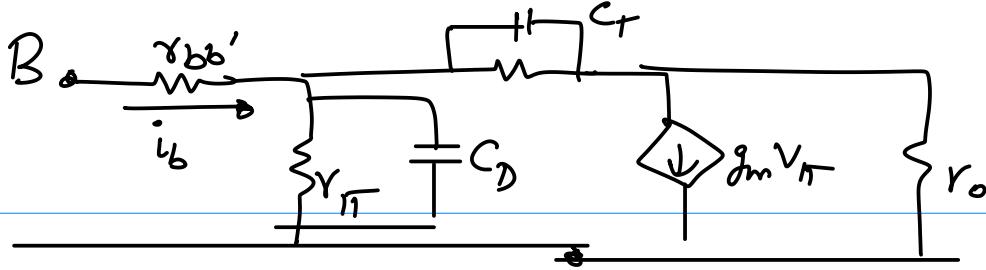

if freq. is low (close to DC)

[Cap act as O.C. for DC & almost O.C. for low freq.]

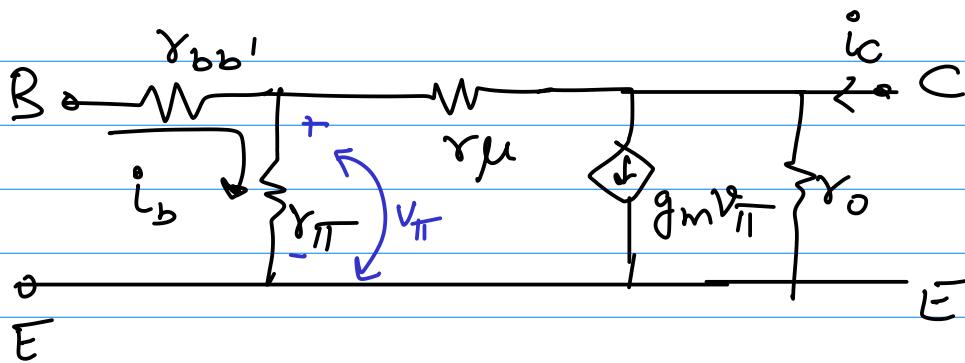So, Low freq. small signal model - $[C_D, G \approx \text{O.C.}]$




$$v_{\pi} = i_b \gamma_{\pi}$$

if γ_0 is ignored (v.v. high $\sim \text{O.C.}$)
(neglig. early effect)

Also since $r_{\mu} = \text{v.v. high} \sim \text{O.C.}$

Simplified hybrid-\$\pi\$ model -

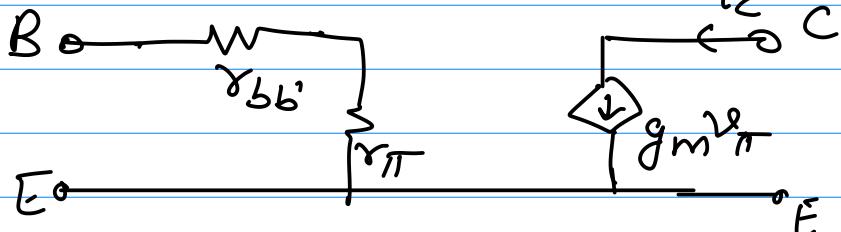

$$i_c = g_m v_{\pi}$$

$$v_{\pi} = i_b \gamma_{\pi}$$

$$i_c = g_m i_b \gamma_{\pi}$$

$$g_m \gamma_{\pi} = \frac{\dot{i}_c}{\dot{i}_b} = \beta \quad (\text{active mode})$$


$$g_m = \frac{|\dot{I}_{CQ}|}{V_T}$$

$$\gamma_{\pi} = \frac{\beta}{g_m} = \frac{\beta}{|I_{CQ}|} \cdot V_T$$

$$\gamma_{\pi} = \frac{V_T}{|\dot{I}_{BQ}|}$$

Using the low freq. Small Signal hybrid- π model -

CE Amplifier

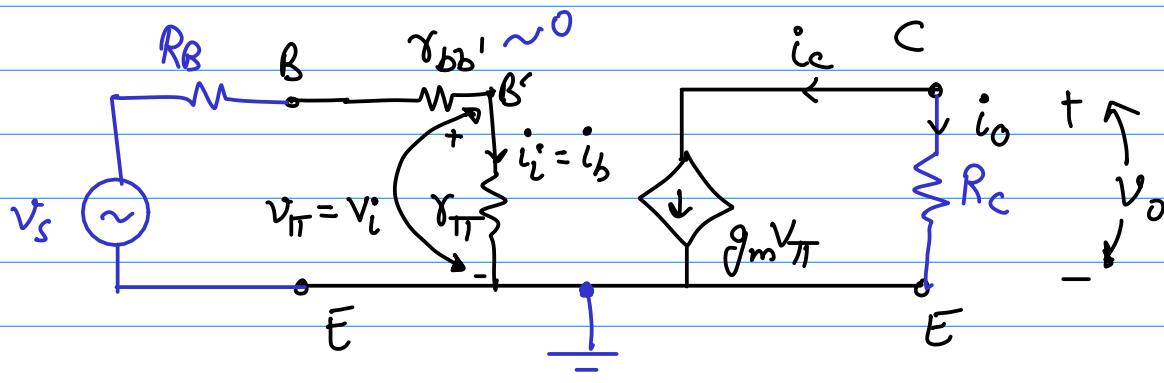


Current Gain (A_i) -

$$A_i = \frac{\dot{i}_o}{\dot{i}_i} = -\frac{\dot{i}_c}{\dot{i}_b} = -\beta$$


$$\dot{i}_o = -\dot{i}_c$$

$$\dot{i}_i = \dot{i}_b$$

$$A_i = -\beta$$

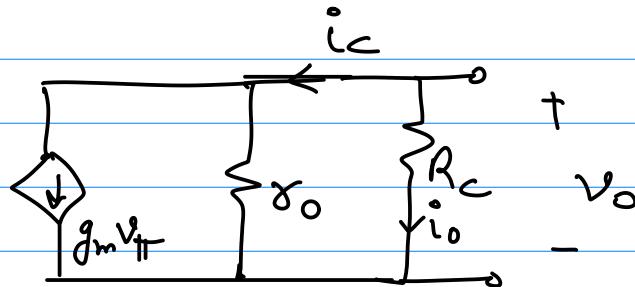


→ Input Resistance (R_i) -

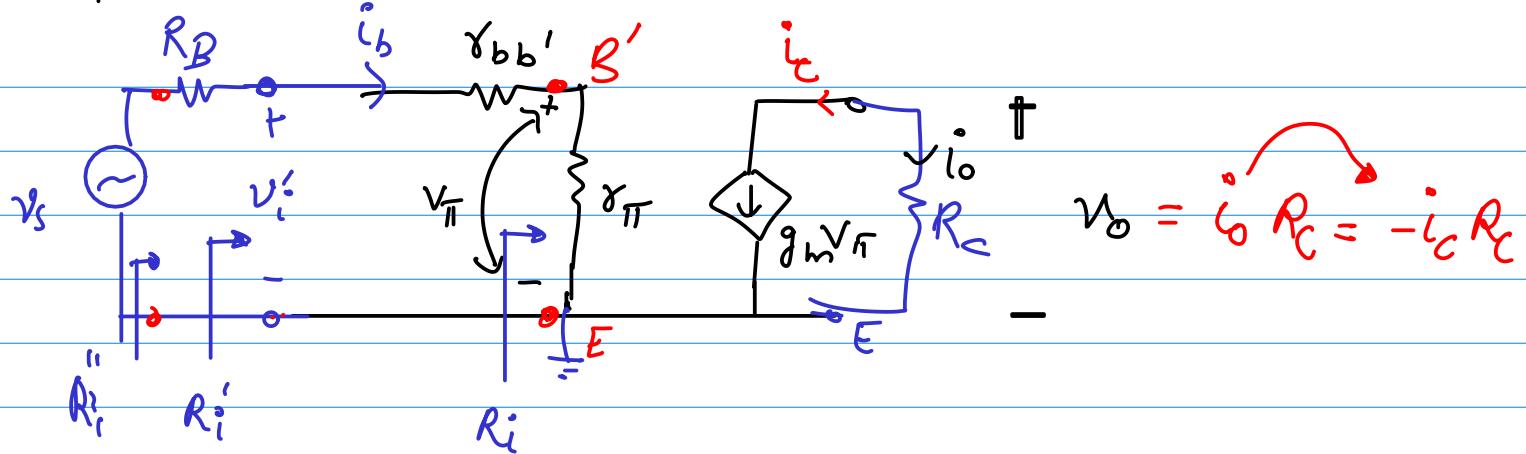

$$R_i = \frac{V_i}{i_b} = r_{\pi}$$



$$R_i' = \frac{V_i'}{i_b} = r_{\pi} + r_{bb'}$$

seen by

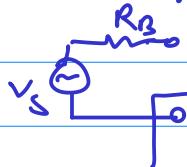

$$R_i'' = R_B + r_{bb'} + r_{\pi}$$

seen by V_s

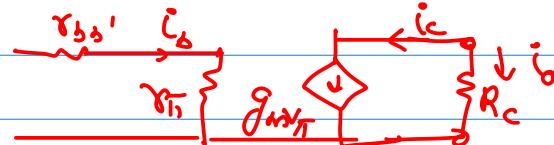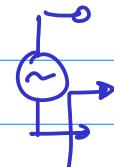

→ Voltage Gain - $(A_V) = \frac{V_o}{V_i} = \frac{i_o R_C}{i_b r_{\pi}} = -\frac{i_c R_C}{i_b r_{\pi}}$

$$V_o = -i_c R_C$$

$$= -g_m V_T R_C$$

$$V_i = V_T$$


$$\therefore A_V = -\frac{g_m V_T R_C}{r_{\pi}}$$

$$A_V = -\beta \frac{R_C}{r_{\pi}}$$

$$A_V = -g_m R_C$$

$$\therefore g_m = \frac{\beta}{r_{\pi}}$$

If early effect is significant

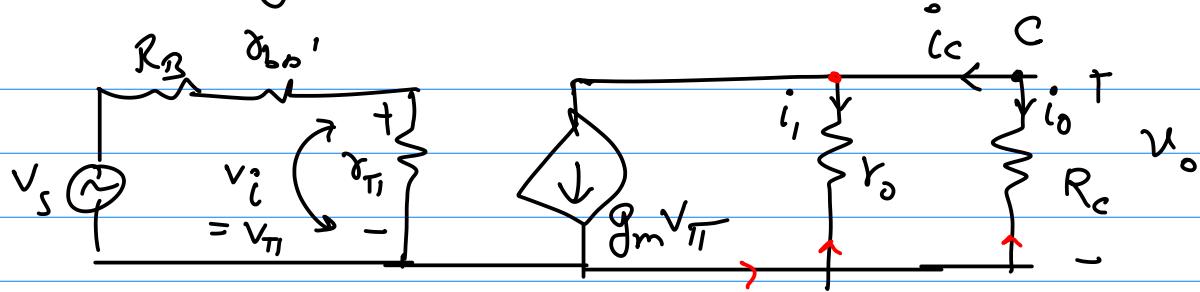

$$A_v = \frac{V_o}{V_i} = ?$$

$$i_1 = \frac{V_o}{r_o} \quad (\text{Ohm's law})$$

$$V_o = i_o R_C = -i_C R_C$$

$$i_C = g_m V_{\pi} + i_1$$

$$i_C = g_m V_{\pi} + \frac{V_o}{r_o}$$

$$V_o = - \left[g_m V_{\pi} + \frac{V_o}{r_o} \right] R_C$$

$$V_o \left(1 + \frac{R_C}{r_o} \right) = - g_m V_{\pi} R_C \Rightarrow V_o = \frac{-g_m V_{\pi} R_C}{(r_o + R_C)}$$

$$R_C \parallel r_o = \frac{R_C r_o}{R_C + r_o}$$

$$V_o = -g_m V_{\pi} \left[R_C \parallel r_o \right]$$

$$V_i = V_{\pi}$$

$$\text{So, } A_v = \frac{V_o}{V_i} = - \frac{g_m V_{\pi} \left[R_C \parallel r_o \right]}{r_o}$$

$$A_v = -g_m \left[R_C \parallel r_o \right] = -g_m \left(\frac{R_C r_o}{R_C + r_o} \right)$$


A_v has reduced due to early effect ($\because (R_C \parallel r_o) < R_C$)

$$\rightarrow \text{Overall vol. gain} - A_{VS} = \frac{V_o}{V_s}$$

A_V (internal vol. gain)


$$A_{VS} = \frac{V_o}{V_i} \times \frac{V_i}{V_s} =$$
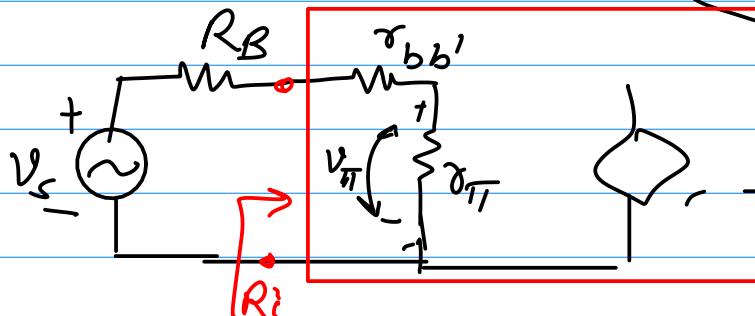
$$\frac{V_o}{V_{II}} \times \frac{V_{II}}{V_s}$$



T

- V_o

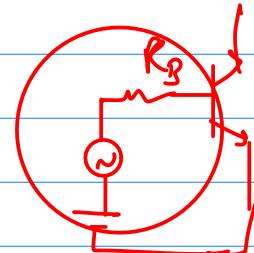

* V_i is only a fraction of the source V_s

$$V_{\pi} = V_i = \left[\frac{\gamma_{\pi}}{(R_B + \gamma_{bb'} + \gamma_{\pi})} \right] \times V_s \Rightarrow \frac{V_{\pi}}{V_s} = \frac{\gamma_{\pi}}{(R_B + \gamma_{bb'} + \gamma_{\pi})}$$

if $R_i = \gamma_{bb'} + \gamma_{\pi}$ → i/p resistance seen between B & E terminal

$$\frac{V_{\pi}}{V_s} = \frac{\gamma_{\pi}}{R_B + R_i}$$

if $\gamma_{bb'} \ll \gamma_{\pi}$

$$R_i \approx \gamma_{\pi}$$

$$\frac{V_{\pi}}{V_s} \approx \frac{R_i}{R_B + R_i}$$

$$A_{VS} = \frac{V_o}{V_{\pi}} \times \frac{V_{\pi}}{V_s} = A_V \times \frac{V_{\pi}}{V_s}$$

Shivam **

Sahil 389
Shashank 421 **

$$A_{VS} = -g_m (R_c || \gamma_0) \times \frac{R_i}{R_B + R_i}$$

To get highest A_{vs} ($A_{vs} = A_v$)

$$\frac{R_i}{R_B + R_i} \approx 1$$

So, $R_i \gg R_B$ is desirable

$$R_i \approx 1k\Omega \text{ for CE}$$

* So, R_B should be small




Sarthak 379 **

but if R_B is too small,
BJT saturates \rightarrow not an amp (ifst).

→ Output resistance $R_o \rightarrow$

Steps:

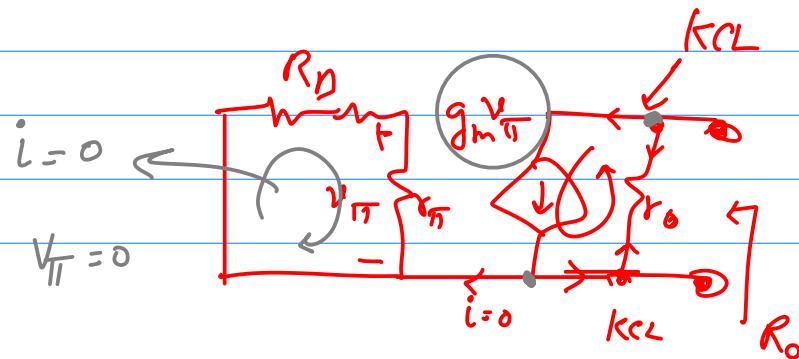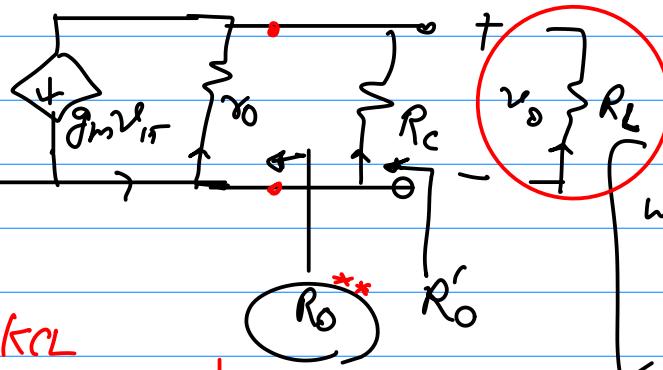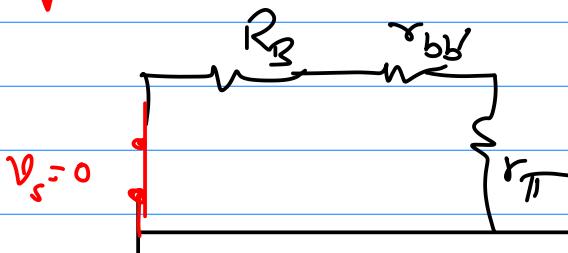1. Remove the load if any
2. Remove all sources. i.e. all voltage sources (independent) to be short circuited and all current sources (independent) should be open circuited
3. Find the equivalent (net) resistance between the output terminals $= R_o$





$$V_T = 0 \quad [\because V_s = 0]$$

$$g_m V_T = 0$$

$$g_m v_T = 0$$

\equiv O.C.

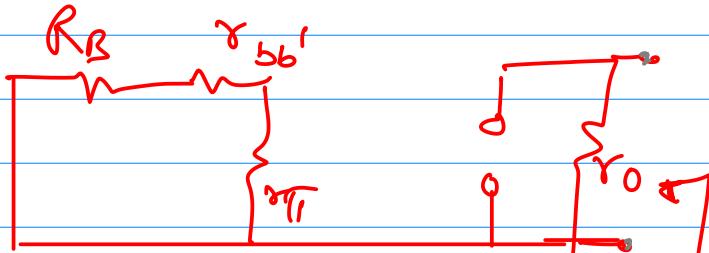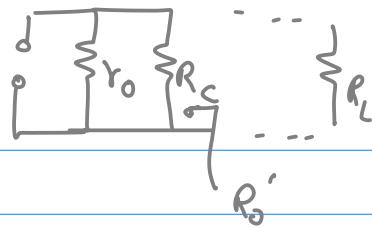

$$R_O' = R_C \parallel r_o$$

$$R_O = r_o \parallel \infty = r_o$$


Abstract 18

$$R_O = r_o$$


(if R_C is the load)

if early effect is negligible, $r_o \rightarrow \infty$

$$R_O \rightarrow \infty$$

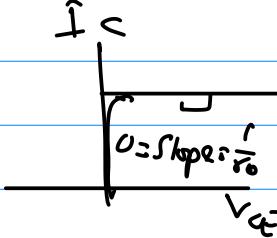

$$\frac{R_O'}{r_o}$$

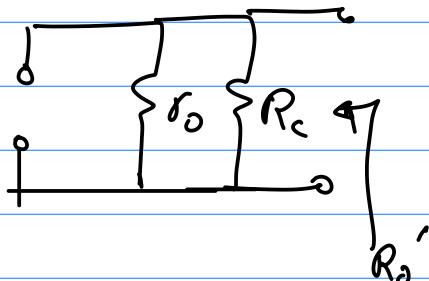

$$R_O' = r_o \parallel R_C$$

* R_O should be as high as possible so that entire current $g_m V_i$ can go to the load

→ Power Gain -

$$A_p = \frac{V_o \cdot I_o}{V_i \cdot I_i} = A_v \cdot A_i$$

$$A_p = A_i \cdot A_v = (-\beta) (-g_m R_C)$$


neglecting early effect

$$A_p = + \frac{\beta^2 R_C}{r_T} = \beta^2 \left(\frac{R_C}{r_T} \right)$$


$$A_p \approx \beta^2$$

so, highest power gain in C.E.

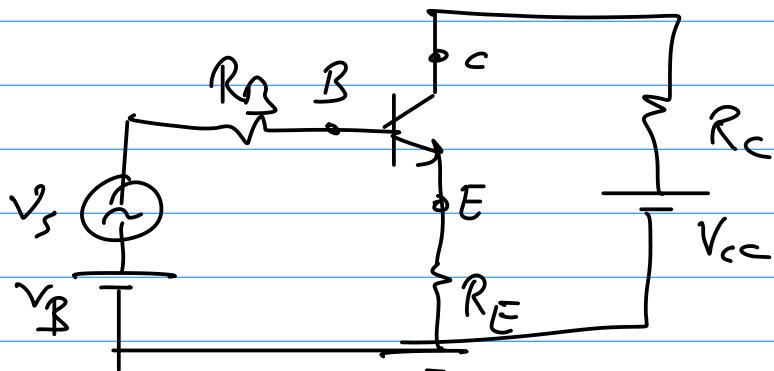CE with Emitter resistance (Self-biasing) :



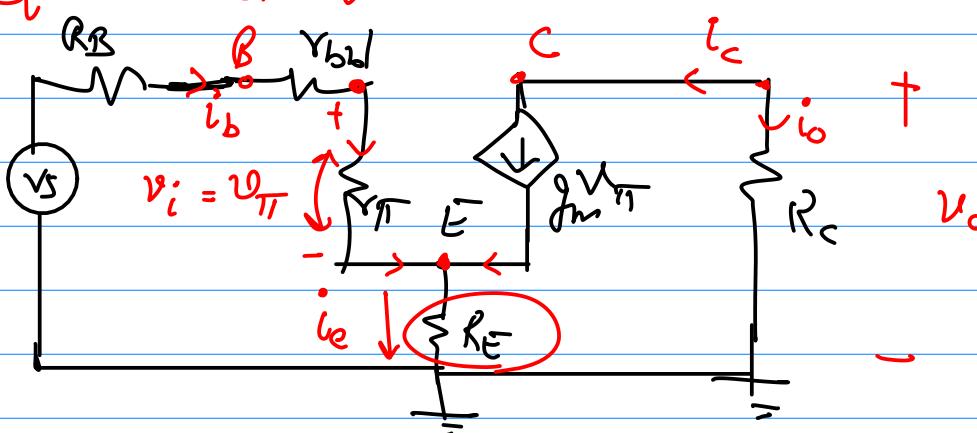Small signal equivalent circuit \Rightarrow



(ignoring early effect)

$$i_o = -i_c = -g_m v_{pi}$$

$$i_b = i_b + i_c$$


(KCL at E)

$$\rightarrow \text{Current Gain} - A_i = \frac{i_o}{i_i} = -\frac{i_c}{i_b} = -\frac{g_m v_{pi}}{v_{pi}/r_{pi}} = -g_m r_{pi} = -\beta$$

$$A_i \approx -\beta$$


[Same as before (without R_E)]

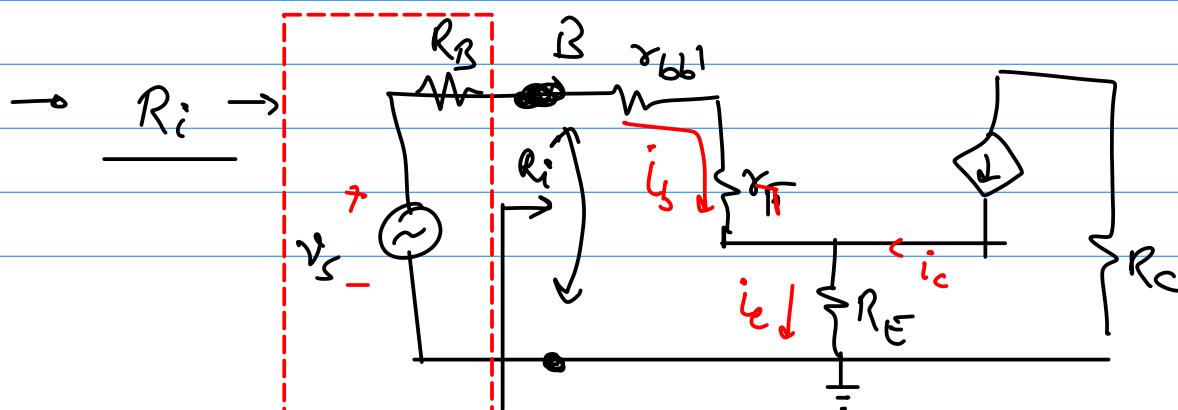* Re resistance does not affect the current gain



HW
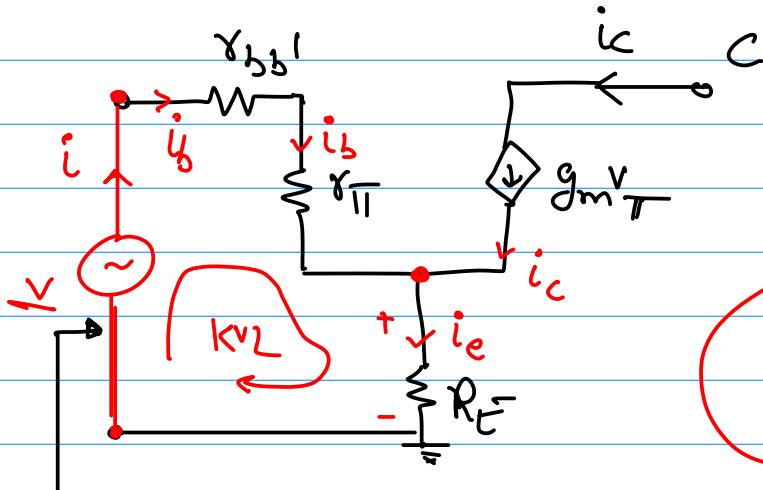
$$R_i = \frac{r_{bb'} + r_T + () R_E}{}$$



$$R_i = \frac{V}{i_b}$$

$$R_i = \frac{V}{i_b}$$

$$V - i_b r_{bb'} - i_b r_T - i_e R_E = 0$$

$$\begin{aligned} i_e &= i_c + i_b = \beta i_b + i_b \\ \Rightarrow i_e &= (1+\beta) i_b \end{aligned}$$

$$V - i_b r_{bb'} - i_b r_T - (1+\beta) i_b R_E = 0$$

$$V = i_b (r_{bb'} + r_T + (1+\beta) R_E)$$

$$\frac{V}{i_b} = R_i = r_{bb'} + r_T + (1+\beta) R_E \quad **$$

$$\text{if } R_E = 0 \Rightarrow R_i = r_{bb'} + r_T$$

* Using R_E has increased R_i by $(1+\beta) R_E$


(Neglecting Early Effect)

→ Voltage Gain -

(internal gain)

$$A_V = \frac{V_o}{V_{\pi}}$$

$$V_o = -i_C R_C = -g_m V_{\pi} R_C$$

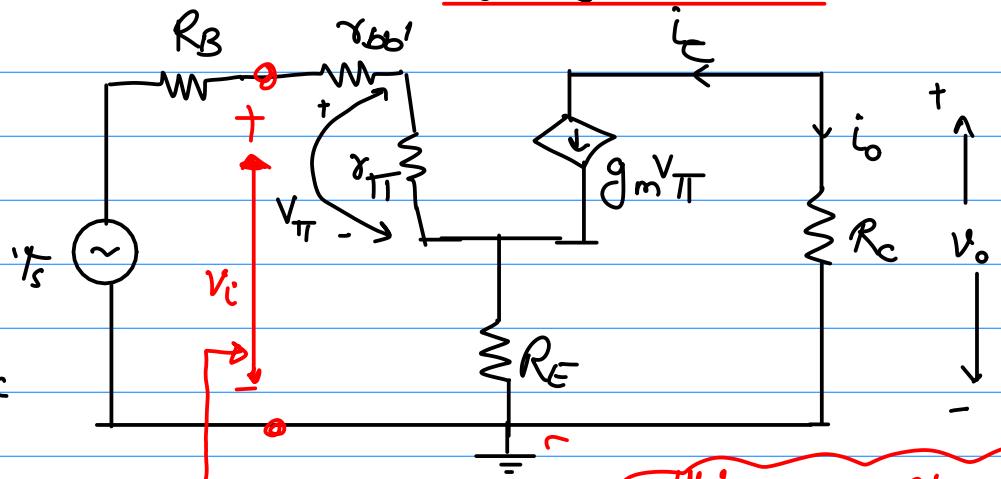

$$A_V = -\frac{g_m V_{\pi} R_C}{V_{\pi}} \Rightarrow A_V = -g_m R_C$$

HW $A_V = \frac{V_o}{V_i} = 1$

→ Including r_o :


$$V_o = -i_C R_C$$

$$i_C = g_m V_{\pi} + i_I$$

$$i_I = \frac{V_{ce}}{r_o} \quad [Ohm's Law]$$

$$V_{ce} = V_o - V_e \quad (= V_C - V_e = V_o - V_e) \quad V_C = V_o$$

$$V_e = i_e R_E \approx i_C R_E$$

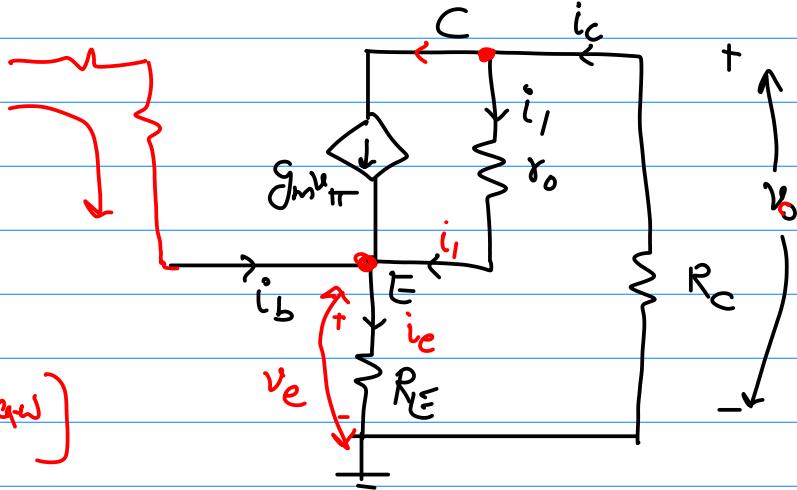

$$[i_e = i_C + i_b \approx i_C] \quad [assuming high \beta]$$

$$\text{So, } V_{ce} = V_o - (i_C) R_E \Rightarrow i_C = g_m V_{\pi} + \frac{1}{r_o} [V_o - i_C R_E]$$

$$i_C \left[1 + \frac{R_E}{r_o} \right] = g_m V_{\pi} + \frac{V_o}{r_o}$$

$$i_C = \left(\frac{r_o}{r_o + R_E} \right) \left[g_m V_{\pi} + \frac{V_o}{r_o} \right] \quad V_o = i_C R_C$$

$$v_o = - \frac{r_o}{r_o + R_E} \left[g_m v_{\pi} + \frac{v_o}{r_o} \right] R_c$$

$$v_o \left[1 + \frac{R_c}{r_o + R_E} \right] = - g_m v_{\pi} \left(\frac{r_o}{r_o + R_E} \right) R_c$$


$$A_v = \frac{v_o}{v_{\pi}} = \frac{-g_m \left(\frac{r_o}{r_o + R_E} \right) R_c}{r_o + R_E + R_c} \times (r_o + R_E)$$

* $A_v = - \frac{g_m r_o R_c}{r_o + R_c + R_E}$

CE without R_E ,
 $A_v = -g_m \left(\frac{r_o R_c}{r_o + R_c} \right)$

* R_E provides -ve feedback which reduces the voltage gain.

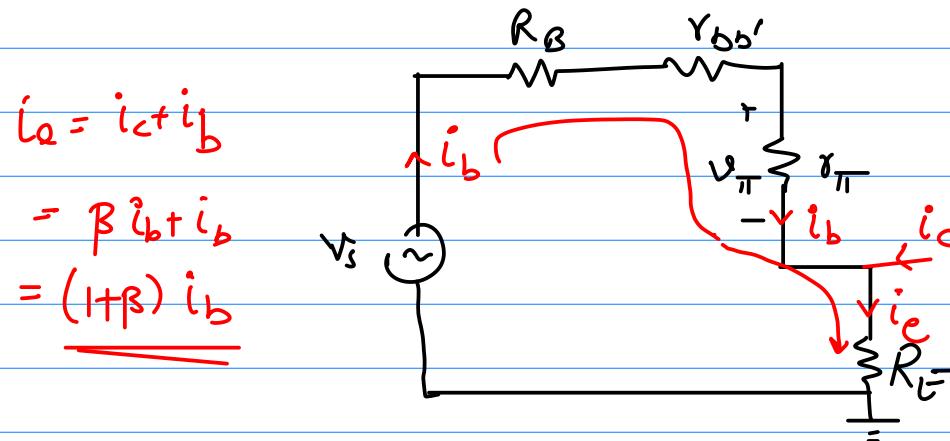→ Overall voltage Gain — $A_{v_s} = A_v \times \frac{v_{\pi}}{v_s}$



$$\begin{aligned} v_s - i_b R_B - i_b r_{bb'} - i_b r_{\pi} \\ - (1 + \beta) i_b R_E = 0 \end{aligned}$$

$$\Rightarrow i_b = \frac{v_s}{R_B + r_{bb'} + r_{\pi} + (1 + \beta) R_E}$$


$$v_{\pi} = i_b r_{\pi} \Rightarrow v_{\pi} = \frac{v_s r_{\pi}}{R_B + r_{bb'} + r_{\pi} + (1 + \beta) R_E}$$

$\Rightarrow \boxed{\frac{v_{\pi}}{v_s} = \frac{r_{\pi}}{R_B + r_{bb'} + r_{\pi} + (1 + \beta) R_E}}$

$$\Rightarrow A_{vs} = -g_m R_c \left(\frac{r_\pi}{R_B + r_{bb'} + r_\pi + (1+\beta)R_E} \right) = -\frac{g_m R_c r_\pi}{R_B + R_i}$$

* A_{vs} has reduced due to use of R_E resistance. [-ve feedback]

→ Output Resistance R_o :

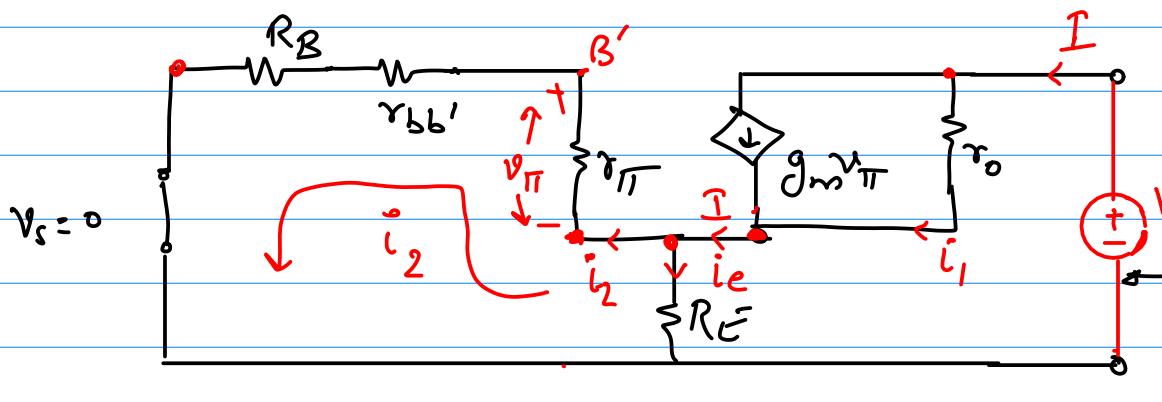


$$V = f(I)$$

$$R_o = \frac{V}{I}$$

HW find $R_o = \frac{V}{I}$


(first ignore r_o , find R_o ,
then solve with r_o)


→ CB amplifier:

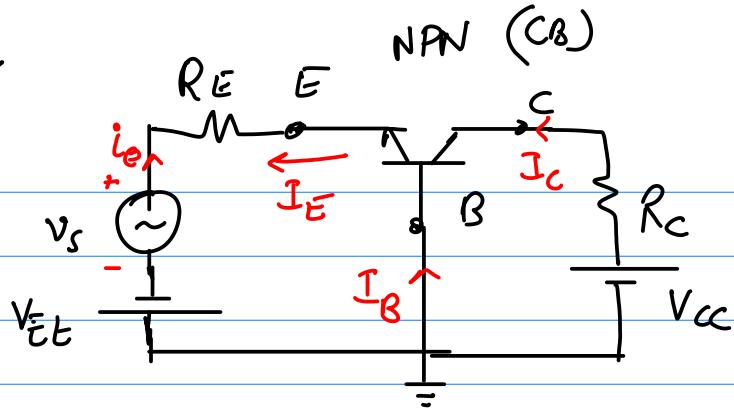

Small signal equivalent -

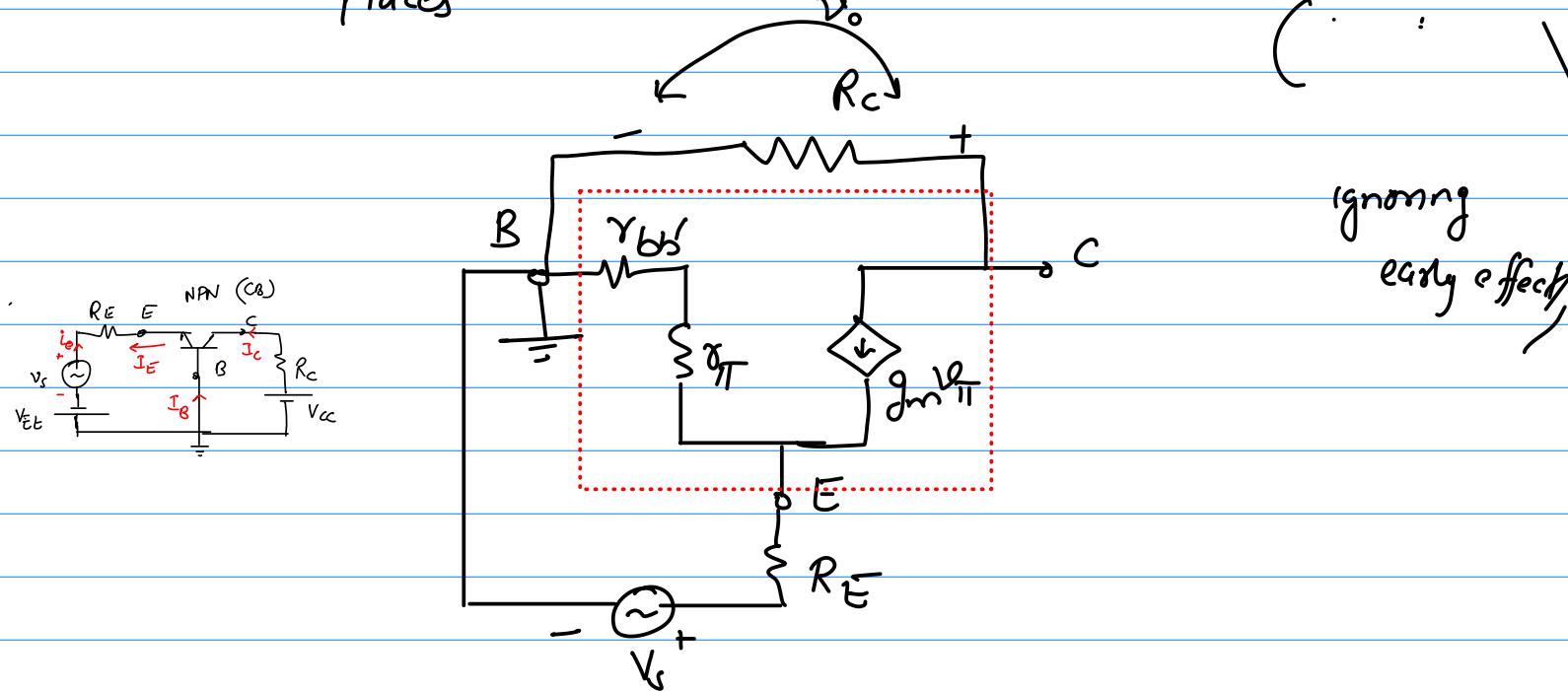- 1) first draw small signal model of BJT alone
- 1.2) Name all the terminals
- 2) Then connect external components in appropriate places



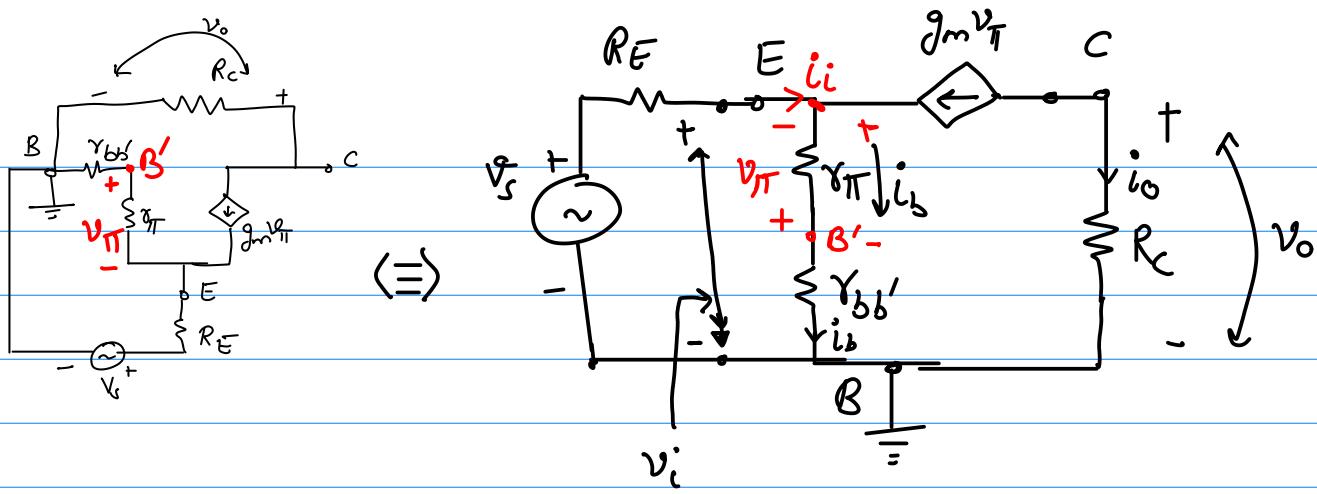

$$\rightarrow R_i = \frac{v_i}{i_i} \rightarrow KVL - v_i + v_{\pi} + v_{\pi} - i_b r_{bb'} = 0$$

$$v_{\pi} = -i_b r_{\pi}, \text{ by KCL, } i_b = i_i + g_m v_{\pi}$$

KVL

$$i_b = i_i + g_m (-i_b r_{\pi})$$

$$i_i = i_b [1 + g_m r_{\pi}]$$

$$i_b = \frac{i_i}{1 + g_m r_{\pi}}$$

$$v_i + \left(-\frac{i_i}{1 + g_m r_{\pi}} \right) r_{\pi} - \left(\frac{i_i}{1 + g_m r_{\pi}} \right) r_{bb'} = 0$$

$$v_i = i_i \left[\frac{r_{\pi}}{1 + g_m r_{\pi}} + \frac{r_{bb'}}{1 + g_m r_{\pi}} \right]$$

Comparing
with CE R_i

$$R_i = \frac{v_i}{i_i} = \frac{r_{\pi} + r_{bb'}}{1 + g_m r_{\pi}}$$

$$= r_{\pi} + r_{bb'}$$

$R_i < R_i$
(CB) (CE)


A1

→ Current Gain A_i :

$$A_i = \frac{i_o}{i_i}$$

$$i_o = -g_m v_{\pi}$$

$$i_i = ?$$

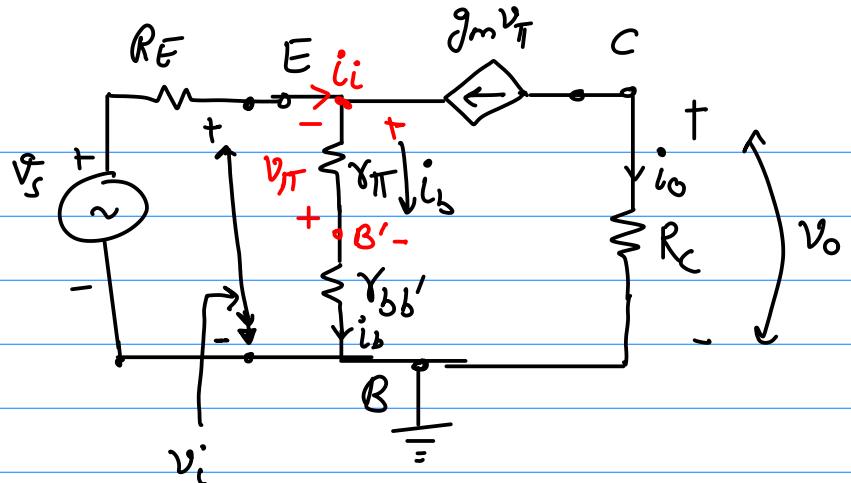

$$i_i + g_m v_{\pi} = i_b$$

$$v_{\pi} = -i_b r_{\pi}$$

$$i_i = i_b [1 + g_m r_{\pi}]$$

$$= -v_{\pi} \left[\frac{1 + g_m r_{\pi}}{r_{\pi}} \right]$$

$$A_i = \frac{+g_m r_{\pi}}{r_{\pi} \left[\frac{1 + g_m r_{\pi}}{r_{\pi}} \right]}$$

$$A_i = \frac{g_m r_{\pi}}{1 + g_m r_{\pi}} = \frac{\beta}{1 + \beta} = \alpha$$